



Aalto University
School of Electrical
Engineering

Lecture 6: Grid-Connected Converters

ELEC-E8402 Control of Electric Drives and Power Converters

Marko Hinkkanen

Spring 2023


Learning Outcomes

After this lecture and exercises you will be able to:

- ▶ Explain the operating principle of the grid converter
- ▶ Explain the principle of grid-voltage orientation
- ▶ Calculate the operating point of the grid converter
- ▶ Tune a simple DC-voltage controller

Balanced 3-phase grid, having zero impedance, will be assumed in this lecture

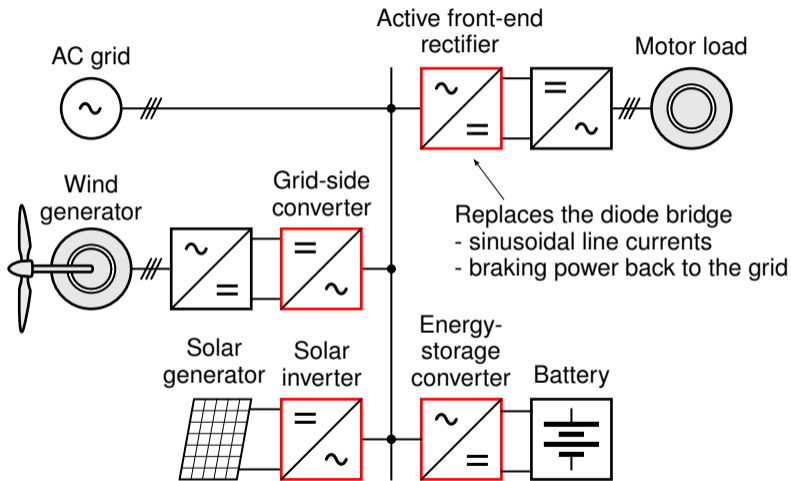Typical Applications: Renewable Energy and 4-Quadrant Drives



Example: 4-MW 690-V Grid-Side Converter of a Wind Generator


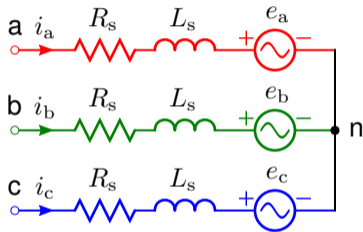


Figure: ABB ACS880

Inductive Filter and Grid Model

Grid-Voltage-Oriented Vector Control

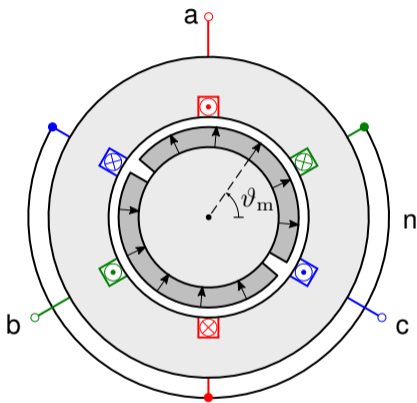
Review: 3-Phase Permanent-Magnet Synchronous Machine



$$e_a = -\omega_m \psi_f \sin(\vartheta_m)$$

$$e_b = -\omega_m \psi_f \sin(\vartheta_m - 2\pi/3)$$

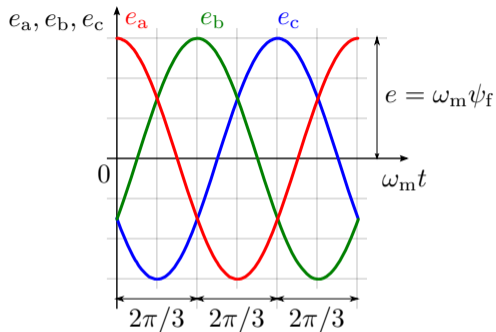
$$e_c = -\omega_m \psi_f \sin(\vartheta_m - 4\pi/3)$$



$$e_a = e \cos(\omega_m t)$$

$$e_b = e \cos(\omega_m t - 2\pi/3)$$



$$e_c = e \cos(\omega_m t - 4\pi/3)$$

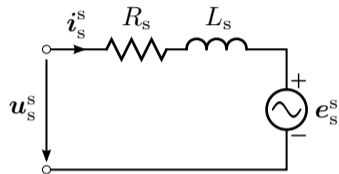

$$e_s = j\omega_m \psi_f e^{j\vartheta_m} \quad \vartheta_m = \int \omega_m dt$$

At constant speed $\vartheta_m = \omega_m t$


2-Level Voltage-Source Converter

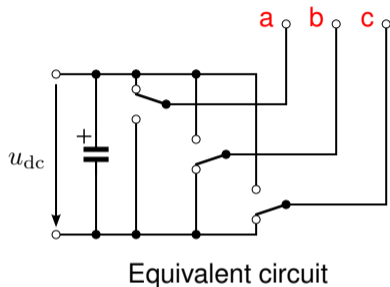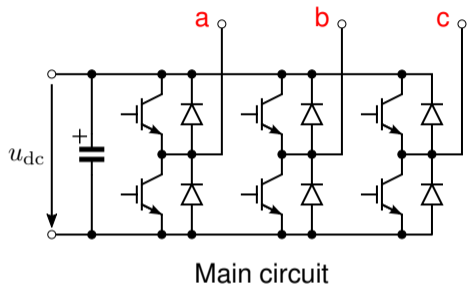

- ▶ 2-level converters are typical in low-voltage applications (< 1 kV)
- ▶ 3-level converters in medium-voltage applications
- ▶ Modular multilevel converters in high-voltage applications (> 10 kV)

Grid Converter: What Is to Be Controlled?

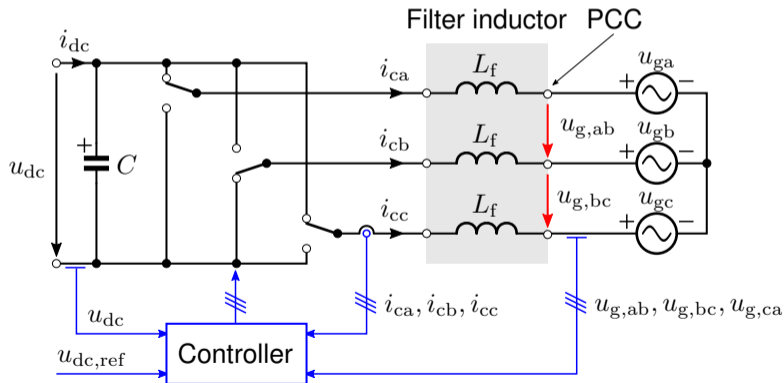- ▶ Active power: often via the DC-bus voltage controller
- ▶ Reactive power: displacement power factor
- ▶ Grid currents: typically 50-Hz sinusoidal waveforms are desired




- ▶ Filter inductors L_f are connected between the converter and the point of common coupling (PCC)
 - ▶ Grid behind the PCC is modeled as a balanced 3-phase voltage source
 - ▶ Harmonics and unbalance may exist in practice (especially during grid faults)
- ▶ Control resembles that of a synchronous motor drive
 - ▶ Grid voltage \sim back-emf
 - ▶ Filter inductor \sim stator inductance
 - ▶ Grid-voltage measurement \sim rotor-position measurement
- ▶ Grid converter can operate as **a rectifier or as an inverter**
 - ▶ Depends on the direction of the power flow

Space Vector Model: 3-Phase Grid Behind a Filter Inductor

Analogy to the synchronous machine model

- ▶ Converter voltage $u_c \sim u_s$
- ▶ Converter current $i_c \sim i_s$
- ▶ Filter inductance $L_f \sim L_s$
- ▶ Filter resistance $R_f \sim R_s$
- ▶ Grid voltage $u_g \sim e_s$
- ▶ Grid angular frequency $\omega_g \sim \omega_m$
- ▶ Grid-voltage angle $\vartheta_g \sim \vartheta_m$

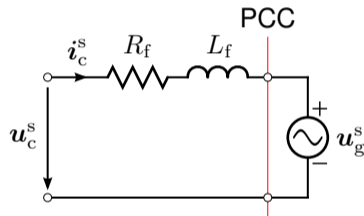Voltage magnitude u_g and frequency ω_g are constant in normal conditions. In the following, $R_f = 0$ will be assumed.



$$u_g^s = u_g e^{j\vartheta_g} \quad \vartheta_g = \int \omega_g dt$$

Inductive Filter and Grid Model

Grid-Voltage-Oriented Vector Control

Space-Vector Model: Synchronous Coordinates Rotating at ω_g

$$L_f \frac{d\mathbf{i}_c}{dt} = \mathbf{u}_c - \mathbf{u}_g - j\omega_g L_f \mathbf{i}_c$$

- Components of the space vectors

$$\mathbf{i}_c = i_{cd} + j i_{cq} \quad \mathbf{u}_c = u_{cd} + j u_{cq} \quad \mathbf{u}_g = u_{gd} + j u_{gq}$$

- Active power fed to the grid at the PCC

$$p_g = \frac{3}{2} \operatorname{Re} \{ \mathbf{u}_g \mathbf{i}_c^* \} = \frac{3}{2} (u_{gd} i_{cd} + u_{gq} i_{cq})$$

- Reactive power at the PCC

$$q_g = \frac{3}{2} \operatorname{Im} \{ \mathbf{u}_g \mathbf{i}_c^* \} = \frac{3}{2} (u_{gq} i_{cd} - u_{gd} i_{cq})$$

Grid-Voltage Coordinates


- ▶ Real axis (d-axis) of the coordinate system is fixed to the grid-voltage vector

$$\mathbf{u}_g = u_{gd} + j u_{gq} = u_g + j0$$

- ▶ Active power and reactive power

$$p_g = \frac{3}{2} u_g i_{cd} \quad q_g = -\frac{3}{2} u_g i_{cq}$$

Grid-Voltage-Oriented Vector Control

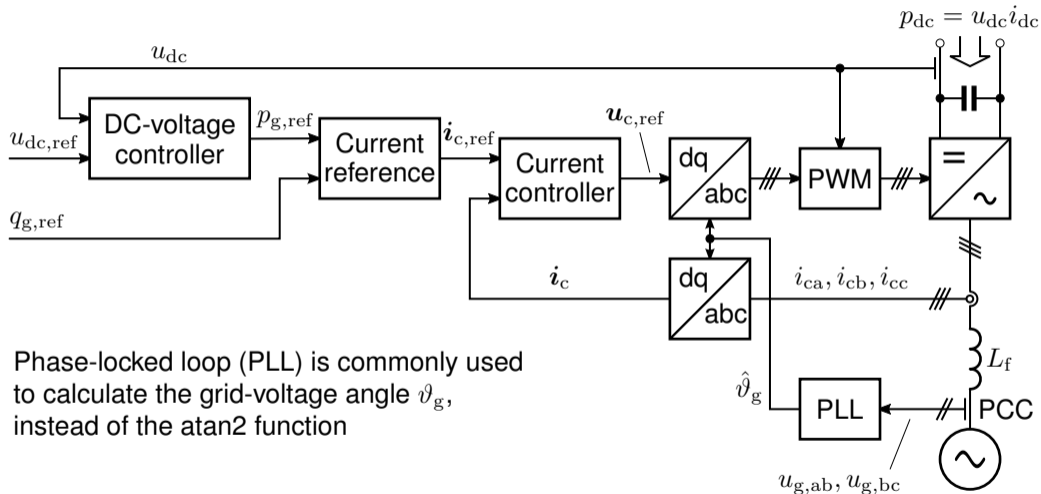

Phase-locked loop (PLL) is commonly used to calculate the grid-voltage angle \hat{v}_g , instead of the atan2 function

Current References

- ▶ Components of the current reference $\mathbf{i}_{c,\text{ref}} = i_{cd,\text{ref}} + j i_{cq,\text{ref}}$

$$i_{cd,\text{ref}} = \frac{2p_{g,\text{ref}}}{3u_g} \quad i_{cq,\text{ref}} = -\frac{2q_{g,\text{ref}}}{3u_g}$$


- ▶ Voltage u_g is constant in normal conditions
- ▶ Reactive power is often controlled to be zero, $i_{cq,\text{ref}} = 0$

Phase-Locked Loop¹

- ▶ Grid-voltage vector is measured

$$\mathbf{u}_g^s = u_g e^{j\vartheta_g}$$

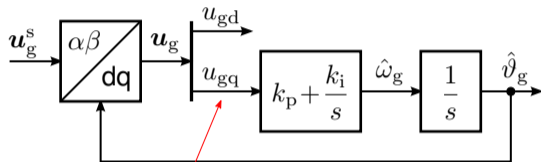- ▶ Angle ϑ_g can be noisy and it is not directly used in control
- ▶ PLL tracks ϑ_g and filters its noise and harmonics above the PLL bandwidth (without steady-state error)
- ▶ Additional filters and features could be included in the PLL



The PLL drives the signal u_{gq} to zero, leading to $\hat{\vartheta}_g = \vartheta_g$ and $u_{gd} = u_g$ in ideal conditions

¹Kaura and Blasko, "Operation of a phase locked loop system under distorted utility conditions," *IEEE Trans. Ind. Appl.*, 1997.

DC-Bus Voltage Dynamics


- ▶ Converter is assumed to be lossless

$$C \frac{du_{dc}}{dt} = i_{dc} - \frac{p_c}{u_{dc}}$$

- ▶ Can be rewritten using the capacitor energy

$$\frac{dW_{dc}}{dt} = u_{dc}i_{dc} - p_c = u_{dc}i_{dc} - \frac{dW_f}{dt} - p_g$$

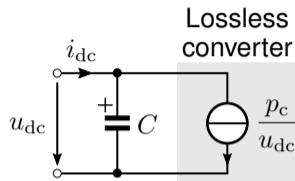- ▶ Ideal power control: $p_g = p_{g,ref}$
- ▶ $dW_f/dt = 0$ can be assumed
- ▶ Power $u_{dc}i_{dc}$ acts as a load disturbance



$$p_c = \frac{3}{2} \operatorname{Re}\{\mathbf{u}_c \mathbf{i}_c^*\}$$

$$W_{dc} = \frac{1}{2} C u_{dc}^2$$

$$W_f = \frac{3}{2} L_f i_c^2$$

Further Details

- ▶ Additional functions for grid faults
 - ▶ Identification of both positive and negative sequences of the grid voltage
 - ▶ Current control for both positive and negative sequences
 - ▶ Grid-fault identification algorithms
 - ▶ Operation during the grid fault as set in grid codes
(e.g. supporting the grid voltage by feeding the reactive power to the grid)
- ▶ LCL filter is more compact than the L filter
 - ▶ Resonance of the LCL filter has to be taken into account in the current controller
 - ▶ For example, a state-feedback controller can be used
- ▶ Active filtering of the grid-current harmonics is possible