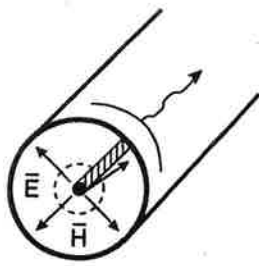



Transmission lines

- Electromagnetic waves can propagate in free space ← review this! based on Maxwell's equations!
- * but also they can be guided by conducting or dielectric boundaries
- Transmission-line behaviour; occurs when $\lambda \ll$ length of transmission line
- Transmission lines = guiding devices for the electromagnetic field
- The electromagnetic fields are TEM (transverse electromagnetic mode) if the conductors are ideal (zero-resistance); otherwise there will be a small axial component of the electromagnetic field.


Types of transmission lines




(a) = COAXIAL LINE

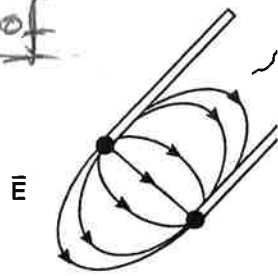


(b) = TWO-WIRE TRANSMISSION LINE

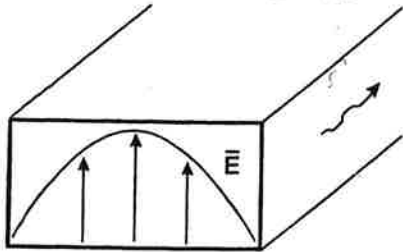


(c) = WAVEGUIDE (COPLANAR)

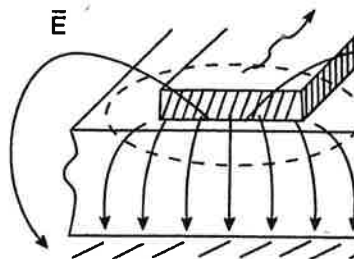

(d) = MICROSTRIP LINE

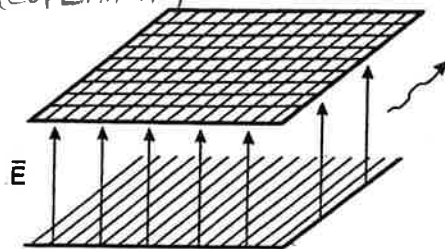


(e) = PARALLEL-PLATE WAVEGUIDE

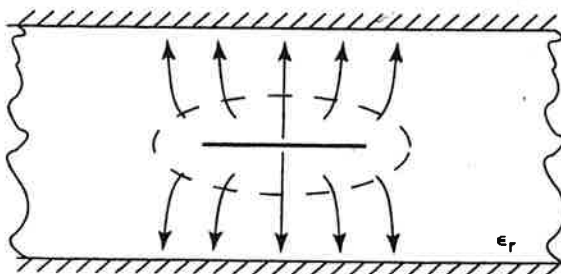


(f) = STRIPLINE

E ———
H - - -

EXAMPLE: The coaxial line

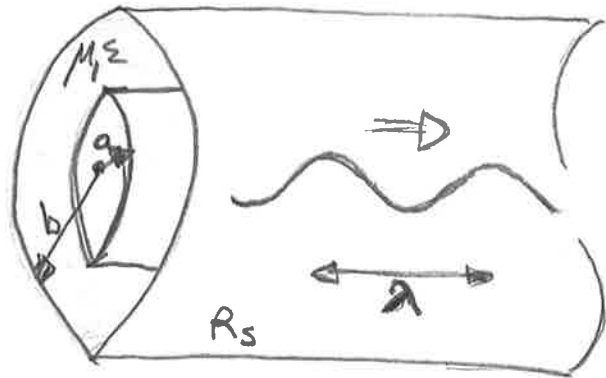

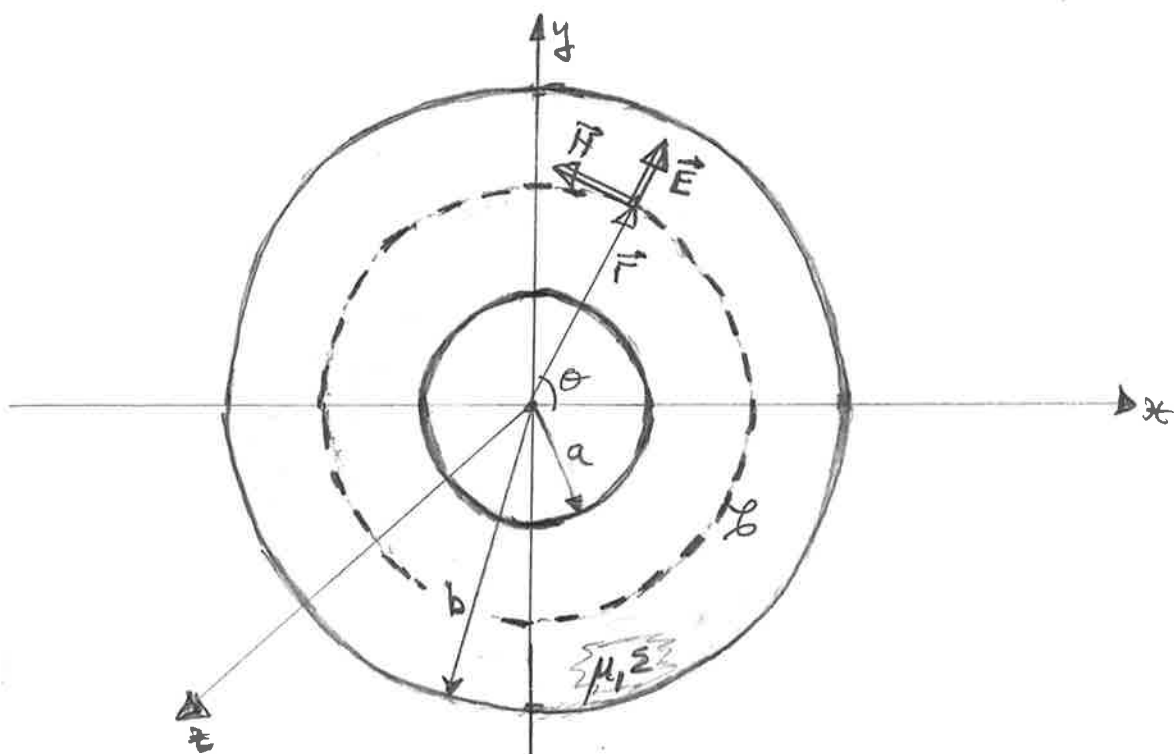
- How to calculate the \vec{E} , \vec{H} fields inside?



Electric field

$$\vec{E} = \frac{V_0}{\ln \frac{b}{a}} \frac{\hat{r}}{r}$$

Proof:

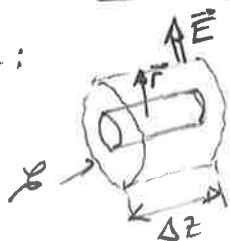

$$\nabla \cdot \vec{D} = \rho \Rightarrow$$

$$\int d\vec{s} \cdot \vec{E} = \int \frac{\rho}{\epsilon} dV \quad (\text{Gauss' law})$$

$$\downarrow \quad \downarrow$$

$$2\pi r (\Delta z) \cdot E \quad \frac{1}{\epsilon} (\Delta z) \cdot \rho \pi a^2$$

Therefore

$$E = \frac{1}{r} \cdot \frac{\rho a^2}{2\epsilon}$$

Also $V_0 = \int_a^b dr \cdot E$

$$= \int_a^b \frac{dr}{r} \cdot \frac{\rho a^2}{2\epsilon} = \frac{\rho a^2}{2\epsilon} \ln \frac{b}{a} \rightarrow \frac{\rho a^2}{2\epsilon} = \frac{V_0}{\ln \frac{b}{a}}$$

So $\vec{E} = \frac{V_0}{\ln \frac{b}{a}} \frac{\hat{r}}{r}$

Magnetic field

$$\vec{H} = \frac{I_0}{2\pi r} \hat{\phi}$$

$$\nabla \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t}$$


$$\oint \vec{H} \cdot d\vec{l} = \int \vec{J} \cdot d\vec{s} = I_0$$

$$\text{or } 2\pi r \cdot H = I_0 \Rightarrow H = \frac{I_0}{2\pi r} \hat{\phi}$$

Towards a distributed model of inductances, capacitances, resistances, conductances

Problem: how to connect the electric and magnetic fields to circuit-elements;

Answer: via stored or dissipated energy

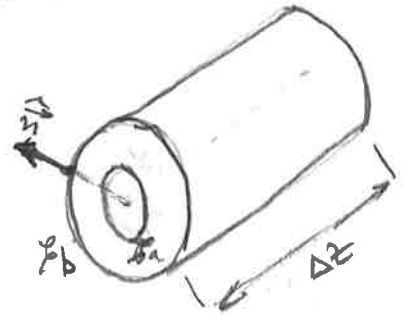

① Inductance per unit length

$$\text{magnetic energy} = \frac{\mu}{4} \int ds \cdot (\Delta z) H^2 = \frac{L' \Delta z I_0^2}{4} \Rightarrow L' = \frac{\mu}{I_0^2} \int ds H^2$$

$$L' = \frac{\mu}{I_0^2} \int ds H^2 = \frac{\mu}{I_0^2} \cdot I_0^2 \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{1}{(2\pi r)^2} = \frac{\mu}{2\pi} \ln \frac{b}{a}$$

$$\boxed{L' = \frac{\mu}{2\pi} \ln \frac{b}{a}}$$

(measured in H/m)

② Capacitance per unit length

$$\text{electrostatic energy} = \frac{\epsilon}{4} \int ds \cdot (\Delta z) \cdot E^2 = \frac{C' \Delta z V_0^2}{4} \Rightarrow C' = \frac{\epsilon}{V_0^2} \cdot \int ds \cdot E^2$$

$$C' = \frac{\epsilon}{V_0^2} \int ds E^2 = \frac{\epsilon}{V_0^2} \cdot V_0^2 \cdot \frac{1}{\ln^2 \frac{b}{a}} \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{1}{r^2} = 0$$

$$\boxed{C' = \frac{2\pi \epsilon}{\ln \frac{b}{a}}}$$

(measured in F/m)

③ Resistance per unit length

$$\text{power dissipated in the lossy conductors} = \frac{R_s}{2} \int_{\mathcal{S}_a + \mathcal{S}_b} dl \cdot \Delta z \cdot \mathbf{J}_s^2 = \frac{R_s}{2} \Delta z \cdot \int_{\mathcal{S}_a + \mathcal{S}_b} dl \cdot H^2 = \frac{R' \Delta z I_0^2}{2}$$

Here R_s = surface resistance (measured in Ω)

$\mathbf{J}_s = \hat{n} \times \mathbf{H}$ = surface current density (measured in A/m)

\hat{n} = vector unit pointing outwards

(normal to the conducting surface)

$$R' = \frac{R_s}{I_0^2} \int_{\mathcal{S}_a + \mathcal{S}_b} dl \cdot H^2$$

$$R' = \frac{R_s}{I_0^2} \int_{\mathcal{S}_a + \mathcal{S}_b} dl \cdot H^2 = \frac{R_s}{(2\pi)^2} \left[\int_0^{2\pi} d\theta \cdot a \cdot \frac{1}{a^2} + \int_0^{2\pi} d\theta \cdot b \cdot \frac{1}{b^2} \right] = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$$


we integrate over the perimeters of circles of radius a or b

$$\boxed{R' = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)}$$

(measured in Ω/m)

• Resistance per unit length \rightarrow a bit more in-depth if you are interested

Take a slab of metal:

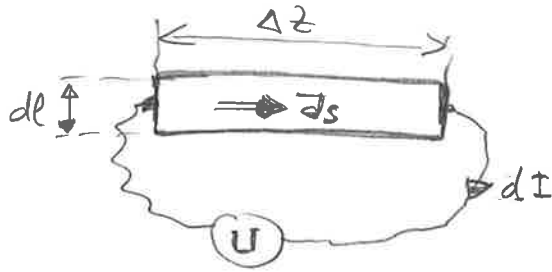

We have defined

$$\text{The current density } \vec{J} = \frac{dI}{dS} = \frac{\text{charge/time}}{\text{area}}$$


but for sheets of metals we can define

$$\vec{J}_s = \frac{dI}{dl} = \frac{\text{charge/time}}{\text{unit length across the sheet}}$$

Then $R_s \equiv \frac{U/\Delta z}{\vec{J}_s} = \text{surface resistance} \leftarrow \text{units of Ohm}$

$$\begin{aligned} \text{So power dissipated} &= \frac{1}{2} \int dI \cdot U = \frac{1}{2} \Delta z \cdot \int dl \cdot (R_s \vec{J}_s) \cdot \vec{J}_s \\ &= \frac{1}{2} \Delta z \int dl \cdot R_s \vec{J}_s^2 \end{aligned}$$

We also have

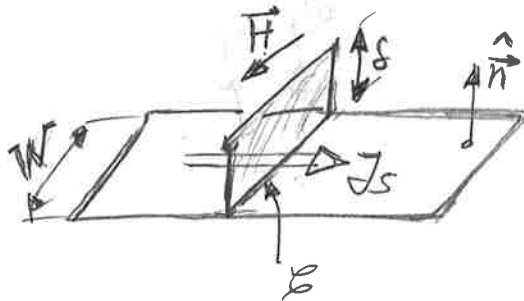

Let us take \vec{H} like in this figure, which is the case for the coaxial transmission line

$$\begin{aligned} \text{Then } \oint_{\mathcal{C}} \vec{H} \cdot d\vec{l} &= H \cdot W \\ &= \int_S \left(\vec{J} + \frac{\partial \vec{D}}{\partial t} \right) \cdot d\vec{S} = \underbrace{\vec{J} \cdot \delta \cdot W}_{= \vec{J}_s} \end{aligned}$$

\Rightarrow

$$\vec{J}_s = \vec{H},$$

More generally, for an arbitrary vector \vec{H} ,

$$\vec{J}_s = \hat{n} \times \vec{H}$$

④ Conductance (radial) per unit length

$$\Sigma = \Sigma' - i \Sigma'' = \Sigma_0 \Sigma_r (1 - i \tan \delta)$$

$$\Sigma' = \Sigma_0 \Sigma_r$$

$\Sigma'' = \Sigma \tan \delta \rightarrow$ dissipation in the dielectric between the core metal and the outside shield.

$$\text{power dissipated} = \frac{\omega \Sigma''}{2} \int ds \cdot \Delta z \cdot E^2 = \frac{G' V_0^2}{2} \rightarrow G' = \frac{\omega \Sigma''}{V_0^2} \cdot \int ds \cdot E^2$$

$$\Rightarrow G' = \frac{\omega \Sigma''}{V_0^2} \int ds \cdot E^2 = \frac{\omega \Sigma''}{V_0^2} \cdot \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{V_0^2}{r^2 \ln \frac{b}{a}} \Rightarrow \boxed{G' = \frac{2\pi \omega \Sigma''}{\ln \frac{b}{a}}}$$


(measured in S/m)

Examples of materials used in coaxes

Conductor	Copper Cu	Aluminum Al	Silver Ag	Gold Au
Resistivity ρ [mΩ·m] ↓ 10^{-9} "nano"	16.9	26.7	16.3	22.0

Dielectric	Dry air	Polyethylene	PTFE	PVC
Σ_r	1.0006	2.2	2.1	3.2
$\tan \delta$	low	0.0002	0.0002	0.001
Resistivity (Ω·m)	high	10^{15}	10^{15}	10^{15}
Breakdown voltage (kV/m)	3	47	59	34

Other transmission lines:

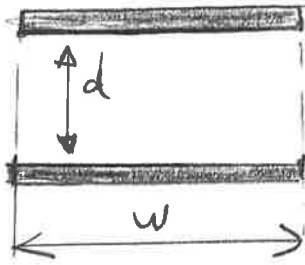


$$L' = \frac{\mu d}{w}$$

$$C' = \frac{\epsilon' w}{d}$$

$$R' = \frac{2R_s}{w}$$

$$G' = \frac{\omega \epsilon'' w}{d}$$

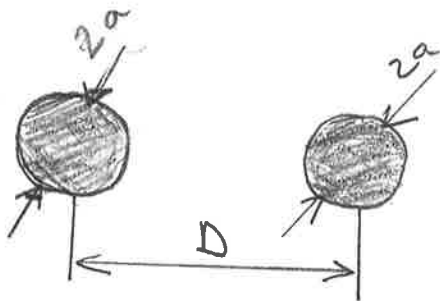

$$L' = \frac{\mu}{\pi} \cosh^{-1} \frac{D}{2a}$$


$$C' = \frac{\pi \epsilon'}{\cosh^{-1} \frac{D}{2a}}$$

$$R' = \frac{R_s}{\pi a}$$

$$G' = \frac{\pi \omega \epsilon''}{\cosh^{-1} \frac{D}{2a}}$$

TRANSMISSION LINES - general models

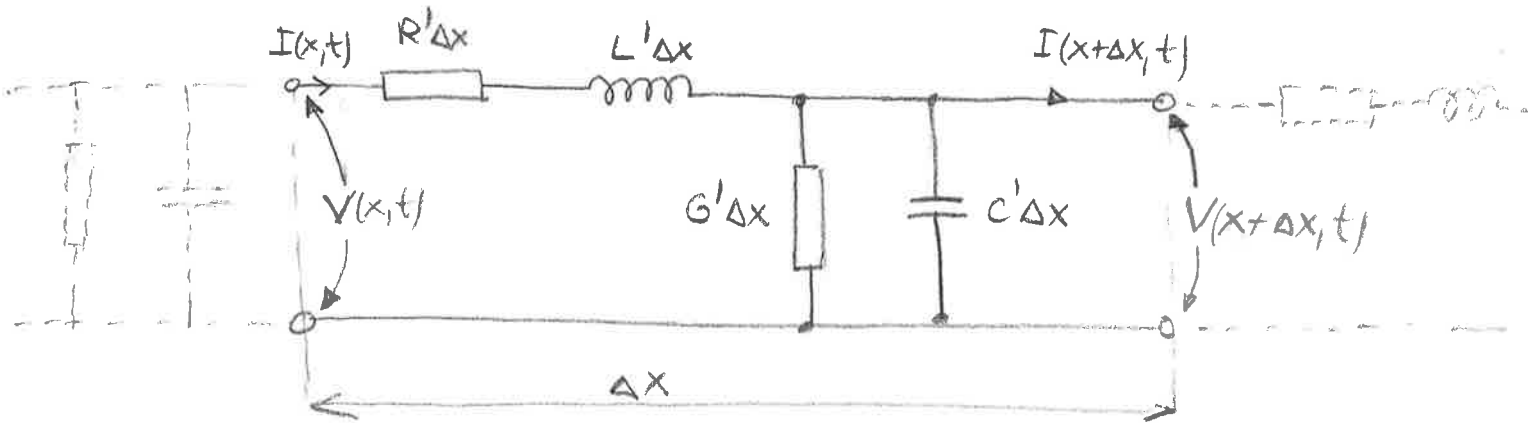- If the length of a circuit is $\geq \lambda$ we have to use either a simulator of Maxwell's equations or a distributed model of lumped elements.
- TLs = two parallel conductors that guide the electromagnetic field
examples: two-wire lines, striplines, microstrip lines



R', L', G', C' = resistance, inductance, conductance, capacitance per unit length.

KIRCHHOFF says:

$$\begin{cases} V(x,t) = I(x,t)R'\Delta x + L'\Delta x \cdot \frac{\partial I(x,t)}{\partial t} + V(x+\Delta x,t) \\ I(x,t) = V(x+\Delta x,t)G'\Delta x + C'\Delta x \frac{\partial V(x+\Delta x,t)}{\partial t} + I(x+\Delta x,t) \end{cases}$$

$\Delta x \rightarrow 0$

$$\begin{cases} -\frac{\partial V(x,t)}{\partial x} = R' I(x,t) + L' \frac{\partial I(x,t)}{\partial t} \\ -\frac{\partial I(x,t)}{\partial x} = G' V(x,t) + C' \frac{\partial V(x,t)}{\partial t} \end{cases}$$

Therefore,

$$\begin{cases} -\frac{\partial^2 V(x,t)}{\partial x^2} = -R'(G'V(x,t) + C' \frac{\partial V(x,t)}{\partial t}) - L'(G' \frac{\partial V(x,t)}{\partial t} + C' \frac{\partial^2 V(x,t)}{\partial t^2}) \\ -\frac{\partial^2 I(x,t)}{\partial x^2} = -G'(R'I(x,t) + L' \frac{\partial I(x,t)}{\partial t}) - C'(R' \frac{\partial I(x,t)}{\partial t} + L' \frac{\partial^2 I(x,t)}{\partial t^2}) \end{cases}$$

or

$$\begin{cases} \frac{\partial^2 V(x,t)}{\partial x^2} = L'C' \frac{\partial^2 V(x,t)}{\partial t^2} + (RC' + LG') \frac{\partial V(x,t)}{\partial t} + R'G'V(x,t) \\ \frac{\partial^2 I(x,t)}{\partial x^2} = L'C' \frac{\partial^2 I(x,t)}{\partial t^2} + (RC' + LG') \frac{\partial I(x,t)}{\partial t} + R'G'I(x,t) \end{cases}$$

Harmonic signals:

$$V(x,t) = V(x) e^{i\omega t}$$

$$I(x,t) = I(x) e^{i\omega t}$$

$V(x), I(x)$ = phasors

$$\Rightarrow \begin{cases} \frac{d^2 V(x)}{dx^2} - \gamma^2 V(x) = 0 \\ \frac{d^2 I(x)}{dx^2} - \gamma^2 I(x) = 0 \end{cases}$$

$$\gamma = \alpha + i\beta =$$

$$= \sqrt{(R' + i\omega L')(G' + i\omega C')}$$

γ = propagation constant

α = attenuation constant

β = phase constant

$$\Rightarrow \boxed{V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x}}$$

general solution

From $-\frac{\partial V(x,t)}{\partial x} = R'I(x,t) + L'\frac{\partial I(x,t)}{\partial t}$

we get $I(x) = -\frac{1}{R' + i\omega L'} \frac{dV(x)}{dx}$

or

$$I(x) = \frac{1}{Z_0} V^+ e^{-\gamma x} - \frac{1}{Z_0} V^- e^{\gamma x}$$

where

$$Z_0 = \sqrt{\frac{R' + i\omega L'}{G' + i\omega C'}} = \text{characteristic impedance of the transmission line}$$

$$= I^+ e^{-\gamma x} + I^- e^{\gamma x} \quad \text{where } I^\pm = \pm \frac{V^\pm}{Z_0}$$

Lossless transmission case: $R' = G' = 0$

$$\gamma = i\beta = i\omega \sqrt{LC'}$$

$$Z_0 = \frac{L}{Y_0} = \sqrt{\frac{L}{C'}} \rightarrow \text{now independent of frequency!}$$

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC'}} = \text{phase velocity}$$

Note: free-space impedance = 377 Ω

Exercise: Show that for the low-loss case $R' \ll \omega L', G' \ll \omega C'$ we have

$$\beta \approx \omega \sqrt{LC'}$$

$$\alpha \approx \frac{1}{2} \sqrt{LC'} \left(\frac{R'}{L} + \frac{G'}{C'} \right)$$

Standardized values:

Z_0	Application
50 Ω	Instrumentation, communication
75 Ω	TV, VHF radio
300 Ω	RF
600 Ω	audio

• A note on the meaning of $V^+ e^{-\gamma x}$ and $V^- e^{+\gamma x}$.

These are phasors of waves propagating in the positive direction of the x -axis, respectively negative direction.

To see this, consider the "+" wave

$$V^+ e^{-\gamma x} e^{i\omega t} = V^+ e^{-\alpha x} e^{i\omega(t - \frac{x}{v_p})} \quad \text{where } \gamma = \alpha + i\beta$$

$$v_p = \frac{\omega}{\beta}$$

$$t - \frac{x}{v_p} = \varphi = \text{constant} \rightarrow \text{means}$$

$$x = + \frac{t v_p}{1} - \varphi$$

(propagation in the positive direction)

Differently, the "-" wave is

$$V^- e^{+\gamma x} e^{i\omega t} = V^- e^{-\alpha x} e^{i\omega(t + \frac{x}{v_p})}$$


$$t + \frac{x}{v_p} = \varphi \Rightarrow x = - \frac{t v_p}{1} - \varphi$$

(propagation in the negative direction)

So V^+ = forward wave

V^- = associated with reflection from a load

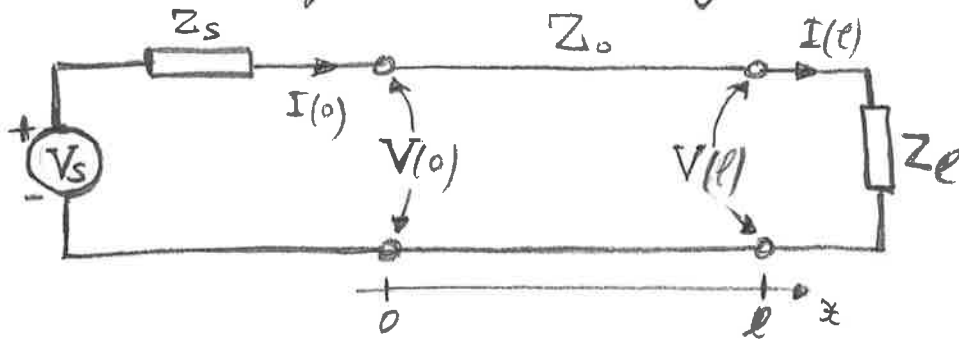• Incident and reflected waves along a loaded transmission line



line terminated
in a
load impedance
 Z_l

$$V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x}$$

$$I(x) = I^+ e^{-\gamma x} + I^- e^{\gamma x}$$

$$I^\pm = \pm \frac{V^\pm}{Z_0}$$

$$\begin{cases} V(0) = V_s - Z_s I(0) & \text{--- Kirchhoff's law} \\ V(l) = Z_l I(l) \end{cases}$$

or;

$$\begin{cases} V^+ + V^- = V_s - \frac{Z_s}{Z_0} (V^+ + V^-) \\ V^+ e^{-\gamma l} + V^- e^{\gamma l} = \frac{Z_l}{Z_0} (V^+ e^{-\gamma l} - V^- e^{\gamma l}) \end{cases}$$

• Define a reflection coefficient at the load $x=l$

$$\Gamma_V = \frac{V^- e^{\gamma l}}{V^+ e^{-\gamma l}}$$

$$\rightarrow 1 + \Gamma_V = \frac{Z_l}{Z_0} (1 - \Gamma_V) \Rightarrow \boxed{\Gamma_V = \frac{Z_l - Z_0}{Z_l + Z_0}}$$

We can also define a current reflection coefficient at the load

$$\boxed{\Gamma_I = \frac{I^- e^{\gamma l}}{I^+ e^{-\gamma l}} = -\Gamma_V}$$

• Define the Transmission coefficient at the load $x=l$

$$T_V = \frac{V^+ e^{-\gamma l} + V^- e^{\gamma l}}{V^+ e^{-\gamma l}}$$

$$\text{or } \boxed{T_V = 1 + \Gamma_V}$$

and for current

$$\boxed{T_I = \frac{I^+ e^{-\gamma l} + I^- e^{\gamma l}}{I^+ e^{-\gamma l}} = 1 + \Gamma_I}$$

• Average power delivered to the load

$$\bar{P}_e = \frac{1}{2} \operatorname{Re} [V(l) I^*(l)]$$

$\frac{1}{2}$ - comes from the fact that the field is harmonic

$$\begin{aligned} \text{Now } 1 - \Gamma_V &= \frac{I^- e^{\gamma l} + I^+ e^{-\gamma l}}{I^+ e^{-\gamma l}} = \frac{I(l)}{I^+ e^{-\gamma l}} \\ 1 + \Gamma_V &= \frac{V^+ e^{-\gamma l} + V^- e^{\gamma l}}{V^+ e^{-\gamma l}} = \frac{V(l)}{V^+ e^{-\gamma l}} \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow$$

$$(1 - \Gamma_V^*)(1 + \Gamma_V) = \frac{V(l) I^*(l)}{I^{+*} V^+ e^{-\gamma l} (e^{-\gamma l})^*} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow$$

but $I^+ = \frac{V^+}{Z_0}$


$$\begin{aligned} V(l) I^*(l) &= \frac{1}{Z_0} |V^+ e^{-\gamma l}|^2 \cdot \underbrace{(1 - \Gamma_V^*)(1 + \Gamma_V)}_{\equiv 1 - \Gamma_V^* + \Gamma_V - |\Gamma_V|^2} \\ &\quad \downarrow \\ &\quad \text{imaginary!} \end{aligned}$$

$$\Rightarrow \bar{P}_e = \frac{1}{2Z_0} |V^+ e^{-\gamma l}|^2 (1 - |\Gamma_V|^2)$$

• VSWR (voltage standing-wave ratio)

$$V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x} = V^+ e^{-\gamma x} [1 + \Gamma_V e^{-2\gamma(l-x)}]$$

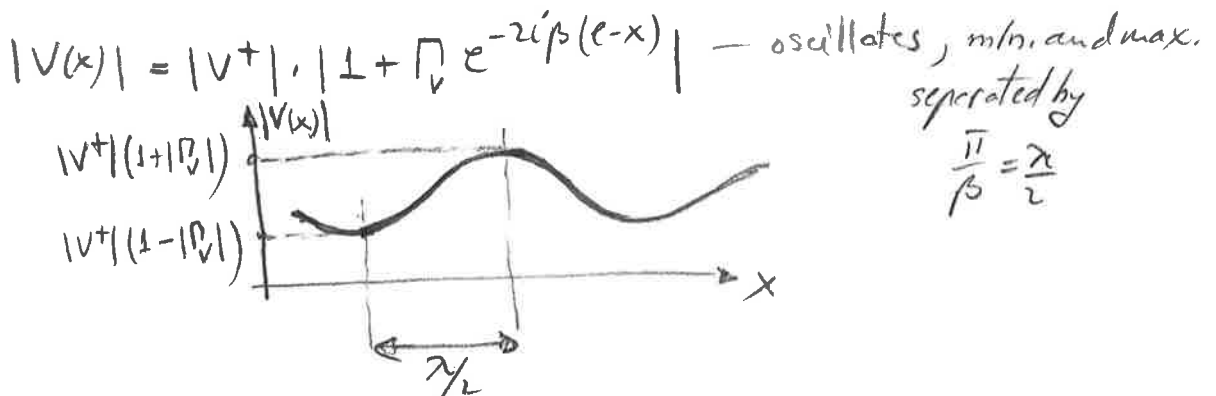Let's consider a lossless line $\alpha = 0$ remember that $\Gamma_V \equiv \frac{V^- e^{\gamma l}}{V^+ e^{-\gamma l}}$
 $\gamma = i\beta = \frac{2\pi i}{\lambda}$



$$\text{VSWR} = \frac{1 + |\Gamma_V|}{1 - |\Gamma_V|} = \text{ratio between the max. line voltage and min. line voltage}$$

• Impedance along the line

$$Z(x) \equiv \frac{V(x)}{I(x)} = Z_0 \frac{V^+ e^{-\gamma x} + V^- e^{\gamma x}}{V^+ e^{-\gamma x} - V^- e^{\gamma x}} = Z_0 \frac{1 + \Gamma_V e^{-2\gamma(l-x)}}{1 - \Gamma_V e^{-2\gamma(l-x)}}$$

take $x=0 \rightarrow$ we get $Z(0) \equiv Z_{in}$ = input impedance of the line,
i.e. the impedance seen when looking toward the load.

$$Z_{in} = Z_0 \cdot \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l}$$

— can be verified immediately
by recalling that

$$\Gamma_V = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Note that in general $Z_{in} \neq Z_0$, so the termination matters!

and also Z_{in} is frequency-dependent

References:

- David M. Pozar — Microwave Engineering
- R.E. Collin — Foundations for Microwave Engineering