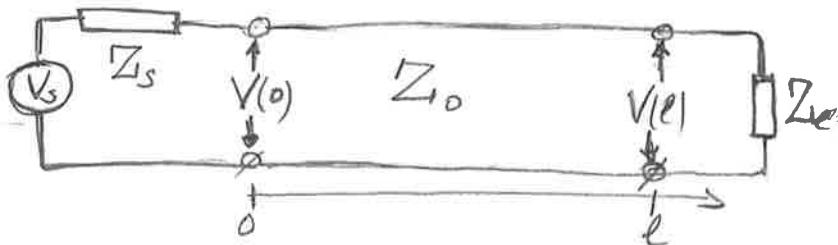


# Resonators from transmission lines

• Review from last lecture:



$$\Gamma_v = \frac{Z_e - Z_0}{Z_e + Z_0} = -\Gamma_I$$

$$T_v = 1 + \Gamma_v^2 \quad T_I = 1 + \Gamma_I^2$$

$$\bar{P}_e = \frac{1}{2Z_0} |V^+ e^{-j\delta l}|^2 (1 - |\Gamma_v|^2)$$

$$VSWR = \frac{1 + |\Gamma_v|}{1 - |\Gamma_v|}$$

$$Z_{in} = Z_0 \cdot \frac{Z_e + Z_0 \tanh \gamma l}{Z_0 + Z_e \tanh \gamma l}$$


## EXAMPLES OF LOADS (TERMINATIONS)

### 1) Matched load

$$Z_e = Z_0$$

$$\Rightarrow \Gamma_v = \frac{Z_e - Z_0}{Z_e + Z_0} = 0$$

No reflection!

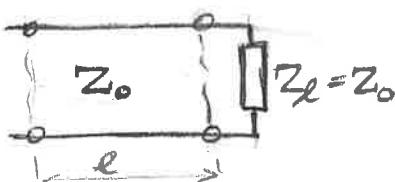

$$VSWR = 1, \quad P_e = \frac{1}{2Z_0} |V^+|^2 e^{-2\alpha l} \quad \begin{aligned} &\text{- power delivered} \\ &\text{is maximal,} \\ &\text{it is only} \\ &\text{attenuated if } \alpha \neq 0 \end{aligned}$$


$$Z_{in} = Z_0$$

### 2) Open-circuit

$$Z_e = \infty$$

$$\Gamma_v = \frac{Z_e - Z_0}{Z_e + Z_0} = 1$$


$$Z_{in} = Z_0 \coth \gamma l$$

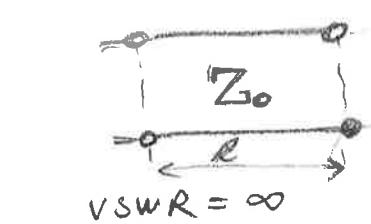

$$\text{For } \alpha = 0 \text{ (lossless)} \\ Z_{in} = -i Z_0 \cot \frac{2\pi l}{\lambda}$$

$$P_e = 0 \quad \begin{aligned} &\text{- compare } P_{in} \\ &\text{with } P_{DC} \text{ - case} \\ &\text{where all input} \\ &\text{power is} \\ &\text{delivered!} \end{aligned}$$

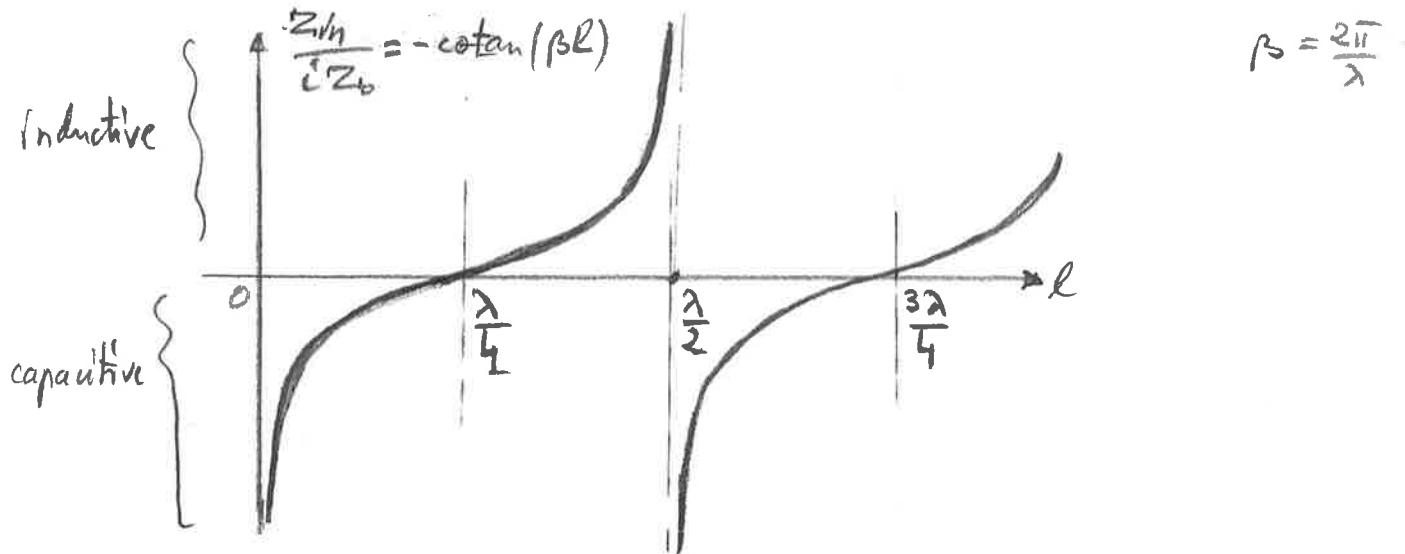
if  $l = \frac{\lambda}{4}$ ,  $Z_{in} = 0$   
so the open line will look as a short circuit!


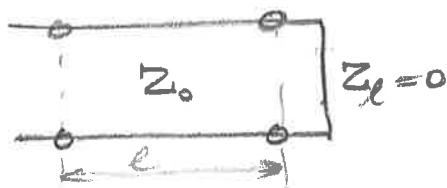
### 3) Short-circuit

$$Z_L = 0$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$



$$VSWR = \infty \quad P_L = 0$$


$$Z_{in} = Z_0 \tanh \beta l$$

$$\text{For } \alpha = 0 \text{ (lossless)} \quad \beta = \frac{2\pi}{\lambda}$$

$$Z_{in} = iZ_0 \tan \frac{2\pi l}{\lambda}$$


if  $l = \frac{\lambda}{4}$ ,  $Z_{in} = \infty$   
so the shorted line  
looks like an  
infinite impedance  
to a source!

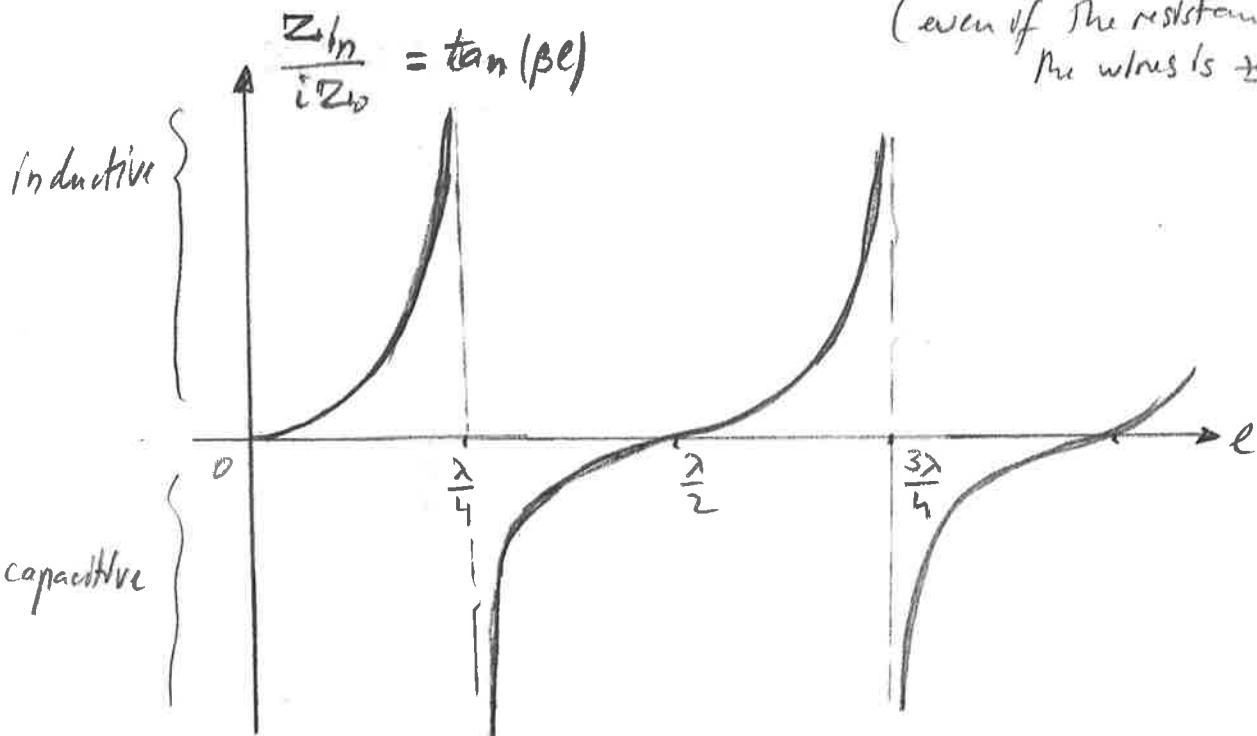(even if the resistance of  
the wires is zero!)


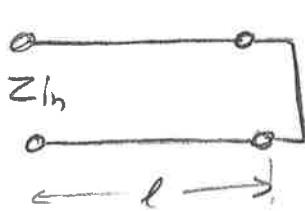
## Resonators from transmission lines

- It is possible to make resonators from transmission lines, 3D cavities, etc.
- The most usual case is the short-circuited transmission-line resonator.



$$Z_e = 0$$

$$Z_{in} = Z_0 \tanh(\alpha l + i \beta l)$$

$$= Z_0 \frac{\tanh \alpha l + i \tan \beta l}{1 + i \tan \beta l \tanh \alpha l}$$

If losses are not too large,  $\alpha l \ll 1$ , we have  $\tanh \alpha l \approx \alpha l$

so  $Z_{in} = Z_0 \frac{\alpha l + i \tan \beta l}{1 + i \alpha l \tan \beta l}$

Now, recall

$$\text{that } \beta = \frac{\omega}{v_p} = \omega \sqrt{L/C} \quad v_p = \frac{1}{\sqrt{L/C}}$$

see Lecture 3

$$Z_0 \approx \sqrt{\frac{L}{C}}$$

$$\alpha \approx \frac{R'}{2} \sqrt{\frac{C}{L}}$$

we also take  $G' = 0$

We will consider  $\beta l = \pi$  or  $l = \frac{\lambda_0}{2}$

as the resonance condition, leading to

$$\text{a resonance frequency } \omega_0 \quad \frac{\omega_0}{v_p} l = \omega_0 \sqrt{L/C} l = \pi$$

$$\text{so } \omega_0 = \frac{\pi C}{l \sqrt{L/C}}$$

You can see that  $\omega_0 = 2\pi \times \omega_0$  where  $\omega_0 = \frac{v_p}{Z_0} = \frac{v_p}{Z_e}$  so everything is consistent,  
 $\omega_0$  = oscillation frequency

We can expand around this point

$$\tan \beta l \approx \tan \left( \pi + \pi \frac{w-w_0}{\omega_0} \right) = \tan \pi \frac{w-w_0}{\omega_0} \simeq \pi \frac{w-w_0}{\omega_0}$$


if  $|w-w_0| \ll \omega_0$

So

$$Z_{in} = Z_0 \frac{\alpha l + i \pi \frac{w-w_0}{\omega_0}}{1 + \alpha l \pi \frac{w-w_0}{\omega_0}} \simeq Z_0 \left( \alpha l + i \pi \frac{w-w_0}{\omega_0} \right)$$

$$= \sqrt{\frac{L'}{C}} \left( \frac{l}{2} R' \sqrt{\frac{C}{L'}} + i l \sqrt{L'C} (w-w_0) \right) = \frac{l}{2} R' l + i L' l (w-w_0)$$

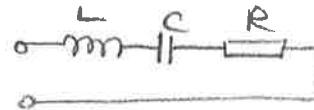- Suppose now that we look back at a series RLC circuit



$$Z = R + i \frac{L}{\omega} (w^2 - w_0^2)$$

$$\simeq R + 2iL(w-w_0) \text{ near resonance, } w \approx w_0$$

Therefore we can identify  $R = \underline{\underline{R'}}$  and  $L = \underline{\underline{L'}}$

$$\text{Quality factor } Q = \frac{\omega_0 L}{R} = \frac{\omega_0 L'}{R'} = \frac{\beta_0}{2\alpha}$$

- Interesting question to think about: why do we get the factor  $\frac{1}{2}$  in the RLC equivalent above?

Because the current

in the short-circuited line is half a sinusoid,

therefore we obtain only half of the total resistance and inductance of the full length  $l$ .

To see this explicitly, let us write the solution

$$\begin{cases} V(x) \simeq V^+ e^{-i\beta x} + V^- e^{i\beta x} & \text{— here we neglect } \alpha \\ I(x) \simeq -\frac{\beta}{\omega L} (-V^+ e^{-i\beta x} + V^- e^{i\beta x}) \end{cases}$$

Since  $I(0) = 0 \Rightarrow V^+ = V^-$  at this point

(also you can see that  $\Gamma_v = \frac{V^-}{V^+} e^{+2i\beta l} = -1$  and  $\beta l = \pi$ )

$$\begin{cases} V(x) = 2V^+ \cos \beta_0 x \\ I(x) = -\frac{2i\beta_0}{\omega L} V^+ \sin \beta_0 x = I^+ \sin \beta_0 x \end{cases}$$

Therefore the magnetic field energy

$$\begin{aligned} \bar{W}_L &= \int_0^{\lambda_0/2} dx \cdot \frac{1}{2} L' |I(x)|^2 = \frac{1}{2} |I^+|^2 L' \int_0^{\lambda_0/2} \sin^2 \beta_0 x dx \\ &= \frac{\lambda_0}{16} |I^+|^2 L' \end{aligned}$$

$$\bar{W}_C = \bar{W}_L \text{ at resonance} \quad \text{so} \quad \bar{W} = \bar{W}_C + \bar{W}_L = \frac{\lambda_0}{8} L' |I^+|^2$$

$$\begin{aligned} \bar{P} &= \frac{1}{2} \int_0^{\lambda_0/2} dx \cdot R' |I(x)|^2 = \frac{R'}{2} |I^+|^2 \int_0^{\lambda_0/2} \sin^2 \beta_0 x dx \\ &\text{so} \quad \bar{P} = \frac{\lambda_0}{8} R' |I^+|^2 \end{aligned}$$

$$\text{Therefore } Q = \frac{\omega_0 \bar{W}}{\bar{P}} = \frac{\omega_0 L'}{R'}$$

$$\text{or: } Q = \frac{\pi}{\ell R'} \sqrt{\frac{L'}{Q}} = \frac{\pi Z_0}{\ell R'} = \frac{\pi}{2 \ell \alpha}$$

$$\text{where we used } \alpha \approx \frac{R}{2Z_0}, \quad \omega_0 = \frac{\pi}{\ell \sqrt{LC}}$$

## REFERENCES

- David M. Pozar - Microwave Engineering
- R.E. Collin - Foundations for Microwave Engineering