



**Aalto University
School of Electrical
Engineering**

**Lecture 9:
Grid Converters: Power Angle Equation, LCL Filter
ELEC-E8402 Control of Electric Drives and Power Converters**

Marko Hinkkanen

Spring 2023

Learning Outcomes

After this lecture you will be able to:

- ▶ Derive the power angle equation and draw the corresponding vector diagrams
- ▶ Explain why a filter is needed between the converter and the grid
- ▶ Explain the most important characteristics of an LCL filter and compare it to an L filter

Some experimental examples are also included, but their details are not covered

Power Angle Equation



PWM Voltage

LCL Filter

Inductor Size

Example of Experimental Results

Space-Vector Equivalent Circuit

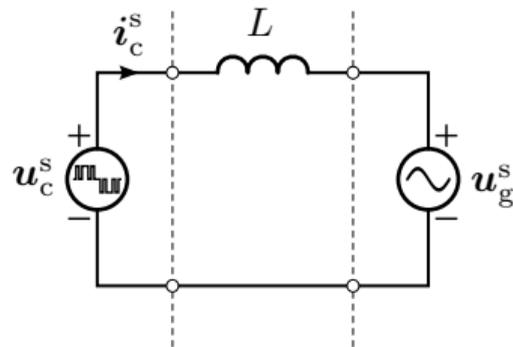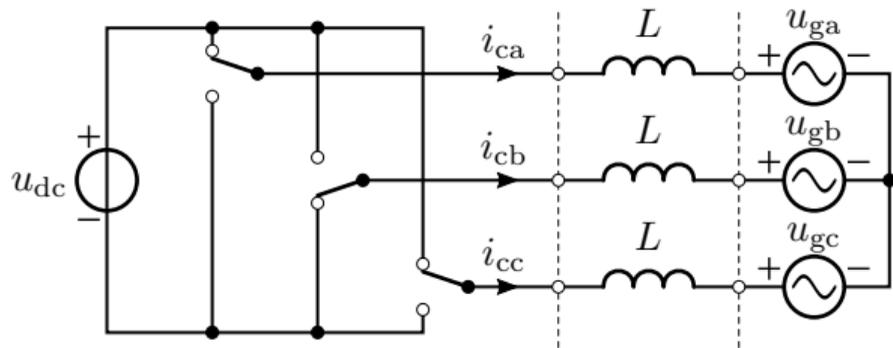

In synchronous coordinates:
$$L \frac{di_c}{dt} = u_c - u_g - j\omega_g L i_c$$

The inductance L is the total inductance of the filter and the grid. It is also to be noted that the converter voltage u_c contains PWM harmonics.

Power Angle Equation

- ▶ Power fed to the grid

$$\begin{aligned} p_g &= \frac{3}{2} \operatorname{Re} \{ \mathbf{u}_g \mathbf{i}_c^* \} \\ &= \frac{3}{2} |\mathbf{u}_g| |\mathbf{i}_c| \cos \varphi \end{aligned}$$


where φ is the angle between \mathbf{u}_g and \mathbf{i}_c

- ▶ Consider the steady state and the fundamental component

$$\mathbf{i}_c = \frac{\mathbf{u}_c - \mathbf{u}_g}{j\omega_g L}$$


- ▶ Substituting \mathbf{i}_c to the power expression yields the power angle equation

$$\begin{aligned} p_g &= \frac{3}{2} \frac{1}{\omega_g L} \operatorname{Im} \{ \mathbf{u}_c \mathbf{u}_g^* \} \\ &= \frac{3}{2} \frac{|\mathbf{u}_c| |\mathbf{u}_g|}{\omega_g L} \sin \delta \end{aligned}$$

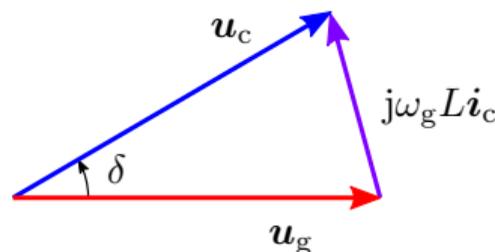

If per-unit values are used, the factor $3/2$ in the power equation and the factor $3n_p/2$ in the torque equation disappear.

Examples: Strong Grid and Very Weak Grid

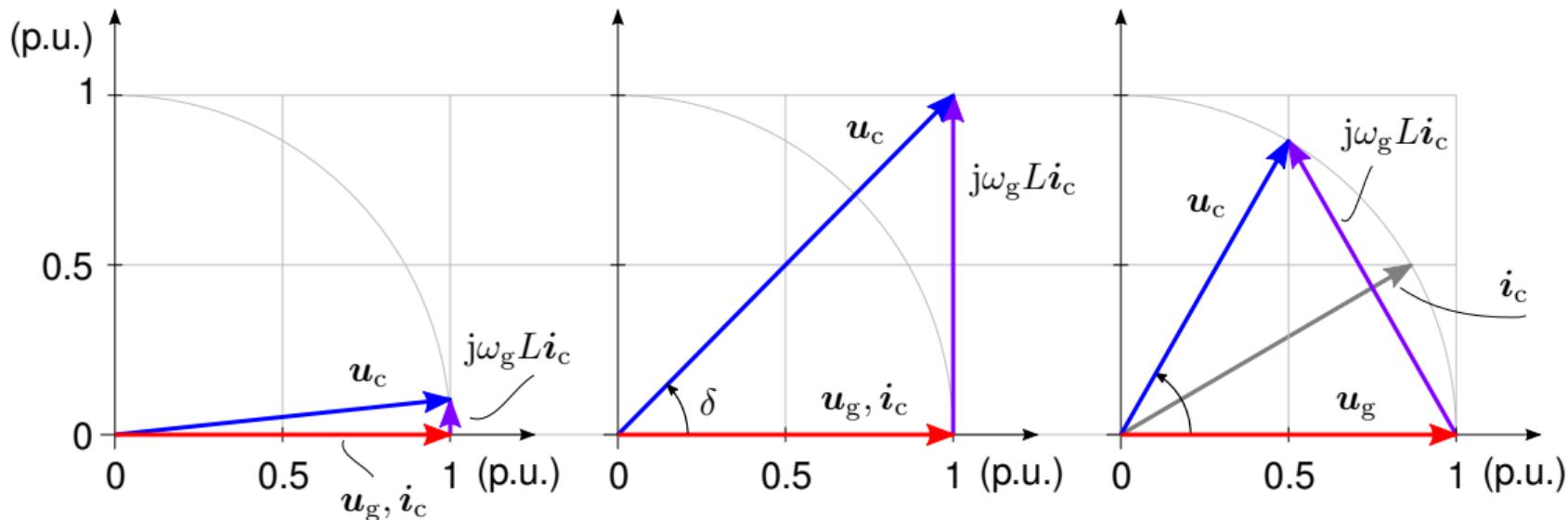

Strong grid: $L = 0.1$ p.u.
 $\cos \varphi = 1, p_g = 1$ p.u.

Very weak grid: $L = 1$ p.u.
 $\cos \varphi = 1, p_g = 1$ p.u.

Very weak grid: $L = 1$ p.u.
 $|u_c| = 1$ p.u.

The converter current $|i_c| = 1$ p.u., the grid voltage $|u_g| = 1$ p.u., and the grid frequency $\omega_g = 1$ p.u. are assumed in all three example cases.

Observations

- ▶ Capability to feed active power to the grid reduces with the increasing grid inductance for the given voltage and current capacity
 - ▶ Case 1: $|\mathbf{u}_c| \approx 1.005$ p.u.
 - ▶ Case 2: $|\mathbf{u}_c| = \sqrt{2}$ p.u. ≈ 1.41 p.u., need for higher u_{dc} and voltage rating
 - ▶ Case 3: $|\mathbf{u}_c| = 1$ p.u. but the power $p_g = \sqrt{3}/2$ p.u. ≈ 0.87 p.u. is limited
- ▶ Maximum available converter voltage is $u_{c,max} = u_{dc}/\sqrt{3}$
- ▶ Short-circuit ratio (SCR) is the inverse of L in per units
 - ▶ Grid is considered weak if $SCR < 3$ (corresponding to $L > 0.33$ p.u.)
- ▶ Stability of the control system may also limit the maximum power in weak grids
- ▶ These considerations are approximately valid also for an LCL filter, which behaves as an L filter at lower frequencies

Power Angle Equation

PWM Voltage


LCL Filter

Inductor Size


Example of Experimental Results

PWM Voltage: Symmetrical Suboscillation Method (SVPWM)

Fundamental cycle

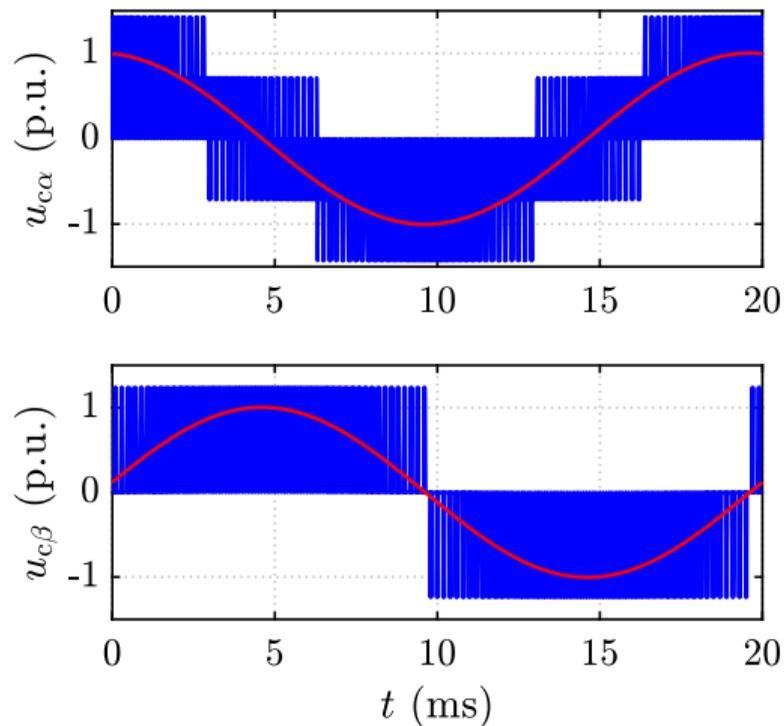

Zoomed waveforms

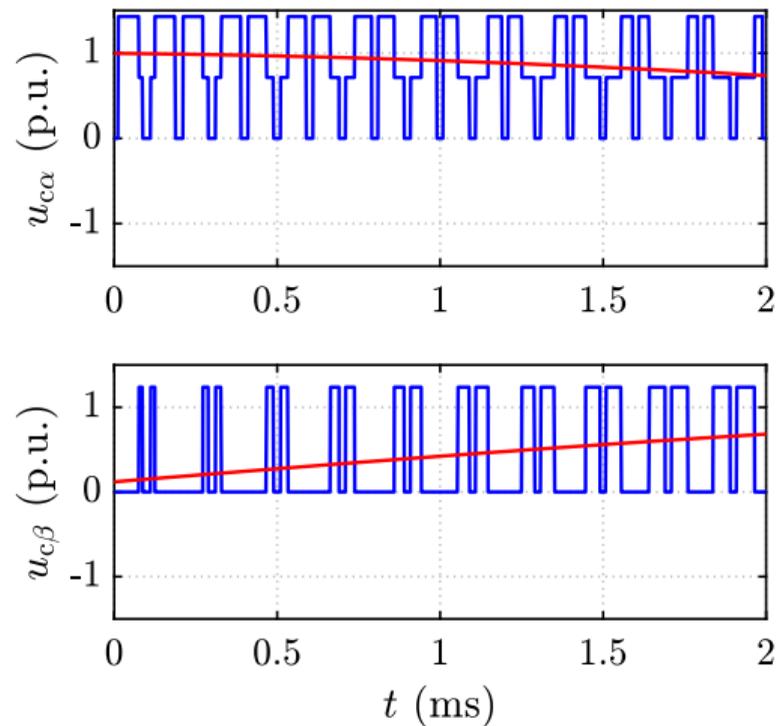



PWM Voltage Spectrum

Spectrum depends on

- ▶ Modulation method (SVPWM, DPWM, ...)
- ▶ Operating point (DC-bus voltage, AC voltage)
- ▶ Ratio between the switching frequency and the fundamental frequency
- ▶ Parasitic issues (inverter dead time, clock resolution, ...)

Spectrum can be determined, e.g., by means of the discrete Fourier transform

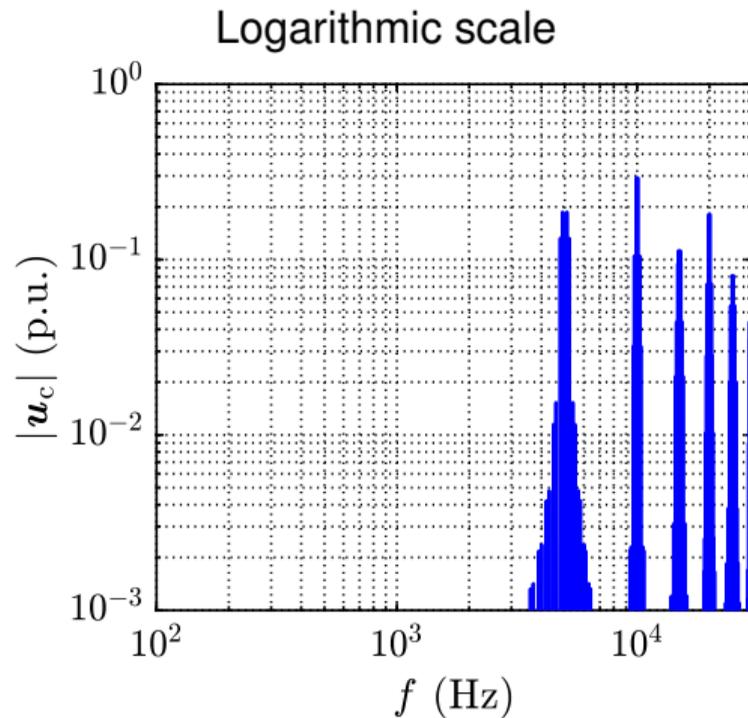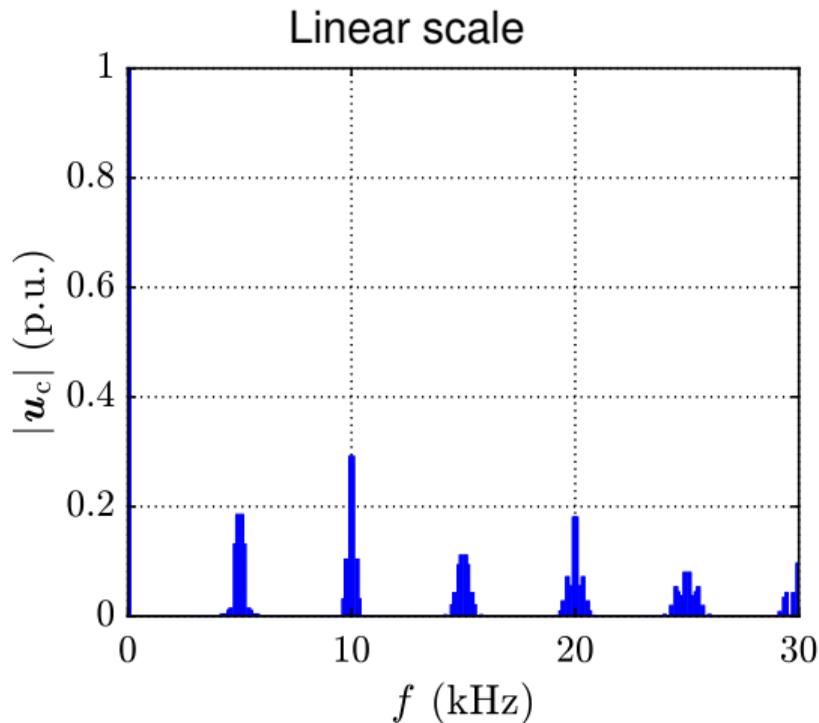- Fundamental frequency 50 Hz, switching frequency 5 kHz



Power Angle Equation

PWM Voltage


LCL Filter

Inductor Size

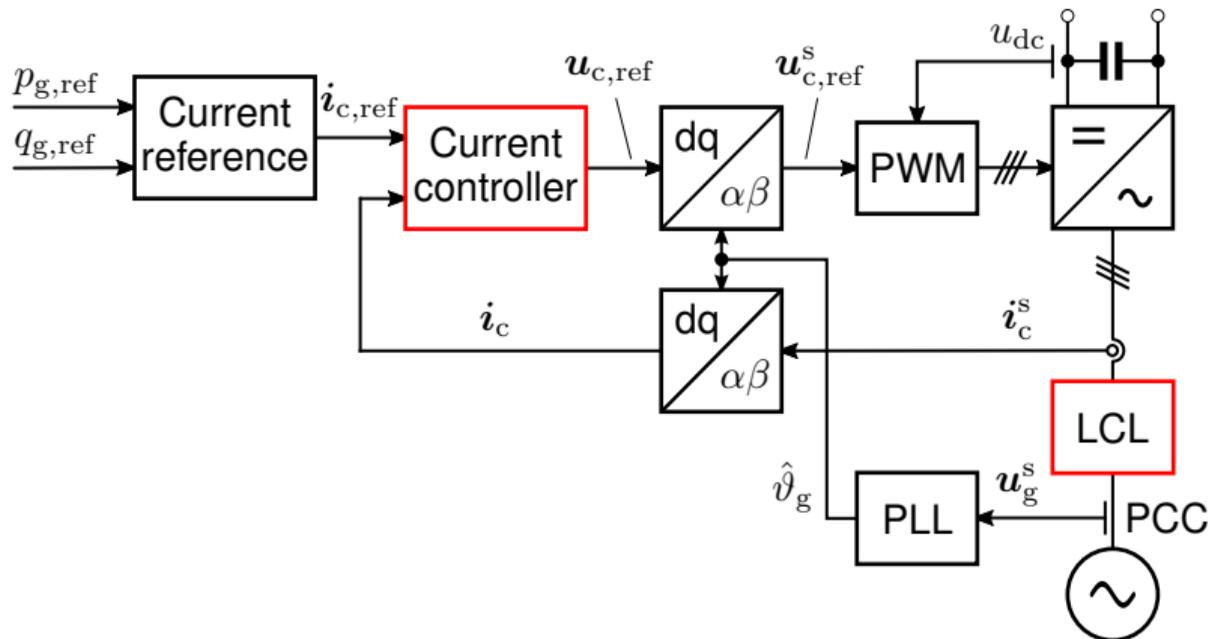Example of Experimental Results

LCL Filters are Commonly Used in Grid Converters

- ▶ Current controller has to damp the LCL resonance (unless damping resistors in the filter are used)
- ▶ Converter current or grid current is measured




LCL Filter: Space-Vector Model

- ▶ Model is presented in stator coordinates
- ▶ Superscript s is dropped to simplify notation
- ▶ Model can be easily transformed to synchronous coordinates

$$\frac{d}{dt} \leftarrow \frac{d}{dt} + j\omega_g \quad \text{in the time domain}$$

$$s \leftarrow s + j\omega_g \quad \text{in the Laplace domain}$$

- ▶ Parasitic losses are omitted

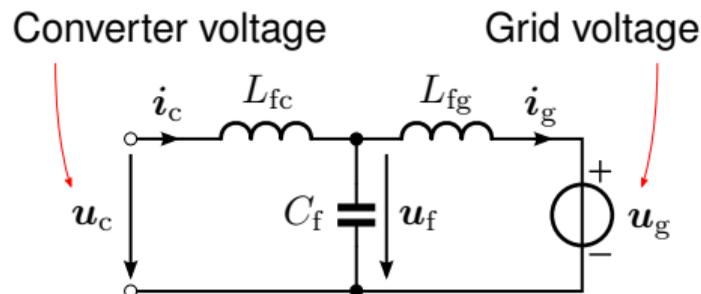

$$L_{fc} \frac{di_c}{dt} = u_c - u_f$$

$$C_f \frac{du_f}{dt} = i_c - i_g$$

$$L_{fg} \frac{di_g}{dt} = u_f - u_g$$

► State-space form

$$\frac{d}{dt} \underbrace{\begin{bmatrix} i_c \\ u_f \\ i_g \end{bmatrix}}_x = \underbrace{\begin{bmatrix} 0 & -1/L_{fc} & 0 \\ 1/C_f & 0 & -1/C_f \\ 0 & 1/L_{fg} & 0 \end{bmatrix}}_A \begin{bmatrix} i_c \\ u_f \\ i_g \end{bmatrix} + \underbrace{\begin{bmatrix} 1/L_{fc} \\ 0 \\ 0 \end{bmatrix}}_{B_c} u_c + \underbrace{\begin{bmatrix} 0 \\ 0 \\ -1/L_{fg} \end{bmatrix}}_{B_g} u_g$$

$$i_c = \underbrace{[1 \ 0 \ 0]}_{C_c} x \quad i_g = \underbrace{[0 \ 0 \ 1]}_{C_g} x$$

► Transfer functions can be expressed using system matrices, for example


$$\frac{i_c(s)}{u_c(s)} = Y_{cc}(s) = C_c(sI - A)^{-1}B_c \quad \frac{i_g(s)}{u_c(s)} = Y_{gc}(s) = C_g(sI - A)^{-1}B_c$$

Transfer Function from u_c to i_c

$$\frac{i_c(s)}{u_c(s)} = Y_{cc}(s) = \frac{1}{sL_{fc}} \frac{s^2 + \omega_z^2}{s^2 + \omega_p^2}$$

- Antiresonance frequency and resonance frequency
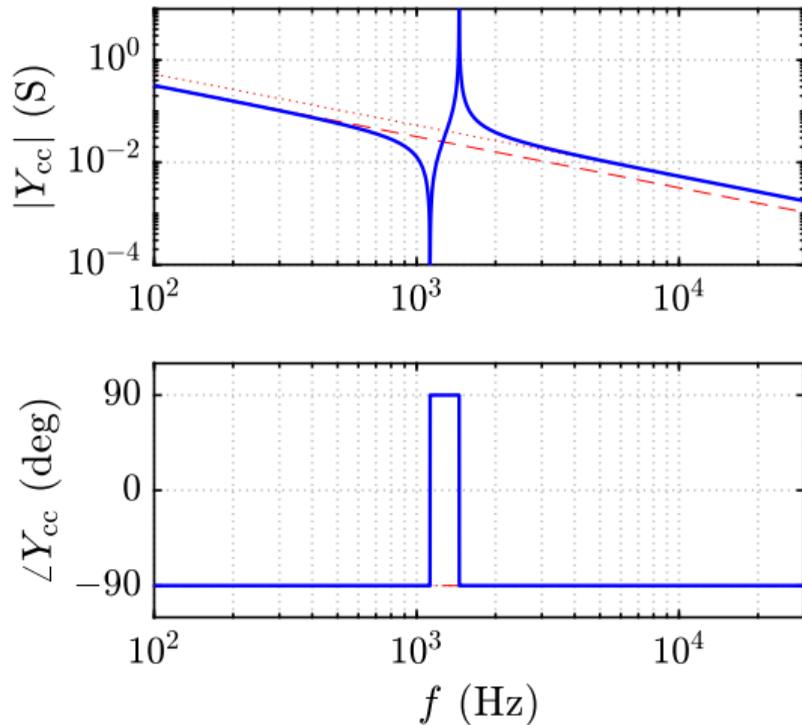
$$\omega_z = \sqrt{\frac{1}{L_{fg}C_f}} \quad \omega_p = \sqrt{\frac{L_{fc} + L_{fg}}{L_{fc}L_{fg}C_f}}$$



Transfer Function from u_c to i_g

$$\frac{i_g(s)}{u_c(s)} = Y_{gc}(s) = \frac{1}{sL_{fc}} \frac{\omega_z^2}{s^2 + \omega_p^2}$$

- Parameters in these examples



$$L_{fc} = 3 \text{ mH} \quad C_f = 10 \text{ } \mu\text{F} \quad L_{fg} = 2 \text{ mH}$$

- Resonance frequencies

$$f_z = \omega_z / (2\pi) = 1.13 \text{ kHz}$$

$$f_p = \omega_p / (2\pi) = 1.45 \text{ kHz}$$

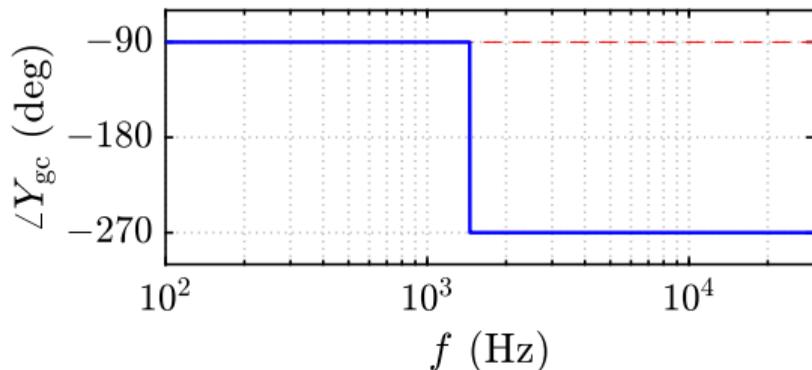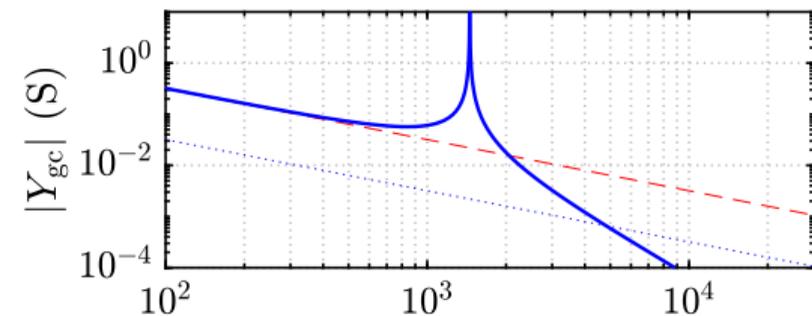- Red dashed line: inductor $L_{fc} + L_{fg}$
- Blue dotted line: $10(L_{fc} + L_{fg})$



Power Angle Equation

PWM Voltage

LCL Filter

Inductor Size

Example of Experimental Results

LCL Filter vs. L Filter

- ▶ Harmonics of the grid current at the PCC should meet the grid code or standard requirements (e.g. THD < 5%)
- ▶ Compare $|Y_{gc}|$ of an LCL filter at 5 kHz to the inductor $10(L_{fc} + L_{fg})$
- ▶ For the same attenuation, the total inductance of the LCL filter can be made much smaller than the pure inductance of the L filter
- ▶ How the inductance value is related to the physical size of the inductor?^{1,2}

¹Kazimierczuk, *High-frequency magnetic components*. Wiley, 2013.

²Koppinen, Rahman, and Hinkkanen, "Effects of the switching frequency of a grid converter on the LCL filter design," in *Proc. IET PEMD*, 2016.

Measure for an Inductor Size: Area Product


- ▶ Stored energy of the inductor

$$W_L = \frac{1}{2}Li^2 = \frac{1}{2}\psi i = \frac{1}{2}(NBA_c)(K_u J A_w / N)$$

- ▶ B is the peak value of the core flux density [T]
(depends on the core material)
- ▶ J is the peak value of the current density [A/m²]
(depends on the cooling)
- ▶ K_u is the window utilization factor
- ▶ For given maximum current i , the inductance is proportional to the area product $A_w A_c$ [m⁴]

$$L = \frac{K_u J B}{i^2} A_w A_c$$

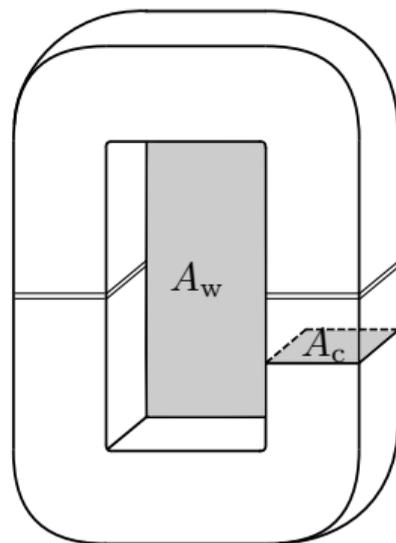- ▶ Required L depends on the switching frequency



Power Angle Equation

PWM Voltage


LCL Filter

Inductor Size


Example of Experimental Results

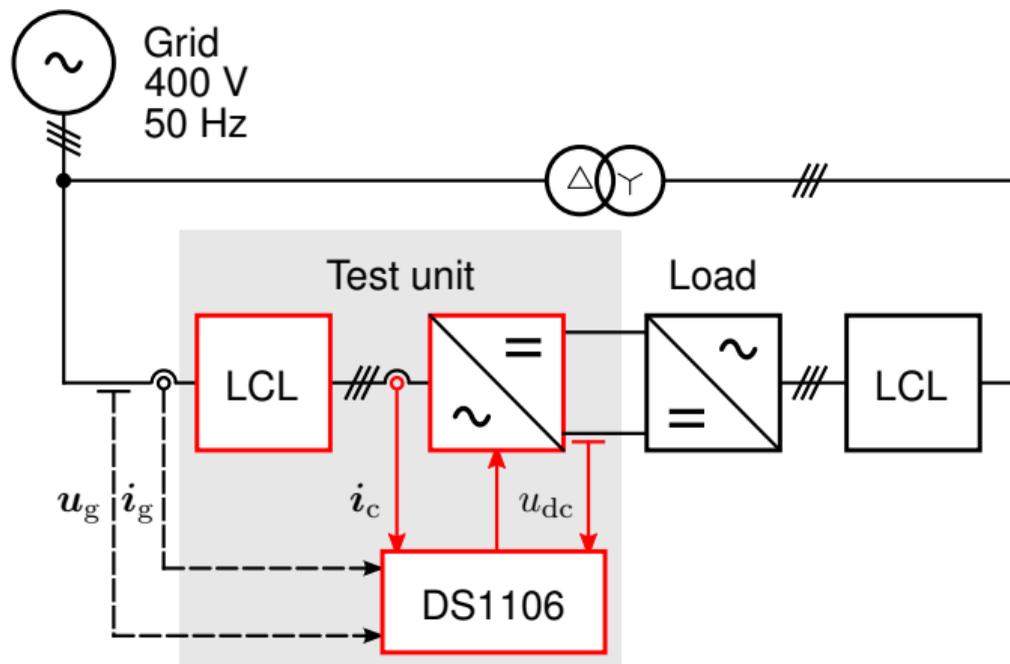Example of Experimental Results

- ▶ 12.5-kVA test converter
- ▶ Switching frequency $f_{sw} = 4$ kHz
- ▶ Filter resonance frequency: $f_p = 1.5$ kHz



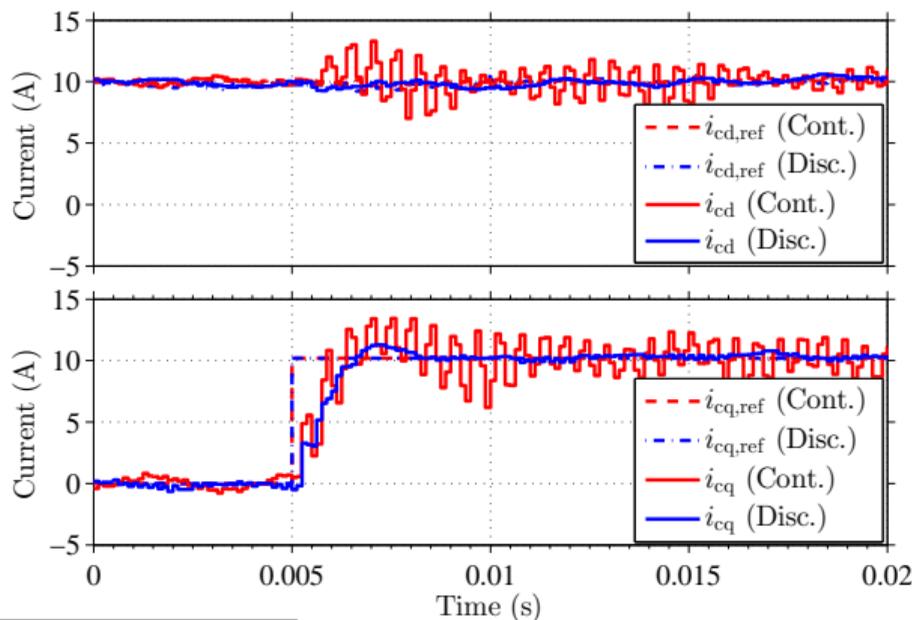- ▶ Low ratio f_{sw}/f_p makes control more difficult
- ▶ Digital delays can be effectively taken into account in the discrete-time design
- ▶ Two state-feedback controllers (same feedback signals and design specs):
continuous-time design with the Tustin method vs. direct discrete-time design³



³Kukkola, Hinkkanen, and Zenger, "Observer-based state-space current controller for a grid converter equipped with an LCL filter: Analytical method for direct discrete-time design," *IEEE Trans. Ind. Appl.*, 2015.