

ELEC-E3530


ELEC-E3530

Integrated Analog Systems L2

SC-integrators

SC-integrators

Forward Euler SC integrator

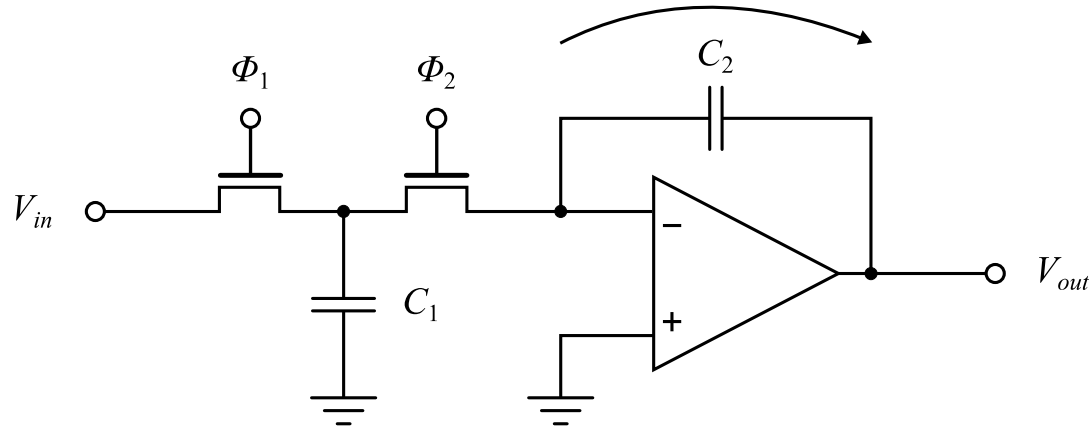

Charge equations:

$$\begin{aligned} \text{phase } \phi_1 : t = t_n : \quad \Delta Q_1(t_n) &= C_1 v_{in}(t_n) \\ \text{phase } \phi_2 : t = t_n + \frac{T}{2} \quad \Delta Q_2\left(t_n + \frac{T}{2}\right) &= C_1 v_{in}(t_n) \\ Q_1 &\rightarrow 0 \end{aligned}$$

Voltage change in C_2

$$\Rightarrow \Delta V_{C_2} = \frac{\Delta Q_2}{C_2} = \frac{C_1}{C_2} v_{in}(t_n)$$

New output voltage value for the next clockcycle:

$$v_{out}(t_n + 1) = -\Delta V_{C_2} + v_{out}(t_n) = v_{out}(t_n) - \frac{C_1}{C_2} v_{in}(t_n)$$

Apply z-transformation

$$\begin{aligned} V_{out}(z)z &= V_{out}(z) - \frac{C_1}{C_2} V_{in}(z) \\ V_{out}(z) &= -\frac{C_1}{C_2} \cdot \frac{1}{z-1} V_{in}(z) \triangleq \underline{-\frac{C_1}{C_2} \frac{z^{-1}}{1-z^{-1}} V_{in}(z)} \end{aligned}$$

Transfer function in z-domain:

$$H(z) = -\frac{C_1}{C_2} \frac{z^{-1}}{1-z^{-1}}$$

Forward Euler transformation!

Analyze frequency distortion:

insert $z=e^{j\omega T}$

$$H(e^{j\omega T}) = -\frac{C_1}{C_2} \frac{1}{e^{j\omega T} - 1} = -\frac{C_1}{C_2} \frac{1}{j\omega T - \omega^2 \frac{T^2}{2} \dots}$$

assume $\omega \ll \frac{1}{T}$

$$\Rightarrow H(e^{j\omega T}) \approx -\frac{C_1}{C_2 T} \frac{1}{j\omega} \Rightarrow$$

SC integrator time - constant :

$$\tau = \frac{C_2 T}{C_1} \triangleq \frac{C_2}{f_{clk} C_1}$$

RC integrator

$$H_{RC}(j\omega) \approx -\frac{1}{j\omega RC} \Rightarrow \underline{\tau = RC}$$

SC integrator time - constant depends on :


$$\tau : \text{a) } \propto \frac{C_2}{C_1}$$

$$\text{b) } \propto \frac{1}{f_{clk}}$$

$$1) \left. \begin{array}{l} \Delta \frac{C_2}{C_1} < 1\% \\ \Delta \frac{1}{f_{clk}} < 1\% \end{array} \right\} \Rightarrow \tau < 1\%$$

- 2) Time-constant does not depend on the capacitor absolute values.
 $\Rightarrow$ minimize the silicon area!

Backward Euler SC integrator

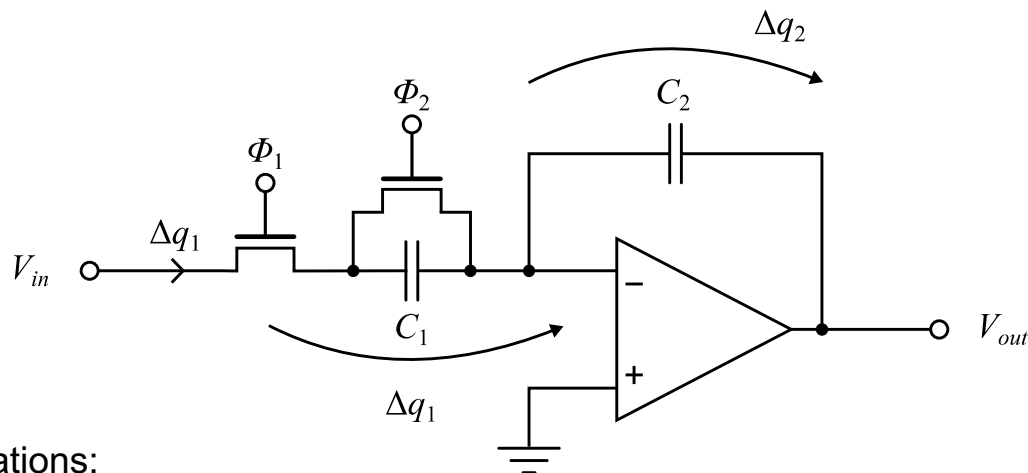

Charge equations:

phase ϕ_1 : $\Delta q_1(t) = C_1 v_{in}(t_n)$

$$\Delta q_2(t) = \Delta q_1(t_n)$$

phase ϕ_2 : $\Delta q_1 = 0$

Voltage change in C_2

$$\Rightarrow \Delta v_{C_2}(t) = \frac{\Delta q_2(t)}{C_2} = \frac{C_1}{C_2} v_{in}(t_n)$$

New output voltage

$$v_{out}(t_n) = v_{out}(t_n - 1) - \Delta V_{C_2}(t)$$

$$v_{out}(t_n) = v_{out}(t_n - 1) - \frac{C_1}{C_2} v_{in}(t_n)$$

Apply z-transformation:

$$V_{out}(z) = V_{out}(z)z^{-1} - \frac{C_1}{C_2} V_{in}(z)$$

Backward Euler transfer function

$$H(z) = \frac{V_{out}(z)}{V_{in}(z)} = -\frac{C_1}{C_2} \frac{1}{1 - z^{-1}}$$

Frequency response


insert $z = e^{j\omega T}$

$$\Rightarrow H(e^{j\omega T}) = \frac{-\frac{C_1}{C_2}}{1 - e^{-j\omega T}} = \frac{-\frac{C_1}{C_2}}{j\omega T + \frac{\omega^2 T^2}{2} + \dots}$$

Assume $\omega \ll f_{clk} \Rightarrow H(e^{j\omega T}) \approx -\frac{C_1}{C_2} \frac{1}{j\omega T}$

$$\Rightarrow \tau = \frac{TC_2}{C_1} \triangleq \frac{C_2}{C_1 f_{clk}}$$

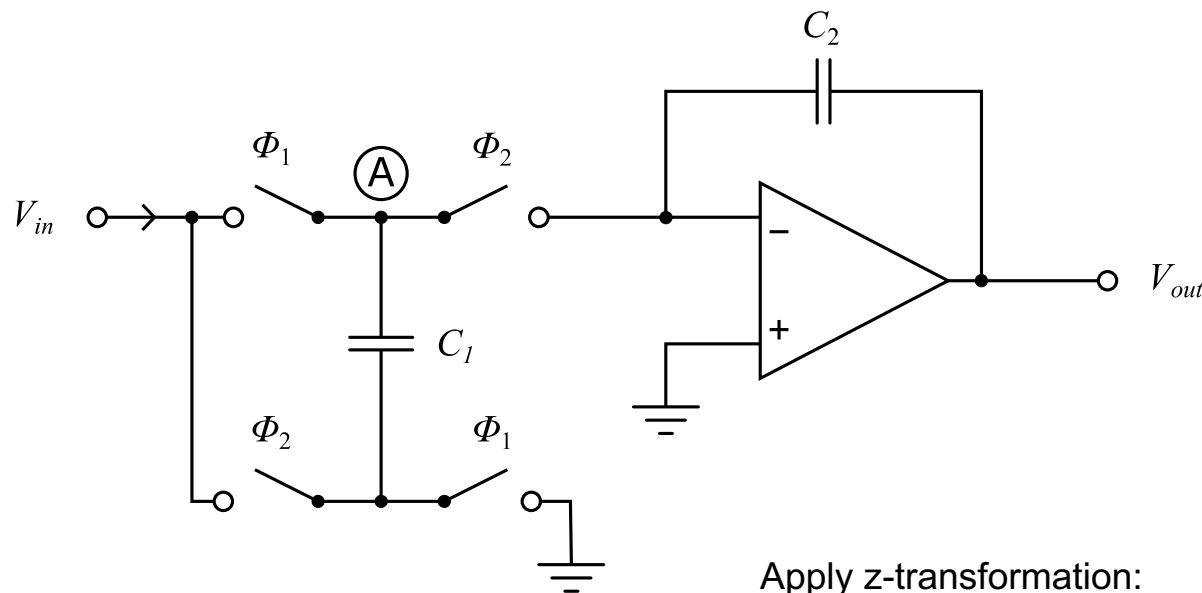SC integrator implementing bilinear transformation



Charge equations:

$$\text{phase } \phi_1: \Delta q_1(nT - T) = C_1 V_{in}(nT - T)$$

$$\text{phase } \phi_2: \Delta q_1(nT) = C_1 [-V_{in}(nT) - V_{in}(nT - T)]$$

$$\Delta q_2(nT) = \Delta q_1(nT)$$

Voltage change in C_2

$$\Rightarrow \Delta V_{C_2}(nT) = \frac{\Delta q_2(nT)}{C_2}$$

New output voltage :

$$V_{out}(nT) = V_{out}(nT - T) + \Delta V_{C_2}(nT)$$

$$V_{out}(nT) - V_{out}(nT - T) = -\frac{C_1}{C_2} [V_{in}(nT) + V_{in}(nT - T)]$$

Apply z-transformation:

$$V_{out}(z) - z^{-1}V_{out}(z) = -\frac{C_1}{C_2} V_{in}(z) + z^{-1}V_{in}(z)$$



$$(1 - z^{-1})V_{out}(z) = -\frac{C_1}{C_2} (1 + z^{-1})V_{in}(z)$$

Solve the transfer function:


$$H(z) = \frac{V_{out}(z)}{V_{in}(z)} = -\frac{C_1}{C_2} \frac{1 + z^{-1}}{1 - z^{-1}} = -\frac{C_1}{C_2} \frac{z + 1}{z - 1}$$

Bilinear transformation!

Parasitic capacitors in SC integrators

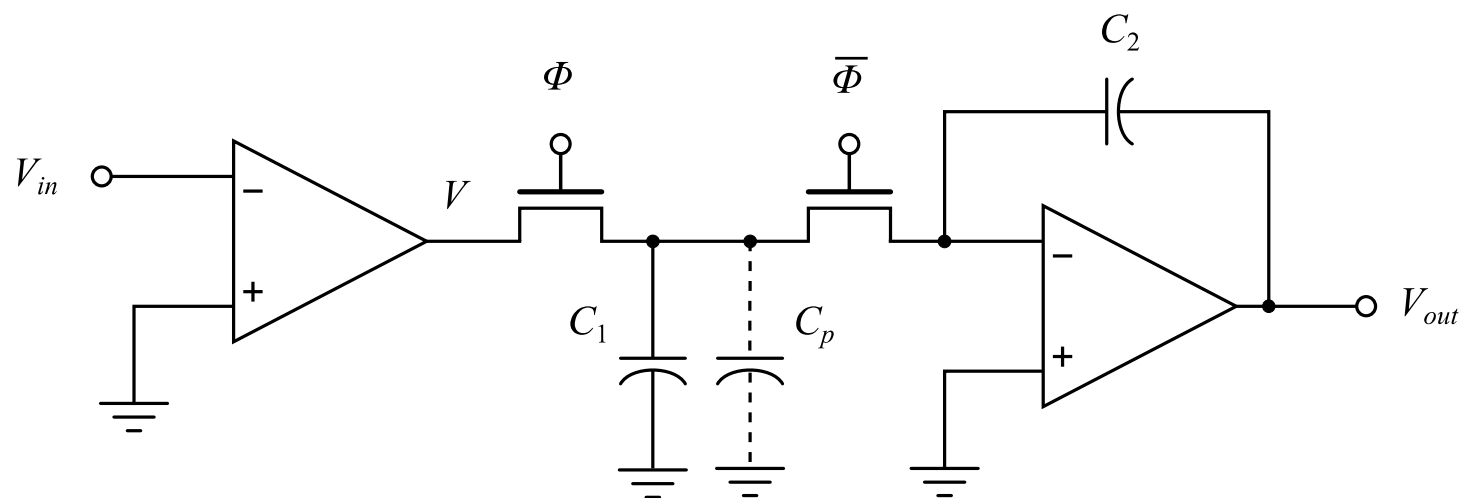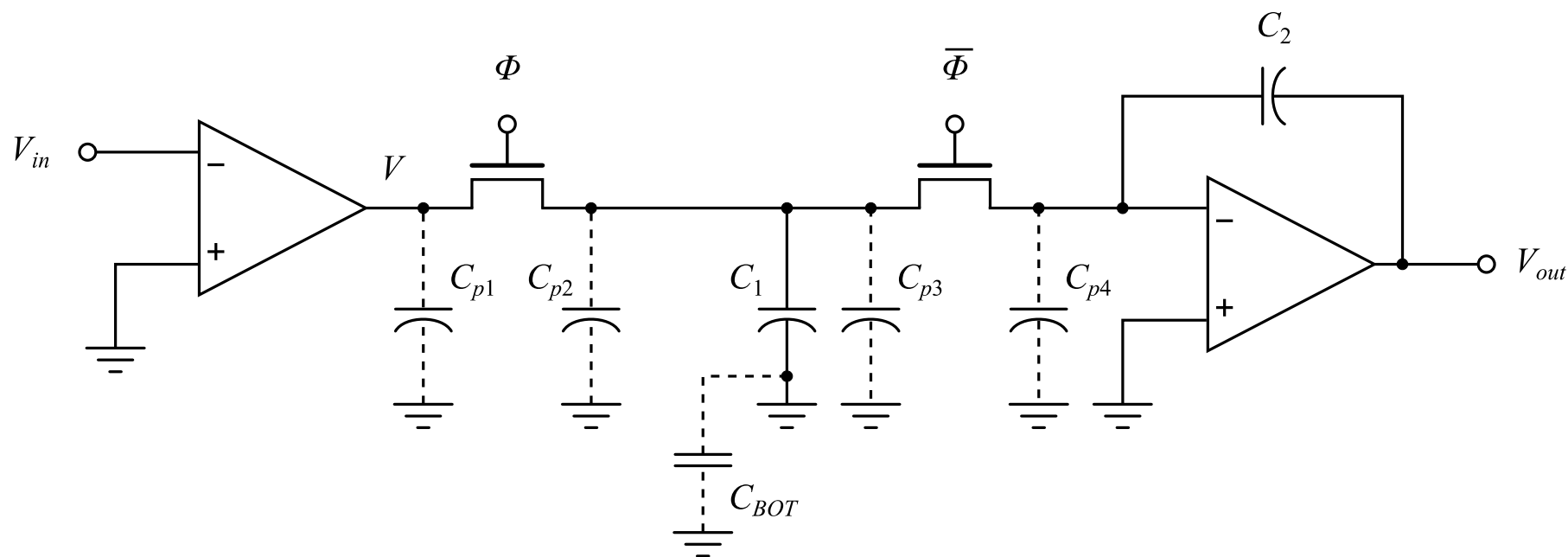

Switched capacitor filters

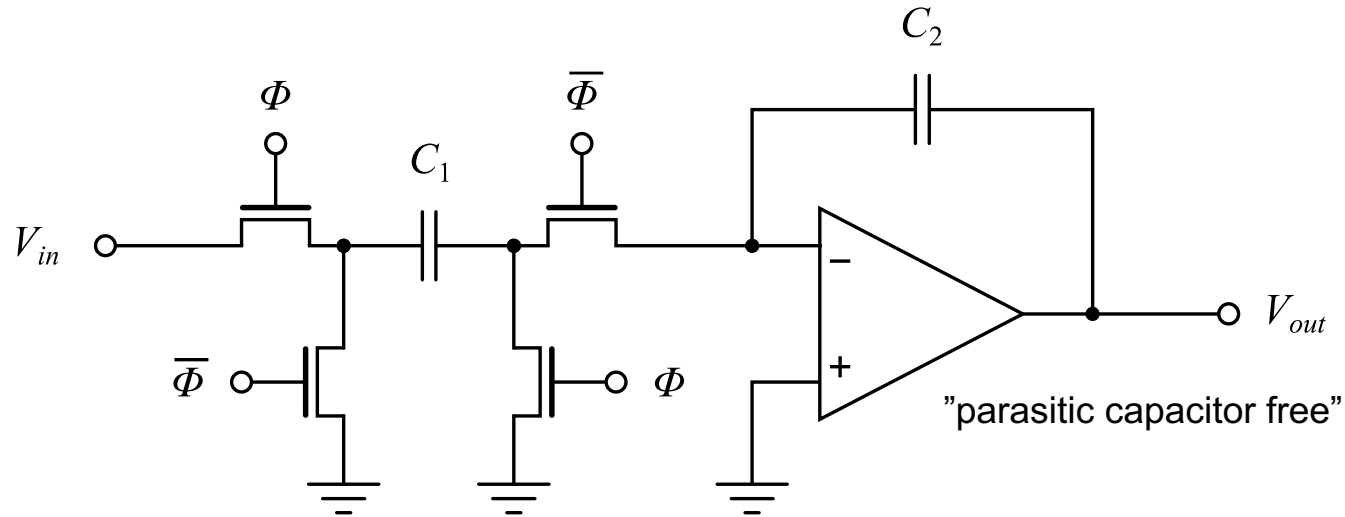

Charge equations:

phase Φ : $Q_1 = C_1 \cdot V_{in}(n-1) = Q_1(n-1)$

$Q_2 = C_2 \cdot V_{out}(n-1) = Q_2(n-1)$

phase $\bar{\Phi}$: $Q_1(n) = 0$

$Q_2(n) = Q_2(n-1) + \Delta Q_2 = C_2 V_{out}(n)$

charge $Q_1(n-1)$ transferred to C_2

$\Delta Q_2 = Q_1(n-1)$

$\Rightarrow Q_2(n) = Q_2(n-1) + Q_1(n-1)$

Insert charges $Q_1(n-1)$, $Q_2(n-1)$ and $Q_2(n)$

$$C_2 V_{out}(n) = C_2 V_{out}(n-1) + C_1 V_{in}(n-1)$$



Apply z-transformation to obtain z-plane transfer function

$$C_2 V_{out}(z) = C_2 z^{-1} V_{out}(z) + C_1 z^{-1} V_{in}(z)$$



$$\Rightarrow H(z) = \frac{V_{out}(z)}{V_{in}(z)} = \frac{z^{-1}}{1 - z^{-1}} \cdot \frac{C_1}{C_2}$$

This is a non-inverting integrator.

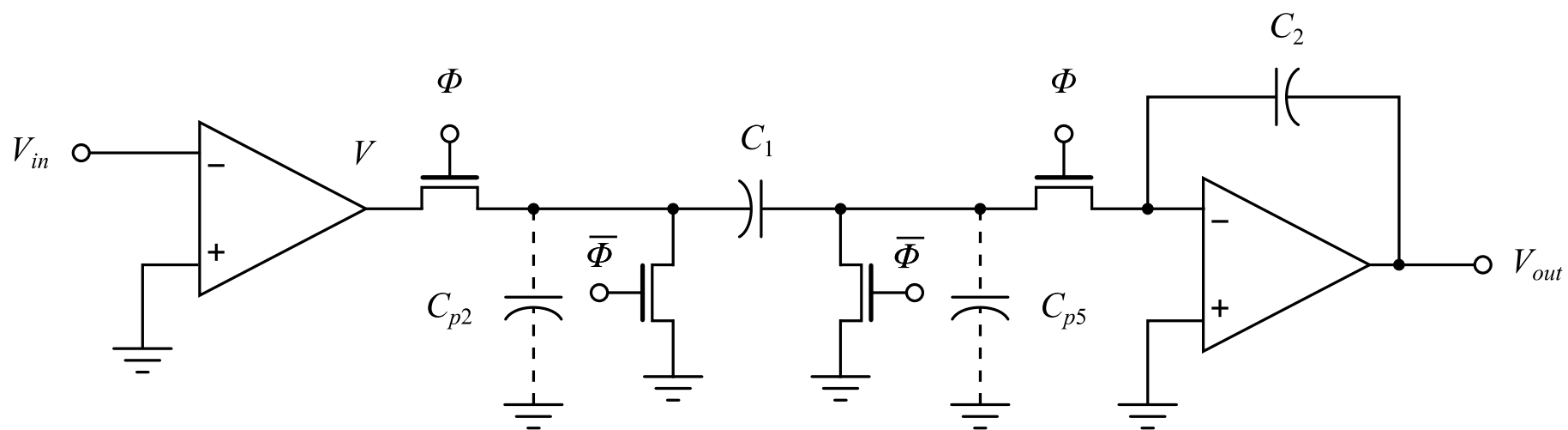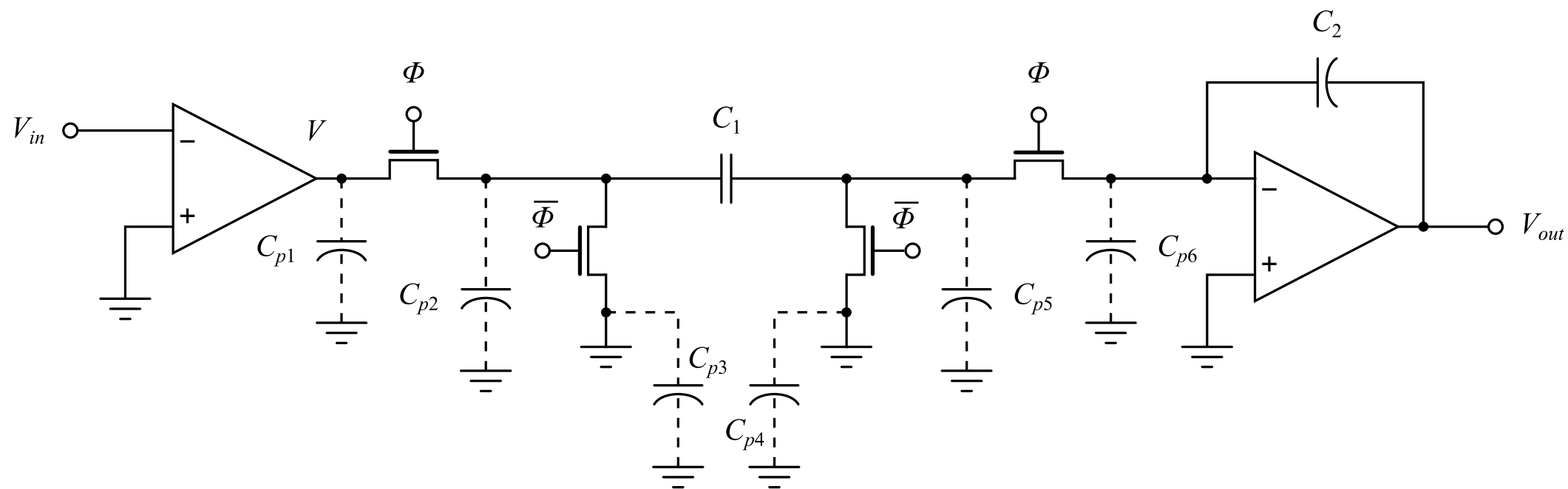Parasitic insensitive inverting SC integrator




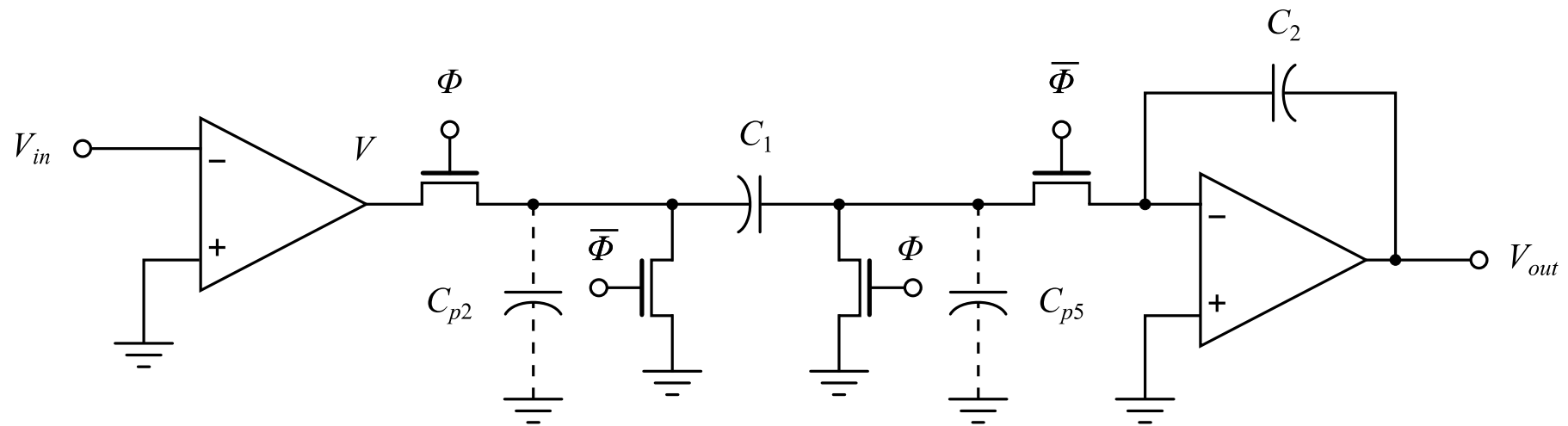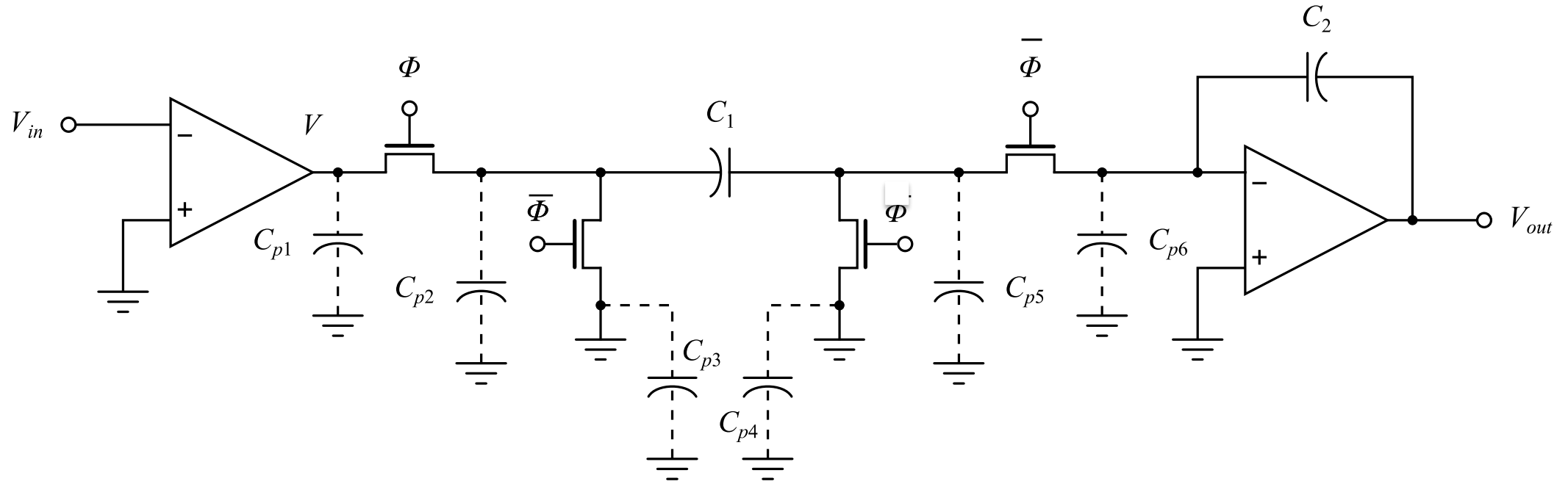Parasitic insensitive non-inverting SC integrator



Lossy SC integrators

Inverting

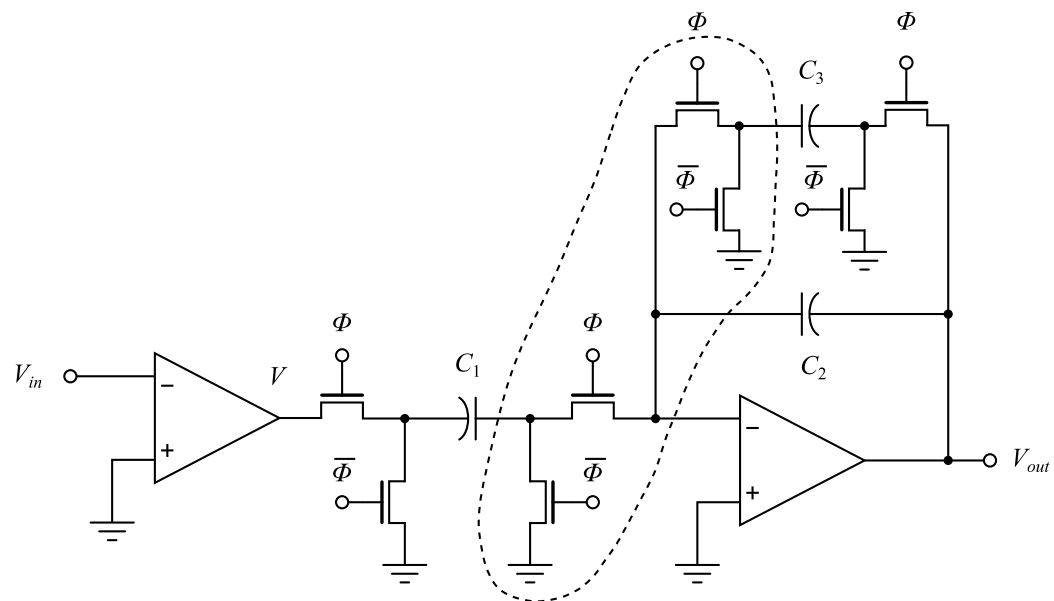

Non-Inverting

