

ELEC-E3530


Integrated Analog Systems L6

Continuous-time and current-mode filters

mode filters

Continuous-time and current-

RC-Integrator

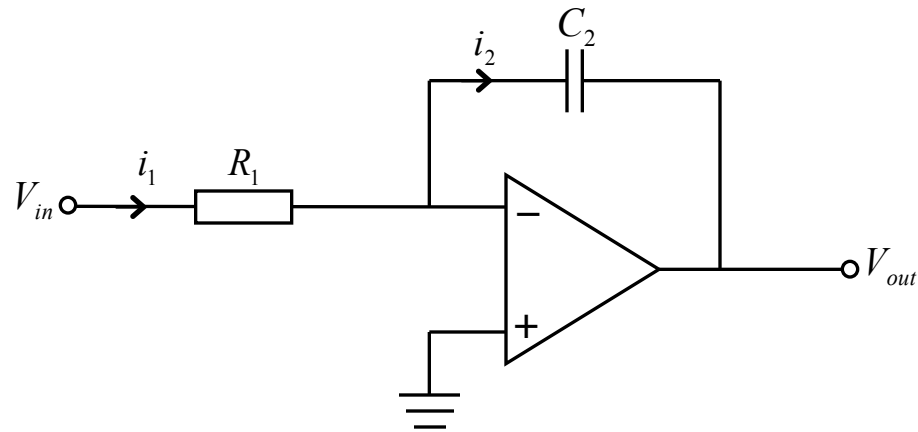

Current equations:

$$i_1 = \frac{V_{in}}{R_1}$$

$$i_2 = -C_2 \frac{dV_{out}}{dt}$$

$$i_1 = i_2$$

solve for V_{OUT}

$$\Rightarrow V_{OUT} = -\frac{1}{R_1 C_2} \int V_{in}(t) dt$$

Laplace-transformation


$$V_{out}(s) = \frac{-V_{in}(s)}{sR_1C_2}$$

$$H(s) = \frac{V_{out}}{V_{in}} = -\frac{1}{sR_1C_2}$$


Component Type	Range of Values	Relative Accuracy	Temperature Coefficient	Voltage Coefficient	Absolute Accuracy
Poly/poly capacitor	0.3 - 0.4 fF/ μ^2	0.06%	25 ppm/ $^{\circ}$ C	- 50 ppm/V	20%
MOS capacitor	0.35 - 0.5 fF/ μ^2	0.06%	25 ppm/ $^{\circ}$ C	- 20 ppm/V	10%
Diffused resistor	10 - 100 ohms/sq.	2% (5 μ m width)	1500 ppm/ $^{\circ}$ C	220 ppm/V	35%
Poly resistor	30 - 200 ohms/sq.	2% (5 μ m width)	1500 ppm/ $^{\circ}$ C	100 ppm/V	30%
Ion impl. resistor	0.5 - 2k ohms/sq.	1% (5 μ m width)	400 ppm/ $^{\circ}$ C	800 ppm/V	5%
p-well resistor	1 - 10k ohms/sq.	2%	8000 ppm/ $^{\circ}$ C	10k ppm/V	40%
pinch resistor	5 - 20k ohms/sq.	10%	10k ppm/ $^{\circ}$ C	20k ppm/V	50%

Variation of Filter Time Constants

untuned:

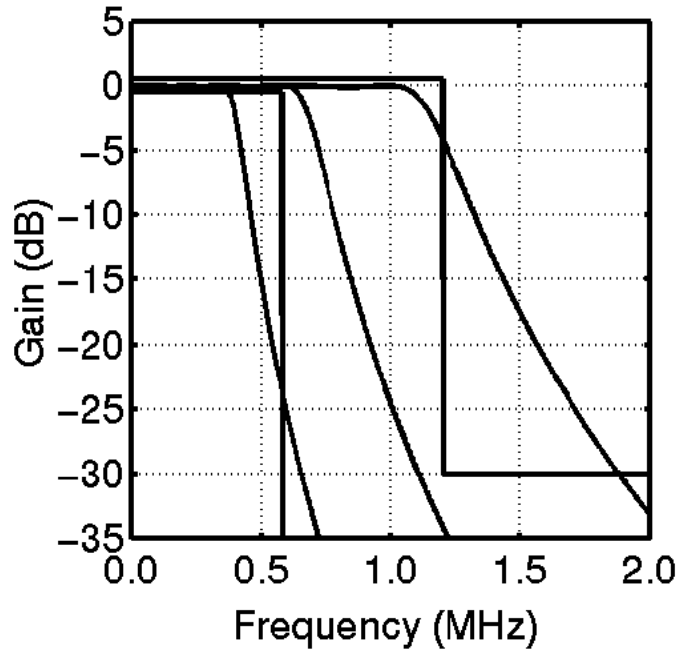


tuned:

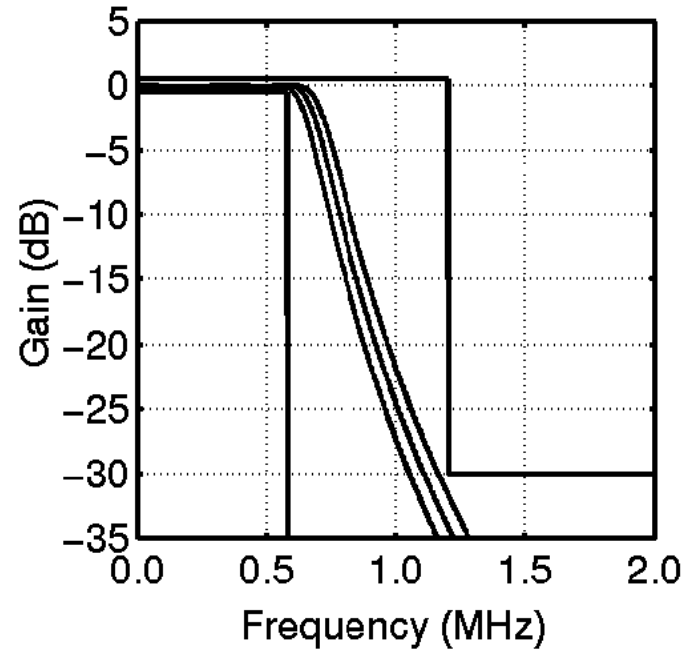

$$\frac{1}{1,7} \leq \frac{RC}{RC_{NOM}} \leq 1,7$$


Tuning accuracy $\pm 5\%$

Fourth-order leapfrog opamp-RC filter

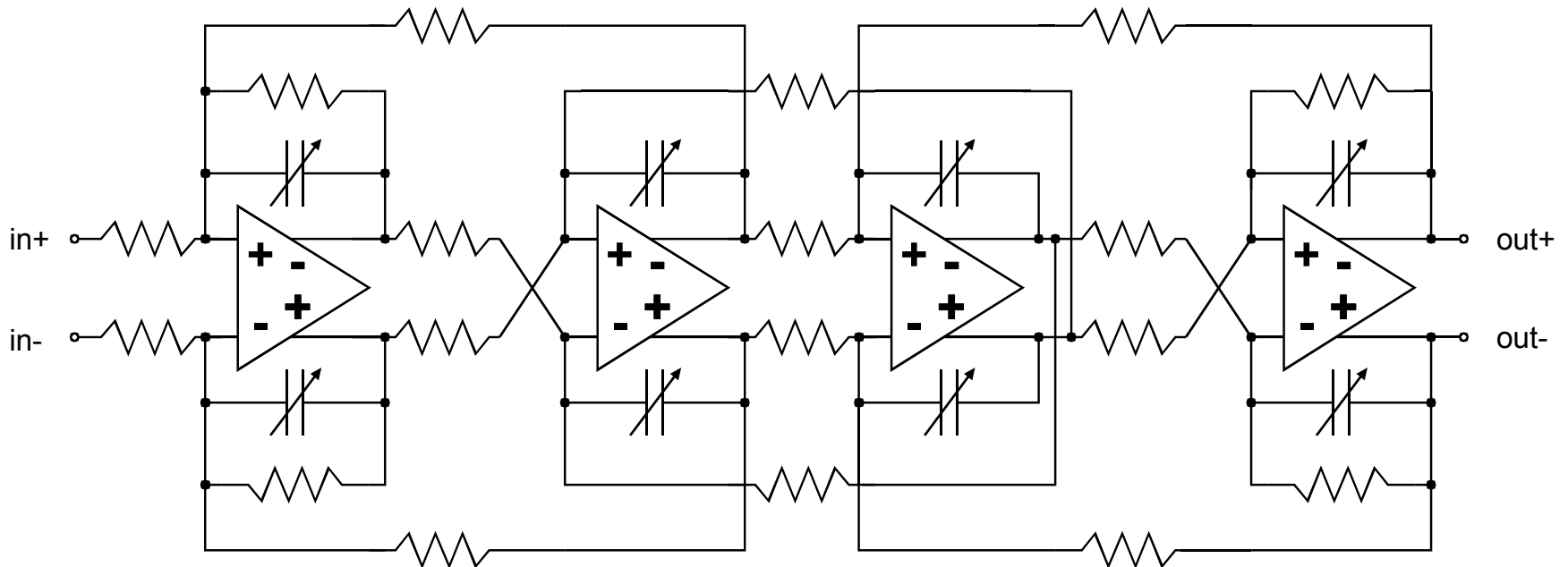


- tuning with switched capacitor matrix
- large area
- extra parasitic capacitors
- switch on-resistance does not affect directly the performance

Resistor tuning

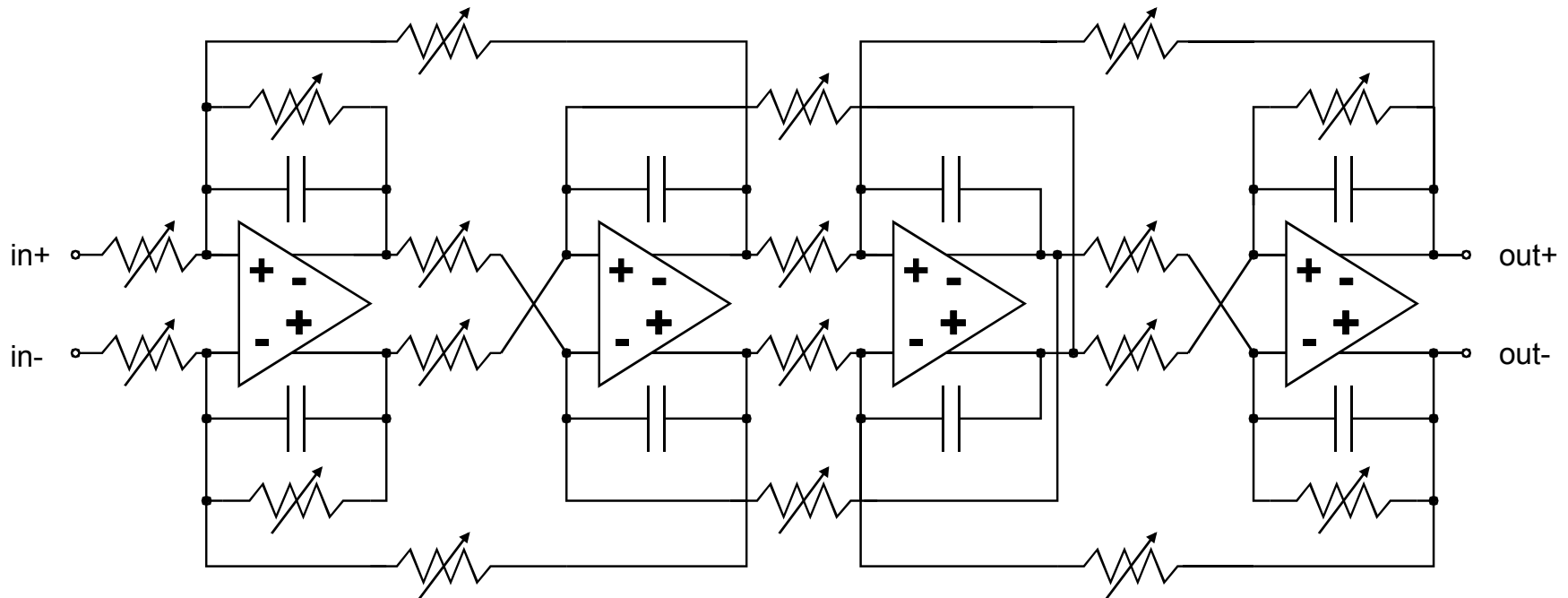


- series or parallel connection of resistors
- switch on-resistor affects the performance

Resistor tuning

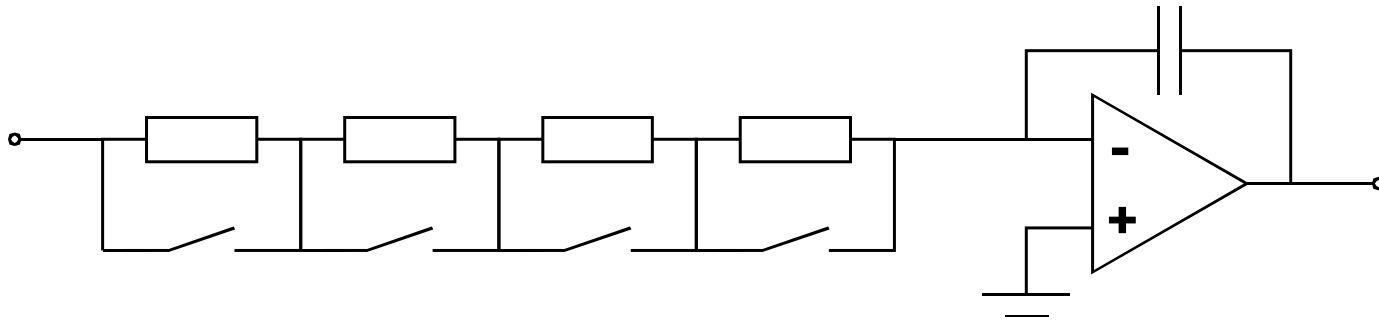

Switch on-resistance signal dependent:

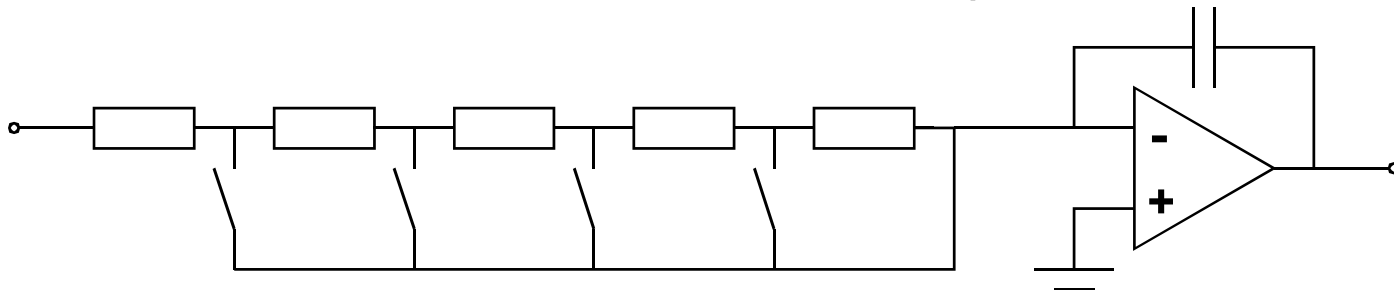
- multiple series on-resistors
- nonlinearity large
- temperature dependence
- process variations




Switch on-resistance not signal dependent:

- single on-resistor
- nonlinearity small
- temperature dependence
- process variations

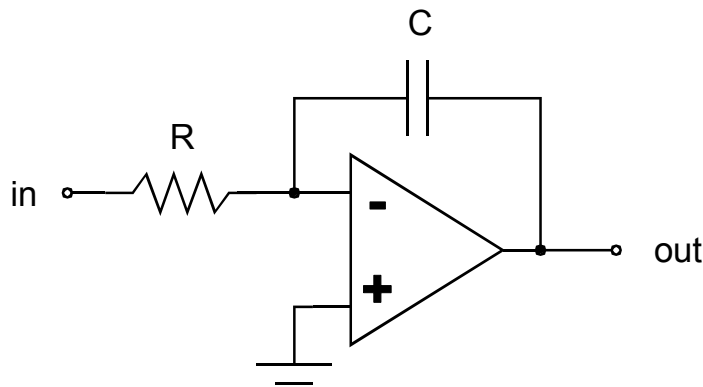Opamp-RC integrator time-constant tuning with a capacitor matrix




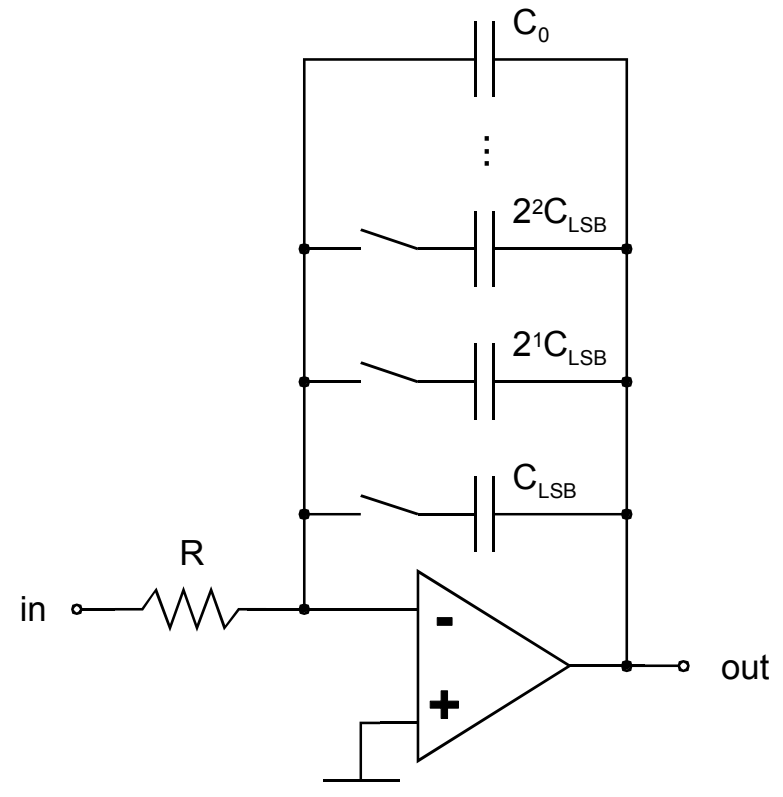time-constant $\tau=RC$
- R and C not matched
(process and temperature)
→ τ varies with factor of 2
for accurate filtering
→ tuning of RC-time constant needed




- tuning with programmable capacitor matrix
or with tunable resistors

Tuning with separate RC-integrator

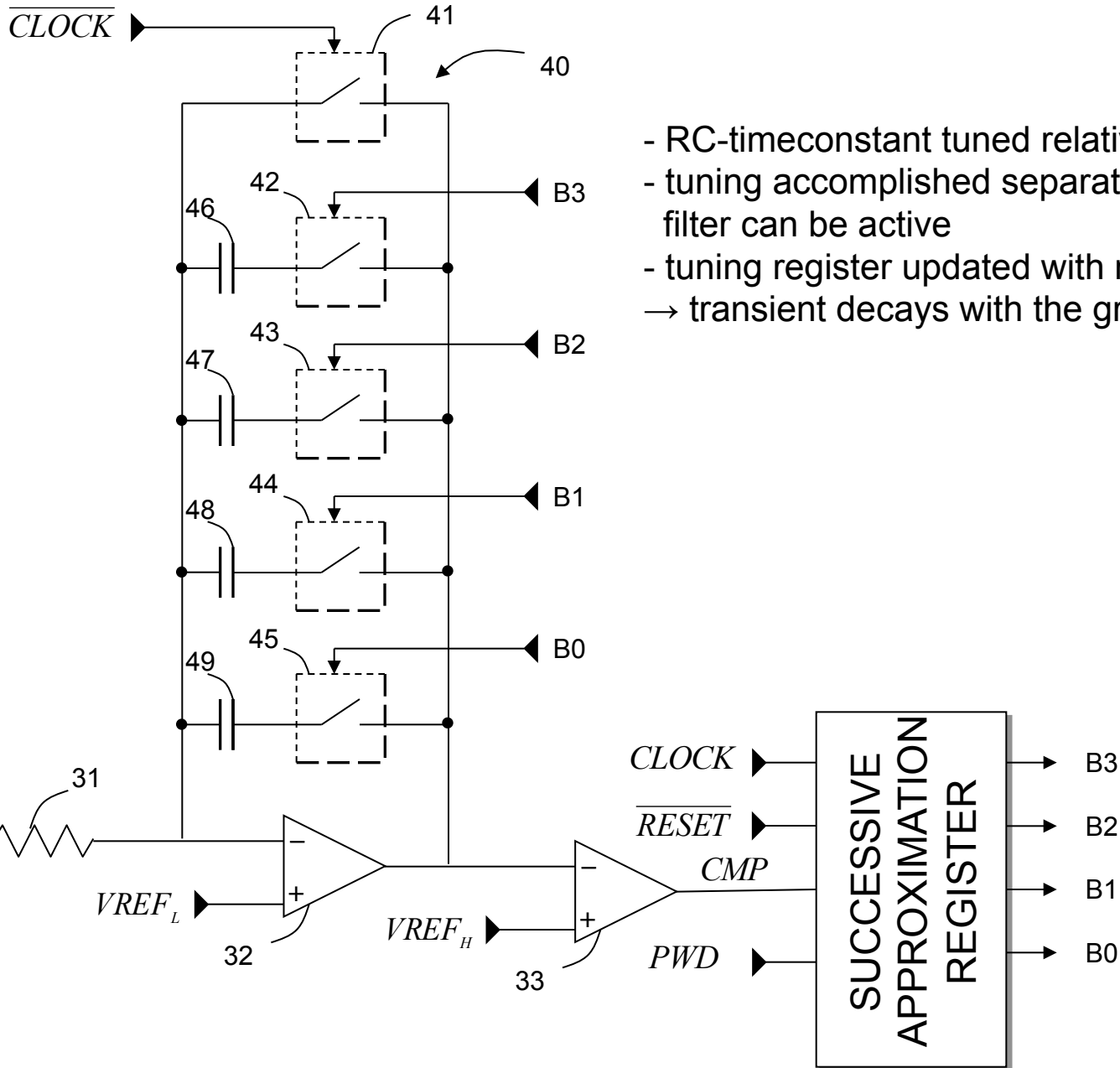

- RC-timeconstant tuned relative to an external clock
- tuning accomplished separately → filter can be active
- tuning register updated with new values → transient decays with the group delay of the filter



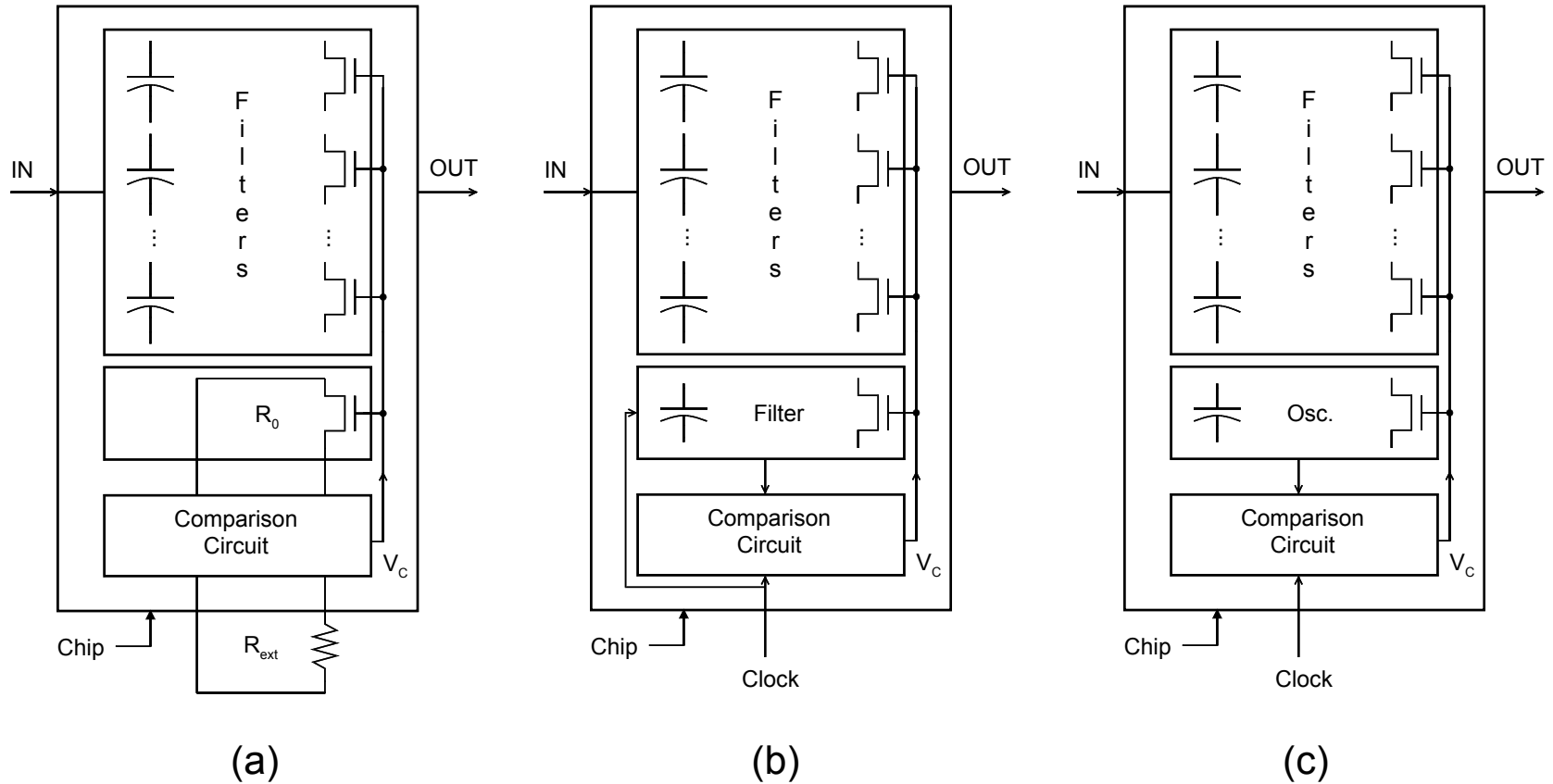
On-chip automatic indirect tuning schemes



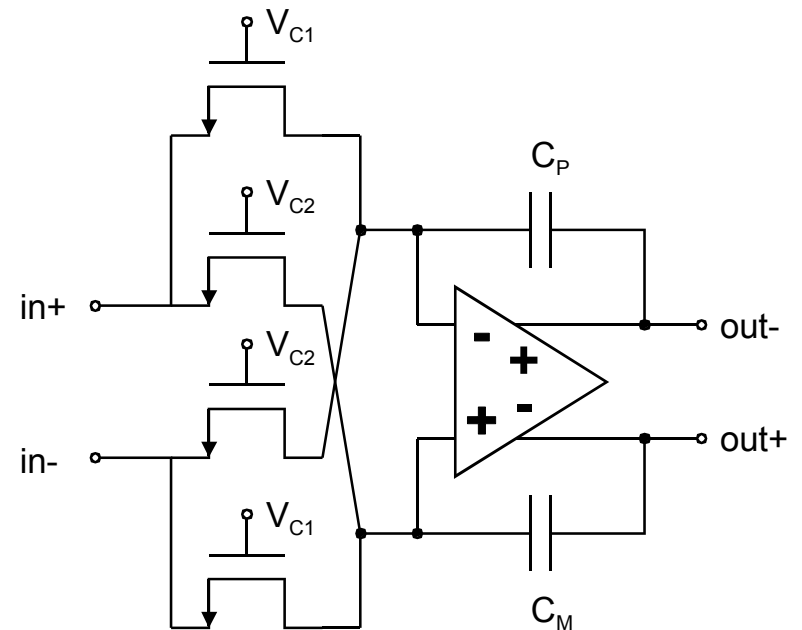
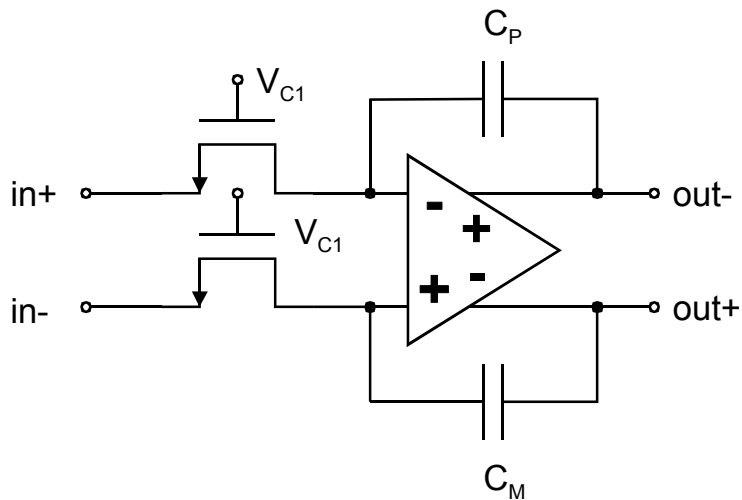
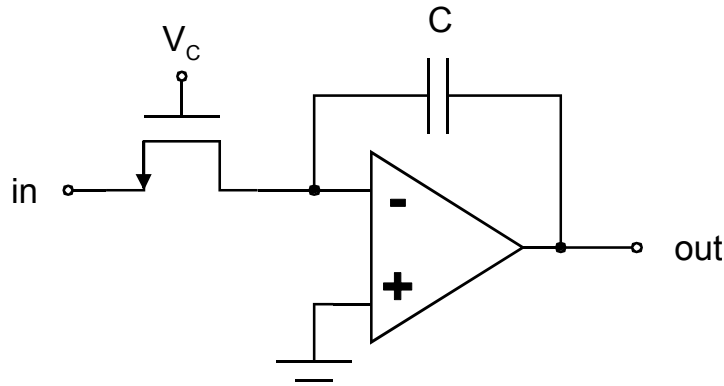
- a) external resistor as reference
- b) external clock and a tunable filter
- c) external clock and a voltage-controlled oscillator

MOSFET-C integrator

In a RC-integrator replace R with MOSFET biased into linear region:



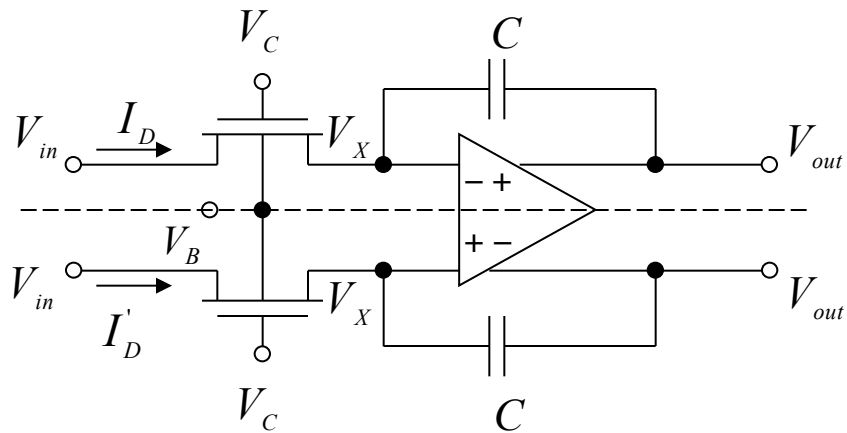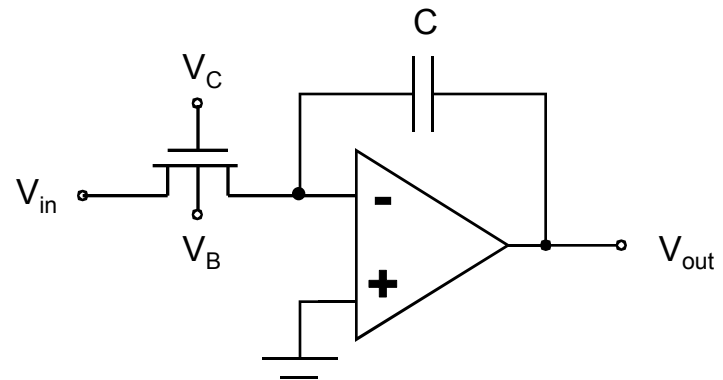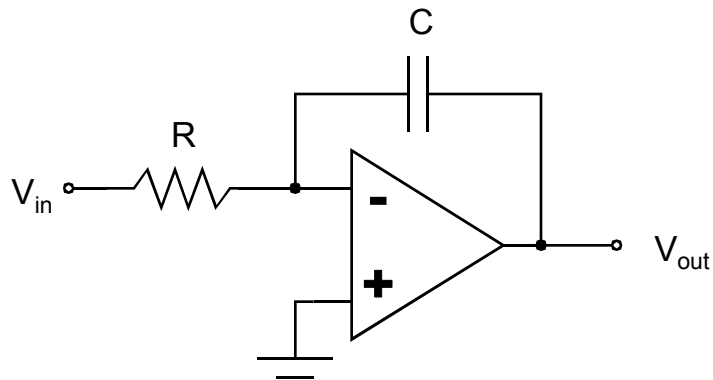Analysing the cancellation of even harmonics



$$V_{out}(t) = -\frac{1}{C} \int_{-\infty}^t I_D dt' + V_x \quad (5a)$$

$$-V_{out}(t) = -\frac{1}{C} \int_{-\infty}^t I'_D dt' + V_x \quad (5b)$$

The solution for V_{out} is obtained by subtracting (5b) from (5a):

$$V_{out}(t) = -\frac{1}{2C} \int_{-\infty}^t (I_D - I'_D) dt' \quad (6)$$

The values of the currents I_D and I'_D are given according to (2):

$$I_D = K \left\{ a_1 [V_{in} - V_x] + a_2 [V_{in}^2 - V_x^2] + a_3 [V_{in}^3 - V_x^3] + \dots \right\} \quad (7a)$$





$$I'_D = K \left\{ a_1 [(-V_{in}) - V_x] + a_2 [(-V_{in})^2 - V_x^2] + a_3 [(-V_{in})^3 - V_x^3] + \dots \right\} \quad (7b)$$

(7b) is subtracted from (7a), all the even order terms and all the terms in V_x cancel out:

$$I_D - I'_D = 2K \left[a_1 V_{in} + a_3 V_{in}^3 + a_5 V_{in}^5 + \dots \right] \quad (8)$$


$$V_{out}(t) \cong -\frac{1}{RC} \int_{-\infty}^t V_{in} dt' \quad (9)$$

Current mode filtering

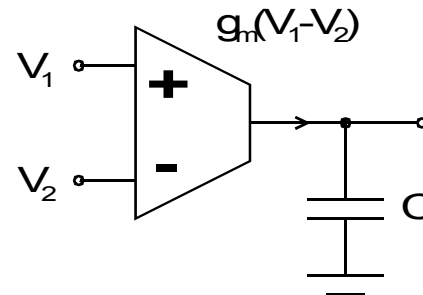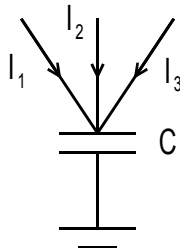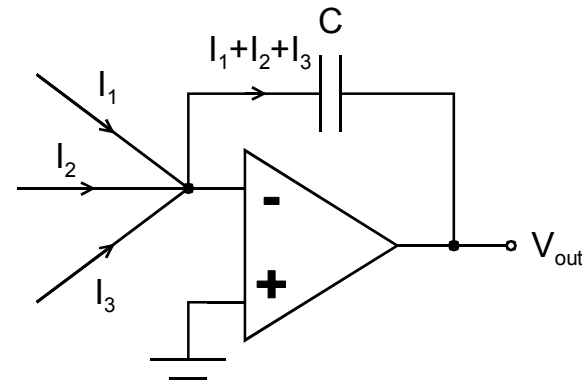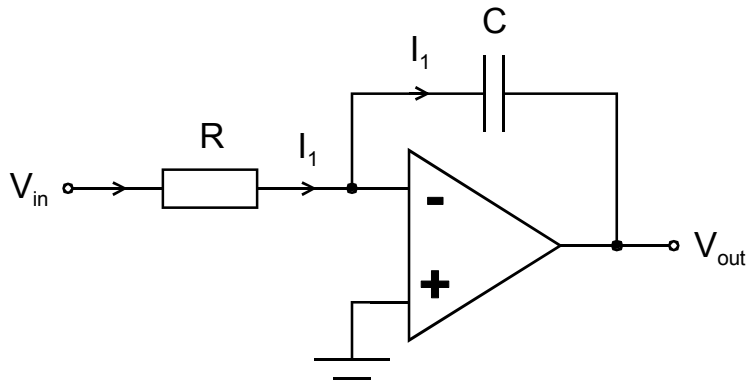

$$f_{GBW} \sim \frac{g_m}{C} \sim f_{3dB}$$

Band-pass filters

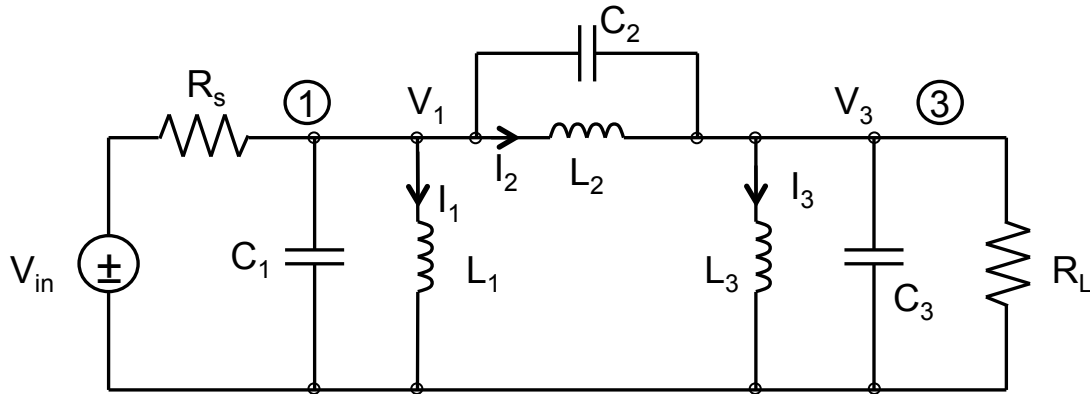

State equations:

$$-V_1 = \frac{-1}{s(C_1 + C_2)} \left[\frac{V_{in} - V_1}{R_s} + sC_2 V_3 - I^{(1)} \right],$$

$$-I^{(1)} = -(I_1 + I_2) = \frac{-1}{sL_{12}} \left[V_1 - \frac{L_1 V_3}{L_1 + L_2} \right],$$


$$V_3 = \frac{-1}{s(C_2 + C_3)} \left[-sC_2 V_1 - I^{(3)} + \frac{V_3}{R_L} \right],$$

$$-I^{(3)} = I_3 - I_2 = \frac{-1}{sL_{32}} \left[-V_3 + \frac{L_3 V_1}{L_3 + L_2} \right],$$


where $L_{12} = L_1 \parallel L_2 = \frac{L_1 L_2}{L_1 + L_2}$.

$$L_{32} = L_3 \parallel L_2$$


Signal flow-graph:

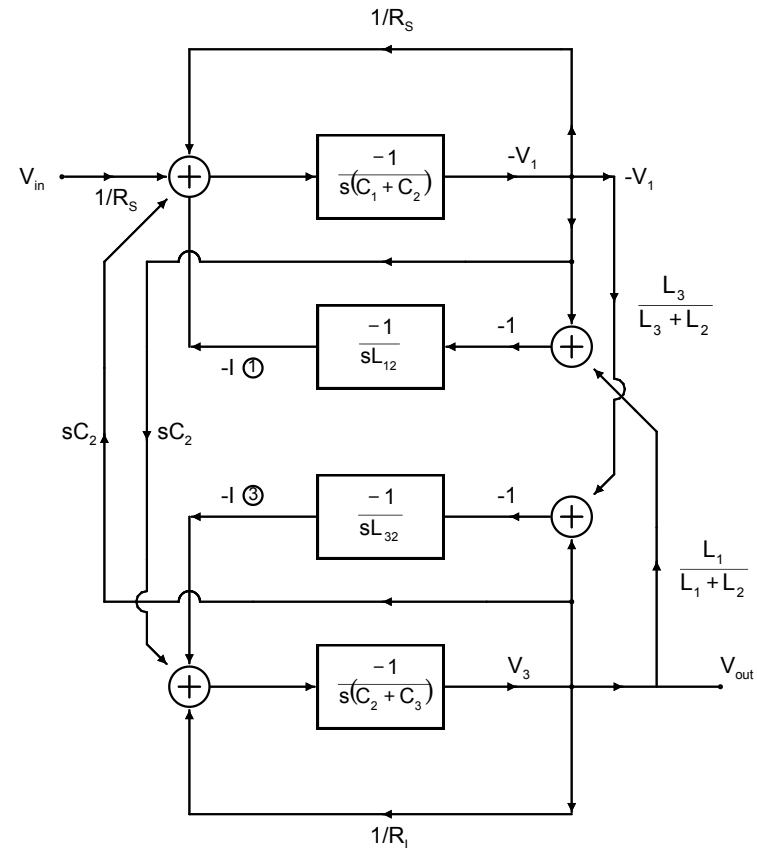

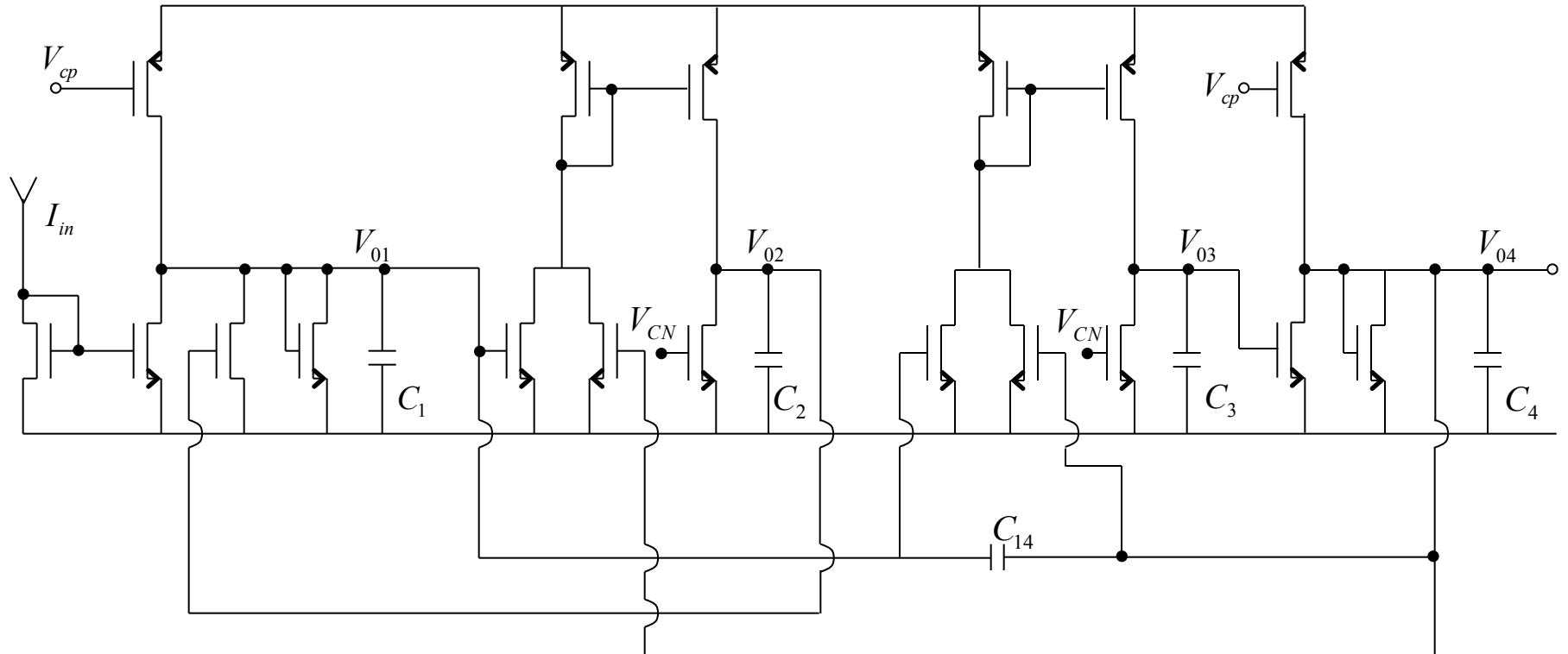Current mode implementation of bandpass filter



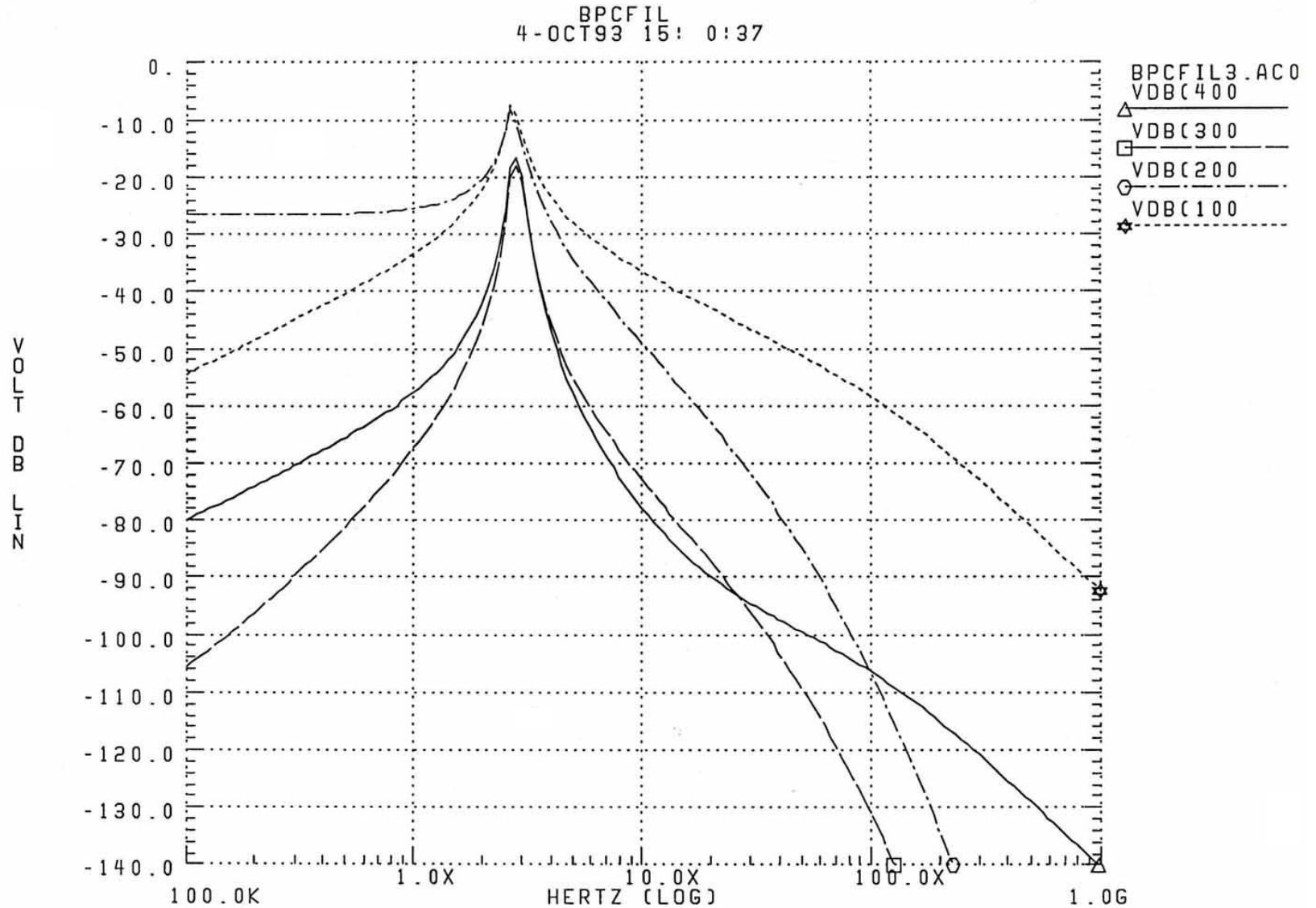Frequency response of current mode BB-filter



High frequency filtering

1) SC:

requirement for OPAMP

$$f_{GBW} \geq 5 \cdot f_{CLK} \geq 10 \cdot f_{3dB}$$

$$\Rightarrow f_{GBW} \geq 50 \cdot f_{3dB}$$

2) RC:

$$f_{GBW} \geq 10 \dots 20 f_{3dB}$$


3) g_m -C:

$$f_{3dB} = f_{GBW}$$

With same C and GBW

g_m C filter capable to 10...50 times higher frequencies than RC and SC filters

Synthesis of g_m -C filters

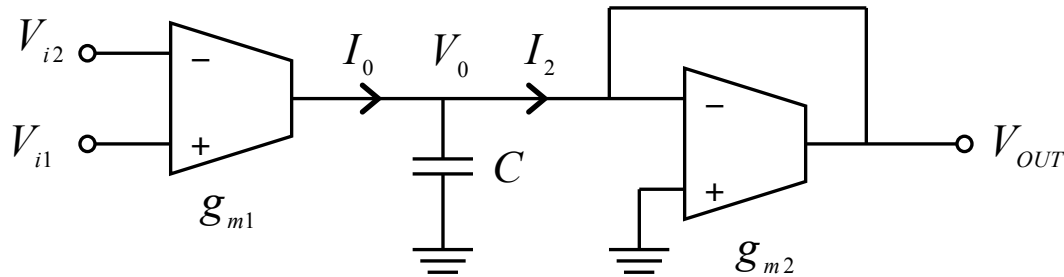

$$I_0 = g_{m1} (V_{i1} - V_{i2})$$

$$I_0 = I_C + I_2$$


$$I_2 = g_{m2} \cdot V_0$$

$$I_0 = sCV_0 + g_{m2} \cdot V_0$$

$$= g_{m1} (V_{i1} - V_{i2})$$

$$\Rightarrow \frac{V_0}{V_{i1} - V_{i2}} = \frac{g_{m1}}{g_{m2} + sC} = \frac{g_{m1}/g_{m2}}{1 + sC/g_{m2}}$$



Lossy integrator

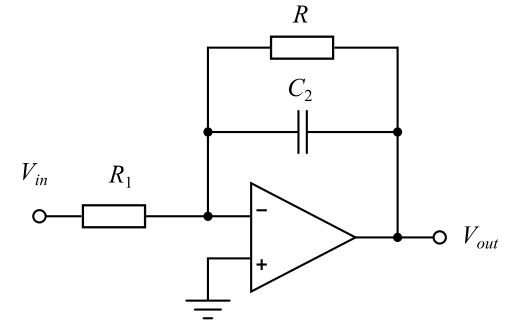

The transfer function of lossy RC integrator:

$$H(\omega) = -\frac{R}{R_1} \frac{1}{1 + j\omega C_2 R} = -\frac{1}{R_1 C_2} \frac{1}{j\omega - \frac{1}{RC_2}}$$

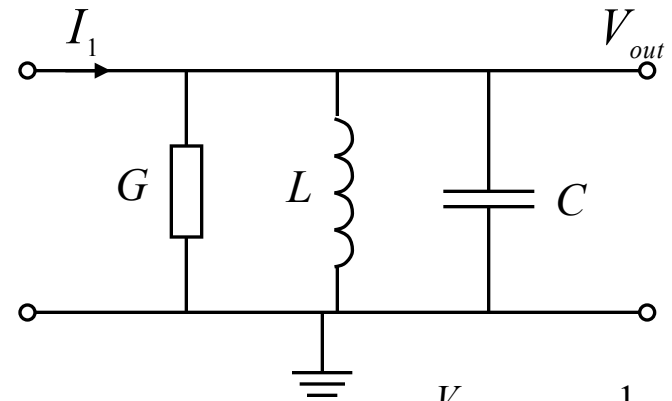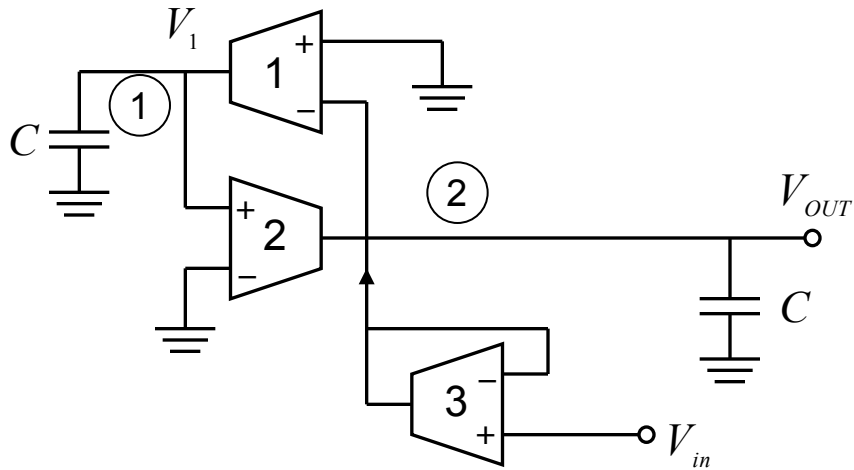g_m -C realization of RLC-resonance circuit



$$\frac{V_8}{I} = \frac{1}{SC + 1/SL + G}$$

$$= \frac{SL}{S^2LC + SLG + 1}$$

OTA currents:

$$I_1 = -g_{m1}V_{out}$$

$$I_2 = g_{m2}V_1$$

$$I_3 = g_{m3}(V_{in} - V_{out})$$

Current equations at nodes ① and ②

$$\textcircled{1} \quad I_1 = SCV_1$$

$$\textcircled{2} \quad I_3 + I_2 = SCV_{out}$$

Inserting currents:

$$\textcircled{1} \quad -g_{m1}V_{out} = SCV_1$$

$$\textcircled{2} \quad g_{m2}V_1 + g_{m3}(V_{in} - V_{out}) = SCV_{out}$$

$$I = g_{m3}V_{in}$$

$$G = g_{m3}$$


$$L = \frac{C}{g_{m1} \cdot g_{m2}}$$

$$C \equiv C$$

Eliminating V_1

$$\frac{V_{out}}{V_{in}} = H_{BP} = \frac{Sg_{m3}C}{S^2C^2 + Sg_{m3}C + g_{m1}g_{m2}}$$

Design of $g_m C$ ladder filters

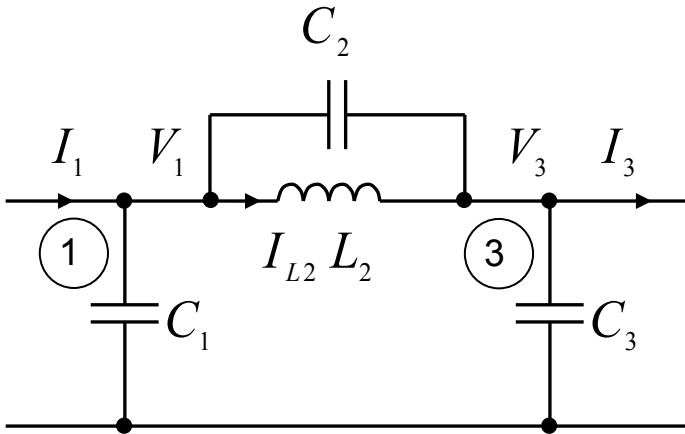

Current equations at nodes ① and ③


$$\begin{aligned} \textcircled{1} \quad I_1 &= SC_1 V_1 + I_{L2} + SC_2 (V_1 - V_3) \\ \textcircled{3} \quad I_3 &= I_{L2} + SC_2 (V_1 - V_3) - SC_3 V_3 \end{aligned} \cdot g_m R$$

\Rightarrow


$$\textcircled{1} \quad g_m (R I_1 - R I_{L2}) = SC_1 R g_m V_1 + SC_2 R g_m (V_1 - V_3)$$

$$\textcircled{3} \quad g_m (R I_{L2} - R I_3) = SC_3 R g_m V_3 + SC_2 R g_m (V_3 - V_1)$$

Current eq. (1)

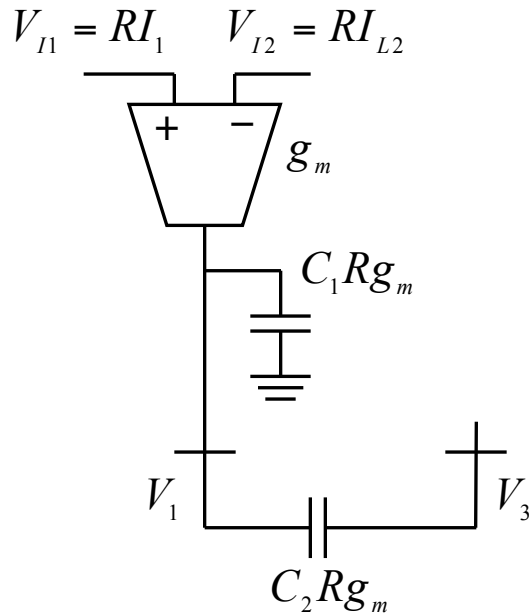

Current eq. (3)

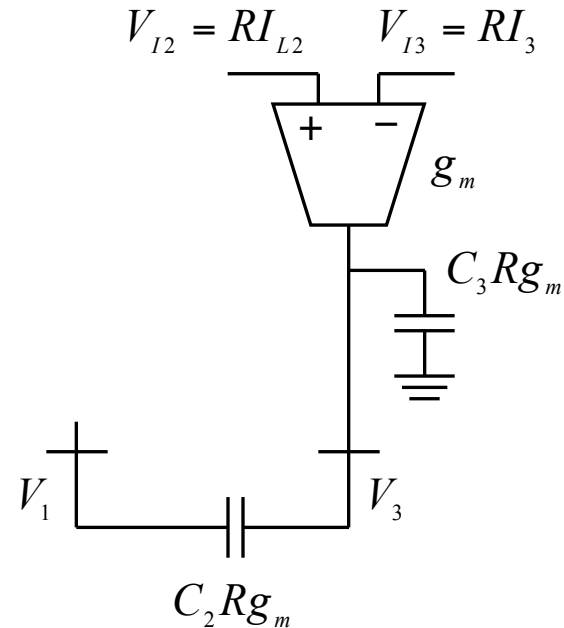


Current of inductor L_2

$$I_{L_2} = \frac{1}{SL_2} (V_1 - V_3) \Big| \cdot R$$

$$\Rightarrow RI_{L_2} = \frac{R}{SL_2} (V_1 - V_3)$$
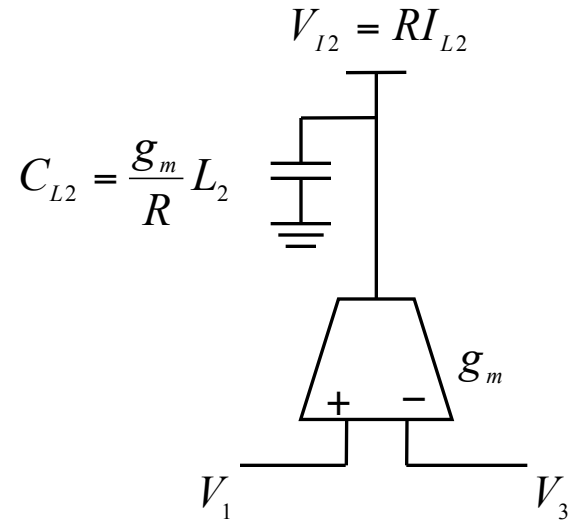
$$V_{I_2} = RI_{L_2} = \frac{R}{SL_2 g_m} \cdot g_m (V_1 - V_3)$$




select:



$$R = \frac{1}{g_m}$$

$$\Rightarrow C_{L_2} = g_m^2 L_2$$

C_1, C_2, C_3 unaltered

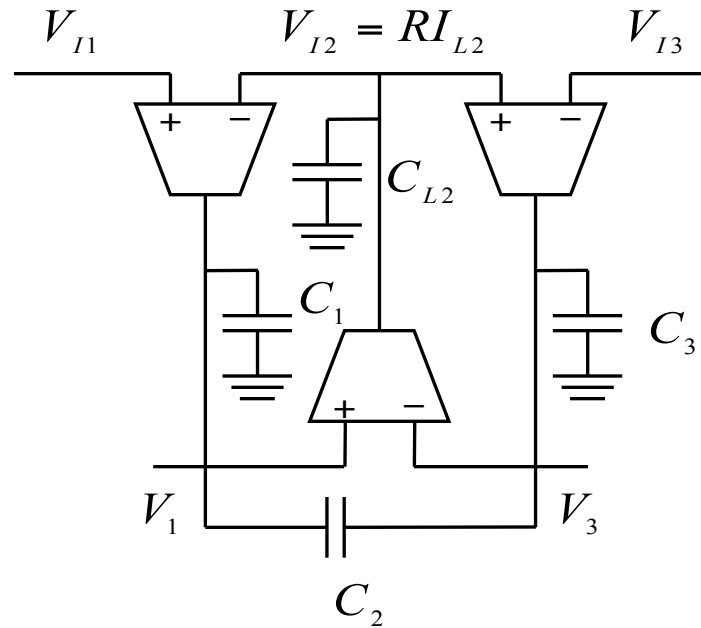

gmC ladder filter implementation

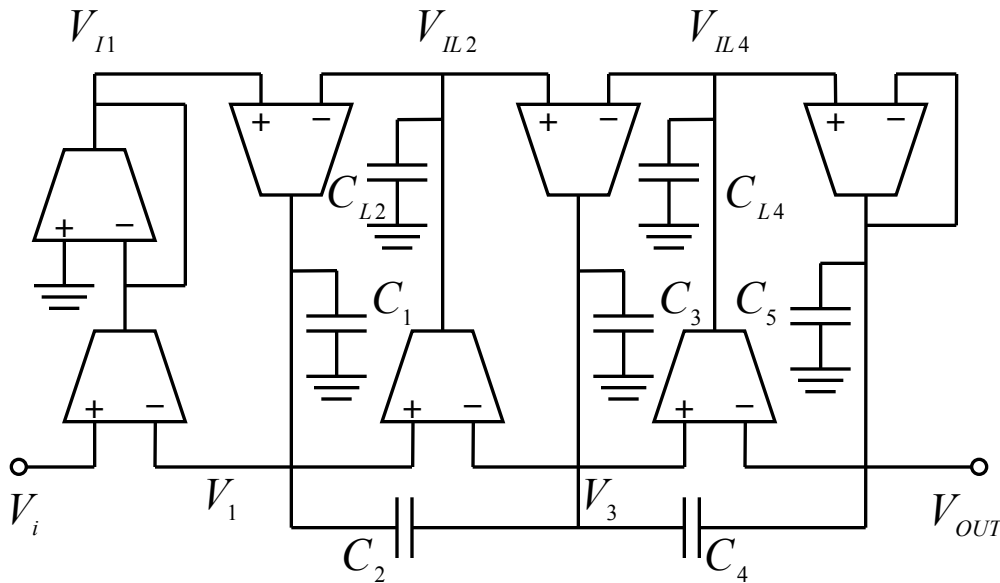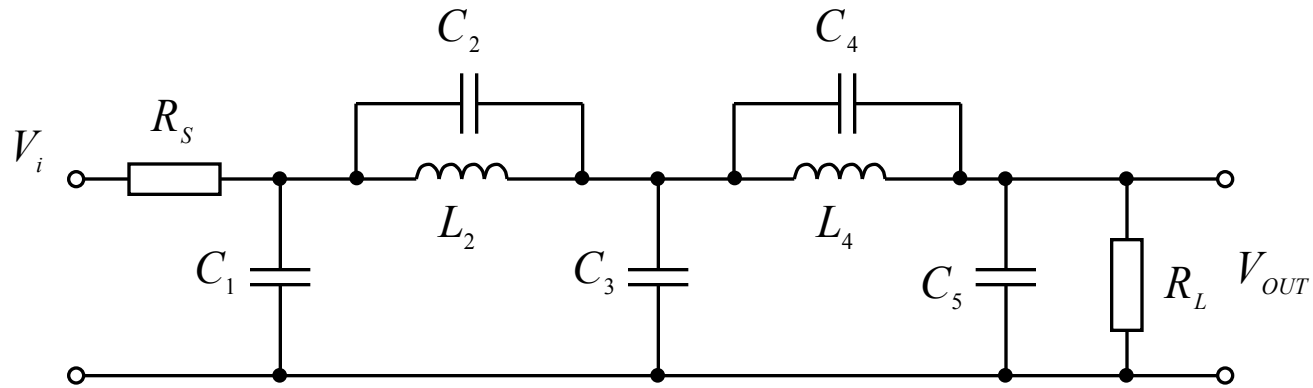

select:



$$R_S = R_L = R = \frac{1}{g_m}$$

$$\Rightarrow C_{L2} = g_m^2 L_2$$

$$C_{L4} = g_m^2 L_4$$

$C_{1..5}$ remain unaltered

Tunable OTA

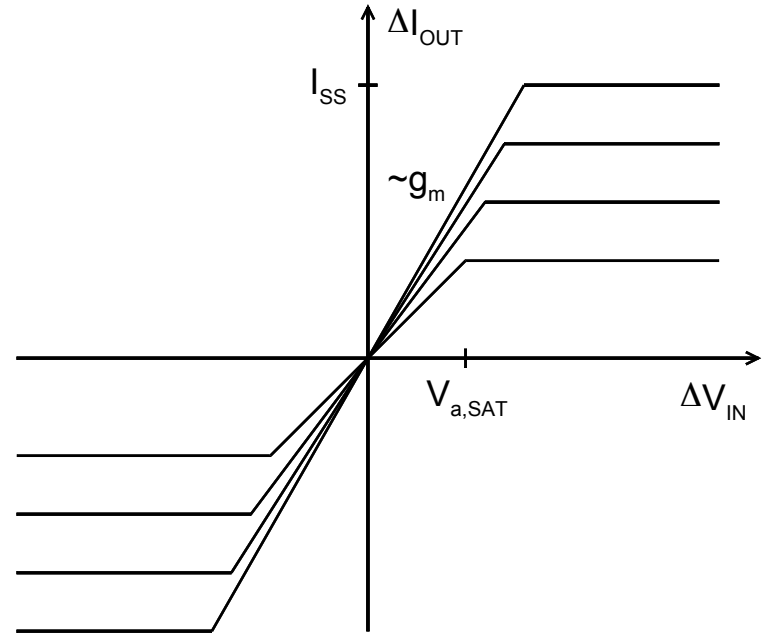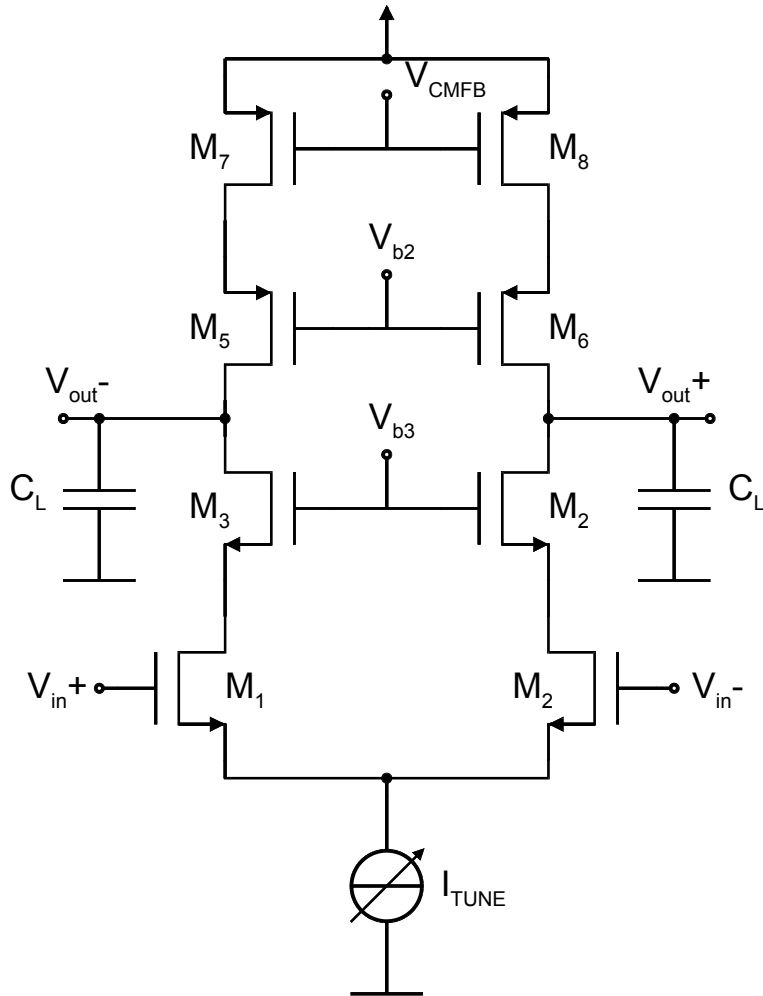


$$I_{SS} \sim I_{tune}$$

$$V_{a,SAT} \sim \sqrt{I_{tune}}$$


$$\sim g_m \sim \sqrt{I_{tune}}$$

- Parasitic capacitors

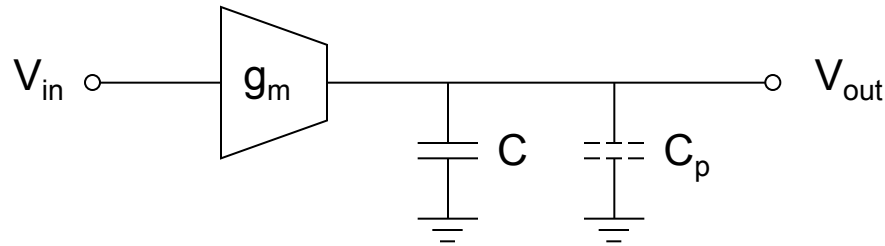

$$C' = C + C_p$$

- C_p is non-linear

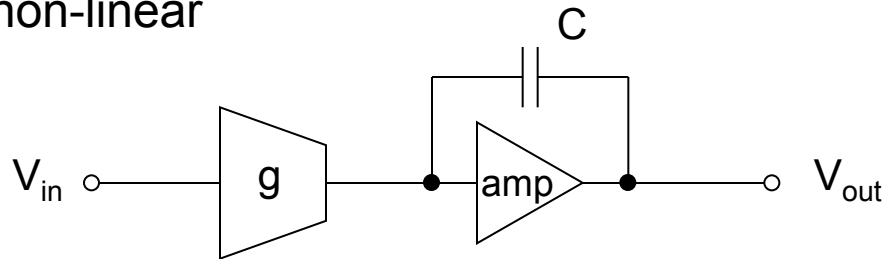

No parasitic affects.
 -limited speed due to amplifier
 -increased power consumption

- If no floating capacitors (i.e. No elliptical transfer function)
 - \Rightarrow transistor only processing
 (fine linewidth digital CMOS)
- Non-linearity of g_m -realisation
 - \Rightarrow THD > 0,1%