

ELEC-E3530

ELEC-E3530


# Integrated Analog Systems

## L8 Digital-to-Analog Converters

L8 Digital-to-Analog Converters

Integrated Analog Systems
 
# Principle block diagram of a D/A converter



# Summary of DACs

DAC Type	Advantage	Disadvantage
Current scaling	Fast, insensitive to switch parasitics	Large element spread, nonmonotonic
Voltage scaling	Monotonic, equal resistors	Large area, sensitive to parasitic capacitance
Charge scaling	Fast, good accuracy	Large element spread, nonmonotonic


# Implementation of a 3-bit voltage-scaling D/A converter

Tap voltages:

$$V_i = \frac{(i-1)R + \frac{R}{2}}{N \cdot R + \frac{R}{2}} \cdot V_{REF} = V_{OUT}$$


$$i = b_3 \cdot 2^2 + b_2 \cdot 2 + b_1$$

$$N = 2^n$$

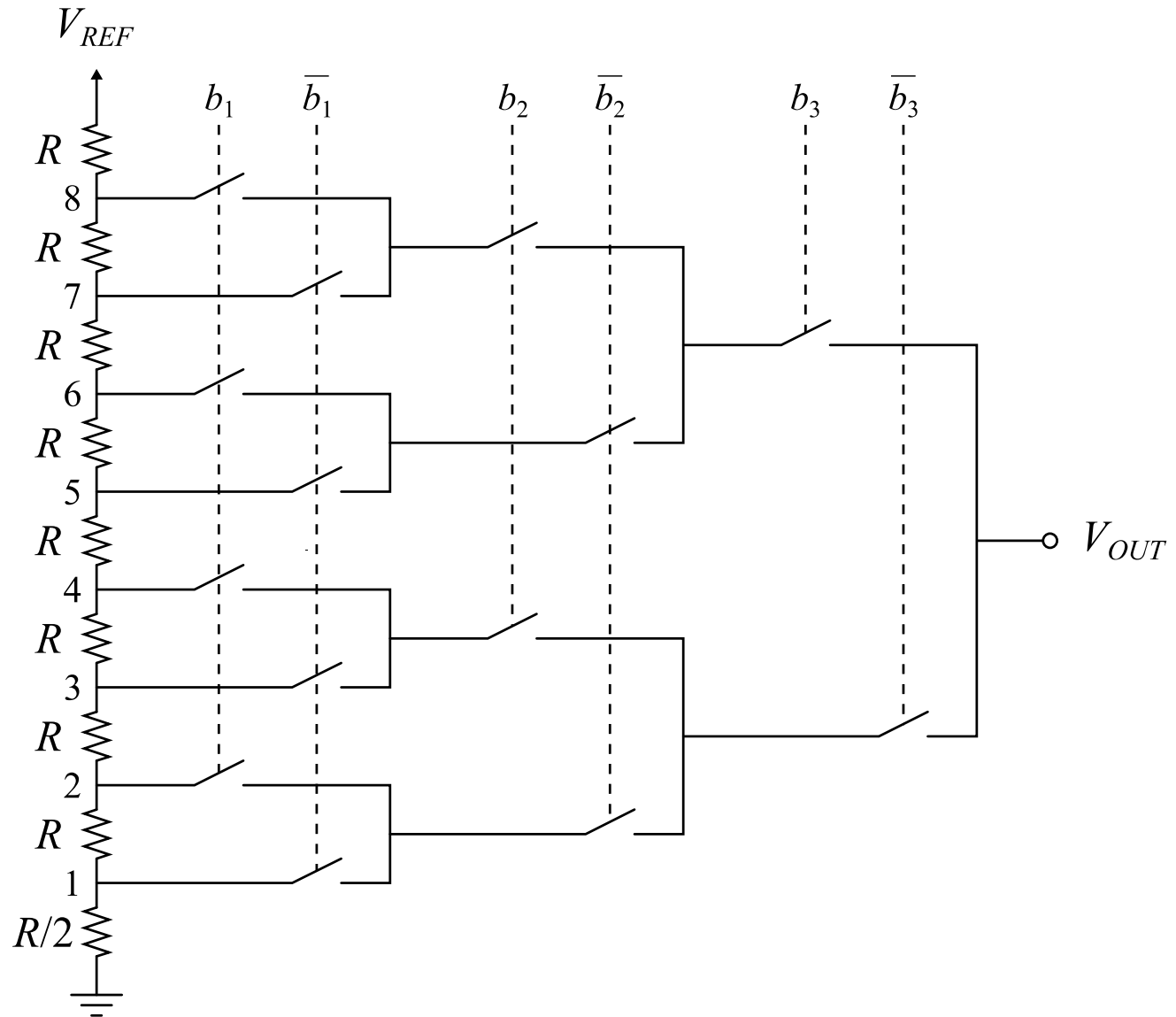
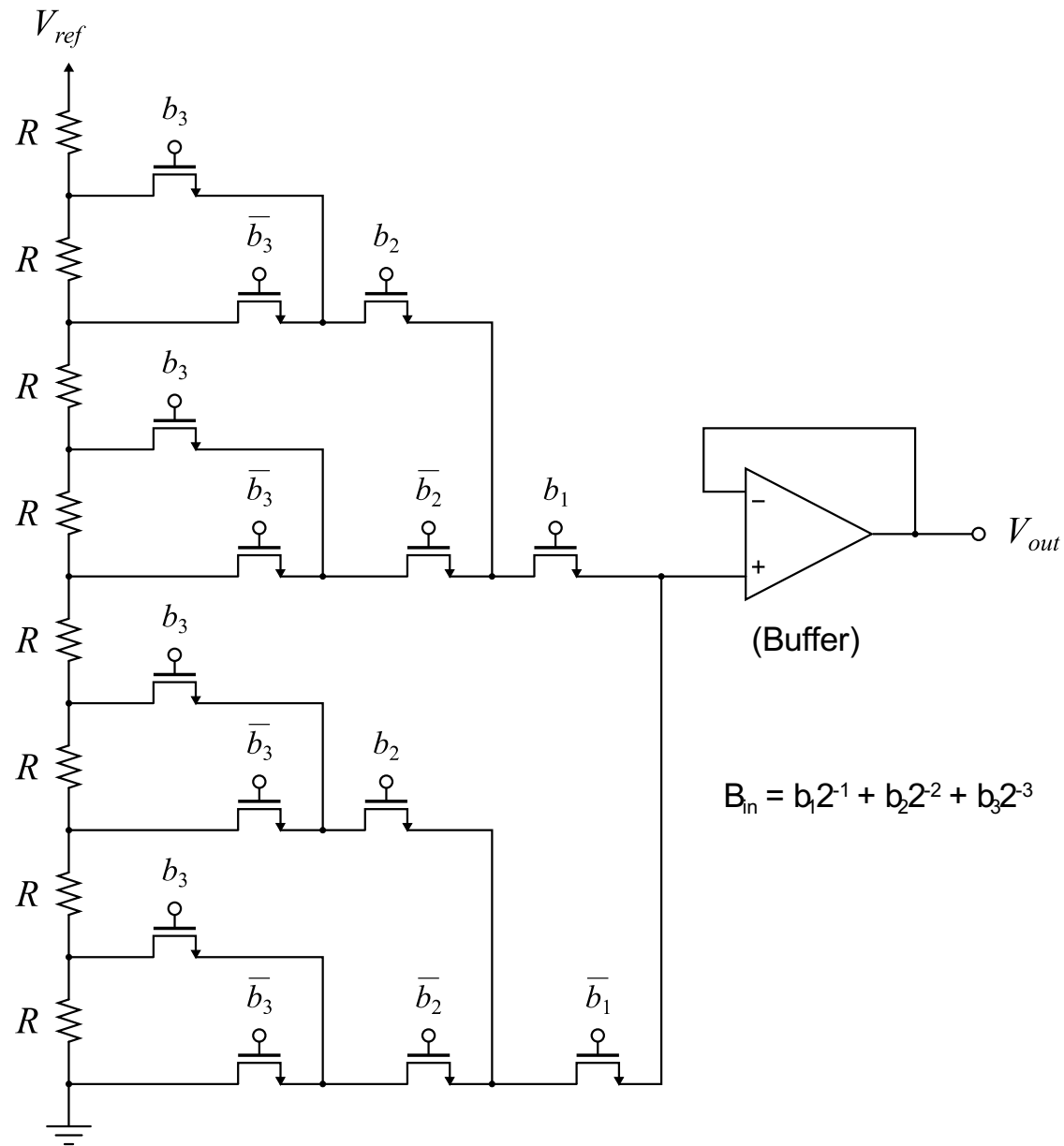
# Binary coded D/A converter

- $2^n$  resistors
- $(2^n - 1) \cdot 2$  switches
- Accuracy limited to 8 bits
- Higher accuracies  
common centroid geometry  
needed  $\rightarrow$  complicated  
wiring
- Speed limited by number  
of series switches
- Glitches f. ex transition  
011  $\rightarrow$  100




# Settling of R-string D/A converter

- When switched the speed is limited by RC time constants of the switches
- Number of switches in series n

R = switch on-resistance

C = switch capacitor

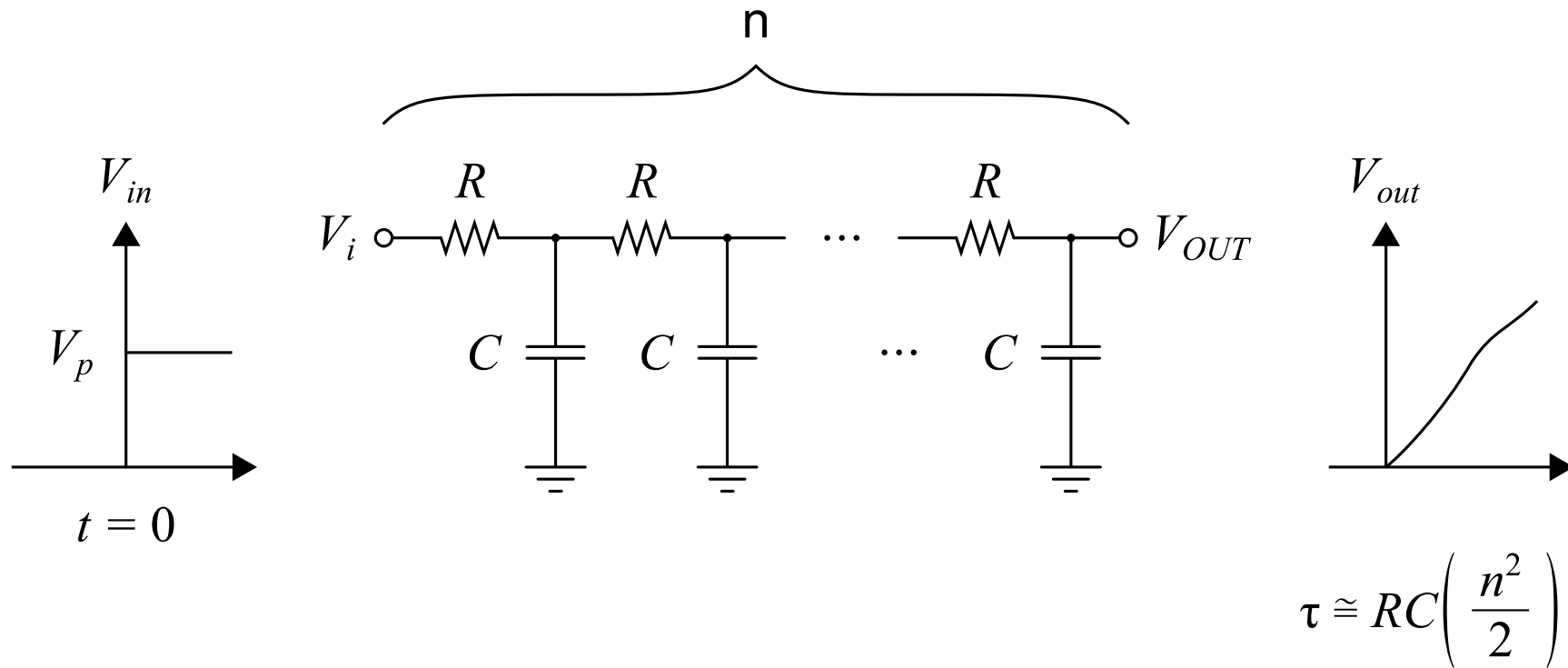

# Linear error in resistors cause integral nonlinearity

Tap voltage  $j$  assuming a linear processing error in resistivity


$$V_j = \frac{\sum_{K=0}^{j-1} (R + k\Delta R)}{\sum_{K=0}^{N-1} (R + k\Delta R)} V_{REF} = \frac{jR + \frac{j(j-1)}{2} \Delta R}{NR + \frac{N(N-1)}{2} \Delta R} V_{REF} \quad (1)$$

The INL profile is given by the difference between (1) and ideal tap voltage,  $jV_{REF}/N$ :

$$INL_j = \frac{j}{N} V_{REF} - \frac{jR + \frac{j(j-1)}{2} \Delta R}{NR + \frac{N(N-1)}{2} \Delta R} V_{REF} \quad (2)$$


Simplifying (2) yields
 
$$INL_j = \frac{j(N-j)}{R + \frac{N-1}{2} \Delta R} \frac{\Delta R}{2N} V_{REF}$$



# Thermometer coded D/A converter


$2^N$  resistors  
(all equal sizes)

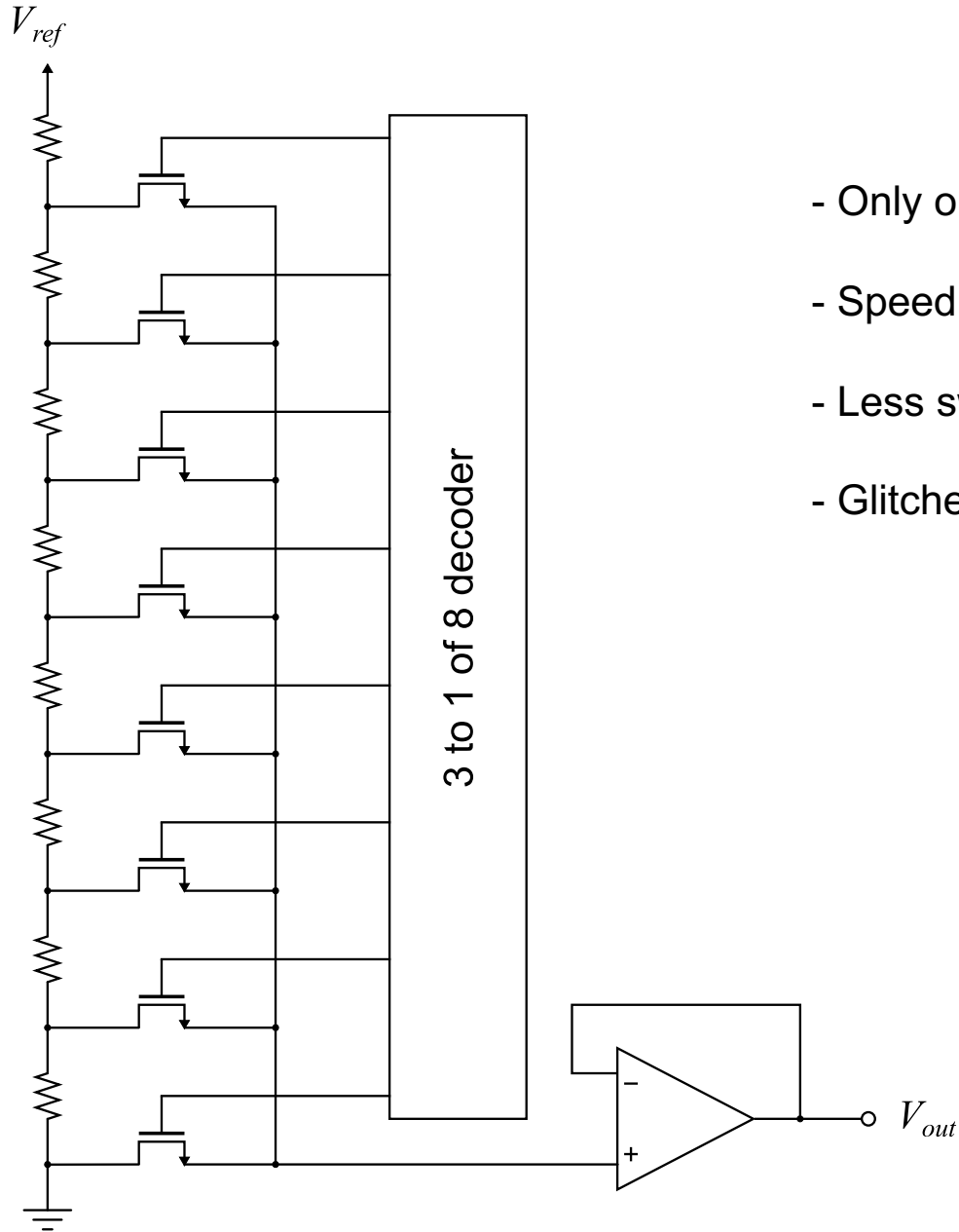

- Only one switch per tap voltage
- Speed limited by only one RC-timeconstant
- Less switches, n-to-2n decoder needed
- Glitches eliminated



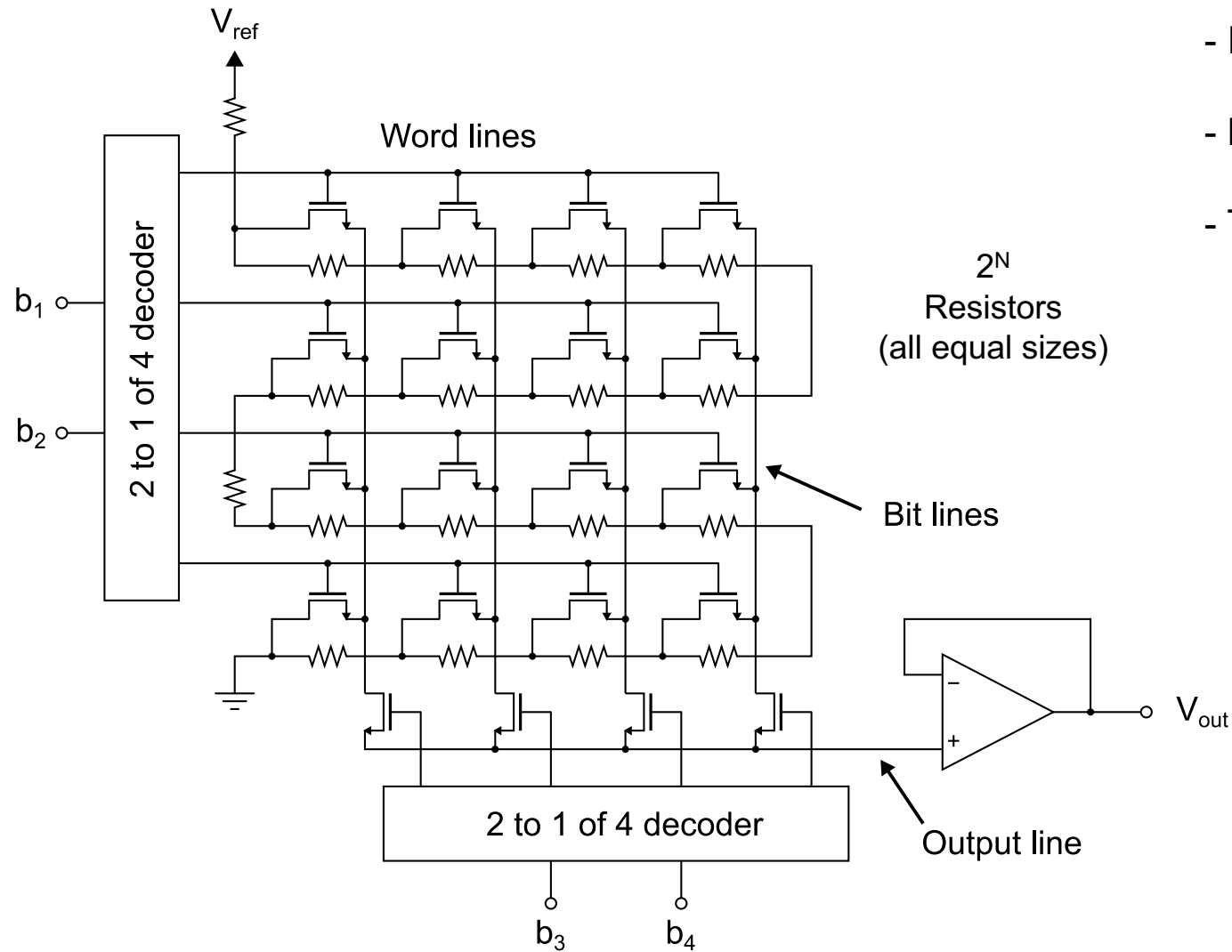
# A 4-bit folded resistor-string D/A converter




- Row and column decoders
- less complex decoders
- Two switches in series

# Multiple R-string 6-bit D/A converter

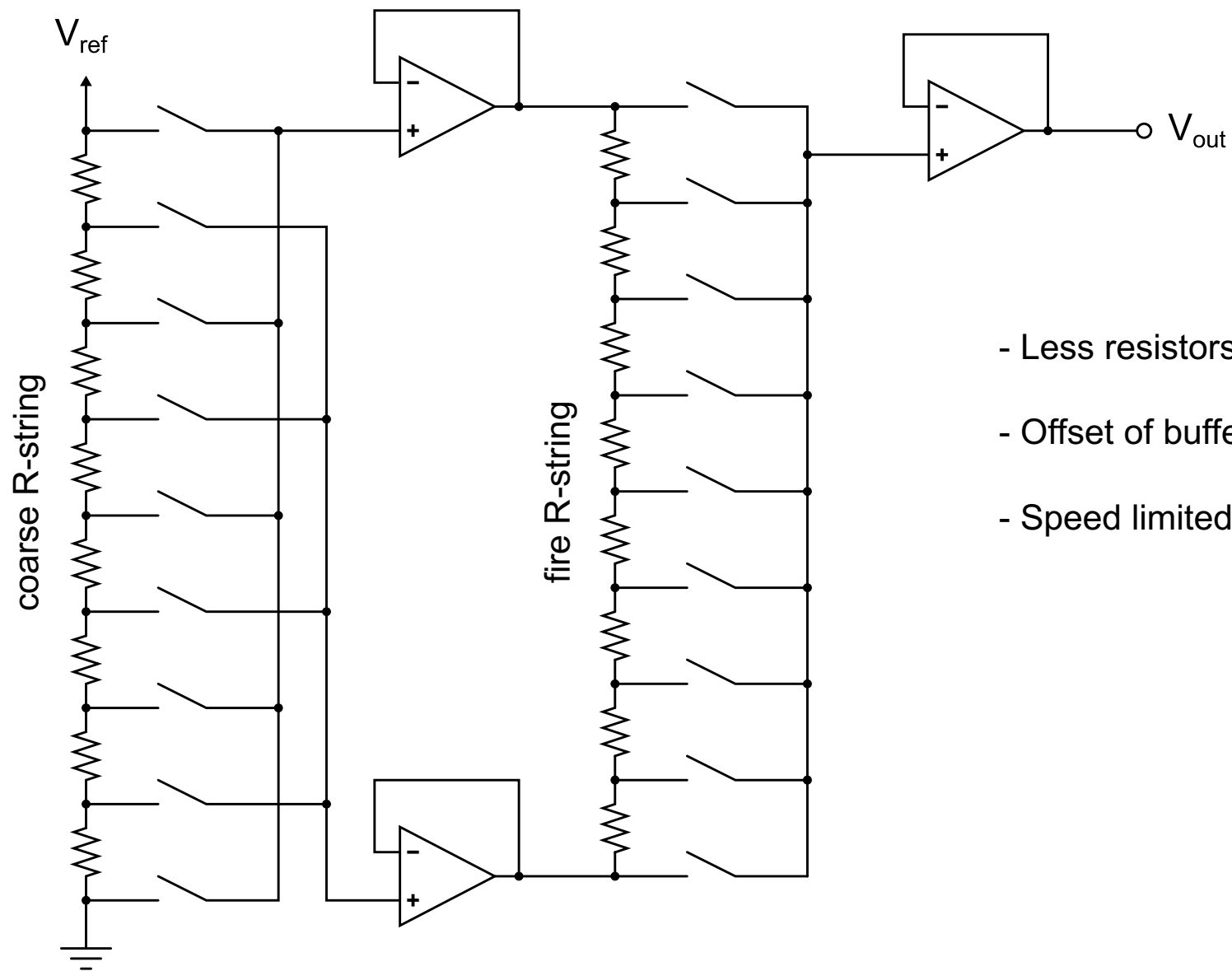

- Less resistors  $2 \times 2^{N/2}$
- Offset of buffer amplifiers
- Speed limited by buffer amplifiers



# Multiple R-string 6-bit D/A converter

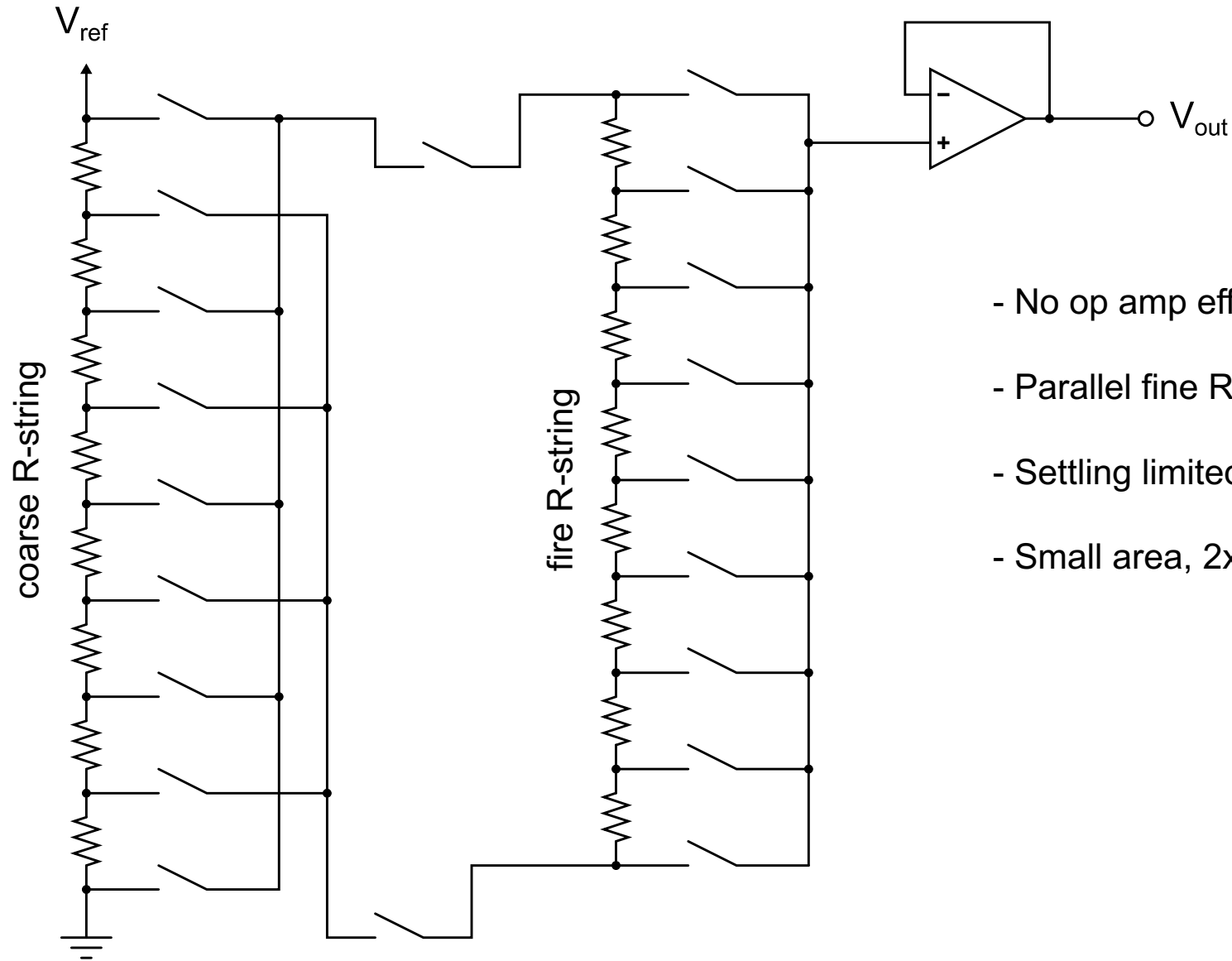

- No op amp effects
- Parallel fine R-string reduces the coarse tap resistor
- Settling limited by the time-constant of fine R-string
- Small area,  $2 \times 2^{N/2}$  resistors

  
# Coarse and fine R-strings without Op Amps

Intermeshed resistor-ladder DACs with (a) one-level multiplexing and (b) two-level multiplexing.




- No offset error due to op amp
- Every coarse tap resistor has a parallel fine R-string of resistors  $\rightarrow$  no error due to parallel connection
- Only one series switch low  $R_{ON}$ , many parallel switches  $\rightarrow$  high C



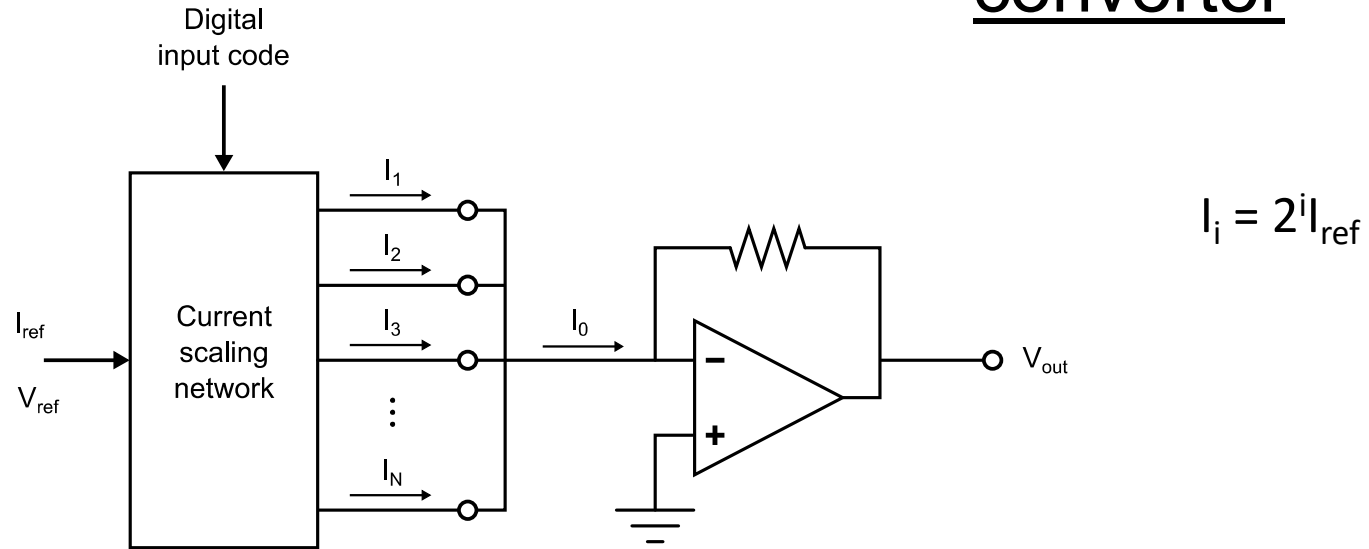
# Conceptual illustration of a current-scaling D/A converter



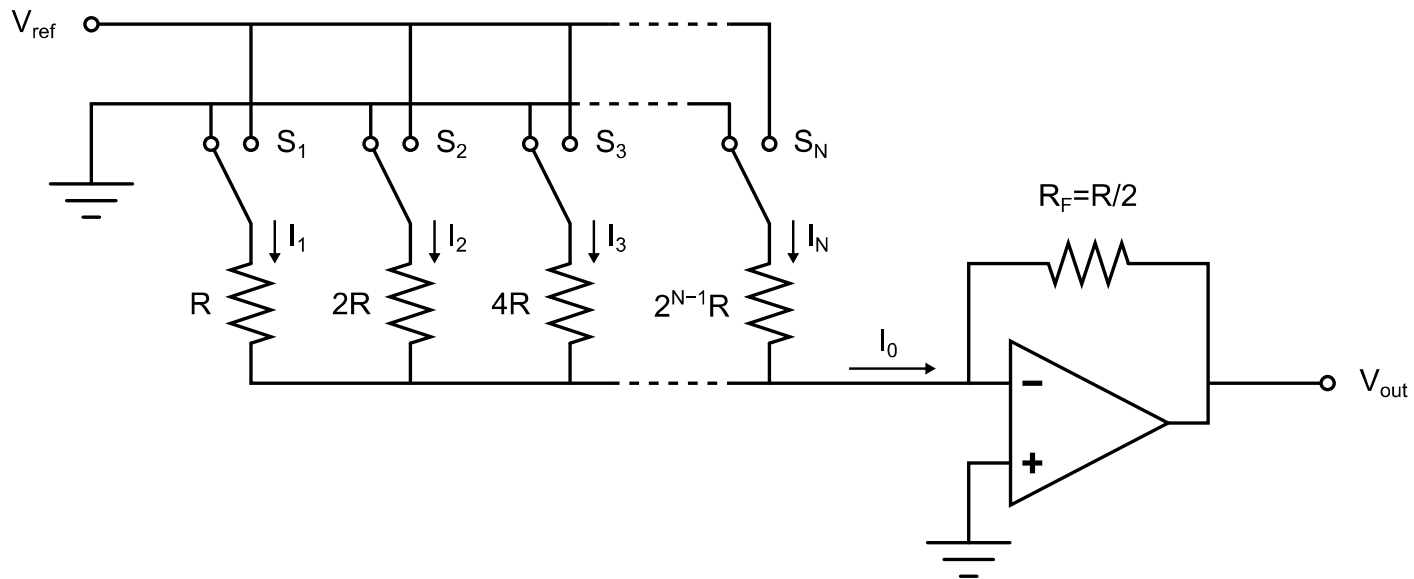Binary weighted resistors convert the  $V_{ref}$  into binary weighted currents.



# Current scaling D/A converter

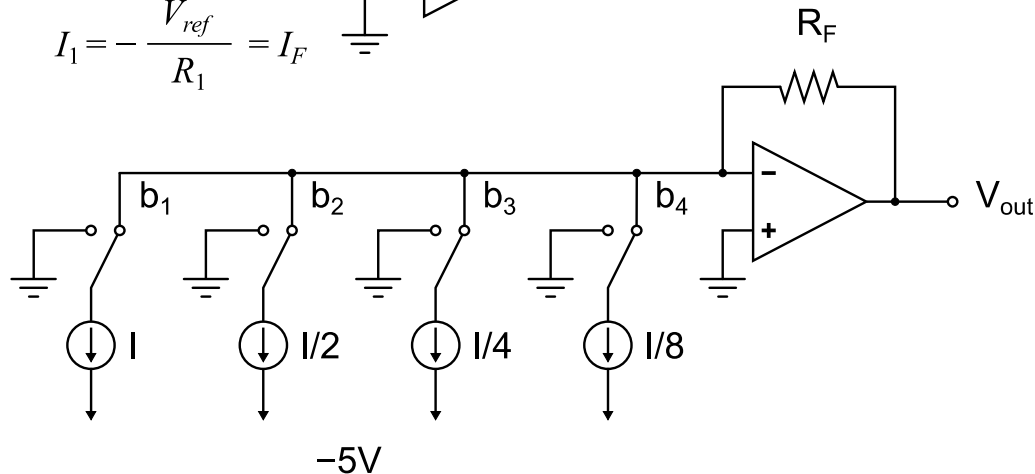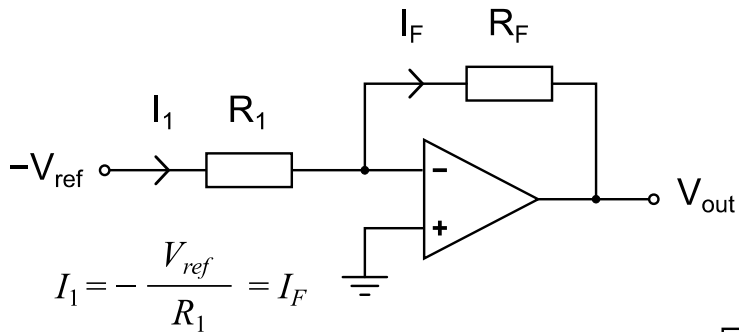 

- Weighted currents generated with weighted resistors

$$I_i = \frac{V_{ref}}{R_i}$$

- Large resistor spread


$$R_{MAX} = 2^n \cdot R_{MIN} \Rightarrow \text{large area}$$

- Switched  $R_{ON}$  in series  $\rightarrow$  non-linearity

- Resistors switched between virtual ground and analog ground

- Speed limited by op amp

# Voltage and current scaling

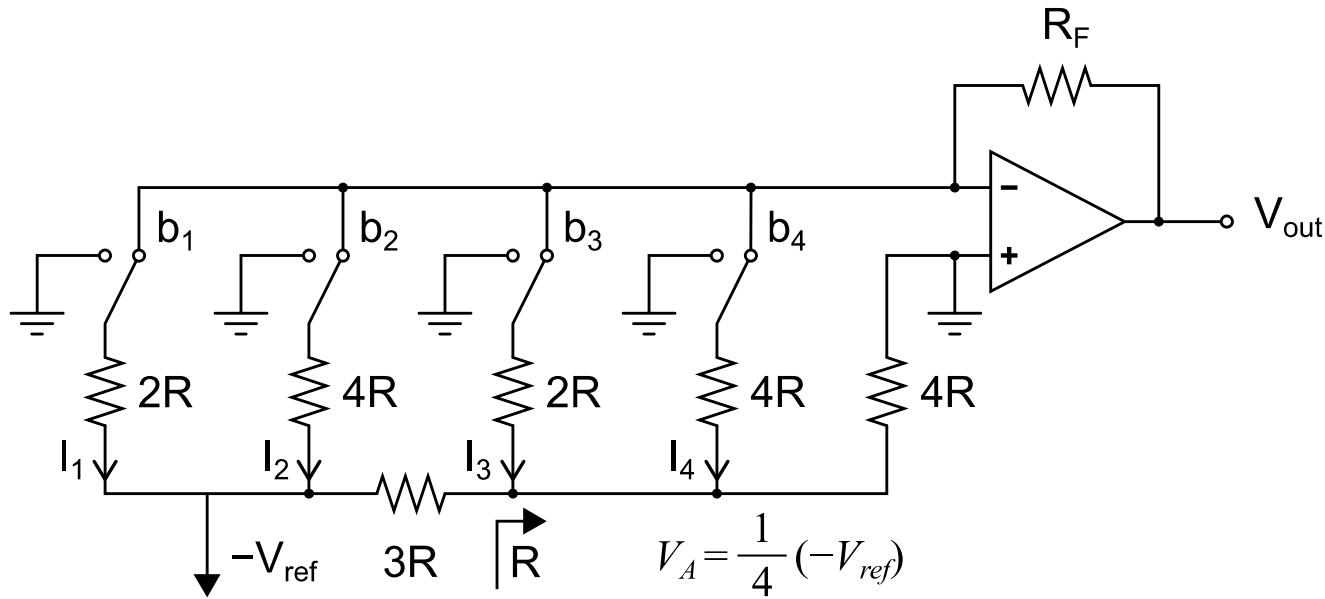

Resistor spread

$$R_{MAX} = 2^{n/2} \cdot R_{MIN}$$

$\Rightarrow$  reduced area

no switch in series with  $3R$

$\Rightarrow$  matching error


Total resistor to ground seen to the right of  $3R$  is  $R = 2R || (4R || 4R)$

The branch currents are:


$$I_1 = \frac{-V_{ref}}{2R} \quad I_3 = \frac{V_A}{2R} = \frac{-V_{ref}}{8R}$$

$$I_2 = \frac{-V_{ref}}{4R} \quad I_4 = \frac{V_A}{4R} = \frac{-V_{ref}}{16R}$$

# R-2R D/A converter

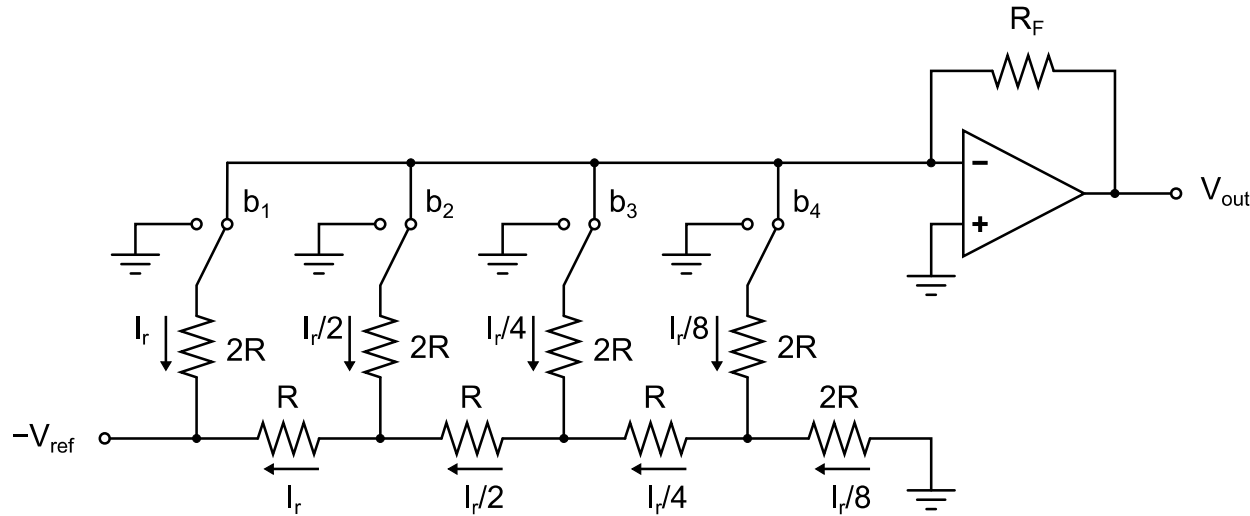

4-bit R-2R based D/A converter

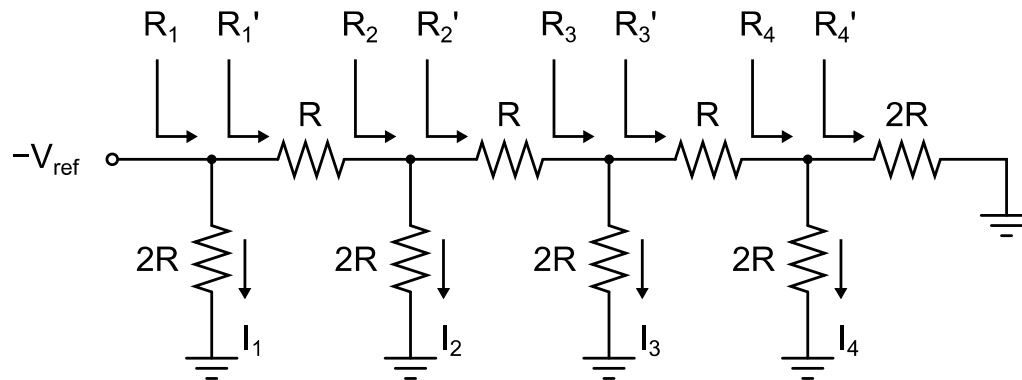

R-2R resistance ladder

$$R'_4 = 2R$$

$$R_4 = 2R \parallel R'_4 = R$$

$$R'_3 = R + R_4 = 2R$$

$$R_3 = 2R \parallel R'_3 = R$$

$$R'_2 = R + R_3 = 2R$$

$$R_2 = 2R \parallel R'_2 = R$$

$$R'_1 = R + R_2 = 2R$$

$$R_1 = 2R \parallel R'_1 = R$$

$$I_1 = \frac{1}{2} \frac{V_{ref}}{R}$$

$$I'_1 = I_1$$

$$I_2 = \frac{1}{2} I'_1 = I'_2 = \frac{1}{2} I_1$$


$$I_3 = I'_3 = \frac{1}{2} I'_2 = \frac{1}{4} I_1$$

$$I_4 = I'_4 = \frac{1}{2} I'_3 = \frac{1}{8} I_1$$

- switch  $R_{ON}$  effects  $2R \rightarrow$  error



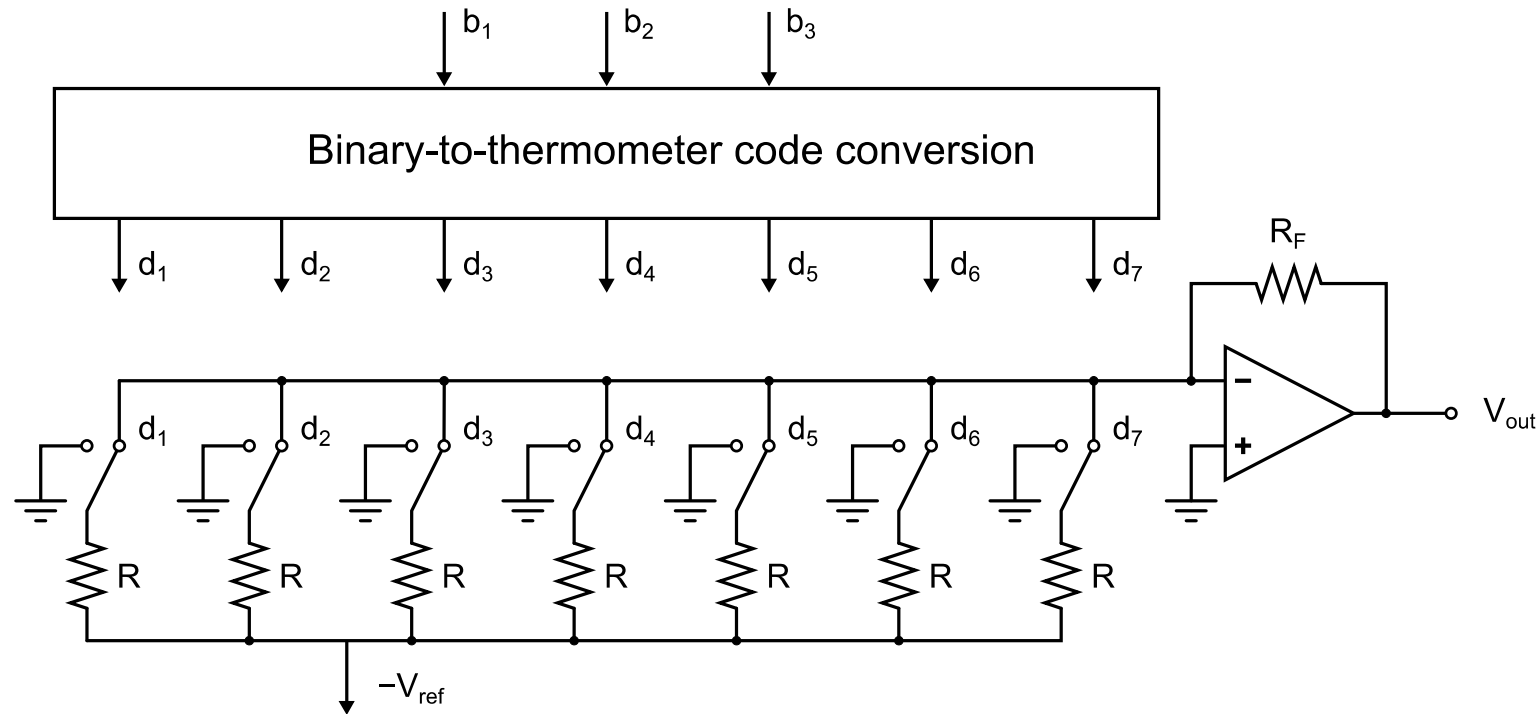
# Thermometer coded current scaling D/A converter



- Glitches eliminated
- Every resistor adds current of 1 LSB
- Switches give equal error for every  $R \rightarrow R_{ON}$  eliminated for first order
- Large  $n$ -to-1 of  $2^n$  decoder needed  $\rightarrow$  complicated wiring for switches


# Binary vs. thermometer coding

 


Deci mal	Binary			Thermometer Code						
	b 1	b 2	b 3	d 1	d 2	d 3	d 4	d 5	d 6	d 7
0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1
2	0	1	0	0	0	0	0	0	1	1
3	0	1	1	0	0	0	0	1	1	1
4	1	0	0	0	0	0	1	1	1	1
5	1	0	1	0	0	1	1	1	1	1
6	1	1	0	0	1	1	1	1	1	1
7	1	1	1	1	1	1	1	1	1	1

Glitches are code i.e. signal dependant and cause spurs in the signal spectrum.

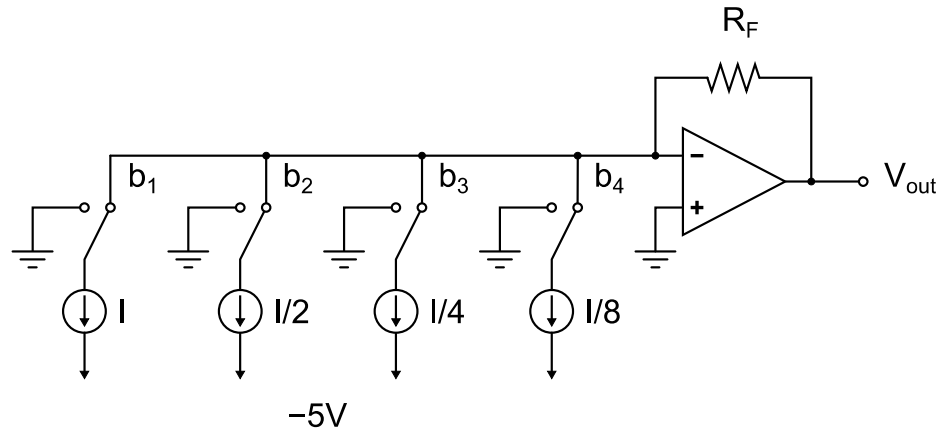
# Binary-weighted current source D/A convertor



 Binary-weighted current-mode D/A converter



 
- Binary weighted currents realized with binary weighted current mirrors
- Switch transistors  $Q_1$  and  $Q_2$  direct the current either to  $V_{ss}$  ( $d_1=0$ ) or to load resistor ( $d_1=1$ )




(a)

(a) Simple current replication;

 
(b) current replication incorporating emitter degeneration.



(b)

 


(a)

 


(b)

 Conversion of output current of an array to voltage using (a) a resistor on (b) a transimpedance amplifier.




All current sources are of equal value.

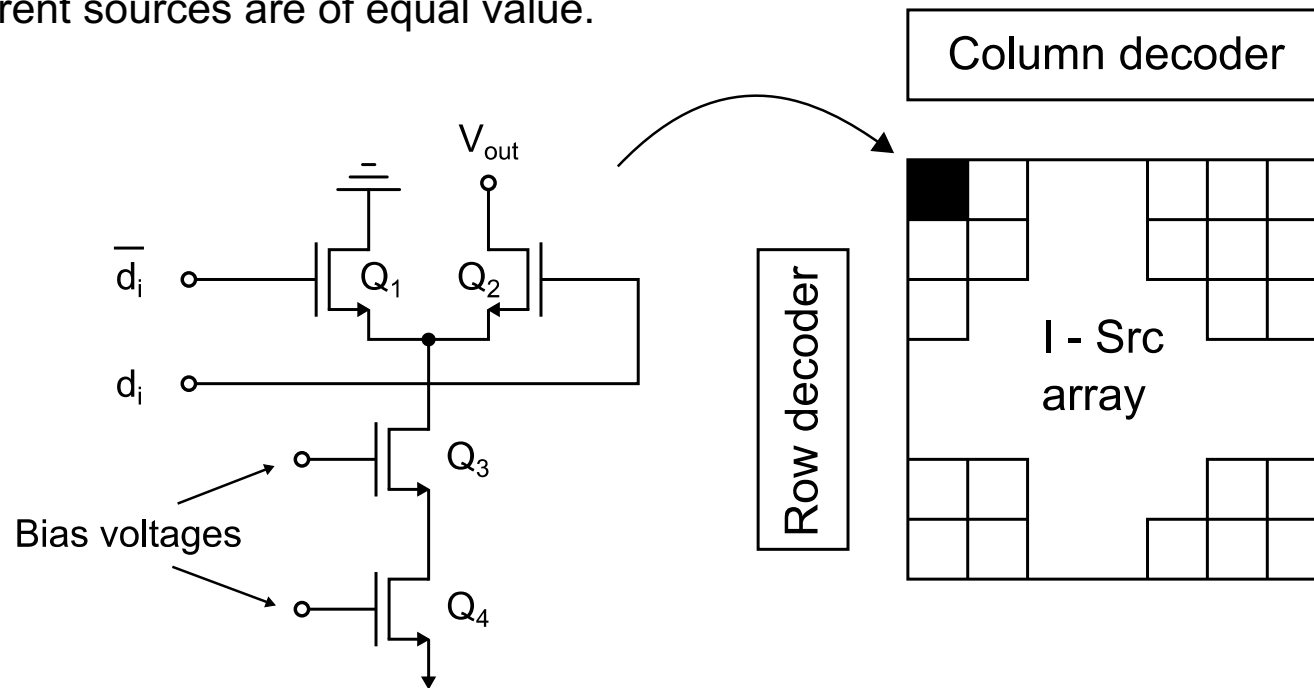


Thermometer-code current-mode D/A converter.  $Q_1$  and  $Q_2$  form the current switch, whereas  $Q_3$  and  $Q_4$  implement a cascode current source.

# 10-bit current-steering DAC

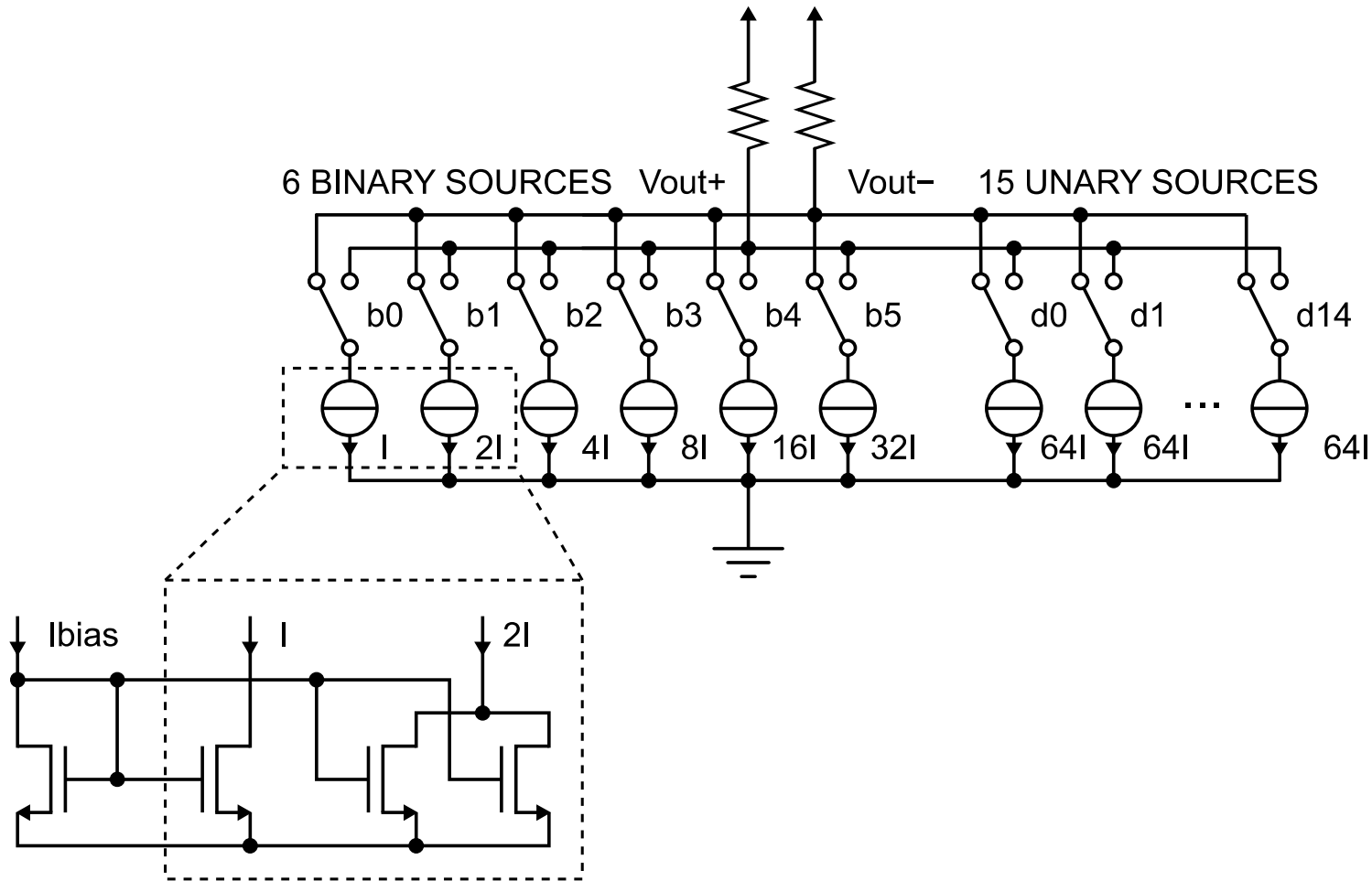


- Currents steered to output by switches controlled by digital input
- Signal current driven to load resistors
- LSBs binary weighted
- MSBs unary
  - Largest current source size and worst glitch energy reduced
- MSB bits has to be thermometer decoded
  - Decoder makes structure more complicated and consumes power and area
- Current sources constructed of unit transistors
- Biasing voltage generated from external bias current with current mirror

# Current switches

 

- Current switches are simple source coupled pairs
- Controlling signals can be pure digital signals (input bit and its inversion)
  - Usually switches are not driven from rail to rail because quite small differential voltage is adequate
- Controlling signal generation and synchronization a key to good performance
  - Imperfect synchronization causes glitches and harmonic distortion
  - Synchronization usually done by flip-flops or latches
  - Flip-flop outputs must be buffered to achieve fast transitions
    - Sturdy inverters driving switch gates

# Current source construction

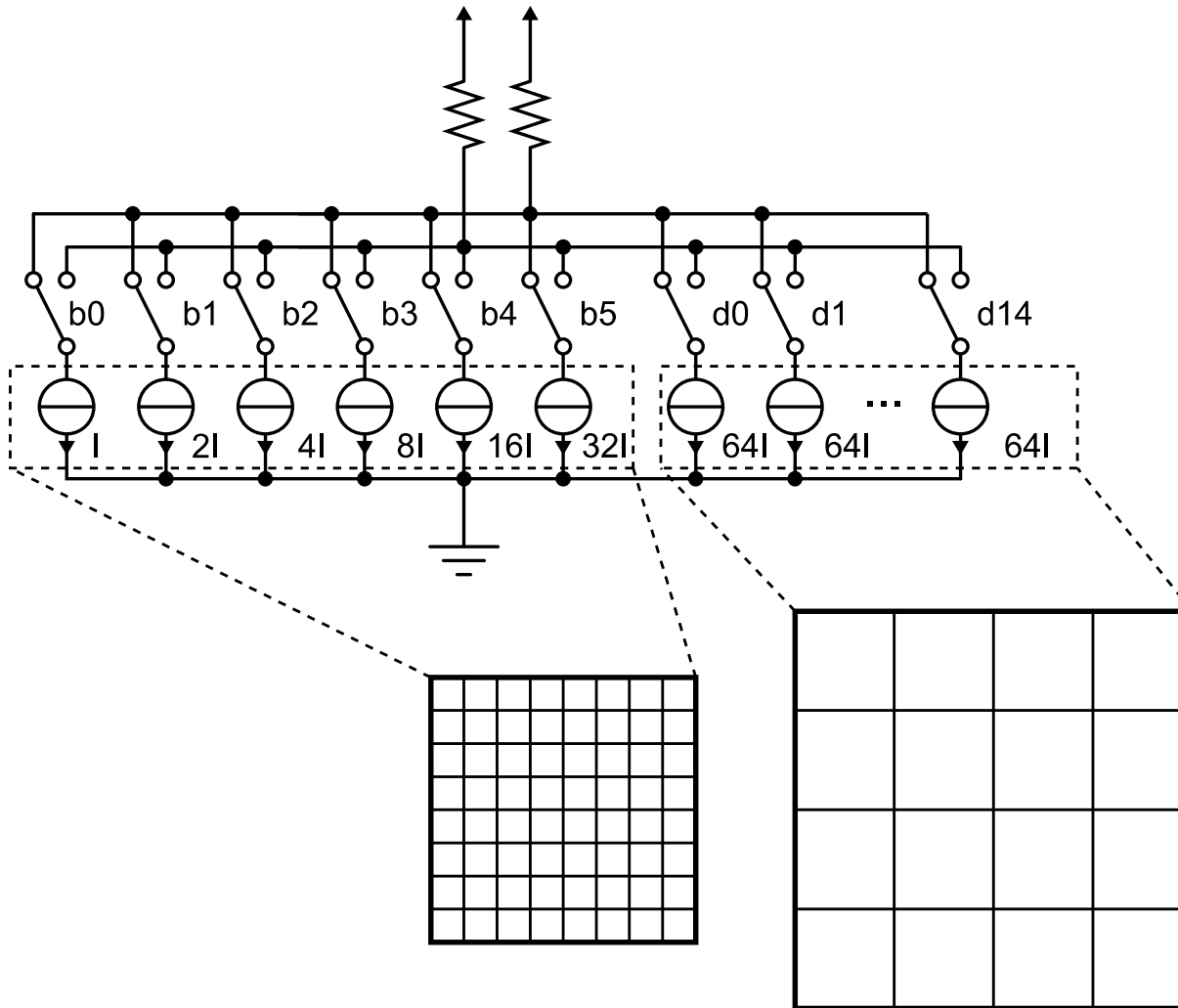

- Unit sources in common centroid layout to compensate for process and temperature variations on chip
  - Odd order gradients cancelled perfectly
  - Effect of even order gradients reduced by using more units
  - Unit placement and switching sequence affects INL
- MSB matrix large to improve matching
- Usage of two or more matrixes reduce the amount of units making implementation easier
- Matrixes and their bias currents have to be matched
  - Mismatch cause non-linearity

LAYOUT



# Random errors

- For a D/A converter to be fully functional, INL error has to be smaller than  $\frac{1}{2}$  LSB (least significant bit)
- Direct relationship exists between INL error and matching properties of used technology expressed by the relative unit current source standard deviation  $\sigma(I_{LSB})/I_{LSB}$
- Parameter determines dimensions of current sources of D/A converter

$$W_{LSB}L_{LSB} = \frac{A_{\beta}^2}{\frac{2\sigma^2(I_{LSB})}{I_{LSB}^2}} + \frac{4A_{VT}^2}{\frac{2\sigma^2(I_{LSB})}{I_{LSB}^2}(V_{GS} - V_T)^2}$$

- Where  $A_{\beta}$  and  $A_{VT}$  are technological parameters,  $(V_{GS}-V_T)$  gate overdrive voltage of current source and  $\sigma(I_{LSB})/I_{LSB}$  unit current source relative standard deviation
- Convenient criterion to determine gate override voltage of current source transistor is to make two mismatches contributing about equal

# Random errors


- Assuming that each unit current source has a value that follows a normal distribution, required accuracy is

$$\frac{\sigma(I_{LSB})}{I_{LSB}} = \frac{1}{2C\sqrt{2^N - 1}}$$

where C depends only on yield requirement and N is number of bits.

- Or partially segmented architectures, INL performance is dependent on segmentation level
- Monte Carlo simulations are therefore used to estimate INL yield as a function of unit current source standard deviation

# Small signal model of D/A converter

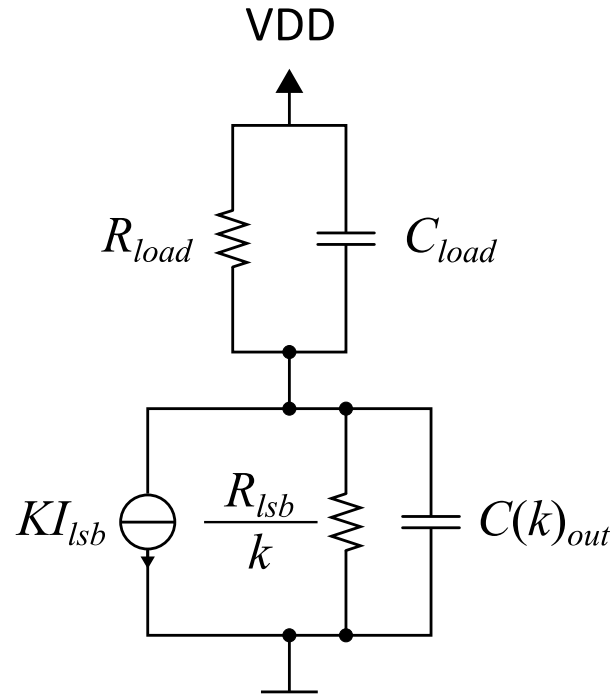

- Output current is

$$I_{out} = \frac{I_{lsb}}{\frac{1}{k} + \frac{Z_{load}}{Z_{lsb}}}$$



where k is the digital code, Rload is the load resistance, Cload is the load capacitance, Rlsb is the LSB current source resistance, Cout is the parasitic capacitance, and Ilsb is the LSB current.

- If  $Z_{LSB}$  finite,  $I_{out}$  is a non-linear function causing harmonic distortion
- Output current does not depend linearly on digital input code, when output impedance is finite

$$INL_{se}(k) = \frac{\frac{kZ_{load}}{1 + \frac{kZ_{load}}{Z_{lsb}}} - \frac{kZ_{load}}{1 + \frac{Z_{load}(2^N - 1)}{Z_{lsb}}}}{\frac{Z_{load}}{1 + \frac{Z_{load}(2^N - 1)}{Z_{lsb}}}} I_{lsb} = \frac{Z_{load}}{Z_{lsb}} k(2^N - 1 - k) I_{lsb}$$

, where N is the number of the bits.



# Cascode transistor

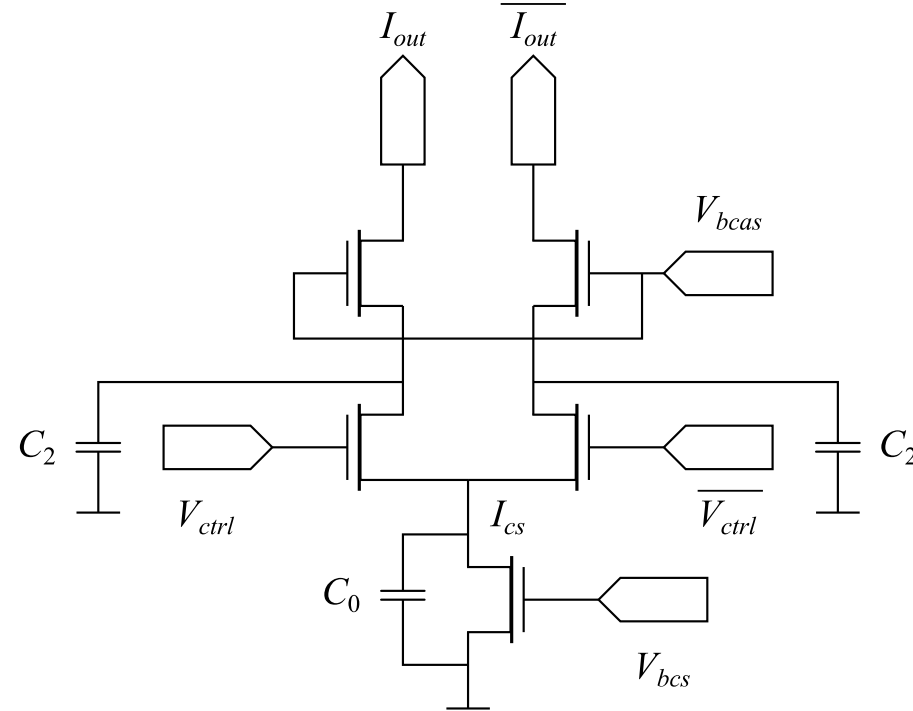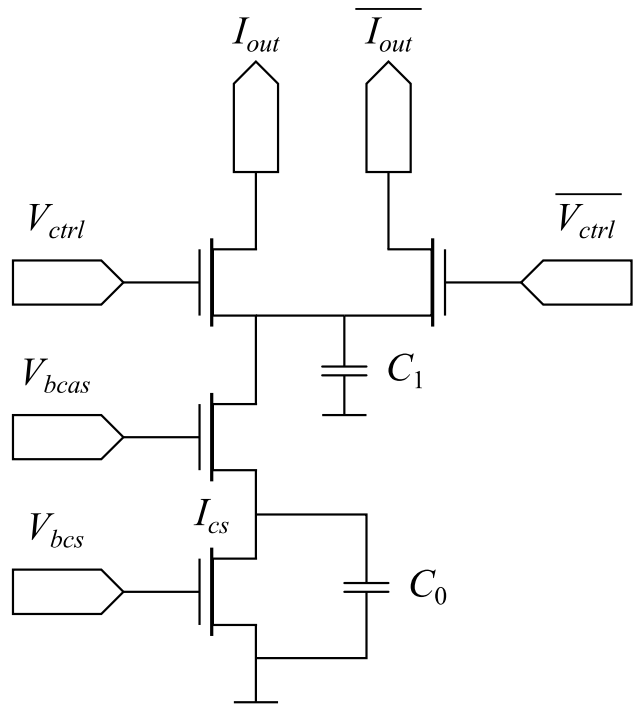

- Cascode transistor multiplies current source output impedance by their gain
- Other advantage is that cascode transistors isolate the current switches and current sources
- Two cascode transistors to enhance output impedance → additional bias voltage and reduces output voltage range
- Cascode transistors could also be added between current switches and output

  
# Glitches reduction

A key aspect of performance of D/A converter is output glitch, which is mainly due to following effects:




- 1) Imperfect synchronization of control signals of current switches  
→ D flip-flop or latch placed symmetrically near switches, switch drivers load matching
- 2) Charge and discharge of parasitic capacitances associated with current sources  
→  $C_0$  is minimized by layout techniques and using cascode devices
- 3) Feedthrough of digital input data to output  
→ Low swing signals minimize capacitively coupled switching noise, dummy switches
- 4) Switching transistors being simultaneously in off state  
→ high crossing point signals guarantee both switch transistors do not turn off at the same time

# Glitches reduction

 

- If both switching transistors are turned off, output node of the current source will rapidly discharge and current source will turn off
- To recover from this condition, current source must progress through the linear region and back into saturation
- The situation can, however, be improved by setting the crosspoint of the control signals at the optimum high level
- D/A converter output could be reduced by restricting the control voltage swing
- Because switches source voltage follows during the transitions control voltage (not linearly), it is possible to reduce this variation by decreasing control voltage swing
- Code dependent power supply and clock jitter → adding dummy switch drivers and switches
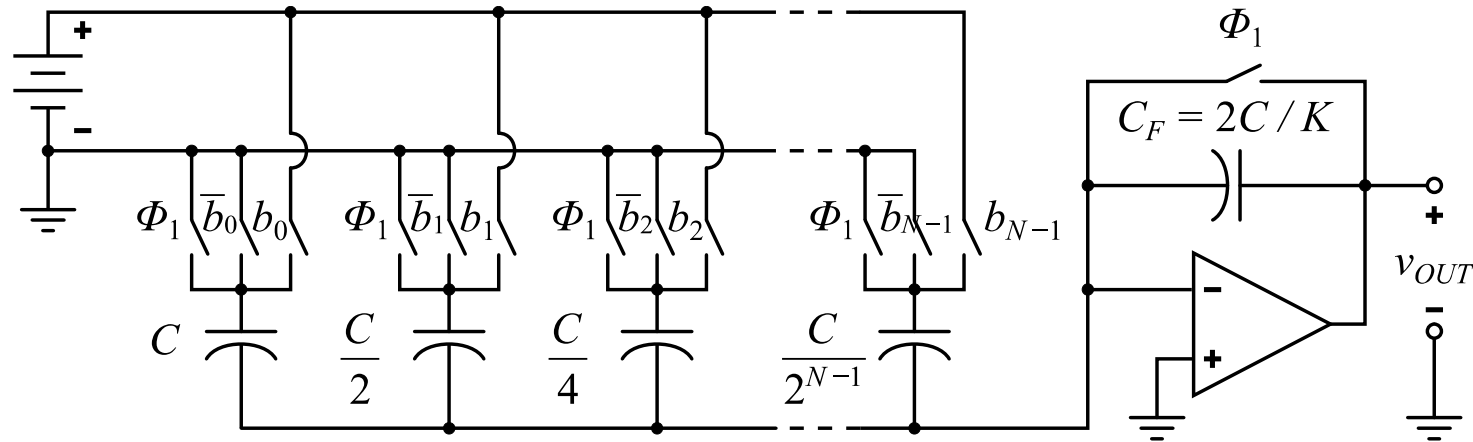
# Binary-weighted, charge amplifier DAC implementation



1. DAC is essentially a binary-weighted charge amplifier
2. During the  $\phi_1$  clock phase, all capacitors are discharged to zero volts
3. Capacitors are autozeroed. During the  $\phi_2$  clock phase, the switch labeled  $b_i$  or  $\bar{b}_i$  is closed
4. Polarity is changed by reversing the polarity of  $V_{REF}$
5. No floating nodes
6. No terminating capacitor to make the sum equal to  $2C$
7. Speed limited by the op amp



$$v_{OUT} = \frac{-K}{2C} \left( b_0 C + \frac{b_1 C}{2} + \frac{b_2 C}{2} + \dots + \frac{b_{N-1} C}{2^{N-1}} \right) V_{REF}$$

$$= -K \left( \frac{b_0}{2} + \frac{b_1}{4} + \frac{b_2}{8} + \dots + \frac{b_{N-1}}{2^N} \right) V_{REF}$$

$$(V_{ref} - V_{OUT})C_{eq} = (C_{TOT} - C_{eq}) \cdot V_{OUT}$$

$$V_{REF}C_{eq} = V_{REF} \left( b_1C + \frac{b_2C}{2} + \frac{b_3C}{2^2} + \dots + \frac{b_NC}{2^{N-1}} \right) = C_{tot}V_{OUT} = 2CV_{OUT}$$
 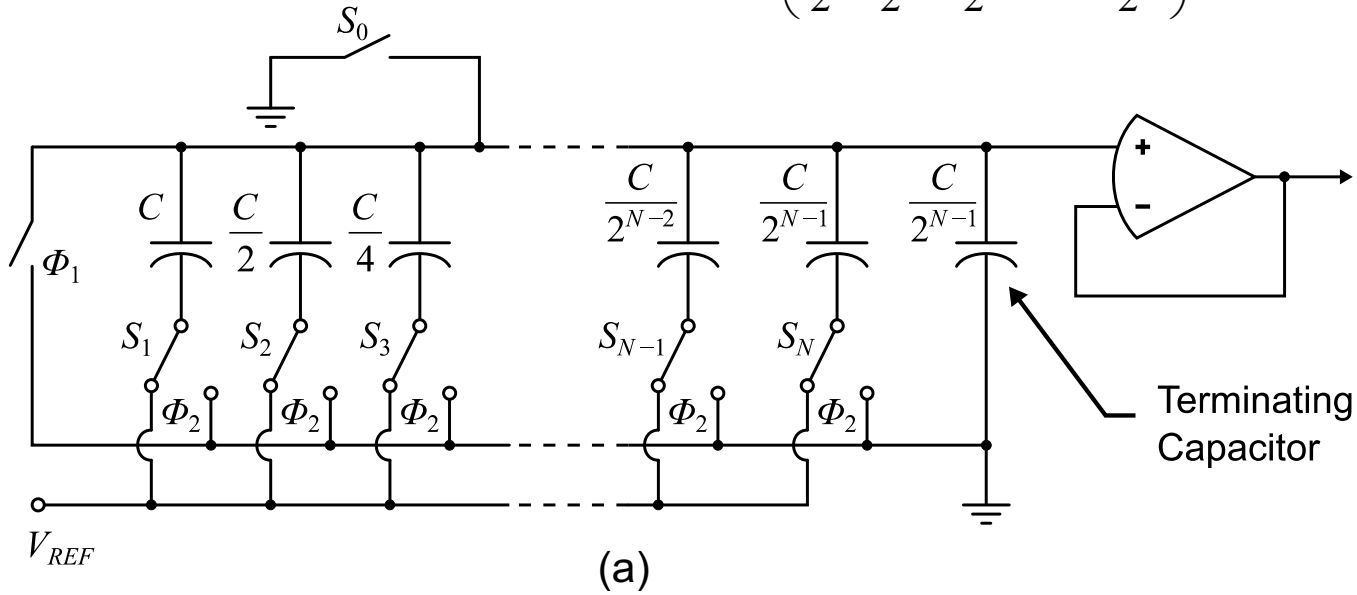
$$V_{REF} \left( \frac{b_1}{2} + \frac{b_2}{2^2} + \frac{b_3}{2^3} + \dots + \frac{b_N}{2^N} \right) = V_{OUT}$$



(a) Charge-scaling D/A converter. Switches  $S_i$  close to  $V_{ref}$  if  $b_i = 1$  or ground if  $b_i = 0$  during  $\Phi_2$ . All switches are connected to ground during  $\Phi_1$ .

(b) Equivalent circuit of (a).



$$C_{MAX} = C + \Delta C$$

$$C_{MIN} = C - \Delta C$$

Worst-case output for the  $i$ th capacitor

$$v_{out}(actual) = \frac{(C \pm \Delta C)/2^{i-1}}{2C} V_{REF} = \frac{V_{REF}}{2^i} \pm \frac{\Delta C \cdot V_{REF}}{2^i C} = \frac{2^N}{2^i} \pm \frac{2^N \Delta C}{2^i C} LSBs$$

The  $INL$  for the  $i$ th-bit is give as

$$INL(i) = v_{out}(actual) - v_{out}(ideal) = \frac{\pm 2^N \Delta C}{2^i C} = \frac{\pm 2^{N-i} \Delta C}{C} LSBs$$

The worst-case occurs for  $i=1$

$$INL = \pm 2^{N-1} \frac{\Delta C}{C} LSBs$$


The worst-case DNL for the binary-weighted capacitor arrays is found when the MSB changes.

$$v_{OUT} = \frac{C_{eq}}{(2C - C_{eq}) + C_{eq}} v_{REF}$$


$C_{eq}$  represents the capacitors whose bits are 1 and  $(2C - C_{eq})$  represents the capacitors whose bits are 0. The worst-case DNL can be expressed as

$$DNL = \frac{v_{step}(worst\ case)}{v_{step}(ideal)} - 1 = \frac{v_{OUT}(1000....) - v_{OUT}(0111....)}{LSB} - 1$$

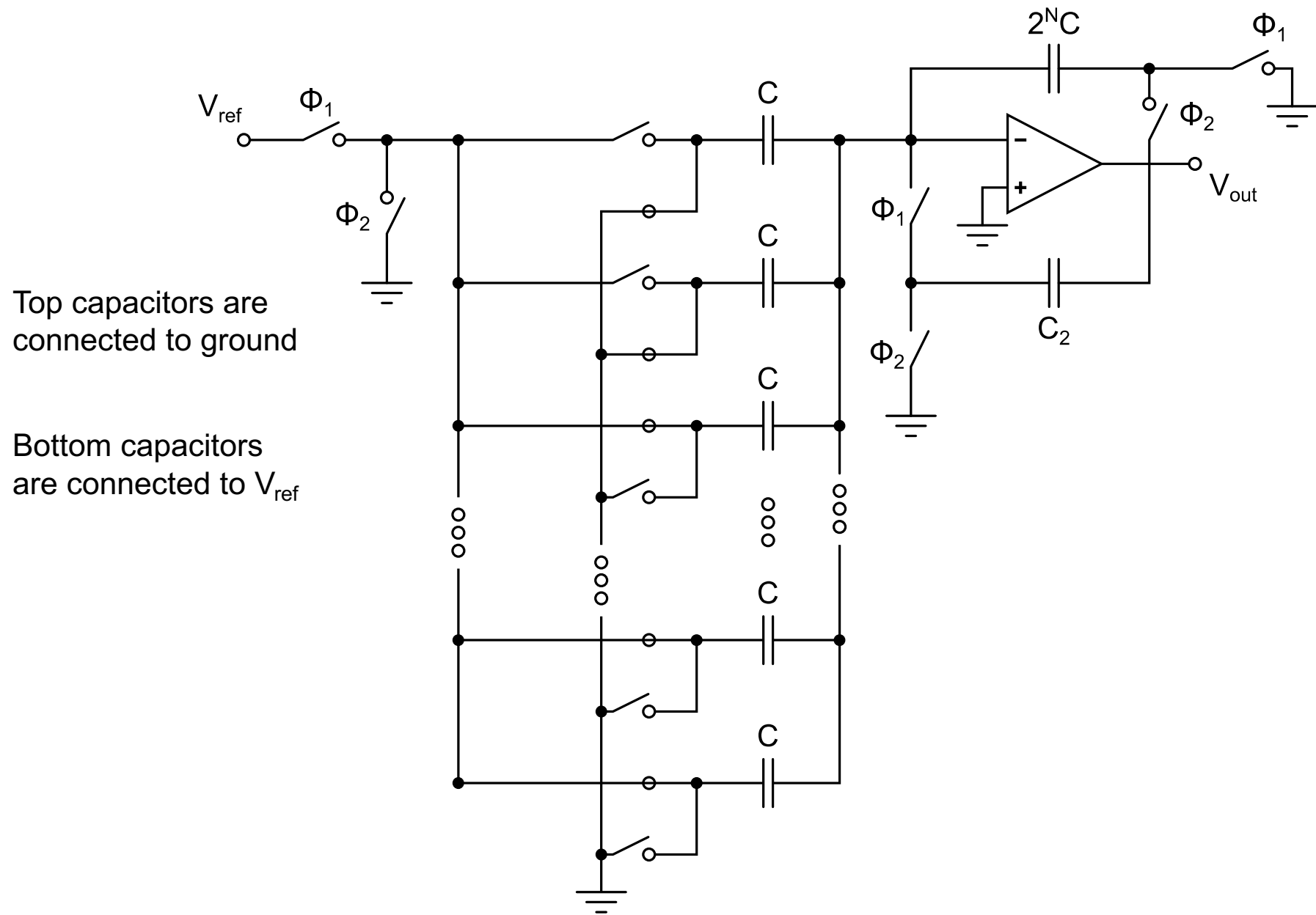
$$= \frac{\left( \frac{C + \Delta C}{(C + \Delta C) + (C - \Delta C)} \right) v_{REF} - \left( \frac{(C + \Delta C) \left( 1 - \frac{2}{2^N} \right)}{(C + \Delta C) + (C - \Delta C)} \right) v_{REF}}{\frac{v_{REF}}{2^N}} - 1 = 2^N \left( \frac{C + \Delta C}{2C} \right) - 2^N \left( \frac{C - \Delta C}{2C} \right) \left( 1 - \frac{2}{2^N} \right) - 1 = (2^N - 1) \frac{\Delta C}{C} LSBs$$



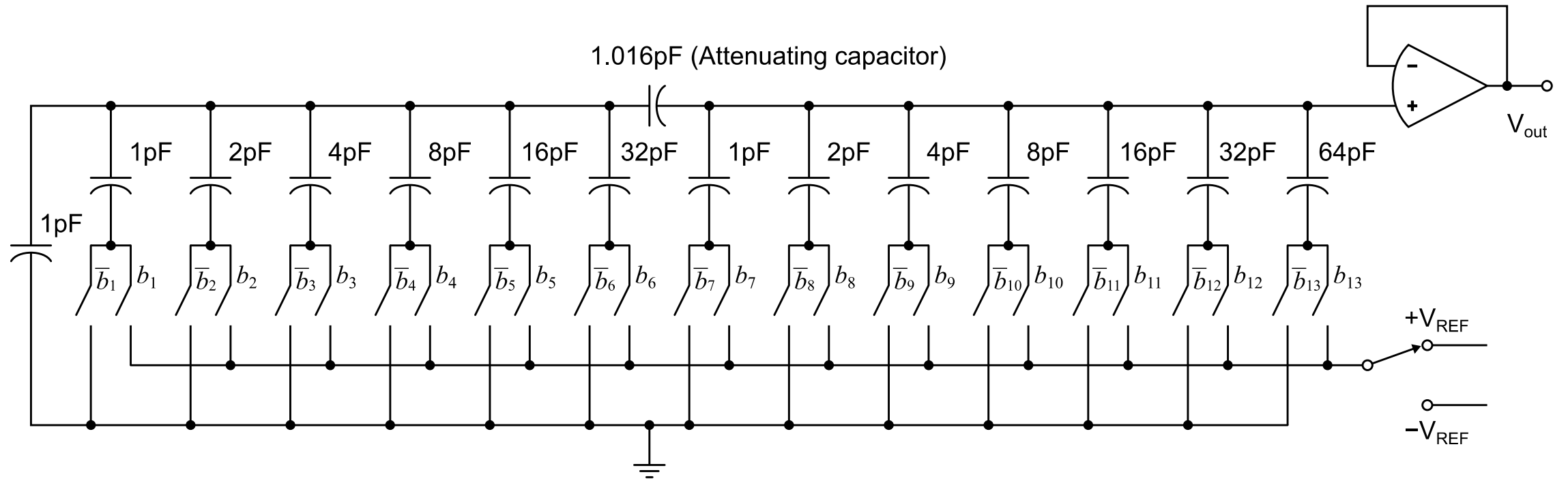
Thermometer-code charge-redistribution D/A converter.



 A 13-bit two-stage MDAC. Note that whether or not the  $\phi_2$  switches close depends upon the state of the binary variable,  $b_1$ .




An equivalent circuit of (a).

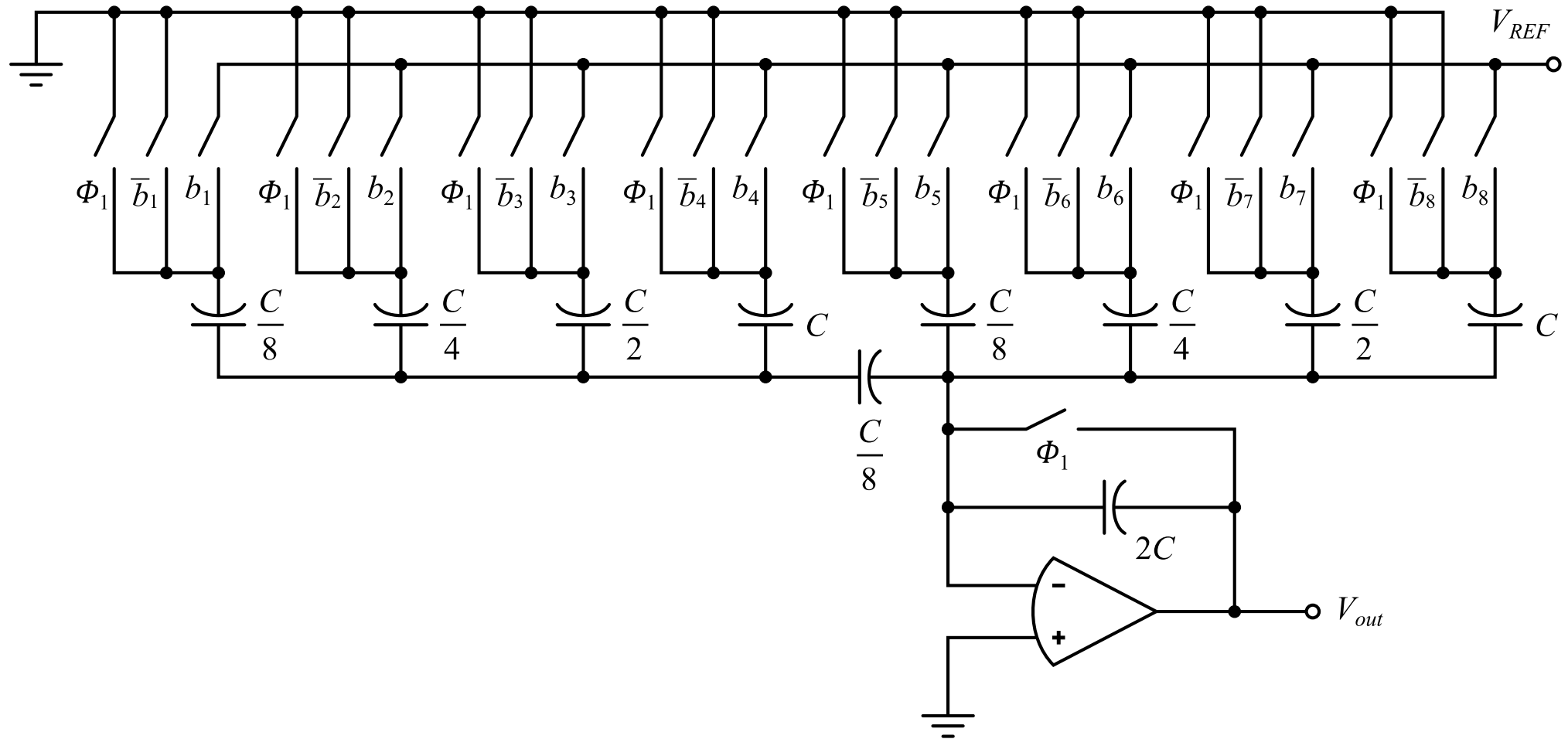

A charge-scaling D/A converter that is insensitive to nodal-capacitive parasitics.
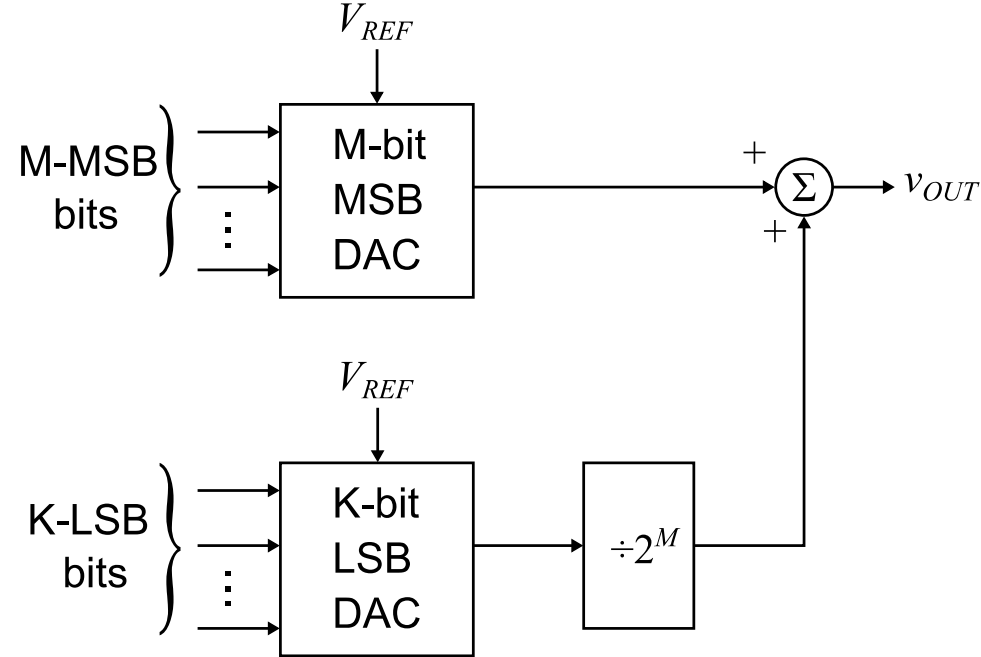
## Combining of M-bit and K-bit subDAC to form an M+K-bit DAC




$$v_{OUT} = \left( \frac{b_0}{2} + \frac{b_1}{4} + \dots + \frac{b_{M-1}}{2^M} \right) V_{REF} + \left( \frac{1}{2^M} \right) \left( \frac{b_M}{2} + \frac{b_{M+1}}{4} + \dots + \frac{b_{M+K-1}}{2^K} \right) V_{REF}$$

or

$$v_{OUT} = \left( \frac{b_0}{2} + \frac{b_1}{4} + \dots + \frac{b_{M-1}}{2^M} + \frac{b_M}{2^{M+1}} + \frac{b_{M+1}}{2^{M+2}} + \dots + \frac{b_{M+K-1}}{2^{M+K}} \right) V_{REF}$$
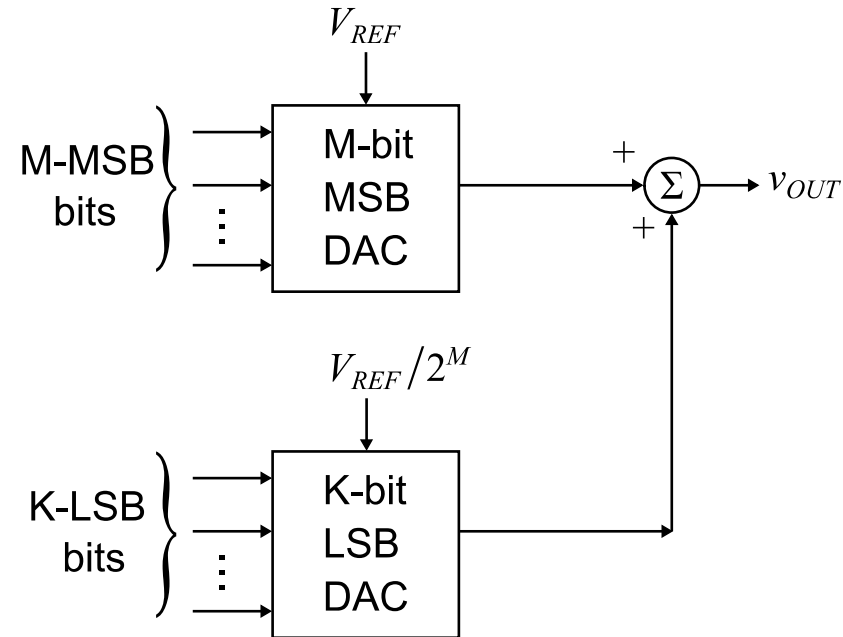
## Combining of M-bit and K-bit subDAC to form an M+K-bit DAC by dividing the $V_{REF}$




$$v_{OUT} = \left( \frac{b_0}{2} + \frac{b_1}{4} + \dots + \frac{b_{M-1}}{2^M} \right) V_{REF} + \left( \frac{b_M}{2} + \frac{b_{M+1}}{4} + \dots + \frac{b_{M+K-1}}{2^K} \right) \left( \frac{V_{REF}}{2^M} \right)$$

or


$$v_{OUT} = \left( \frac{b_0}{2} + \frac{b_1}{4} + \dots + \frac{b_{M-1}}{2^M} + \frac{b_M}{2^{M+1}} + \frac{b_{M+1}}{2^{M+2}} + \dots + \frac{b_{M+K-1}}{2^{M+K}} \right) V_{REF}$$
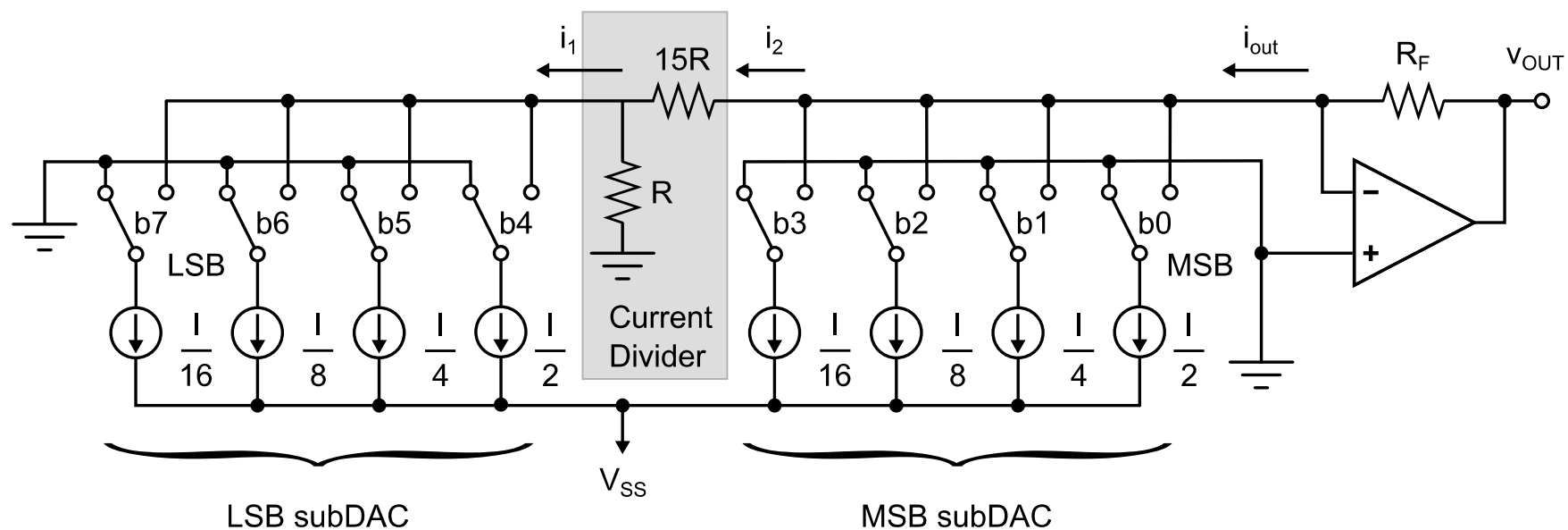
# Combination of current scaling subDACs using a current divider




- current division by  $\frac{R}{R+15R}$  for LSB subDAC
- wasted power

 Use current multiplier between LSB and MSB current sources






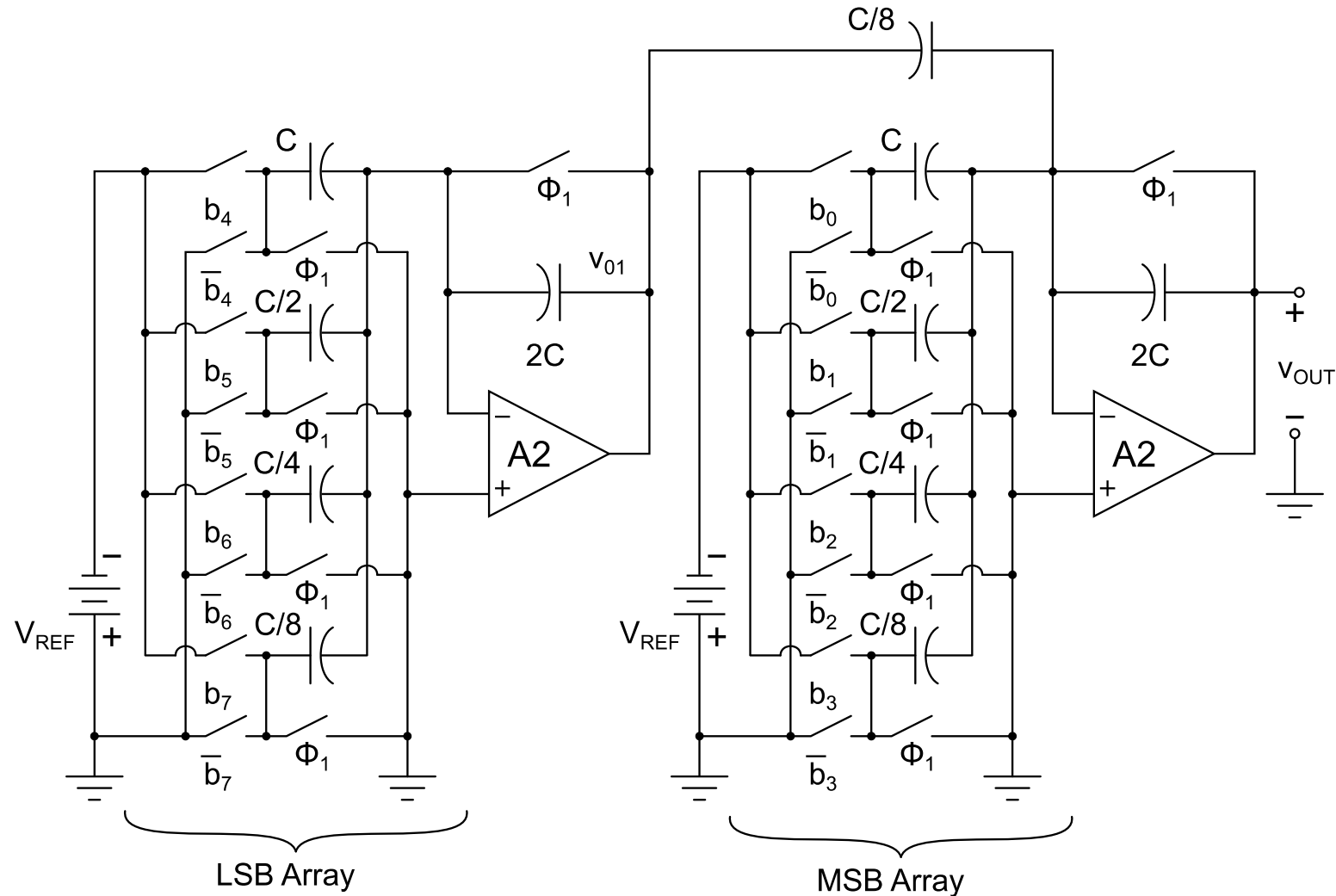Combination of two 4-bit, binary-weighted, charge amplifier subDACs to form an 8-bit, binary-weighted




   
# Operation of the serial charge-redistribution DAC



$$C_1 = C_2$$

$$b_0 = 1, b_1 = 1, b_2 = 0, b_3 = 1$$