

Clicker lecture 2 of Topic 2: Smith chart and impedance matching


31 Jan, 2019

Registration

Go with your mobile phone to
premo.aalto.fi/mwe1

Fill your full name into the text field for registration.

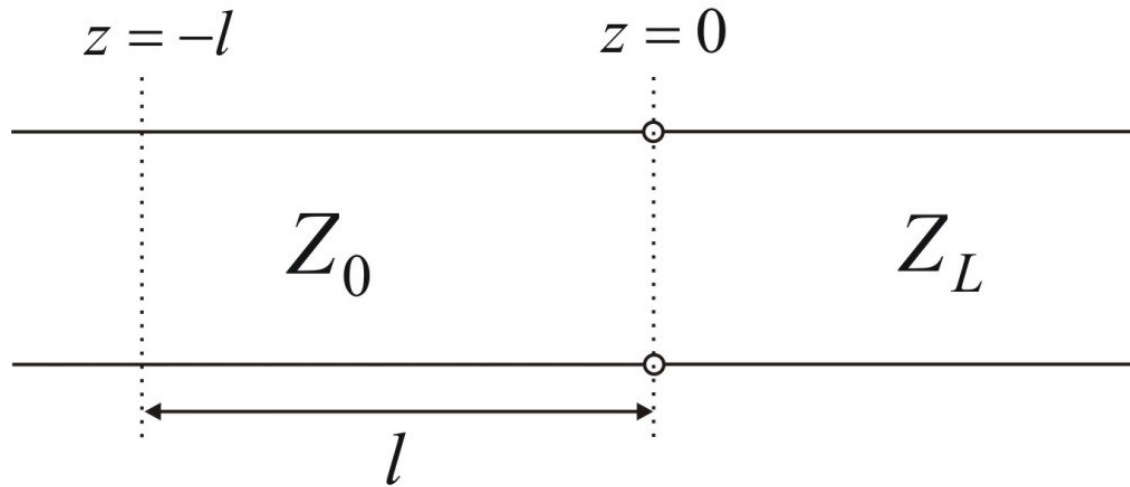
Q1a: The signal propagates to the positive z direction. $Z_0 \neq Z_L$. How much (%) of the **power** is transmitted to the line whose impedance is Z_L



$$\begin{aligned} Z_L &= 2.0 \, \Omega \\ Z_0 &= 1.0 \, \Omega \end{aligned}$$

1. 11 %
2. 33%
3. 66%
4. 89%
5. None of above
6. I don't know

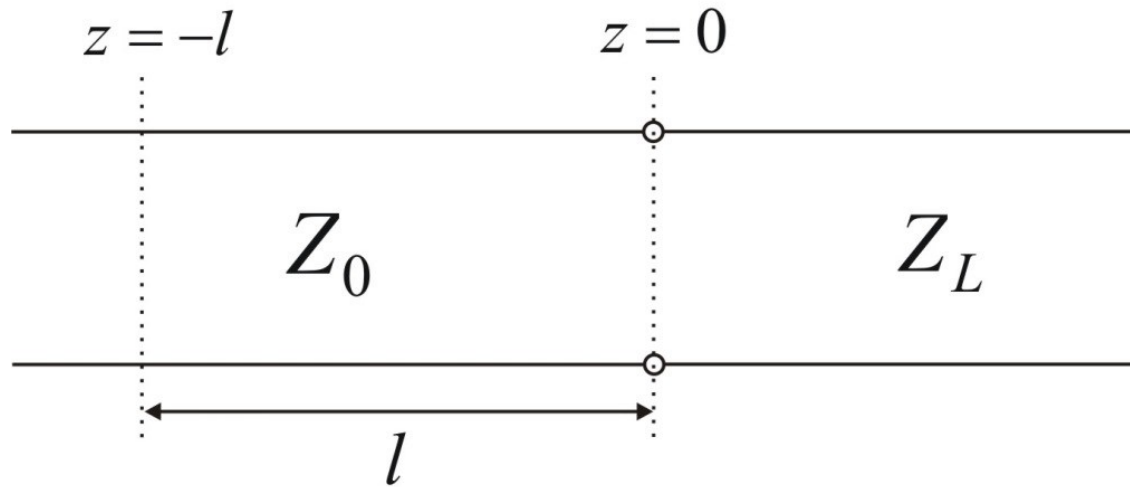Q1b: The signal propagates to the positive z direction. $Z_0 \neq Z_L$. How much (%) of the **power** is transmitted to the line whose impedance is Z_L



$$\begin{aligned} Z_L &= 2.0 \, \Omega \\ Z_0 &= 1.0 \, \Omega \end{aligned}$$

1. 11 %
2. 33%
3. 66%
4. 89%
5. None of above

$\rho = -1$

If impedance plane: $z = 0 \rightarrow$ short circuit

If admittance plane: $y = 0 \rightarrow$ open circuit

direction
towards
generator

inductive
reactance
or
capacitive
susceptance

capacitive
reactance
or
inductive
susceptance

$\rho = +1$

If impedance plane: $z = \infty \rightarrow$ open circuit


If Admittance plane: $y = \infty \rightarrow$ short circuit

Centre: $\rho = 0$
matched load
 r or $g = 1$ and x or $b = 0$,



$u =$
 $\text{Re}\{\rho\}$

$v = \text{Im}\{\rho\}$

$r = 1$
circle


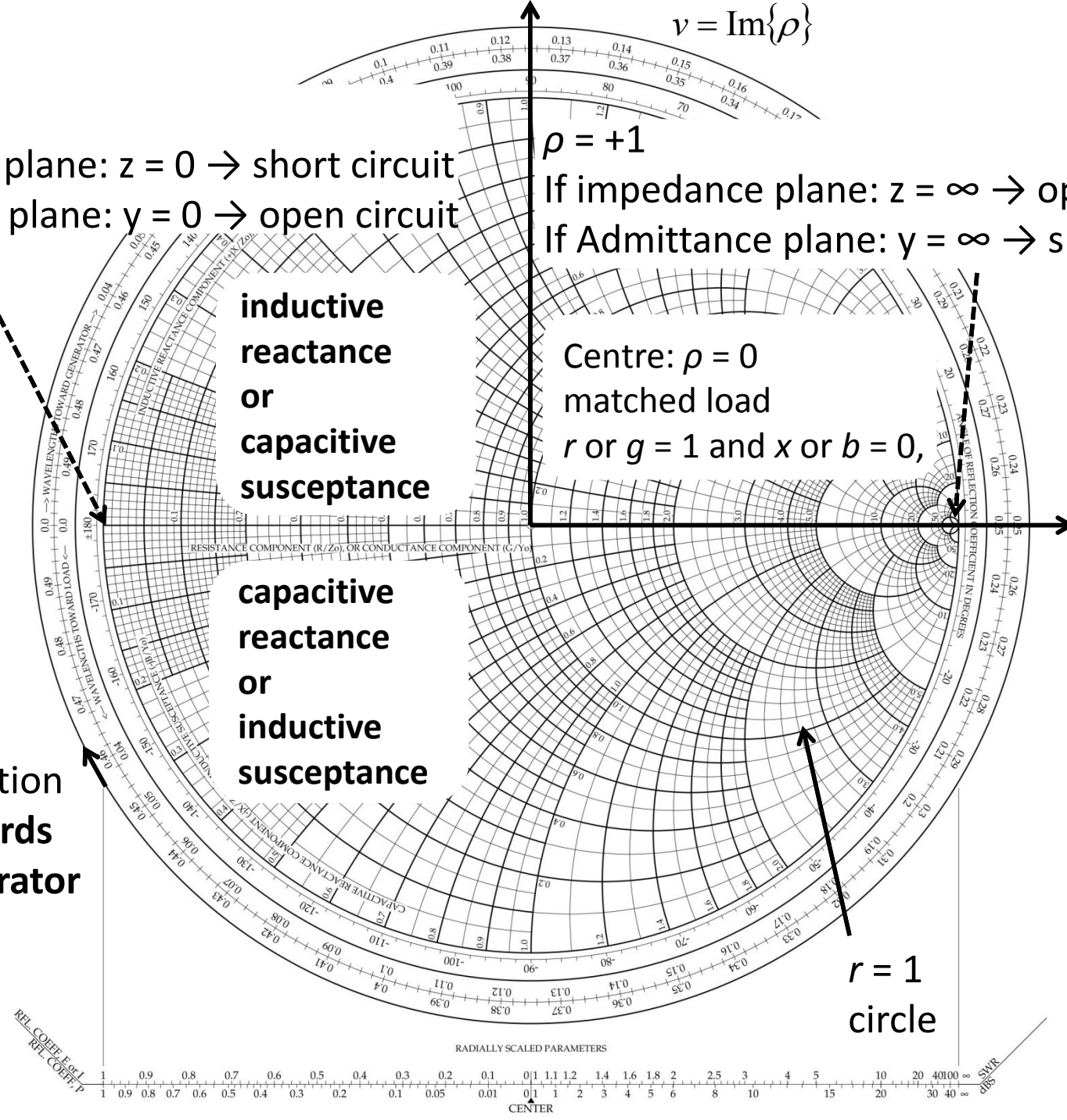


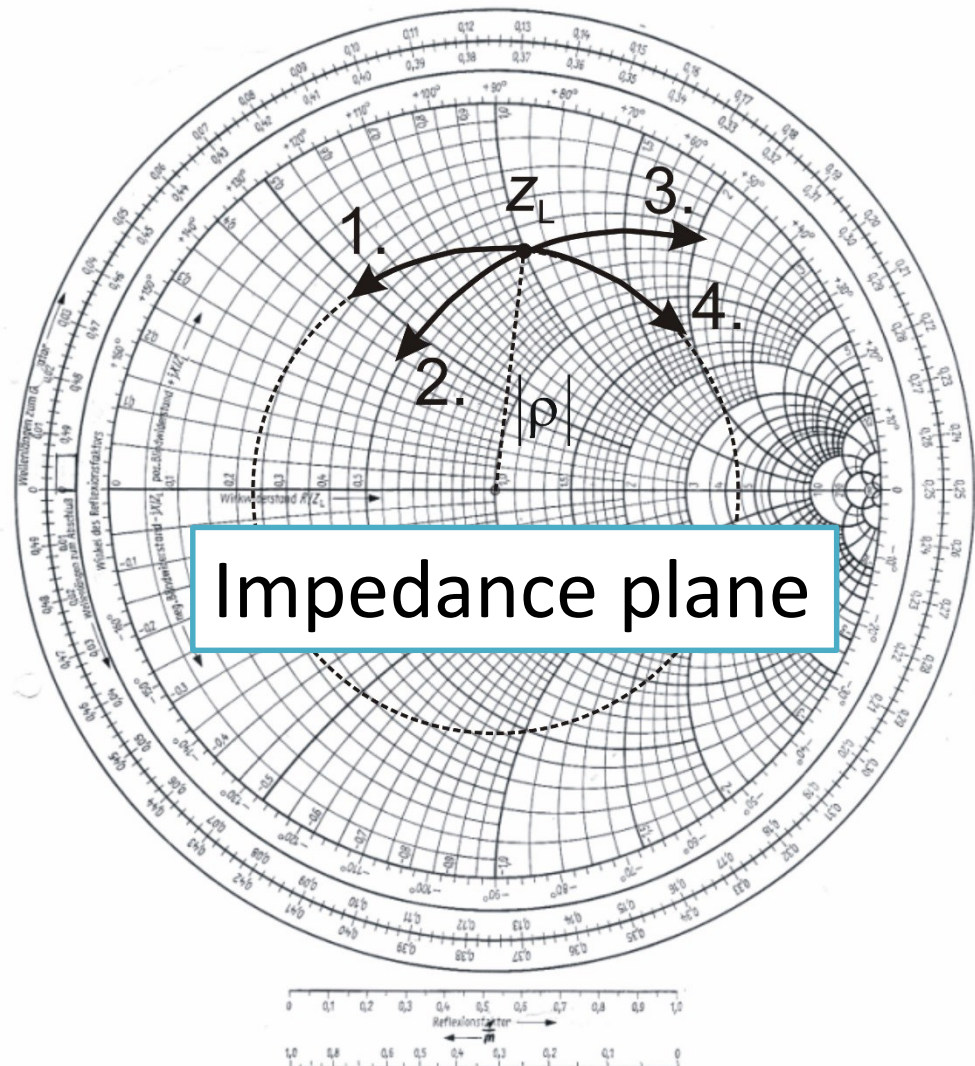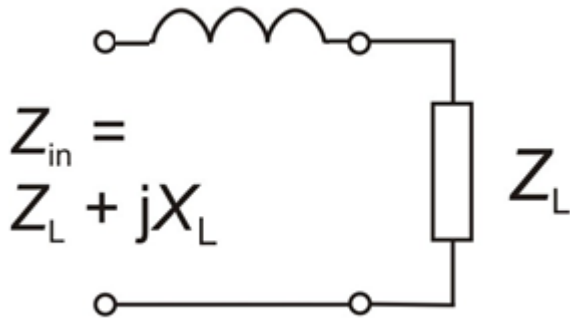Q2a: Which of the following transitions on the Smith chart (1-5) corresponds to adding a **series inductor** in the **impedance plane**?





5. None of them
6. I don't know

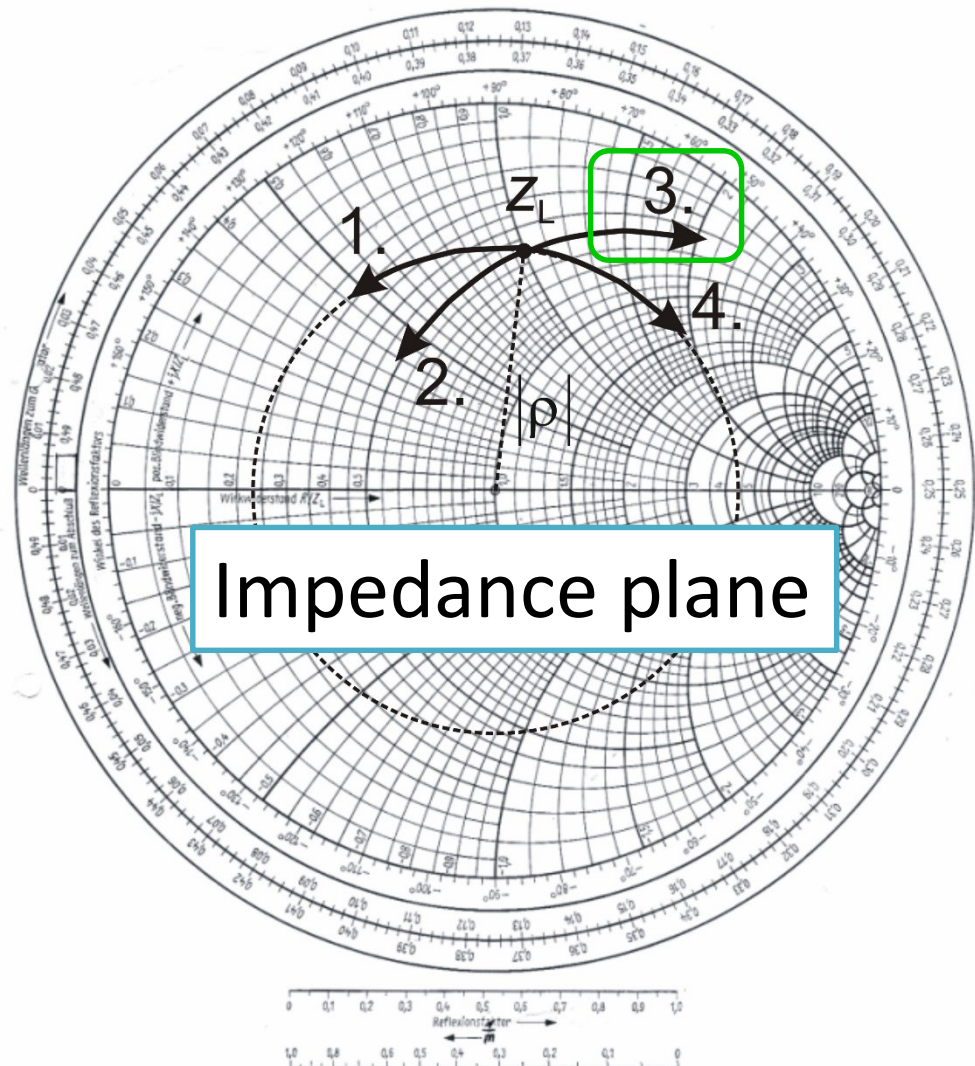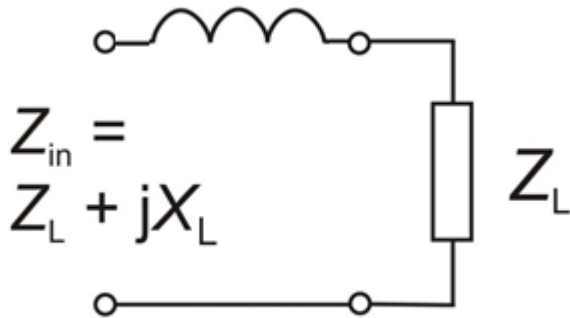Q2b: Which of the following transitions on the Smith chart (1-5) corresponds to adding a **series inductor** in the **impedance plane**?





5. None of them

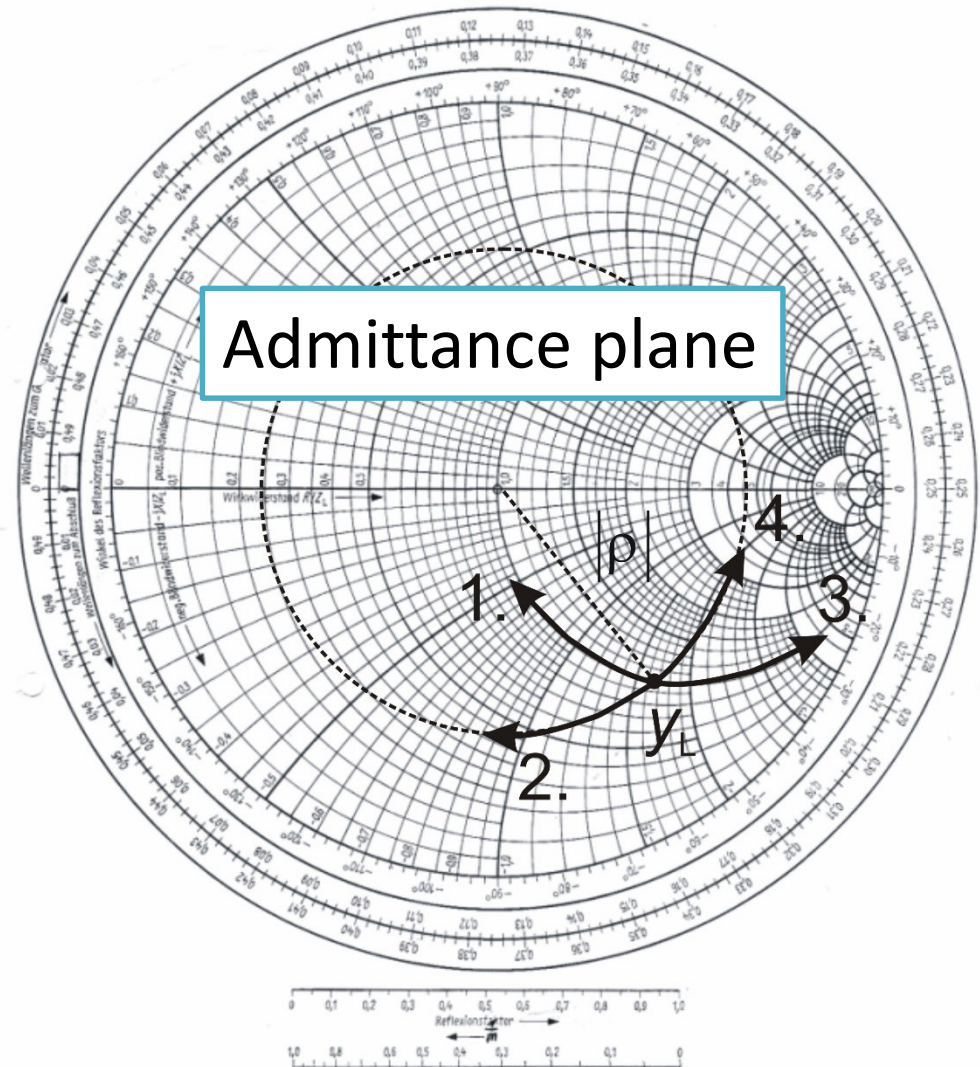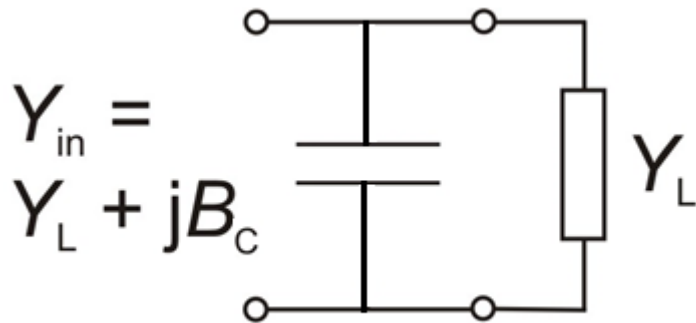Q3a: Which of the following transitions on the Smith chart (1-5) corresponds to adding a **parallel capacitor** in the **admittance plane**?





5. None of them
6. I don't know

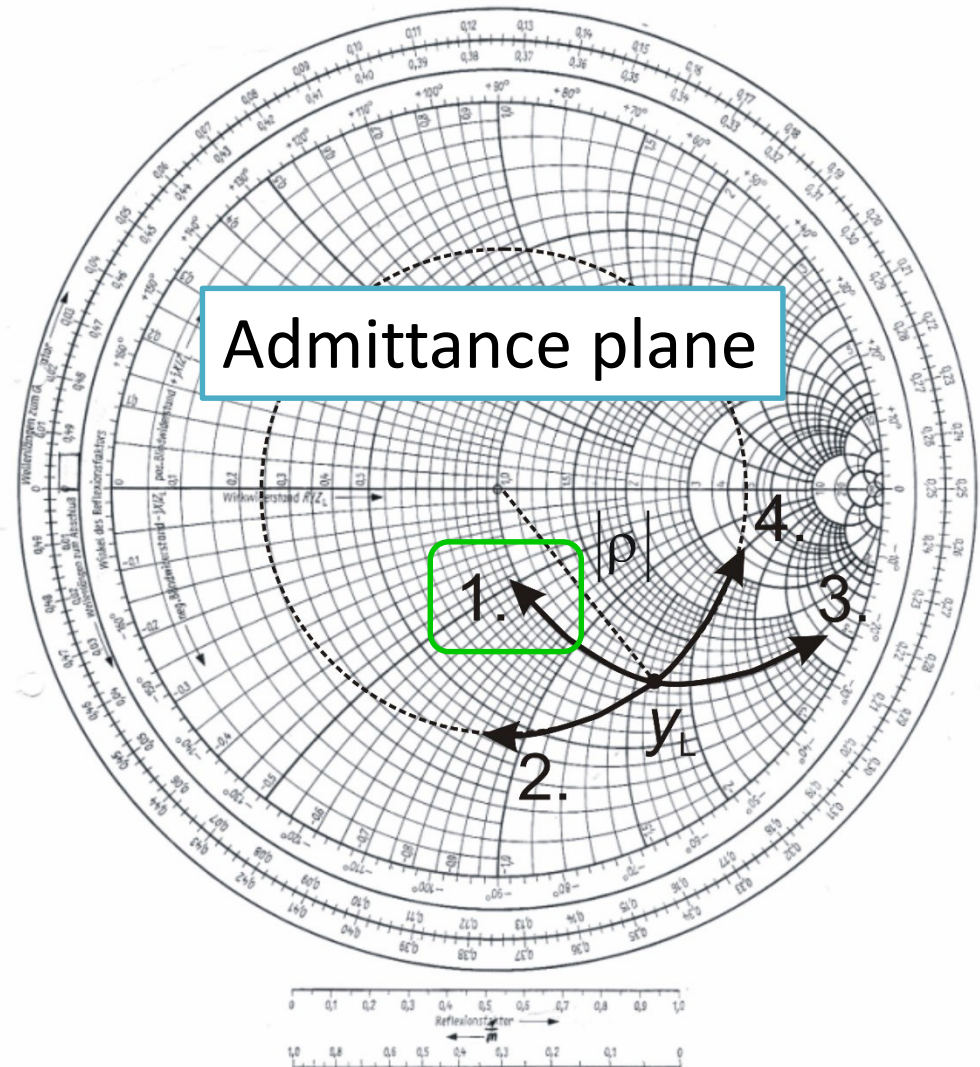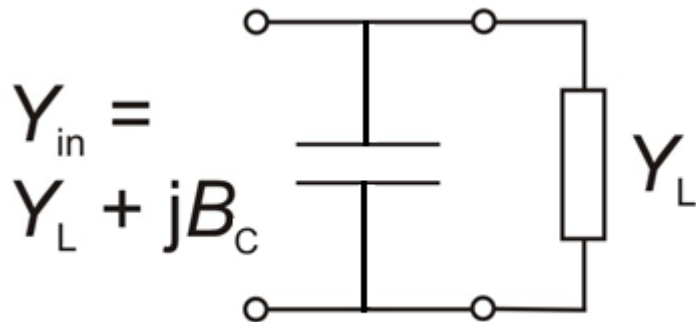Q3b: Which of the following transitions on the Smith chart (1-5) corresponds to adding a **parallel capacitor** in the **admittance plane**?





5. None of them

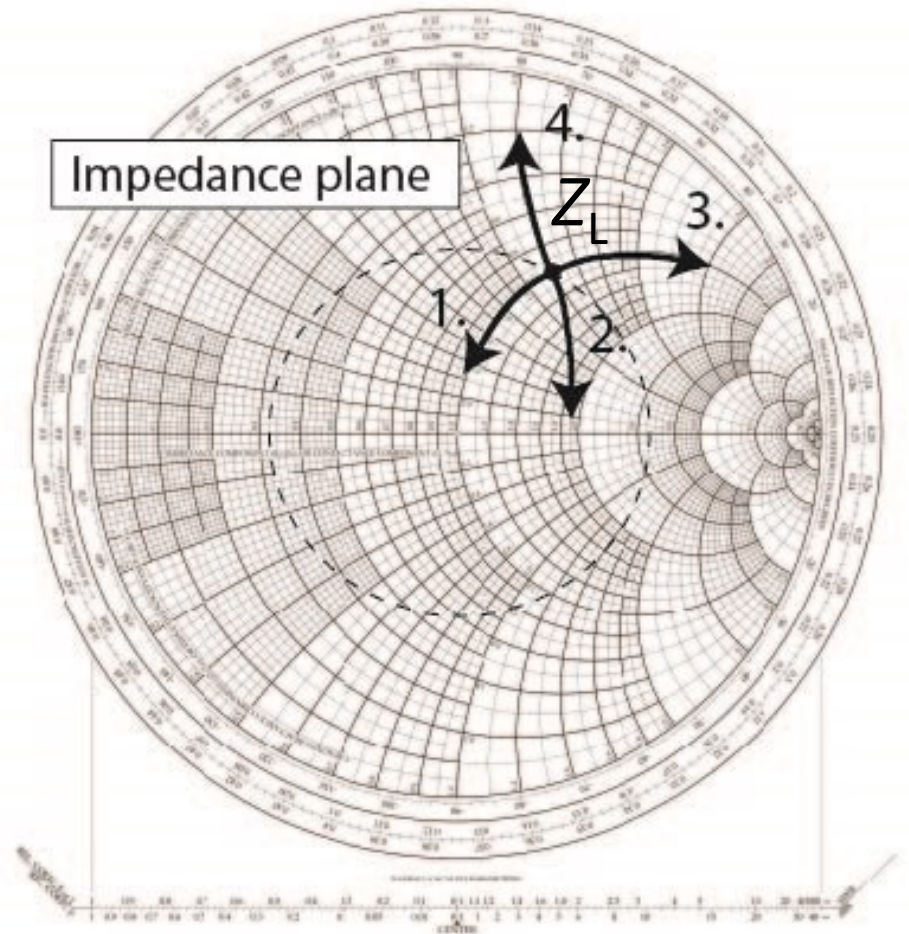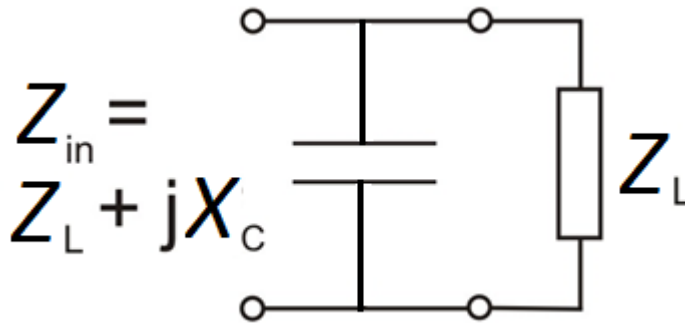Q4a: Which of the following transitions on the Smith chart (1-4) corresponds to adding a **parallel capacitor** in the **impedance plane**?



- 5. None of above
- 6. I don't know




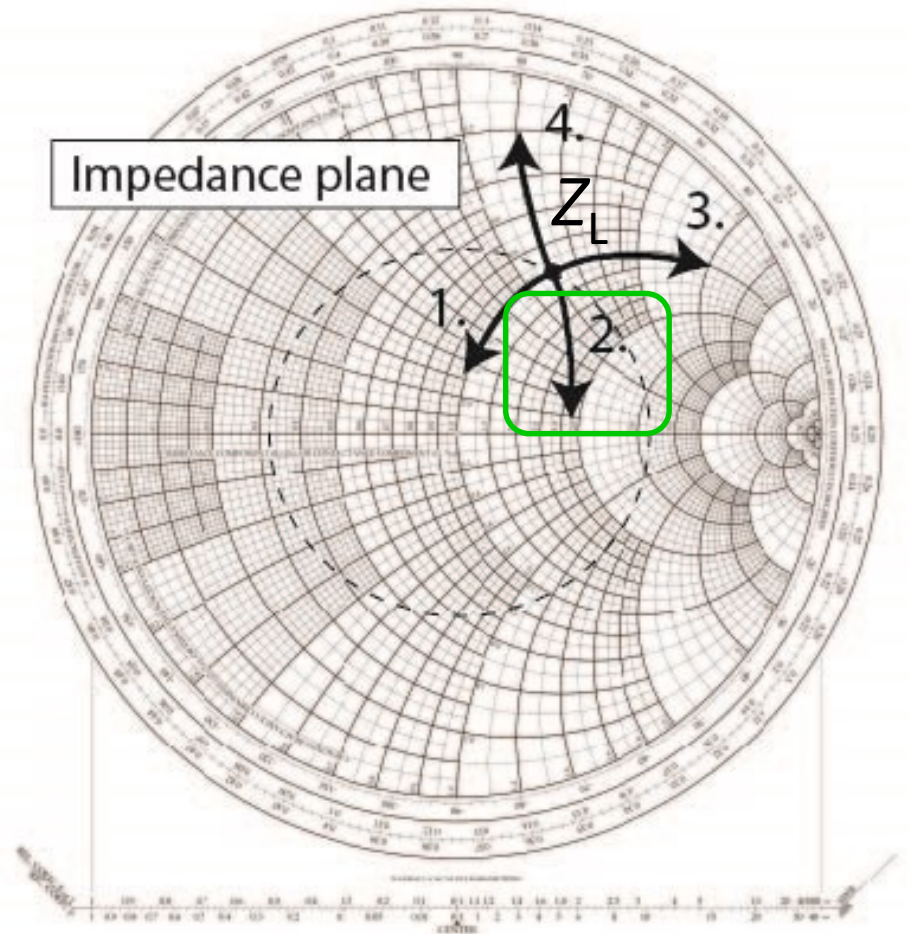
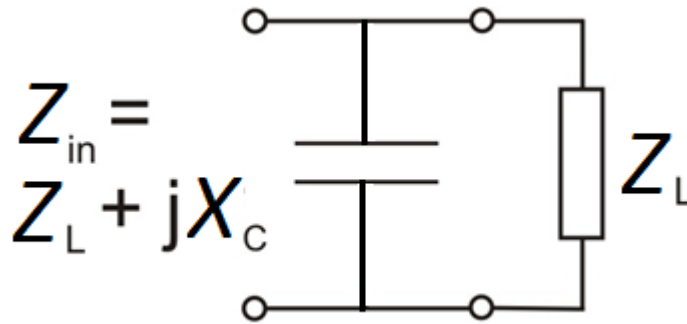
Q4b: Which of the following transitions on the Smith chart (1-4) corresponds to adding a **parallel capacitor** in the impedance plane?



5. None of above


Q5: Which of the following lumped element L-section matching circuits (1-4) is/are **suitable** for matching Z_L ?

Choose one or more.

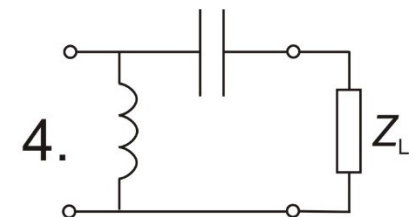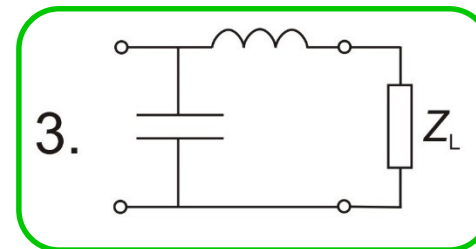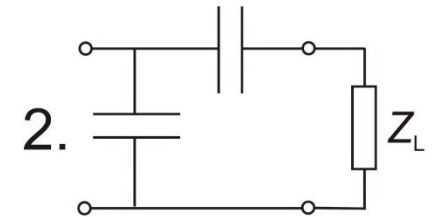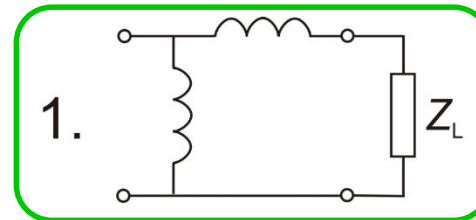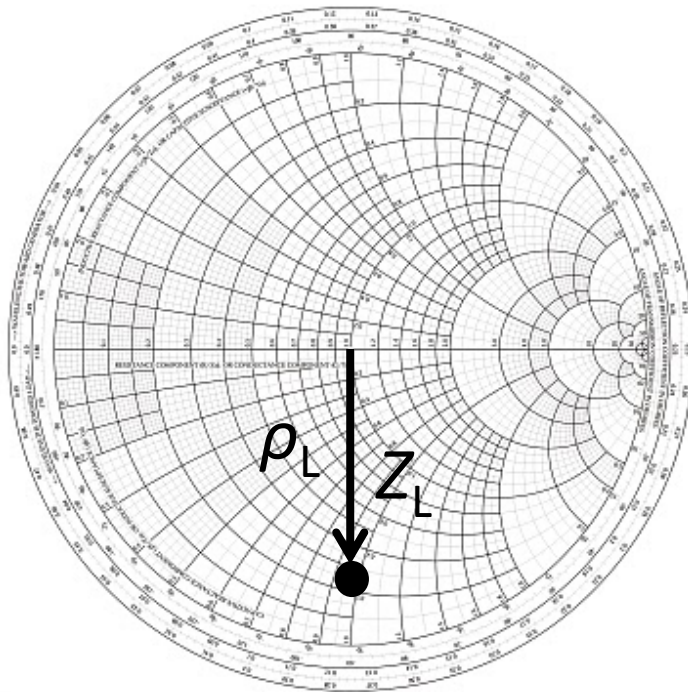

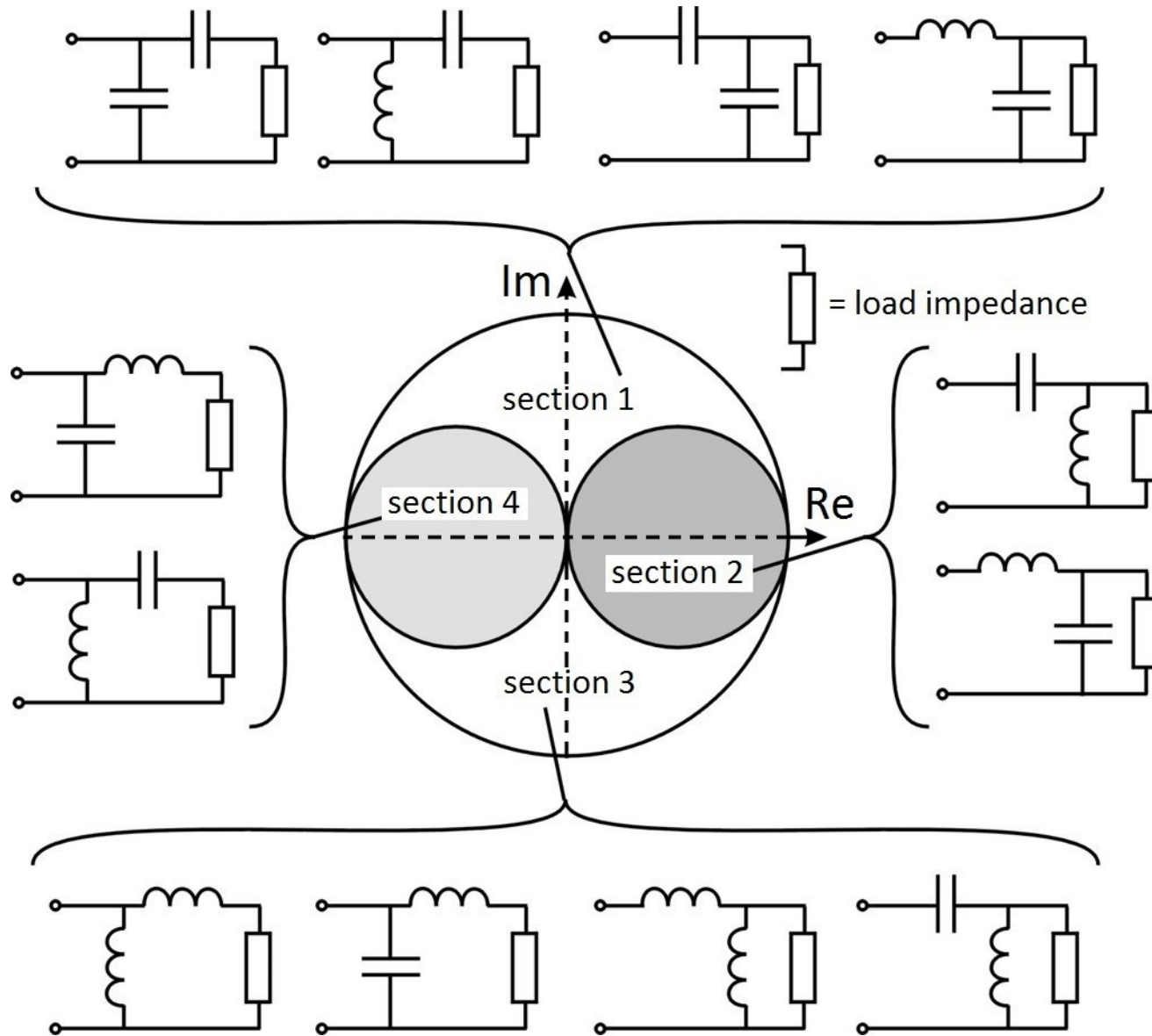5. None of them
6. I don't know



Lumped-element L-section matching circuit topologies



Q6: Which of the following transitions on the Smith chart (1-4) can correspond to adding a **transmission line**?



Choose one or more.

- 5. None of them
- 6. I don't know

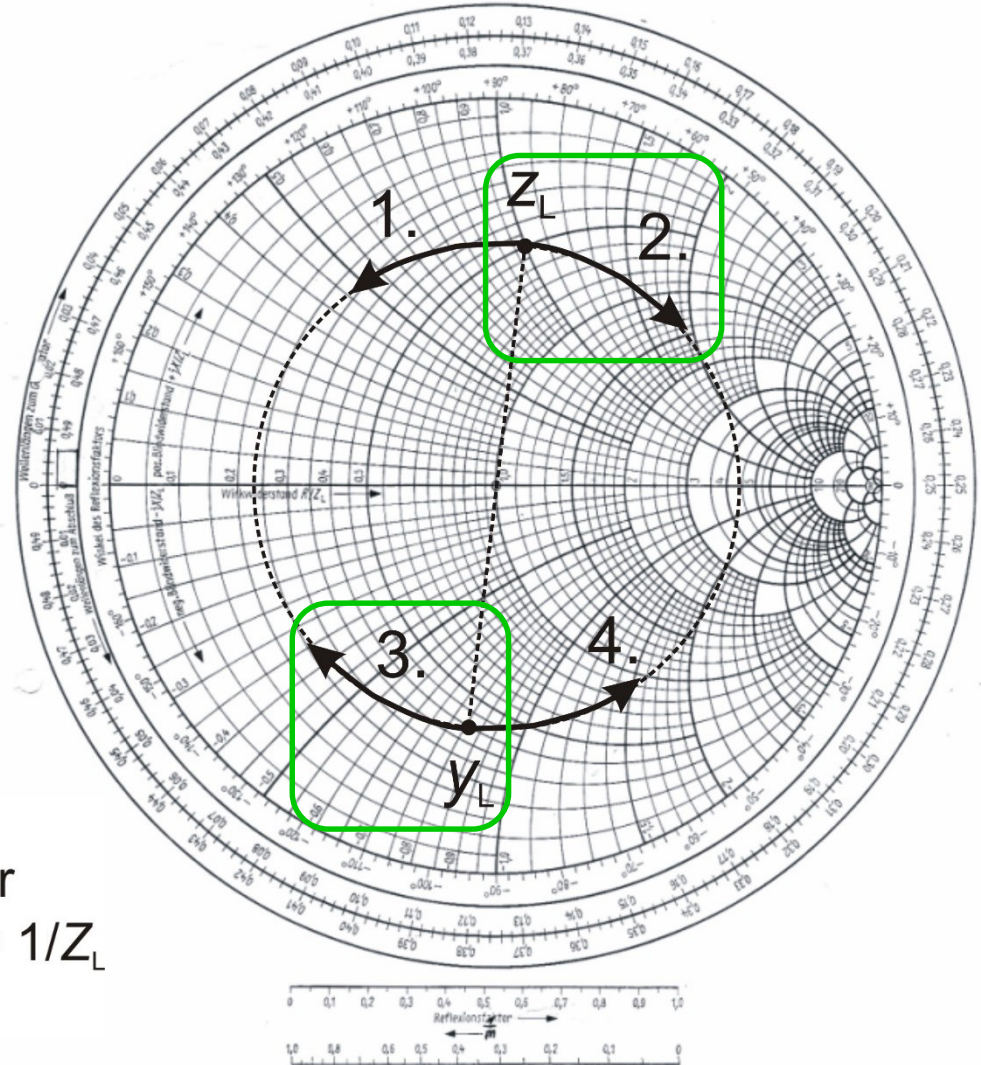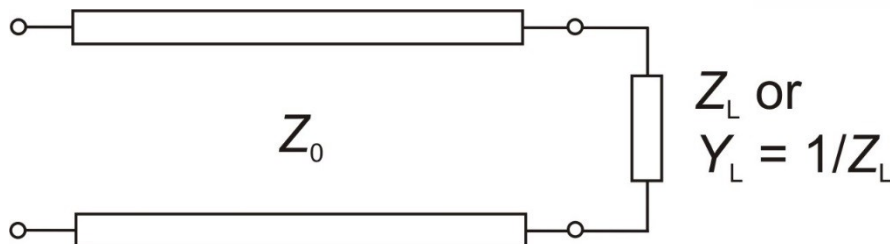

Q7a: The normalised admittance of a **short-circuited** stub is $\mathbf{y} = \mathbf{j}b = -\mathbf{j}$ (seen from the input) . What is the length of the stub in λ ?

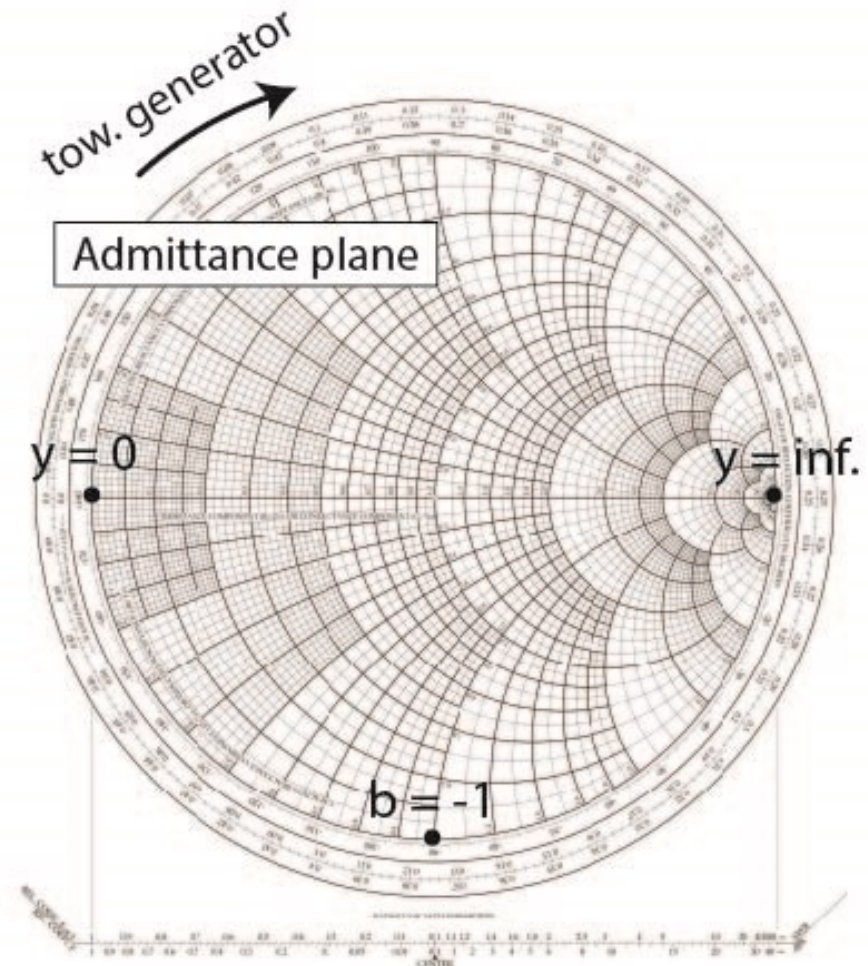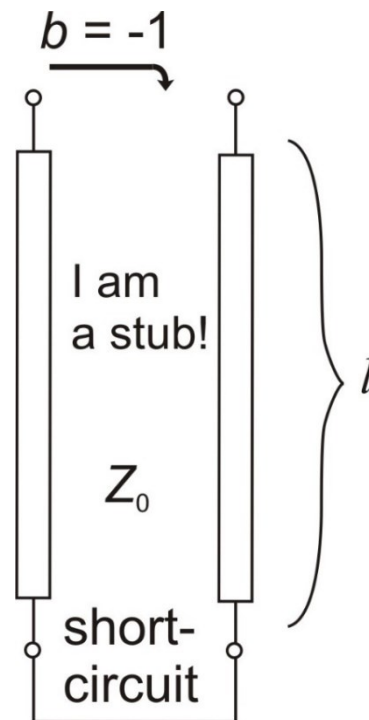1. 0.0624λ
2. 0.125λ
3. 0.25λ
4. 0.375λ
5. 0.50λ
6. I don't know



Q7b: The normalised admittance of a **short-circuited** stub is $\mathbf{y} = \mathbf{j}b = -\mathbf{j}$ (seen from the input) . What is the length of the stub in λ ?



1. 0.0624λ

2. 0.125λ

3. 0.25λ

4. 0.375λ


5. 0.50λ

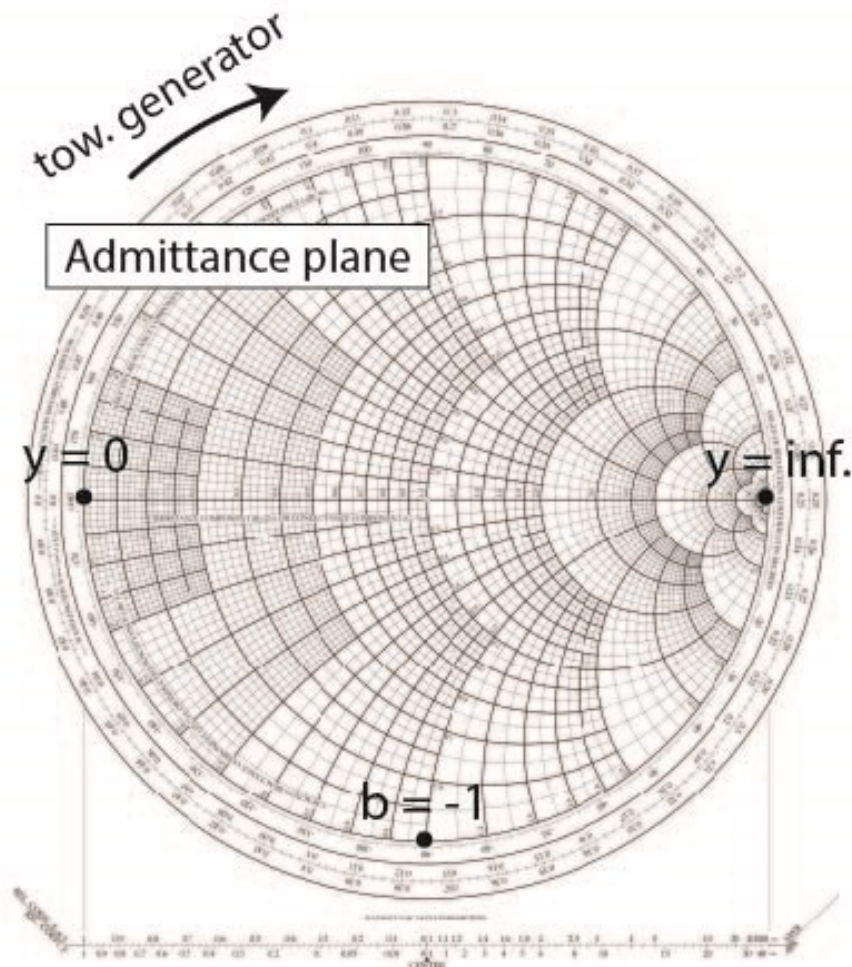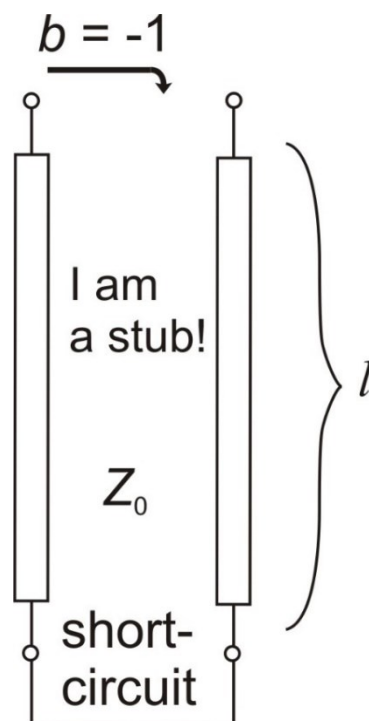

Frequency response

Read: "Quantity" (in dB) is presented as a function of frequency.
or

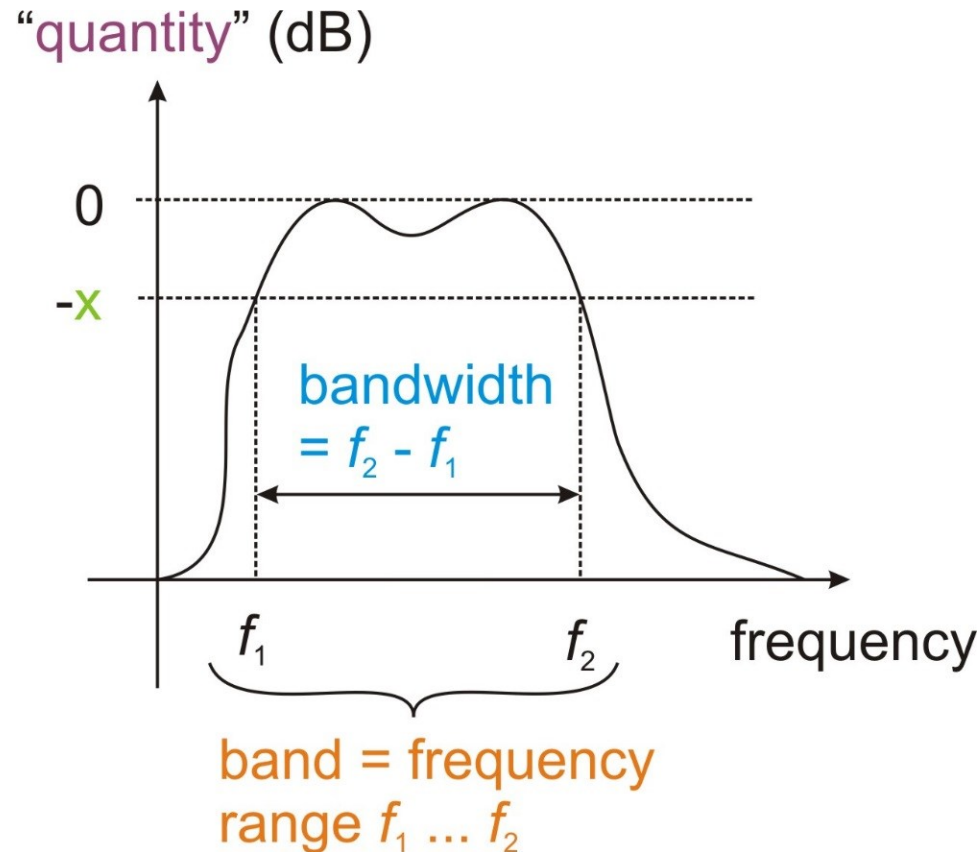
Read: The frequency response of "quantity" in the decibel scale



Band or Bandwidth?

- **Band** is a range of frequencies, for instance, **2.4 ... 2.5 GHz**
- The corresponding **bandwidth** (= the width of the band): **100 MHz** (= $2.5 - 2.4$ GHz)

“quantity” (dB)

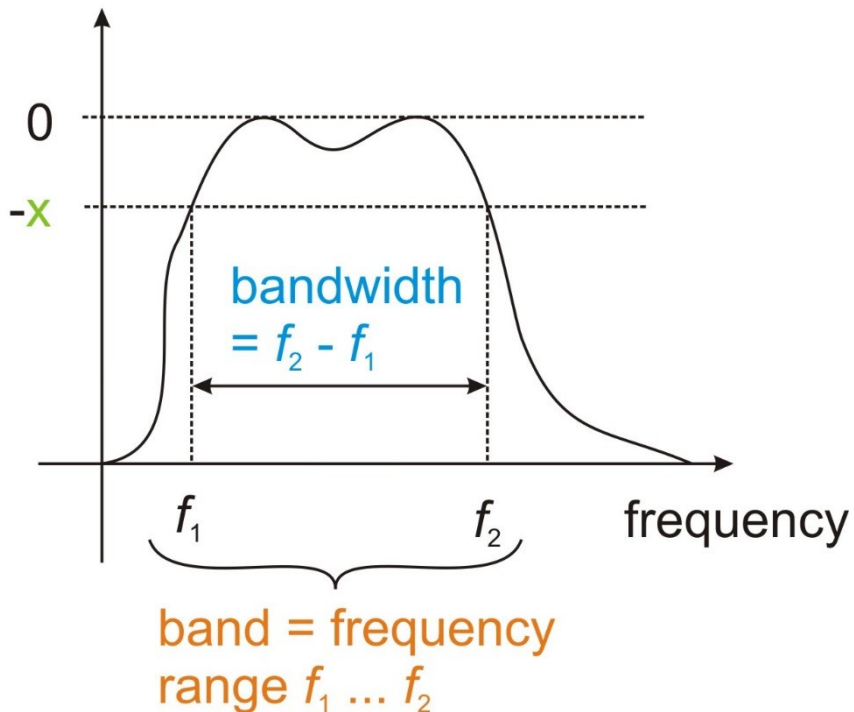

”Quantity” (-)x-dB **bandwidth**

For instance,
amplifier **gain** (-)3-dB **bandwidth**

Means the width of the frequency range where the attenuation of the gain is **less than 3 dB**.

Also called “half-power bandwidth”.