

Clicker lecture 1 of Topic 3:
Resonators and microwave circuits and
network analysis

Feb 7, 2019

Tacoma bridge 1940

- [Tacoma bridge 1940](#) near Seattle
- What went wrong? (Washington, USA)

Today's agenda: we will talk about the resonance phenomenon and microwave filters based on resonant circuits.

Why? Various microwave components (such as *filters, oscillators, microwave cavities, antennas*) are based on the resonance phenomenon.

Registration

Go with your mobile phone to


presemo.aalto.fi/mwe1

Fill your full name into the text field for registration.


Q1: Which of the following is/are **not** related to the resonance phenomenon? Choose one or more.

1. Ability to store energy and transfer energy between two different storage modes. The modes are out-of-phase.
2. Oscillation at the maximum amplitude
3. Outside force
4. Frequency selective operation
5. Losses, e.g. due to friction or resistance, that cause damping
6. A "pure" standing wave in a transmission line
7. Microwave filter
8. Series RLC (resistance inductor capacitor) circuit
9. Forward propagating wave in a transmission line
10. Operation of a half-wave dipole antenna

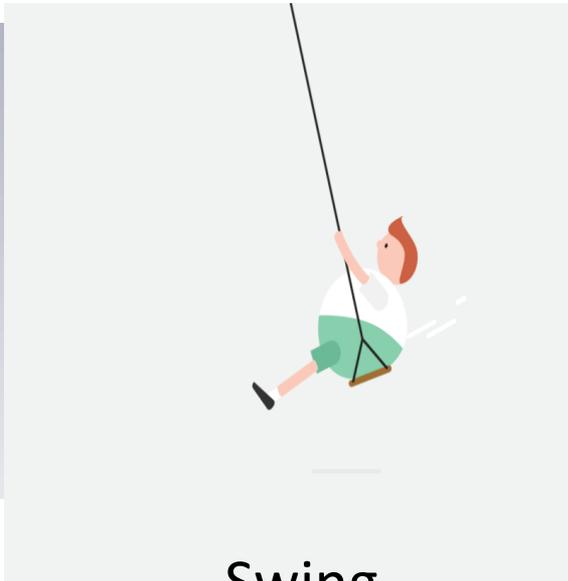
Examples: what are the two storage modes?




Swing

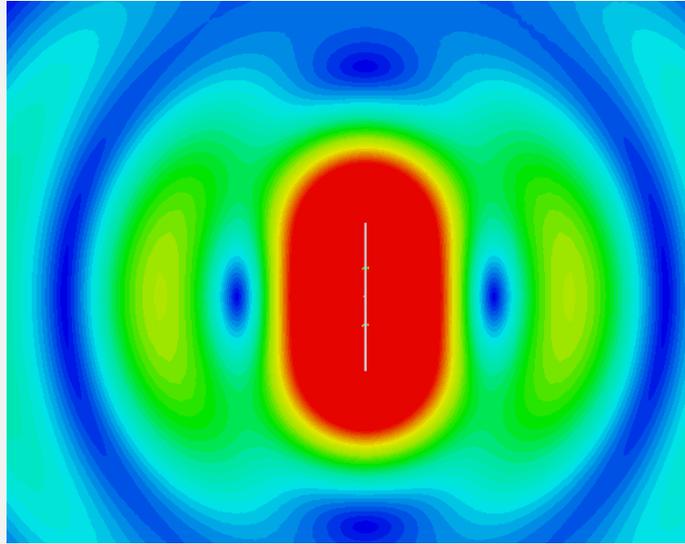

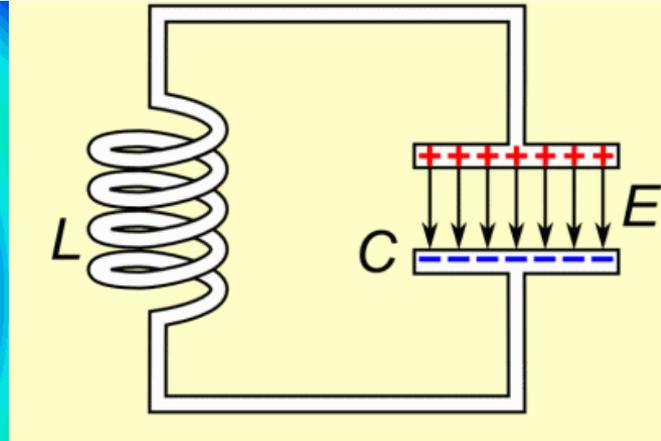A half-wave dipole antenna
(here E field strength shown)



LC resonator circuit

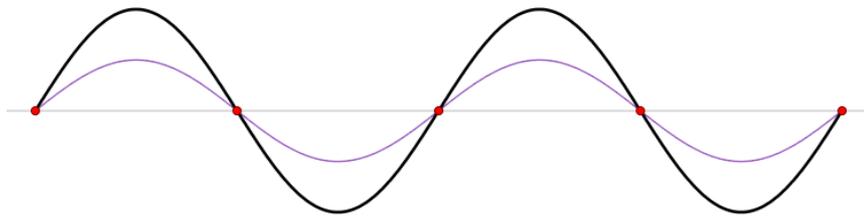


Pure standing wave



Tacoma
bridge
(1940)


Frequency-selective, resonant behaviour

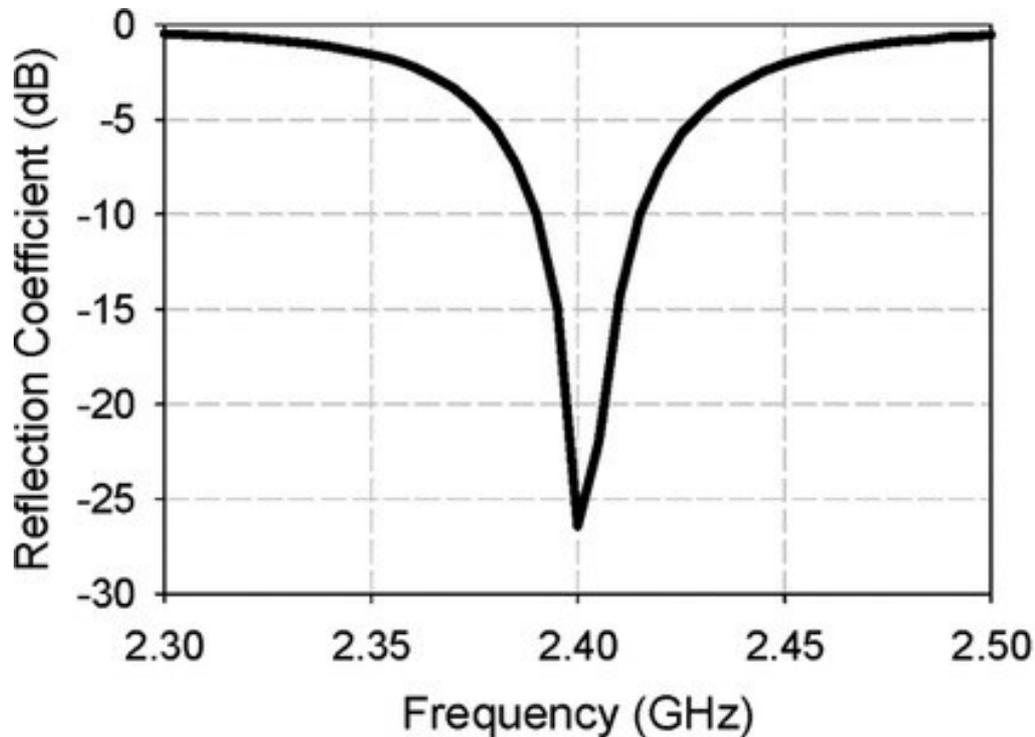One can recognize a resonant behaviour from a strong frequency-selective response like this.



Band or bandwidth?

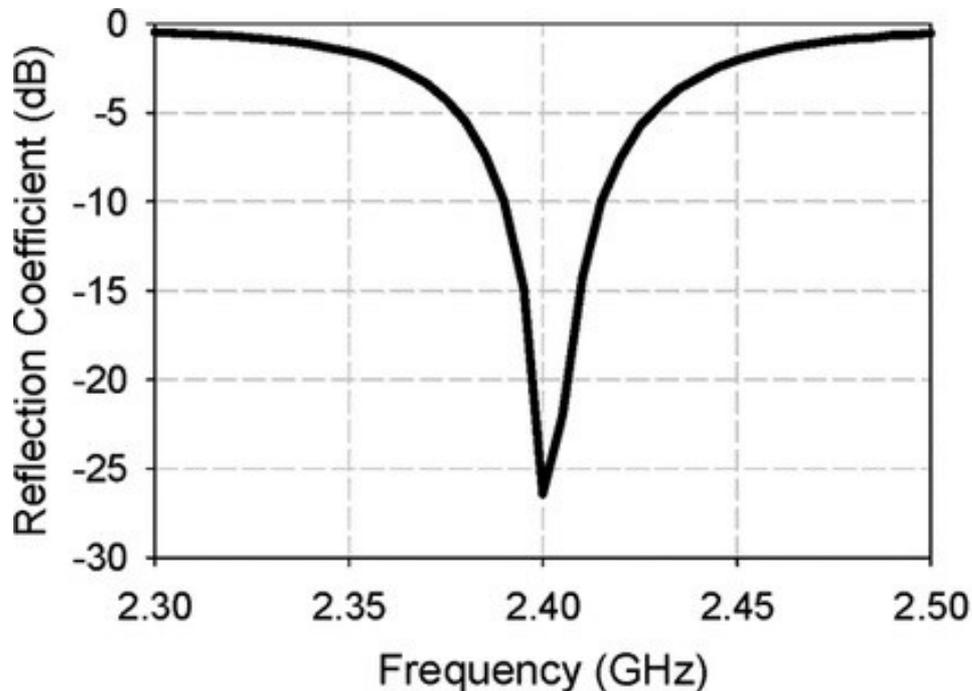- **Band** is a *range of frequencies*, for instance, **2.3 ... 2.5 GHz**
- The corresponding **bandwidth** is the *width of the band*: **200 MHz** (= 2.5 – 2.3 GHz)




The impedance matching
-10-dB (reflection coefficient)
band & **bandwidth**.

Means the **band** where the
impedance matching (reflection
coefficient) is better (=lower)
than -10 dB.


- The -10-dB **band** 2.39 ... 2.42 GHz
- The -10-dB **bandwidth** 0.030 GHz = 30 MHz

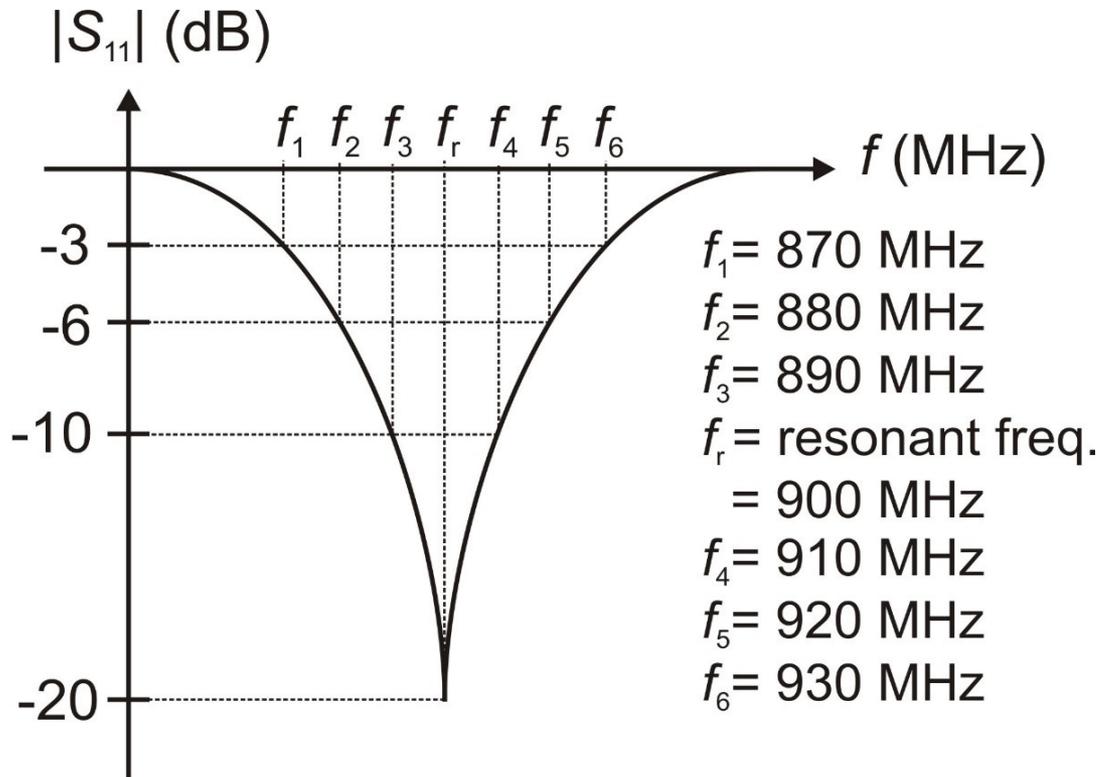Q2: The figure shows the frequency response of a resonant component. What is the **bandwidth (MHz)** where **less than 25%** of the power is reflected?





1. 0 MHz
2. 10 MHz
3. 20 MHz
4. 40 MHz
5. 60 MHz
6. None of above

Load + matching circuit = resonator

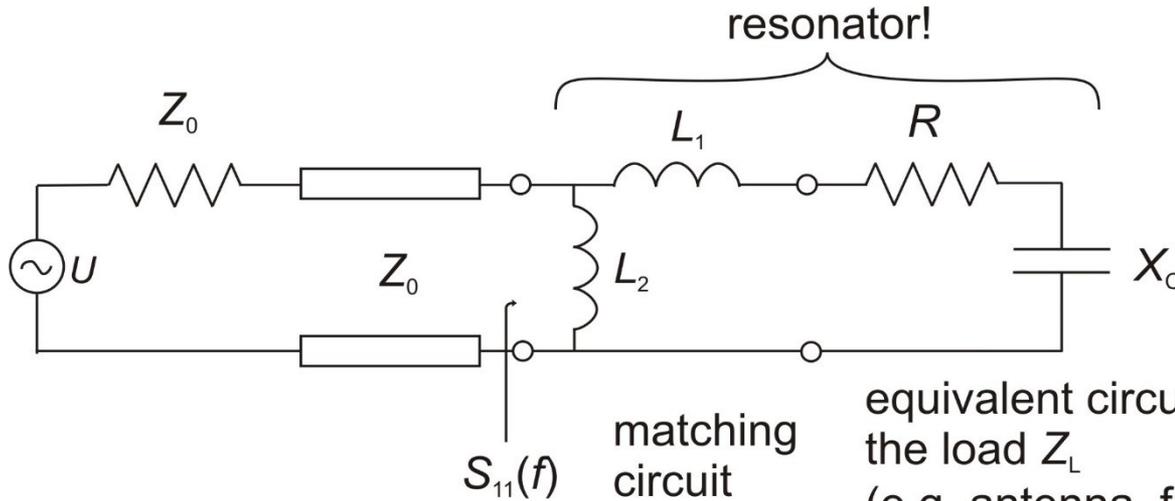

equivalent circuit of the load Z_L
(e.g. antenna, filter, amplifier, mixer etc.)

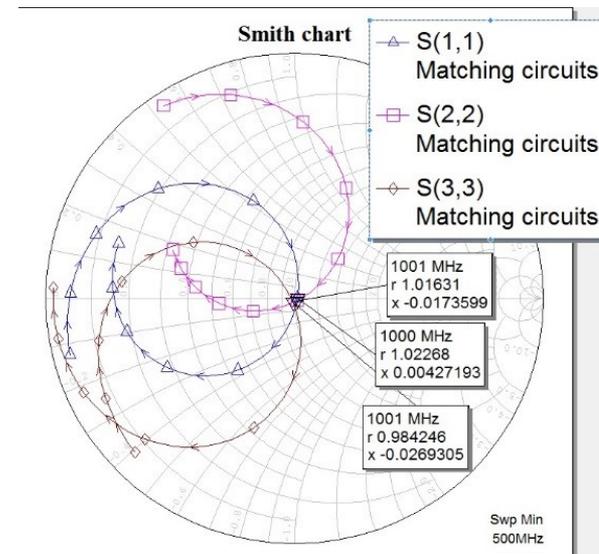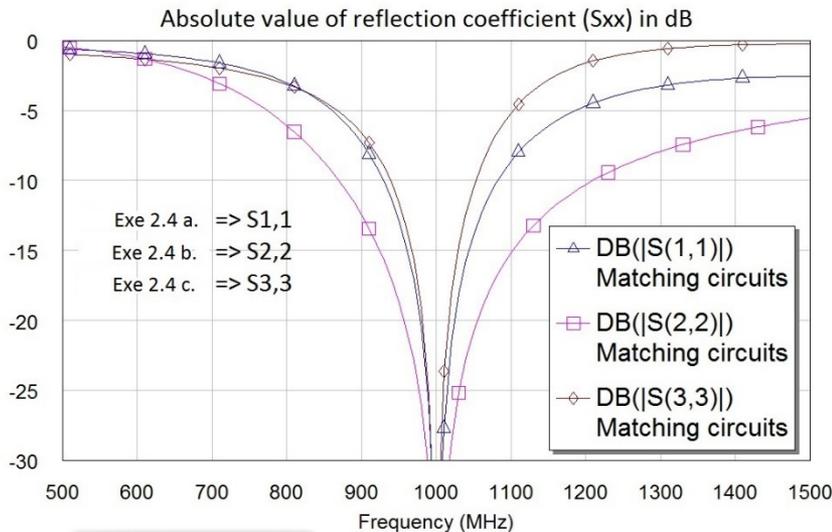
How does the resonance behavior take place?



Q3: The curves below show the impedance of a resonator as a function of angular frequency. What is the **type** of the resonator?



R = resistance, X = total reactance, X_L = inductive reactance, X_C = capacitive reactance, Z = impedance

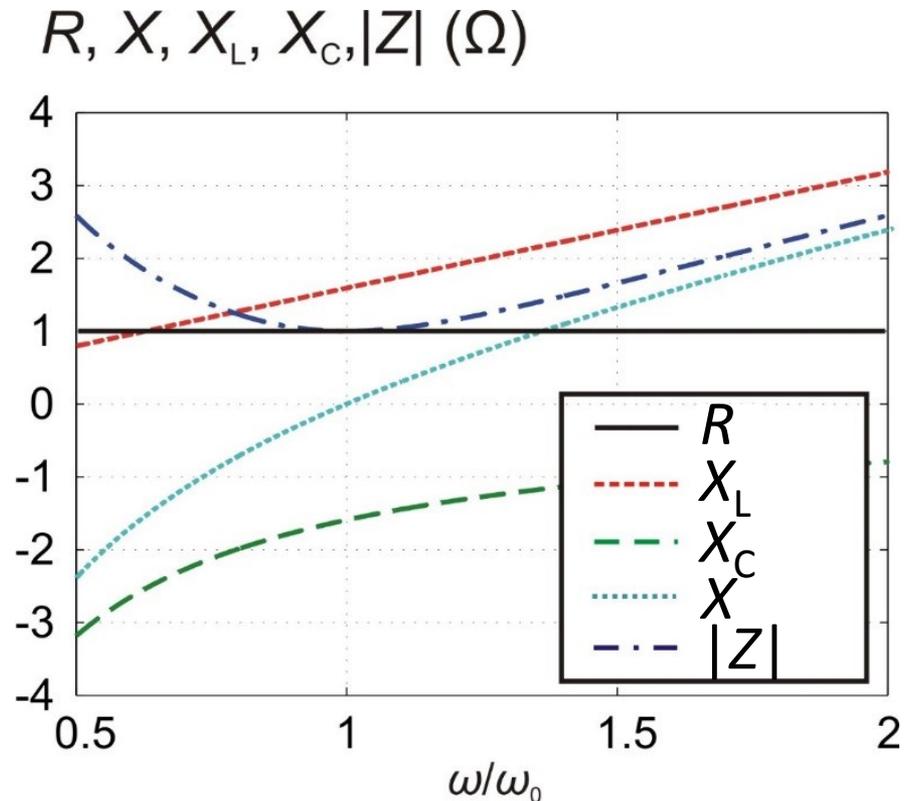1. Series resonant circuit
2. Parallel resonant circuit
3. L-section lumped element matching circuit
4. Dual-resonant matching circuit
5. None of above
6. I don't know




Series RLC circuit

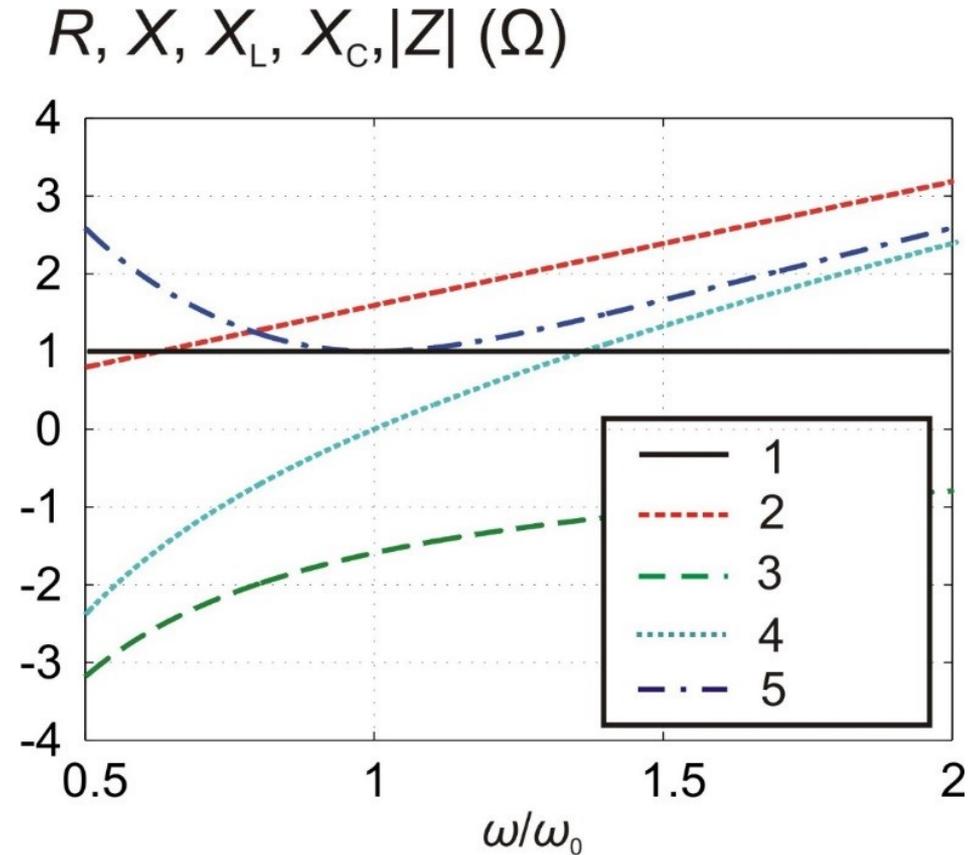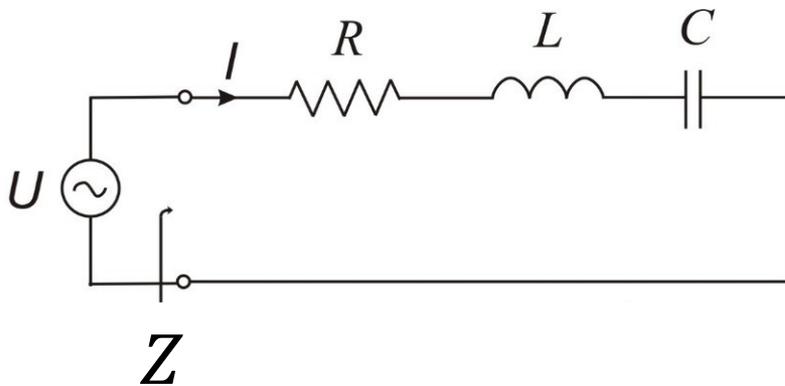The simplest form of resonator is good for understanding the phenomenon!



$$Z = R + jX = R + j(X_L - X_C) = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

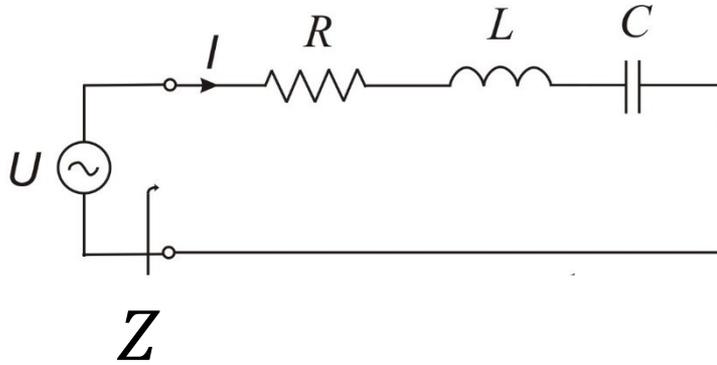
Q4: Which of alternatives is the definition of the resonant frequency



$$\begin{aligned} Z &= R + jX = R + j(X_L - X_C) \\ &= R + j\left(\omega L - \frac{1}{\omega C}\right) \end{aligned}$$


1. A time-average energy in the **electric** mode takes place
2. Energy in the **magnetic** mode is at its maximum
3. Amplitude of the current (oscillation) is at its maximum
4. The inductance L equals the capacitance C
5. None of above
6. I don't know

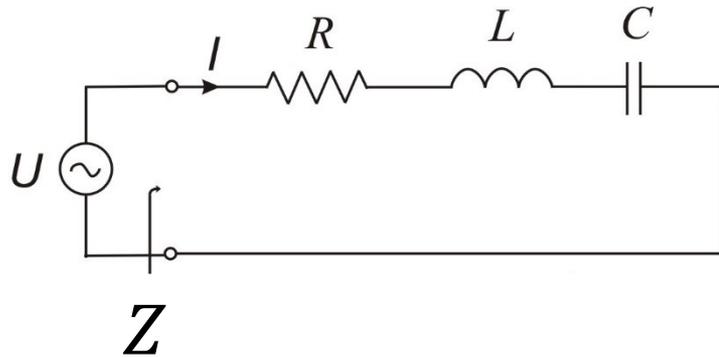Q5: At which normalized angular frequency the resonator is in the resonance?



$$Z = R + jX = R + j(X_L - X_C)$$
$$= R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$R, X, X_L, X_C, |Z|$ (Ω)

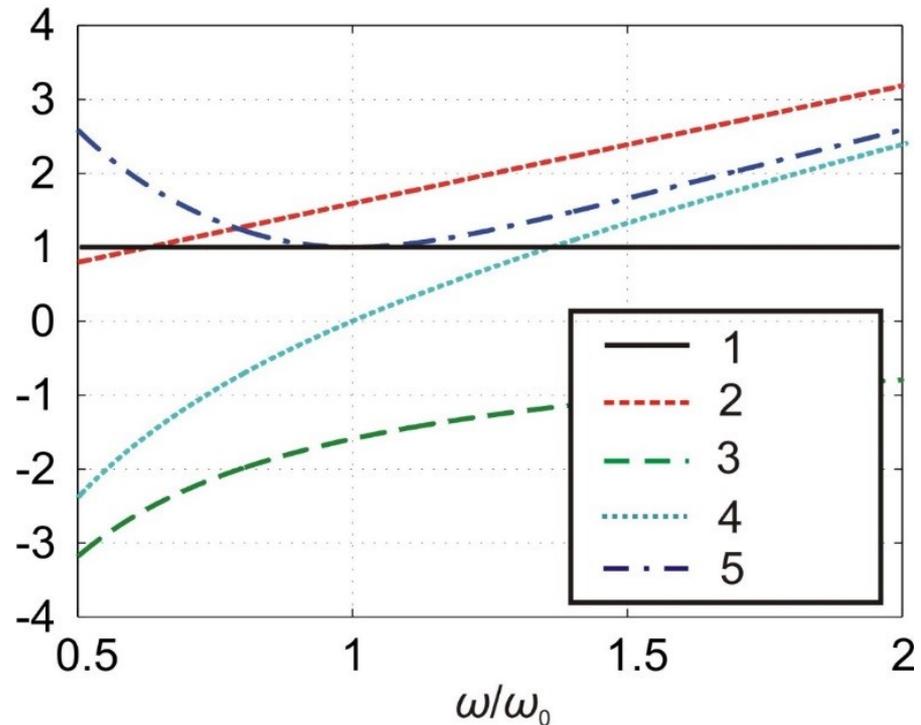

1. $\omega = 0.5$ rad/s
2. $\omega = 1.0$ rad/s
3. $\omega = 1.5$ rad/s
4. $\omega = 2.0$ rad/s
5. None of above
6. I don't know

Q6: A 2-port with lumped impedance Z is connected between two transmission lines (with Z_0). What is the input impedance Z_{in} seen in Port 1 to the **right** (towards Port 2)?

Assume lines very long.

1. $Z_{in} = Z$


2. $Z_{in} = Z_0$

3. $Z_{in} = Z + Z_0$


4. $Z_{in} = Z \cdot Z_0 / (Z + Z_0)$

5. None of above

6. I don't know

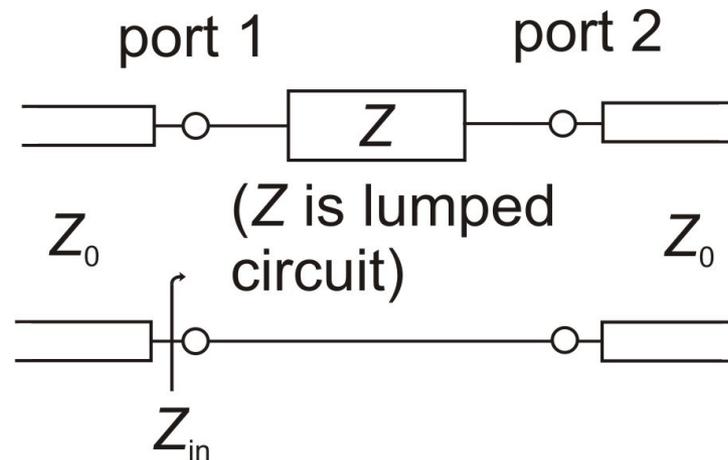


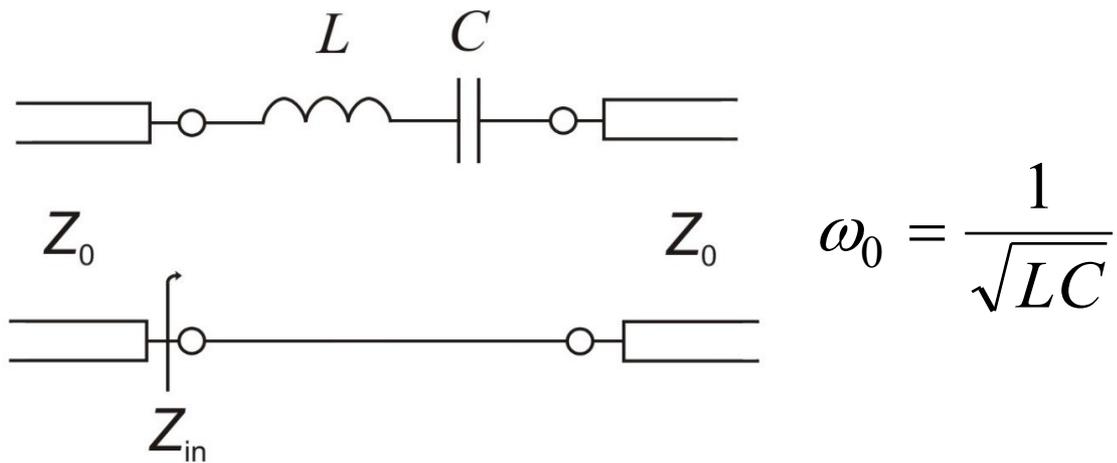Q7: This LC series circuit topology might work as ...



1. Low-pass filter below ω_0
2. High-pass filter above ω_0
3. Band-pass filter around ω_0
4. Band-stop filter around ω_0
5. None of above
6. I don't know

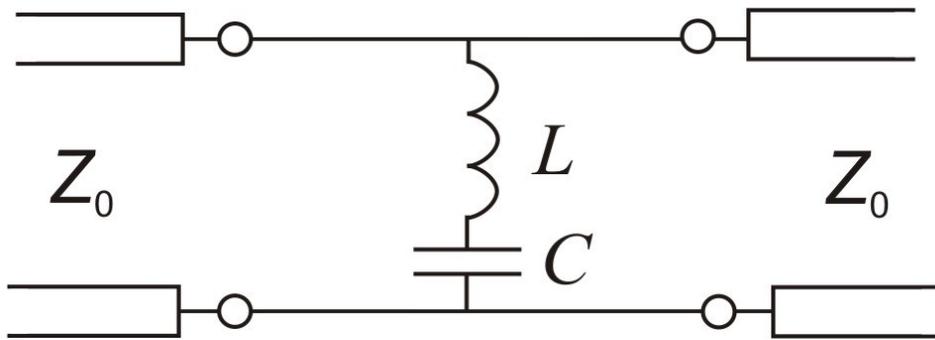
Q8: This LC series circuit topology might work as ...



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

1. Low-pass filter below ω_0
2. High-pass filter above ω_0
3. Band-pass filter around ω_0
4. Band-stop filter around ω_0
5. None of above
6. I don't know

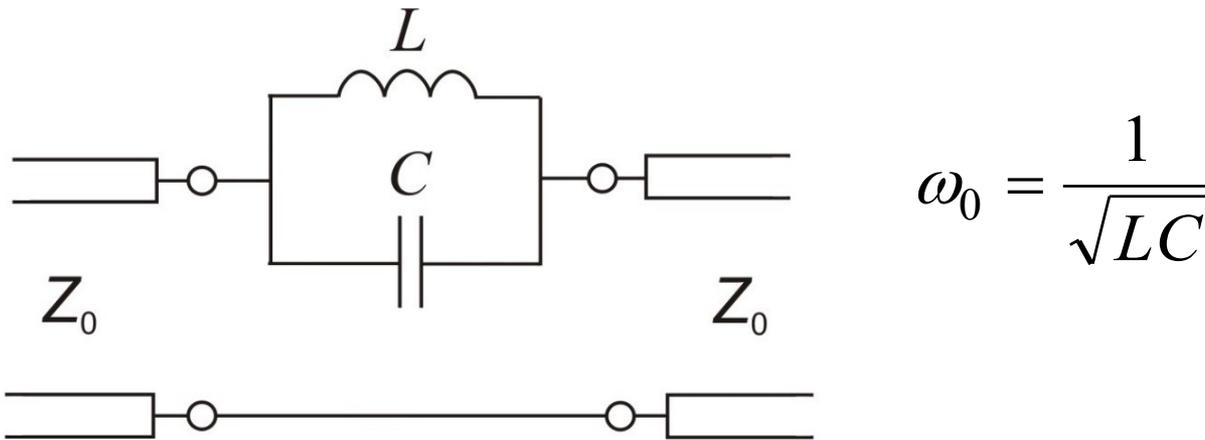Q9: This LC parallel circuit topology might work as ...



1. Low-pass filter below ω_0
2. High-pass filter above ω_0
3. Band-pass filter around ω_0
4. Band-stop filter around ω_0
5. None of above
6. I don't know