



Aalto University
School of Electrical
Engineering

Hybrid Switched Capacitor Power Converters: Resonant Operation

Okko Järvinen

Department of Electronics and Nanoengineering
Aalto University, School of Electrical Engineering

15.5.2019

Outline

Introduction

Resonant Operation

Resonant SC Topologies

Implementation Examples

Conclusion & Homework

Outline

Introduction

Resonant Operation

Resonant SC Topologies



Implementation Examples

Conclusion & Homework

Introduction


- ▶ In SC power converters, capacitors are typically charged/discharged by other capacitors or voltage sources → high current transients → reduced efficiency
- ▶ The transients can be reduced by
 - ▶ Large capacitors
 - ▶ High switching frequencies
 - ▶ Interleaving
 - ▶ **Soft-charging & resonant operation**

Introduction

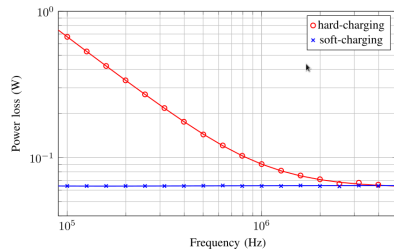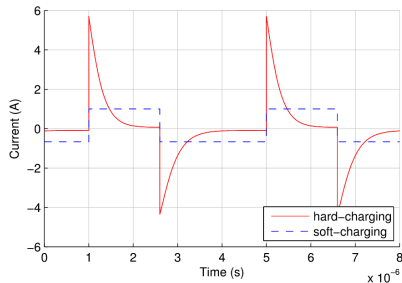

► Soft-charging → reduced current transients → reduced losses

Introduction

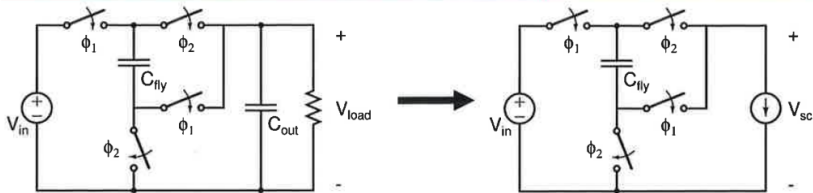

- ▶ Soft-charging achieved by using a current-source load
- ▶ Current-source load allows instant voltage change at its terminal \rightarrow the voltage mismatch between flying capacitor and load can be accommodated

Outline

Introduction

Resonant Operation

Resonant SC Topologies

Implementation Examples

Conclusion & Homework

Resonant Operation



- ▶ The goal is to achieve soft-charging operation in order to minimize charge redistribution losses
- ▶ Soft-charging can be achieved using current-source load

Resonant Operation

- ▶ The goal is to achieve soft-charging operation in order to minimize charge redistribution losses
- ▶ Soft-charging can be achieved using current-source load
- ▶ Or an inductor!


Resonant Operation

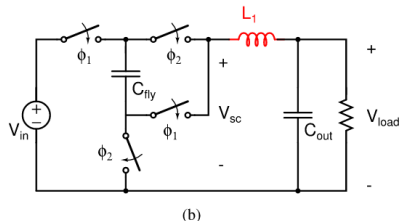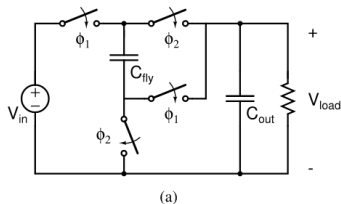- ▶ 2-to-1 SC power converter with output inductor
- ▶ Inductor allows instant voltage change at its terminal \rightarrow behaves as a controlled current source



Resonant Operation

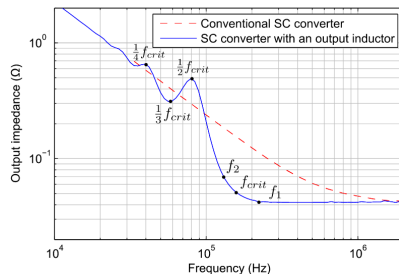- Output inductor can lower the output impedance compared to conventional SC converter
- Same efficiency as conventional SC converter, but with lower frequency or smaller capacitor values




$$P_{loss} \propto \frac{1}{f_{sw}}, \frac{1}{C_{fly}}$$

Resonant Operation

Resonant frequency is



$$f_{crit} = \frac{1}{2\pi\sqrt{LC}},$$

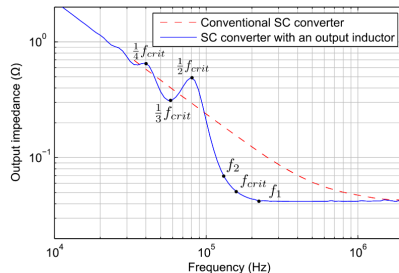where C is the collective capacitance in series with the inductor.





Resonant Operation

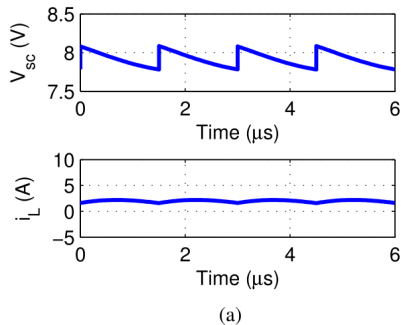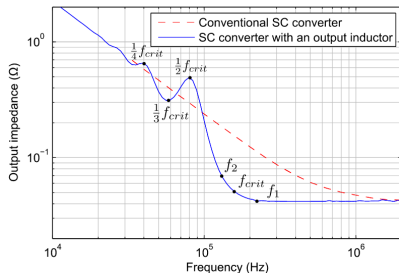- ▶ In this case, $f_{sw} = f_1$
- ▶ Current transients eliminated \rightarrow soft-charging





Resonant Operation

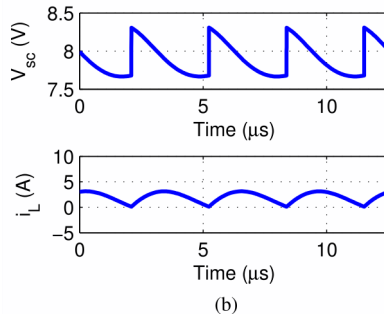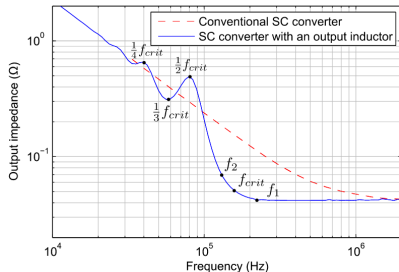- ▶ In this case, $f_{sw} = f_{crit}$
- ▶ Current reaches zero \rightarrow zero-current switching (ZCS) achievable at the resonant frequency



Resonant Operation

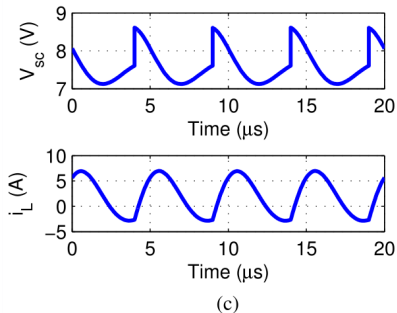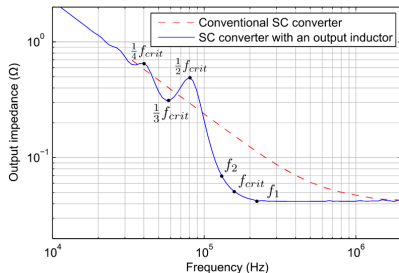- ▶ In this case, $f_{sw} = f_2$
- ▶ Current becomes negative as well \rightarrow RMS value increases \rightarrow impedance increases





Resonant Operation

- For conventional SC, switch on-resistance determines the region of operation

$$f_{crit} = \frac{1}{2\pi R_{ESR}C}$$

- For resonant SC, the critical frequency is decoupled from the resistance

$$f_{crit} = \frac{1}{2\pi\sqrt{LC}}$$

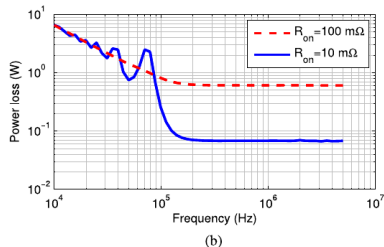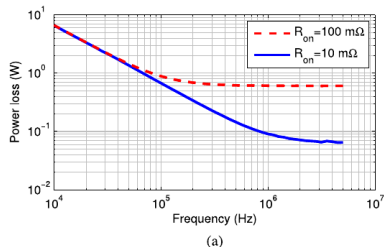

Resonant Operation

- ▶ Soft-charging operation
 - ▶ As flat current profile as possible
 - ▶ Good for heavy loading where conduction loss dominates
- ▶ Resonant ZCS operation
 - ▶ Slight current variance to allow zero current at switching instants
 - ▶ Good for lighter loads or high frequency operation where switching loss dominates

Common Goal

Improved efficiency

Outline

Introduction

Resonant Operation

Resonant SC Topologies

Implementation Examples

Conclusion & Homework

Resonant SC Topologies

- ▶ Full ZCS operation on all switches can be achieved if the topology is compatible with **full soft-charging operation**
 1. Current-source load
 2. No voltage-mismatch among flying capacitors during phase transitions
- ▶ Typically achievable with just one inductor at the output

Resonant SC Topologies


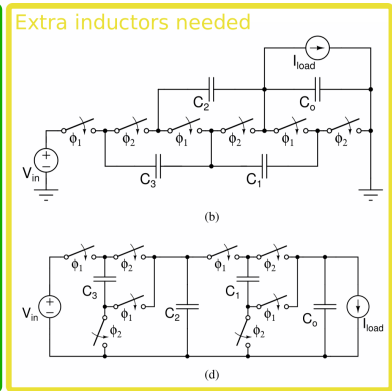
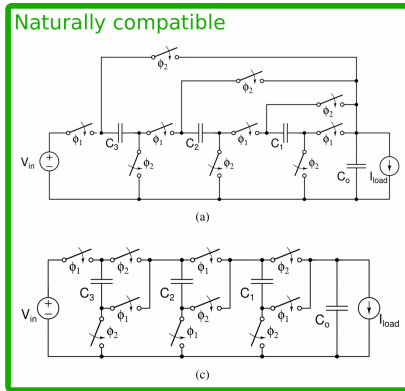


Fig. 13. Common SC converter topologies. (a) 4-to-1 series-parallel. (b) 3-to-1 ladder. (c) 5-to-1 Fibonacci. (d) 4-to-1 doubler.

Resonant SC Topologies

Fibonacci


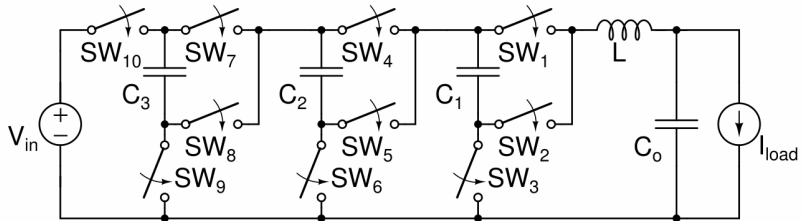


- Single inductor added to output enables ZCS resonant operation

Resonant SC Topologies


Fibonacci

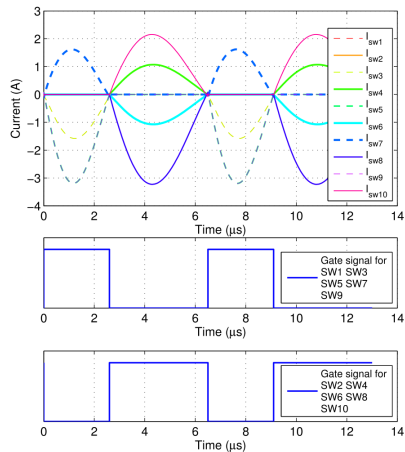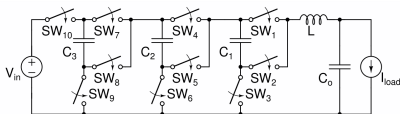- During the switching instants, all switch currents are effectively zero \rightarrow resonant ZCS operation



Resonant SC Topologies

Ladder

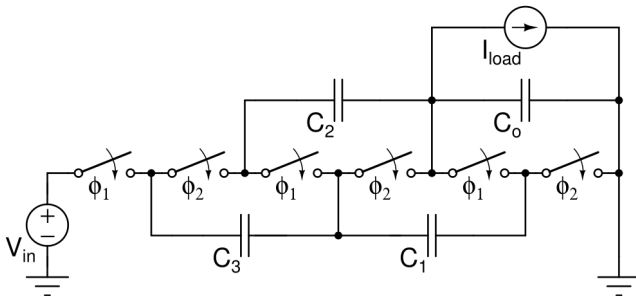


- ▶ Not naturally compatible with full soft-charging
- ▶ Can be made compatible by adding an inductor in series with every capacitor

Resonant SC Topologies


Ladder

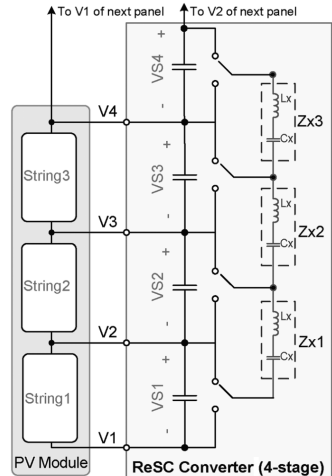- ▶ Series inductors L_X added
- ▶ Even with multiple additional inductors, the resonant ladder converter can be useful for balancing series-connected loads
 - ▶ Solar PV systems
 - ▶ Battery equalizers
 - ▶ Series-stacked digital loads



Resonant SC Topologies

4-to-1 Doubler

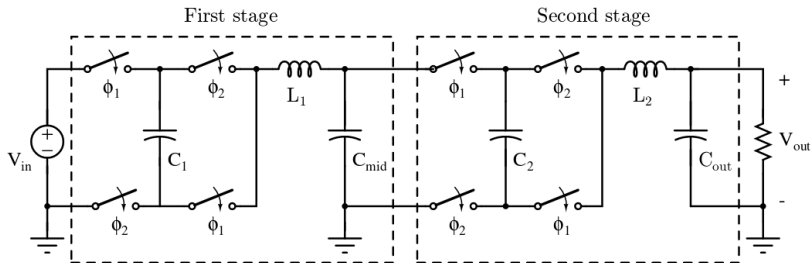

- ▶ One inductor added at the output of each stage
- ▶ For N-to-1 doubler can be operated in resonant ZCS mode with \sqrt{N} inductors

Outline

Introduction

Resonant Operation


Resonant SC Topologies

Implementation Examples

Conclusion & Homework

Implementation Examples


1: Resonant 2-to-1 Converter [4]

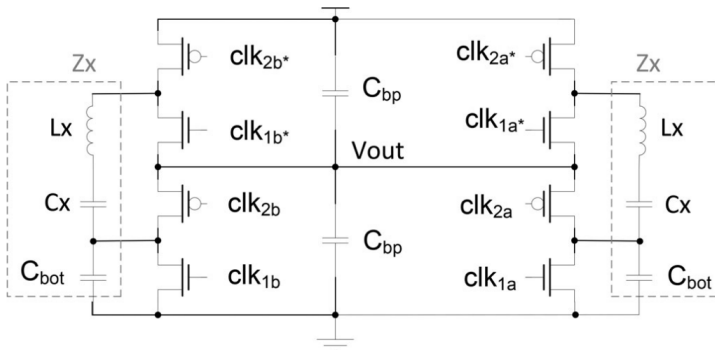

- Two-phase 2-to-1 converter


Implementation Examples

1: Resonant 2-to-1 Converter [4]

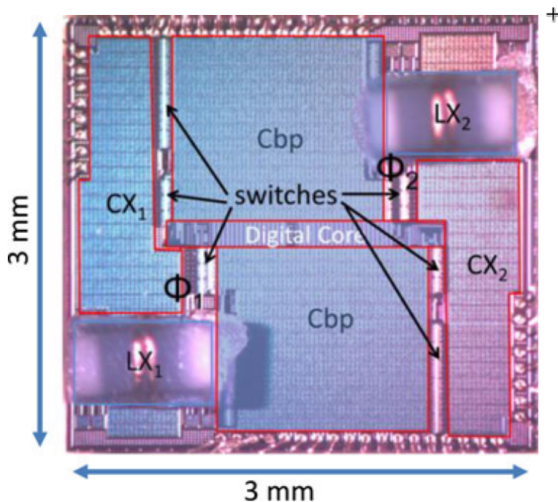

Implementation Examples


1: Resonant 2-to-1 Converter [4]

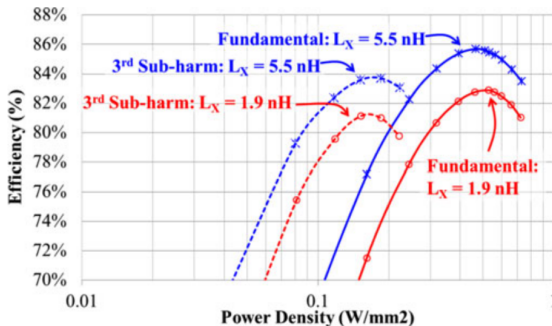

► $f_{sw} = 30$ MHz, $P_{out} = 3.35$ W


Implementation Examples

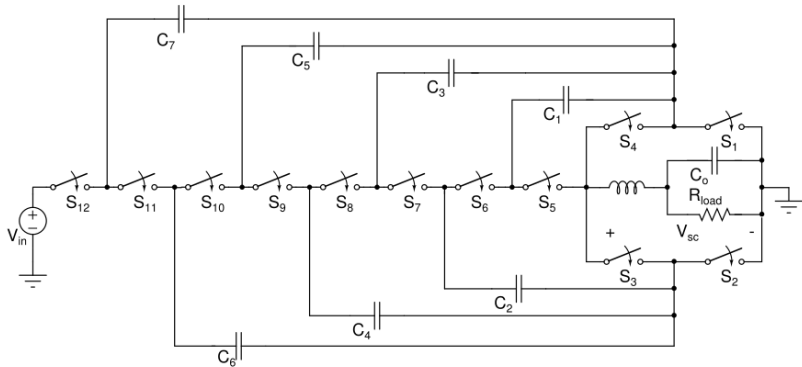2: Resonant 8-to-1 Dickson SC Converter [1]



Implementation Examples

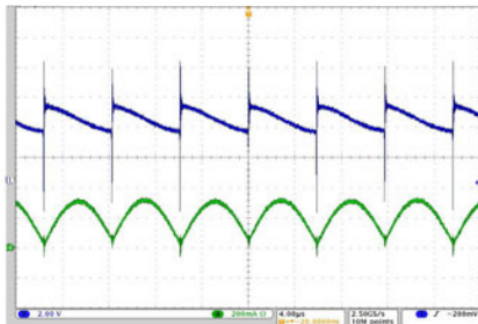
2: Resonant 8-to-1 Dickson SC Converter [1]



- Resonant ZCS operation at $f_{crit} = 90 \text{ kHz}$

Implementation Examples

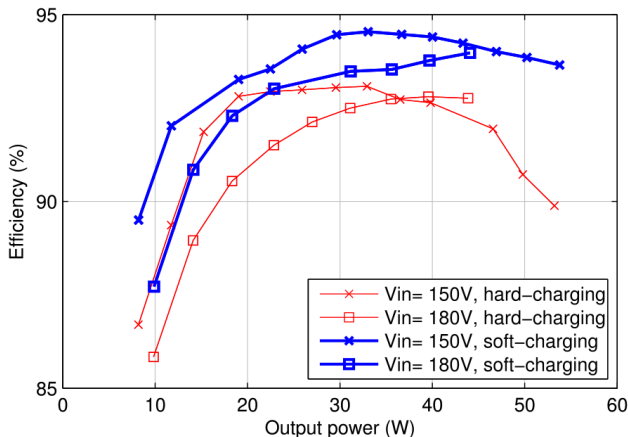2: Resonant 8-to-1 Dickson SC Converter [1]



► $f_{sw} = 250 \text{ kHz}$, $P_{out} = 53 \text{ W}$

Outline

Introduction

Resonant Operation


Resonant SC Topologies

Implementation Examples

Conclusion & Homework

Conclusion & Homework

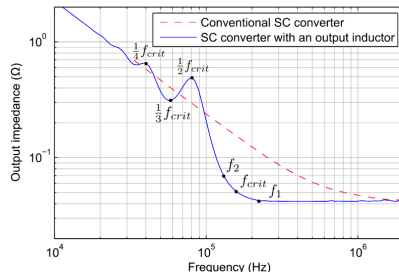- ▶ Soft-charging can be achieved with an inductor
- High-efficiency operation at lower frequency or with smaller capacitors
- ▶ Operating at the resonant frequency of the circuit, zero-current switching can be achieved
- Minimized switching loss due to ZCS operation, minimized charge redistribution loss due to soft-charging



Homework

Briefly explain how the on-resistance of the switches affects the resonant operation of the hybrid SC converter.

See Section III in:

Y. Lei and R. C. N. Pilawa-Podgurski, "A General Method for Analyzing Resonant and Soft-Charging Operation of Switched-Capacitor Converters," in IEEE Transactions on Power Electronics, vol. 30, no. 10, pp. 5650-5664, Oct. 2015.

References

1. Y. Lei and R. C. N. Pilawa-Podgurski, "A General Method for Analyzing Resonant and Soft-Charging Operation of Switched-Capacitor Converters," in IEEE Transactions on Power Electronics, vol. 30, no. 10, pp. 5650-5664, Oct. 2015.
2. Z. Ye, Y. Lei and R. C. N. Pilawa-Podgurski, "A resonant switched capacitor based 4-to-1 bus converter achieving 2180 W/in^3 power density and 98.9% peak efficiency," 2018 IEEE Applied Power Electronics Conference and Exposition (APEC), San Antonio, TX, 2018, pp. 121-126.
3. J. T. Stauth, M. D. Seeman and K. Kesarwani, "A Resonant Switched-Capacitor IC and Embedded System for Sub-Module Photovoltaic Power Management," in IEEE Journal of Solid-State Circuits, vol. 47, no. 12, pp. 3043-3054, Dec. 2012.
4. K. Kesarwani, R. Sangwan and J. T. Stauth, "Resonant-Switched Capacitor Converters for Chip-Scale Power Delivery: Design and Implementation," in IEEE Transactions on Power Electronics, vol. 30, no. 12, pp. 6966-6977, Dec. 2015.