


Wireless power transfer techniques

Ali Saleem (ali.saleem@aalto.fi)

Aalto University, School of Electrical Engineering

May 29, 2019

Wired vs Wireless

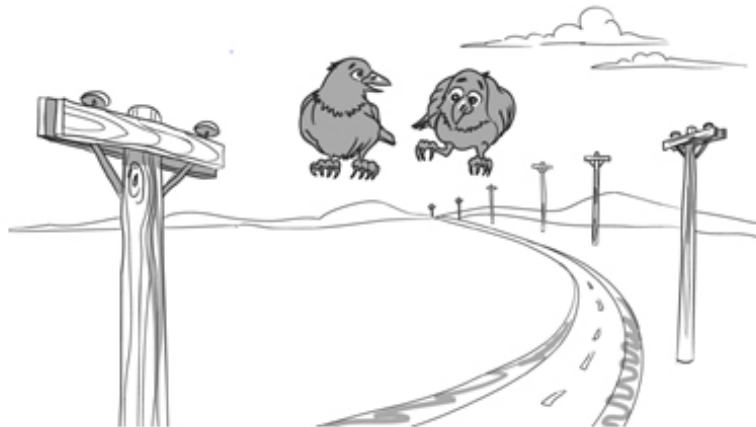


TELL ME AGAIN THE BENEFITS OF WIRELESS.

Applications

- ▶ Implantable medical devices (IMDs)— μW
- ▶ Radio frequency identification— mW
- ▶ Contact less memory— mW
- ▶ Wireless chargers— W
- ▶ Wearable devices— W
- ▶ Wafer level testing— W
- ▶ Electric vehicles— kW

Radiation Exposure

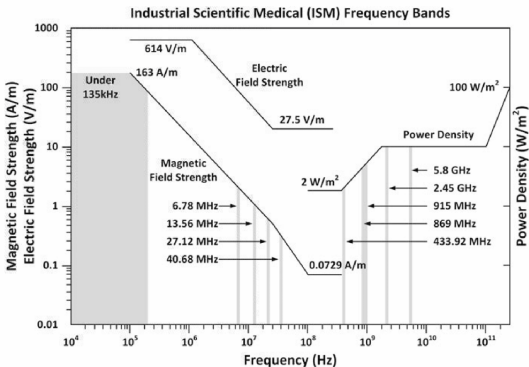- ▶ X-rays/Gamma Rays
- ▶ RF/Microwaves
- ▶ Basic restrictions



- ▶ Human tissue specific absorption rate (SAR)

Modes of transfer

- ▶ Near field ($\lambda \ll d$)
- ▶ Far field ($\lambda \gg d$)

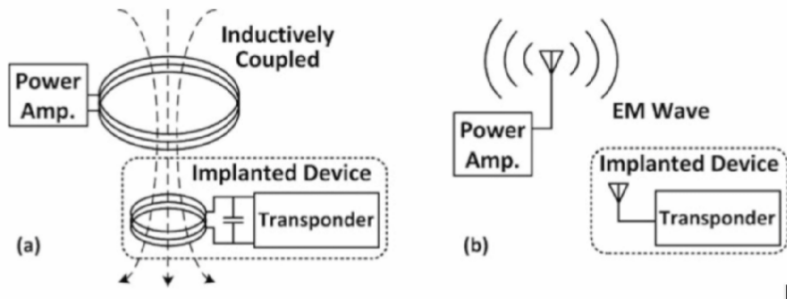


Figure: (a) Near field WPT (b) Far field WPT

Modes of transfer (contd.)

- ▶ Path loss for two isotropic transmit/receive antennas

$$A_{PATH} = -20 \log\left(\frac{4\pi d}{\lambda}\right)$$

- ▶ Resonance frequency: $F_{res} = \frac{1}{2\pi\sqrt{LC}}$

- ▶ ISM bands(13.56 MHz; 6.78 MHz/100–200 KHz)

¹Depending on the coupling coefficient (k) and distance (d)

- ▶ Tightly coupled or inductive systems (d < 4cm as per Qi standard²)
- ▶ Loosely coupled or resonant system (Spatial freedom, Multiple devices)

¹Wireless Charging: Inside the technology

²Another standard is AirFuel Alliance

Wireless charging standards

- ▶ Qi/AirFuel: 5W (mobile) / 15W (laptop)

Standard	Qi	Airfuel
Frequency	87–205 KHz	6.78 ± 15 KHz
Coils	Multiple	One
Data Communication	Load modulation	Bluetooth

Table: Comparison of standards³

Design Challenge: Signal+Power processing; transmission frequency, process technology, resonator topology, output regulation etc.

³Alternatively, a long range WPT using 2.45 GHz or 5.8 GHz can also be used.

Generic inductively coupled WPT


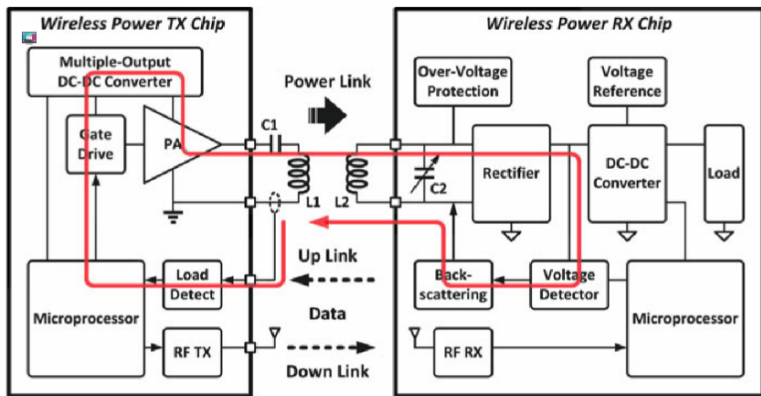


Figure: Block diagram of WPT with TX chip capable of powering up RX chip while enabling wireless communication

WPT system

- ▶ Power amplifier
- ▶ Resonating Coils
- ▶ Rectifiers(AC → DC)
- ▶ Regulators
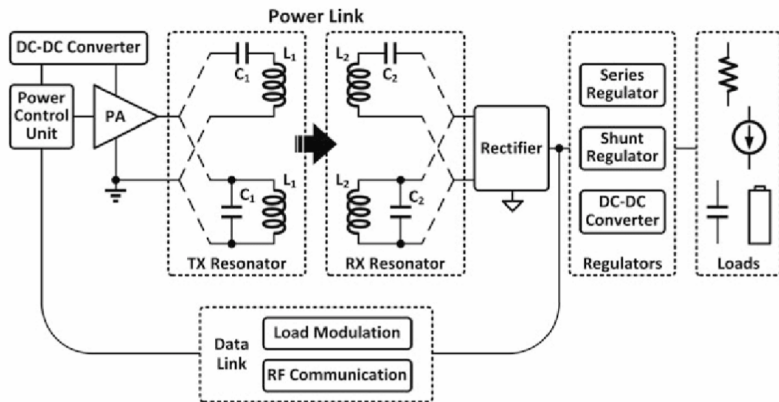
$$\eta_{TOTAL} = \eta_{DC-DC} \times \eta_{PA} \times \eta_{LINK} \times \eta_{RECT} \times \eta_{REG}$$



Power control strategies-PA

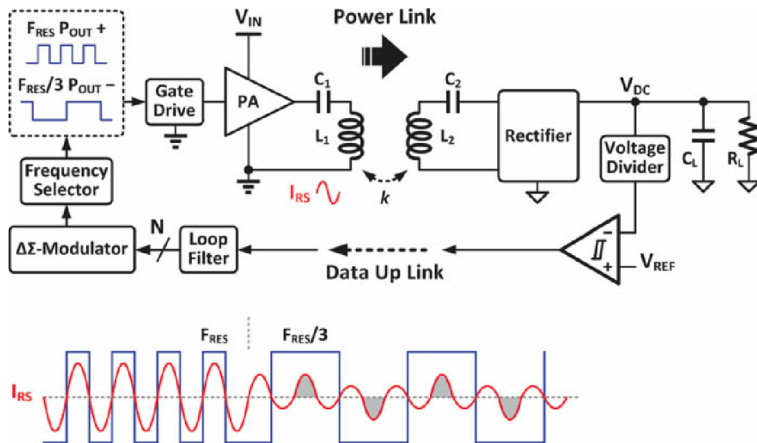


Figure: Transmission frequency hopping⁴

⁴ Shinoda R, Tomita K, Hasegawa Y, Ishikuro H (2012) Voltage-boosting wireless power delivery system with fast load tracker by $\Delta\Sigma$ -modulated sub-harmonic resonant switching. In: IEEE international solid-state circuits conference digest of technical papers (ISSCC), 2012, pp 288â290

Power control strategies-PA

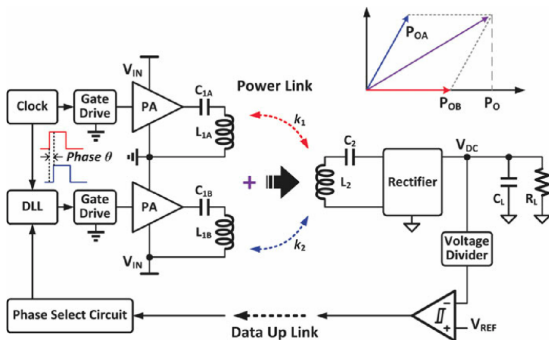


Figure: DLL based power control approach⁵

$$P_o = P_{PA} \times (1 + \cos\theta)$$

⁵K. Tomita, R. Shinoda, T. Kuroda and H. Ishikuro, "1-W 3.3–16.3 V Boosting Wireless Power Transfer Circuits With Vector Summing Power Controller," in IEEE Journal of Solid-State Circuits, vol. 47, no. 11, pp. 2576-2585, Nov. 2012. doi: 10.1109/JSSC.2012.2211698

Power control strategies-Rectifier

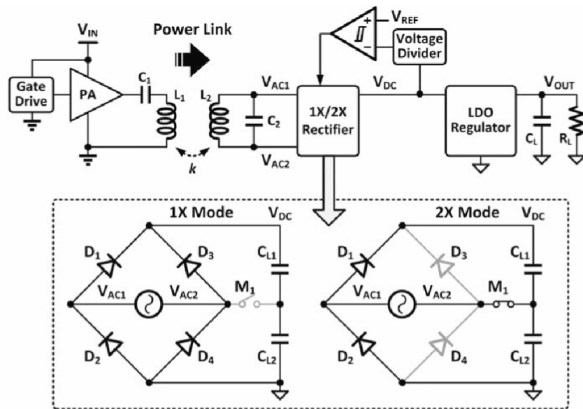


Figure: Reconfigurable rectifier⁶

⁶ Lee H-M, Ghovanloo M (2012) An adaptive reconfigurable active voltage doubler/rectifier for extended-range inductive power transmission. IEEE Transac Circuits Syst II Express Briefs 59:481â 485. doi:10.1109/TCSII.2012.2204840

Power control strategies-Rectifier

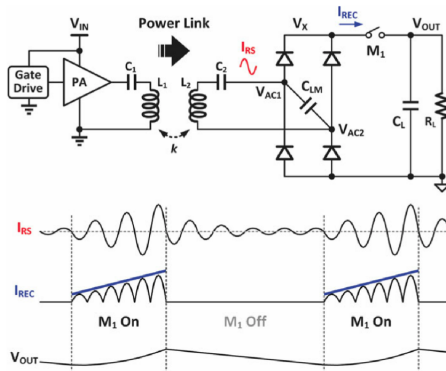


Figure: Pulse width modulation regulating rectifier⁷

$$P_{Cond.loss} = \frac{1}{NT} \int_{t_0}^{t_0+NT} I_{REC}^2 \cdot R_{ON} dt$$

7

Power control strategies-Rectifier

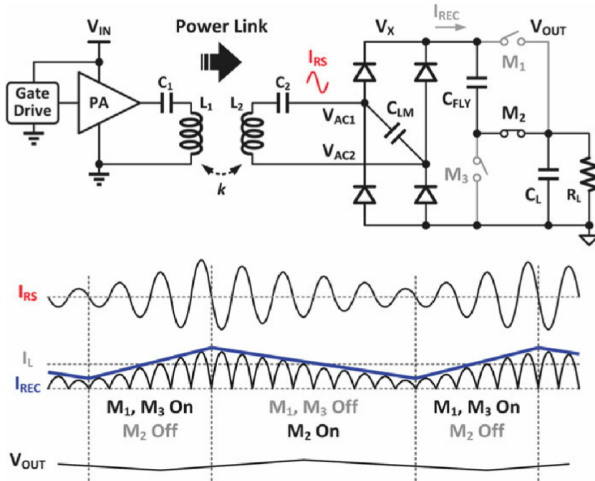


Figure: Pulse width modulation regulating rectifier⁸

⁸ Li X, Tsui C-Y, Ki W-H (2015) A 13.56 MHz wireless power transfer system with reconfigurable resonant regulating rectifier and wireless power control for implantable medical devices. IEEE J Solid State Circuits 50:978â989. doi:10.1109/JSSC.2014.2387832

Power control strategies-Rectifier

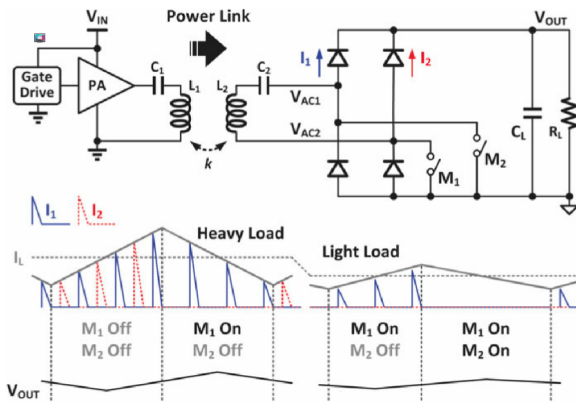


Figure: Pulse width modulation regulating rectifier⁹

⁹ Cheng L, Ki W-H, Wong Y-T, Yim T-S, Tsui C-Y (2016) A 6.78MHz 6W wireless power receiver with a 3-Level $1X/\frac{1}{2}X/0X$ reconfigurable resonant regulating rectifier. In: 2016 IEEE international solid-state circuits conference (ISSCC), pp 376â377

Power control strategies-Rectifier

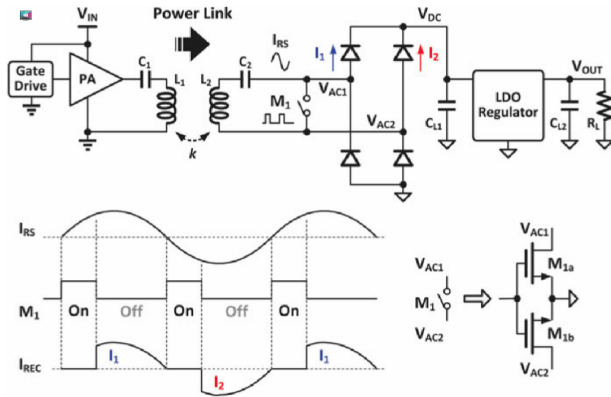


Figure: Pre-rectifier regulation¹⁰

► Zero-current switching

¹⁰

Kiani M, Lee B, Yeon P, Ghovanloo M (2015) A Q-modulation technique for efficient inductive power transmission.

IEEE J Solid State Circuits 50:2839â2848. doi:10.1109/JSSC. 2015.2453201

Power control strategies-Rectifier

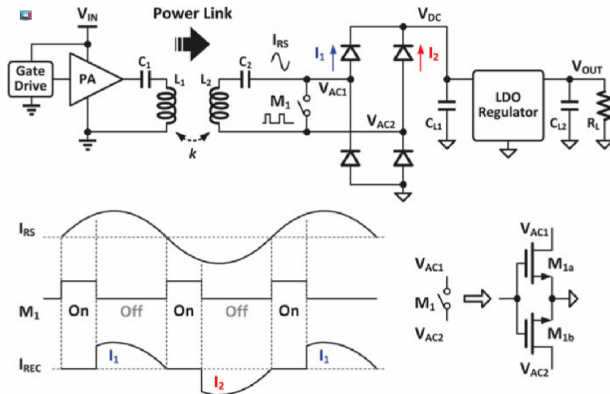


Figure: Pre-rectifier regulation¹¹

$$\blacktriangleright R_{L,EQ} = R_L(8/\pi^2)(1 - D)^2$$

¹¹ Kiani M, Lee B, Yeon P, Ghovanloo M (2015) A Q-modulation technique for efficient inductive power transmission.

IEEE J Solid State Circuits 50:2839â2848. doi:10.1109/JSSC. 2015.2453201

Power control strategies-Multilevel Rectifier

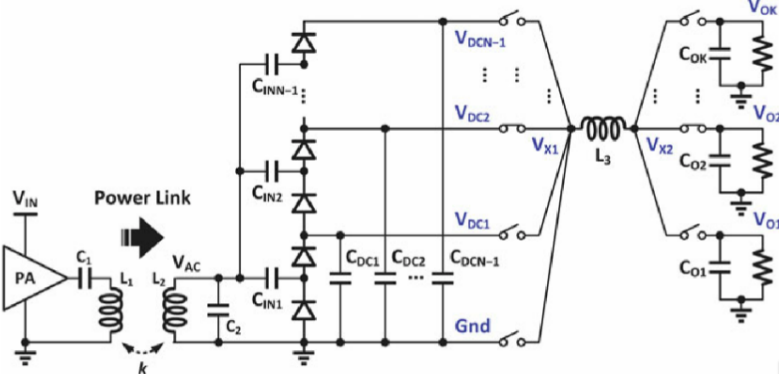


Figure: Single inductor multiple output operation (SIMO)

Power control strategies-SIMO

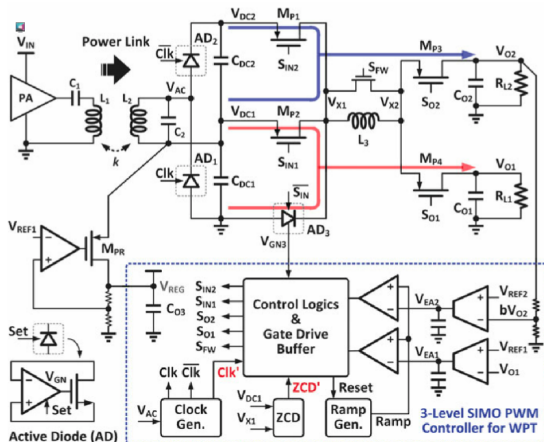


Figure: A 2X rectifier and 3-level SIMO converter

Power control strategies-SIMO

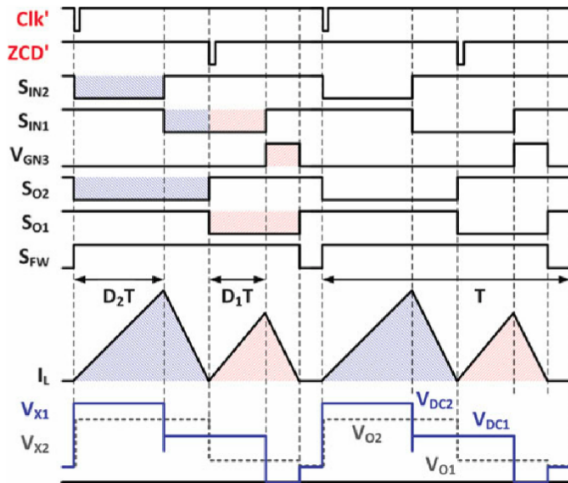


Figure: A 2X rectifier and 3-level SIMO converter

Coupled Coils

Coupled coil–Transformer model

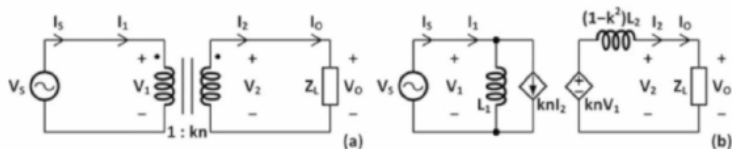


Figure: Transformer model of coupled coils

Mutual coupling = M

Coupling factor = $k = M / \sqrt{L_1 L_2}$

Turn-ratio = $n = \sqrt{L_1 / L_2}$

$$V_2(s) = \frac{M}{L_1} (sL_1 I_1 - sM I_2) - sL_2 I_2 + s \frac{M^2}{L_1 L_2} L_2 I_2$$

Coupled coil–Reflected Impedance model

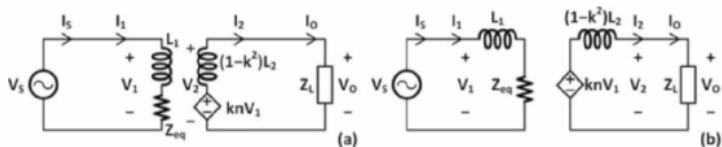


Figure: Reflected impedance model

Mutual coupling = M

Coupling factor = $k = M / \sqrt{L_1 L_2}$

Turn-ratio = $n = \sqrt{L_1 / L_2}$

$$Z_{eq}(s) = \frac{M^2 \omega^2}{sL_2 + Z_L(s)}$$

Coupled coil–Link Efficiency

- ▶ Link voltage gain = $\frac{V_o}{V_s}$
- ▶ Link efficiency = $\eta = \frac{P_o}{P_s}$
- ▶ Parasitic model (Section 3.2-3.3)

Coupled coil

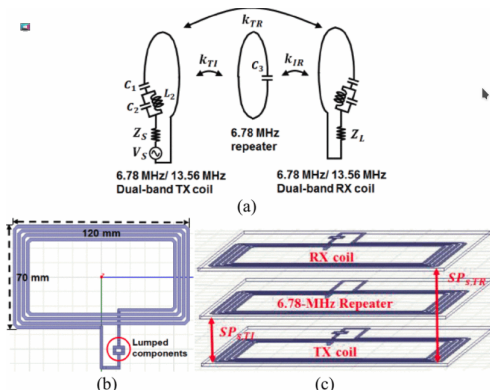


Figure: coil sizes¹²

¹²M. Kung and K. Lin, "A 6.78 MHz and 13.56 MHz dual-band coil module with a repeater for wireless power transfer systems," 2016 IEEE International Symposium on Antennas and Propagation (APSURSI), Fajardo, 2016, pp.

157-158. doi: 10.1109/APS.2016.7695787

Integrated coils

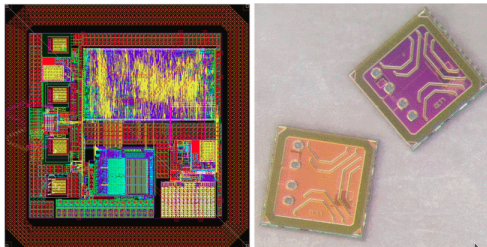


Figure: Integrated coils : Area < 1mm^2

13

¹³W. Pachler, W. BÄ¶sch, G. Holweg and G. Hofer, "A novel booster antenna design coupled to a one square millimeter coil-on-chip RFID tag enabling new medical applications," 2013 European Microwave Conference, Nuremberg, 2013, pp. 1003-1006. doi: 10.23919/EuMC.2013.6686829

Summary

- ▶ WPT system/modes
- ▶ System level optimization
- ▶ Rectifiers
- ▶ Coils

- ▶ References: Images from Google repository and IEEE.
- ▶ Book:CMOS Integrated Circuit Design for Wireless Power Transfer Yan Lu and Wing-Hung Ki

Homework

Draw the transistor level diagram of a Full bridge rectifier.

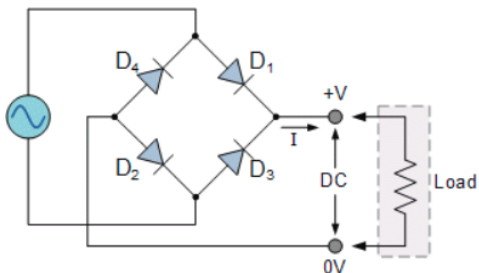


Figure: Replace diodes with transistors