


**Problem 1: Transfer functions of a DC motor**

The block diagram of a DC motor is shown in the figure.

(a) Derive the transfer functions

$$G_{\omega u}(s) = \frac{\omega_M(s)}{u_a(s)} \quad \text{and} \quad G_{\omega T}(s) = \frac{\omega_M(s)}{T_L(s)}$$

(b) Replace the electric dynamics of the machine with the DC gain and formulate the transfer functions  $G_{\omega u}(s)$  and  $G_{\omega T}(s)$ .

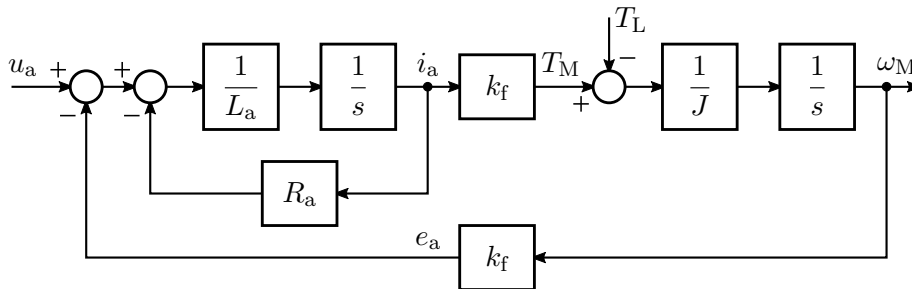

**Problem 2: Current ripple**

The parameters of a DC motor are:  $R_a = 1 \Omega$ ,  $L_a = 10 \text{ mH}$ , and  $k_f = 4 \text{ Vs}$ . The average steady-state current taken by the motor is  $I_a = 100 \text{ A}$  and the rotor speed is  $560 \text{ r/min}$ . The motor is supplied from a four-quadrant DC-DC converter, where the unipolar PWM is applied. The DC-bus voltage is  $U_{dc} = 450 \text{ V}$  and the switching (carrier) frequency is  $f_{sw} = 4 \text{ kHz}$ . Calculate the peak-to-peak current ripple.

