

Different kinds of Transformers




Outcome of this lecture

At the end of this lecture you will be able to:


- Explain the operation principle of a transformer
- Model a transformer with a lumped-parameters equivalent circuit
- Calculate the parameters of the equivalent circuit from measurements
- Use the equivalent circuit to calculate
 - The power balance
 - The efficiency
- Understand what the harmonics in three phases transformers mean and how they are produced
- You will also learn about different possible connections of three phase transformers.

Transformers applications

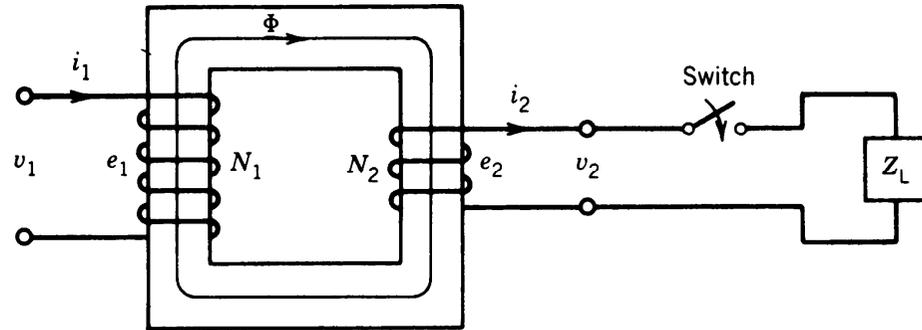- Change voltage level
- Isolation of circuits
- Match the impedance





Power transmission

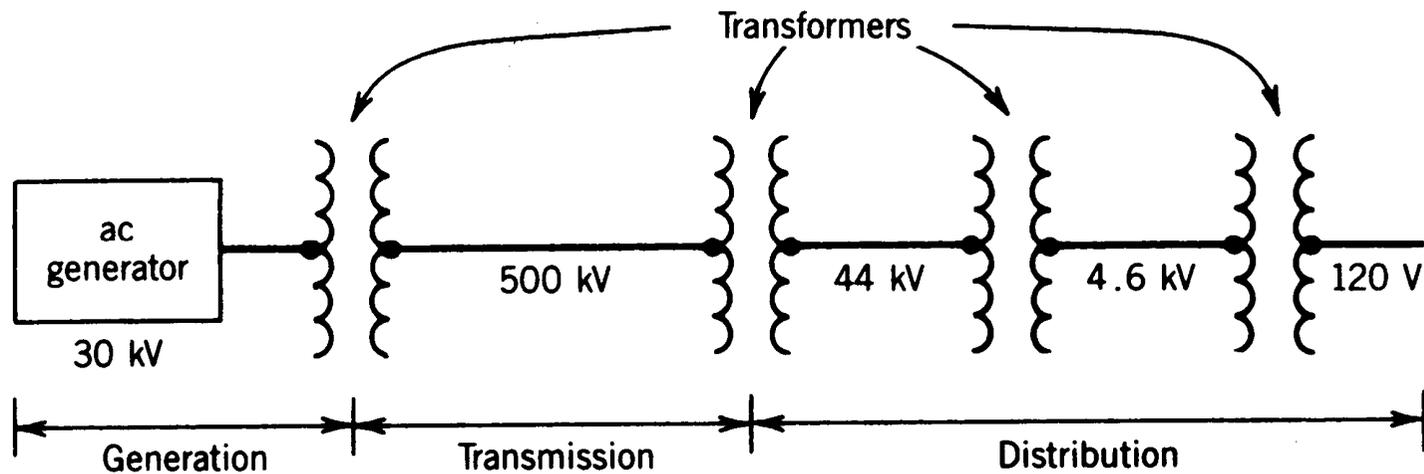


General power system configuration

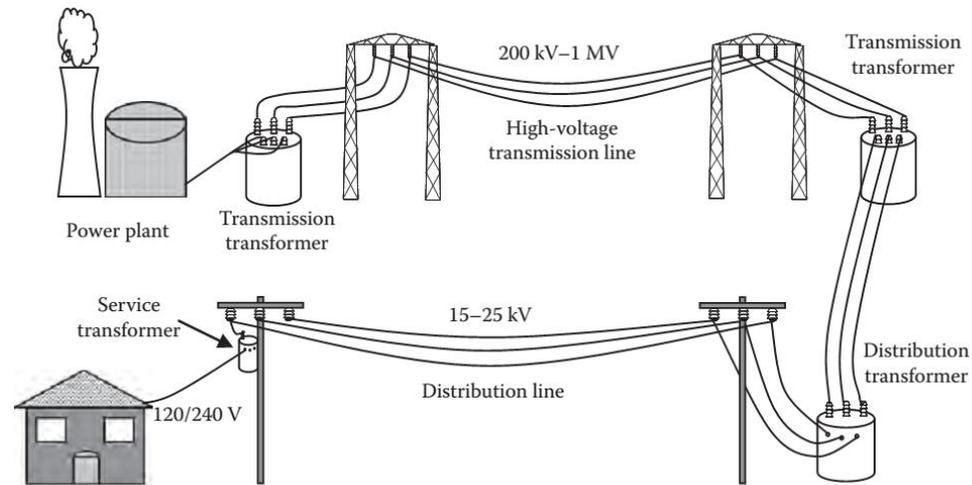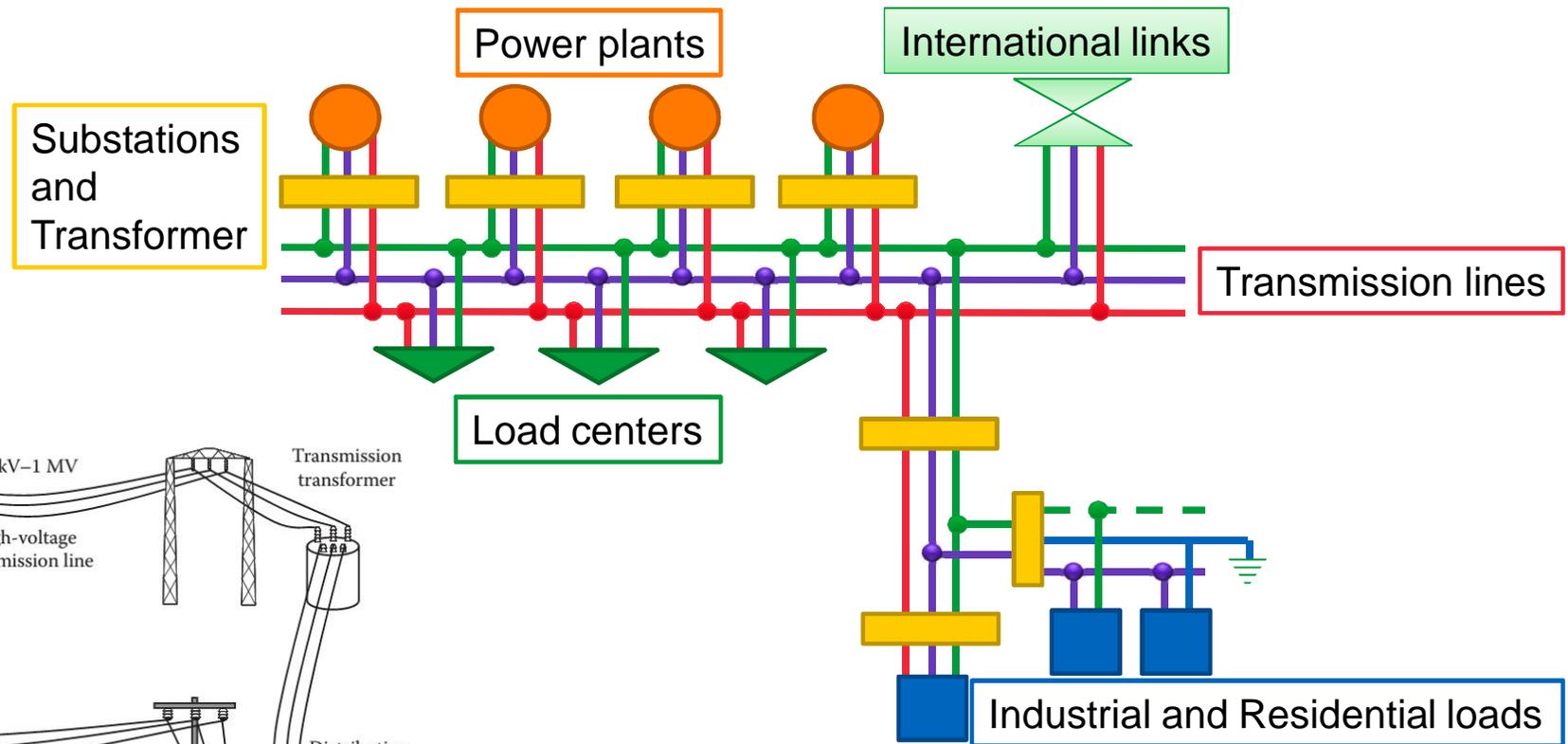- The quasi totality of the electric power generated worldwide is three-phase.




Transformer structure

Core-type

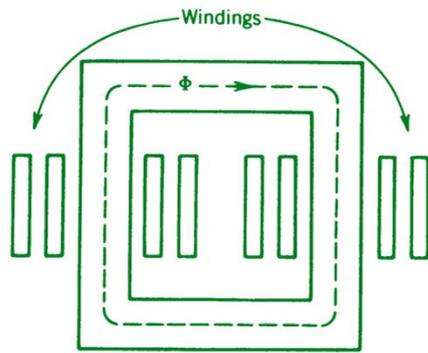


(a)

Shell-type

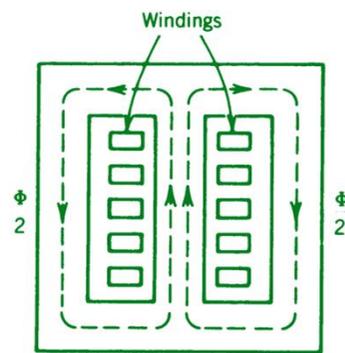

(b)

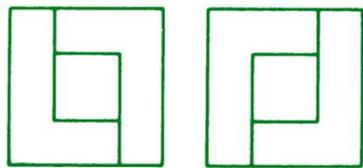


First layer

Second layer

(c)

L-shaped lamination

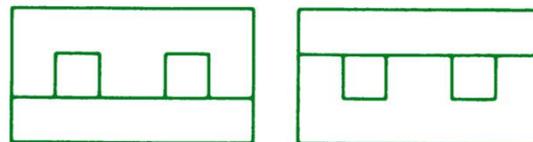

First layer


Second layer

(d)

E-shaped lamination




Core-type 3 phases version

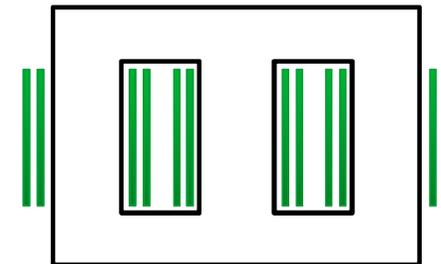

Cross section of the iron core and the windings

Ideal Transformer

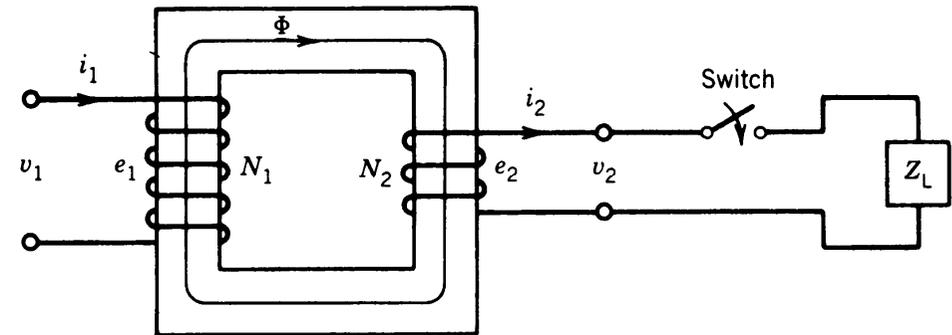- No losses
- No leakage
- No current needed for magnetizing



- Voltages

$$\left. \begin{aligned} v_1 = e_1 = N_1 \frac{dF}{dt} \\ v_2 = e_2 = N_2 \frac{dF}{dt} \end{aligned} \right\} \Rightarrow \frac{v_1}{v_2} = \frac{N_1}{N_2} = a$$

turns ratio

- Power


$$v_1 i_1 = v_2 i_2$$

- Currents


$$N_1 i_1 - N_2 i_2 = 0 \Rightarrow \frac{i_1}{i_2} = \frac{N_2}{N_1} = \frac{1}{a}$$

Impedance transfer

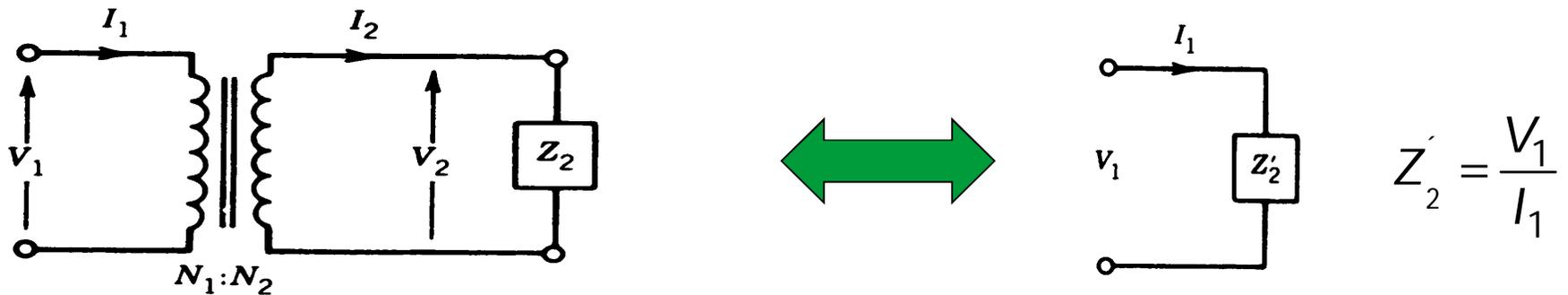How an impedance at the terminals of the secondary is seen from the primary side.



$$Z_2 = \frac{V_2}{I_2}$$

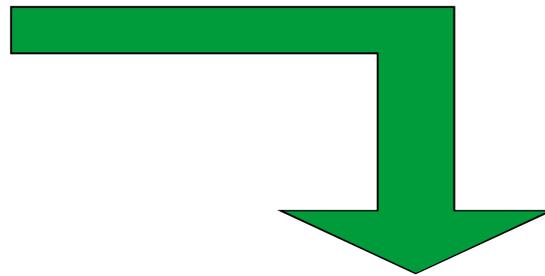

$$\frac{V_1}{V_2} = a$$

$$\frac{I_1}{I_2} = \frac{1}{a}$$



$$Z'_2 = a^2 Z_2$$

Polarity


- Current entering **identical terminals** produce fluxes in the **same direction**



e_{12} and e_{34} are in phase.

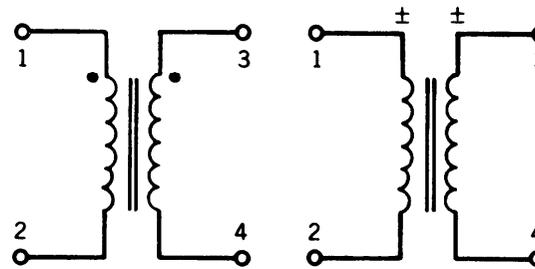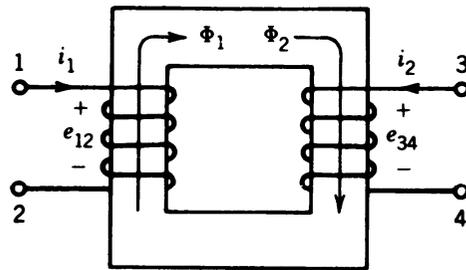

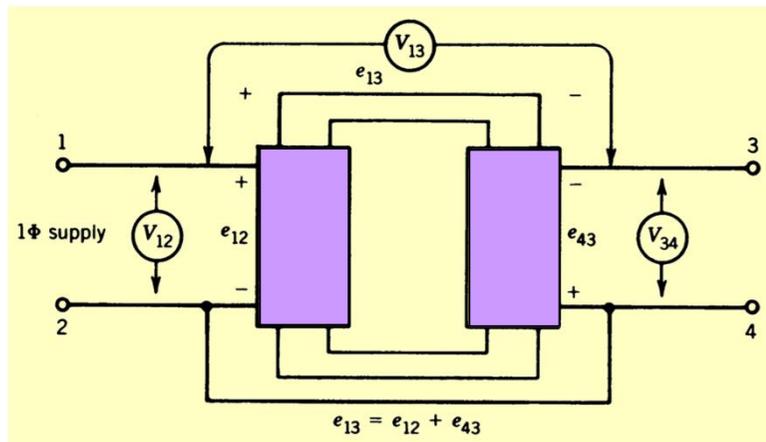Why this is important ?
 Why we cannot measure the voltages with a voltmeter ?



If $V_{13} @ V_{12} + V_{34}$ then 1 and 4 identical


If $V_{13} @ V_{12} - V_{34}$ then 1 and 3 identical

Parallel operation


Polarity mismatch



Circulating current.

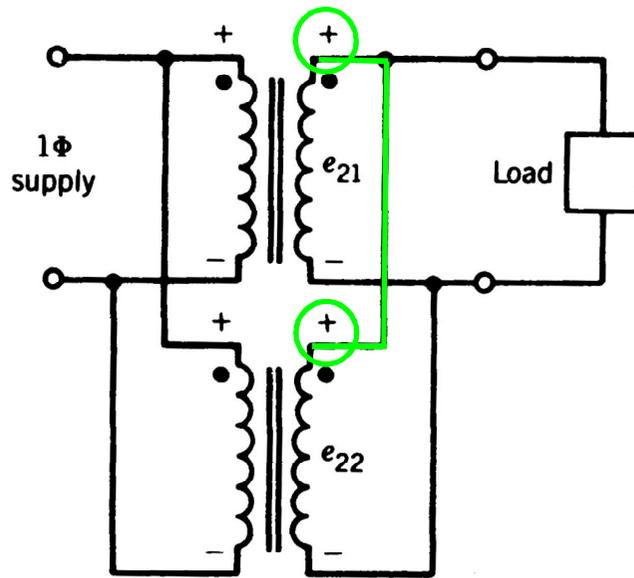


Correct connection

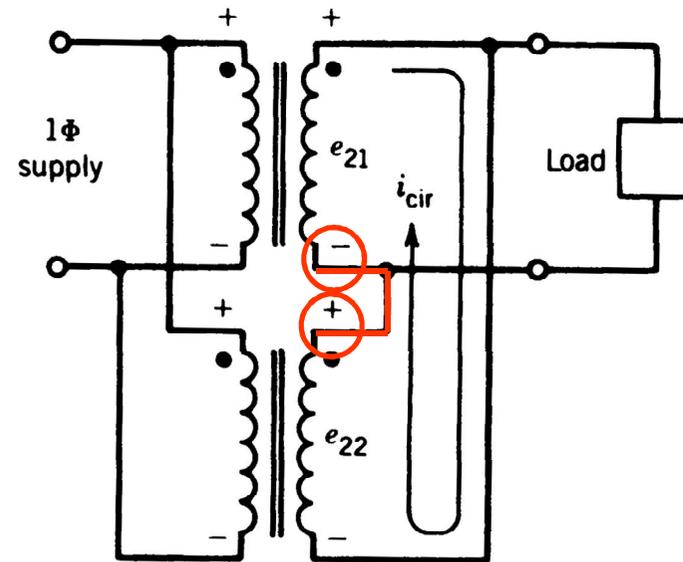

Wrong connection

Practical transformer

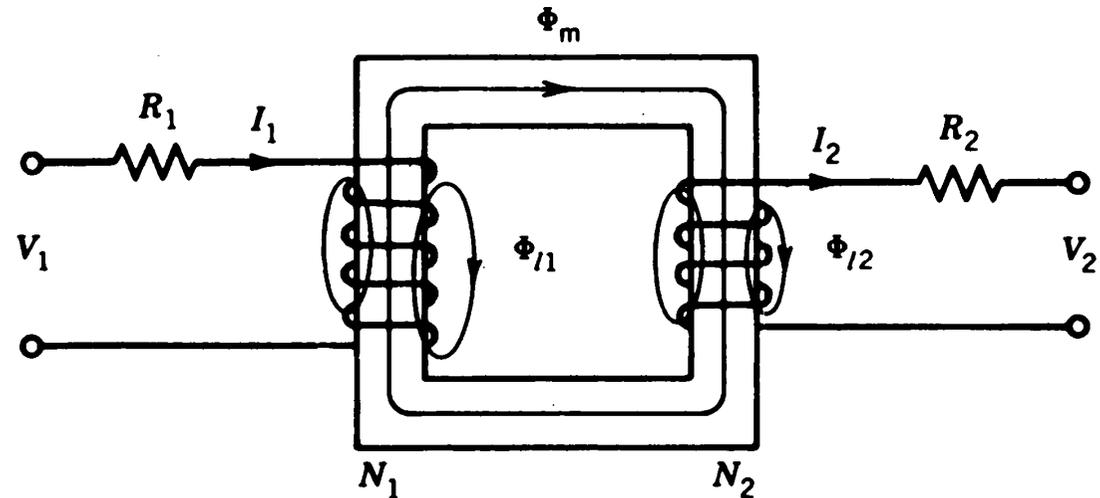
- Winding resistance
- Flux leakage
- Finite permeability
- Core losses



Transformer model is based on

- Physical reasoning
- Mathematic model of coupled circuits



Lumped-parameters equivalent circuit

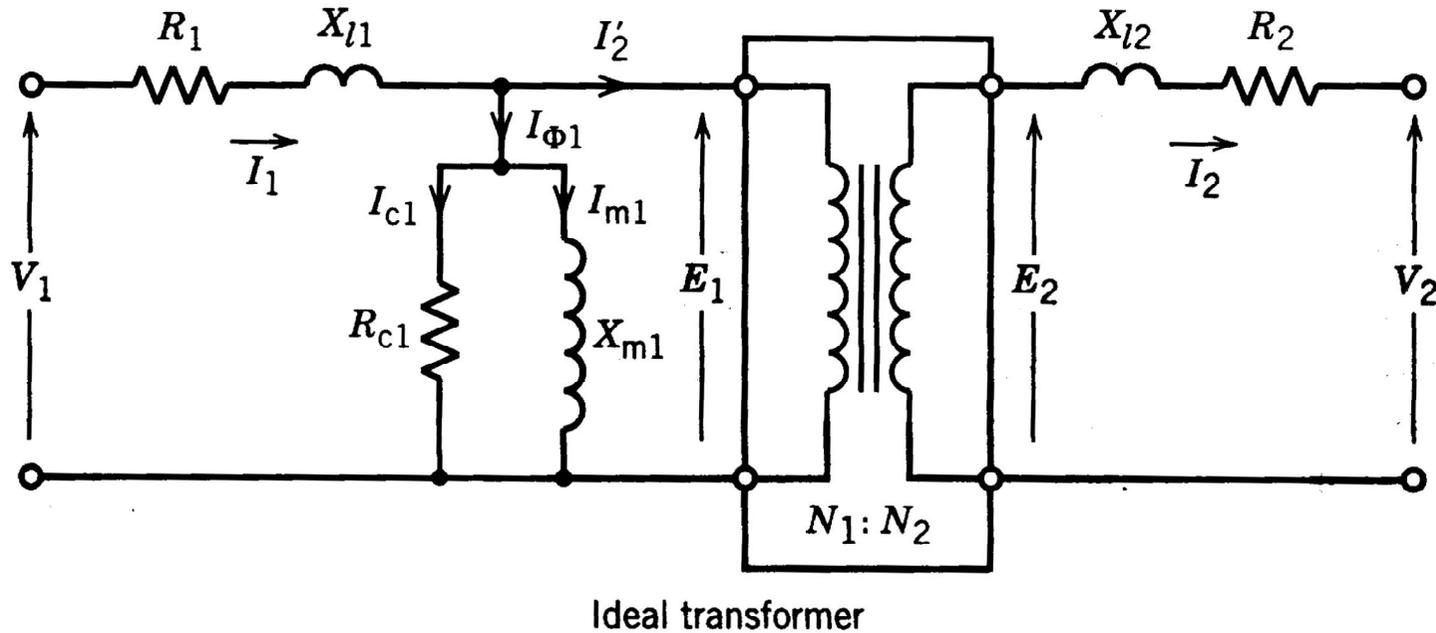

- Winding resistance in series with leakage inductance
- Magnetizing inductance in parallel with core resistance

Referred equivalent circuits

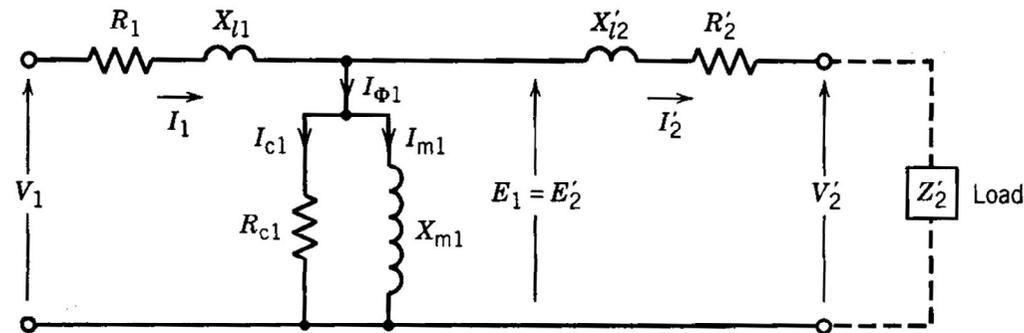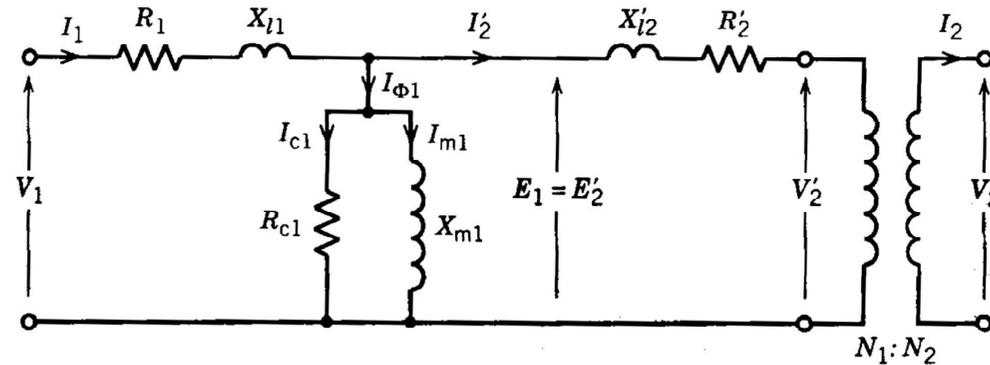- Practical transformer = Lumped parameters circuit + Ideal transformer




- Ideal transformer can be shifted to either side
- Circuit parameters are reduced to the appropriate values




Approximate Equivalent Circuits

- $I_1 R_1$ and $I_1 X_{l1}$ are small
- $|E_1| = |V_1|$
- Shunt branch can be moved to supply terminal

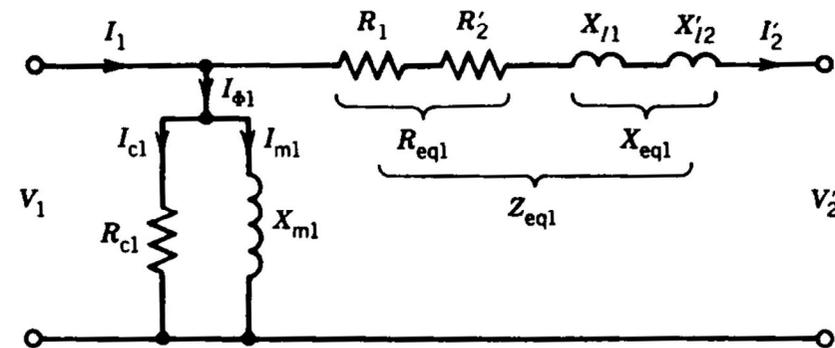


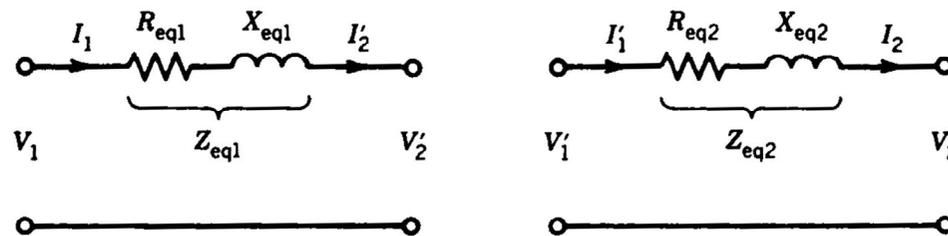- I_F small (5% of rated current)
- Shunt branch removed




Equivalent Circuit Parameters

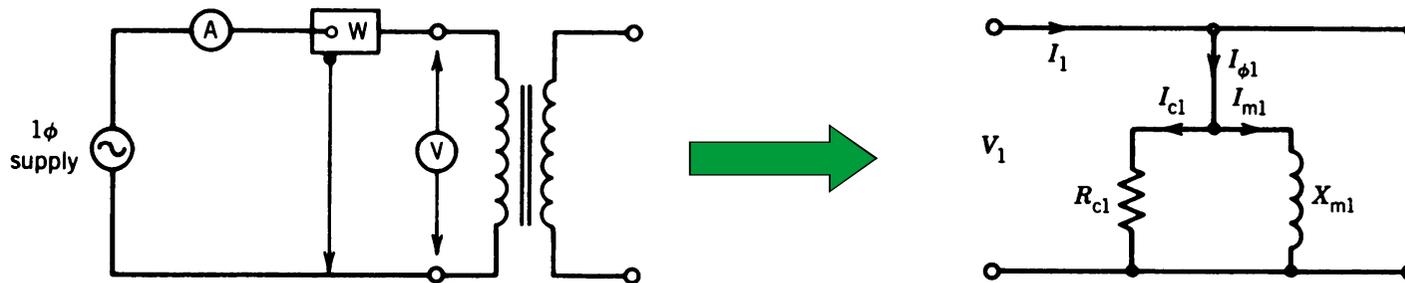- **No-load test** (rated voltage on one side whereas the other side is open)



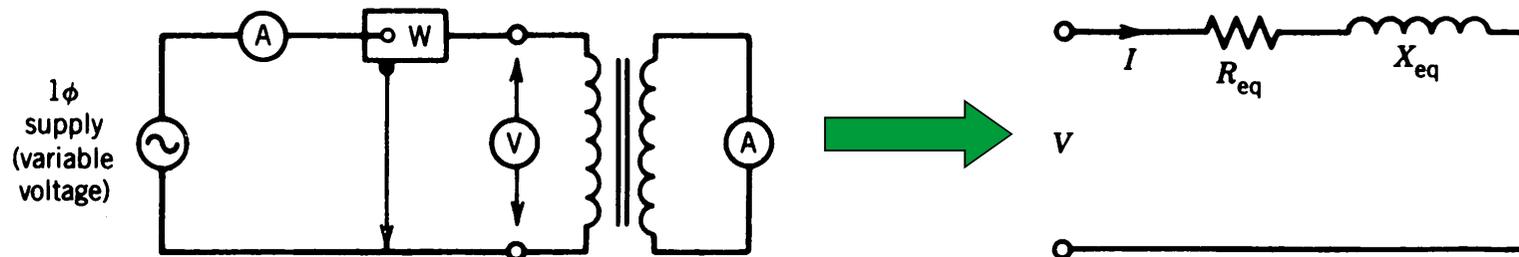
- **Short-Circuit test** (rated current on one side whereas the other side is short-circuited)



- Nameplate: S (kVA), V_1/V_2 (V)


Voltage regulation

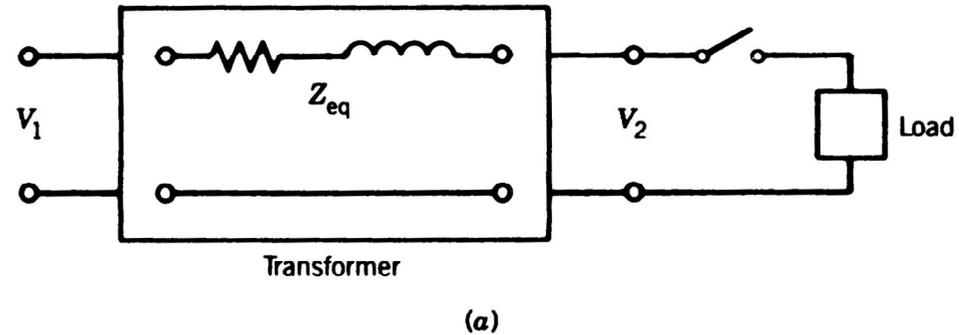- At no load: $V_2 = V_1/a$
- Loaded: $V_2 = V_1/a \pm \Delta V_2$



- Voltage regulation =

$$\frac{|V_2'|_{NL} - |V_2'|_L}{|V_2'|_L}$$

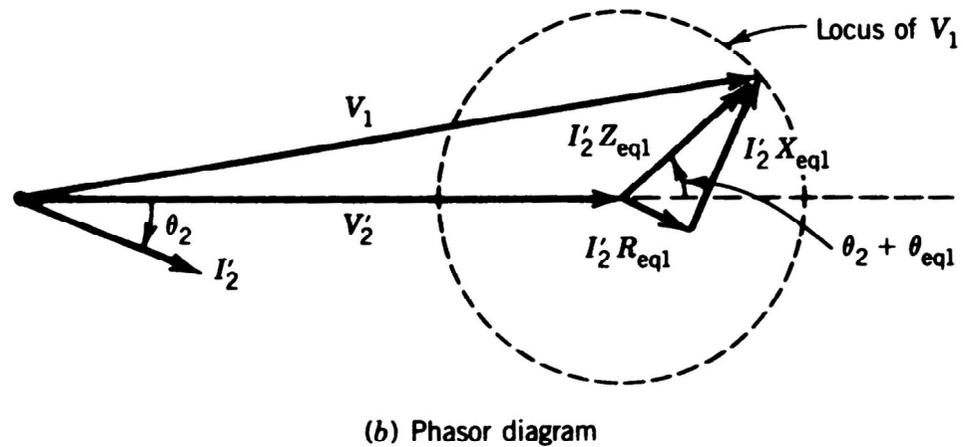

- Maximum voltage regulation occur if $\theta_L = -\theta_{eq1}$

Efficiency

- Efficiency

$$h = \frac{P_{out}}{P_{out} + P_c + P_{cu}}$$

$$h = \frac{V_2 I_2 \cos q_2}{V_2 I_2 \cos q_2 + P_c + I_2^2 R_{eq2}}$$



Fixed V_2 and θ_2


Fixed V_2 and I_2

$$P_c = I_2^2 R_{eq2}$$

$$\cos q_2 = 1$$

- All-day efficiency

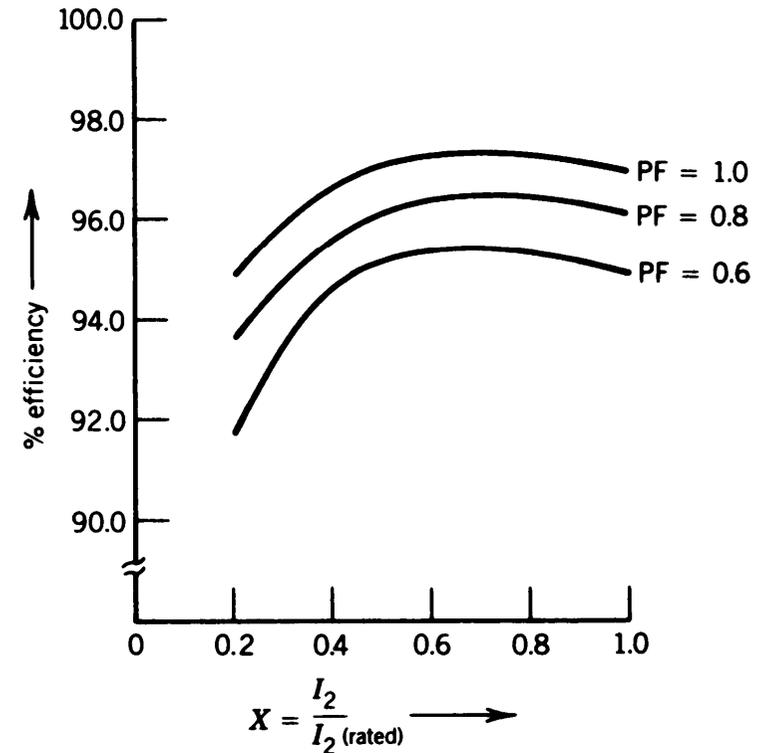
$$h_{AD} = \frac{\text{energy output over 24 hours}}{\text{energy input over 24 hours}}$$



A figure of merit for distribution transformer

Autotransformer

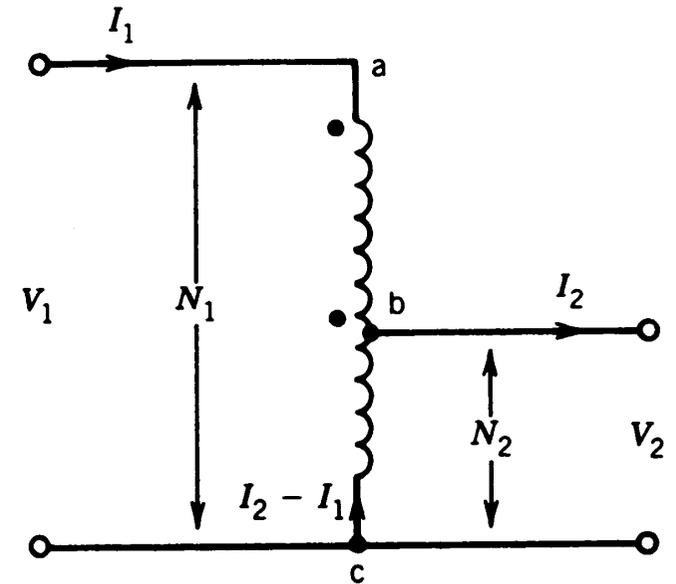- Same operation as two windings transformer
- Physical connection from primary to secondary
- Sliding connection allows for variable voltage
- Higher kVA delivery than two windings connection




- Autotransformer does not provide isolation between primary and secondary!
- Risk of hazard if not carefully connected and used

Three-phase transformer


- Three similar single-phase transformers connected to form a three-phase transformer
- Four possible connection:
Y- Δ Δ -Y Δ - Δ Y-Y
- Some connections result in phase shift

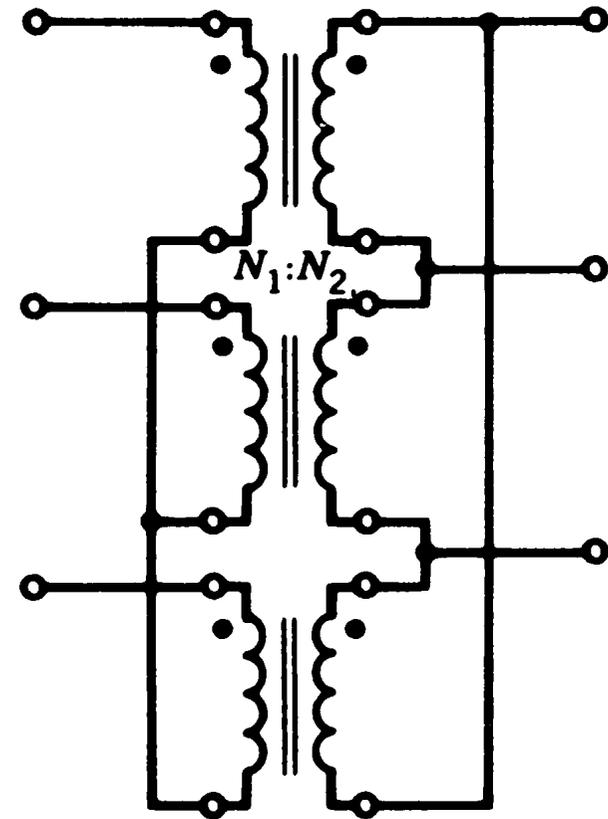Can you make a sketch of the connections?




3-phase voltage generation

- Simple generator

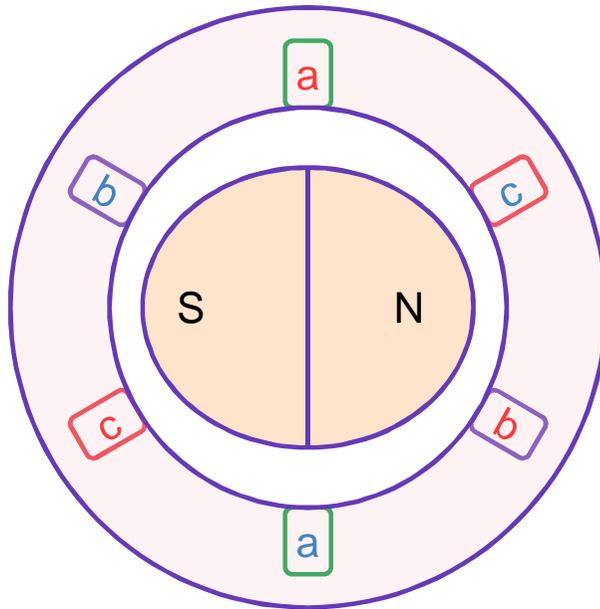


$$e = N \frac{dF}{dt}$$

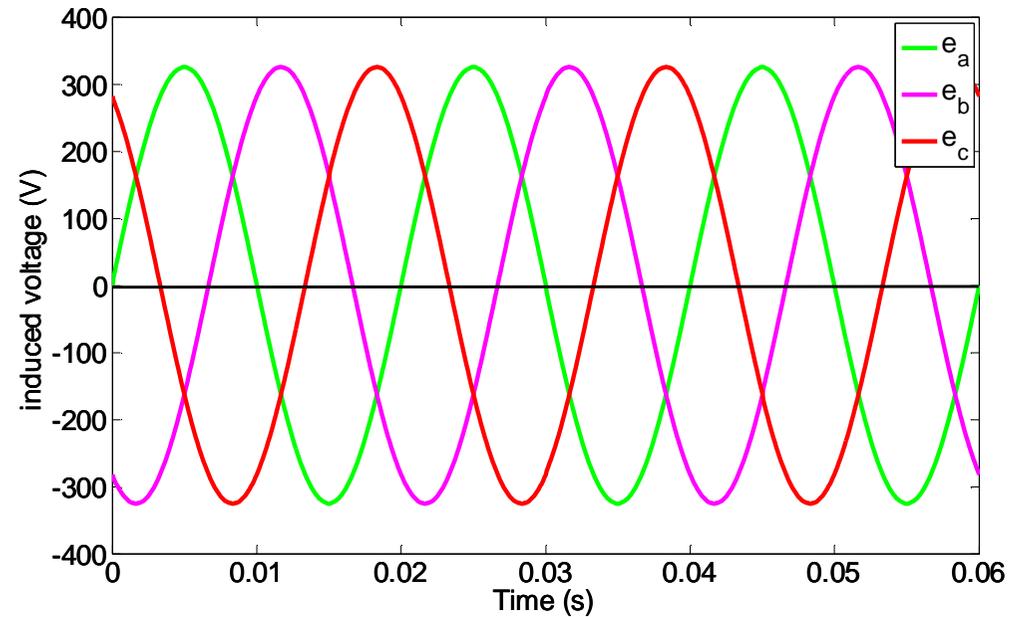

q Better utilization of iron and other materials

Connecting the 3-phase voltages

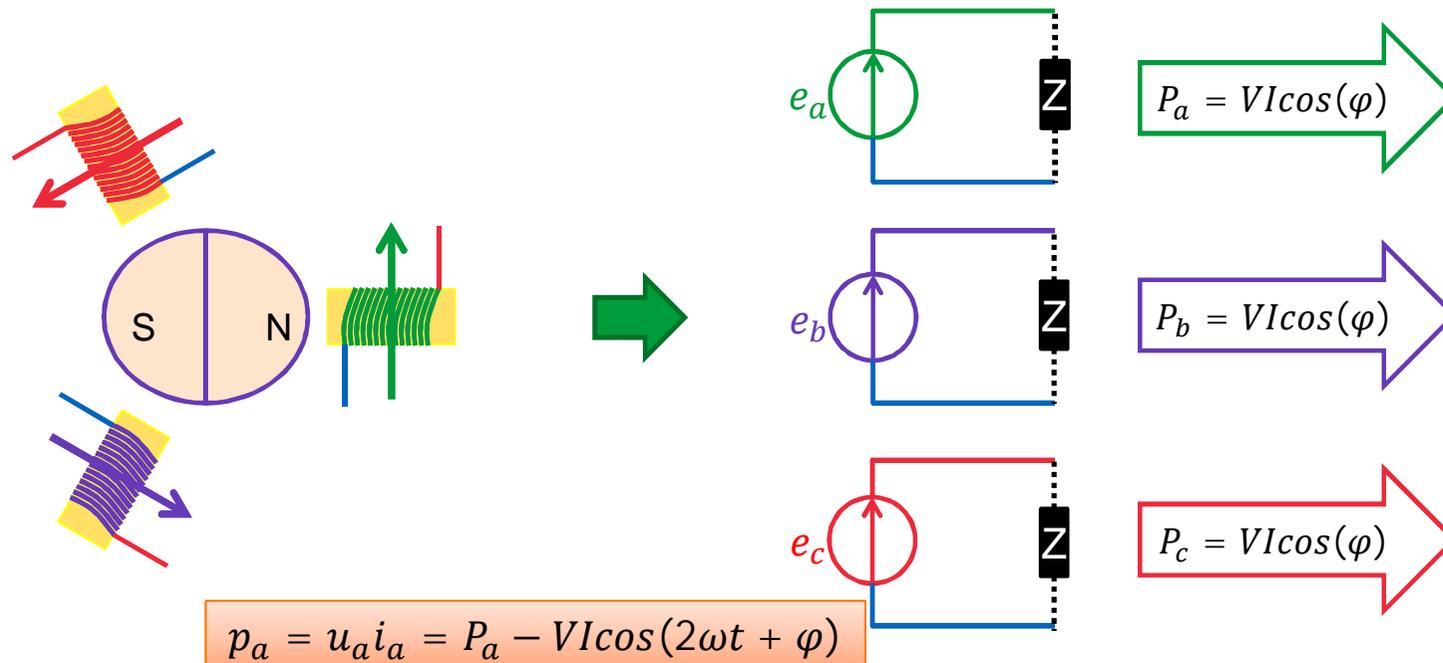
- 3 single-phase circuits at different phase angle!



- q The average power over one period is constant
- q The instantaneous power is pulsating

Connecting the 3-phase voltages

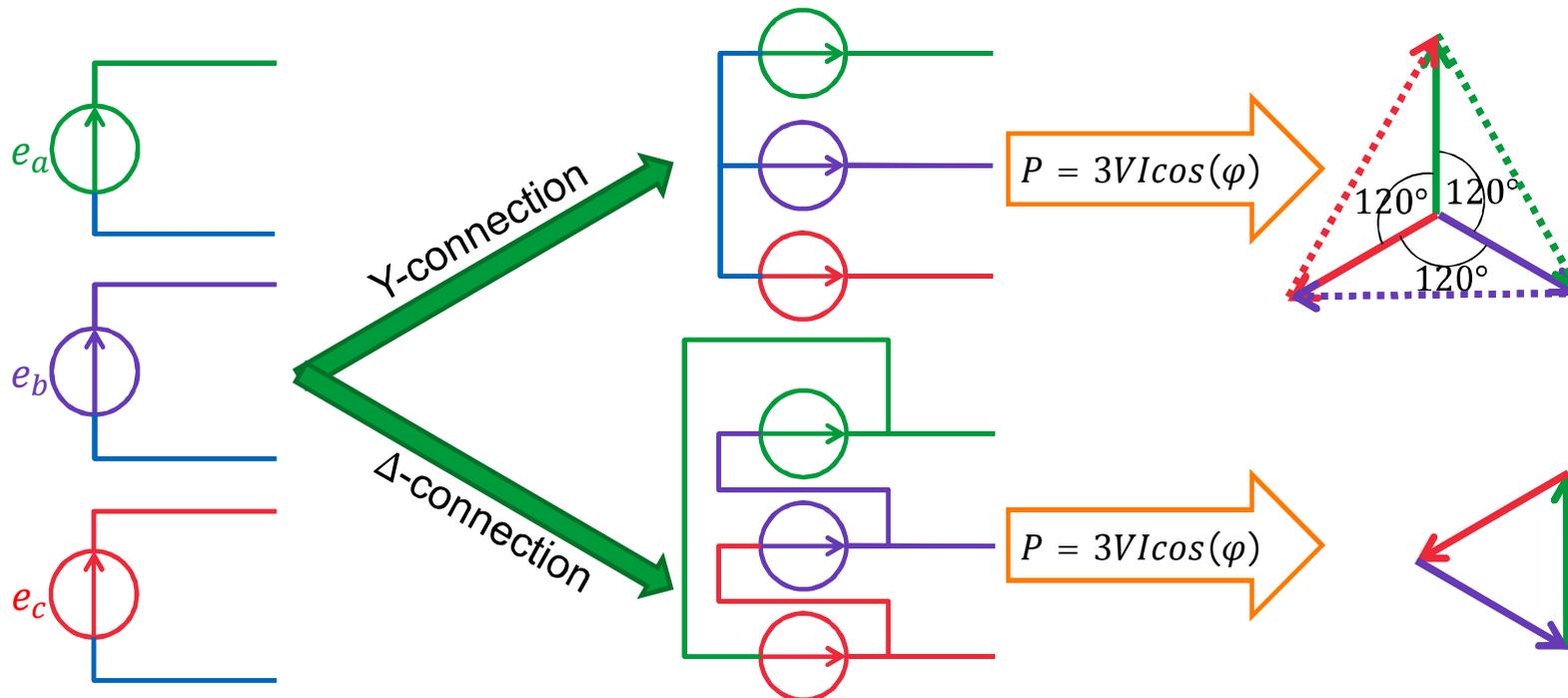- The potential difference is known but not the potentials !




$$p = u_a i_a + u_b i_b + u_c i_c = 3P_a$$


- q The same power can be transferred with only 3 wires instead of 6
- q The instantaneous power of 3 phase system is constant over time

Connections

- Y- Δ is used for voltage step-down

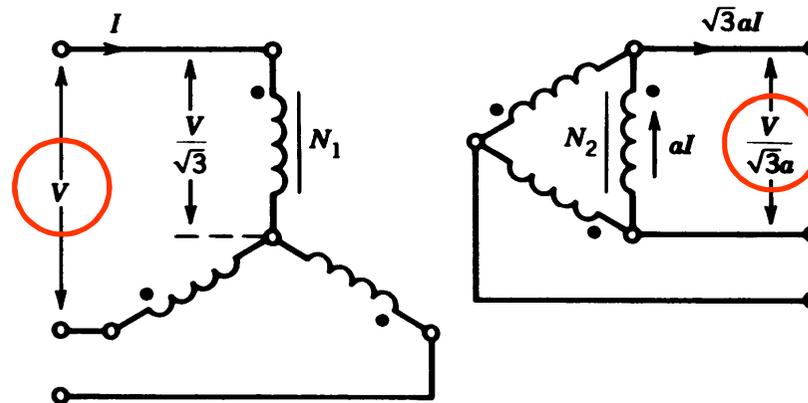


- Δ -Y is used for voltage step-up

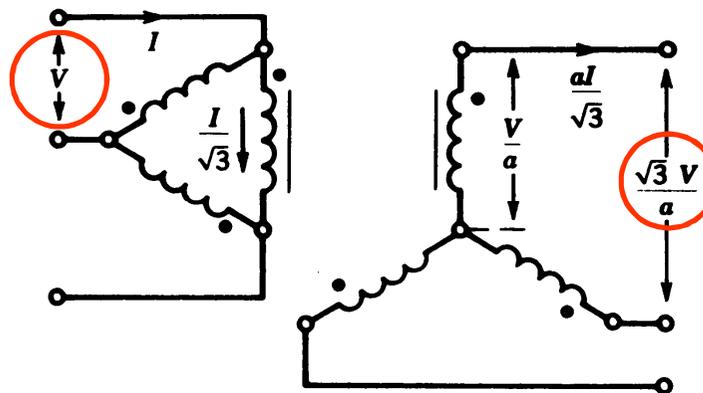


Connections - continue

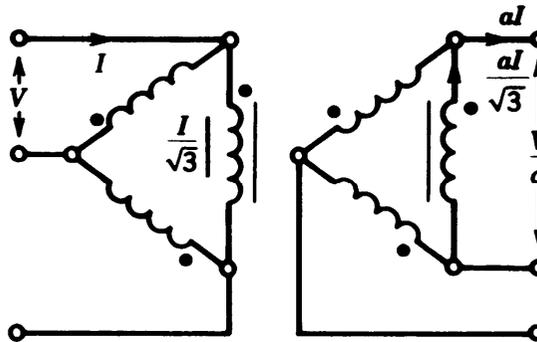
- Δ - Δ only possibility for open-delta connection



- Y-Y seldom used

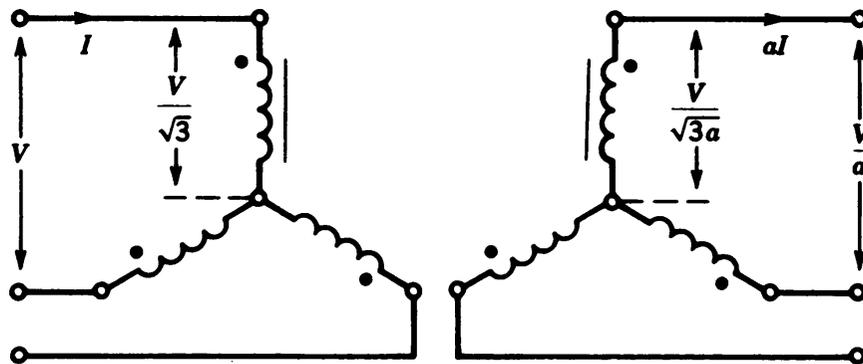

Phase shift

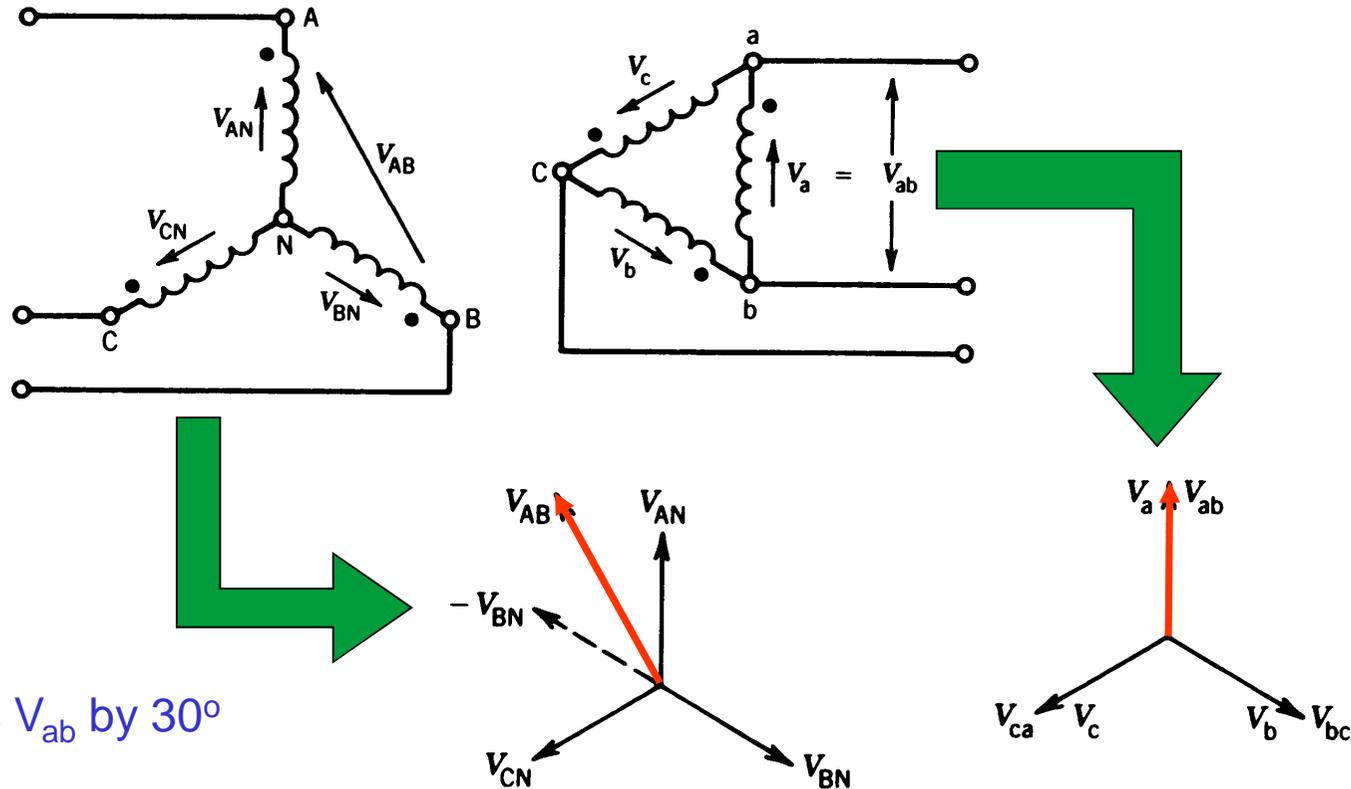

- $V_{AN} \parallel V_a$
- V_{AB} leads V_{ab} by 30°


- Δ -Y also provides line-to-line phase shift
- Y-Y and Δ - Δ connections have no phase shift

Can you draw the phasor diagram for Δ -Y connection?

Single-phase equivalent circuit


Validity conditions:

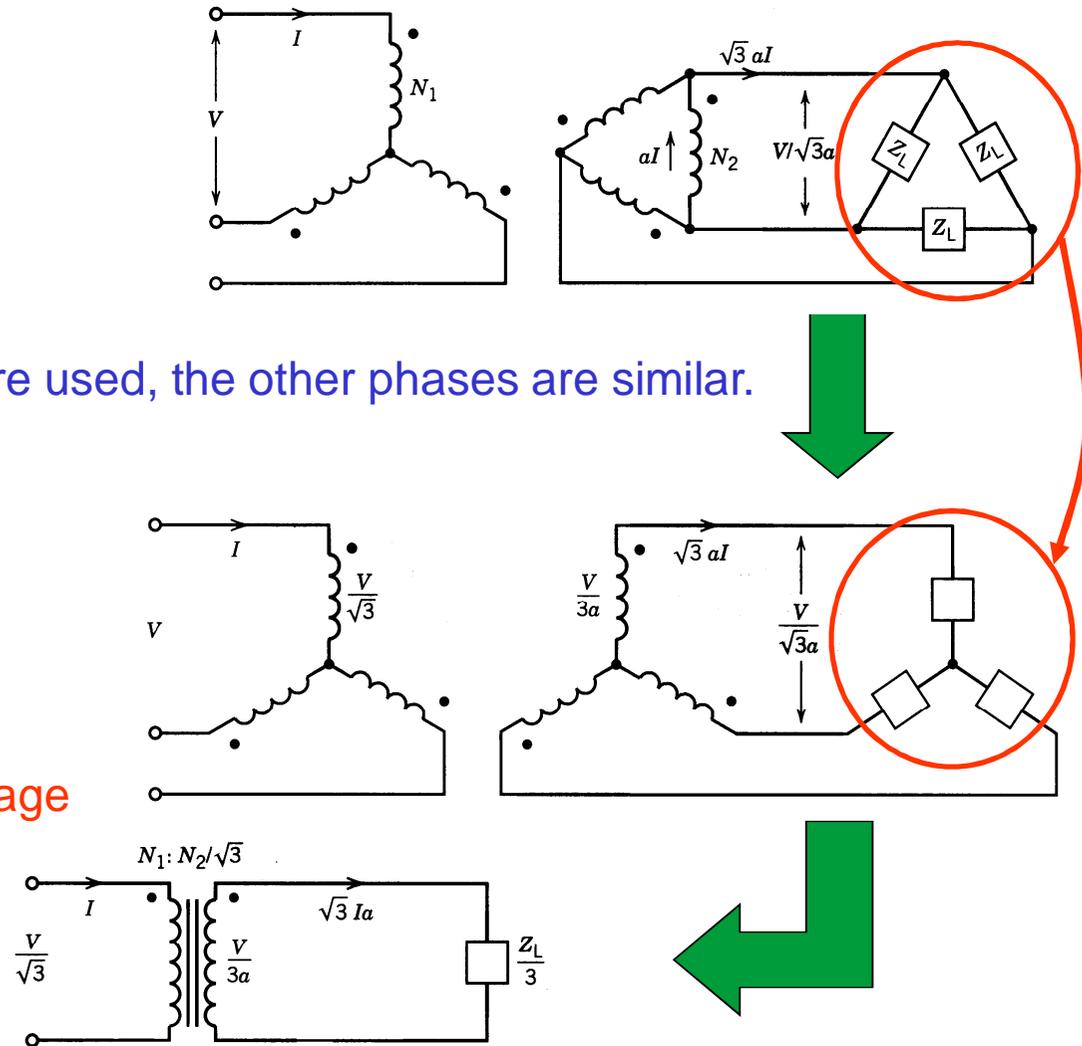- Identical transformers
- Balanced source and load
- Only one phase variables are used, the other phases are similar.
- Equivalent Y-representation
- Line-to-neutral = phase voltage



Three-phase transformer - open delta connection

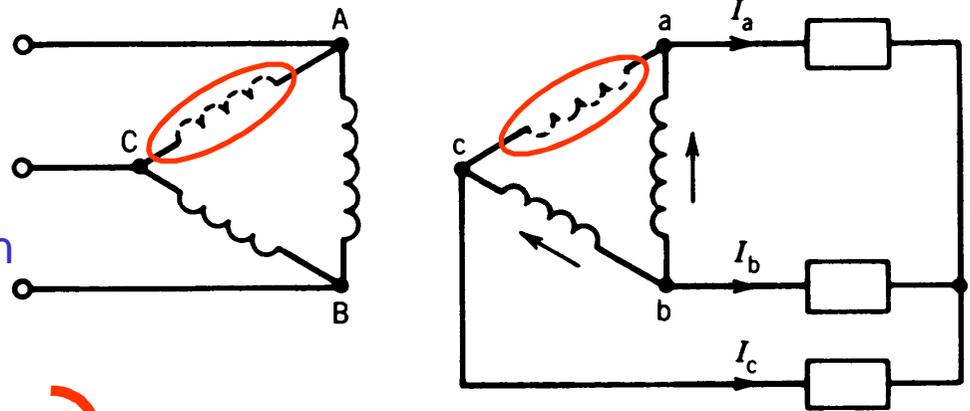
- One phase can be removed
- Operation at reduced load
- Possible only in Δ - Δ connection



$$P_{bc} = V_{bc} I_c \cos(30 - f)$$

$$P_V = P_{ab} + P_{bc} = 2VI \cos 30^\circ$$


$$P_D = 3VI$$

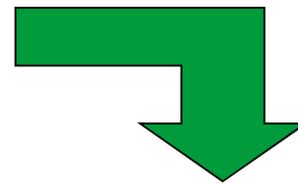

$$\frac{P_V}{P_D} = \frac{2 \cos 30^\circ}{3} = 0.58$$


Three-phase transformer unit

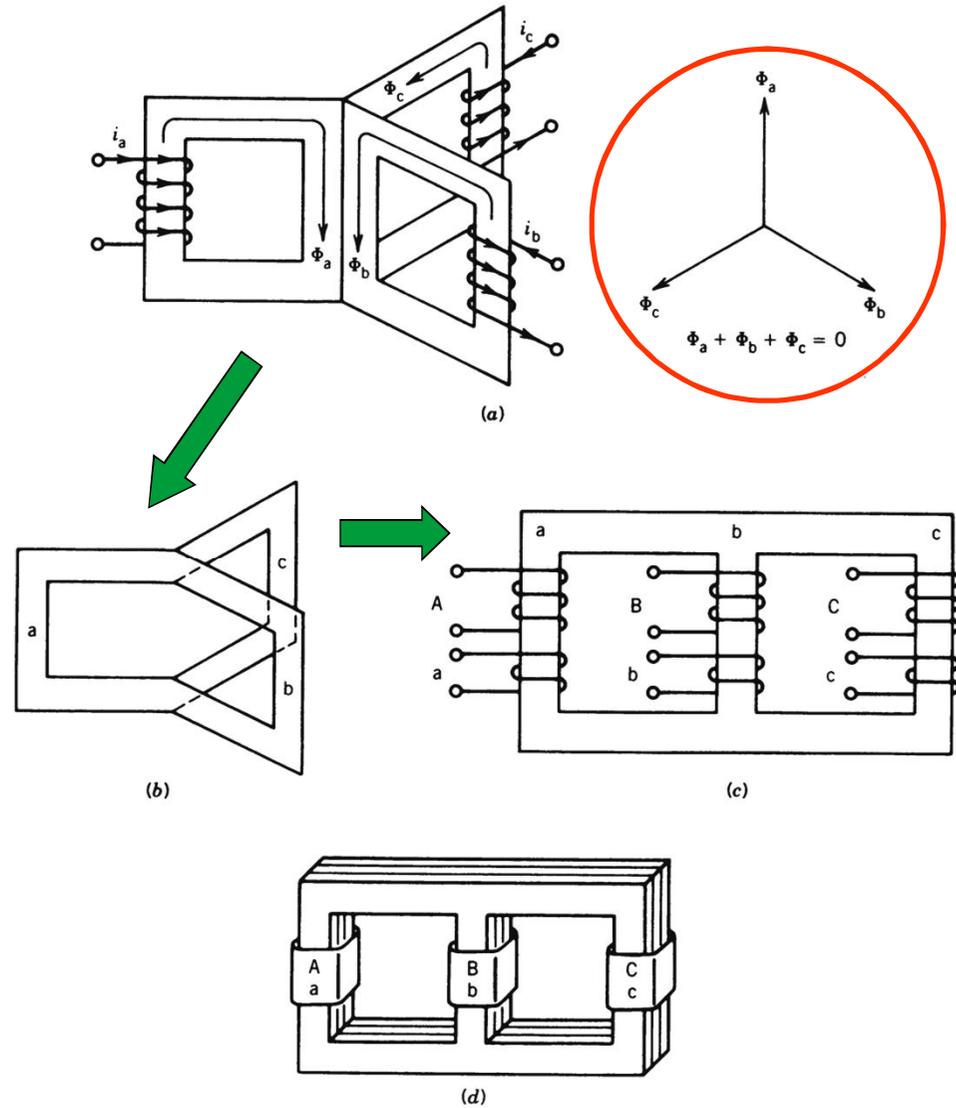- Balanced three-phase voltage
- Balanced three-phase flux
- Return leg can be removed
- In-plan construction easy to manufacture
- Same operation as transformer bank




Harmonics in Three-Phase Transformer Banks

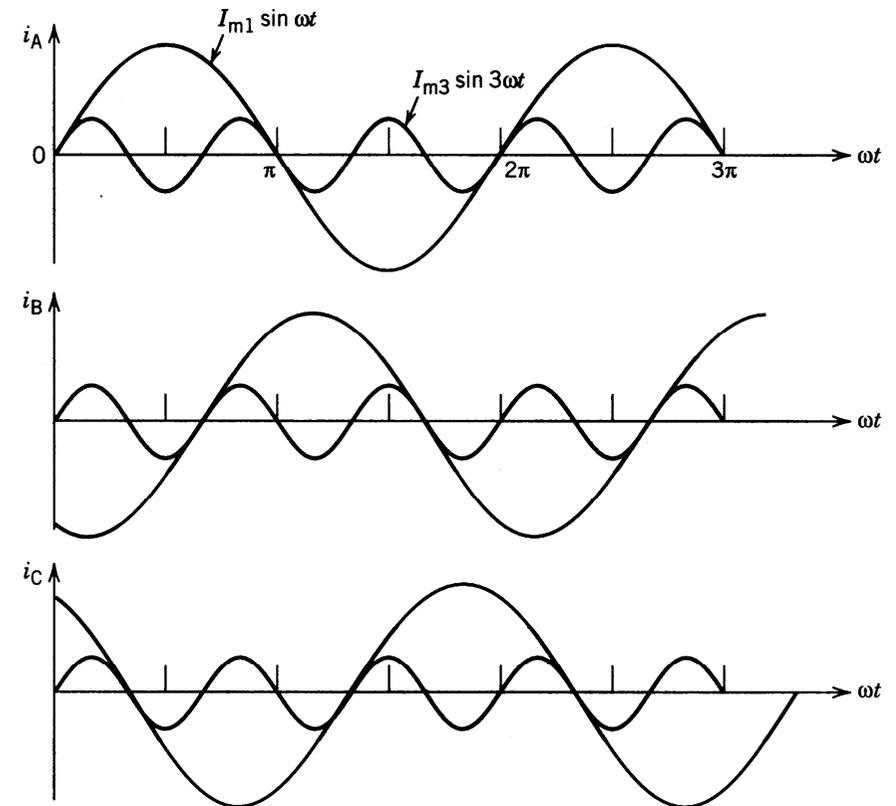- Transformers are designed to operate at saturation
- Exciting current is non-sinusoidal with predominant third harmonic
- Third harmonics are in phase
- Third harmonic exists either in currents or in fluxes



Harmonics in Three-Phase Transformer Banks Yy+d

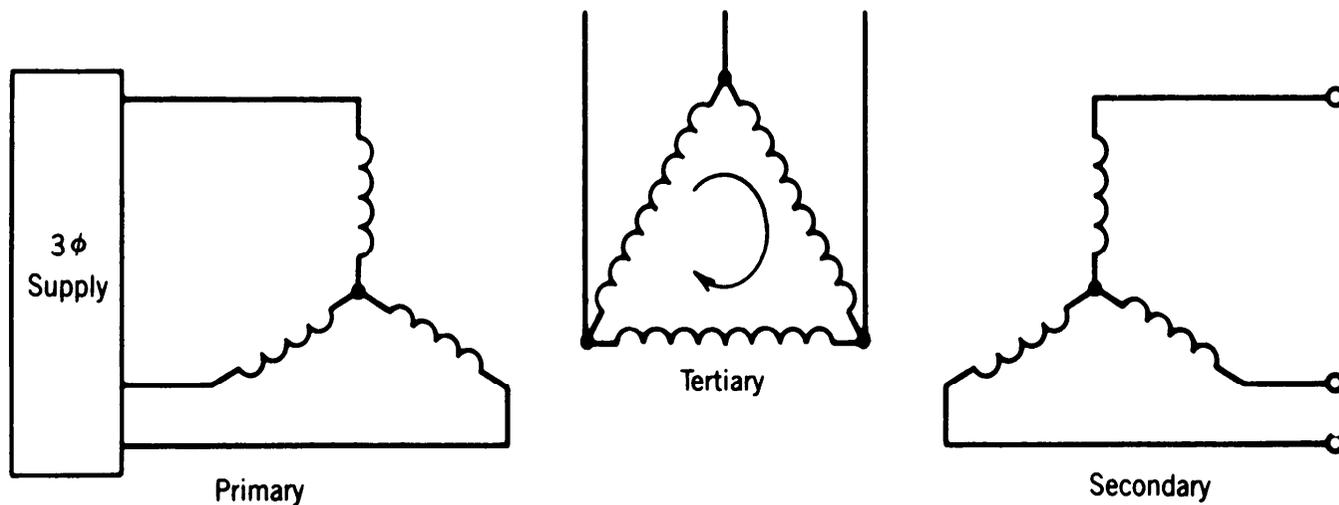- Third harmonic current prohibited from both sides
- Tertiary provides the missing third harmonic current
- Voltages sinusoidal
- Tertiary can supply auxiliary load if needed





Per-unit system

- Base (reference) value of the quantity $P_{\text{base}}, V_{\text{base}}$

$$I_{\text{base}} = \frac{P_{\text{base}}}{V_{\text{base}}}$$
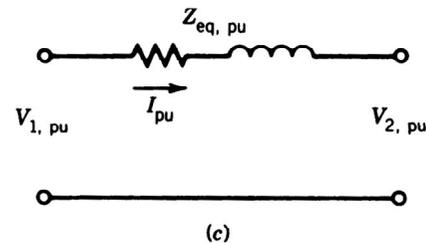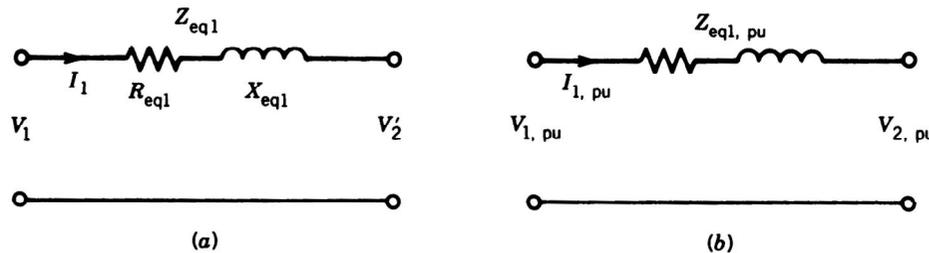
$$Z_{\text{base}} = \frac{V_{\text{base}}}{I_{\text{base}}}$$



$$\text{pu-quantity} = \frac{\text{actual } q}{\text{base } q}$$

- pu voltage equation and full load copper losses

$$V_{1, \text{pu}} = I_{1, \text{pu}} Z_{\text{eq1, pu}} + V_{2, \text{pu}} \quad \text{Independent of the side}$$

$$P_{\text{Cu, FL}} = R_{\text{eq1, pu}}$$