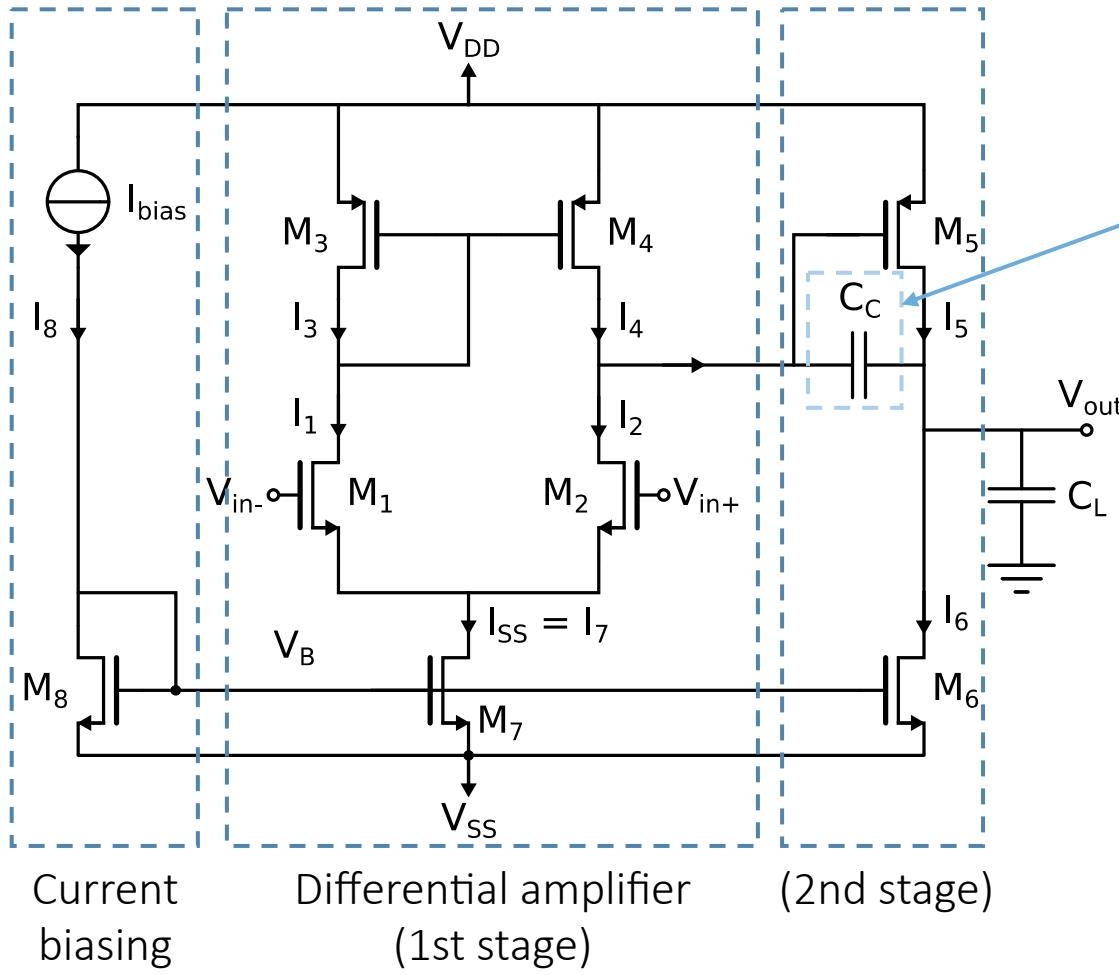


ELEC-E3510 Basics of IC Design

Lecture 5: Two stage amplifiers


Operational amplifier




Compensation

- 2 gain stages (80...120dB)
- Differential input stage
- Miller compensation
- Current biasing

Symbol:

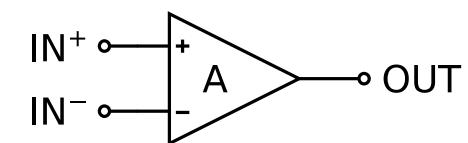

Two stage amplifier

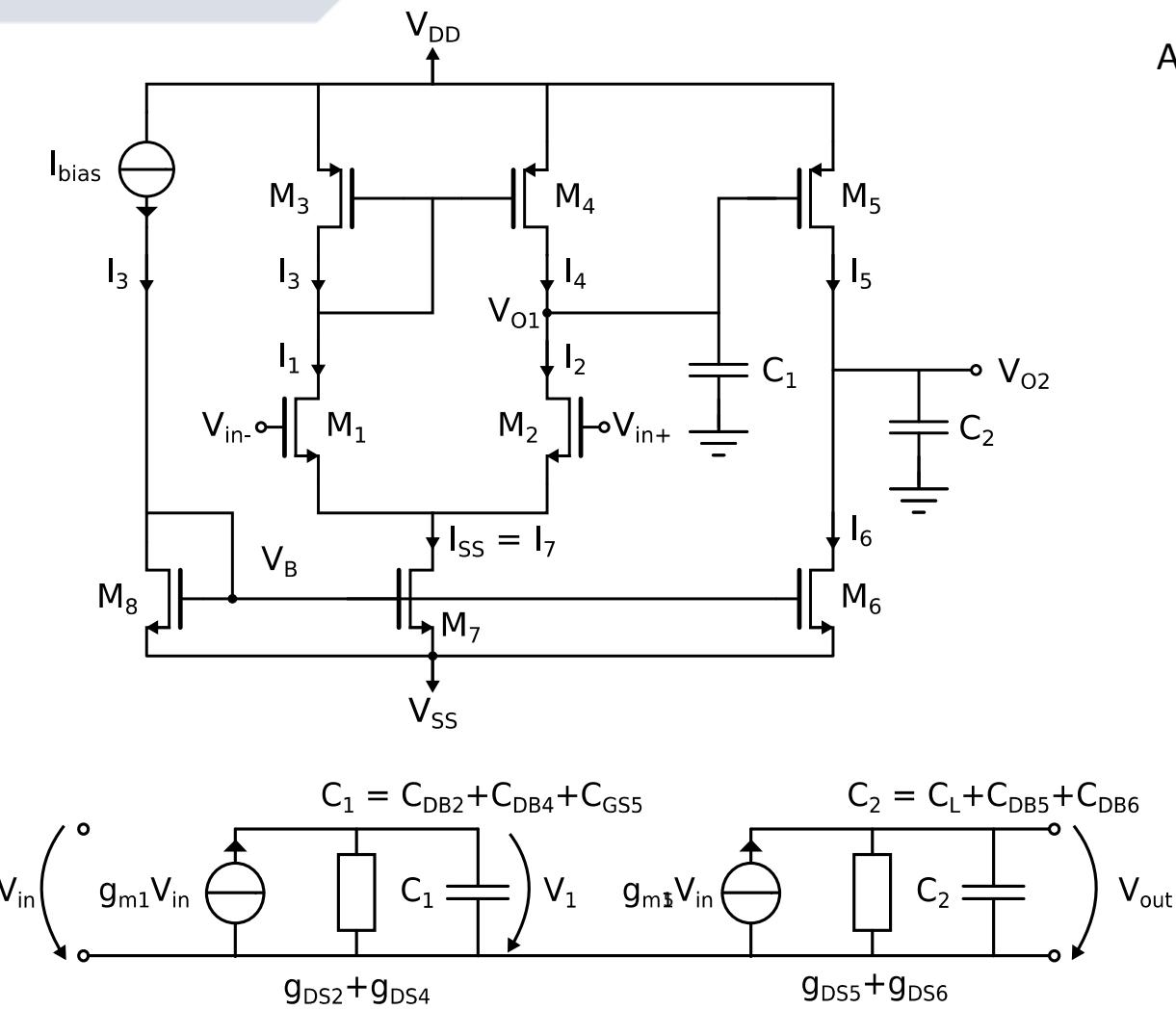



Assume single pole approximation for the gain stages:

$$A_1(s) = \frac{V_1}{V_{in}} = \frac{A}{1 + \frac{s}{s_{p1}}} ; \quad \begin{cases} A_1 = \frac{g_{m1}}{g_{DS2} + g_{DS4}} \\ s_{p1} = \frac{g_{DS2} + g_{DS4}}{C_1} \end{cases}$$

$$A_2(s) = \frac{V_{out}}{V_1} = \frac{A_2}{1 + \frac{s}{s_{p2}}} ; \quad \begin{cases} A_2 = \frac{g_{m5}}{g_{DS5} + g_{DS6}} \\ s_{p2} = \frac{g_{DS5} + g_{DS6}}{C_2} \end{cases}$$

$$A(s) = A_1(s) \cdot A_2(s) = \frac{A_1 A_2}{\left(1 + \frac{s}{s_{p1}}\right) \left(1 + \frac{s}{s_{p2}}\right)}$$
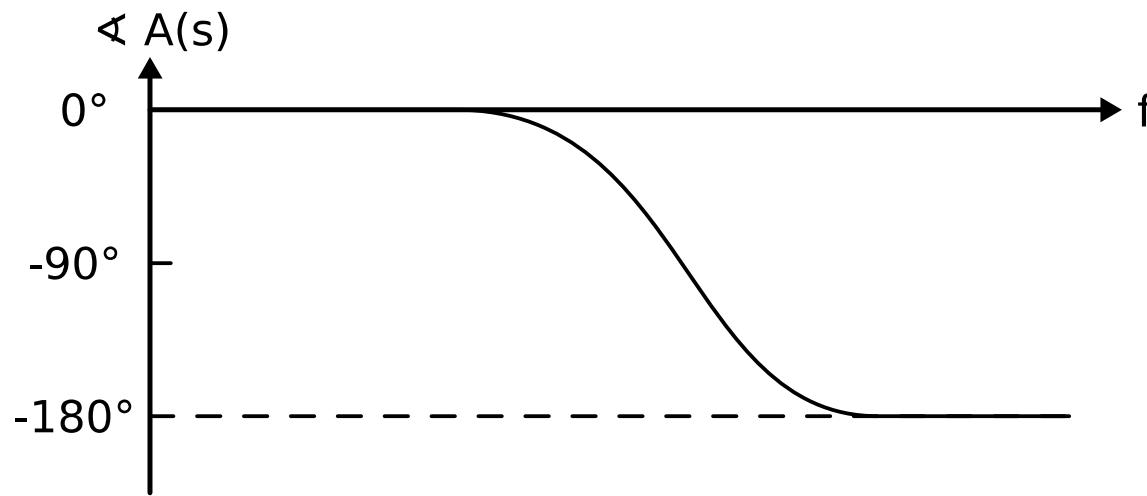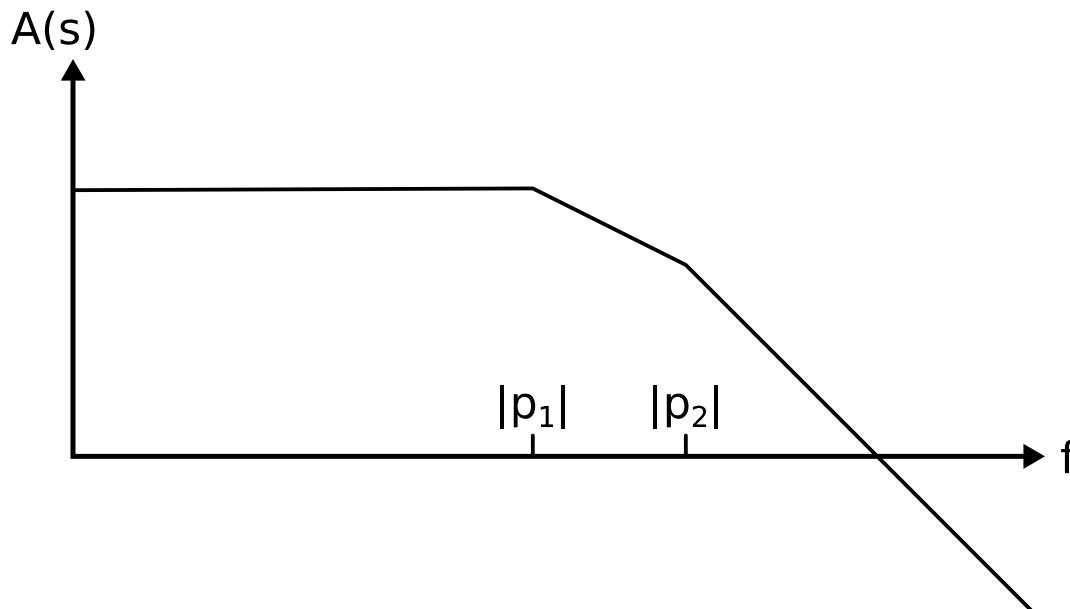
$$A_1 A_2 = \frac{g_{m1} g_{m5}}{(g_{DS2} + g_{DS4})(g_{DS5} + g_{DS6})}$$



Two poles are:

$$s_{p1} = \frac{g_{DS2} + g_{DS4}}{C_1}$$

$$s_{p2} = \frac{g_{DS5} + g_{DS6}}{C_2}$$

Typically

$$g_{DS2} \approx g_{DS4} \approx g_{DS5} \approx g_{DS6}$$

$$C_2 = (5 \dots 10) \cdot C_1$$


p_1 and p_2 are close to each other

⇒ poor phase margin

An additional pole p_3 will make the system unstable

⇒ frequency compensation needed!

Stability of cascaded amplifiers

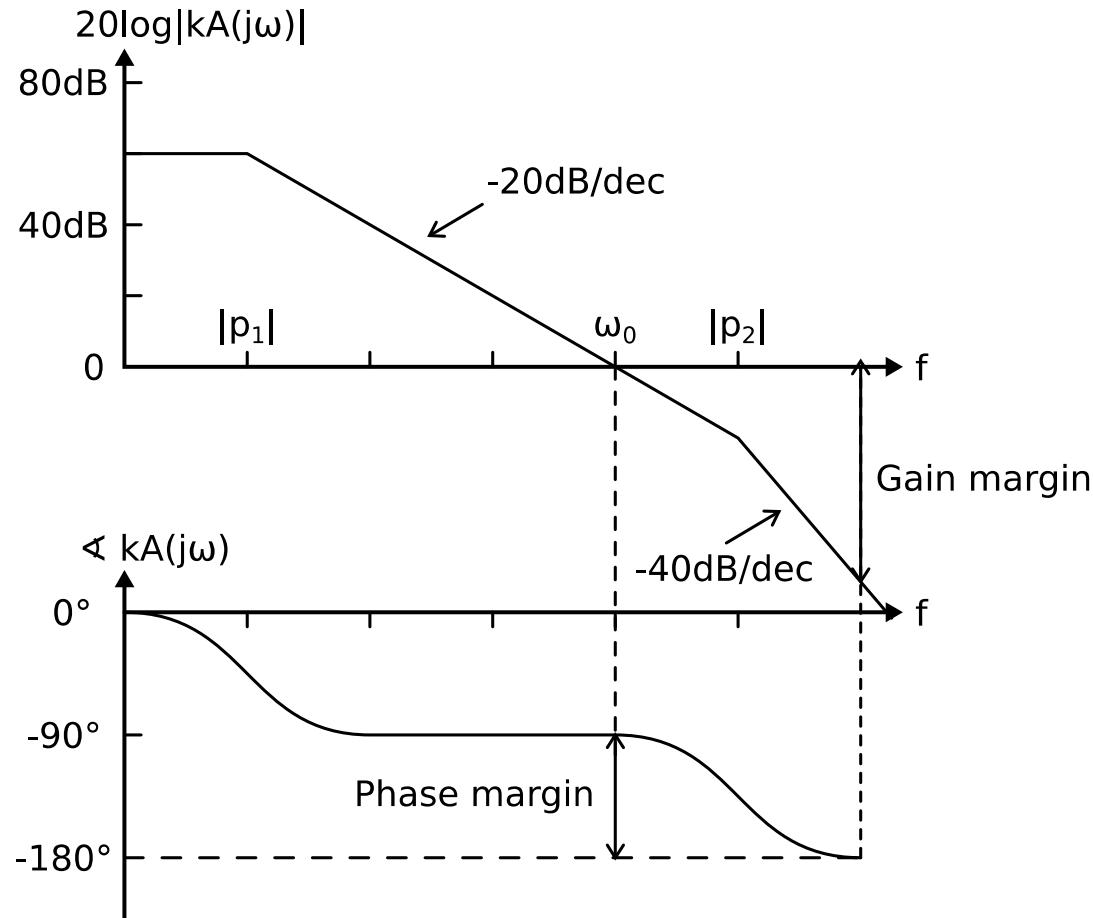

Stability:

$$|kA(s)| < 1, \text{ when phase shift is } -180^\circ$$

Define:

$$|kA(j\omega_0)| = 1 \quad @ \quad \omega = \omega_0$$

Check for the stability:


$$\text{Phase margin: } PM = \text{phase}(kA_v(j\omega_0)) + 180^\circ$$

$$\text{Gain margin: } GM[\text{dB}] = 20\log|kA_v(j\omega_{180^\circ})|$$

For stability: $PM > 45^\circ$

$$GM < -12\text{dB}$$

Compensation

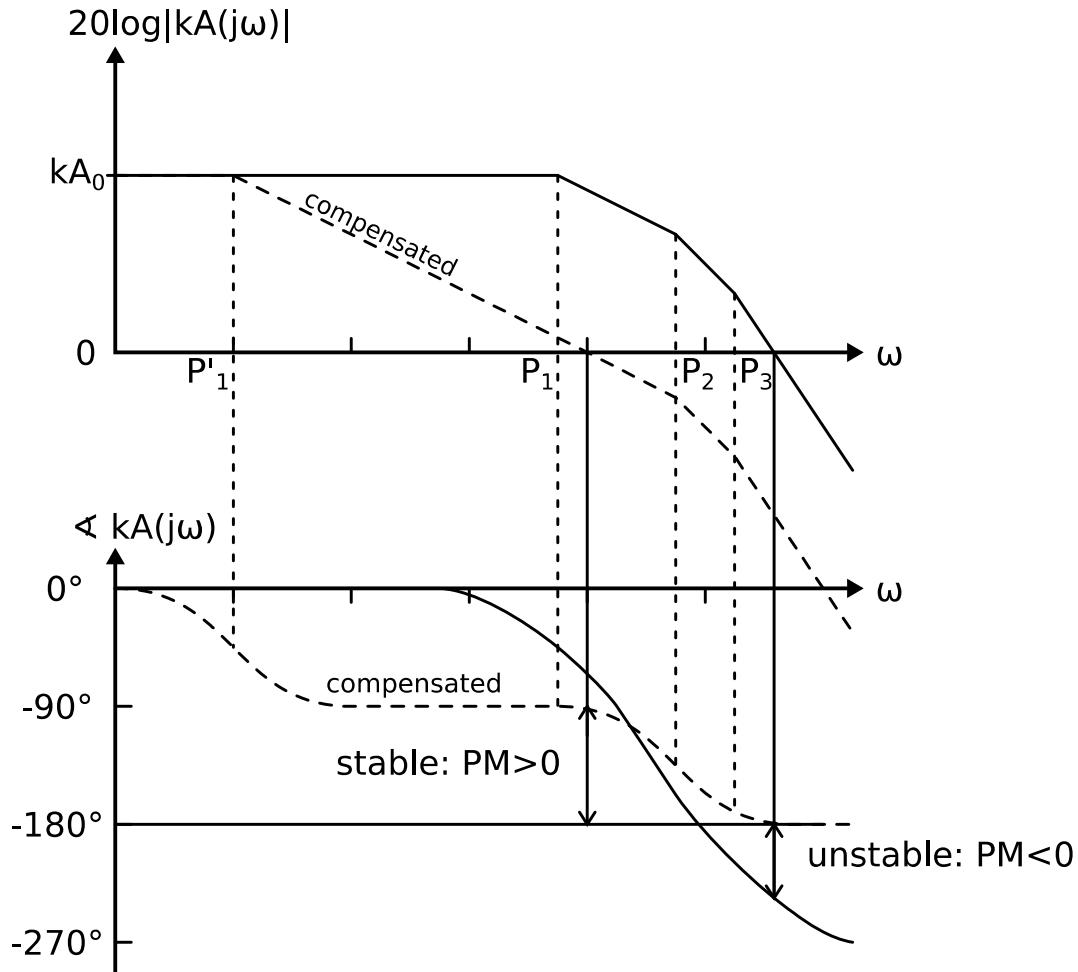

Uncompensated

$$p_1 \lesssim p_2 \lesssim p_3$$

Compensated


$$p_1' \ll p_2, p_3$$

p_1' becomes the dominant pole

Miller compensation!

$$P_1' \ll p_2$$

Miller compensation

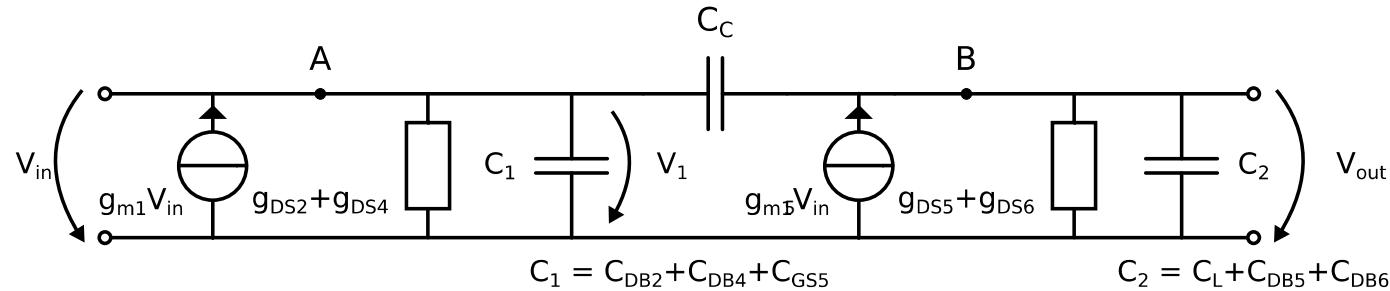


Current equations at nodes A and B


$$\begin{aligned} A & -g_{m1}V_{in} + (g_{DS2} + g_{DS4} + sC_1)V_1 + sC_c(V_1 - V_{out}) = 0 \Big| : V_{in} \\ B & sC_c(V_{out} - V_1) - g_{m5}V_1 + (g_{DS5} + g_{DS6} + sC_2)V_{out} = 0 \end{aligned}$$

Eliminate $\frac{V_1}{V_{in}}$, and solve $A(s) = \frac{V_{out}}{V_{in}}$
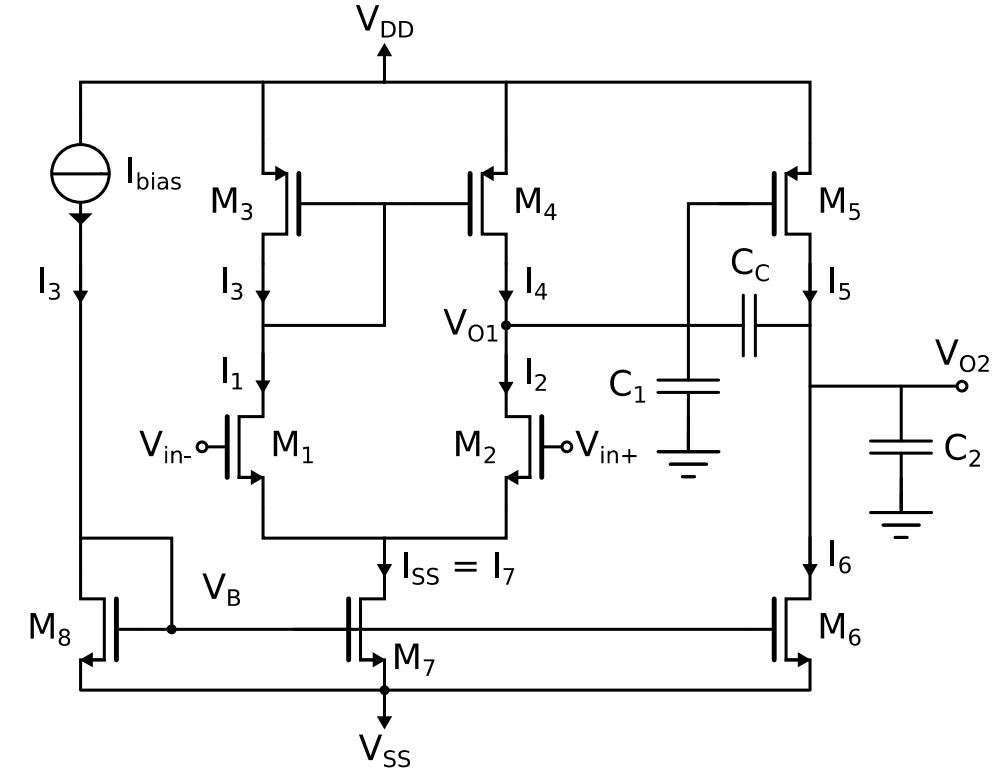
$$A(s) = \frac{V_{out}}{V_{in}} = \frac{g_{m1} \cdot \left(\frac{g_{m5} - sC_c}{C_1 C_2 + C_1 C_c + C_2 C_c} \right)}{s^2 + s \left(\frac{(C_2 + C_c)(g_{DS2} + g_{DS4}) + (C_1 + C_c)(g_{DS5} + g_{DS6}) + g_{m5}C_c}{C_2 C_1 + C_c C_2 + C_c C_1} \right) + \frac{(g_{DS2} + g_{DS4})(g_{DS5} + g_{DS6})}{C_1 C_2 + C_1 C_c + C_2 C_c}}$$



Pole splitting

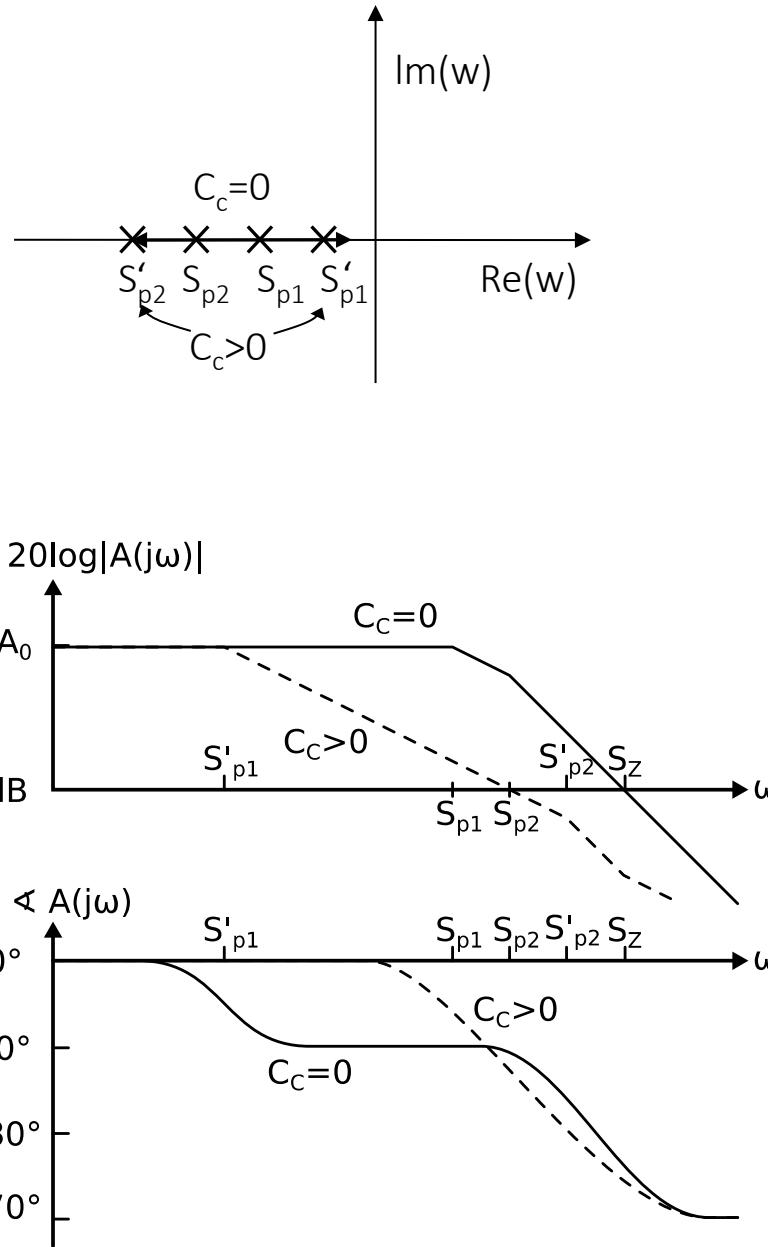

DC-gain $A_0 = A(s=0)$:

$$A_0 = \frac{g_{m1} \cdot g_{m5}}{(g_{DS2} + g_{DS4})(g_{DS5} + g_{DS6})}$$

Miller zero:

$$S_z = \frac{g_{m5}}{C_c}$$

Assume dominant pole approximation, i.e. $|s_{p2}| \gg |s_{p1}|$
 s_{p1} and s_{p2} are solved from the denominator of $A(s)$:

$$\Rightarrow (s + s_{p1})(s + s_{p2}) = s^2 + s(s_{p1} + s_{p2}) + s_{p1} \cdot s_{p2} \approx s^2 + s \cdot s_{p2} + s_{p1} \cdot s_{p2}$$



$$\begin{aligned} \Rightarrow s_{p1} &\approx \frac{-(g_{DS2} + g_{DS4})(g_{DS5} + g_{DS6})}{(C_2 + C_c)(g_{DS2} + g_{DS4}) + (C_1 + C_c)(g_{DS5} + g_{DS6}) + g_{m5} \cdot C_c} \\ &\approx -\frac{(g_{DS2} + g_{DS4})(g_{DS5} + g_{DS6})}{g_{m5} \cdot C_c} \\ &= -\frac{g_{m1}}{A_0 C_c} \end{aligned} \quad ; \text{assume: } g_m \gg g_{DS}$$

$$s_{p2} \approx -\frac{g_{m5} \cdot C_c}{C_1 C_2 + C_1 C_c + C_2 C_c} \approx -\frac{g_{m5}}{C_2} \quad C_2, C_c \gg C_1$$

Poles are separated by $\sim A_0$
i.e. DC gain of the amplifier

$$\text{GBW} = A_0 |s_{p1}| = \frac{g_{m1}}{C_c}$$

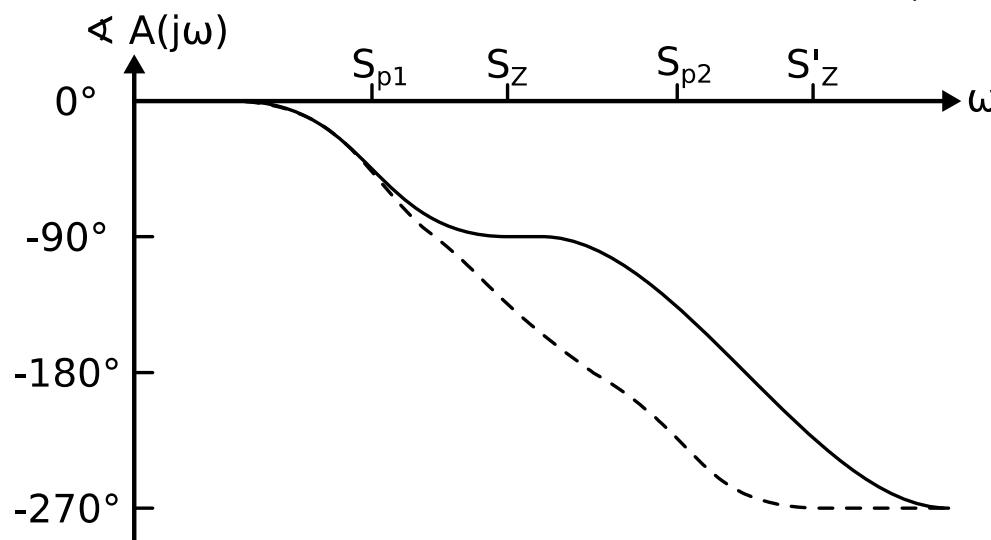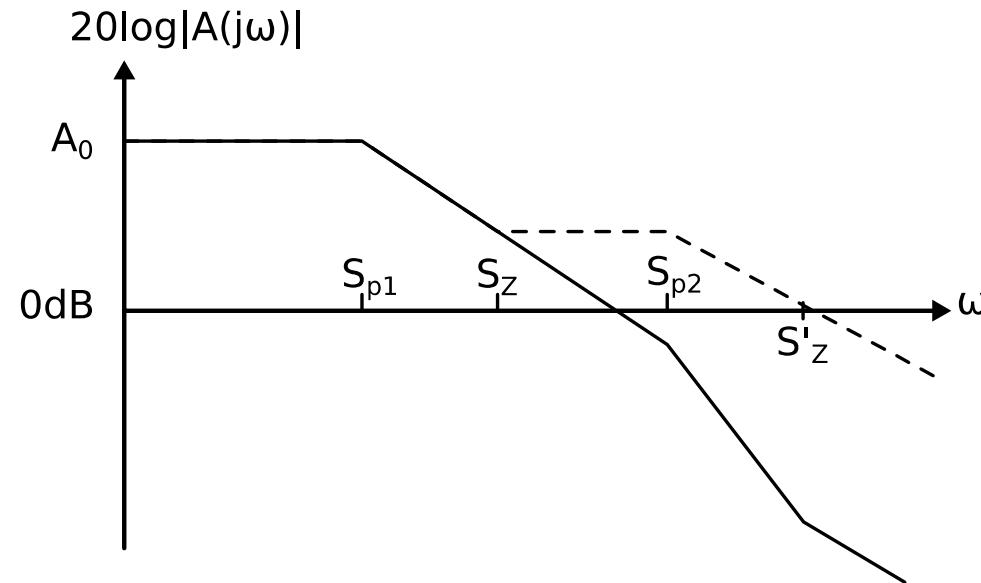Miller zero may cause a stability problem



Miller zero is in the right-hand s-plane causing an additional -90° phase shift.

For stability we have to design:



$$\Rightarrow |S_z| > |S_{p2}|$$

$$\Rightarrow \frac{1}{C_C} > \frac{C_C}{C_A C_2 + (C_A + C_2) C_C} \approx \frac{1}{C_2}$$

\Rightarrow Block the “feedforward” path through C_C !

If $|S_z| < \text{GBW}$, the amplifier is unstable

Blocking feedforward through C_C

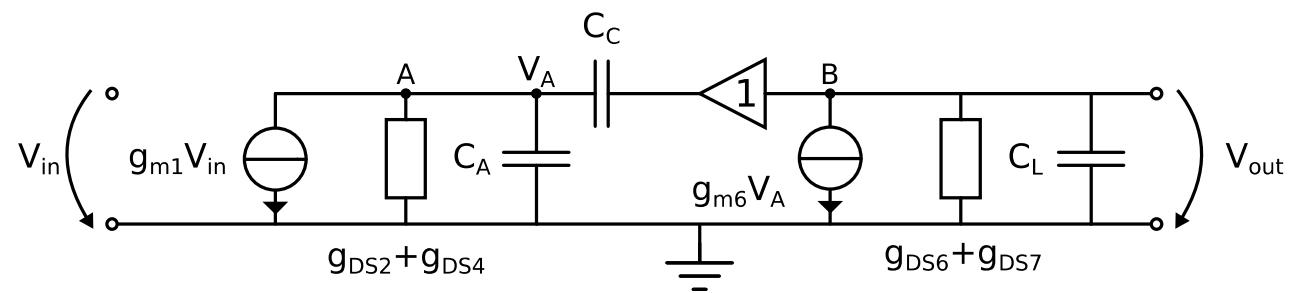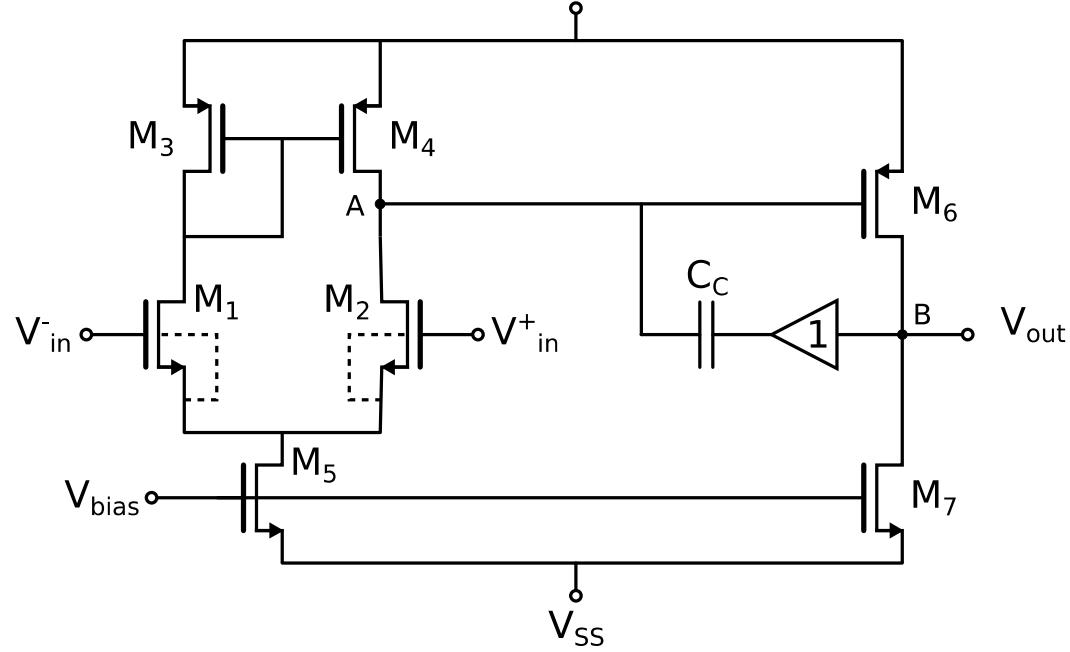

Current equations at nodes A and B:

$$A: \quad g_{m1}V_{in} + (g_{DS2} + g_{DS4} + sC_A)V_A + sC_C(V_A - V_{OUT}) = 0$$

$$B: \quad g_{m6}V_A + (g_{DS6} + g_{DS7} + sC_L)V_{OUT} = 0$$

Eliminate $V_A \Rightarrow$

$$A = \frac{V_{in}}{V_{OUT}} = \frac{-g_{m1} \cdot g_{m6}}{s^2 C_L (C_A + C_C) + s [(C_A + C_C)(g_{DS6} + g_{DS7}) + C_L(g_{DS2} + g_{DS4}) + C_C g_{m6}] + (g_{DS2} + g_{DS4})(g_{DS6} + g_{DS7})}$$

$$A = \frac{A_0}{(s + s_{p1})(s + s_{p2})}$$

$$A_0 = \frac{-g_{m1} \cdot g_{m6}}{(g_{DS2} + g_{DS4})(g_{DS6} + g_{DS7})}$$

Poles: $s_{p1} = -\frac{g_{m1}}{A_0 C_C}$


$$s_{p2} = -\frac{g_{m6} C_C}{C_A C_L + (C_A + C_L) C_C} \approx -\frac{g_{m6}}{C_L}$$

$$GBW = \frac{g_{m1}}{C_C}$$


Source follower:

$$A(s) = \frac{1 + s/s_z}{1 + s/s_p} \quad |s_z| \approx |s_p| = \frac{g_{m8}}{C_{GS8}} \gg s_{p2}, GBW$$


Implementation with the source-follower

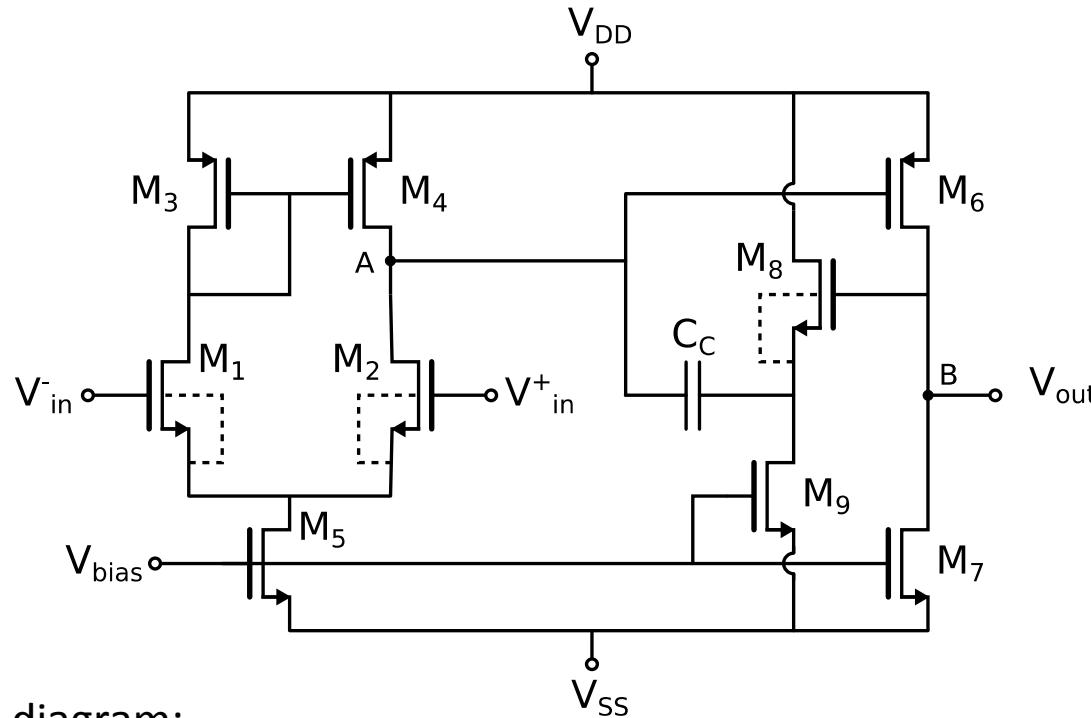

Small-signal circuit diagram:

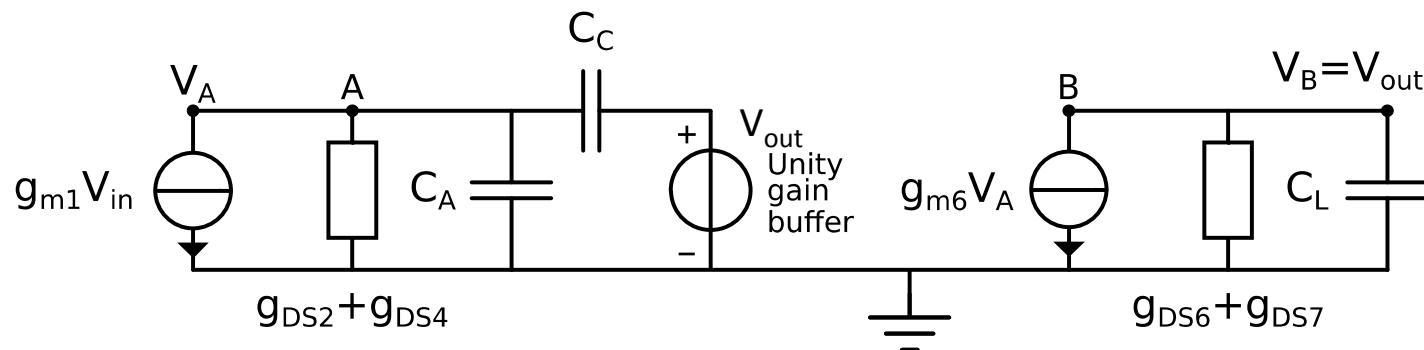


Lead compensation

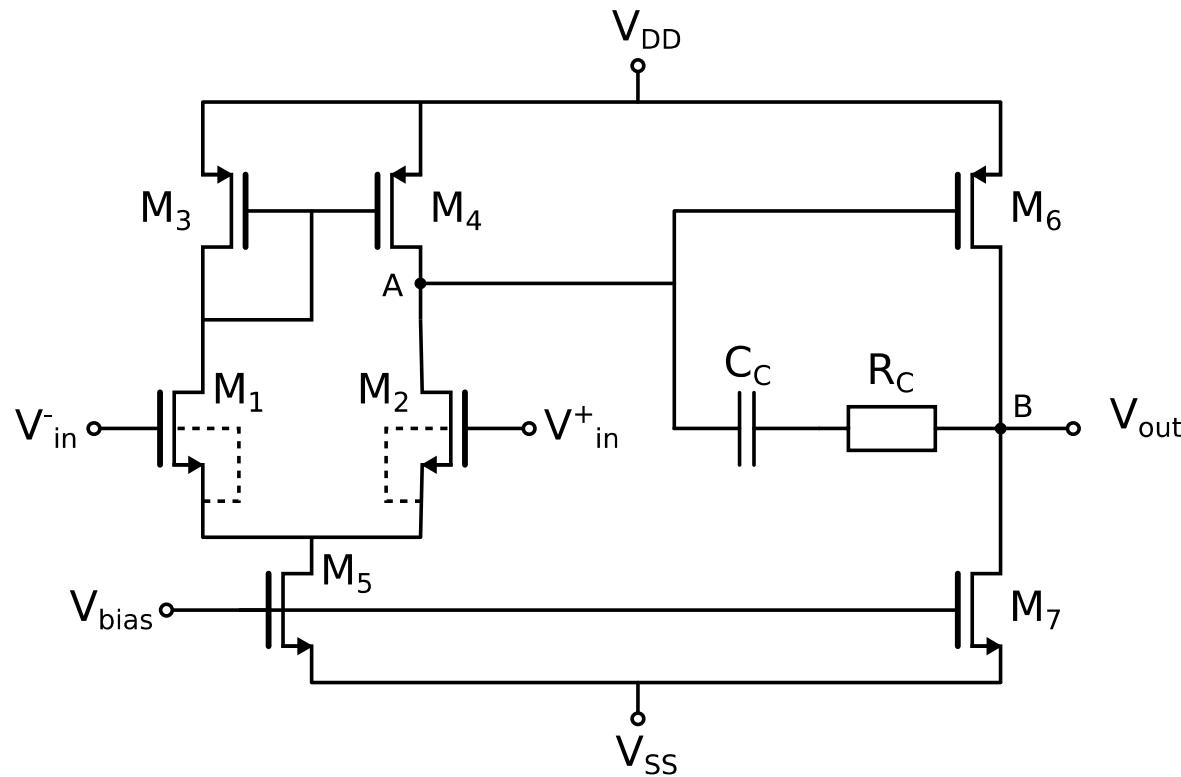

Phase margin is improved by moving Miller-zero to left-hand s-plane with a series compensation resistor R_C i.e. lead compensation.

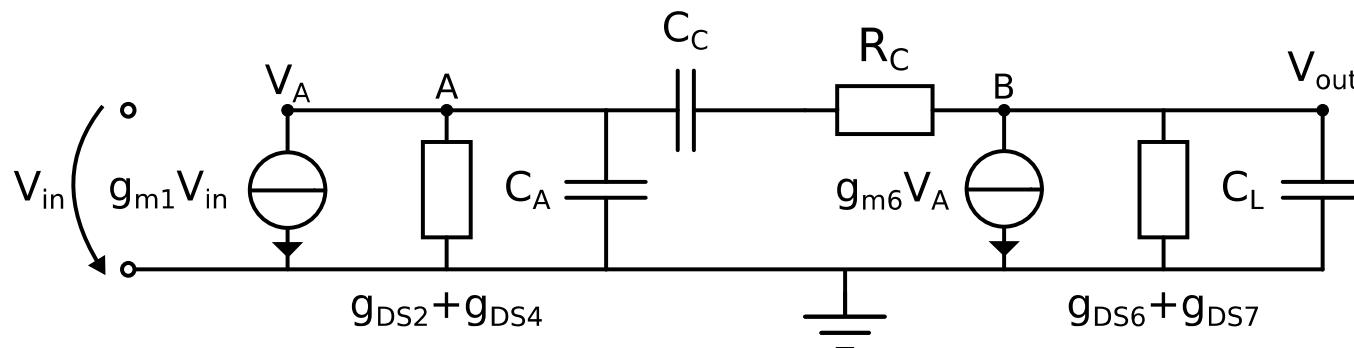Resistor R_C is implemented with a linear region MOS-transistor or a CMOS transmission gate in which transistor gates are connected to V_{DD} and V_{SS}.



In Miller compensated amplifier replace C_C with Y_C

Gain transfer-function:

$$A_v(s) = -\frac{A_0 \left(1 - \frac{s}{s_z}\right)}{\left(1 + \frac{s}{s_{p1}}\right)\left(1 + \frac{s}{s_{p2}}\right)\left(1 + \frac{s}{s_{p3}}\right)}$$


where

$$A_0 = \frac{g_{m1} \cdot g_{m6}}{(g_{DS2} + g_{DS4})(g_{DS6} + g_{DS7})}$$

and poles are

$$s_{p1} = -\frac{g_{m1}}{A_0 C_C}$$
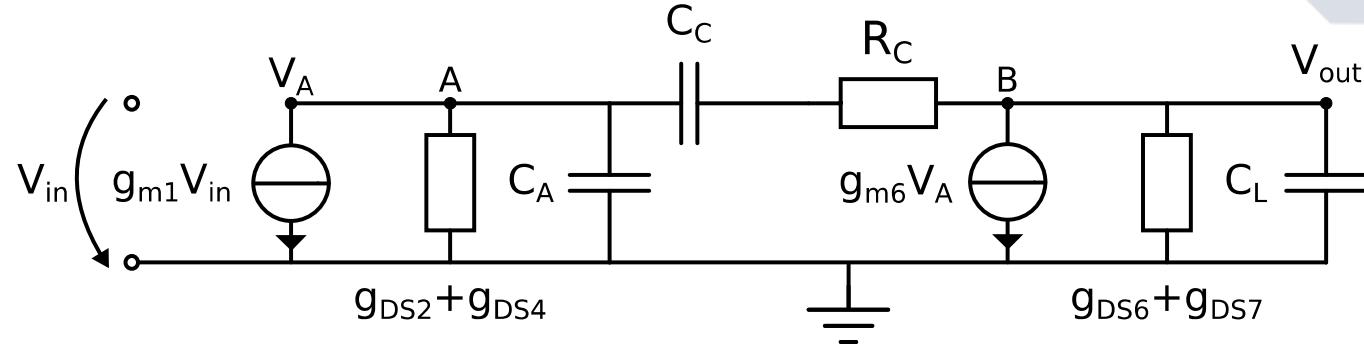
$$s_{p2} = -\frac{g_{m6} C_C}{C_A C_L + (C_A + C_L) C_C}$$



New pole due to compensation:

$$s_{p3} = -\frac{1}{R_C} \left(\frac{1}{C_C} + \frac{1}{C_A} + \frac{1}{C_L} \right)$$

The zero is given by

$$s_z = -\frac{1}{\left(R_C - \frac{1}{g_{m6}}\right) C_C}$$

Compensation resistor R_C is used to eliminate Miller-zero or to move the zero to left-hand s-plane:

Zero elimination:

$$s_z \rightarrow \infty \Rightarrow R_C = \frac{1}{g_{m6}}$$

assume $s_{p3} \gg s_{p1}, s_{p2} \Rightarrow$

$$\text{PM} > 45^\circ \Rightarrow |s_{p2}| > A_0 |s_{p1}| = \text{GBW}$$

Design principle:

$$\Rightarrow \frac{g_{m6}}{C_L} > \frac{g_{m1}}{C_C}$$

Problems with process variations:

impossible to keep Miller-zero at infinity, it may move to right-hand s-plane causing stability problems.





Move zero to left-hand s-plane:

Zero located in the left half plane, if

$$R_C > \frac{1}{g_{m6}}$$

phase shift $+90^\circ$!

Improves phase margin!

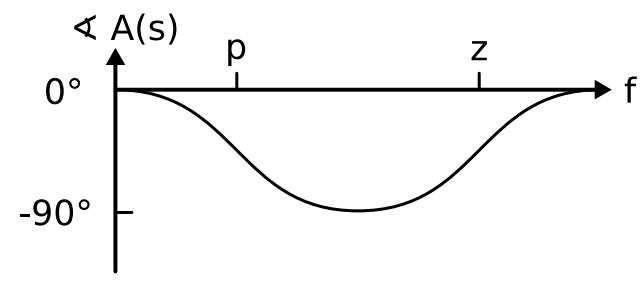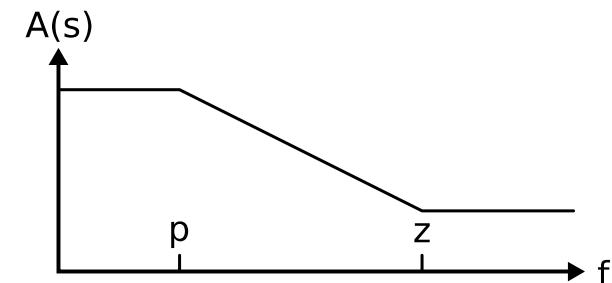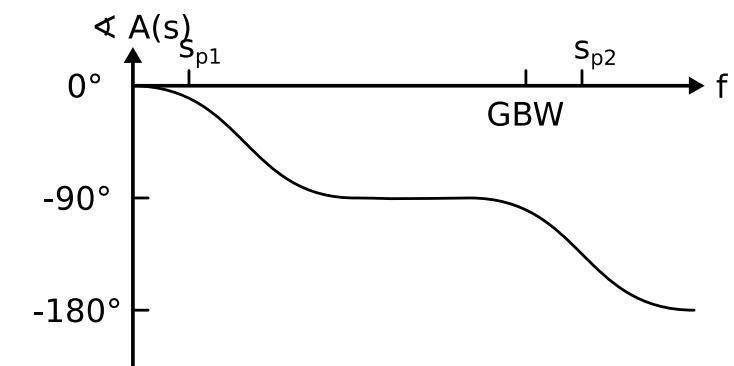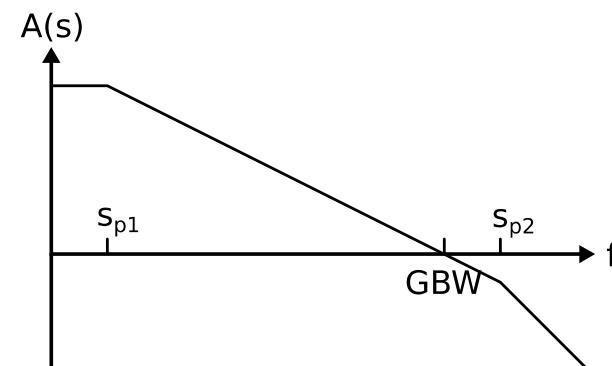


Compensation strategies

- Move the zero to left-hand s-plane either to compensate s_{p2} or s_{p3} .

Lead compensation:

- Phase shift of the zero in the left-hand s-plane is $+90^\circ$
- ⇒ Improves PM
- ⇒ Higher GBW is possible

Compensation strategies

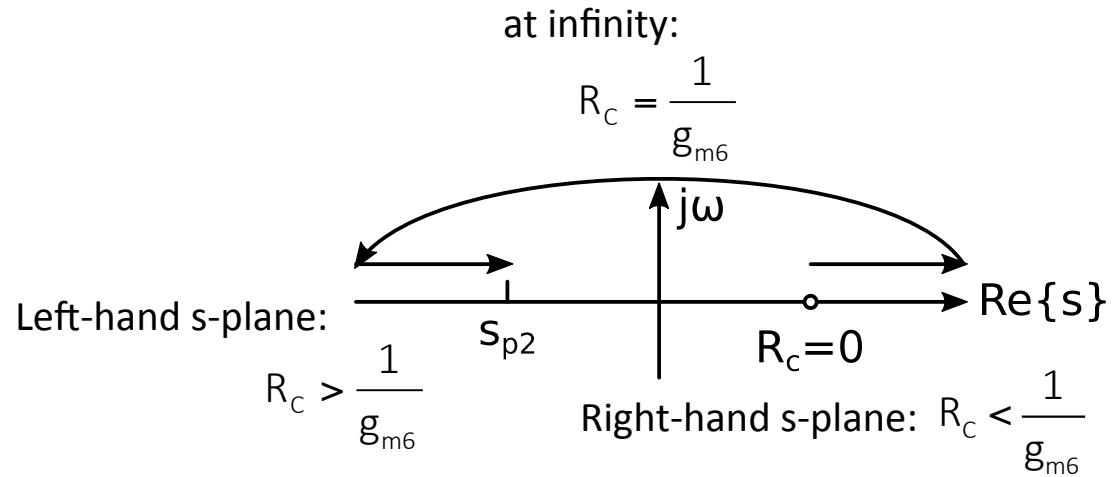


Pole-zero cancellation:

$$\Rightarrow s_z = s_{p2}$$


$$\Rightarrow R_c = \frac{C_C + C_A + C_L}{C_C(g_{m6})}$$

Increased bandwidth!

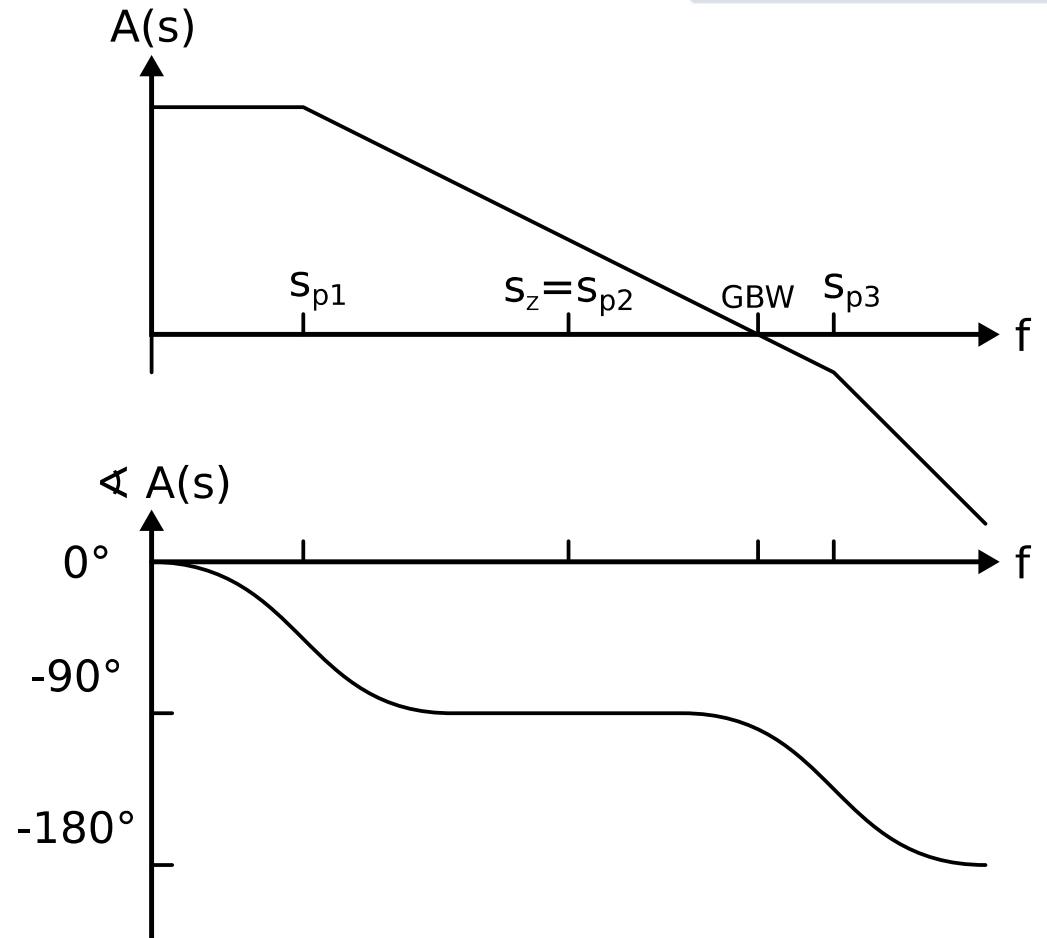

$$\Rightarrow |s_{p3}| > \text{GBW} = A_0 |s_{p1}| \Rightarrow \text{PM} > 45^\circ$$


Problem with pole-zero cancellation

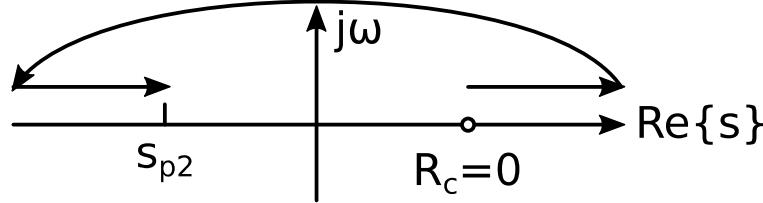



Process variations causes mismatch in pole-zero compensation, which slows down settling of the transients:

$$H(t) = k_1 e^{-\text{GBW} \cdot t} + k_2 e^{-s_{p3} \cdot t}$$
$$k_2 = f(z - p_3)$$

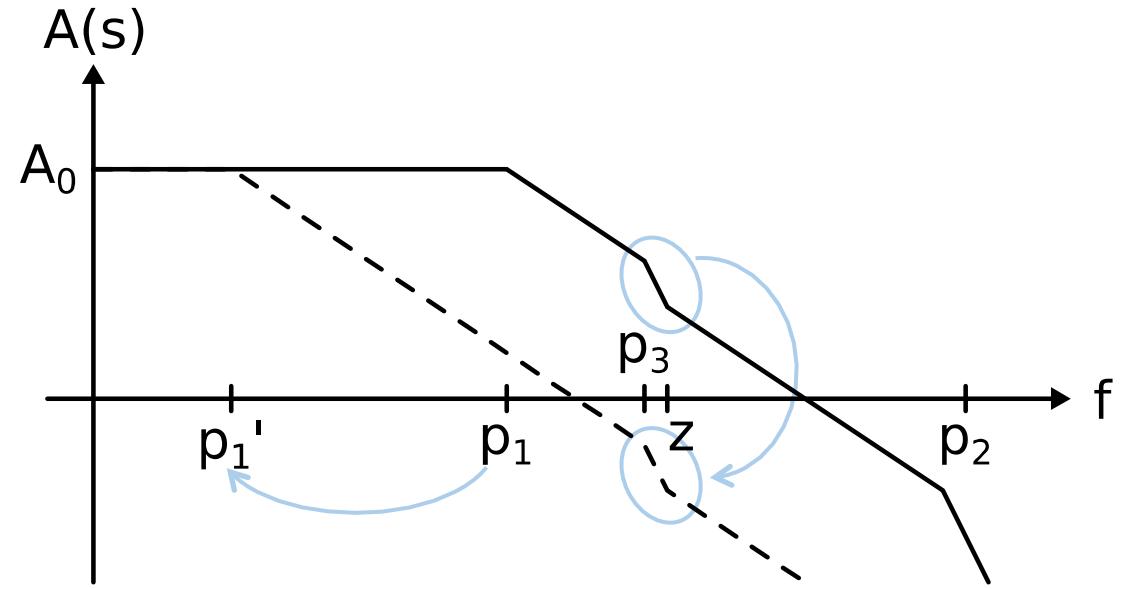In this case compensate so that $\text{GBW} = 2s_{p3}$



Push-Pull output stage

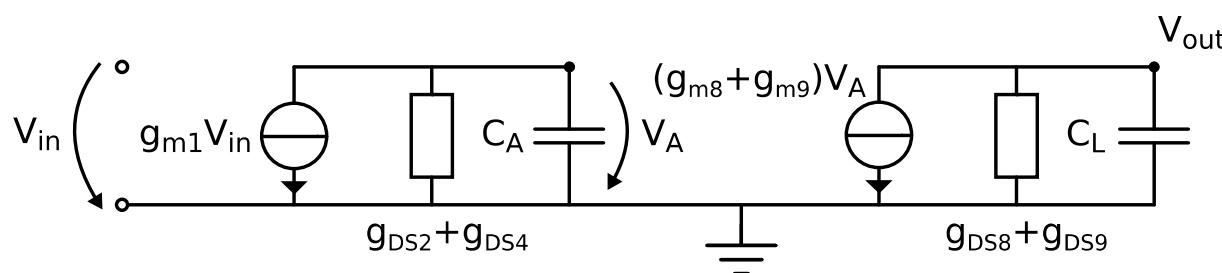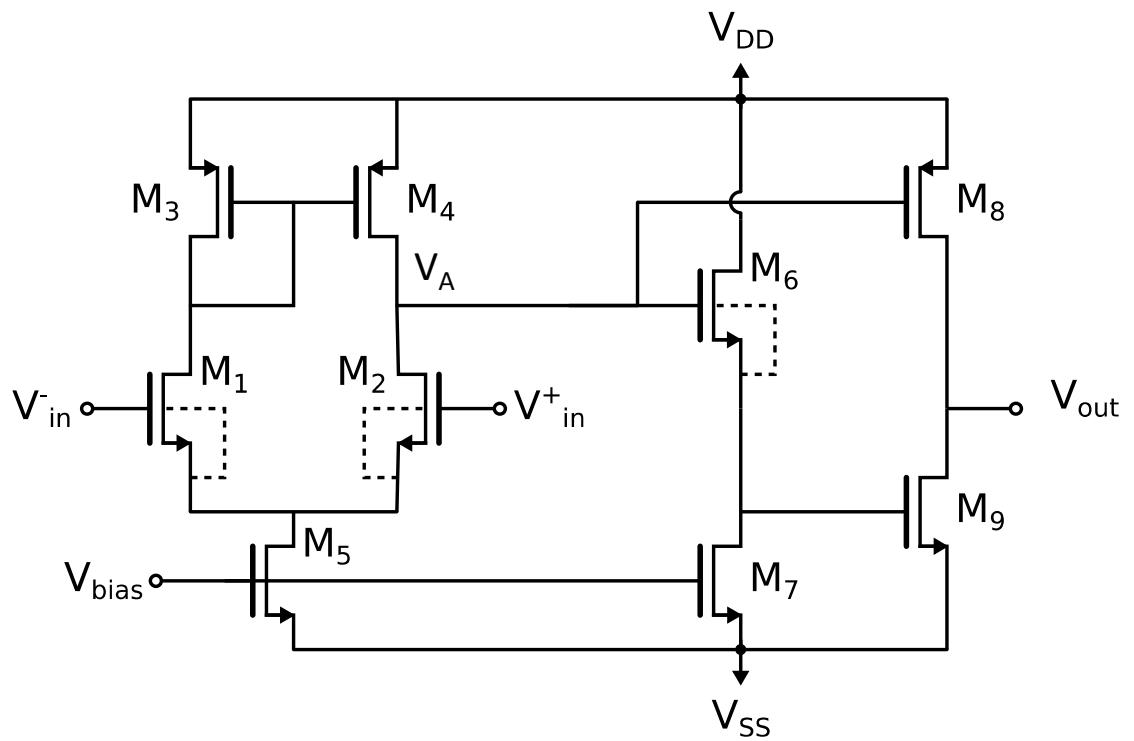

Assume source follower BW>>GBW!
Source follower:

$$A(s) = \frac{A_0 \left(1 + \frac{s}{s_z}\right)}{1 + \frac{s}{s_p}} \quad A \approx 1$$

$$s_z \approx s_p = \frac{g_{m6}}{C_{GS6}}$$

$$A(s) = -\frac{A_0}{\left(1 + \frac{s}{s_{p1}}\right)\left(1 + \frac{s}{s_{p2}}\right)}$$

$$A_0 = \frac{g_{m1}(g_{m8} + g_{m9})}{(g_{DS2} + g_{DS4})(g_{DS8} + g_{DS9})}$$


poles :

$$s_{p1} = -\frac{g_{DS2} + g_{DS4}}{C_A}$$


$$s_{p2} = -\frac{g_{DS8} + g_{DS9}}{C_L}$$

$$\text{assume } |s_{pss}| = \frac{g_{m6}}{C_{GS6}} \gg |s_{p2}|, |s_{p1}|$$

Compensation of push-pull output stage:

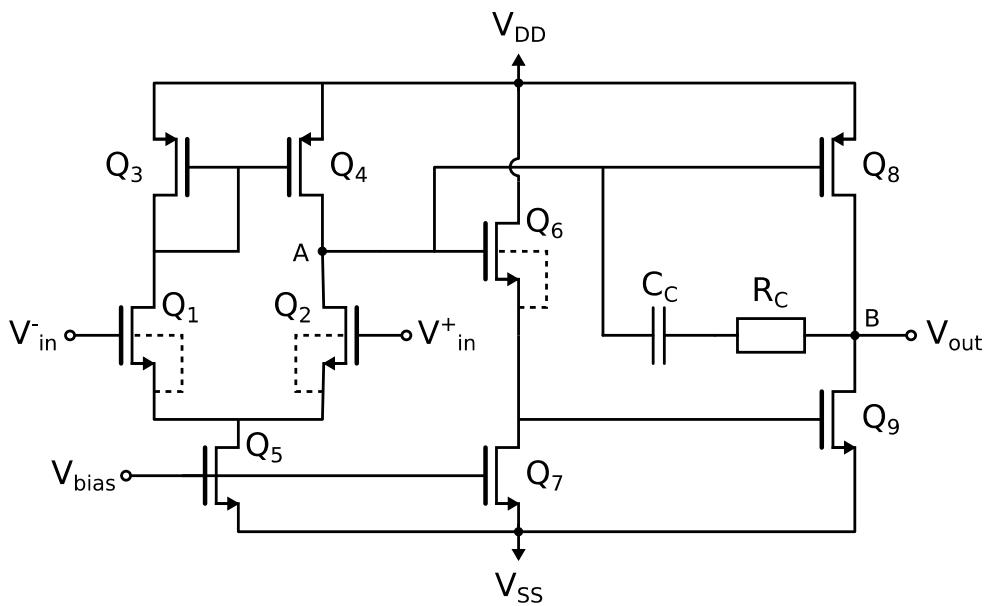

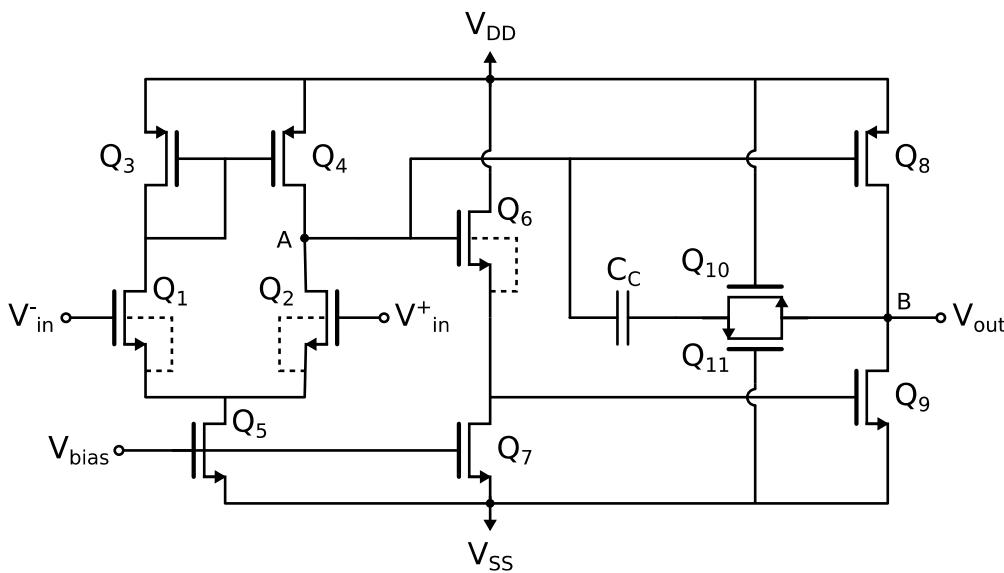Lead compensation of push-pull output stage.



Implement R_C with CMOS transmission gate:

$$R_C \approx \frac{1}{g_{m10} + g_{m11}} = \frac{1}{g_{m8} + g_{m9}}$$

In Miller compensated amplifier replace C_C with Y_C

$$A_v(s) = -\frac{A_0 \left(1 - \frac{s}{s_z}\right)}{\left(1 + \frac{s}{s_{p1}}\right)\left(1 + \frac{s}{s_{p2}}\right)\left(1 + \frac{s}{s_{p3}}\right)}$$

where

$$A_0 = \frac{g_{m1} \cdot (g_{m8} + g_{m9})}{(g_{DS2} + g_{DS4})(g_{DS8} + g_{DS9})}$$

New pole due to compensation:

$$s_{p3} = -\frac{1}{R_C} \left(\frac{1}{C_C} + \frac{1}{C_A} + \frac{1}{C_L} \right)$$

and poles are

$$s_{p1} = -\frac{g_{m1}}{A_0 C_C}$$

$$s_{p2} = -\frac{(g_{m8} + g_{m9}) C_C}{C_A C_L + (C_A + C_L) C_C}$$

The zero is given by

$$s_z = -\frac{1}{\left(R_C - \frac{1}{g_{m8} + g_{m9}}\right) C_C}$$

Zero located in the left half plane, if

$$R_c > \frac{1}{g_{m8} + g_{m9}}$$

→ phase shift $+90^\circ$!





Zero elimination:

$$s_z \rightarrow \infty \Rightarrow R_c = \frac{1}{g_{m8} + g_{m9}}$$

assume: $s_{p3} \gg s_{p1}, s_{p2} \Rightarrow$


$$\text{PM} > 45^\circ \Rightarrow |s_{p2}| > A_0 |s_{p1}| = \text{GBW}$$
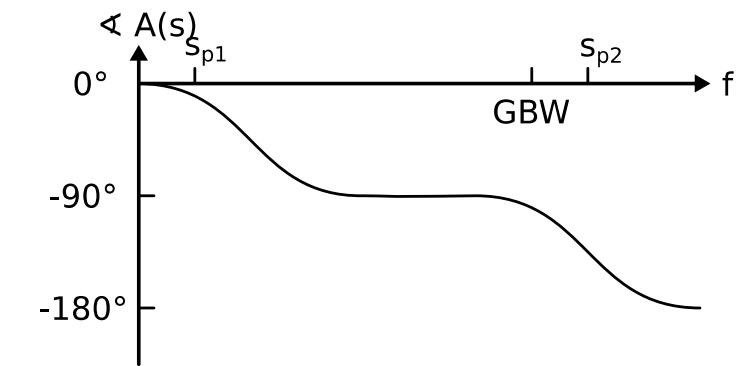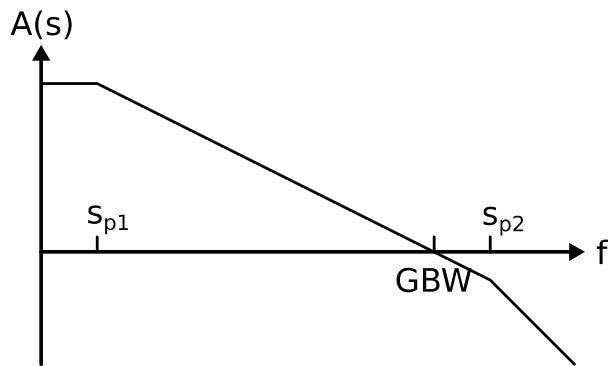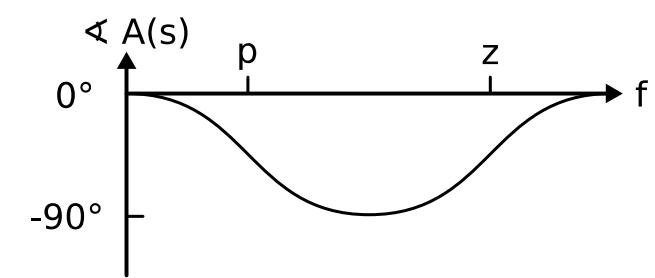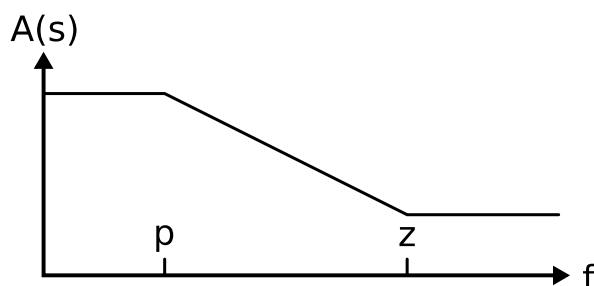
$$\Rightarrow \frac{g_{m8} + g_{m9}}{C_L} > \frac{g_{m1}}{C_C}$$



at infinity:

$$R_c = \frac{1}{g_{m8} + g_{m9}}$$

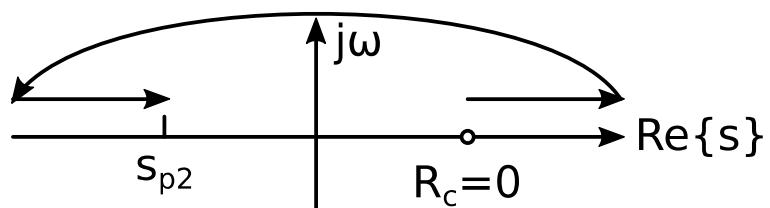

Left-hand s-plane:



$$R_c > \frac{1}{g_{m8} + g_{m9}}$$

right-hand s-plane: $R_c < \frac{1}{g_{m8} + g_{m9}}$

Pole-zero cancellation:

$$\Rightarrow s_z = s_{p2}$$
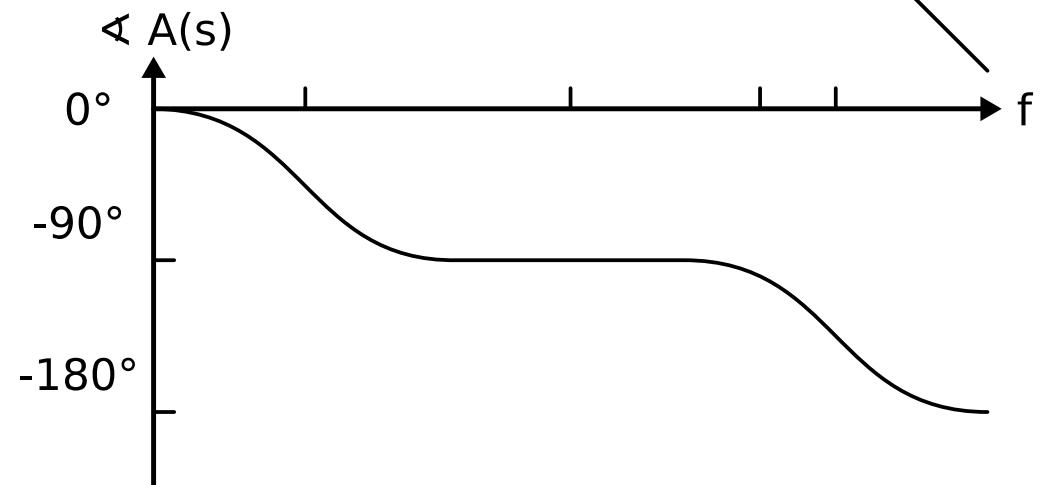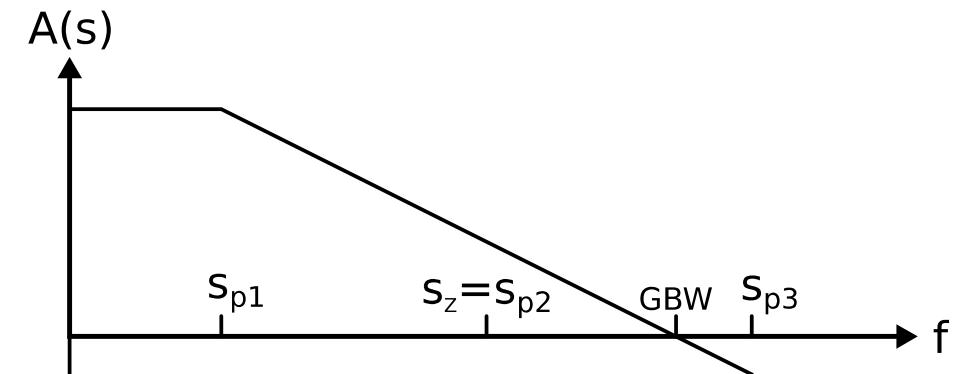
$$\Rightarrow R_c = \frac{C_C + C_A + C_L}{C_C(g_{m8} + g_{m9})}$$



$$\Rightarrow |s_{p3}| > \text{GBW} = A_0 |s_{p1}| \Rightarrow \text{PM} > 45^\circ$$