Microwave engineering I (MiWE I)

Interactive lecture 1 of Topic 1
Transmission line theory
January 13, 2022

The main learning outcome of the course is to create readiness to work in microwave engineering related tasks and projects and enable further studies and continuous learning in microwave engineering.



Topic 1: Learning outcomes and content

- The student can
 - **explain** the wave propagation of a radio-frequency signal in transmission lines (such as signal propagation, attenuation, reflection),
 - calculate and simulate (AWR) related circuit parameters (such as voltage, current, power, characteristic impedance, loss, reflection coefficient) related to transmission lines,
 - design transmission lines (such as microstrip lines) with calculations and AWR simulations.
- Transmission line model, wave equations and its solution (Pozar Chapter 2.1) MAIN Wave propagation along a transmission line and characteristic impedance (2.1, 2.7) TOPIC 5
- Connection of the transmission line theory and EM field theory (2.2)
- Microstrip line (3.8)
- Voltage reflection from an impedance discontinuity and standing wave along a transmission line (2.3)

These lecture slides and notes are not designed for self-study. Please, use the course book chapters 2 and 3 for self-study.

The "world" becomes wireless, why do we still study transmission line theory?


Coaxial cable, e.g., in

- WiFi router
- TV antenna cable
- measurement devices,
- etc.



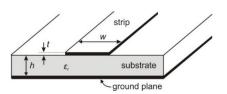Microwave amplifier integrated on printed circuit board (consists of transistor and microstrip lines)







Mobile phone disassembled – lots of transmission lines are needed for signal transfer




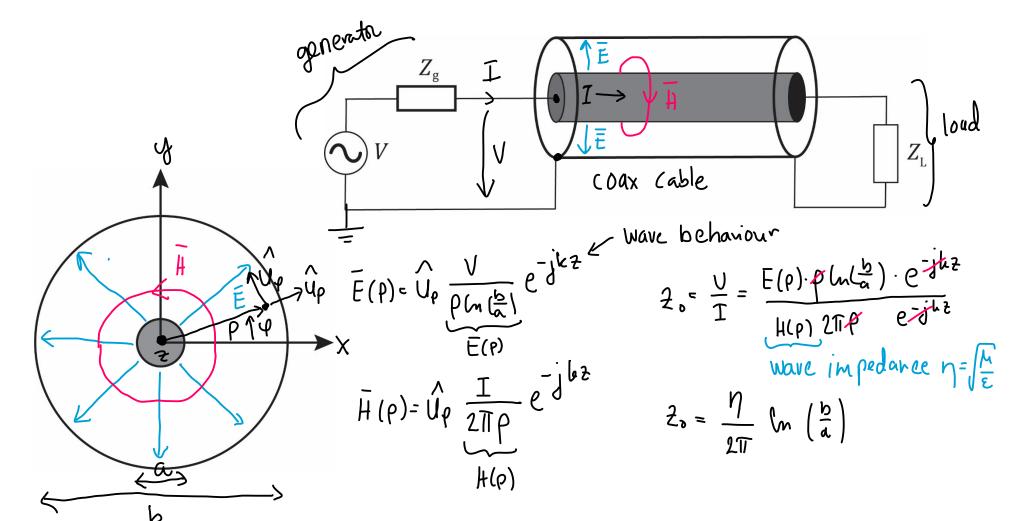Transmission line carries a wave with E and H fields



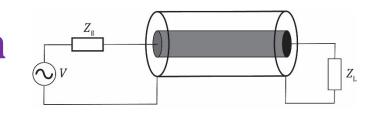
The wave behaviour is visible in the time-domain presentation



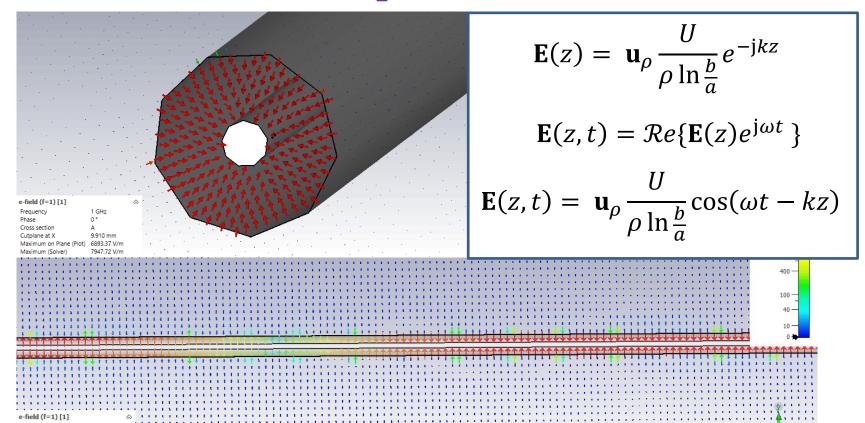


W= 2114

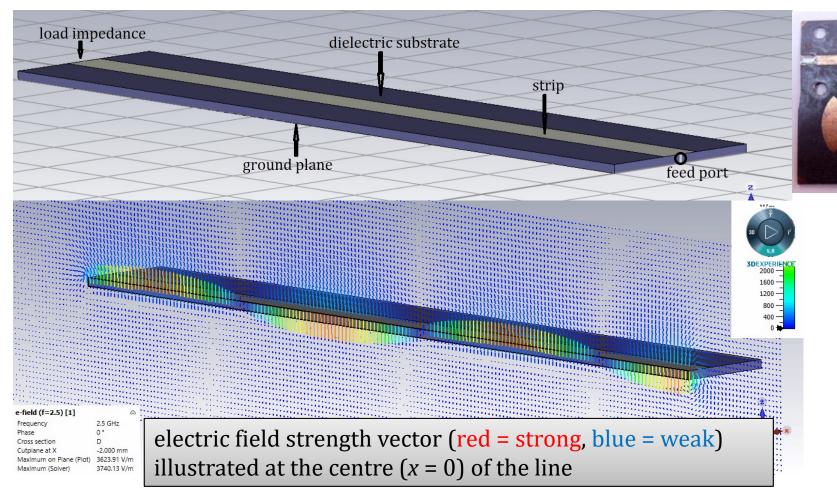Microstrip line is one important transmission line in microwave engineering



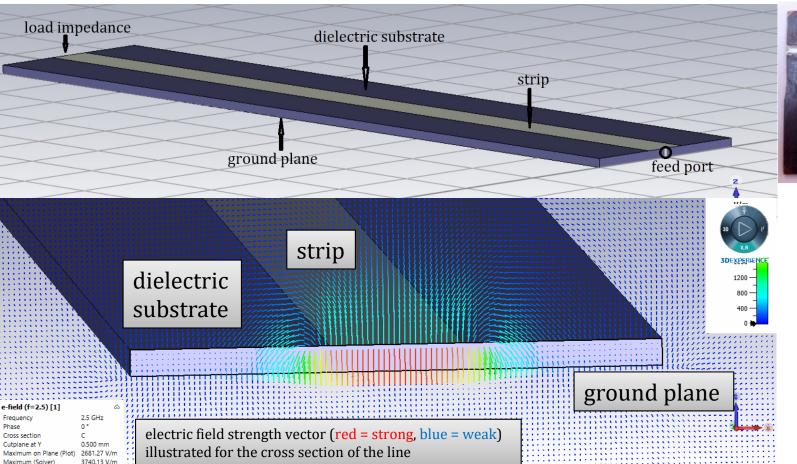Microstrip line is one important transmission line in microwave engineering






Exercise problem 3 of Topic 1.


The plug-in-type design formulas in Pozar chapter 3.8.

Transmission line theory and wave equations

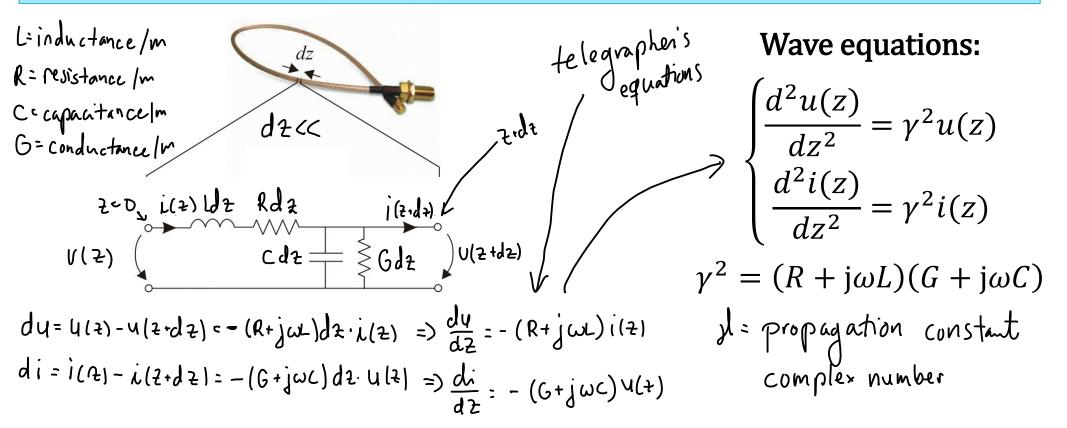Components and lines whose physical length is a fraction (?) of the wavelength or longer must be analysed using the transmission line theory



One solution of the wave equations

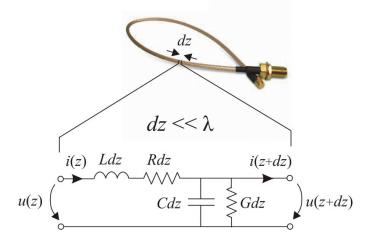

$$\begin{cases} \frac{d^2u(z)}{dz^2} = \gamma^2 u(z) \\ \frac{d^2i(z)}{dz^2} = \gamma^2 i(z) \end{cases}$$

$$\begin{cases} \frac{d^2u(z)}{dz^2} = \gamma^2 i(z) \\ \frac{d^2i(z)}{dz^2} = \gamma^2 i(z) \end{cases}$$

$$\begin{cases} \frac{d^2u(z)}{dz^2} = \gamma^2 u(z) \\ \frac{d^2i(z)}{dz^2} = \gamma^2 i(z) \end{cases}$$

$$u(z,t) = \Re\{u(z) \cdot e^{j\omega t}\}$$

Lossless case:
$$R = 0$$
, $G = 0$


Lossless case:
$$R = 0$$
, $G = 0$ $\int_{a}^{2} j\omega L j\omega L = \int_{a}^{2} \omega^{2} LC \Rightarrow \int_{a}^{2} j\omega \sqrt{LC} = \int_{\beta}^{2} \omega^{2} LC \Rightarrow \int_{\beta}^{2} j\omega \sqrt{LC} \Rightarrow \int_{\beta}^{2} j\omega \sqrt{L$

One solution:
$$U(2)=U^{\dagger}e^{-\frac{1}{2}\beta^{2}}$$
 $\lambda(2)=\lambda^{\dagger}e^{-\frac{1}{2}\beta^{2}}$

11+ real number

U(7,t)=Re {u(+)·e jut } : U+cos(wt-(52) Time-domain presentation:

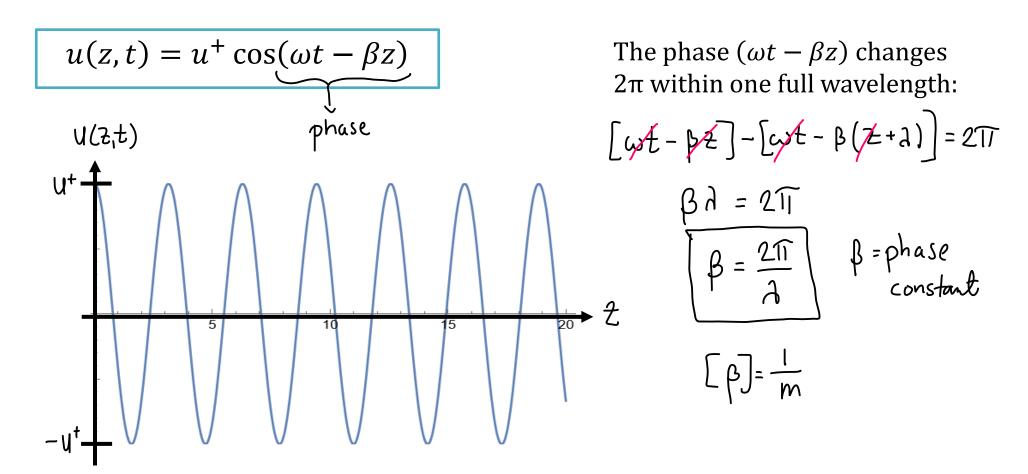
This wave propagates to positive z-direction




Wave travelling in the +z direction in a lossless line

$$u(t,z) = u^+ \cos(\omega t - \beta z)$$

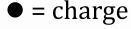= **E** field vector, represents "voltage"
$$u(z,t)$$



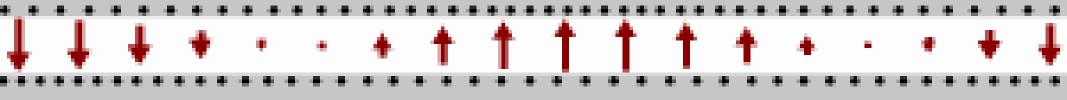

When to apply the transmission line theory?

$$z = 0 \qquad z = l \qquad u(t,z) = u^{+} \cos(\omega t - \beta z)$$

$$U(2=0) = u^{+} \qquad U(2=1) \qquad U(1+0) = U^{+} \cos(\omega t - \beta z)$$

$$U(2=0) = u^{+} \qquad U(2=1) \qquad U(2=1) \qquad U(2=1) \qquad v^{+} \qquad v^{-} \qquad v^$$

Q1: What is the <u>maximum length *l*</u> of the line when the phase difference of the voltage in the line is no

the phase difference of the voltage in the line is no more than 10 degrees? Select one alternative:
$$z=0 \iff z=l$$
 137. 1. $l=\frac{1}{5}\lambda=0.20\lambda$

$$u(t = 0, z = 0)$$
 $u(t = 0, z = l)$
= $u^{+} \cos(0)$ = $u^{+} \cos(-\beta l)$

Phase diff. BL =
$$\frac{2\pi}{3}$$
·L = 360° $\frac{L}{3}$ = 10°
 $L = \frac{10^{\circ}}{360^{\circ}}$ $A = \frac{1}{36}$ A

$$12^{1}$$
 1 1 $-\frac{1}{1}$ 1 $-\frac{1}{1}$ 2 $-\frac{1}{1}$

10% 2.
$$l = \frac{1}{10}\lambda = 0.10\lambda$$

6% 3.
$$l = \frac{1}{12}\lambda = 0.083\lambda$$
 $58\% l = \frac{1}{36}\lambda = 0.028\lambda\%$

6 % 5.
$$l = \frac{1}{72}\lambda = 0.014\lambda$$

0 /. 6.
$$l = \frac{1}{99}\lambda = 0.010\lambda$$

Q2: What is the physical interpretation of this solution?

$$\begin{cases} \frac{d^2u(z)}{dz^2} = \gamma^2 u(z) \\ \frac{d^2i(z)}{dz^2} = \gamma^2 i(z) \end{cases}$$

Note! Plus sign!
$$u(z) = ue^{+\gamma z} = ue^{+\alpha z} e^{+j\beta z}$$

Select the best alternative.


This solution is a wave travelling...

in the +z direction with an exponential damping factor

in the +z direction with an exponential growth factor

in the +*z* direction with constant magnitude

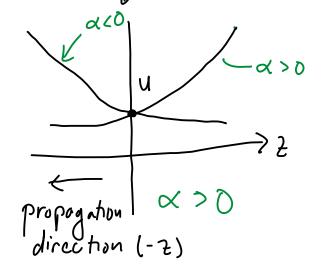in the -z direction with an exponential damping factor in the -z direction with an exponential growth factor in the -z direction with constant magnitude




A wave travelling in the +z direction with an exponential damping factor

$$\gamma = \pm \sqrt{(R + j\omega L)(G + j\omega C)}$$
= complex propagation constant
$$= \alpha + j\beta \quad \text{(unit 1/m)}$$

$$u(z) = u^- e^{+\gamma z}$$

$$u(z,t) = \Re\{u(z)e^{j\omega t}\}$$

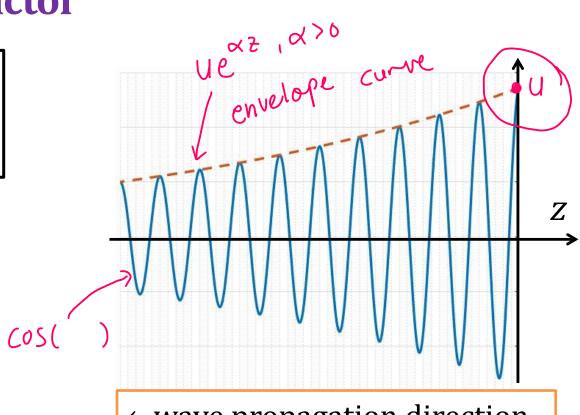the sign of d selected So that the solution is physical



 \leftarrow wave propagation direction

lossless line
$$u^{+} = 1 \text{ V}; \beta = 2 \frac{1}{\text{m}}; \alpha = 0$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$

$$\cdot \cos(\omega t - \beta z)$$

$$u(z,t) = u^{+}e^{\alpha z}$$


$$u(z,t) = u^{+}e^{\alpha z}$$

$$v(z,t) = u^{+}e^{\alpha z}$$

$$v(z,t$$

-1.0

Full solution of the wave equations

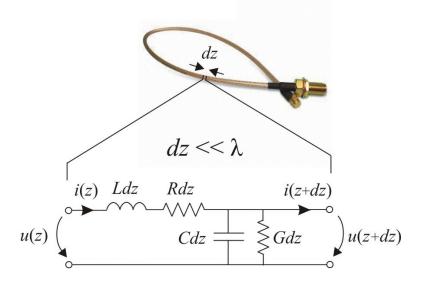


$$\begin{cases} U(z) = U^{\dagger} e^{-J^{2}} + U^{-} e^{+J^{2}} \\ i(z) = i^{\dagger} e^{-J^{2}} + i^{-} e^{+J^{2}} \end{cases}$$

$$\gamma = \pm \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \alpha + j\beta$$

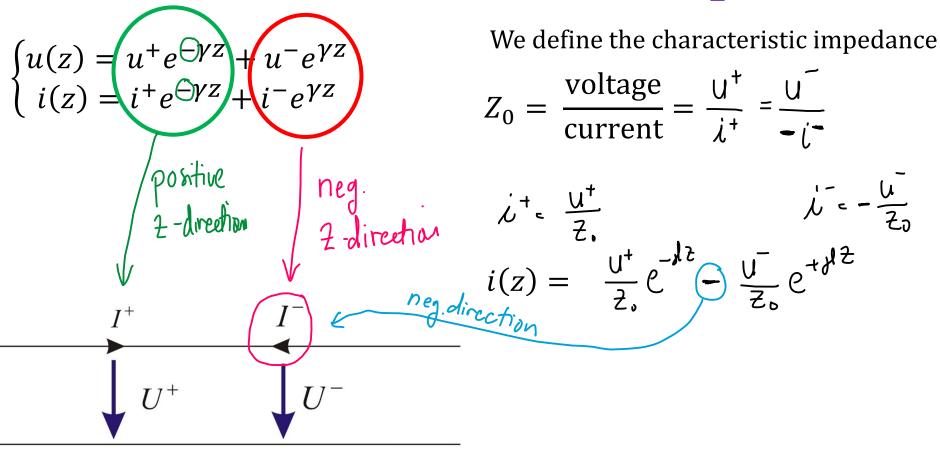Full solution and characteristic impedance



Characteristic impedance relates the voltage and current on the line

$$\frac{du}{dz} = -(R + j\omega L) \cdot i(z)$$
(from slide 8)

$$\frac{du}{dz} = -(R + j\omega L) \cdot i(z)$$
(from slide 8)
$$\begin{cases} u(z) = u^+ e^{-\gamma z} + u^- e^{\gamma z} \\ i(z) = i^+ e^{-\gamma z} + i^- e^{\gamma z} \end{cases} \qquad \gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\frac{dv}{dz} = -v^{+} \int e^{-dz} + v^{-} \int e^{dz} = -(R + j\omega L) \cdot i(z) \quad | \cdot - (R + j\omega L)$$

$$i(z) = \frac{1}{(R + j\omega L)} \left(v^{+} e^{-dz} - v^{-} e^{dz} \right) = i \cdot e^{-dz} + i \cdot e^{dz}$$

$$\frac{1}{(R + j\omega L)} \left(v^{+} = i \cdot e^{-dz} - v^{-} e^{dz} \right) = \frac{1}{i \cdot e^{-dz}} \cdot e^{-dz} + i \cdot e^{dz}$$

$$\frac{1}{(R + j\omega L)} \left(v^{+} = i \cdot e^{-dz} - v^{-} e^{-dz} \right) = \frac{1}{i \cdot e^{-dz}} \cdot e^{-dz} + i \cdot e^{-dz}$$

$$\frac{1}{(R + j\omega L)} \left(v^{+} = i \cdot e^{-dz} - v^{-} e^{-dz} \right) = \frac{1}{i \cdot e^{-dz}} \cdot e^{-dz} + i \cdot e^{-dz}$$

$$\frac{1}{(R + j\omega L)} \left(v^{+} = i \cdot e^{-dz} - v^{-} e^{-dz} \right) = \frac{1}{i \cdot e^{-dz}} \cdot e^{-dz} + i \cdot e^{-dz}$$

$$\frac{1}{(R + j\omega L)} \left(v^{+} = i \cdot e^{-dz} - v^{-} e^{-dz} \right) = \frac{1}{i \cdot e^{-dz}} \cdot e^{-dz} + i \cdot e^{-dz}$$

$$\frac{1}{(R + j\omega L)} \left(v^{+} = i \cdot e^{-dz} - v^{-} e^{-dz} \right) = \frac{1}{i \cdot e^{-dz}} \cdot e^{-dz} + i \cdot e^{-dz}$$

$$\frac{1}{(R + j\omega L)} \left(v^{+} = i \cdot e^{-dz} - v^{-} e^{-dz} - v^{-} e^{-dz} \right) = \frac{1}{i \cdot e^{-dz}} \cdot e^{-dz} + i \cdot e^{-dz}$$

$$\frac{1}{(R + j\omega L)} \left(v^{+} = i \cdot e^{-dz} - v^{-} e^{-dz} - v^{-} e^{-dz} + i \cdot e^{-dz} \right) = \frac{1}{i \cdot e^{-dz}} \cdot e^{-dz} + i \cdot e^{-dz}$$

In-class task: average power of a lossy transmission line

Let us assume that the transmission line has some resistive losses – i.e., in the equivalent circuit model R and/or $G \neq 0$.

A wave travels in the positive +z direction only. Let the average power at z = 0 be P_0 and it depends upon the voltage u^+ and the characteristic impedance Z_0 .

Starting from the definition of the average power, derive a formula for the average power P(z) of a lossy transmission line in a location z (>0).

The teacher is available here to help you! Do not hesitate to ask!

Return your effort in the return box in MyCourses under Topic 1 latest at 12 noon today. It is completely okay if it is not correct or ready at the end, the most important thing is that you try to do it!

$$P(z) = \frac{1}{2} \Re\{u(z) \cdot i^*(z)\}$$

* is the complex conjugate $\Re e$ denotes the real part

$$u(z) = u^{+}e^{-\gamma z}$$

$$i(z) = i^{+}e^{-\gamma z}$$

$$Z_{0} = \frac{u^{-}}{z}$$

Lecture task: average power of a lossy transmission line - solution

$$P(z) = \frac{1}{2} \mathcal{R}e\{u(z) \cdot i^*(z)\} = \frac{1}{2} \mathcal{R}\{u^+ e^{-\gamma z} \cdot (i^+ e^{-\gamma z})^*\}$$

$$P(z) = \frac{1}{2} \mathcal{R}e\left\{u^+ e^{-\gamma z} \cdot \left(\frac{u^+}{Z_0}\right)^* (e^{-\gamma z})^*\right\} \qquad \gamma = \alpha + j\beta$$

$$P(z) = \frac{1}{2} \mathcal{R}e\left\{u^+ e^{-\gamma z} \cdot \left(\frac{u^+}{Z_0}\right)^* (e^{-\gamma z})^*\right\} \qquad \gamma = \alpha + j\beta$$

$$P(z) = \frac{1}{2} \mathcal{R}e \left\{ \underbrace{u^{+}(u^{+})^{*}}_{|u^{+}|^{2}} \frac{1}{Z_{0}^{*}} \underbrace{e^{-\alpha z} e^{-\alpha z}}_{\text{purely real}} \underbrace{e^{-j\beta z} e^{+j\beta z}}_{1} \right\}$$

$$P(z) = \underbrace{\frac{1}{2} |u^+|^2 \mathcal{R}e\left\{\frac{1}{{Z_0}^*}\right\}}_{P(z=0)=P_0} \cdot e^{-2\alpha z}$$
 The average power decays twice as fast as the voltage and the current. This makes sense as the power is the product of the voltage and the current.

If we set the condition of the lossless line; $\alpha = 0$ and Z_0 is real, we get a familiar formula:

$$P(z) = \frac{|u^+|^2}{2Z_0}$$

What's up on Monday

- Find the exercise problems (1-4) of Topic 1 in MyCourses
- The exercise session takes place on Monday morning
- We reserve everyone a 15-minute one-to-one session with one of the course teachers. See further instructions in MyCourses.
- We assume you to return 1-2 of the problems during the pre-booked meeting.

