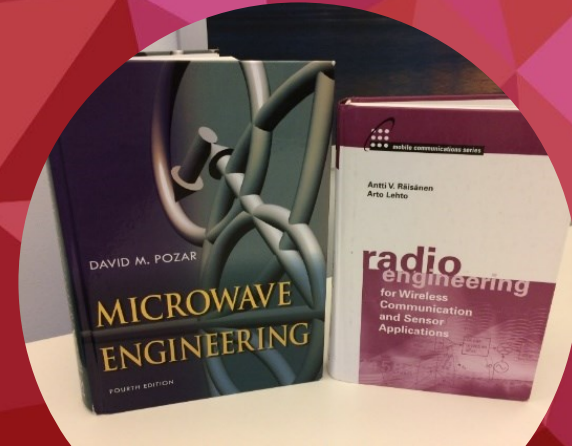


# Microwave engineering I (MiWE I)

Interactive lecture 2 of Topic 1  
Transmission line theory  
January 20, 2022

*The main learning outcome of the course is to create readiness to work in microwave engineering related tasks and projects and enable further studies and continuous learning in microwave engineering.*



# Topic 1: Learning outcomes and content

- The student can
  - **explain** the wave propagation of a radio-frequency signal in transmission lines (such as signal propagation, attenuation, reflection),
  - **calculate** and **simulate** (AWR) related circuit parameters (such as voltage, current, power, characteristic impedance, loss, reflection coefficient) related to transmission lines,
  - **design** transmission lines (such as microstrip lines) with calculations and AWR simulations.
- Transmission line model, wave equations and its solution (Pozar Chapter 2.1)
- Wave propagation along a transmission line and characteristic impedance (2.1, 2.7)
- Connection of the transmission line theory and EM field theory (2.2)
- Microstrip line (3.8)
- Voltage reflection from an impedance discontinuity and standing wave along a transmission line (2.3) TODAY

} WEEK  
AGO

These lecture slides and notes are not designed for self-study.  
Please, use the course book chapters 2 and 3 for self-study.

# Recap of the last week session on one slide

Wave equations:

$$\frac{d^2 u(z)}{dz^2} = \gamma^2 u(z); \quad \frac{d^2 i(z)}{dz^2} = \gamma^2 i(z)$$


$$\gamma = \pm \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$= \alpha + j\beta$$

$$\begin{cases} u(z) = u^+ e^{-\gamma z} + u^- e^{\gamma z} \\ i(z) = i^+ e^{-\gamma z} + i^- e^{\gamma z} \end{cases}$$

forward  
wave

reverse  
wave

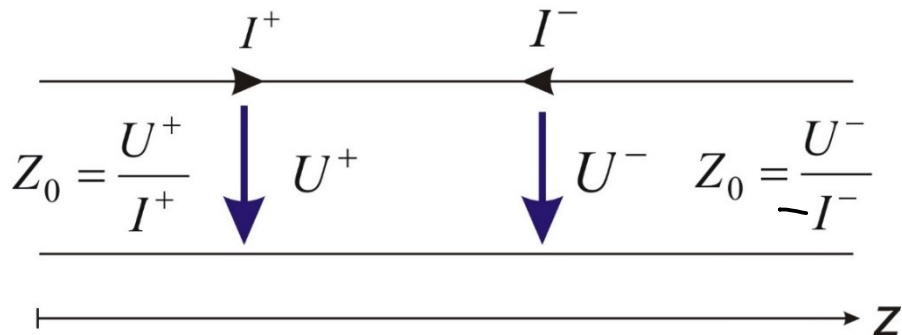

Characteristic impedance (Ω):

$$Z_0 = \frac{\text{voltage}}{\text{current}} = \frac{u^+}{i^+} = \frac{u^-}{i^-}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad \left. \begin{array}{l} R=0 \\ G=0 \end{array} \right\} Z_0 = \sqrt{\frac{L}{C}} \quad \frac{dB}{m}$$

$$i(z) = \frac{u^+}{Z_0} e^{-\gamma z} - \frac{u^-}{Z_0} e^{\gamma z}$$

neg. z  
direction

In-class task final answer:

$$P(z) = \frac{1}{2} |u^+|^2 \underbrace{\text{Re} \left\{ \frac{1}{Z_0^*} \right\}}_{P(z=0)=P_0} \cdot e^{-2\alpha z}$$

**Previous in-class task: the power decays as  $e^{-2\alpha z}$  along the line**

$$P(z) = \frac{1}{2} \operatorname{Re}\{u(z) \cdot i^*(z)\} = \frac{1}{2} \mathcal{R}\{u^+ e^{-\gamma z} \cdot (i^+ e^{-\gamma z})^*\}$$

$$P(z) = \frac{1}{2} \operatorname{Re}\left\{u^+ e^{-\gamma z} \cdot \left(\frac{u^+}{Z_0}\right)^* (e^{-\gamma z})^*\right\} \quad a \cdot a^* = |a|^2$$

$$P(z) = \frac{1}{2} \operatorname{Re}\left\{\underbrace{u^+ (u^+)^*}_{|u^+|^2} \frac{1}{Z_0^*} \underbrace{e^{-\alpha z} e^{-\alpha z}}_{\text{purely real}} \underbrace{e^{-j\beta z} e^{+j\beta z}}_1\right\} \quad \operatorname{Re}\left\{\frac{1}{z_0^*}\right\} \neq \frac{1}{\operatorname{Re}\{z_0^*\}}$$

$$P(z) = \underbrace{\frac{1}{2} |u^+|^2 \operatorname{Re}\left\{\frac{1}{Z_0^*}\right\}}_{P_0 = P(z=0)} \cdot e^{-2\alpha z} = \frac{1}{2} |u^+|^2 \frac{\operatorname{Re}\{Z_0\}}{|Z_0|^2} \cdot e^{-2\alpha z}$$


# 1 Np = 8.6859 dB

$$P(z=1m) = \underset{\substack{\uparrow \\ P(z=0)}}{P_0} e^{-2\alpha \cdot 1m}$$

$$\begin{aligned} L(\text{dB}) &= -10 \log_{10} \frac{P(z=1m)}{P_0} = -10 \log e^{-2\alpha \cdot 1m} \\ &= \alpha \cdot 10 \cdot 2 \cdot 1m \log_{10} e = \alpha \cdot \underbrace{20m \cdot \log e}_{1\text{Np} = 8,6859 \cdot \text{dB}} \end{aligned}$$

$$L(\text{dB}) = \alpha \left[ \frac{1}{m} \right] \cdot 8,6859 \quad \text{dB} \quad \left( \frac{\text{dB}}{m} \right)$$
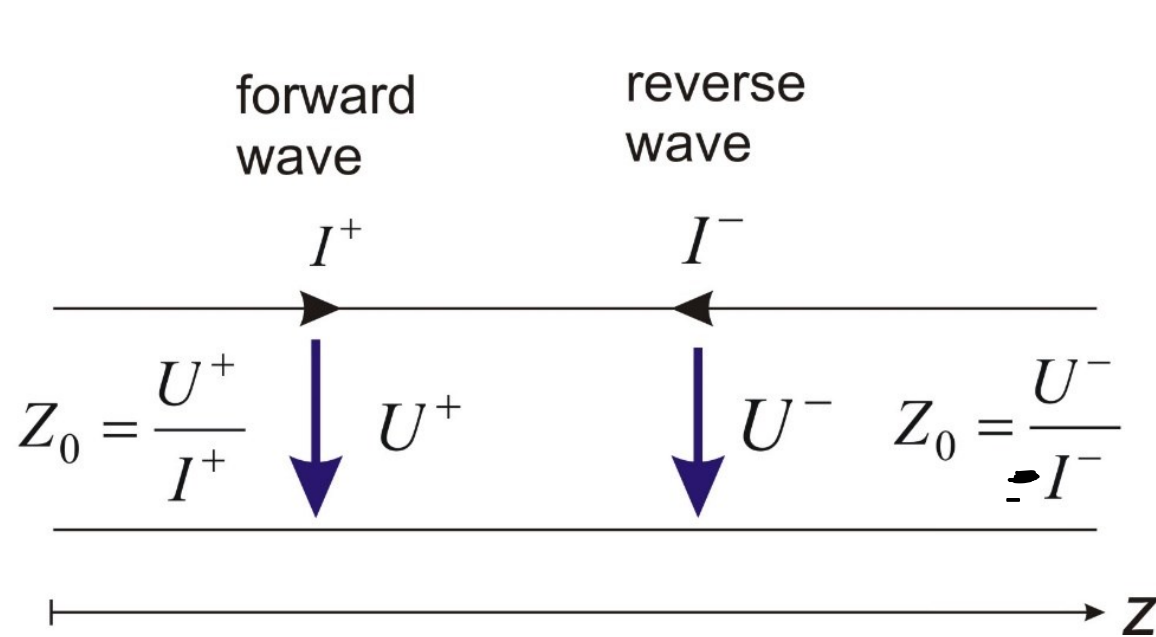
# Q1: What does the given power $P$ mean physically?



$$P = \frac{|u^{\oplus}|^2}{2Z_0}$$

↑  
forward

$Z_0$  assumed real number.

- 0% 1. Total loss power due to the resistive losses on the line.
- 7% 2. Peak power of the wave propagating in the positive +z direction.
- 67% **3.** Average power flow of a wave propagating in the positive +z direction. %
- 13% 4. Instantaneous power propagating in the positive +z direction when  $z = 0$ .
- 10% 5. Net power flow (= forward power - reverse power) on the line.
- 0% 6. Reflected power from the mismatched load impedance ( $Z_L \neq Z_0$ ).

$$U^+ = \text{peak voltage}$$

$$U_{\text{rms}} = \frac{U^+}{\sqrt{2}}$$

$$p(x) = u(t) \cdot i(t)$$

↑  
instantaneous power

10% 3%


# Wave travelling in the +z direction with constant magnitude

● = charge (electron)


red colour = positive potential

blue colour = negative potential

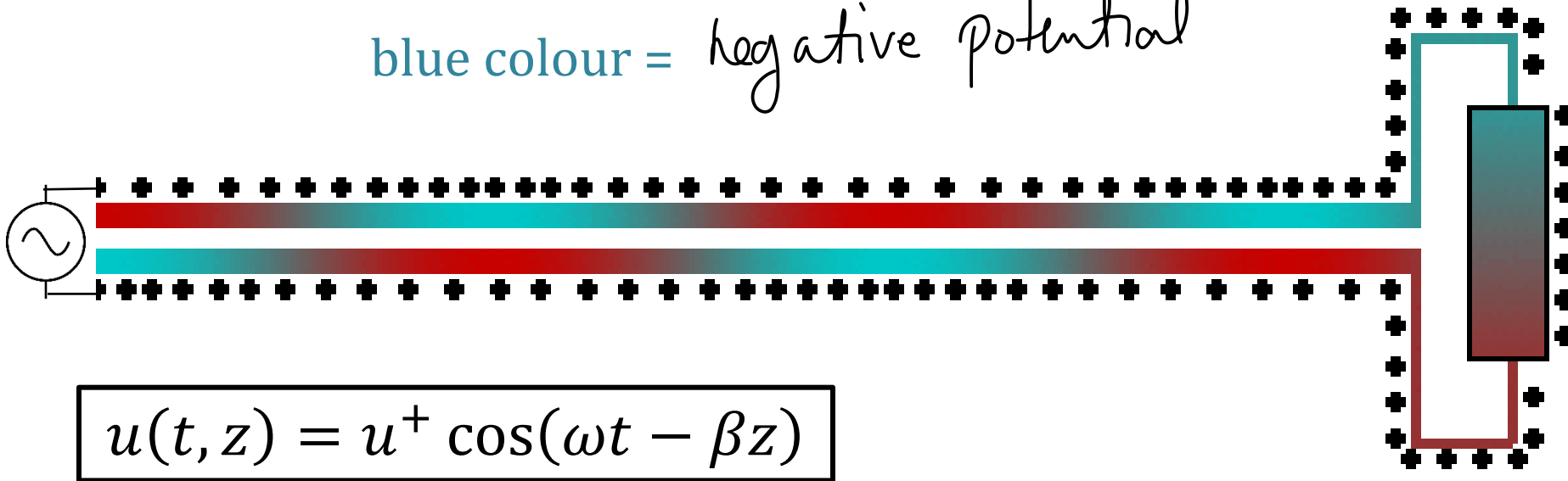impedance-  
matched load  
- no reflection!


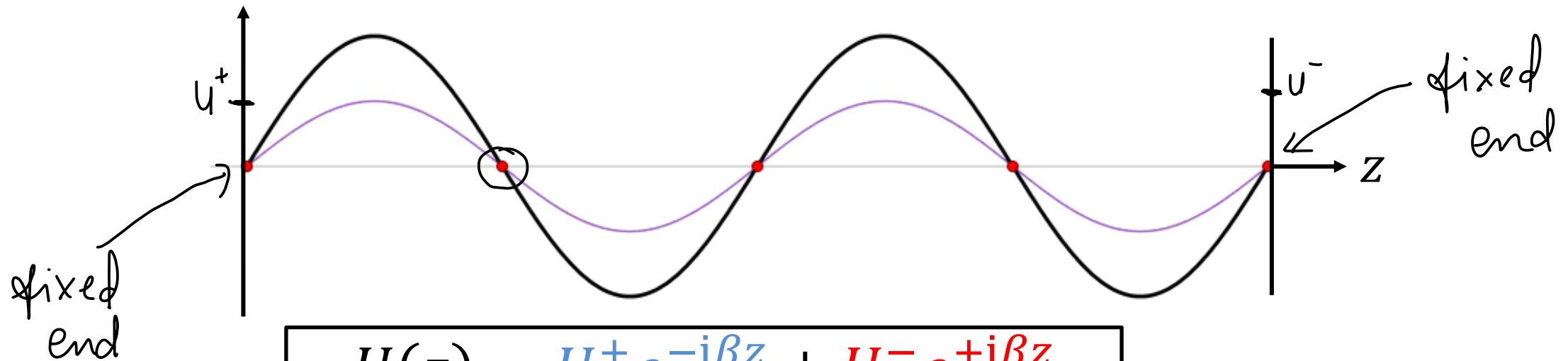
# Standing wave is a superposition (interference) of two opposite-travelling waves





$$U(z) = U^+ e^{-j\beta z} + U^- e^{+j\beta z}$$

- Blue curve = forward-propagating wave
  - Red curve = reverse-propagating wave
  - Black curve = sum of waves
  - Red dots ● = nodes
  - The "dome" between the red dots = antinode  
"extrema" / supremum
- $|U_{max}| = U^+ + U^-$   
 $|U_{min}| = 0$   
 $VSWR = \frac{|U_{max}|}{|U_{min}|} = \frac{U^+ + U^-}{0} = \infty$




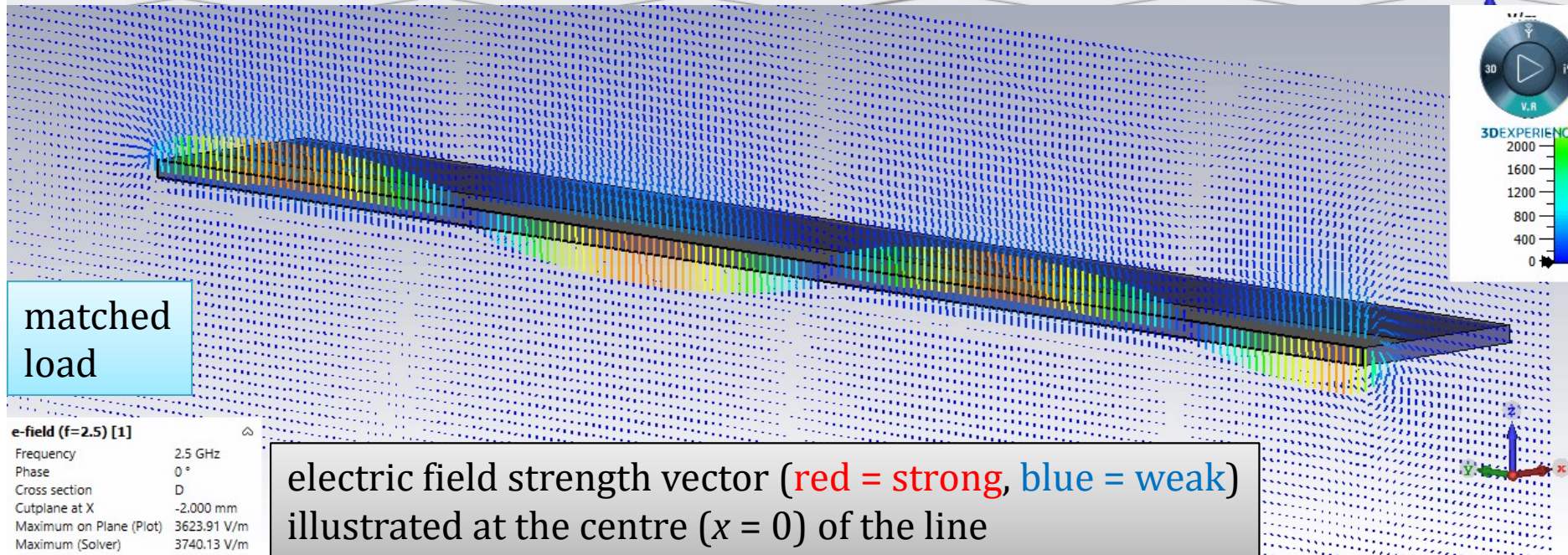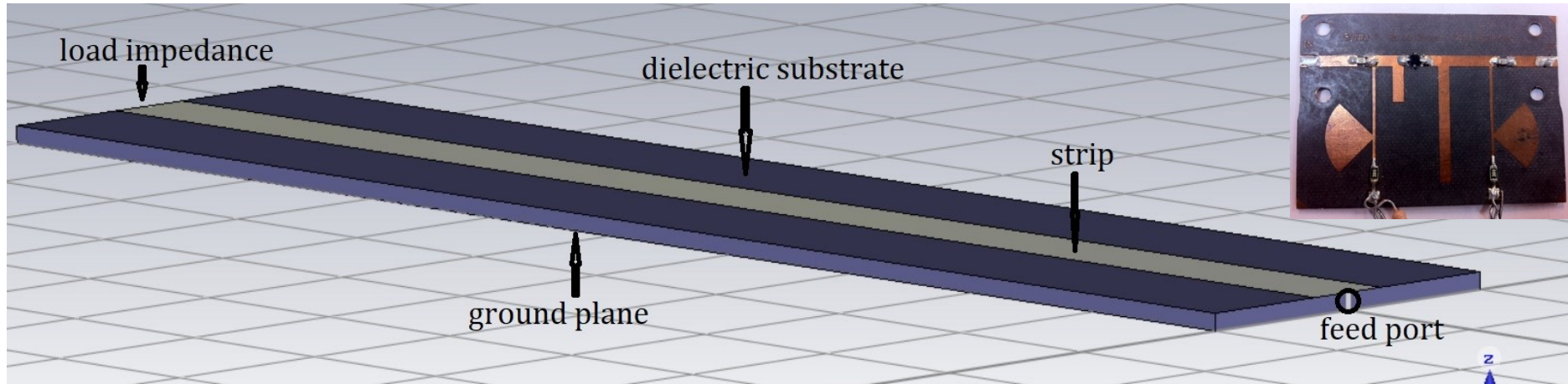
# Forward propagating wave in a 50- $\Omega$ microstrip line - **matched** load impedance





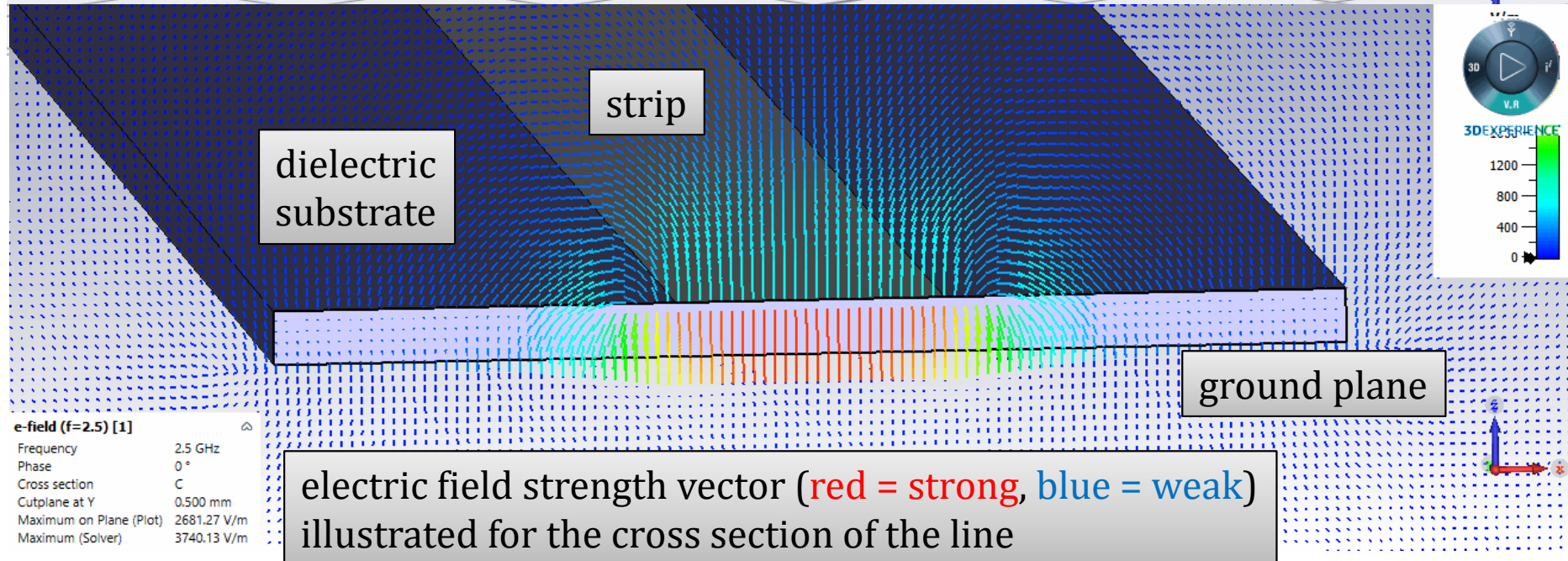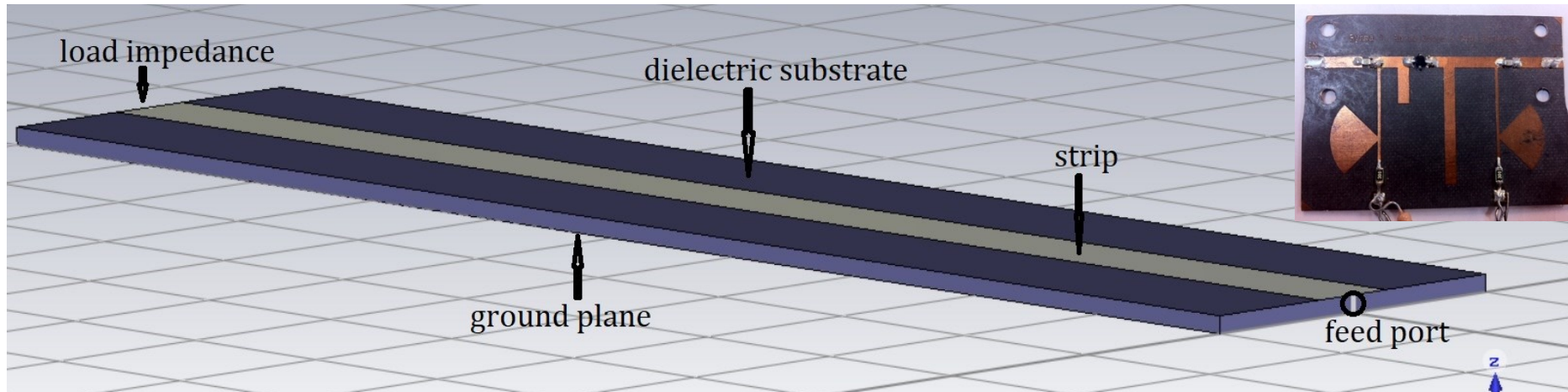
# Forward propagating wave in a 50- $\Omega$ microstrip line - **matched** load impedance





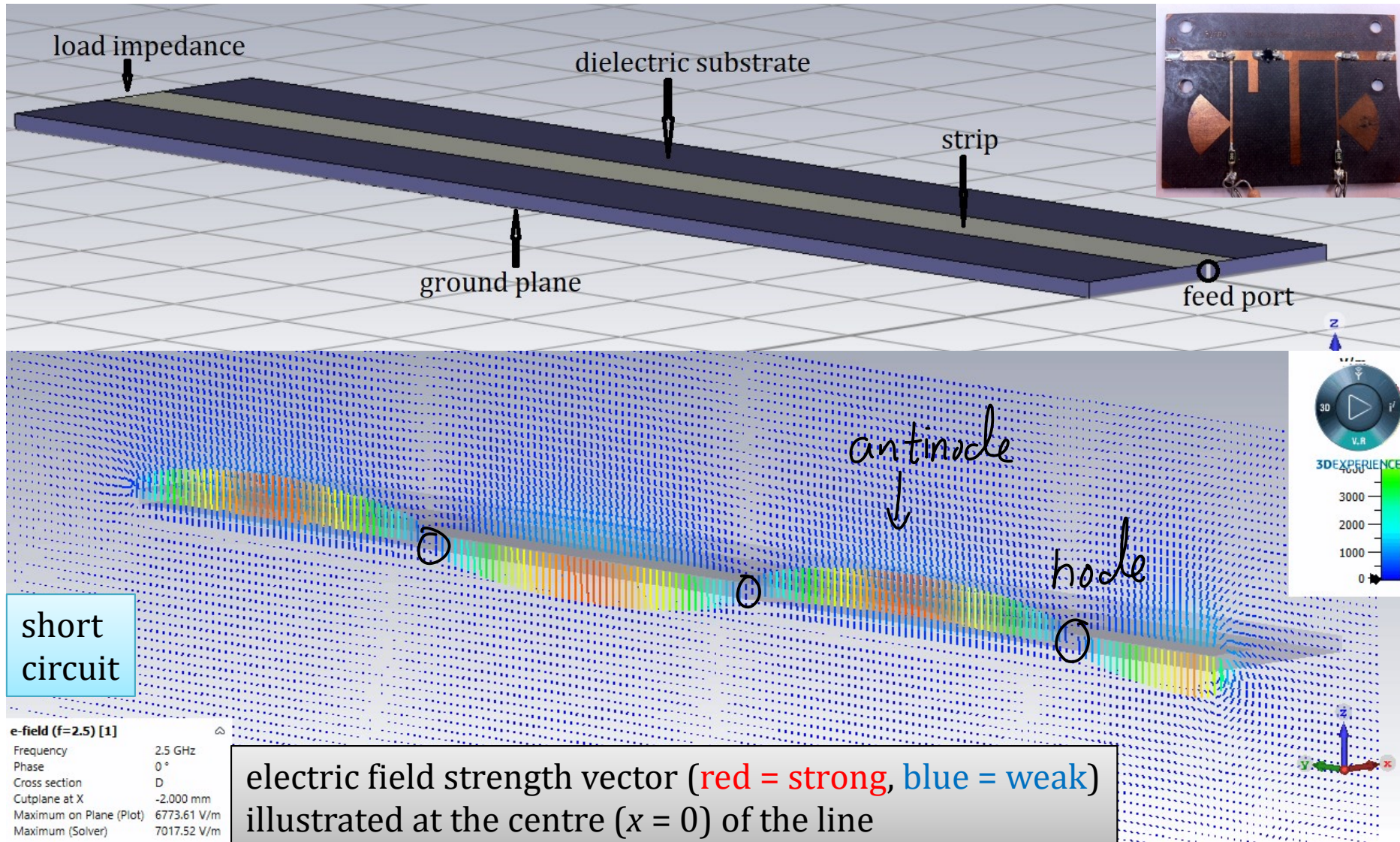
# Stationary standing wave in a 50-Ω microstrip line – **short circuit** as the load impedance



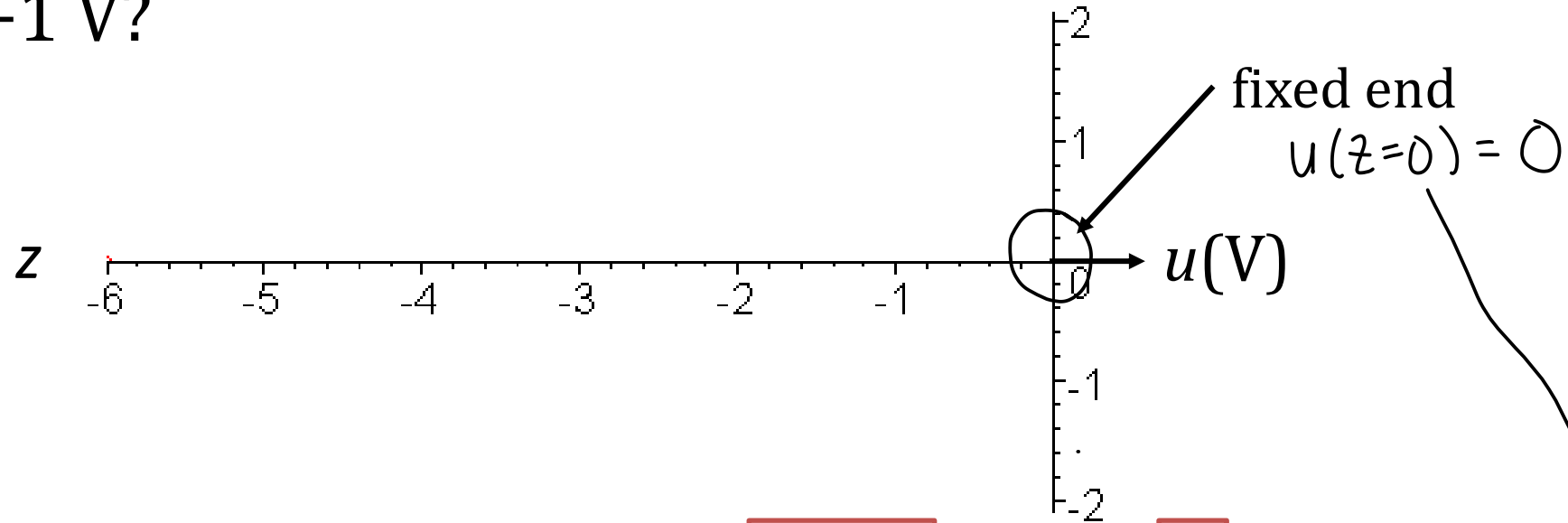Q2. What is the value  $u^-$  of the **reverse-propagating** voltage wave when  $u^+ = +1$  V?



2. vote



- 7% 1.  $u^- = +2$  V  
 6% 47% 2.  $u^- = +1$  V  
 3% 3.  $u^- = 0$  V  
 94% 40% **4.**  $u^- = -1$  V  
 3% 5.  $u^- = -2$  V  
 6. I don't know

+1 V


?

$$u(z) = u^+ e^{-j\beta z} + u^- e^{+j\beta z}$$

$$u(z=0) = u^+ e^{-j0} + u^- e^{j0} = u^+ + u^- = 0 \text{ V}$$

$$u^- = -u^+ = -1 \text{ V}$$

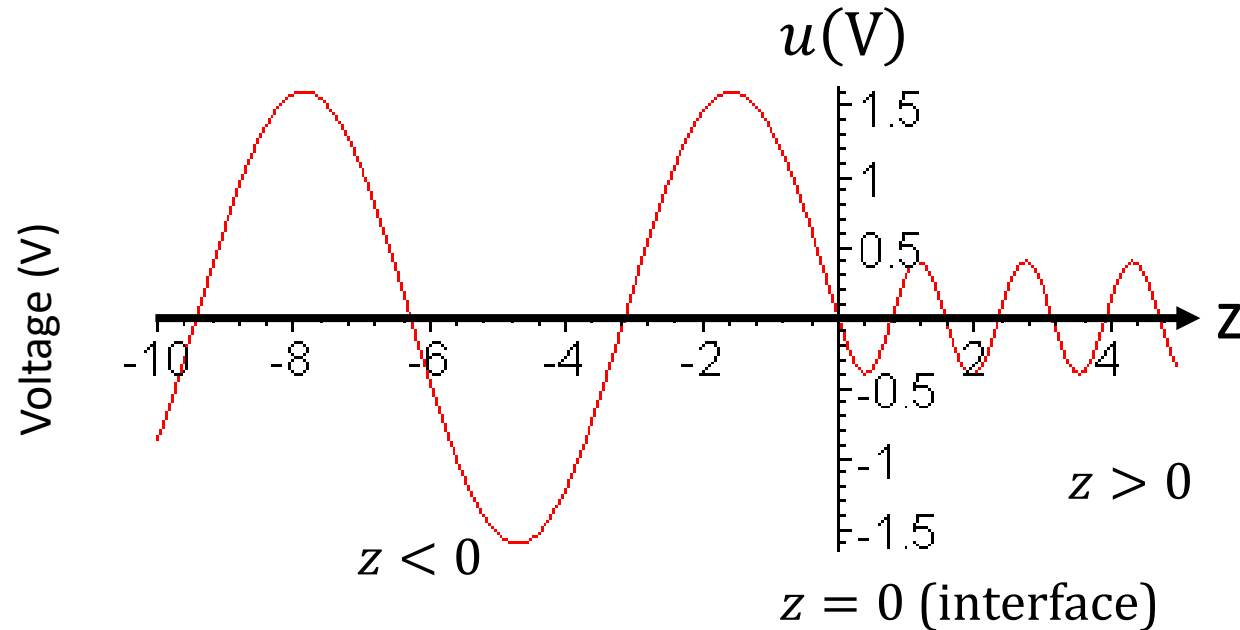Q3. Interface of two **unequal** characteristic impedances at  $z = 0$ .  
 What kind of wave takes place in the **region  $z < 0$** ?



$$u(z \leq 0) = u^+ e^{-j\beta z} + u^- e^{+j\beta z}$$


transmitted voltage

$$u(z > 0) = u^T e^{-j\beta z}$$


137. 1. A pure forward (to positive  $z$ ) propagating wave - i.e.,  $u^- = 0$  V.
07. 2. A pure reverse (to negative  $z$ ) propagating wave - i.e.,  $u^+ = 0$  V.
137. 3. A stationary standing wave - i.e., the net power flow is zero,  $|u^+| = |u^-|$
717. 4. A partial standing wave - i.e., net power flow forward (to positive  $z$ ),  $|u^+| > |u^-|$ .
37. 5. I don't know


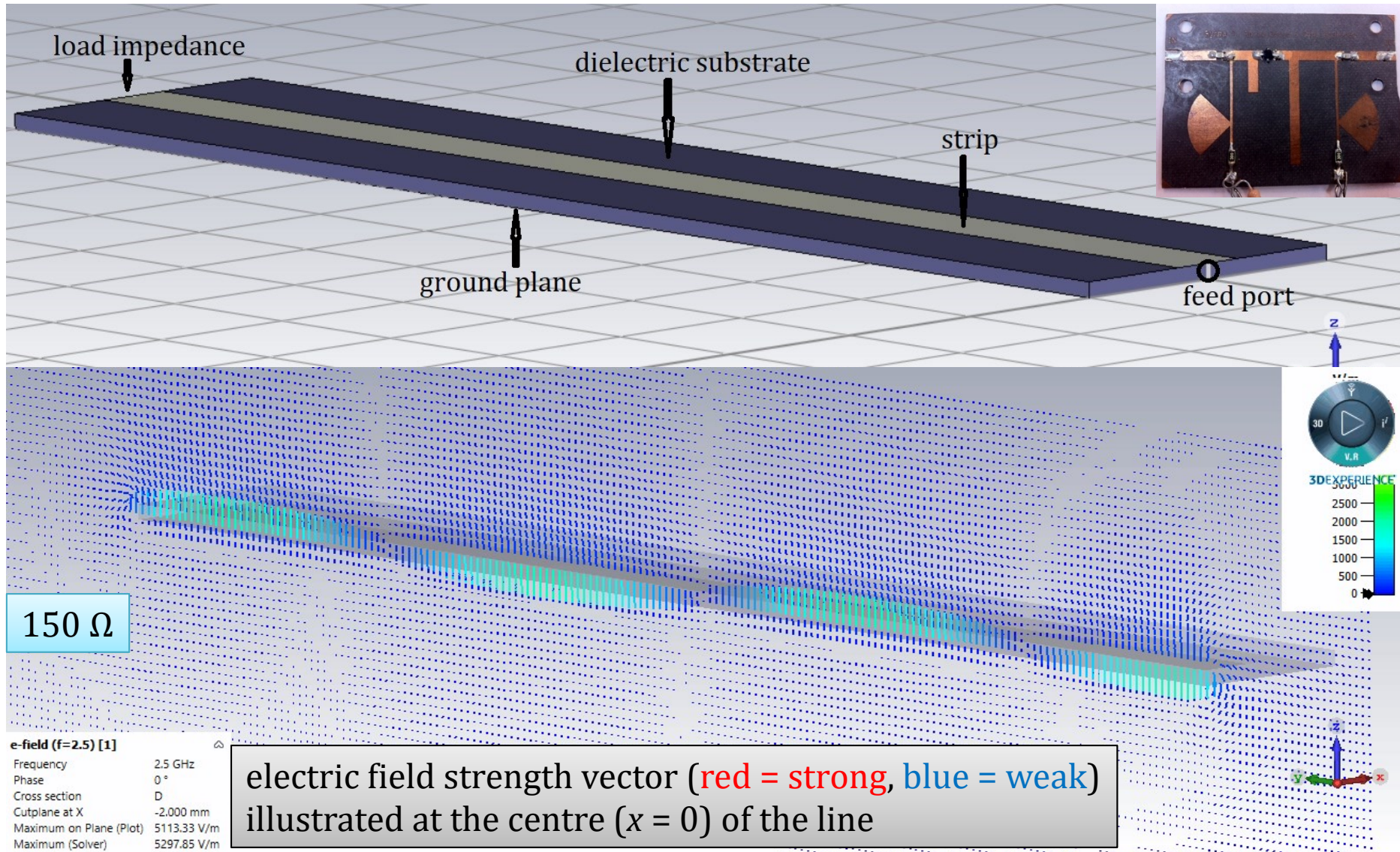
# Partial standing wave in a 50- $\Omega$ microstrip line - 150 $\Omega$ as the load impedance



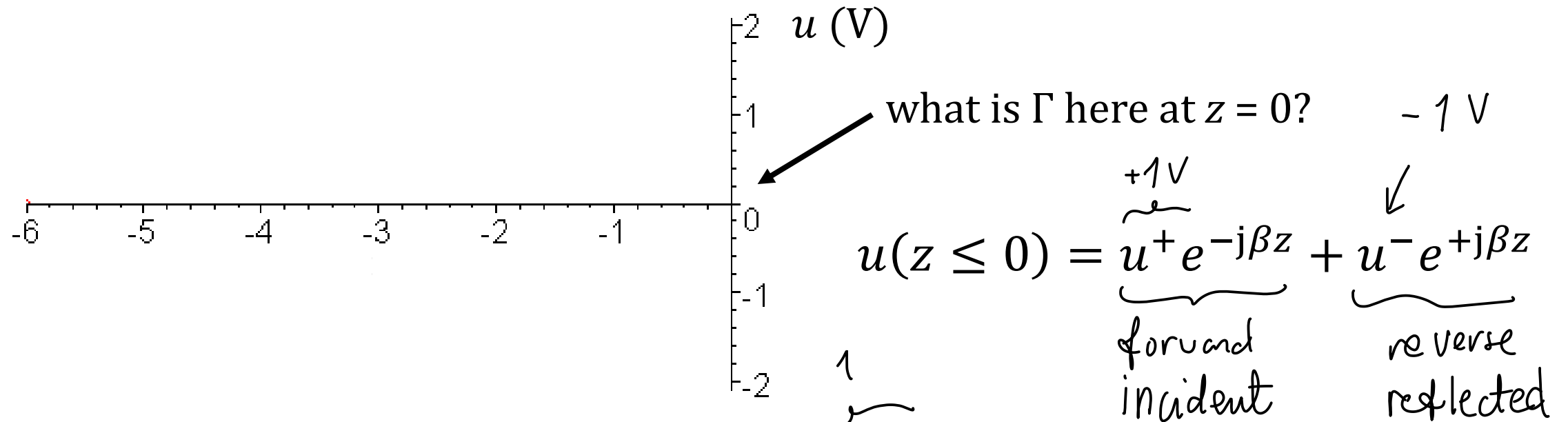
# Voltage reflection coefficient $\Gamma$ is defined as the ratio of the reflected and incident waves



$$\Gamma = \frac{\text{reflected voltage (at } z = 0\text{)}}{\text{incident voltage (at } z = 0\text{)}} = \frac{\overbrace{u^- e^{+j\beta \cdot 0}}^1}{\underbrace{u^+ e^{-j\beta \cdot 0}}_1} = \frac{u^-}{u^+} = \frac{-1\text{ V}}{+1\text{ V}} = -1$$

$\Gamma = -1$  means short circuit

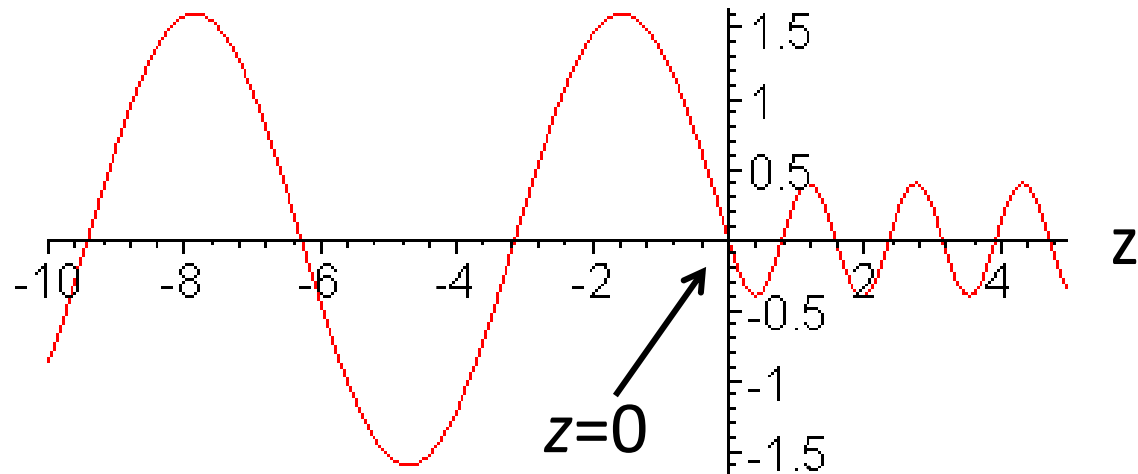Q4.  $u^+ = +1$  V. What is the voltage reflection coefficient  $\Gamma$  at  $z = 0$ ?



+1 V

$$u(z \leq 0) = u^+ e^{-j\beta z} + u^- e^{+j\beta z}$$

$$u(z > 0) = u^T e^{-j\beta z}$$

+0.4 V

$$\Gamma = \frac{u^-}{u^+}$$

3% 1.  $\Gamma = 0$

2. vote 9% 2.  $\Gamma = -1$

↓ 0% 3.  $\Gamma = 1$

21% 35% 4.  $0 < \Gamma < 1$

79% 50% **5.**  $-1 < \Gamma < 0$

3% 6. I don't know

$$u(z=0) = u^+ e^{-j\beta \cdot 0} + u^- e^{+j\beta \cdot 0} = u^+ + u^- = 0.4 \text{ V}$$


$$u^- = 0.4 \text{ V} - 1 \text{ V}$$

$$u^- = -0.6 \text{ V}$$

$$\Gamma = \frac{u^-}{u^+} = \frac{-0.6 \text{ V}}{+1 \text{ V}} = -0.6 (< 0)$$


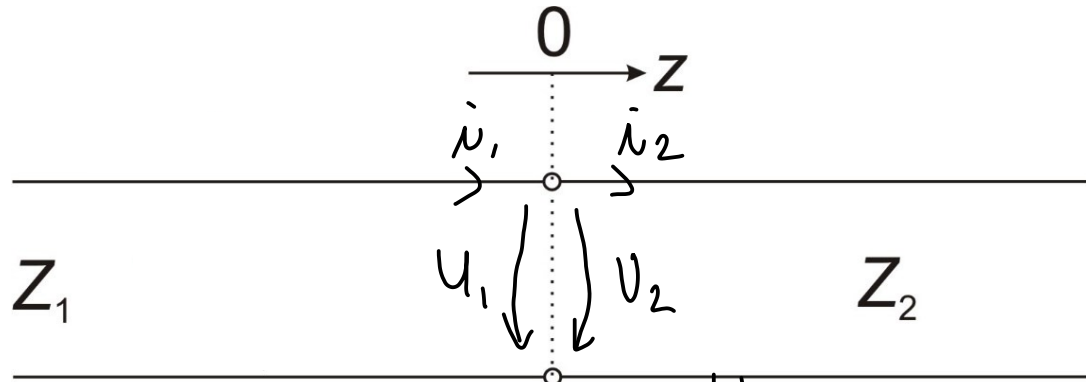
# Voltage and current are continuous in the interface ( $z = 0$ )




voltage is continuous :  $U_1 = U_2$

current —||— :  $i_1 = i_2$

⏟  
Kirchhoff's (I)  
current law

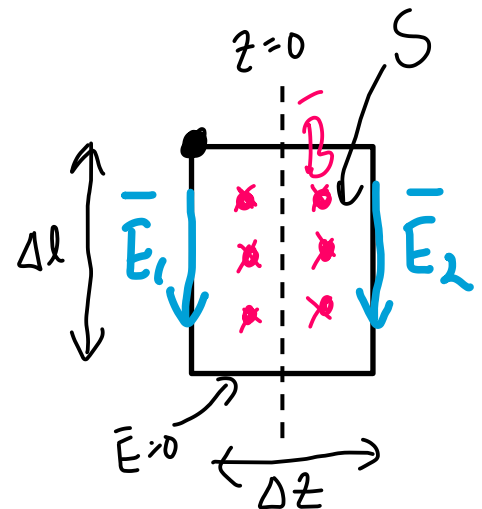Faraday's law :  $\nabla \times \vec{E} = -j\omega \vec{B} \Leftrightarrow \oint \vec{E} \cdot d\vec{l} = -j\omega \iint \vec{B} \cdot d\vec{S}$  ← select integration path/area freely




$$\oint \vec{E} \cdot d\vec{l} =$$

$$\vec{E}_1 \cdot \Delta l - E_2 \Delta l \xrightarrow{\Delta z \rightarrow 0} \underbrace{E_1 \Delta l}_{U_1} - \underbrace{E_2 \Delta l}_{U_2} = 0 \Leftrightarrow \boxed{U_1 = U_2}$$

$$\iint \vec{B} \cdot d\vec{S} = B \cdot \delta z \cdot \Delta l \xrightarrow[\delta z \rightarrow 0]{\Delta z \rightarrow 0} 0$$
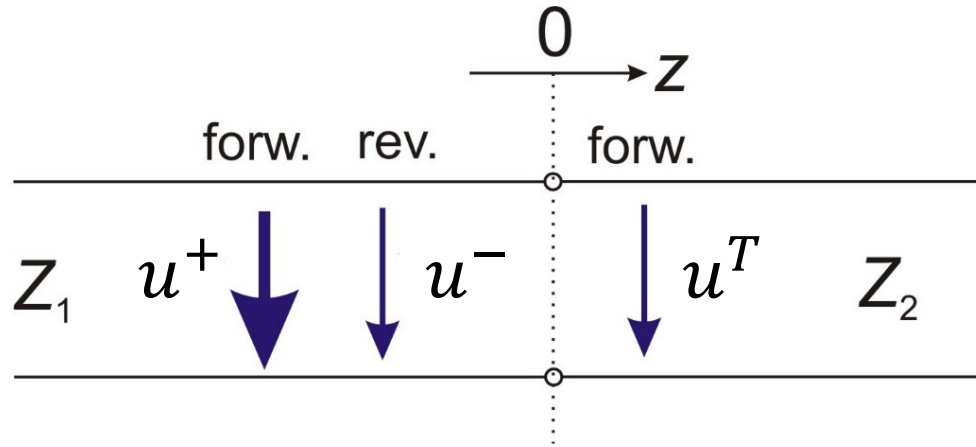
# Voltage and current are continuous in the interface ( $z = 0$ )



$$u(z = 0) = u^+ e^{-j\beta z} + u^- e^{+j\beta z} = u^T e^{-j\beta z}$$

$$I(z = 0) = \frac{u^+}{Z_1} e^{-j\beta z} - \frac{u^-}{Z_1} e^{+j\beta z} = \frac{u^T}{Z_2} e^{-j\beta z}$$

neg. current direction

$$\Gamma = \frac{u^-}{u^+}$$

Transmission coefficient:

$$T = \frac{u^T}{u^+}$$

voltage continuity

$$\begin{cases} u(z=0) = u^+ + u^- = u^T \\ i(z=0) = \frac{u^+}{Z_1} - \frac{u^-}{Z_1} = \frac{u^T}{Z_2} \end{cases}$$

$$\frac{u^-}{u^+} = \Gamma = \text{voltage refl. coeff.}$$


$$\Gamma = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

$$T = \frac{u^T}{u^+} = \frac{\text{transmitted voltage}}{\text{incident voltage}} = \frac{u^+ + u^-}{u^+}$$

$\Gamma$  is complex number / phasor

$$= \frac{u^+}{u^+} + \frac{u^-}{u^+} = 1 + \Gamma = T$$

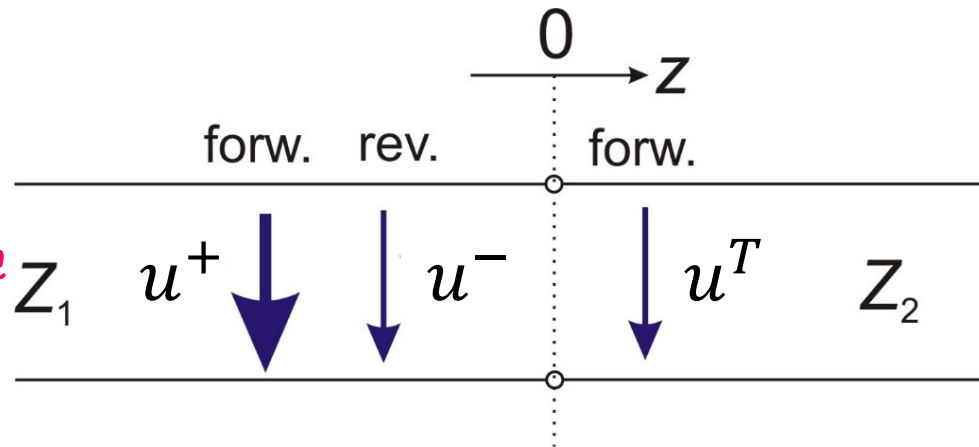Q5:  $\Gamma = -0.6$  and  $V^+ = 1$  V. What is the **maximum** instantaneous voltage of the standing wave in  $z \leq 0$ ?



$$u(z \leq 0) = u^+ e^{-j\beta z} + u^- e^{+j\beta z}$$

$$u(z > 0) = u^T e^{-j\beta z}$$

$$u^+ = 1 \text{ V}, \Gamma = -0.6, u^T = 0.4 \text{ V}$$

$$\Gamma = \frac{u^-}{u^+} = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$



$$T = \frac{u^T}{u^+} = 1 + \Gamma$$

$$u(z=0) = u^+ + u^- = u^T = 0.4 \text{ V} \Leftrightarrow u^- = -0.6 \text{ V}$$

$$z \leq 0 \quad u(z) = 1 \text{ V} \cdot \underbrace{e^{-j\beta z}}_{+1} - 0.6 \text{ V} \cdot \underbrace{e^{+j\beta z}}_{-1}$$

$$|U_{\max}| = 1 \text{ V} \cdot 1 - 0.6 \text{ V} (-1) = 1 \text{ V} + 0.6 \text{ V} = 1.6 \text{ V}$$

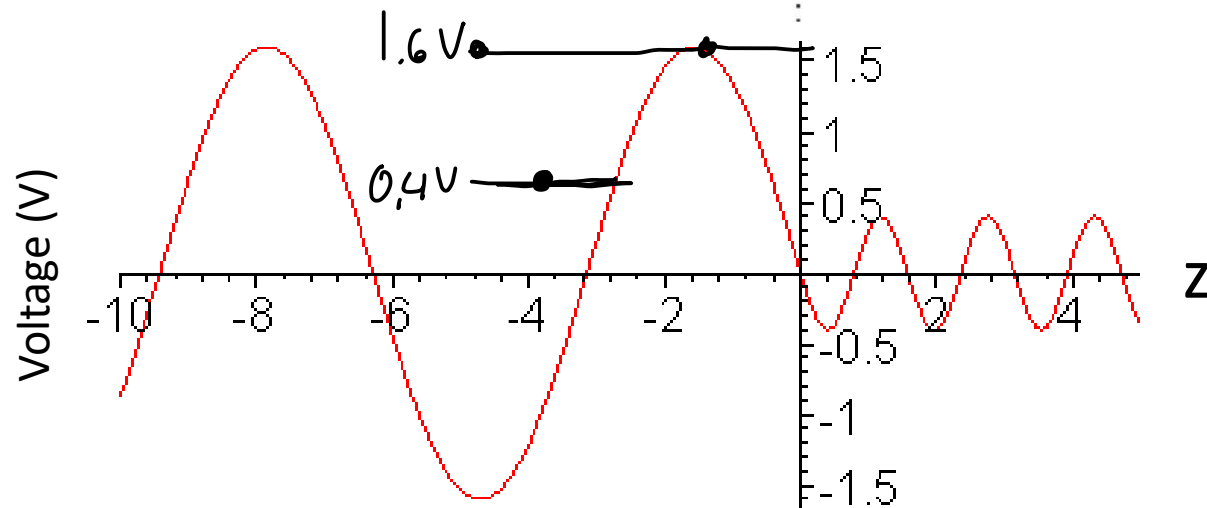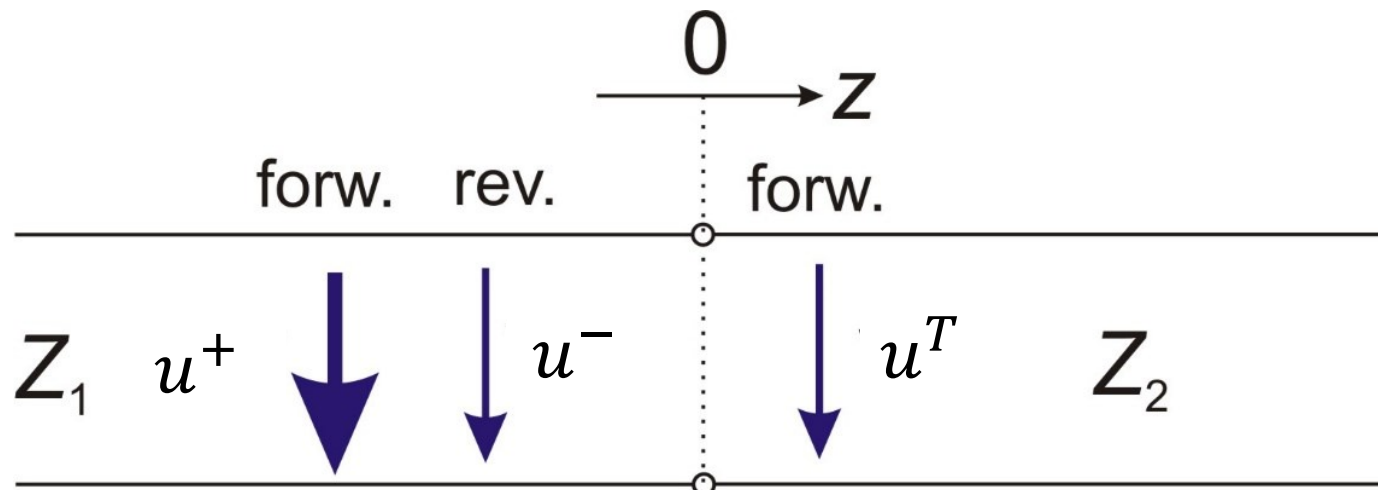- 2 vote ↓
- 13% 22% 1. 0.4 V
- 3% 2. 0.6 V
- 6% 3. 1 V
- 9% 4. 1.4 V
- 88% 56% 5. 1.6 V
- 3% 6. I don't know



$$u^+ = 1 \text{ V}, u^- = -0.6 \text{ V}$$

$$u^T = 0.4 \text{ V}$$


$$\Gamma = \frac{V^-}{V^+} = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

$$T = \frac{V^T}{V^+} = 1 + \Gamma$$

$$u(z \leq 0) = 1 \text{ V} \cdot e^{-j\beta z} - 0.6 \text{ V} \cdot e^{+j\beta z}$$

$$u(z > 0) = 0.4 \text{ V} \cdot e^{-j\beta z}$$
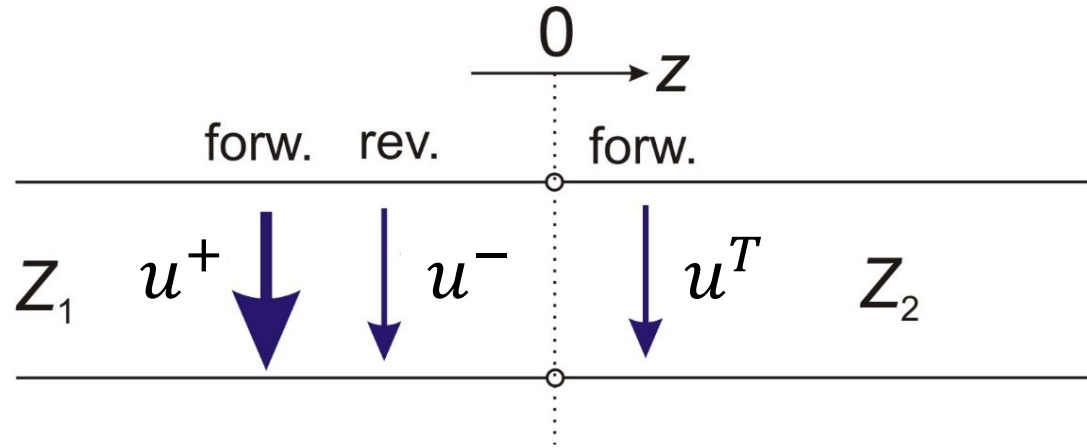
# Envelope of the standing wave has a $\lambda/2$ periodicity



$$\Gamma = \frac{u^-}{u^+} = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

$$T = \frac{u^T}{u^+} = 1 + \Gamma$$


$$u(z) = u^+ e^{-j\beta \cdot z} + u^- e^{+j\beta \cdot z} = u^+ e^{-j\beta z} + \Gamma \cdot u^+ e^{-j\beta z} = u^+ e^{-j\beta z} (1 + \Gamma e^{j2\beta z})$$

$$|u(z)| = |u^+ e^{-j\beta z}| |1 + \Gamma e^{j2\beta z}| = \pm |u^+| |1 + \Gamma e^{j2\beta z}|$$

$$i(z) = \frac{u^+}{Z_1} e^{-j\beta \cdot z} - \frac{u^-}{Z_1} e^{+j\beta \cdot z} = \frac{u^+}{Z_1} e^{-j\beta z} - \frac{\Gamma u^+}{Z_1} e^{+j\beta z} = \frac{u^+}{Z_1} e^{-j\beta z} (1 - \Gamma e^{j2\beta z})$$

$$|i(z)| = \pm \left| \frac{u^+}{Z_1} \right| |1 - \Gamma e^{j2\beta z}|$$

instantaneous voltage  $u(z, t)$

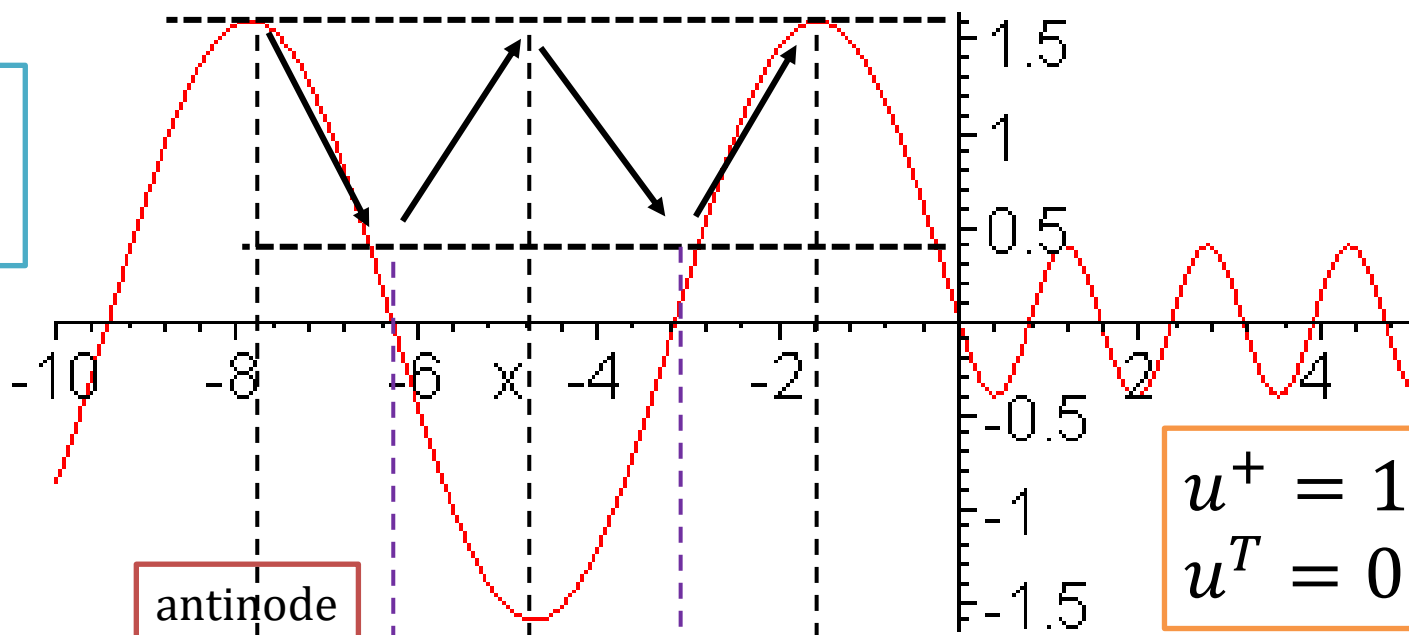

$$u^+ = 1 \text{ V}, u^- = -0.6 \text{ V}$$


$$u^T = 0.4 \text{ V}$$

antinode

Voltage Standing Wave Ratio:


$$VSWR = \frac{|u_{max}|}{|u_{min}|} = \frac{1.6 \text{ V}}{0.4 \text{ V}} = 4$$

envelope  $\pm |u(z)|$

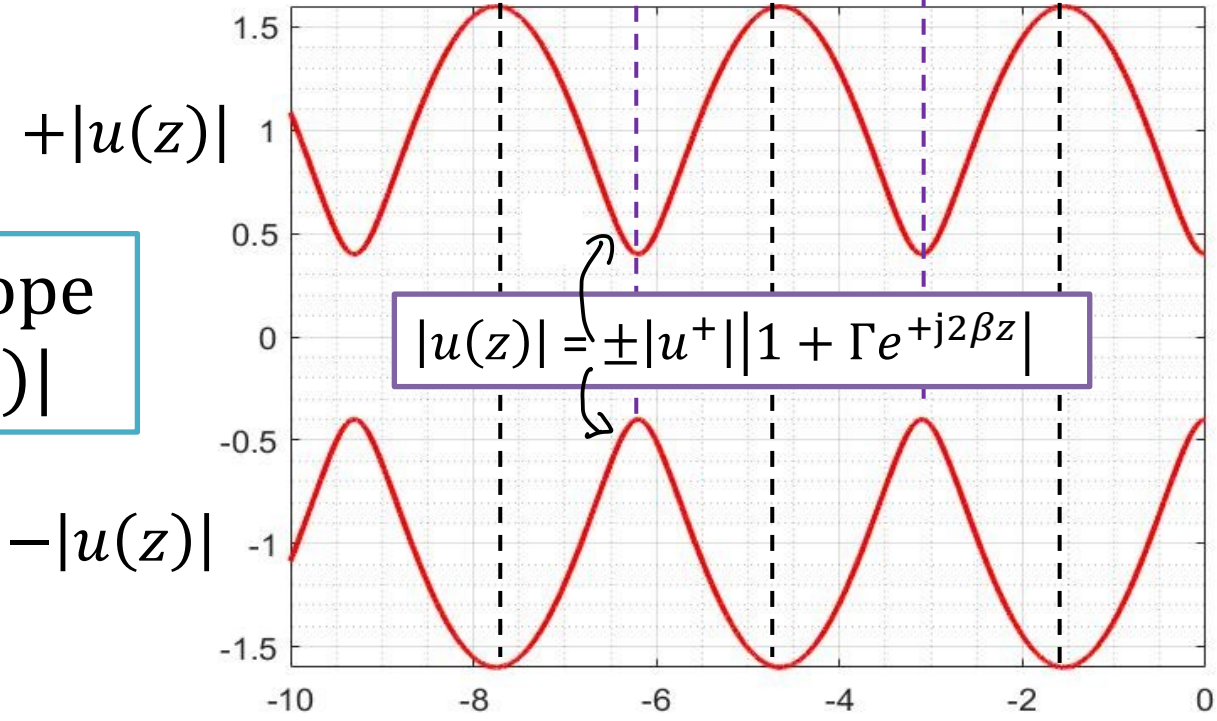

$$|u(z)| = \pm |u^+| |1 + \Gamma e^{j2\beta z}|$$

# In-class task

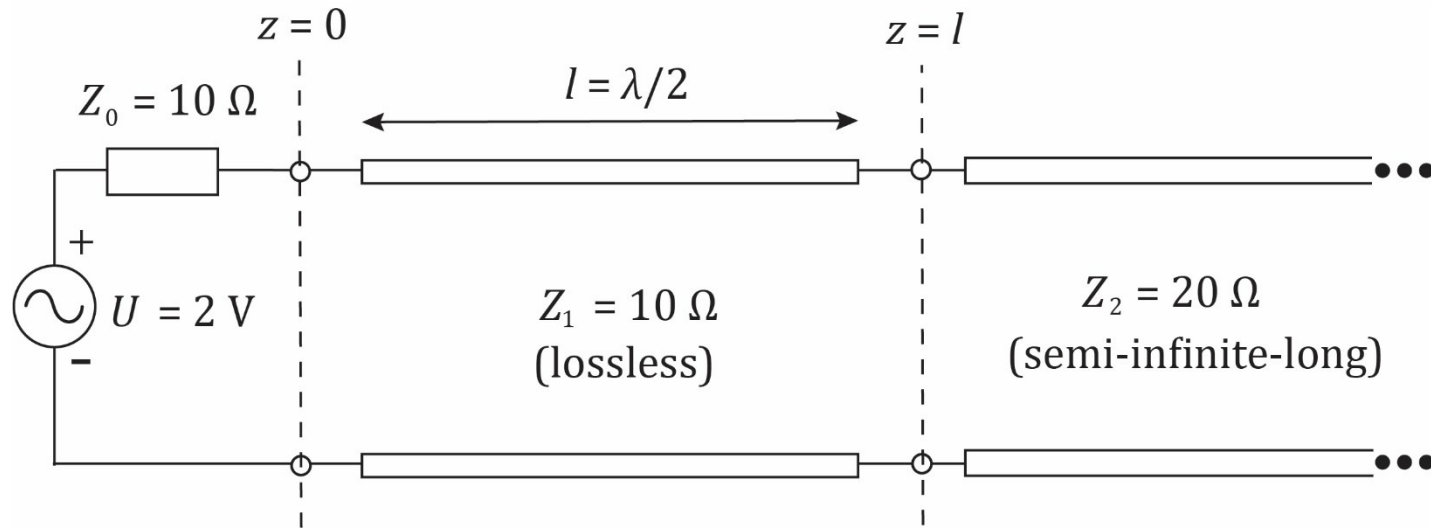

$$u(z) = u^+ e^{-j\beta \cdot z} + u^- e^{+j\beta \cdot z}$$

$$I(z) = \frac{u^+}{Z_1} e^{-j\beta \cdot z} - \frac{u^-}{Z_1} e^{+j\beta \cdot z}$$

$$\Gamma = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$


Determine the numerical values of the

- 1) voltage of the forward-propagating wave  $u^+$ ,
- 2) transmitted voltage amplitude  $u^T = u(z = l)$  in region  $z \geq l$ ,
- 3) total voltage  $u(z = 0)$  and total current  $i(z = 0)$ ,
- 4) input impedance  $Z(z = 0) = \frac{u(z=0)}{i(z=0)}$  looking into +z direction.
- 5) Answer the question: why the input impedance  $Z(z = 0) \neq Z_1$ ?

The teachers will be circleing in the breakout rooms for help.

Return your effort in the return box in MyCourses at the end of the session, latest at 12:30 pm.

# In-class task

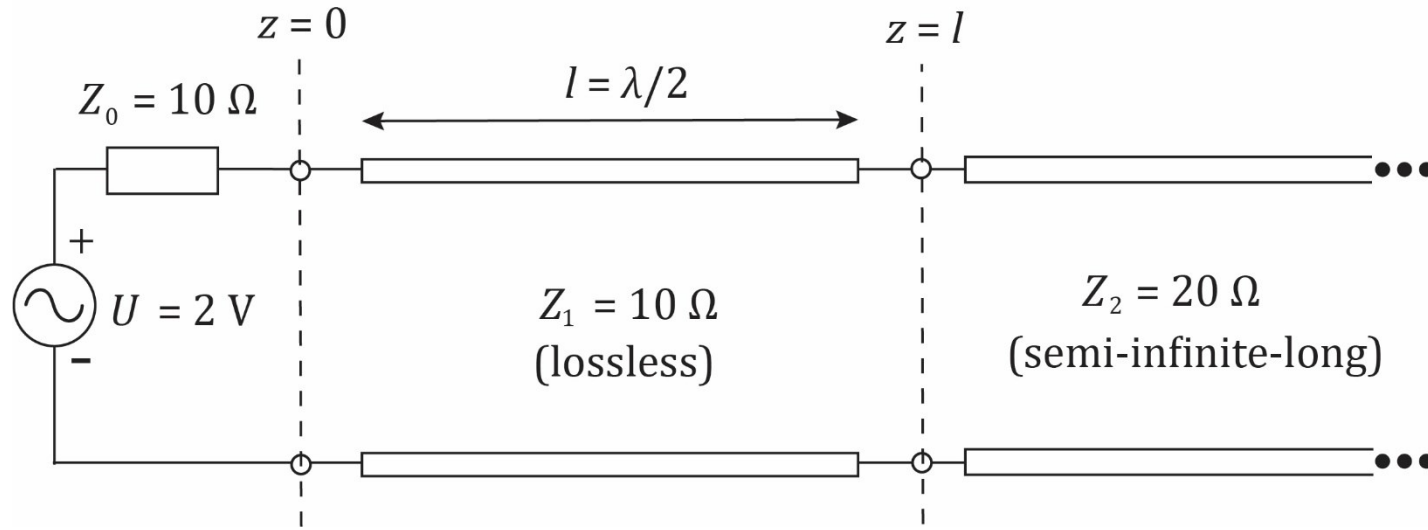

Determine the numerical values of the

- 1) voltage of the forward-propagating wave  $u^+$ ,
- 2) transmitted voltage amplitude  $u^T = u(z = l)$  in region  $z \geq l$ ,
- 3) total voltage  $u(z = 0)$  and total current  $i(z = 0)$ ,
- 4) input impedance  $Z(z = 0) = \frac{u(z=0)}{i(z=0)}$  looking into  $+z$  direction.
- 5) Answer the question: why the input impedance  $Z(z = 0) \neq Z_1$ ?

1) At  $z = 0$ , the forward-propagating wave sees only the impedance  $Z_1$  of the first transmission line. Hence, we have a voltage division of  $U$  between  $Z_1$  and  $Z_0$ . See further details in Chapter 2.8 ("Transients of transmission lines").  $u^+ = U \frac{Z_1}{Z_0 + Z_1} = 1\text{ V}$

2) First, we determine the value of the voltage reflection coefficient at  $z = l$ :  $\Gamma = \frac{u^- e^{+j\beta \cdot l}}{u^+ e^{-j\beta \cdot l}} = \frac{u^- e^{+j\frac{2\pi}{\lambda} \cdot \frac{\lambda}{2}}}{u^+ e^{-j\frac{2\pi}{\lambda} \cdot \frac{\lambda}{2}}} = \frac{u^- e^{+j\pi}}{u^+ e^{-j\pi}} = \frac{u^- (-1)}{u^+ (-1)} = \frac{u^-}{u^+} = \frac{Z_2 - Z_1}{Z_2 + Z_1} = \frac{1}{3}$ .

Then we can calculate the voltage  $u^T = u(z = \frac{\lambda}{2}) = u^+ e^{-j\frac{2\pi}{\lambda} \cdot \frac{\lambda}{2}} + u^- e^{+j\frac{2\pi}{\lambda} \cdot \frac{\lambda}{2}} = u^+ e^{-j\pi} + \Gamma u^+ e^{+j\pi} = u^+ (-1 - \frac{1}{3} \cdot 1) = -\frac{4}{3} u^+ = -\frac{4}{3}\text{ V}$

3) Total voltage at  $z = 0$ ,  $u(z = 0) = u^+ e^{-j0} + u^- e^{+j0} = u^+ + \Gamma u^+ = u^+ (1 + \Gamma) = \frac{4}{3}\text{ V}$

Total current at  $z = 0$ ,  $i(z = 0) = \frac{u^+}{Z_1} e^{-j0} - \frac{u^-}{Z_1} e^{+j0} = \frac{u^+}{Z_1} - \Gamma \frac{u^+}{Z_1} = \frac{u^+}{Z_1} (1 - \Gamma) = \frac{1}{15}\text{ A}$

4) The input impedance looking into  $+z$  direction  $Z(z = 0) = \frac{u(z=0)}{i(z=0)} = \frac{\frac{4}{3}\text{ V}}{\frac{1}{15}\text{ A}} = 20\ \Omega$ .

5) The total input impedance is affected by the reflected wave, too. This is more discussed in the next lecture on 27.1.