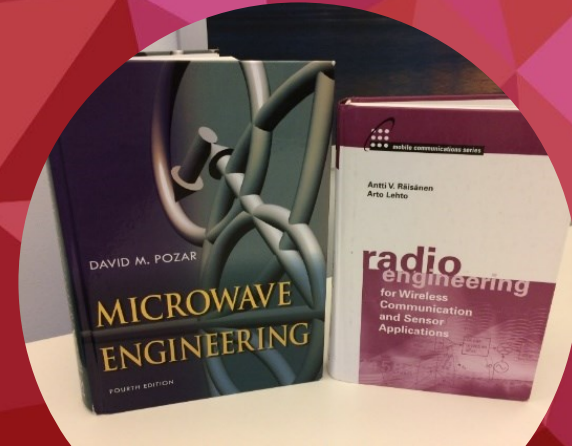


Microwave engineering I (MiWE I)

Interactive lecture 2 of Topic 3
Scattering parameters
February 17, 2022

The main learning outcome of the course is to create readiness to work in microwave engineering related tasks and projects and enable further studies and continuous learning in microwave engineering.






Topic 3: Learning outcomes and content

- The student can
 - **analyze** the operation of basic microwave circuits and resonators based on calculations and simulations (AWRDE).
 - **model** and **analyze** the operation of microwave circuits and resonators with suitable circuit parameters, especially the scattering parameters (S-parameters).
- Series and parallel resonant circuits (Pojar chapter 6.1)
- The scattering matrix (Pojar chapter 4.3)
- The transmission (ABCD) matrix (Pojar chapter 4.4)

These lecture slides and notes are not designed for self-study.
Please, use the course book chapters 4 and 6 for self-study.


amplitude of oscillation

HIGH QUALITY FACTOR

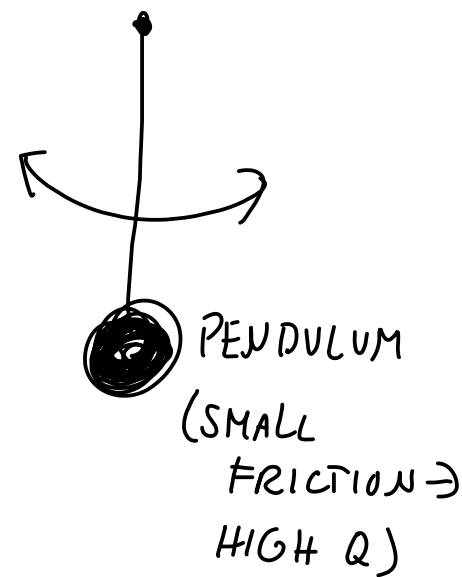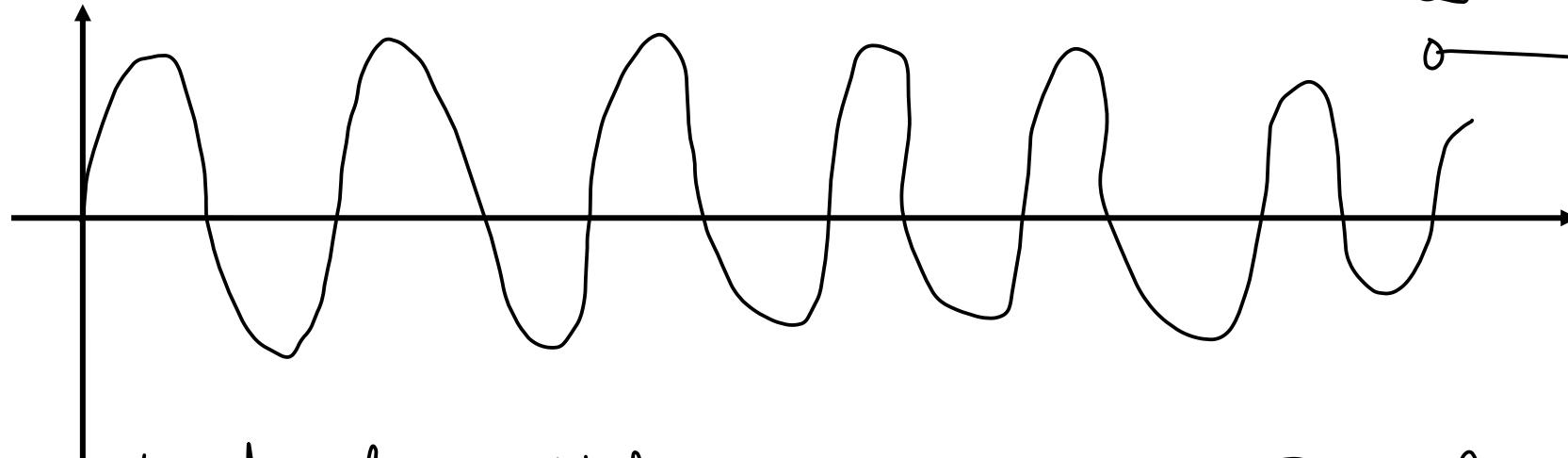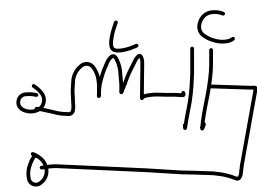

amplitude of oscillation

LOW QUALITY FACTOR

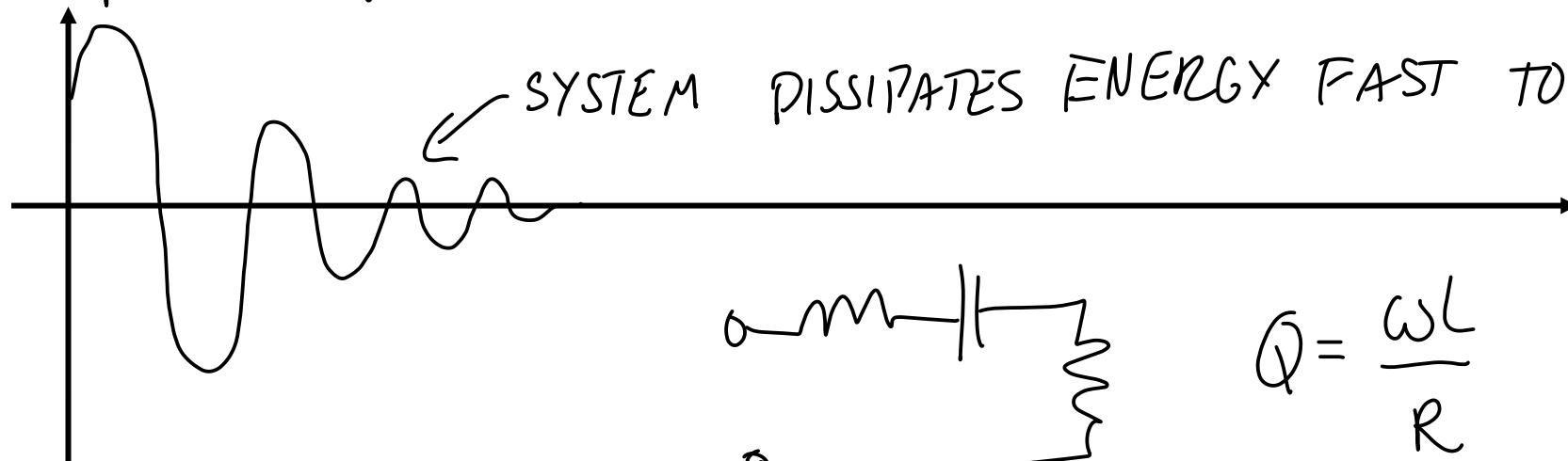

SYSTEM DISSIPATES ENERGY FAST TO THE INTERNAL LOSSES




$$Q = \frac{\omega L}{R}$$

↑

if R large → Q is small

In-class task in Breakout rooms

"tangent formula"

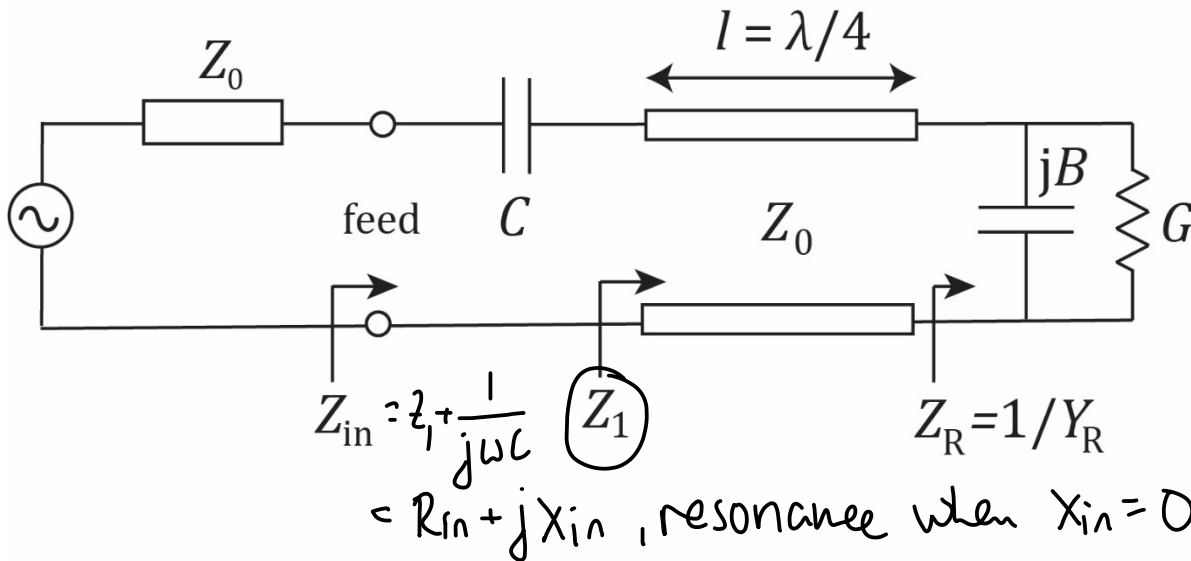

$$G = \frac{1}{50} \text{ S}$$

$$B = \frac{1}{100} \text{ S}$$

$$C = 6.3 \text{ pF}$$

$$Z_0 = 50 \text{ } \Omega$$

$$Z_1 = Z_0 \frac{Z_R + jZ_0 \tan(\beta l)}{Z_0 + jZ_R \tan(\beta l)}$$

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2} \quad \tan\left(\frac{\pi}{2}\right) = \infty$$

$$Z_1 = Z_0 \frac{jZ_0}{jZ_R} = \frac{Z_0^2}{Z_R} = Z_0^2 Y_R$$


- Calculate analytically or graphically using the Smith chart (see the next page), at which frequency the circuit is in resonance – i.e., calculate at which frequency $Z_{in} = Z_0$.
- Explain, how is it possible that the circuit is in resonance even though there are no inductive components in the circuit.
- If you have time, simulate the input reflection coefficient with AWRDE in the frequency range of 0.5-1.5 GHz.
- Return your effort (e.g., analytic calculation) in MyCourses latest at 12:30.

In-class task

$$G = \frac{1}{50} \text{ S} ; B = \frac{1}{100} \text{ S}$$

$$C = 6.3 \text{ pF} ; Z_0 = 50 \Omega$$
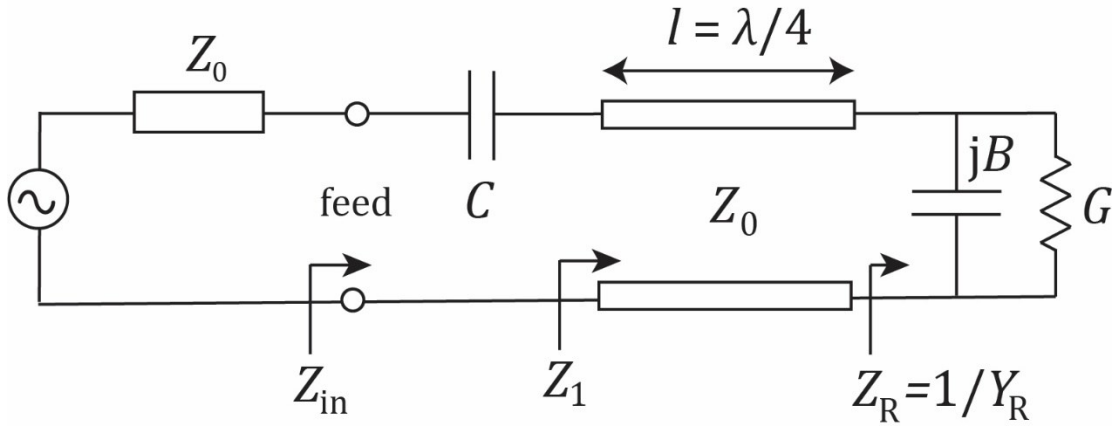
$$Z_1 = Z_0 \frac{Z_R + jZ_0 \tan(\beta l)}{Z_0 + jZ_R \tan(\beta l)}$$



$$Y_R = G + jB = \left(\frac{1}{50} + j\frac{1}{100}\right) \text{ S} ; Z_R = \frac{1}{Y_R}$$

$$\tan\left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}\right) = \tan\left(\frac{\pi}{2}\right) = \infty$$

$$a) Z_1 = Z_0 \frac{Z_R + jZ_0 \tan(\beta l)}{Z_0 + jZ_R \tan(\beta l)} = Z_0 \frac{\frac{Z_R}{\tan(\beta l)} + jZ_0}{\frac{Z_0}{\tan(\beta l)} + jZ_R} = Z_0 \frac{jZ_0}{jZ_R} = \frac{Z_0^2}{Z_R} = Z_0^2 \cdot Y_R = (50\Omega)^2 \cdot \left(\frac{1}{50} + j\frac{1}{100}\right) \text{ S}$$

$$= 50 + j25 \Omega$$


The circuit is in resonance if $-\frac{1}{\omega C} = -25 \Omega \Leftrightarrow f = \frac{-1}{-25\Omega \cdot 2\pi \cdot 6.3 \cdot 10^{-12} \text{ F}} = 1.0 \text{ GHz}$

b) $\lambda/4$ long transmission line moves a capacitive impedance Z_R into an inductive impedance Z_1 . Inductance comes through the phasing of the transmission line.

In-class task

$$G = \frac{1}{50} \text{ S} ; B = \frac{1}{100} \text{ S}$$
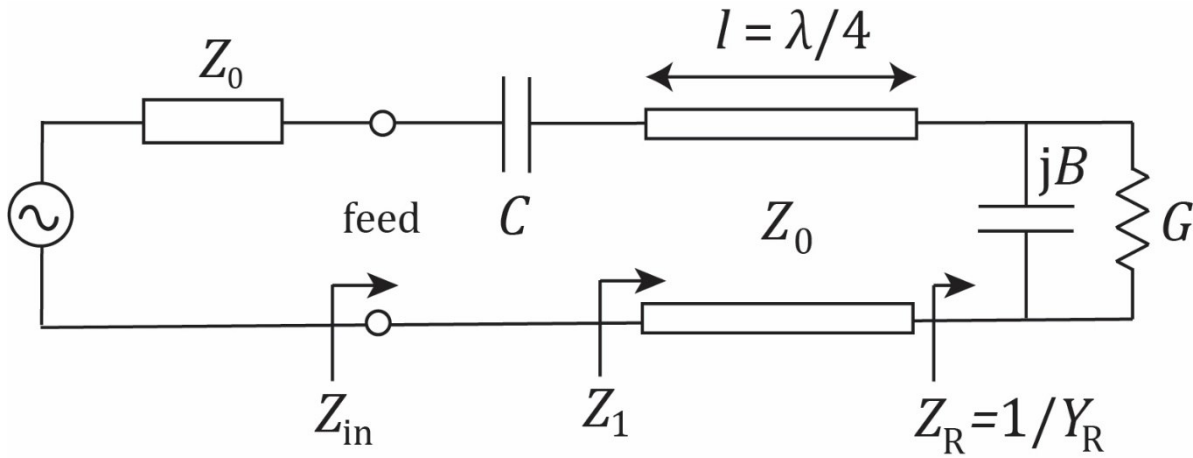
$$C = 6.3 \text{ pF} ; Z_0 = 50 \text{ } \Omega$$







$$Y_R = G + jB ; y_{R0} = \frac{Y_R}{Y_0} = \frac{\frac{1}{50} + j\frac{1}{100} \text{ S}}{\frac{1}{50} \text{ S}} = 1 + j0.5$$

rotate $\lambda/4$ towards the load in position y ,
then rotate another $\lambda/4$ to the impedance scale

$$z_1 = 1 + j0.5 \Rightarrow Z_1 = z_1 Z_0 = 50 + j25 \text{ } \Omega$$
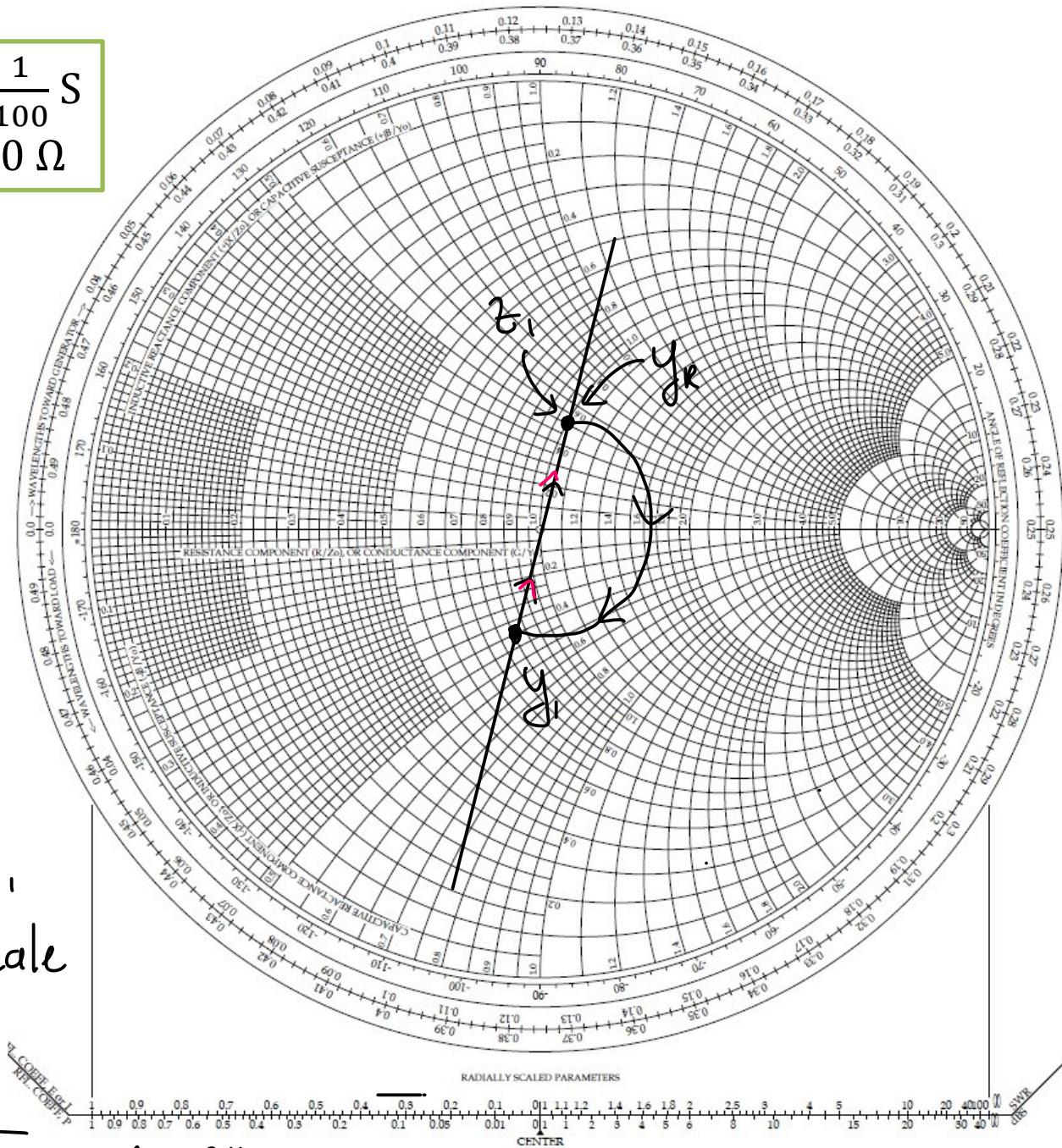
$$\text{Hence } -\frac{1}{\omega C} = -25 \text{ } \Omega \Rightarrow \omega = \frac{1}{(-25 \text{ } \Omega) \cdot 2\pi \cdot 6.3 \cdot 10^{-12} \text{ F}} = 1.0 \text{ GHz}$$



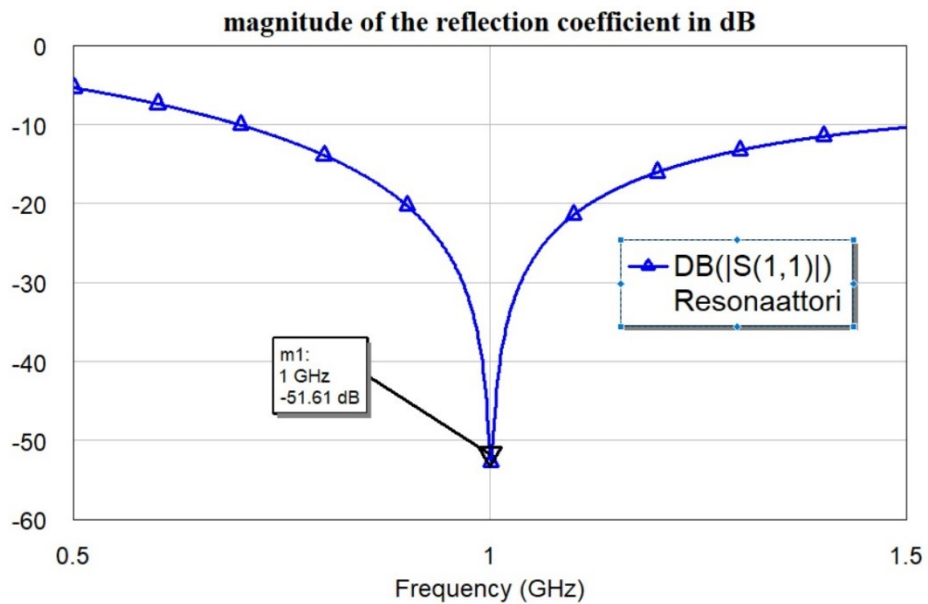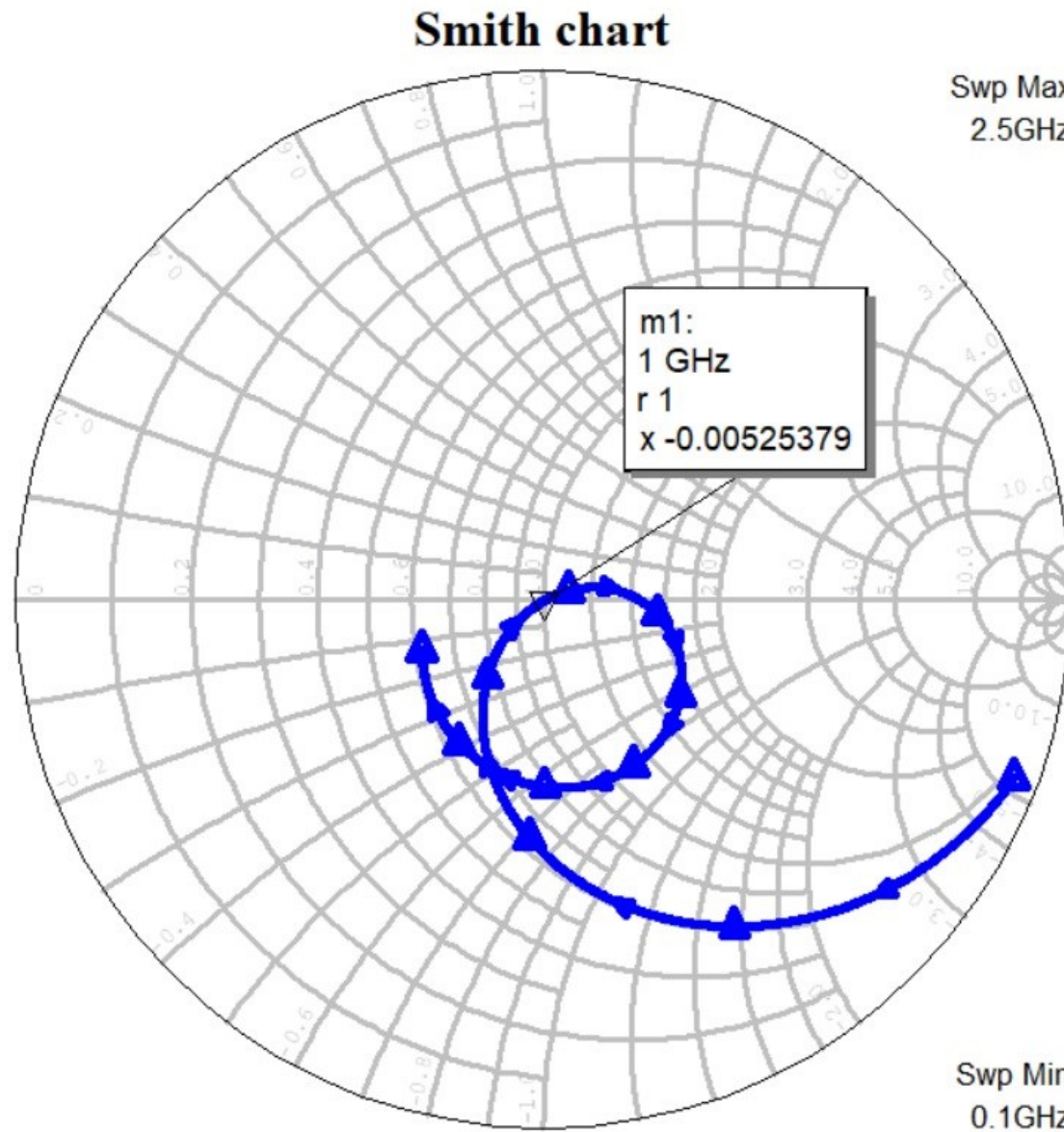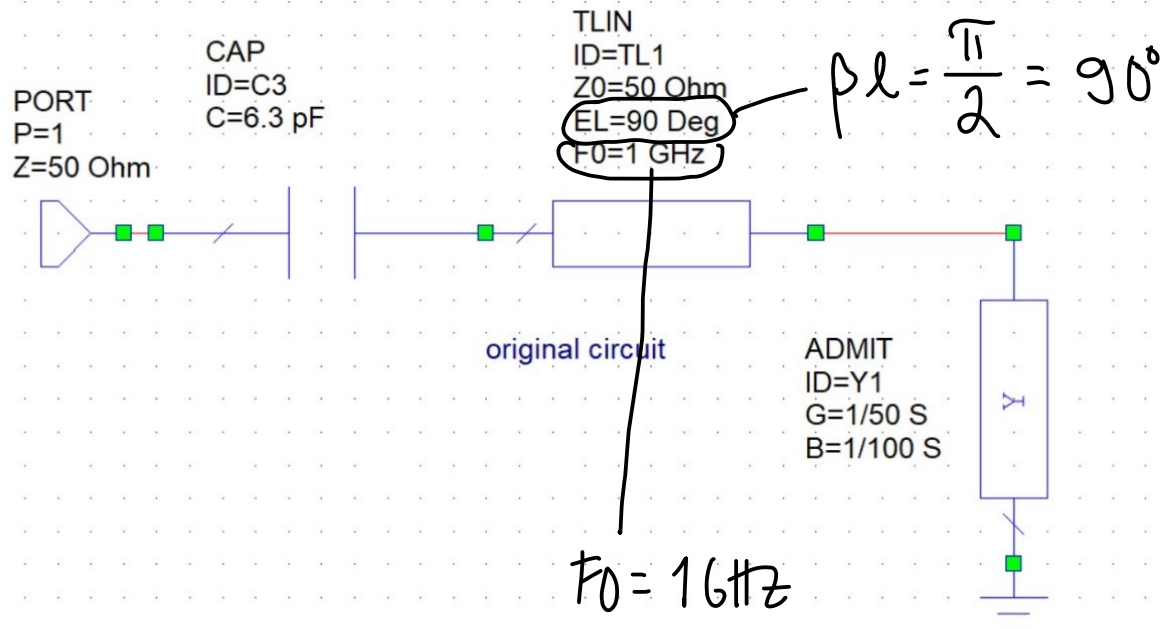


Q1: A 2-port with lumped impedance Z is connected between two transmission lines (with Z_0). What is the input impedance Z_{in} seen in Port 1 to the **right** (towards Port 2)? Assume the transmission lines semi-infinite long


FIRST VOTE

SECOND VOTE

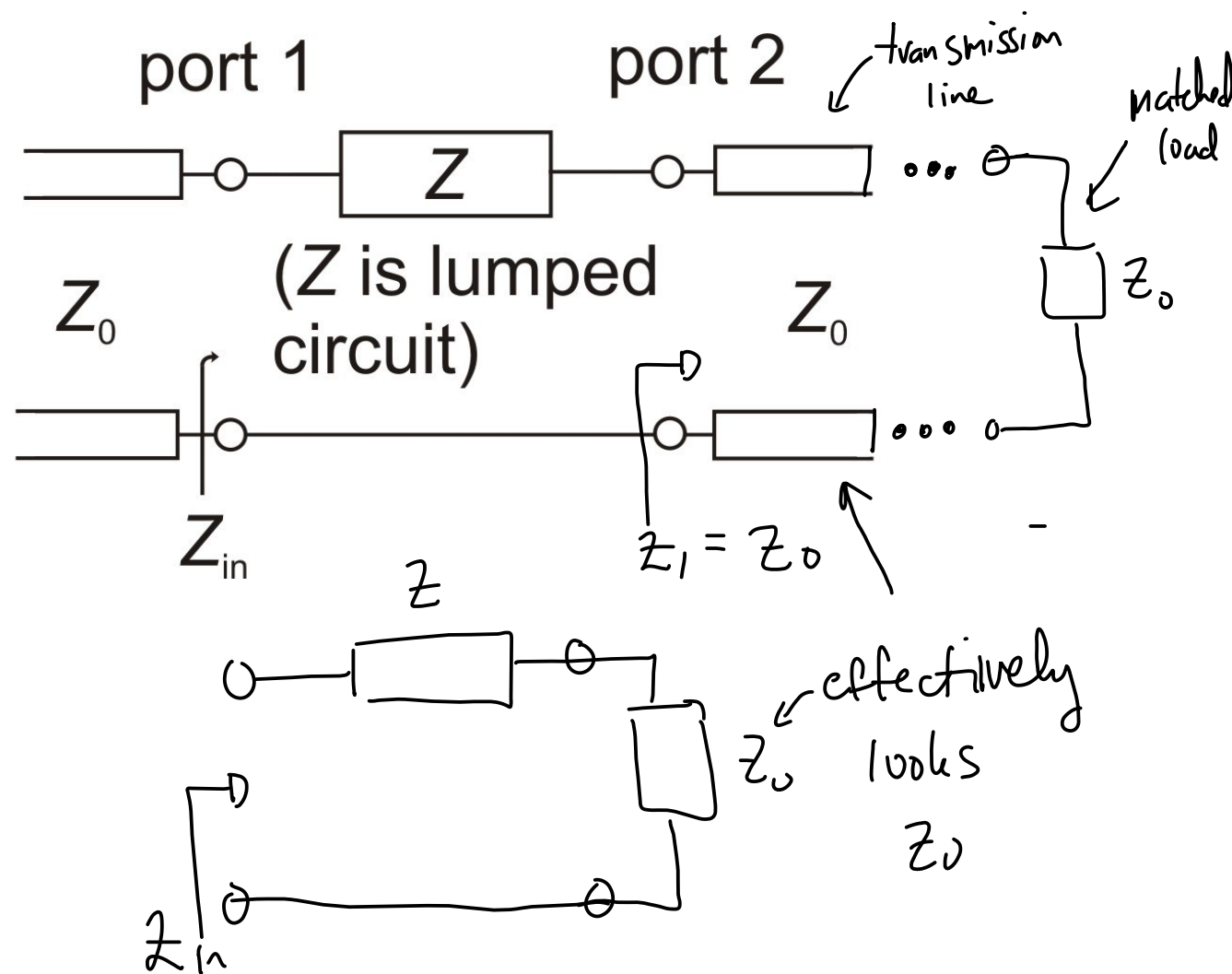- ↓
- 21%. 1. $Z_{in} = Z$ 0%.
- 4%. 2. $Z_{in} = Z_0$ 0%.
- 46% 3. $Z_{in} = Z + Z_0$ 90%. CORRECT ANSWER
- 25%. 4. $Z_{in} = \frac{Z \cdot Z_0}{Z + Z_0}$ 10%.
- 0%. 5. $Z_{in} = \infty$ (open circuit) 0%.
- 4%. 6. I don't know



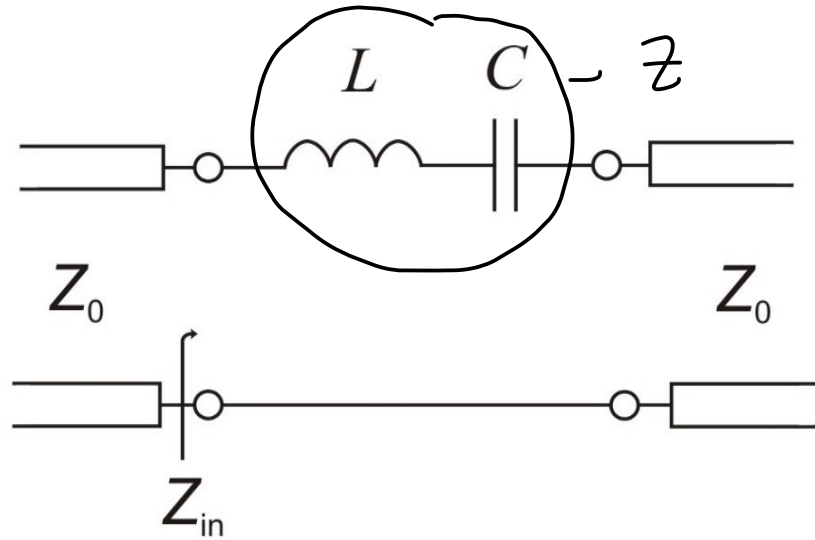
Q2: This LC series circuit topology might work at $\omega_0 = \frac{1}{\sqrt{LC}}$ as ...




$$Z = j\omega L + \frac{1}{j\omega C}$$

$$\text{at } \omega_0 = \frac{1}{\sqrt{LC}} ; \quad Z = 0 ; \quad Z_{in} = Z_0$$

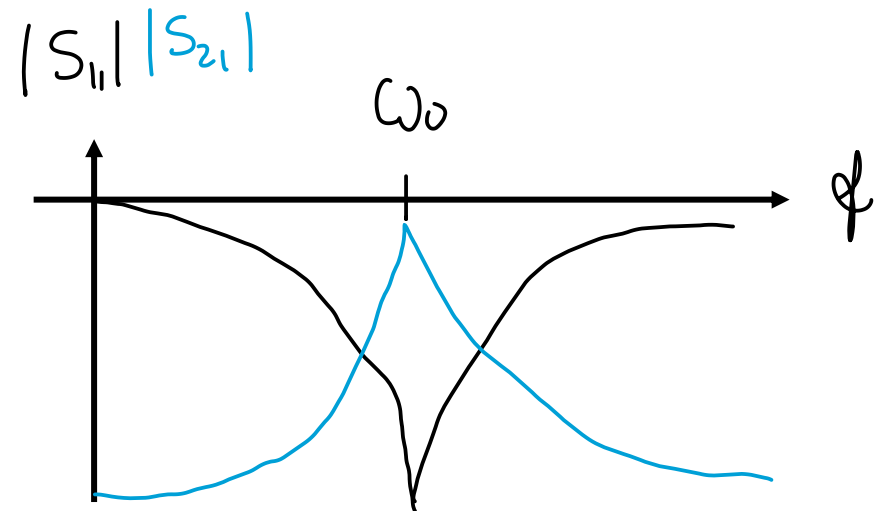
- 0% 1. Low-pass filter below ω_0
- 10% 2. High-pass filter above ω_0
- 69% **3.** Band-pass filter around ω_0
- 17% 4. Band-stop filter around ω_0
- 3% 5. I don't know



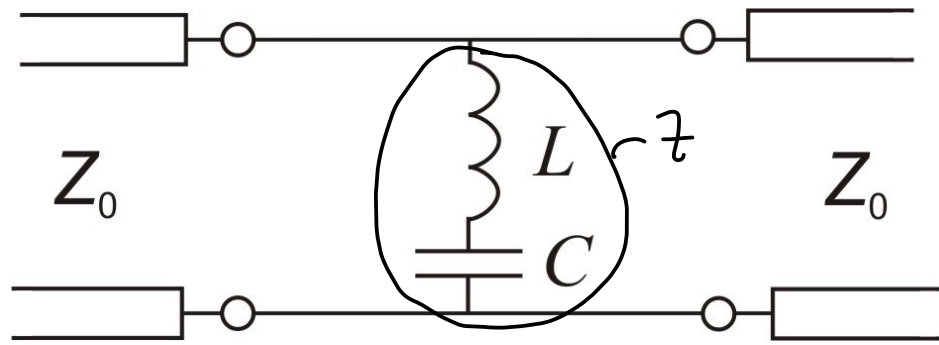
Q3: This LC series circuit topology might work at $\omega_0 = \frac{1}{\sqrt{LC}}$ as ...



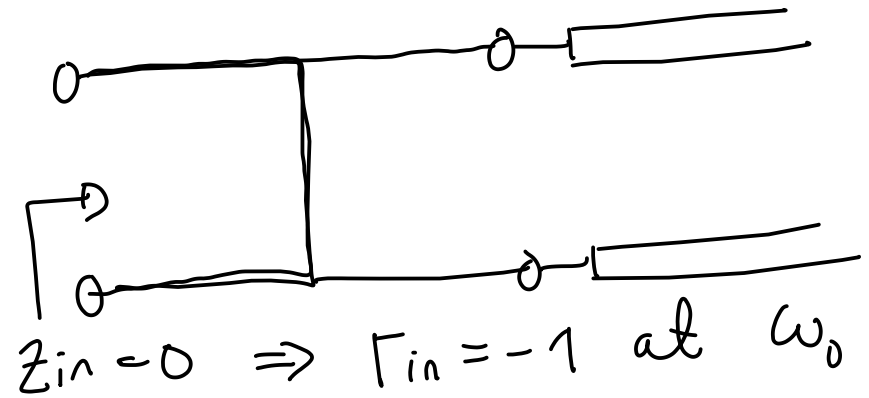
$Z = 0$ at $\omega_0 = \frac{1}{\sqrt{LC}}$



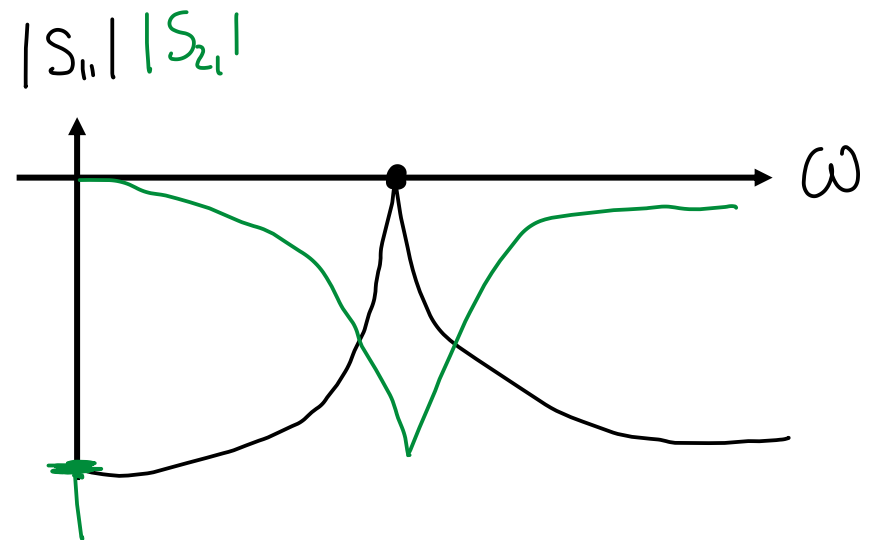- 3% 1. Low-pass filter below ω_0
- 0% 2. High-pass filter above ω_0
- 10% 3. Band-pass filter around ω_0
- 77% **4.** Band-stop filter around ω_0
- 10% 5. I don't know



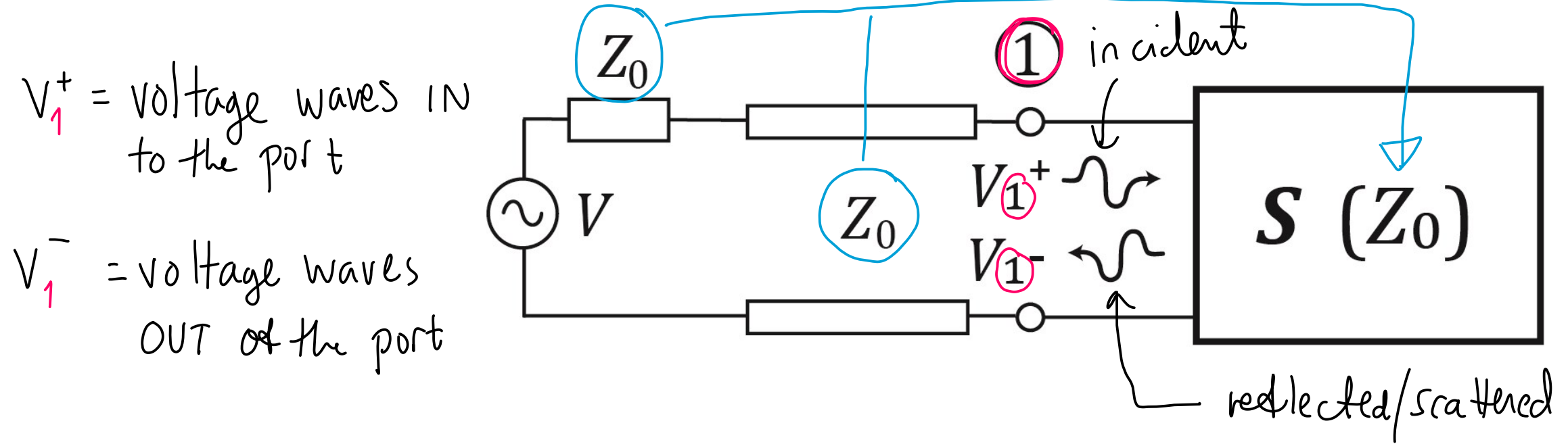The scattering parameters deal with voltage waves that incident (V^+) and scatter (V^-) in the designated ports




$$S_{11} = \frac{\text{scattered (reflected) voltage}}{\text{incident voltage}} = \frac{V_1^-}{V_1^+} = \Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

SINGLE PORT \rightarrow ONE SINGLE VALUE S_{11} (complex number)

S_{11} is traditional reflection Coef.

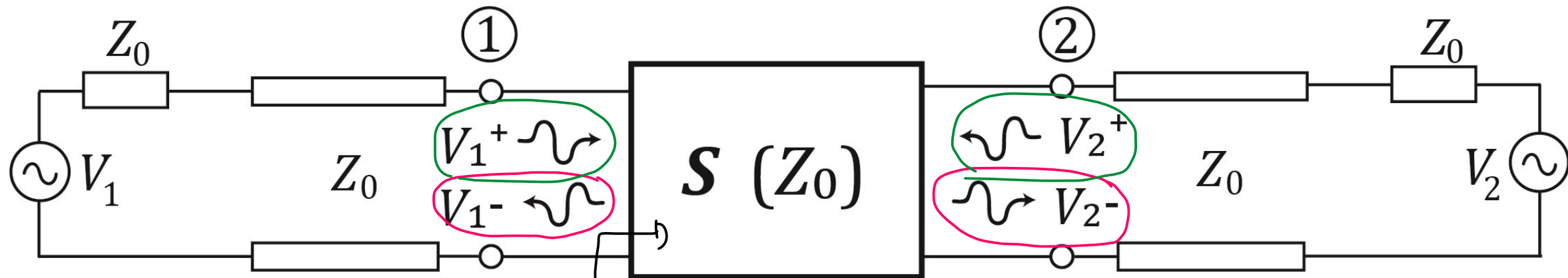The S matrix describes the full relationship between designated ports in terms of voltage waves



$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

↑
voltage
wave
OUT

2 × 2
matrix
2 ports


↑
Voltage
wave
IN

$S_{11} = \Gamma_{in}$

$$\begin{cases} V_1^- = S_{11} \cdot V_1^+ + S_{12} \cdot V_2^+ \\ V_2^- = S_{21} \cdot V_1^+ + S_{22} \cdot V_2^+ \end{cases}$$

S_{nm} ← port n signal IN
↑
port m signal OUT

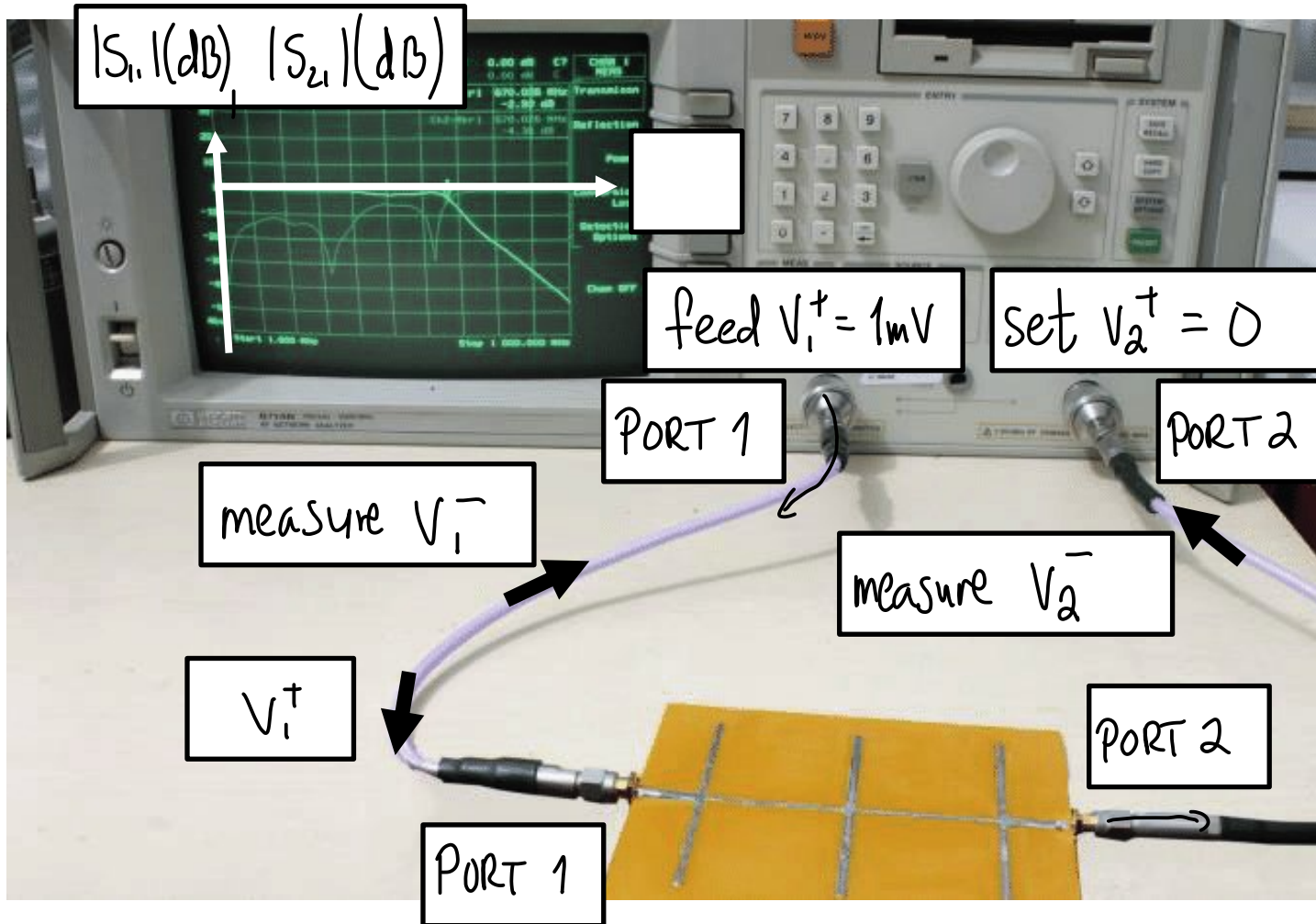The scattering parameters can be measured with vector network analyzer (VNA), simulated with circuit or EM simulator or calculated pen & paper method




$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix} \Big|_{V_2^+ = 0}$$

$$\begin{cases} V_1^- = S_{11} \cdot V_1^+ + 0 \\ V_2^- = S_{21} \cdot V_1^+ + 0 \end{cases}$$

$$\Rightarrow \begin{cases} S_{11} = \frac{V_1^-}{V_1^+} \text{ when } V_2^+ = 0 \\ S_{21} = \frac{V_2^-}{V_1^+} \text{ , when } V_2^+ = 0 \end{cases}$$

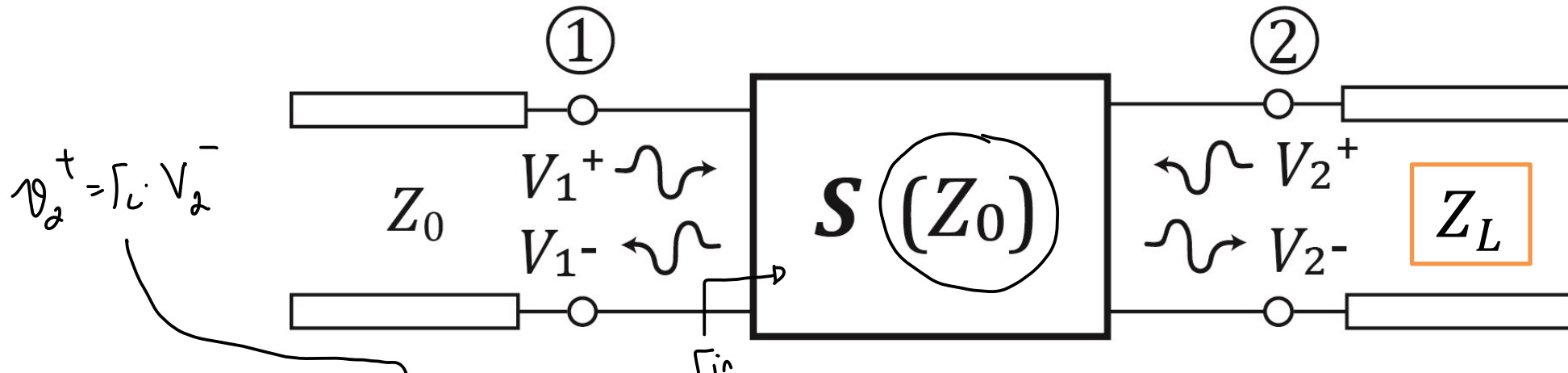If $Z_L \neq Z_0$ in port 2, the input reflection $\Gamma_{in} \neq S_{11}$



$$V_2^+ = \Gamma_L V_2^-$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\begin{cases} V_1^- = S_{11} V_1^+ + S_{12} V_2^+ \\ V_2^- = S_{21} V_1^+ + S_{22} V_2^+ \end{cases} \Leftrightarrow$$


$$\begin{cases} V_1^- = S_{11} V_1^+ + S_{12} \Gamma_L V_2^- \\ V_2^- = S_{21} V_1^+ + S_{22} \Gamma_L V_2^- \end{cases}$$

refl. volt.
indep. volt.
 $\Gamma_L = \frac{V_2^+}{V_2^-}$

$$\Rightarrow V_2^- (1 - S_{22} \Gamma_L) = S_{21} V_1^+ \Rightarrow V_2^- = \frac{S_{21}}{1 - S_{22} \Gamma_L} V_1^+$$

$$V_1^- = S_{11} V_1^+ + \frac{S_{12} \Gamma_L S_{21}}{1 - S_{22} \Gamma_L} V_1^+ \Rightarrow \frac{V_1^-}{V_1^+} = \Gamma_{in} = S_{11} + \frac{S_{12} \Gamma_L S_{21}}{1 - S_{22} \Gamma_L} \neq S_{11}$$

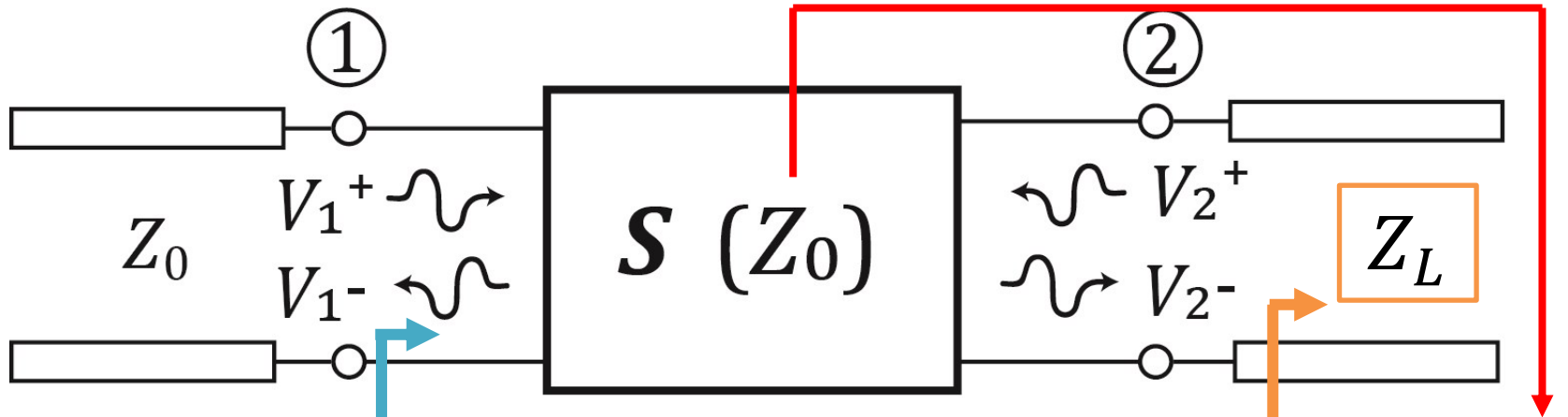If $Z_L \neq Z_0$ in port 2, the input reflection $\Gamma_{in} \neq S_{11}$




$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}\Gamma_L S_{21}}{1 - S_{22}\Gamma_L}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

reflection caused by the **circuit itself** seen in port 1

infinite number of reflections between the **circuit** and the **load Z_L** (a form of a convergent geometric series)

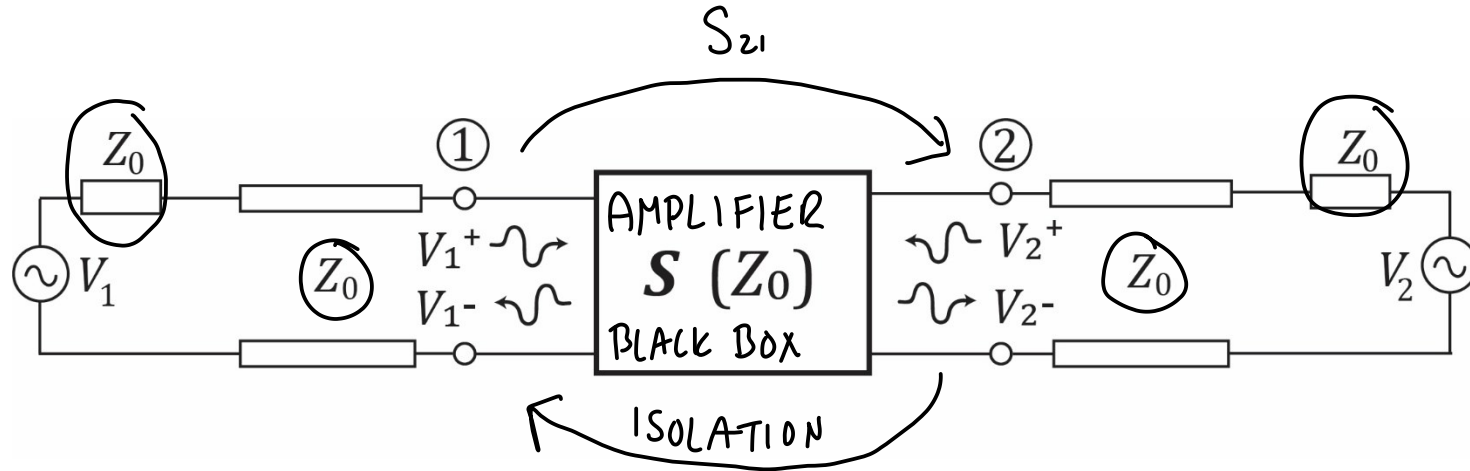The scattering matrix of active components is non-reciprocal and non-symmetric



E.g., a transistor amplifier at f :

$$S = \begin{bmatrix} 0.10 \angle -137^\circ & 0.010 \angle 27^\circ \\ 4.0 \angle -36,18^\circ & 0.10 \angle -88^\circ \end{bmatrix}$$


Matching: $|S_{11}| = |S_{22}| = 0.10 = 10 \log_{10} |S_{11}|^2 = 20 \log 0.10 = 20 \log 10^{-1} = \underline{\underline{-20 \text{ dB}}}$

Power gain (1 \rightarrow 2): $G_{21} = \frac{\frac{|V_2^-|^2}{2Z_0}}{\frac{|V_1^+|^2}{2Z_0}} = \left| \frac{V_2^-}{V_1^+} \right|^2 = |S_{21}|^2 = 10 \log |S_{21}|^2 = \underline{\underline{12 \text{ dB}}}$

Isolation (2 \rightarrow 1): $I_{12} = -10 \log |S_{12}|^2 = -20 \log 10^{-2} = \underline{\underline{+40 \text{ dB}}}$

Q4: Which of the alternatives is/are **false** concerning the two-port in the figure? (select one or more)

- 24%. 1. When inductors are ideal, the circuit is lossless, and the S matrix satisfies $[S]^H[S] = [I]$ TRUE
- 34%. 2. The circuit is **not** perfectly matched; $S_{11} \neq 0$ and $S_{22} \neq 0$ TRUE
- 48%. 3. The circuit is symmetric - i.e., it "looks" the same from each of its ports: $S_{11} = S_{22}$ FALSE
- 34%. 4. The circuit is reciprocal; the S matrix is symmetric $[S] = [S]^T$ TRUE $S_{21} = S_{12}$
- 31%. 5. Power **into** port i given by $P_i^+ = \frac{|V_i^+|^2}{2Z_0}$
- 31%. 6. Power **out** from port i is given by $P_i^- = \frac{|V_i^-|^2}{2Z_0}$ TRUE
- 10%. 7. I don't know
 + = signal IN
 - = signal OUT

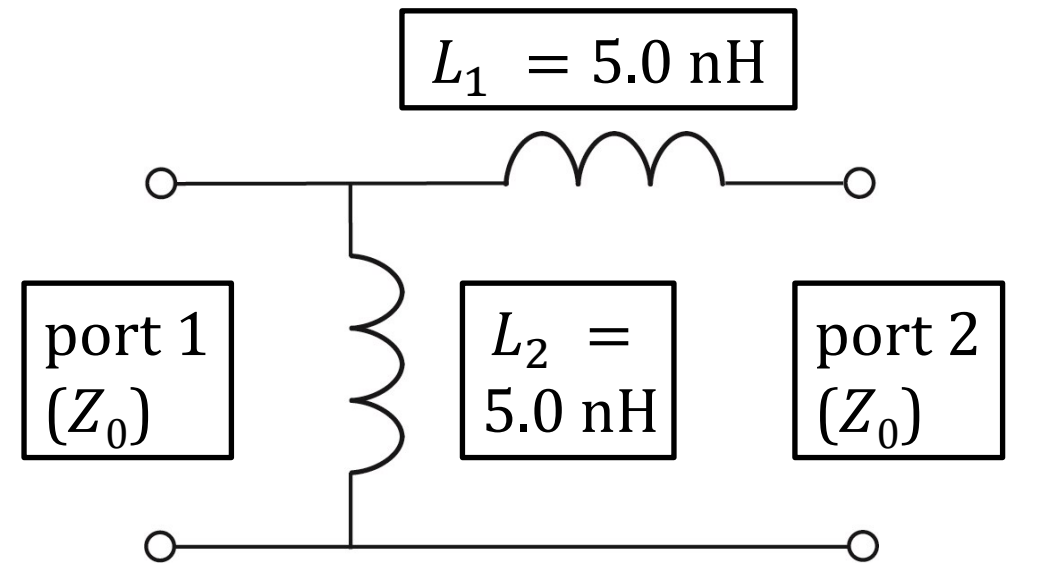

$$P_i^+ = \frac{|V_i^+|^2}{2Z_0}$$

$$P_i^- = \frac{|V_i^-|^2}{2Z_0}$$

$$Z_0 = 50 \Omega$$

$$\begin{bmatrix} V_1^- \\ V_2^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \end{bmatrix}$$

PORT
P=1
Z=50 Ohm


IND
ID=L1
L=5 nH




PORT
P=2
Z=50 Ohm

IND
ID=L2
L=5 nH

Cartesian absolute values

$|S_{11}| = |S_{22}|$??? → SEE NEXT PAGE

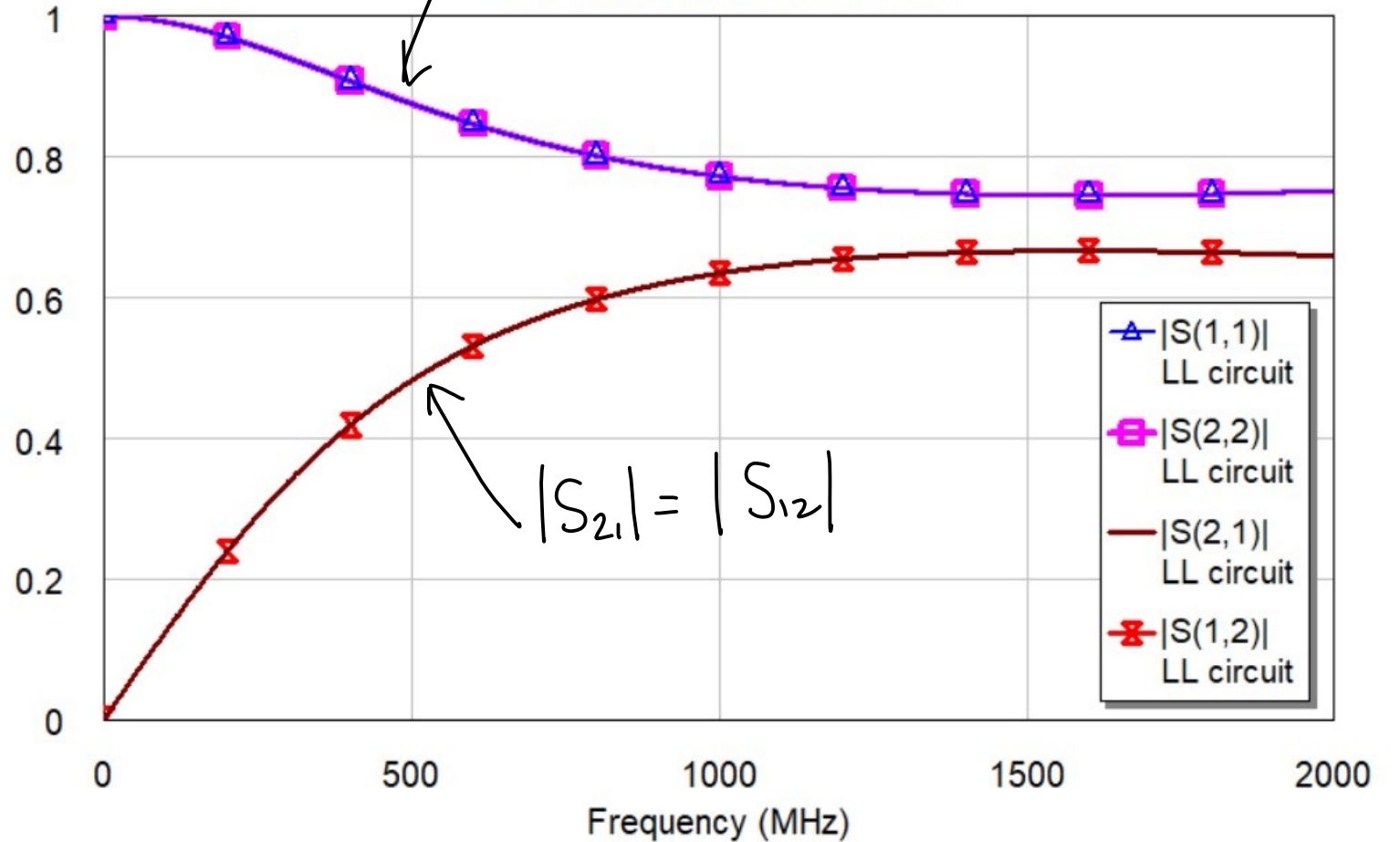

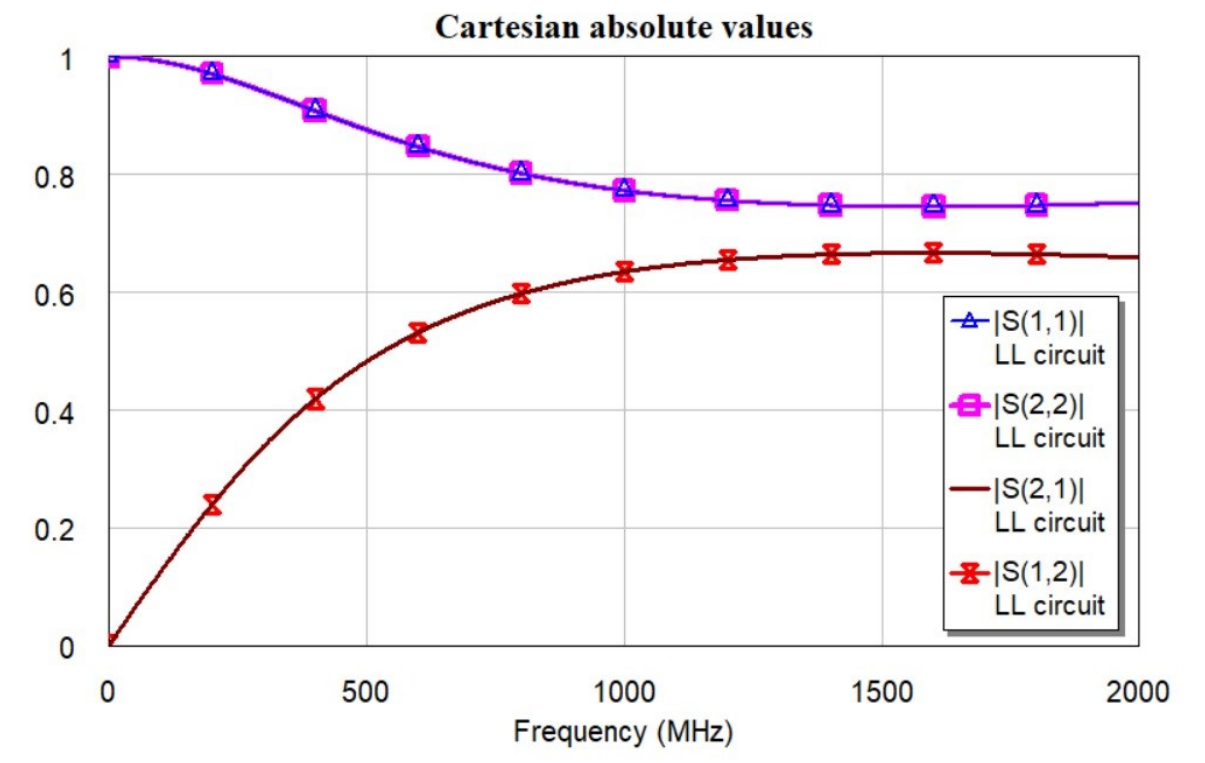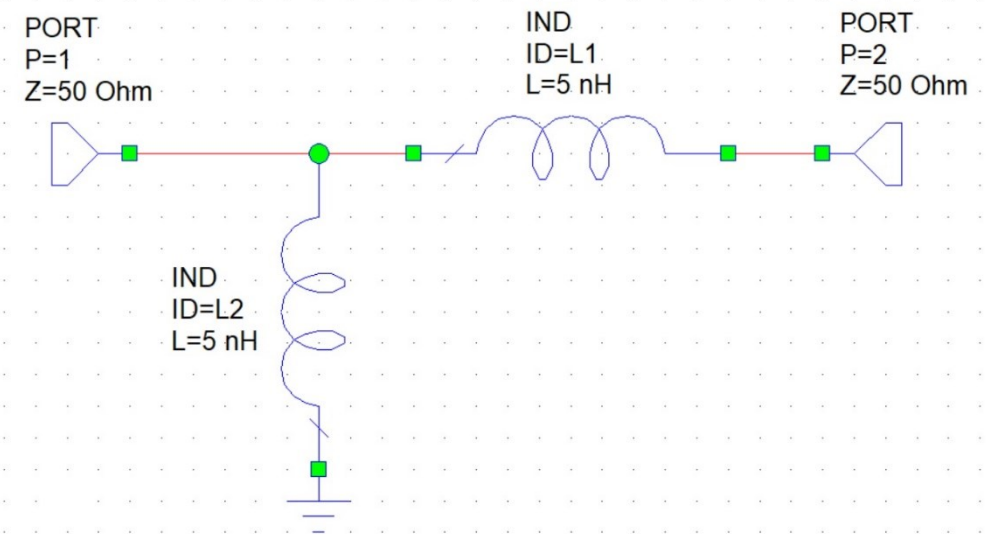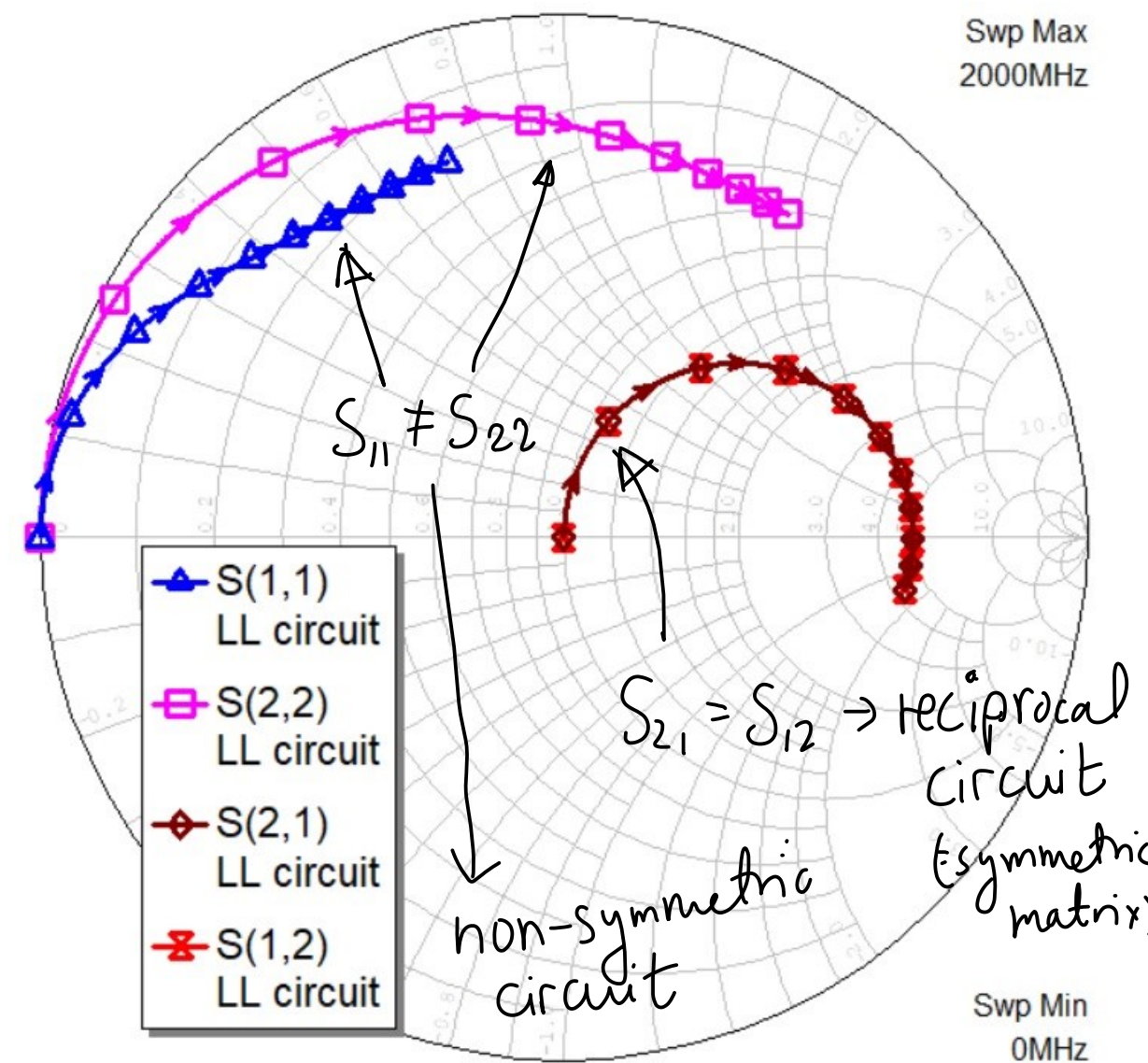

In-class task: combine pairs!

Consider all circuits consist of ideal components and lines!




- I. Does any of the circuits (1.-3.) have **resistive losses**? If yes, which? Which (a.-d.) is the corresponding S matrix?
 - II. Is any of the circuits (1.-3.) **non-symmetric**? If yes, which? Which (a.-d.) is the corresponding S matrix?
 - III. Is any of the circuits (1.-3.) **non-reciprocal**? If yes, which? Which (a.-d.) is the corresponding S matrix?
 - IV. Is any of the circuits (1.-3.) **lossless and symmetric**? If yes, which? Which (a.-d.) is the corresponding S matrix?
- Extra: is any circuit simultaneously **lossless, matched and reciprocal**?

a.
$$S_a = \begin{bmatrix} 0 & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & -\frac{1}{2} & \frac{1}{2} \\ \frac{1}{\sqrt{2}} & \frac{1}{2} & -\frac{1}{2} \end{bmatrix}$$

b.
$$S_b = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

c.
$$S_c = \frac{1}{3} \begin{bmatrix} -1 & 2 & 2 \\ 2 & -1 & 2 \\ 2 & 2 & -1 \end{bmatrix}$$

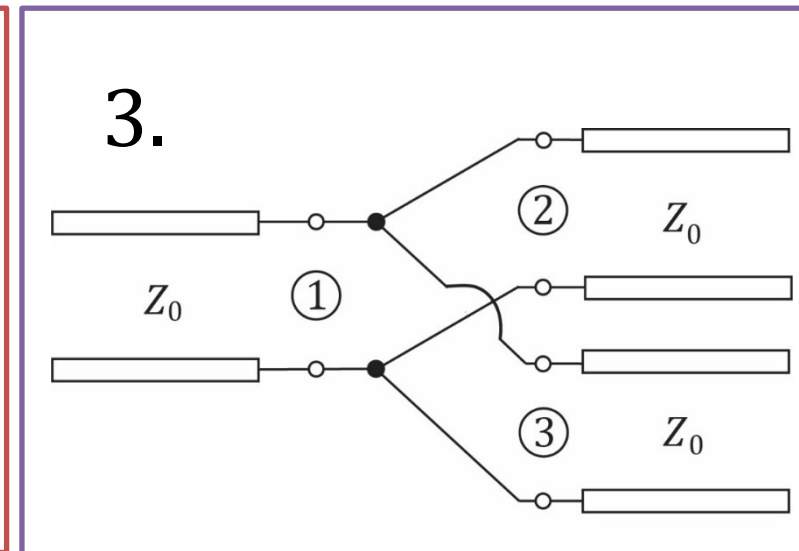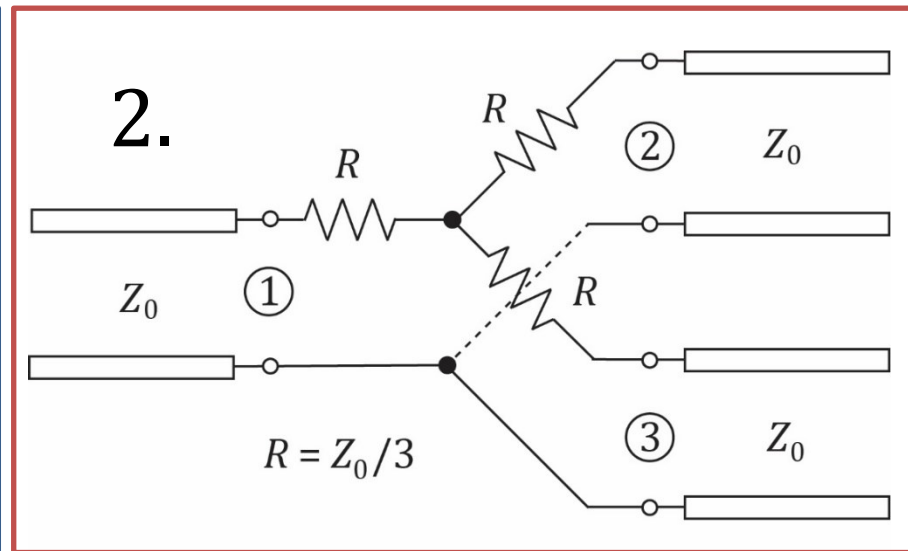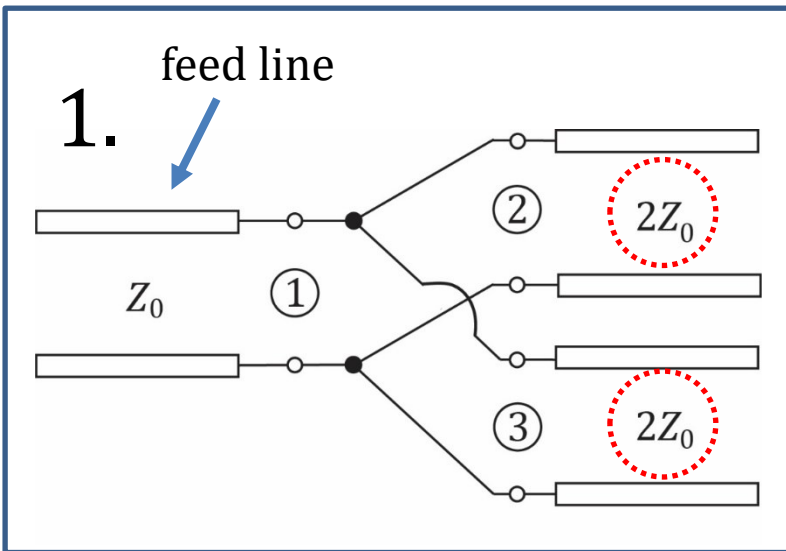d.
$$S_d = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$



In-class task: combine pairs!

Consider all circuits consist of ideal components and lines!

- I. **resistive losses?** Circuit 2. contains resistors – i.e., is lossy. So is matrix d: $|S_{1i}|^2 + |S_{2i}|^2 + |S_{3i}|^2 = \frac{1}{2} \neq 1$
 - II. **non-symmetric?** Circuit 1. is non symmetric. So is matrix a: $S_{11} \neq S_{22}$. (The circuit is lossless and so is its S matrix.)
 - III. **non-reciprocal?** All circuits contain only passive, non-isotropic components → none of the circuits are non-reciprocal. Matrix b. is non-reciprocal.
 - IV. **lossless and symmetric?** Circuit 3. is lossless and symmetric. Its matrix is c.
- Extra: **lossless, matched and reciprocal?** There is no three-port which is lossless, matched and reciprocal. See Pozar C. 7.1.


a.
$$S_a = \begin{bmatrix} 0 & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & -\frac{1}{2} & \frac{1}{2} \\ \frac{1}{\sqrt{2}} & \frac{1}{2} & -\frac{1}{2} \end{bmatrix}$$

b.
$$S_b = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$


c.
$$S_c = \frac{1}{3} \begin{bmatrix} -1 & 2 & 2 \\ 2 & -1 & 2 \\ 2 & 2 & -1 \end{bmatrix}$$

d.
$$S_d = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$

1.

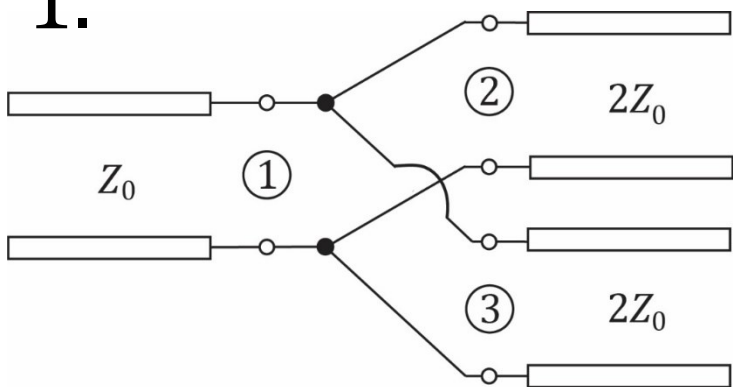

2.

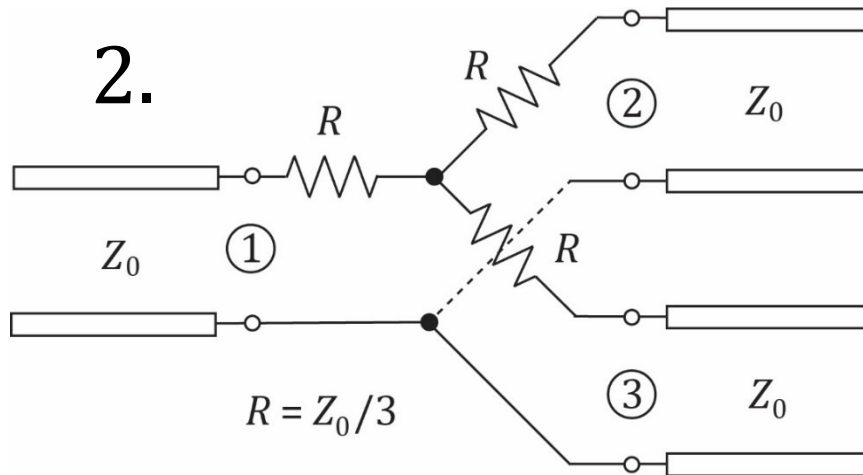

3.

