
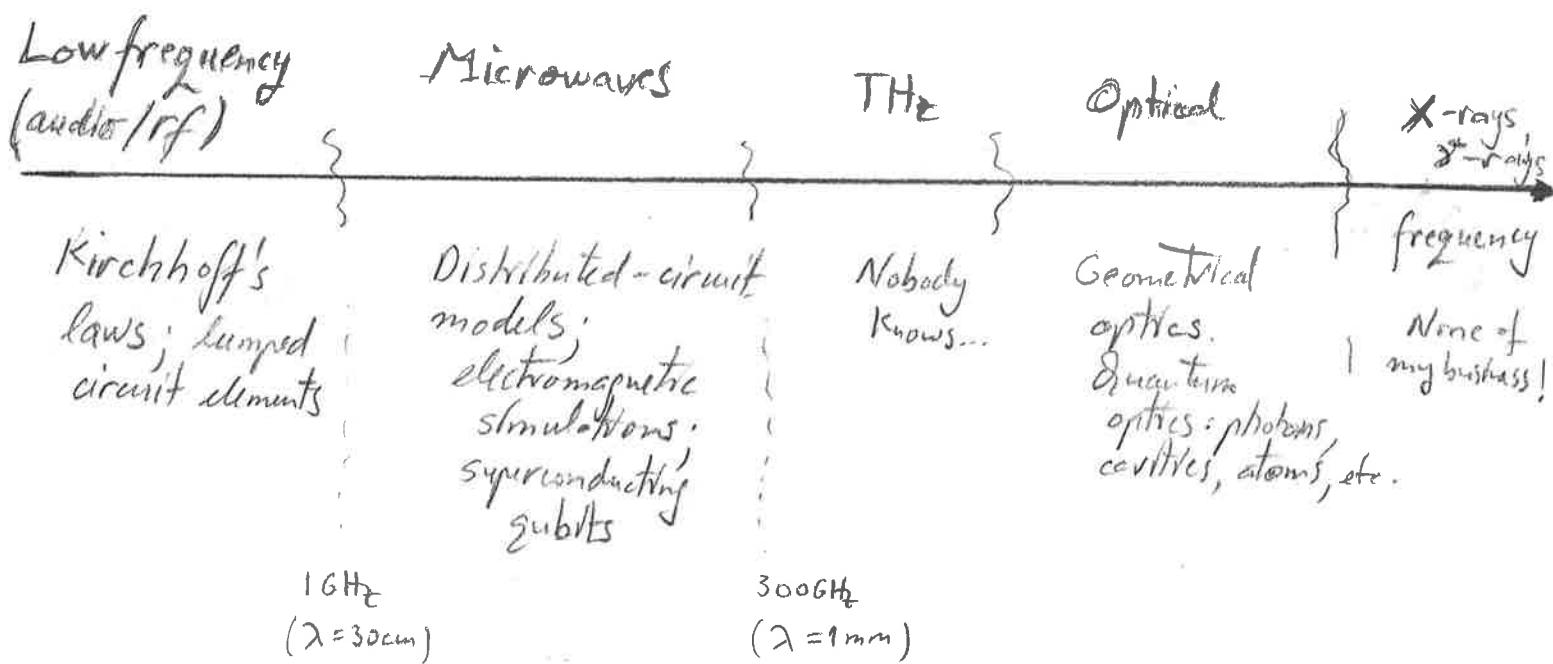


Circuit elements

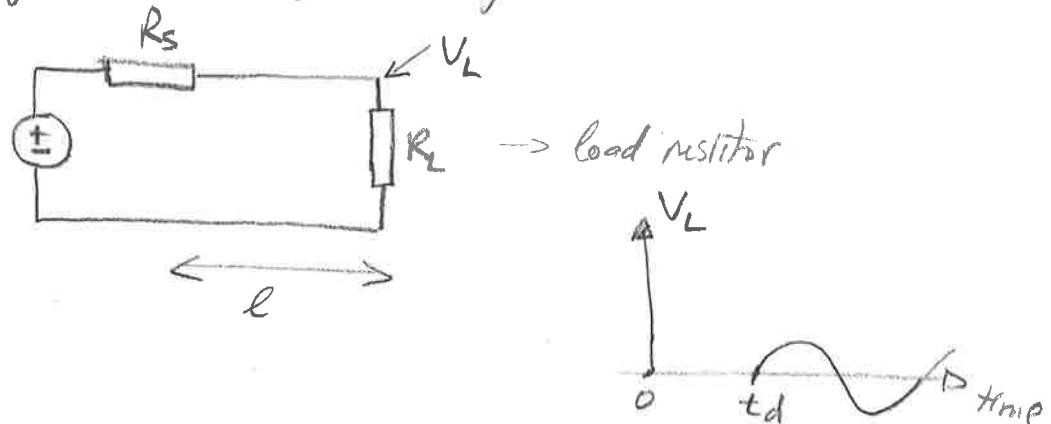- The electromagnetic spectrum as seen by a quantum engineer:



- Why lumped-circuit models don't work at high frequencies?
The speed of light c is large but finite.




$$t_d = \frac{l}{c} = \text{delay time}$$

becomes non-negligible if
 $\lambda \sim l \sim \text{cm}$
frequency $\sim 6 \text{ Hz}$

Some basic concepts - electrical circuits

- electric current

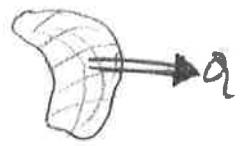
$$I = \frac{dQ}{dt} \quad Q = \int_0^t I dt$$



by convention, the direction of the current is the direction of motion of positive charges.


- work done by an electric field
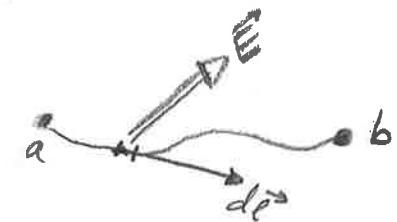
$$W_{ba} = q \int_a^b \vec{E} \cdot d\vec{l}$$



- voltage

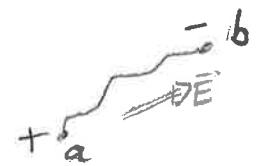
$$V = V_{ba} = V_b - V_a = - \frac{dW_{ba}}{dq} = - \int_a^b \vec{E} \cdot d\vec{l}$$



W_{ba} = work done to transport

the charge q against the field, $W = -W_{ba}$

E.g. capacitor:

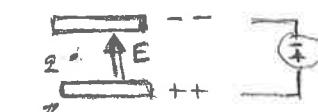

$=$ work done by the field

plate with higher electrical potential

- magnetic flux

$$\text{Node flux: } \phi(t) = \int_{-\infty}^t d\sigma V(\sigma)$$

$$\text{so } V(t) = \frac{d\phi(t)}{dt}$$

- power

$$W(t) = \int_0^t P(\tau) d\tau$$

$$P(t) = \frac{dW(t)}{dt} = \frac{dW(t)}{dq(t)} \cdot \frac{dq(t)}{dt} = V(t) \cdot I(t)$$

$$\text{so } W(t) = \int_0^t V(\tau) \cdot I(\tau) d\tau$$

- phasors

useful concept if:
 - the circuit is linear
 - all independent sources are sinusoidal
 - only steady-state response is desired

$$X(t) = A \cos(\omega t + \phi) = \operatorname{Re}(A e^{i\phi} e^{i\omega t})$$

$X = Ae^{i\phi}$ = phasor = transformation of a sine waveform from time-domain into frequency domain.

Why it is useful? Simple rules:

| variable | phasor |
|--------------------|-------------------------------|
| $X(t)$ | $A e^{i\phi}$ |
| $\frac{dx(t)}{dt}$ | $i\omega \cdot A e^{i\phi}$ |
| $\int dt X(t)$ | $\frac{A e^{i\phi}}{i\omega}$ |

check them based on the definition

• Impedance and admittance

$$Z = \frac{V}{I} \quad \text{with } V \text{ and } I \text{ phasors}$$

$$Z = R + iX \quad \begin{aligned} Z &= \text{Impedance} \\ R &= \text{resistance} \\ X &= \text{reactance} \end{aligned} \quad \text{units: } \Omega \quad (\text{Ohm})$$

$$Y = \frac{1}{Z} = G + iB \quad \begin{aligned} Y &= \text{admittance} \\ G &= \text{conductance} \\ B &= \text{susceptance} \end{aligned} \quad \text{units: } S \quad (\text{Siemens})$$

• ac power and decibels

Suppose $V(t) = V_0 \cos(\omega t + \varphi_V) = \operatorname{Re}[V_0 e^{i\varphi_V} e^{i\omega t}]$. phasor $V_0 e^{i\varphi_V} = V$
 $I(t) = I_0 \cos(\omega t + \varphi_I) = \operatorname{Re}[I_0 e^{i\varphi_I} e^{i\omega t}]$. phasor $I_0 e^{i\varphi_I} = I$

$$\Rightarrow P(t) = V(t) \cdot I(t) = \frac{1}{2} I_0 V_0 \cos(\varphi_V - \varphi_I) + \frac{1}{2} I_0 V_0 \cos[2\omega t + \varphi_V + \varphi_I]$$

↑
instantaneous power

Average power:

$$\bar{P} = \frac{1}{T} \int_0^T P(t) dt = \frac{1}{2} I_0 V_0 \cos(\varphi_V - \varphi_I)$$

↑
average power delivered to a load can be changed by changing the phases!

$$\bar{P} = \frac{1}{2} \operatorname{Re}[V \cdot I^*]$$

This term oscillates and cancels out when averaging

Root-mean square of a periodic signal

$$I(t) = I_0 \cos \omega t \rightarrow I_{\text{rms}}^2 = \frac{1}{T} \int_0^T I^2(t) dt = \frac{I_0^2}{2}$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

$$\downarrow \text{use } \cos^2 \omega t = \frac{1 + \cos 2\omega t}{2}$$

decibel:

$$N(\text{dB}) = 10 \log_{10} \frac{P}{P_{\text{reference}}} \quad \downarrow \\ \text{power in} \\ \text{decibels}$$

P = power
 $P_{\text{reference}}$ = a reference power,
usually 1mW

$$\text{If } P_{\text{reference}} = 1 \text{ mW}, \text{ then } N(\text{dBm}) = 10 \log_{10} \frac{P}{1 \text{ mW}} \quad \downarrow \\ \text{units are "dBm".}$$

Since $P \propto V^2$, we

have $20 \log_{10} \frac{V}{V_{\text{reference}}}$ (in dBV) as another way
to express this.

Examples:

30dB is an increase in power by 1000

20dB $\underline{\hspace{1cm}} \times \underline{\hspace{1cm}} = \underline{\hspace{1cm}} 100$

10dB $\underline{\hspace{1cm}} \times \underline{\hspace{1cm}} = \underline{\hspace{1cm}} 10$

3dB $\underline{\hspace{1cm}} \times \underline{\hspace{1cm}} = \underline{\hspace{1cm}} 2$

0dB $\underline{\hspace{1cm}} \times \underline{\hspace{1cm}} = \underline{\hspace{1cm}} 1$

-3dB is a decrease in power by 2

-10dB $\underline{\hspace{1cm}} \times \underline{\hspace{1cm}} = \underline{\hspace{1cm}} \text{by 10}$


etc.

Circuit elements

Note: an rf-circuit can be constructed from discrete (lumped) elements if the size of each component \ll wavelength of the rf field

RESISTOR

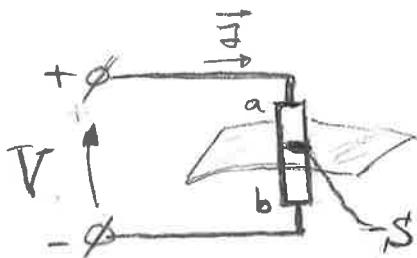Typically a film of conductive material evaporated on a chip.



$$V = V_a - V_b = - \int_b^a \vec{E} \cdot d\vec{l} = \int_a^b \frac{\sigma}{S} \vec{J} \cdot d\vec{l}$$

$\vec{J} = \sigma \cdot \vec{E}$ Ohm's law
 σ = conductivity

If the frequency is not too high,

then \vec{J} = uniform over the cross-section S of the resistor

$$\vec{J} = I/S$$

$$\text{So } V = I \int_a^b \frac{1}{S} dl = IR$$

$$R = \frac{1}{S} \int_a^b dl$$

$$\Rightarrow R = \rho \frac{l}{S}$$

and

$$V = IR$$

$$\rho = \frac{l}{S} = \text{resistivity}$$

$\int_a^b dl = l$ = length of resistor

$$G = \frac{1}{R} = \text{conductance}$$

$$Z(\omega) = R$$

R = resistance

- real
and
frequency
independent


• Instantaneous dissipated power

$$P(t) = V(t) \cdot I(t) = R \cdot I^2(t) = G \cdot V^2(t)$$

• Average dissipated power (for harmonic excitations), $V(t) = V_0 \cos(\omega t)$

$$\bar{P} = \frac{1}{2} R |I_0|^2 = \frac{1}{2} G |V_0|^2$$

INDUCTOR

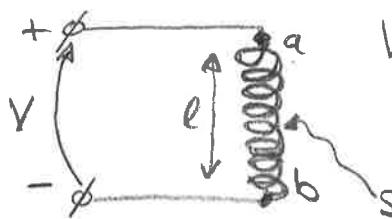

$$V = V_{ab} = V_a - V_b = - \int_b^a \vec{E} d\vec{l} = \iint_S \frac{d\vec{B}(t)}{dt} d\vec{s} = L \frac{dI}{dt}$$

Maxwell-Faraday equation

$$\nabla \times \vec{E} = - \frac{\partial \vec{B}}{\partial t}$$

+ Stokes theorem

Here we assumed \vec{B} uniform over the surface of area S .

$$B = \frac{\mu_0 \mu_r N I}{l} \rightarrow \text{and there are } N \text{ surfaces of area } S$$

$N = \text{no. of turns of the solenoid}$

$\mu_0 = \text{free-space magnetic permeability}$

$$L = \frac{\mu_0 \mu_r N^2 S}{l}$$

$\mu_r = \text{relative permeability}$

- Instantaneous energy stored

$$W_L(t) = \frac{1}{2} L I^2(t)$$

- Average energy stored in ac-harmonic fields

$$\bar{W}_L = \frac{1}{4} L I_0^2$$

So

$$V = L \frac{dI}{dt}$$

therefore

$$Z_L(\omega) = iL\omega$$

because $Z_L(\omega) = \frac{V(\omega)}{I(\omega)}$

Note: The flux variable $\phi = \iint \vec{B} d\vec{s}$ can be used to define a flux at a node with potential V ,


$$\int_{-\infty}^t V(z) dz = \phi(t) \quad \text{since}$$

$$V(t) = \frac{d\phi(t)}{dt}$$

We also have

$$I(t) = \frac{\phi(t)}{L}$$

CAPACITOR

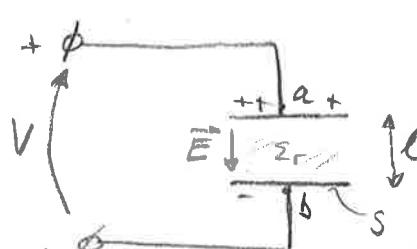

$$V = - \int_b^a \vec{E} d\vec{l} = \frac{Q}{C}$$

$C = \text{capacitance}$

$$C = \frac{\epsilon_0 \epsilon_r S}{l}$$

$$\text{Proof: } E = \frac{Q}{S \epsilon_0 \epsilon_r} = \frac{V}{l} \Rightarrow V = \frac{Q}{\epsilon_0 \epsilon_r S}$$

$\epsilon_0 = \text{free-space electric permittivity}$

$\epsilon_r = \text{relative permittivity}$

$$\text{Also } I(t) = \frac{dQ(t)}{dt} \Rightarrow I(t) = C \cdot \frac{dV(t)}{dt}$$

- Instantaneous energy stored

$$W_c(t) = \frac{1}{2} CV^2(t)$$

- Average energy stored for ac-harmonic fields

$$\overline{W}_c = \frac{1}{4} CV_0^2$$

So $I = C \frac{dV}{dt}$

therefore

$$Z_c(\omega) = \frac{1}{i\omega C}$$

again from

$$Z_c(\omega) = \frac{V(\omega)}{I(\omega)}$$
 and using
the properties of phasors.


More complex networks of inductors, capacitors, resistors

= Kirchhoff's voltage and current laws

- Kirchhoff's voltage law: FOR ANY CLOSED LOOP OF A CIRCUIT, THE ALGEBRAIC SUM OF VOLTAGES OF THE INDIVIDUAL BRANCHES IS ZERO

$$\sum V_k = 0$$

How it works:

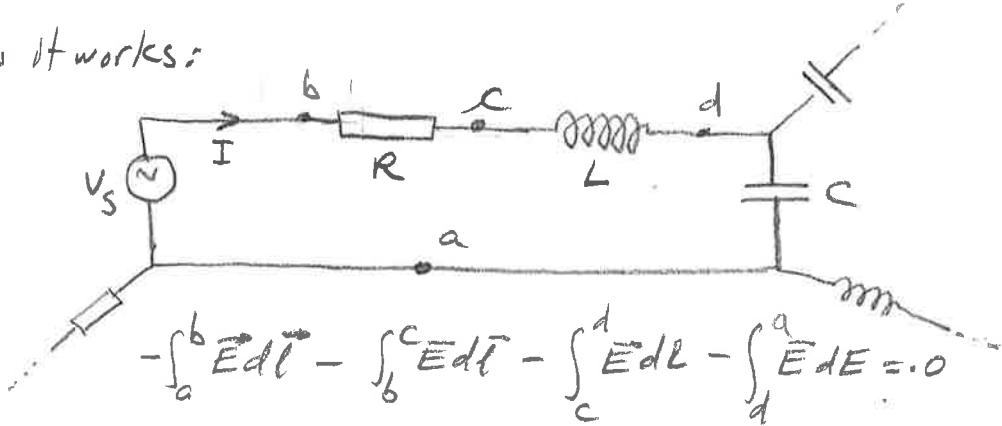


$$\text{or } V_s(t) - R I(t) - L \frac{dI(t)}{dt} - \frac{1}{C} \int_a^t dC I(z) = 0$$


- Kirchhoff's current law: THE ALGEBRAIC SUM OF ALL BRANCH CURRENTS CONFLUENT IN THE SAME NODE IS ZERO

$$\sum I_k = 0$$

How it works:

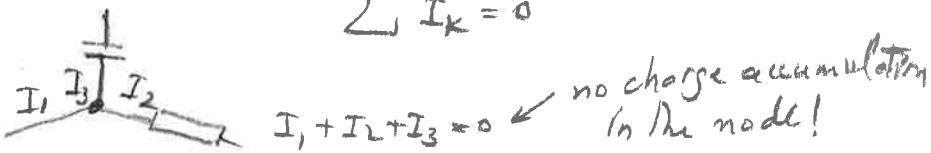

Examples: a series-shunt circuit

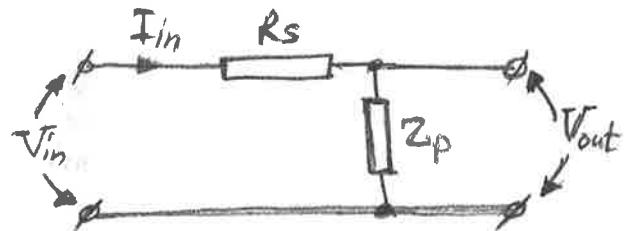

Simple equations for phasors:

$$V_{out} = Z_p I_{in}$$

$$V_{in} = (R_s + Z_p) I_{in}$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{Z_p}{R_s + Z_p} = \text{gain or attenuation}$$

It is convenient to express this in dB:

$$\left| \frac{V_{out}}{V_{in}} \right| (\text{dB}) = 20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right|$$

A few interesting cases:

a)

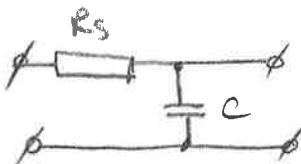

$$Z_p = \frac{1}{i\omega C}$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + i\omega CR_s}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + \omega^2 C^2 R_s^2}}$$

$$\Rightarrow \left| \frac{V_{out}}{V_{in}} \right| (\text{dB}) = -10 \log_{10} [1 + \omega^2 C^2 R_s^2]$$

- works like a low-pass filter with cutoff $\sim 1/R_s C$

b)

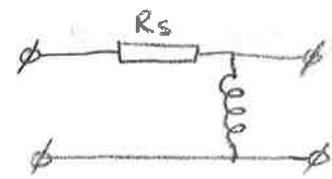

$$Z_p = i\omega L$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{1 - \frac{iR_s}{\omega L}}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (R_s/\omega L)^2}}$$

$$\Rightarrow \left| \frac{V_{out}}{V_{in}} \right| (\text{dB}) = -10 \log_{10} [1 + (R_s/\omega L)^2]$$

- works as a high-pass filter $\omega \gtrsim R_s/L$


c)

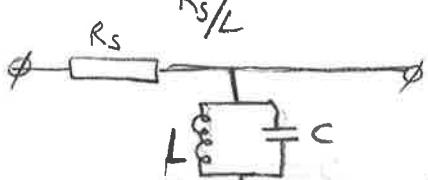

$$Z_p = \frac{i\omega L \cdot \frac{1}{i\omega C}}{i\omega L + \frac{1}{i\omega C}} = \frac{i\omega L}{1 - \omega^2 LC}$$


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{i\omega L}{R_s(1 - \omega^2 LC) + i\omega L}$$

$$\left| \frac{V_{out}}{V_{in}} \right| (\text{dB}) = 20 \log_{10} \frac{\omega L}{\sqrt{R_s(1 - \omega^2 LC)^2 + (\omega L)^2}}$$

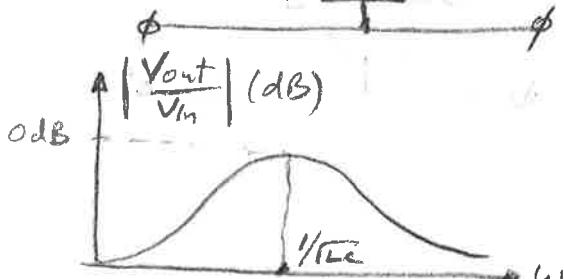

Resonators based on lumped circuit elements

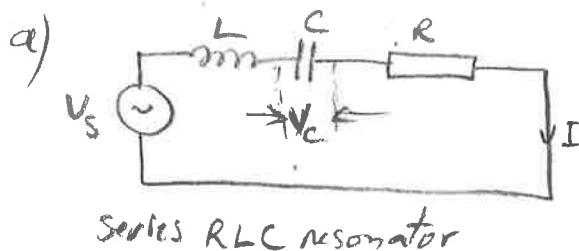R L C components can be used to realize resonators.



$$V_s(\omega) = Z(\omega) \cdot I(\omega)$$

$$Z(\omega) = R + iL\omega + \frac{1}{iC\omega}$$

$$= R + i \frac{L}{\omega} (\omega^2 - \omega_0^2) \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Resonance: $\omega = \omega_0$

$Z(\omega_0) = R \rightarrow$ the impedance is real (resistive)

the reactive part is zero, meaning that the inductor and capacitor reactances cancel each other.

Indeed

$$\begin{cases} \bar{W}_L = \frac{1}{2} L |I|^2 \\ \bar{W}_C = \frac{1}{2} C |V_C|^2 = \frac{1}{2} \frac{|I|^2}{\omega} \end{cases}$$

$$\text{but } |V_C| = \frac{|I|}{\omega}$$

so at resonance

$$\omega = \omega_0 \Rightarrow \bar{W}_L = \bar{W}_C$$

due to

this, the energy oscillates between the capacitor and inductor and the source has to provide only what is lost through R .

• Quality factor - suppose we put some energy $W(0)$ in the resonator.

Due to the resistance R , this will be dissipated.

$$W(t) = W(0) e^{-\frac{\omega_0 t}{Q}}$$

$Q = \text{quality factor}$ - it measures how well the resonator stores energy.

Now

$$-\frac{dW}{dt} = \frac{\omega_0 W}{Q}$$

\bar{P} = average loss in a period

$$\frac{2\pi}{\omega_0} = T = \text{period}$$

$$\bar{P} = \frac{1}{T} \int_0^T -\frac{dW}{dt} dt$$

$$\text{or } \bar{P} = \frac{\omega_0}{Q} \cdot \frac{1}{T} \int_0^T W(t) dt = W_T$$

$$Q = \frac{\omega_0 \bar{W}}{\bar{P}}$$


total energy averaged over a period

But $\left\{ \begin{array}{l} \bar{W} = \bar{W}_C + \bar{W}_L = 2 \cdot \bar{W}_L = \frac{L|I|^2}{2} \\ \bar{P} = R \cdot \frac{|I|^2}{2} \end{array} \right.$

S,

$$Q = \frac{\omega_0 L}{R} = \frac{L}{R} \sqrt{\frac{L}{C}}$$

2 Loading of a resonant circuit -

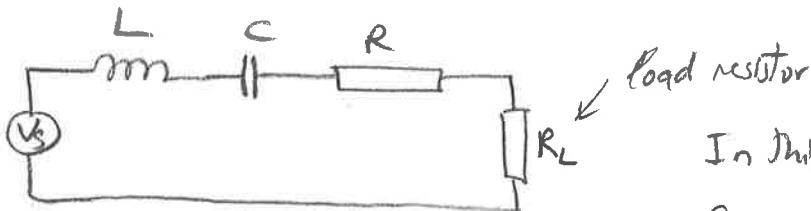

In this case

$$Q_L = \left(\frac{1}{R} + \frac{1}{R_L} \right) \sqrt{\frac{L}{C}} = \text{loaded } Q$$

or $Q_L^{-1} = Q_{ext}^{-1} + Q^{-1}$


simply because now

$$\begin{aligned} Q_L^{-1} &= \frac{\bar{P}}{\omega_0 \bar{W}} = \frac{(R+R_L) \frac{|I|^2}{2}}{\frac{\omega_0 L |I|^2}{2}} \\ &= \frac{R}{\omega_0 L} + \frac{R_L}{\omega_0 L} \end{aligned}$$

$$Q_{ext} = \frac{1}{R_L} \sqrt{\frac{L}{C}} = \text{external } Q$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \text{internal } Q$$

b)

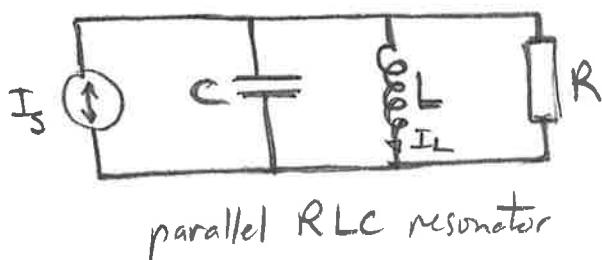

$$Z(\omega) = \frac{1}{G + i \frac{C}{\omega} (\omega^2 - \omega_0^2)} = \frac{1}{Y(\omega)}$$

$$G = \frac{1}{4R}$$

A similar idea: $\bar{W} = \bar{W}_C + \bar{W}_L = \frac{1}{2} |V|^2 \cdot C + \frac{1}{2} L |I_L|^2$

$$\text{But } I_L = \frac{V}{i\omega L}$$


$$= \frac{1}{2} C |V|^2 \text{ at resonance}$$

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$P_T = \frac{1}{2} G |V|^2$$

$$\Rightarrow Q_L = \frac{\omega_0 \bar{W}}{\bar{P}} = \frac{\omega_0 C}{G} = \omega_0 R C = \frac{R}{\omega_0 L} = R \sqrt{\frac{C}{L}}$$

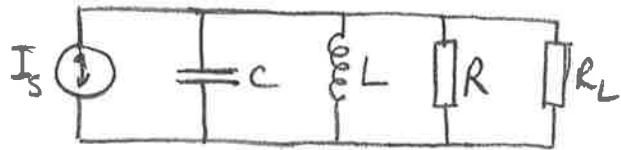= Loading of the parallel RLC resonator =



$$Q_L = \left(\frac{1}{R} + \frac{1}{R_L} \right) \sqrt{\frac{C}{L}} = \text{loaded } Q$$

$$Q_{\text{ext}} = \frac{1}{R_L} \sqrt{\frac{C}{L}} = \text{external } Q$$

$$Q = \frac{1}{R} \sqrt{\frac{C}{L}} = \text{internal } Q$$

$$\text{or } Q_L^{-1} = Q_{\text{ext}}^{-1} + Q^{-1}$$

→ this relation is the same
as for the series RLC
resonator