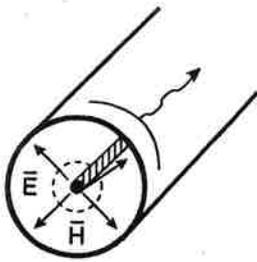



Transmission lines

- Electromagnetic waves can propagate in free space ← review this! based on Maxwell's equations!
* but also they can be guided by conducting or dielectric boundaries
- Transmission-line behaviour; occurs when $\lambda \ll$ length of transmission line
Transmission lines = guiding devices for the electromagnetic field
- The electromagnetic fields are TEM (transverse electromagnetic mode) if the conductors are ideal (zero-resistance); otherwise there will be a small axial component of the electromagnetic field.


Types of transmission lines




(a) = COAXIAL LINE

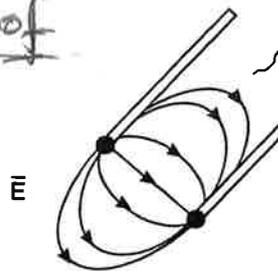


(b) = TWO-WIRE TRANSMISSION LINE

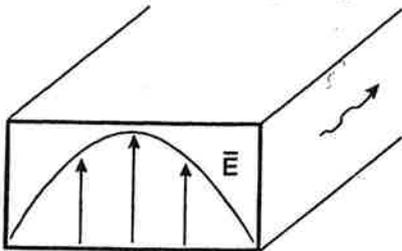


(c) = WAVEGUIDE (COPLANAR)

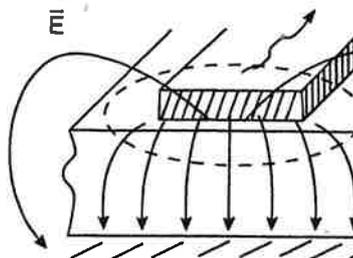

(d) = MICROSTRIP LINE

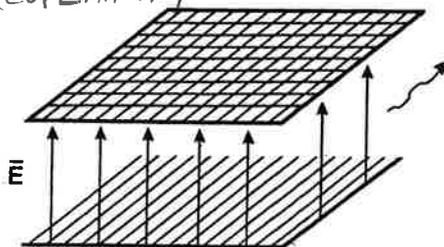


(e) = PARALLEL-PLATE WAVEGUIDE

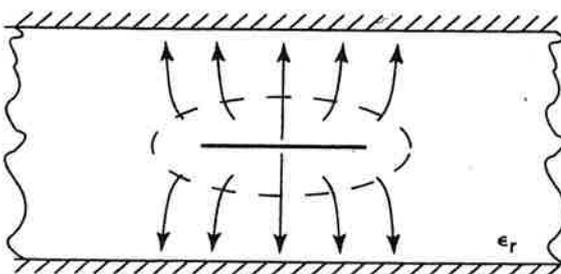


E ———
H - - -

(f) = STRIPLINE

EXAMPLE: The coaxial line

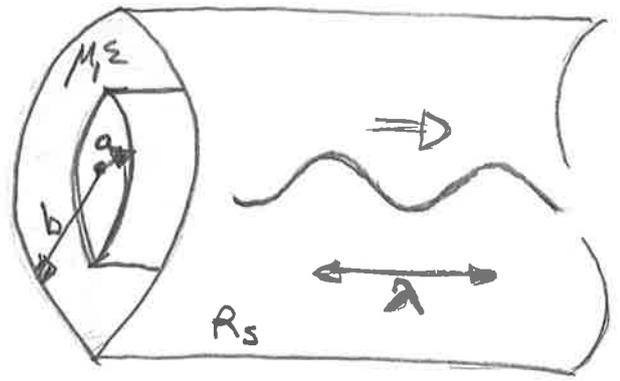

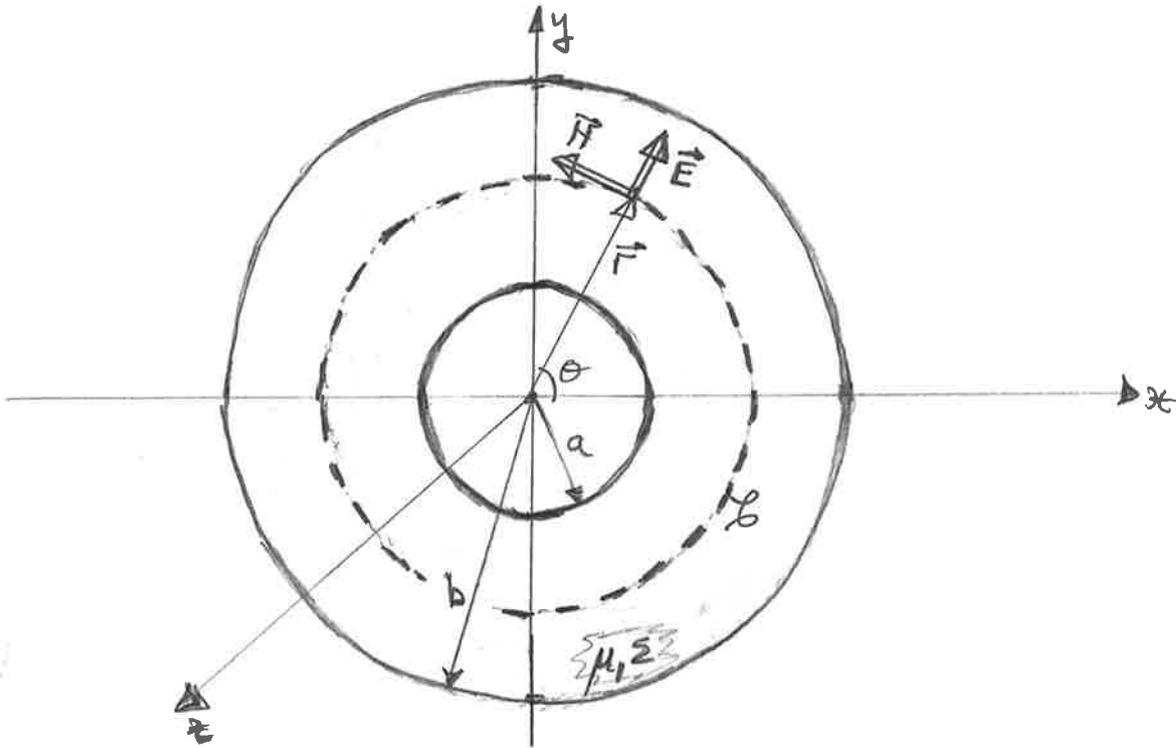
- How to calculate the \vec{E} , \vec{H} fields inside?



Electric field

$$\vec{E} = \frac{V_0}{\ln \frac{b}{a}} \frac{\hat{r}}{r}$$

Proof:

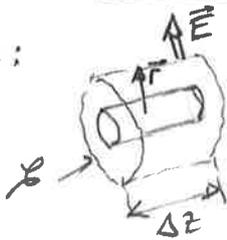

$$\nabla \cdot \vec{D} = \rho \Rightarrow$$

$$\int d\vec{s} \cdot \vec{E} = \int \frac{\rho}{\epsilon} dV \quad (\text{Gauss' law})$$

$$\downarrow \quad \downarrow$$

$$2\pi r (\Delta z) \cdot E \quad \frac{1}{\epsilon} (\Delta z) \cdot \rho \cdot \pi a^2$$

Therefore

$$E = \frac{1}{r} \cdot \frac{\rho a^2}{2\epsilon}$$

$$\text{Also } V_0 = \int_a^b dr \cdot E$$

$$= \int_a^b \frac{dr}{r} \cdot \frac{\rho a^2}{2\epsilon} = \frac{\rho a^2}{2\epsilon} \ln \frac{b}{a} \rightarrow \frac{\rho a^2}{2\epsilon} = \frac{V_0}{\ln \frac{b}{a}}$$

$$\text{So } \vec{E} = \frac{V_0}{\ln \frac{b}{a}} \frac{\hat{r}}{r}$$

Magnetic field

$$\vec{H} = \frac{I_0}{2\pi r} \hat{\phi}$$

$$\nabla \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t}$$


$$\oint \vec{H} \cdot d\vec{l} = \int \vec{J} \cdot d\vec{s} = I_0$$

$$\text{or } 2\pi r \cdot H = I_0 \Rightarrow H = \frac{I_0}{2\pi r} \hat{\phi}$$

Towards a distributed model of inductances, capacitances, resistances, conductances

Problem: how to connect the electric and magnetic fields to circuit-elements

Answer: via stored or dissipated energy

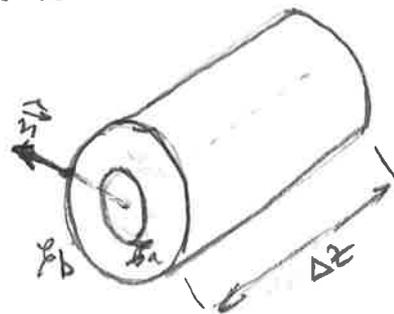

① Inductance per unit length

$$\text{magnetic energy} = \frac{\mu}{4} \int ds \cdot (\Delta z) H^2 = \frac{L' \Delta z I_0^2}{4} \Rightarrow L' = \frac{\mu}{I_0^2} \int ds H^2$$

$$L' = \frac{\mu}{I_0^2} \int ds H^2 = \frac{\mu}{I_0^2} \cdot I_0^2 \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{1}{(2\pi r)^2} = \frac{\mu}{2\pi} \ln \frac{b}{a}$$

$$\boxed{L' = \frac{\mu}{2\pi} \ln \frac{b}{a}}$$

(measured in H/m)

② Capacitance per unit length

$$\text{electrostatic energy} = \frac{\epsilon}{4} \int ds \cdot (\Delta z) \cdot E^2 = \frac{C' \Delta z V_0^2}{4} \Rightarrow C' = \frac{\epsilon}{V_0^2} \int ds \cdot E^2$$

$$C' = \frac{\epsilon}{V_0^2} \int ds E^2 = \frac{\epsilon}{V_0^2} \cdot V_0^2 \cdot \frac{1}{\ln^2 \frac{b}{a}} \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{1}{r^2} \Rightarrow$$

$$\boxed{C' = \frac{2\pi \epsilon}{\ln \frac{b}{a}}}$$

(measured in F/m)

③ Resistance per unit length

$$\text{power dissipated in the lossy conductors} = \frac{R_s}{2} \int_{\beta_a + \beta_b} dl \cdot \Delta z \cdot J_s^2 = \frac{R_s}{2} \Delta z \cdot \int_{\beta_a + \beta_b} dl \cdot H^2 = \frac{R' \Delta z I_0^2}{2}$$

Here R_s = surface resistance

$\vec{J}_s = \hat{n} \times \vec{H}$ = surface current

\hat{n} = vector unit pointing outwards

(normal to the conducting surface)

$$R' = \frac{R_s}{I_0^2} \int_{\beta_a + \beta_b} dl \cdot H^2$$

$$R' = \frac{R_s}{I_0^2} \int_{\beta_a + \beta_b} dl \cdot H^2 = \frac{R_s}{(2\pi)^2} \left[\int_0^{2\pi} d\theta \cdot a \cdot \frac{1}{a^2} + \int_0^{2\pi} d\theta \cdot b \cdot \frac{1}{b^2} \right] = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$$

$$\Rightarrow \boxed{R' = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)}$$

(measured in Ω/m)

④ Conductance (radial) per unit length

$$\Sigma = \Sigma' - i \Sigma'' = \epsilon_0 \epsilon_r (1 - i \tan \delta)$$

$$\Sigma' = \epsilon_0 \epsilon_r$$

$\Sigma'' = \Sigma \tan \delta \rightarrow$ dissipation in the dielectric between the core metal and the outside shield.

$$\text{power dissipated} = \frac{\omega \Sigma''}{2} \int ds \cdot \Delta z \cdot E^2 = \frac{G' V_0^2}{2} \rightarrow G' = \frac{\omega \Sigma''}{V_0^2} \cdot \int ds \cdot E^2$$

$$\Rightarrow G' = \frac{\omega \Sigma''}{V_0^2} \int ds \cdot E^2 = \frac{\omega \Sigma''}{V_0^2} \cdot \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{V_0^2}{r^2 \ln \frac{b}{a}} \Rightarrow \boxed{G' = \frac{2\pi \omega \Sigma''}{\ln \frac{b}{a}}}$$


(measured in S/m)

Examples of materials used in coaxes

Conductor	Copper Cu	Aluminum Al	Silver Ag	Gold Au
Resistivity ρ [mΩ·m] \downarrow 10^{-9} "nano"	16.9	26.7	16.3	22.0

Dielectric	Dry air	Polyethylene	PTFE	PVC
ϵ_r	1.0006	2.2	2.1	3.2
$\tan \delta$	low	0.0002	0.0002	0.001
Resistivity (Ω·m)	high	10^{15}	10^{15}	10^{15}
Breakdown voltage (kV/m)	3	47	59	34

Other transmission lines:

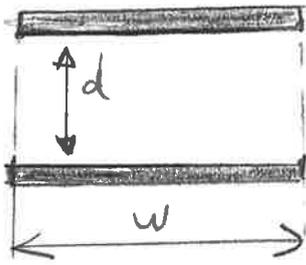


$$L' = \frac{\mu d}{w}$$

$$C' = \frac{\epsilon' w}{d}$$

$$R' = \frac{2R_s}{w}$$

$$G' = \frac{\omega \epsilon'' w}{d}$$

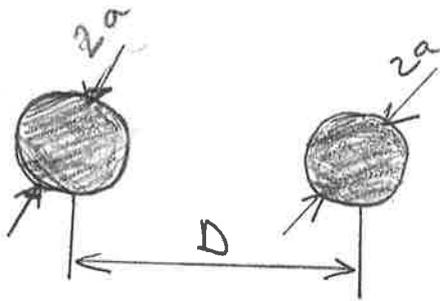

$$L' = \frac{\mu}{\pi} \cosh^{-1} \frac{D}{2a}$$


$$C' = \frac{\pi \epsilon'}{\cosh^{-1} \frac{D}{2a}}$$

$$R' = \frac{R_s}{\pi a}$$

$$G' = \frac{\pi \omega \epsilon''}{\cosh^{-1} \frac{D}{2a}}$$

TRANSMISSION LINES - general models

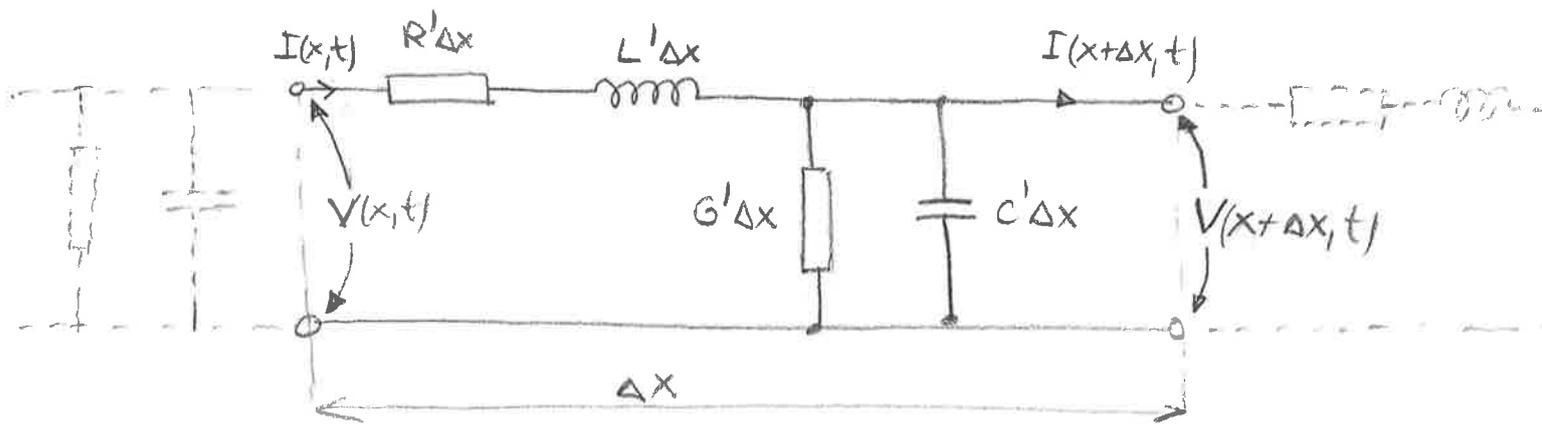- If the length of a circuit is $\geq \lambda$ we have to use either a simulator of Maxwell's equations or a distributed model of lumped elements.
- TLLs = two parallel conductors that guide the electromagnetic field
examples: two-wire lines, striplines, microstrip lines



R', L', G', C' = resistance, inductance, conductance, capacitance per unit length.

KIRCHHOFF says:

$$\begin{cases} V(x,t) = I(x,t)R'\Delta x + L'\Delta x \cdot \frac{\partial I(x,t)}{\partial t} + V(x+\Delta x,t) \\ I(x,t) = V(x+\Delta x,t)G'\Delta x + C'\Delta x \frac{\partial V(x+\Delta x,t)}{\partial t} + I(x+\Delta x,t) \end{cases}$$

$\Delta x \rightarrow 0$

$$\begin{cases} -\frac{\partial V(x,t)}{\partial x} = R' I(x,t) + L' \frac{dI(x,t)}{dt} \\ -\frac{\partial I(x,t)}{\partial x} = G' V(x,t) + C' \frac{\partial V(x,t)}{\partial t} \end{cases}$$

Therefore,

$$\begin{cases} -\frac{\partial^2 V(x,t)}{\partial x^2} = -R'(G'V(x,t) + C' \frac{\partial V(x,t)}{\partial t}) - L'(G' \frac{\partial V(x,t)}{\partial t} + C' \frac{\partial^2 V(x,t)}{\partial t^2}) \\ -\frac{\partial^2 I(x,t)}{\partial x^2} = -G'(R'I(x,t) + L' \frac{\partial I(x,t)}{\partial t}) - C'(R' \frac{\partial I(x,t)}{\partial t} + L' \frac{\partial^2 I(x,t)}{\partial t^2}) \end{cases}$$

or

$$\begin{cases} \frac{\partial^2 V(x,t)}{\partial x^2} = L'C' \frac{\partial^2 V(x,t)}{\partial t^2} + (R'C' + L'G') \frac{\partial V(x,t)}{\partial t} + R'G'V(x,t) \\ \frac{\partial^2 I(x,t)}{\partial x^2} = L'C' \frac{\partial^2 I(x,t)}{\partial t^2} + (R'C' + L'G') \frac{\partial I(x,t)}{\partial t} + R'G'I(x,t) \end{cases}$$

Harmonic signals:

$$V(x,t) = V(x) e^{i\omega t}$$

$$I(x,t) = I(x) e^{i\omega t}$$

$V(x), I(x)$ = phasors

$$\Rightarrow \begin{cases} \frac{d^2 V(x)}{dx^2} - \gamma^2 V(x) = 0 \\ \frac{d^2 I(x)}{dx^2} - \gamma^2 I(x) = 0 \end{cases}$$

$$\gamma = \alpha + i\beta =$$

$$= \sqrt{(R' + i\omega L')(G' + i\omega C')}$$

γ = propagation constant

α = attenuation constant

β = phase constant

$$\Rightarrow \boxed{V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x}}$$

general solution

From $-\frac{\partial V(x,t)}{\partial x} = R I(x,t) + L \frac{\partial I(x,t)}{\partial t}$

we get $I(x) = -\frac{1}{R + i\omega L} \frac{dV(x)}{dx}$

or

$$I(x) = \frac{1}{Z_0} V^+ e^{-\gamma x} - \frac{1}{Z_0} V^- e^{\gamma x}$$

where

$$Z_0 = \sqrt{\frac{R' + i\omega L'}{G' + i\omega C'}} = \text{characteristic impedance of the transmission line}$$

$$= I^+ e^{-\gamma x} + I^- e^{\gamma x} \quad \text{where } I^\pm = \pm \frac{V^\pm}{Z_0}$$

Lossless transmission case: $R' = G' = 0$

$$\gamma = i\beta = i\omega \sqrt{L'C'}$$

$$Z_0 = \frac{L}{C} = \sqrt{\frac{L}{C}}$$

→ now independent of frequency!

Note: free-space impedance = 377Ω

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}} = \text{phase velocity}$$

Exercise: Show that for the

low-loss case $R \ll \omega L, G \ll \omega C$ we have


$$\beta \approx \omega \sqrt{L'C'}$$

$$\alpha \approx \frac{1}{2} \sqrt{L'C'} \left(\frac{R'}{L} + \frac{G'}{C} \right)$$

Standardized values:

Z_0	Application
50Ω	Instrumentation, communication
75Ω	TV, VHF radio
300Ω	RF
600Ω	audio

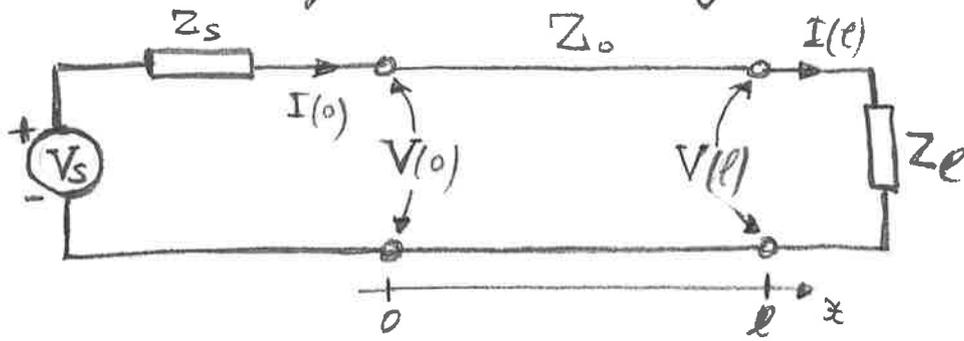• Incident and reflected waves along a loaded transmission line



line terminated
in a
load impedance
 Z_l

$$V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x}$$

$$I(x) = I^+ e^{-\gamma x} + I^- e^{\gamma x}$$

$$I^\pm = \pm \frac{V^\pm}{Z_0}$$

$$\begin{cases} V(0) = V_s - Z_s I(0) & \text{--- Kirchhoff's law} \\ V(l) = Z_l I(l) \end{cases}$$

or:

$$\begin{cases} V^+ + V^- = V_s - \frac{Z_s}{Z_0} (V^+ + V^-) \\ V^+ e^{-\gamma l} + V^- e^{\gamma l} = \frac{Z_l}{Z_0} (V^+ e^{-\gamma l} - V^- e^{\gamma l}) \end{cases}$$

$$V^+ e^{-\gamma l} + V^- e^{\gamma l} = \frac{Z_l}{Z_0} (V^+ e^{-\gamma l} - V^- e^{\gamma l})$$

• Define a reflection coefficient at the load $x = l$

$$\Gamma_V = \frac{V^- e^{\gamma l}}{V^+ e^{-\gamma l}}$$

$$\rightarrow 1 + \Gamma_V = \frac{Z_l}{Z_0} (1 - \Gamma_V) \Rightarrow \boxed{\Gamma_V = \frac{Z_l - Z_0}{Z_l + Z_0}}$$

We can also define a current reflection coefficient at the load

$$\boxed{\Gamma_I = \frac{I^- e^{\gamma l}}{I^+ e^{-\gamma l}} = -\Gamma_V}$$

• Define the transmission coefficient at the load $x = l$

$$T_V = \frac{V^+ e^{-\gamma l} + V^- e^{\gamma l}}{V^+ e^{-\gamma l}}$$

$$\text{sr } \boxed{T_V = 1 + \Gamma_V}$$

and for current

$$\boxed{T_I = \frac{I^+ e^{-\gamma l} + I^- e^{\gamma l}}{I^+ e^{-\gamma l}} = 1 + \Gamma_I}$$

• Average power delivered to the load

$$\bar{P}_e = \frac{1}{2} \operatorname{Re} [V(\ell) I^*(\ell)]$$

$\frac{1}{2}$ - comes from the fact that the field is harmonic

$$\begin{aligned} \text{Now } 1 - \Gamma_V &= \frac{I^- e^{\gamma \ell} + I^+ e^{-\gamma \ell}}{I^+ e^{-\gamma \ell}} = \frac{I(\ell)}{I^+ e^{-\gamma \ell}} \\ 1 + \Gamma_V &= \frac{V^+ e^{-\gamma \ell} + V^- e^{\gamma \ell}}{V^+ e^{-\gamma \ell}} = \frac{V(\ell)}{V^+ e^{-\gamma \ell}} \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow$$

$$\begin{aligned} (1 - \Gamma_V^*)(1 + \Gamma_V) &= \frac{V(\ell) I^*(\ell)}{I^{+*} V^+ e^{-\gamma \ell} (e^{-\gamma \ell})^*} \\ \text{but } I^+ &= \frac{V^+}{Z_0} \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \rightarrow$$


$$\begin{aligned} V(\ell) I^*(\ell) &= \frac{1}{Z_0} |V^+ e^{-\gamma \ell}|^2 \cdot \underbrace{(1 - \Gamma_V^*)(1 + \Gamma_V)}_{\equiv 1 - \Gamma_V^* + \Gamma_V - |\Gamma_V|^2} \\ &\quad \downarrow \\ &\quad \text{imaginary!} \end{aligned}$$

$$\Rightarrow \bar{P}_e = \frac{1}{2Z_0} |V^+ e^{-\gamma \ell}|^2 (1 - |\Gamma_V|^2)$$

• VSWR (voltage standing-wave ratio)

$$V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x} = V^+ e^{-\gamma x} [1 + \Gamma_V e^{-2\gamma(\ell-x)}]$$

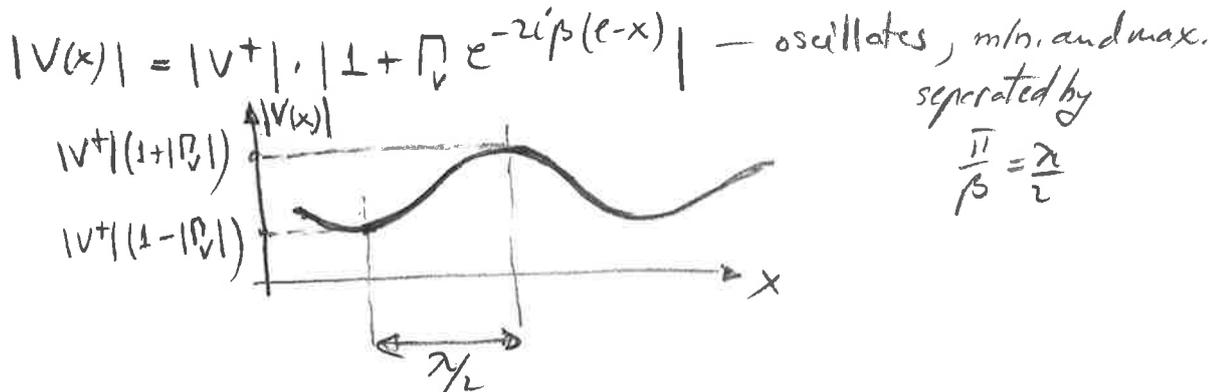Let's consider a lossless line $\alpha = 0$ $\sigma = i\beta = \frac{2\pi i}{\lambda}$ remember that $\Gamma_V \equiv \frac{V^- e^{\gamma \ell}}{V^+ e^{-\gamma \ell}}$



$$\text{VSWR} = \frac{1 + |\Gamma_V|}{1 - |\Gamma_V|} = \text{ratio between the max. line voltage and min. line voltage}$$

• Impedance along the line

$$Z(x) \equiv \frac{V(x)}{I(x)} = Z_0 \frac{V^+ e^{-\gamma x} + V^- e^{\gamma x}}{V^+ e^{-\gamma x} - V^- e^{\gamma x}} = Z_0 \frac{1 + \Gamma_V e^{-2\gamma(l-x)}}{1 - \Gamma_V e^{-2\gamma(l-x)}}$$

take $x=0 \rightarrow$ we get $Z(0) \equiv Z_{in}$ = input impedance of the line, i.e. the impedance seen when looking toward the load.

$$Z_{in} = Z_0 \cdot \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l}$$

— can be verified immediately by recalling that $\Gamma_V = \frac{Z_L - Z_0}{Z_L + Z_0}$

Note that in general $Z_{in} \neq Z_0$, so the termination matters!
and also Z_{in} is frequency-dependent


EXAMPLES OF LOADS (TERMINATIONS)

1) Matched load

$$Z_L = Z_0$$

$$\Rightarrow \Gamma_V \equiv \frac{Z_L - Z_0}{Z_L + Z_0} = 0$$

No reflection!

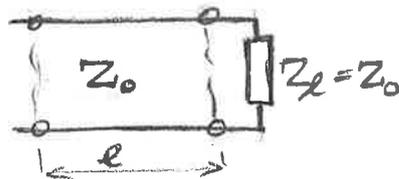

$$VSWR = 1, \quad P_e = \frac{1}{2} |V^+|^2 e^{-2\alpha l}$$


— power delivered is maximal, it is only attenuated if $\alpha \neq 0$

$$Z_{in} = Z_0$$

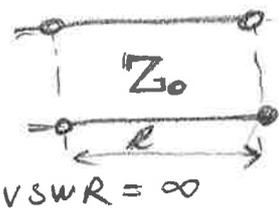2) Open-circuit

$$Z_L = \infty$$

$$\Gamma_V = \frac{Z_L - Z_0}{Z_L + Z_0} = 1$$




$VSWR = \infty$

$P_e = 0$ — compare this with the DC case where all input power is delivered!

$$Z_{in} = Z_0 \coth \gamma l$$

For $\alpha = 0$ (lossless)
 $Z_{in} = -i Z_0 \cotan \frac{2\pi l}{\lambda}$

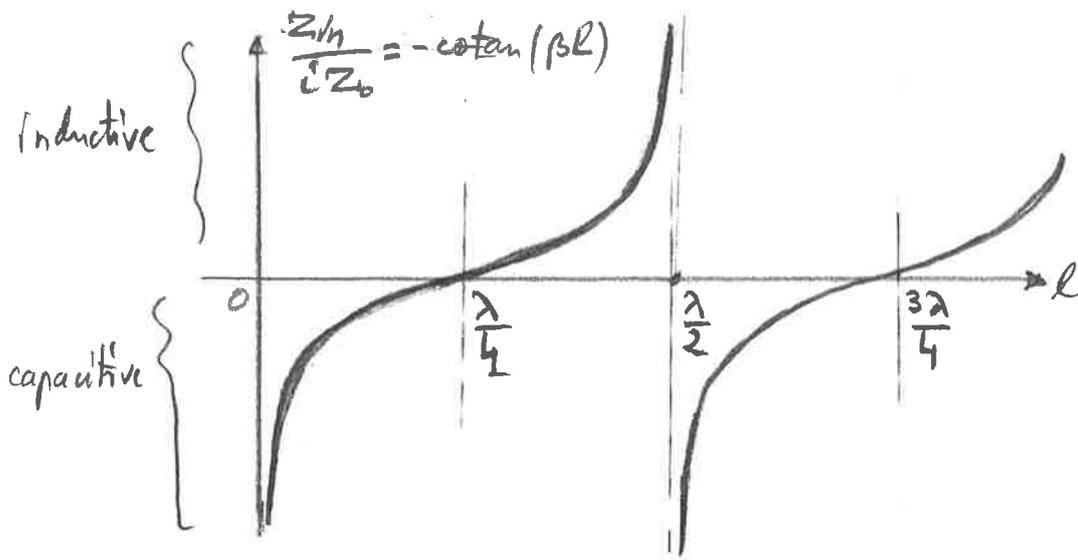
if $l = \frac{\lambda}{4}$, $Z_{in} = 0$ so the open line will look as a short circuit!



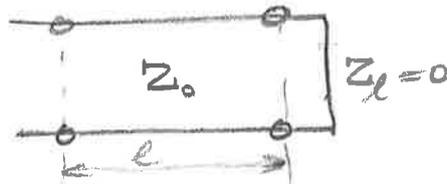3) Short-circuit

$$Z_L = 0$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$



$$VSWR = \infty \quad P_r = 0$$

$$Z_{in} = Z_0 \tanh \gamma l$$


For $\alpha = 0$ (lossless)

$$\beta = \frac{2\pi}{\lambda}$$

$$Z_{in} = i Z_0 \tan \frac{2\pi l}{\lambda}$$


if $l = \frac{\lambda}{4}$, $Z_{in} = \infty$
 so the shorted line looks like an infinite impedance to a source!

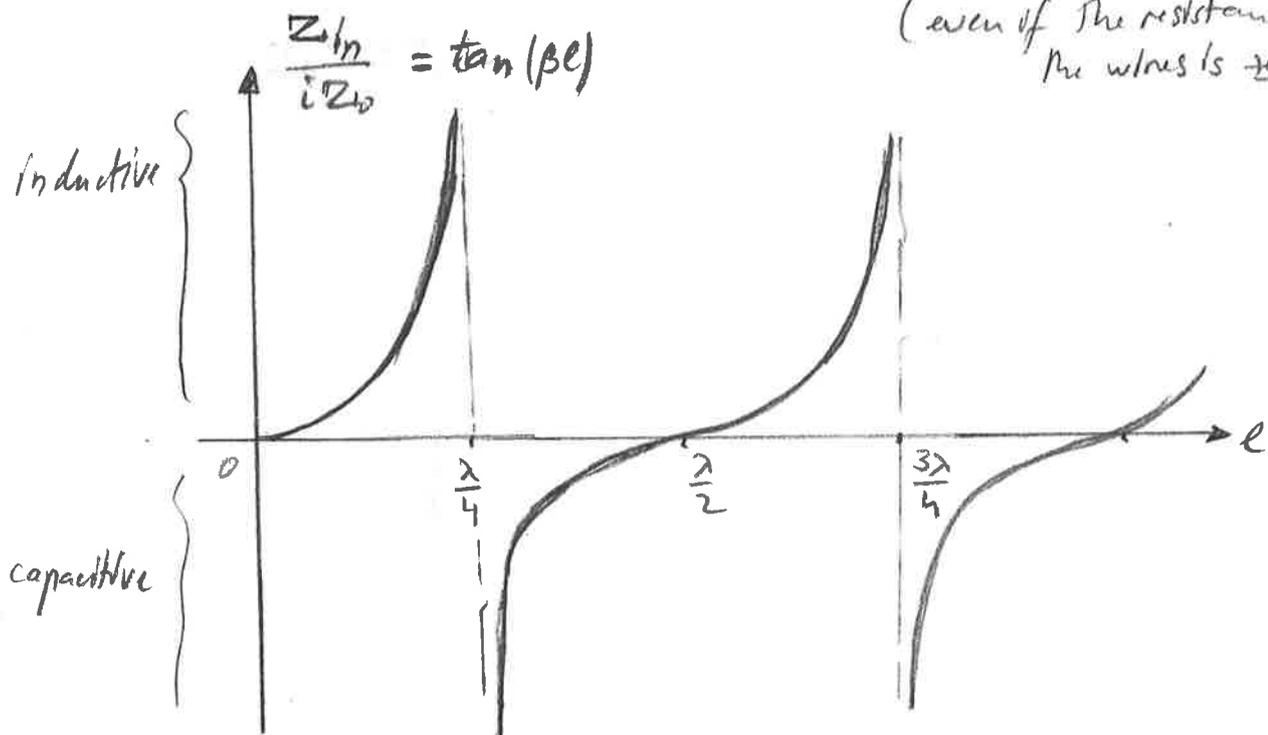(even if the resistance of the wires is zero!)



Resonators from transmission lines

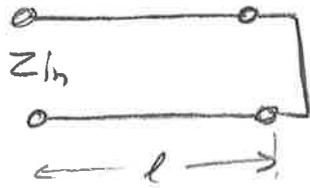- It is possible to make resonators from transmission lines, 3D cavities, etc.
- The most usual case is the short-circuited transmission-line resonator.



$$Z_e = 0$$

$$Z_{in} = Z_0 \tanh(\alpha l + i\beta l)$$

$$= Z_0 \frac{\tanh \alpha l + i \tan \beta l}{1 + i \tan \beta l \tanh \alpha l}$$

If losses are not too large, $\alpha l \ll 1$, we have $\tanh \alpha l \approx \alpha l$

$$\text{so } Z_{in} = Z_0 \frac{\alpha l + i \tan \beta l}{1 + i \alpha l \tan \beta l}$$

Now, recall

$$\text{that } \beta = \frac{\omega}{v_p} = \omega \sqrt{L'C'} \quad v_p = \frac{1}{\sqrt{L'C'}}$$

$$Z_0 = \sqrt{\frac{L'}{C'}}$$

$$\alpha = \frac{R'}{2} \sqrt{\frac{C'}{L'}}$$

$$\text{We will consider } \beta_0 l = \pi \text{ or } l = \frac{\lambda_0}{2}$$

as the resonance condition, leading to

$$\text{a resonance frequency } \omega_0 \quad \frac{\omega_0}{v_p} l = \omega_0 \sqrt{L'C'} l = \pi$$

$$\text{so } \omega_0 = \frac{\pi}{l \sqrt{L'C'}}$$

We can expand around this point

$$\tan \beta l \approx \tan \left(\pi + \pi \frac{\omega - \omega_0}{\omega_0} \right) = \tan \pi \frac{\omega - \omega_0}{\omega_0} \approx \pi \frac{\omega - \omega_0}{\omega_0}$$


if $|\omega - \omega_0| \ll \omega_0$

So

$$Z_{in} = Z_0 \frac{\alpha l + i\pi \frac{\omega - \omega_0}{\omega_0}}{1 + \alpha l \pi \frac{\omega - \omega_0}{\omega_0}} \approx Z_0 \left(\alpha l + i\pi \frac{\omega - \omega_0}{\omega_0} \right)$$

$$= \sqrt{\frac{L}{C}} \left(\frac{l}{2} R' \sqrt{\frac{C}{L}} + i l \sqrt{L' C'} (\omega - \omega_0) \right) = \frac{1}{2} R' l + i L' l (\omega - \omega_0)$$

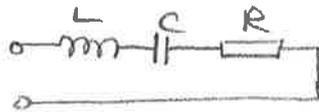• Suppose now that we look back at a series RLC circuit



$$Z = R + i \frac{L}{\omega} (\omega^2 - \omega_0^2)$$

$$\approx R + 2iL(\omega - \omega_0) \text{ near resonance, } \omega \approx \omega_0$$

Therefore we can identify $R = \frac{1}{2} R' l$ and $L = \frac{1}{2} L' l$

$$\text{Quality factor } Q = \frac{\omega_0 L}{R} = \frac{\omega_0 L'}{R'} = \frac{\beta_0}{2\alpha}$$

- Interesting question to think about: why do we get the factor $\frac{1}{2}$ in the RLC equivalent above?

Because the current

in the short-circuited line is half a sinusoid, therefore we obtain only half of the total resistance and inductance of the full length l .

To see this explicitly, let us write the solution

$$\begin{cases} V(x) \approx v^+ e^{-i\beta x} + v^- e^{i\beta x} & \text{— here we neglect } \alpha \\ I(x) \approx -\frac{\beta}{\omega L} (-v^+ e^{-i\beta x} + v^- e^{i\beta x}) \end{cases}$$

Since $I(0) = 0 \Rightarrow v^+ = v^-$ at this point

(also you can see that $\Gamma_V \equiv \frac{v^-}{v^+} e^{2i\beta l} = -1$ and $\beta l = \pi$)

$$\text{So } \begin{cases} V(x) = 2V^+ \cos \beta_0 x \\ I(x) = -\frac{2I^+}{\omega L} V^+ \sin \beta_0 x = I^+ \sin \beta_0 x \end{cases}$$

Therefore the magnetic field energy

$$\begin{aligned} \overline{W}_L &= \int_0^{\lambda_0/2} dx \cdot \frac{1}{4} L' |I(x)|^2 = \frac{1}{4} |I^+|^2 L' \int_0^{\lambda_0/2} \sin^2 \beta_0 x dx \\ &= \frac{\lambda_0}{16} |I^+|^2 L' \end{aligned}$$

$$\overline{W}_C = \overline{W}_L \text{ at resonance} \quad \text{so } \overline{W} = \overline{W}_C + \overline{W}_L = \frac{\lambda_0}{8} L' |I^+|^2$$

$$\overline{P} = \frac{1}{2} \int_0^{\lambda_0/2} dx \cdot R' |I(x)|^2 = \frac{R'}{2} |I^+|^2 \int_0^{\lambda_0/2} \sin^2 \beta_0 x dx$$

$$\text{so } \overline{P} = \frac{\lambda_0}{8} R' |I^+|^2$$

Therefore $Q = \frac{\omega_0 \overline{W}}{\overline{P}} = \frac{\omega_0 L'}{R'}$

$$\text{or: } Q = \frac{\pi}{2R'} \sqrt{\frac{L}{C}} = \frac{\pi Z_0}{2R'} = \frac{\pi}{2l\alpha}$$

where we used $\alpha \approx \frac{R}{2Z_0}$, $\omega_0 = \frac{\pi}{l\sqrt{LC}}$

REFERENCES

- David M. Pozar - Microwave Engineering
- R.E. Collin - Foundations for Microwave Engineering