


Lecture 3

Lecturer: G. S. Paraoanu


*Department of Applied Physics, School of Science,
Aalto University, P.O. Box 15100, FI-00076 AALTO, Finland*

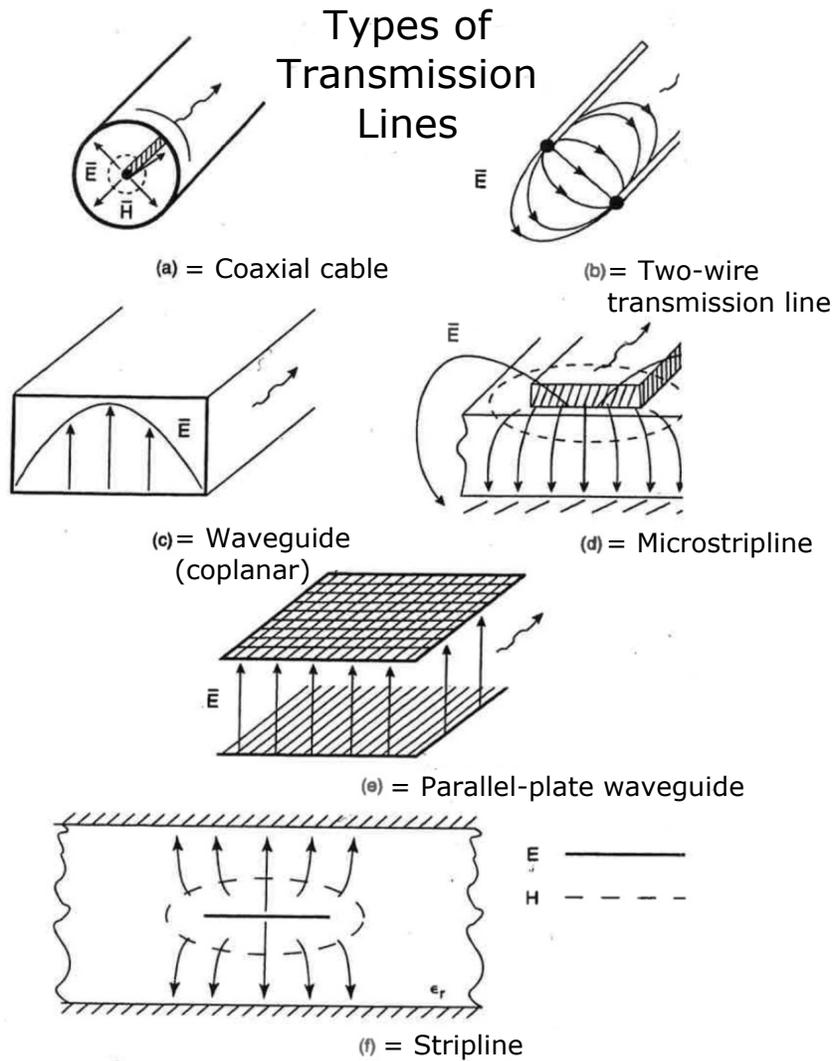I. TRANSMISSION LINES

- Electromagnetic waves can propagate in free space (Review this! Based on Maxwell's equations!). But also they can be guided by conducting or dielectric boundaries.
- Transmission line behavior: occurs when $\lambda \ll$ length of transmission line.
- Transmission lines = guiding devices for the electromagnetic field.
- The electromagnetic fields are TEM (transverse electromagnetic mode) if the conductors are ideal (zero-resistance); otherwise there will be a small axial component of the electromagnetic field.



EXAMPLE: The coaxial line

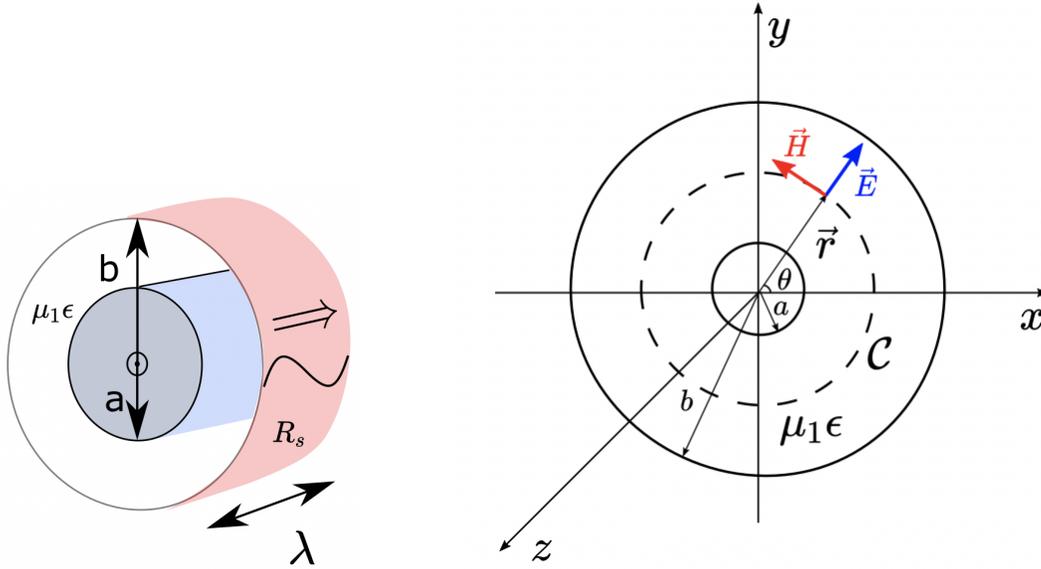


* How to calculate the \vec{E} , \vec{H} fields inside?

Electric Field:
$$\vec{E} = \frac{V_0}{\ln \frac{b}{a}} \hat{r} \quad (1)$$

Proof:

$$\vec{\nabla} \cdot \vec{D} = \rho \implies \int d\vec{S} \cdot \vec{E} = \int \frac{\rho}{2} dV \implies 2\pi r \cdot (\Delta z) \cdot E = \frac{1}{\epsilon} (\Delta z) \cdot \rho \cdot \pi a^2 \quad \therefore E = \frac{1}{r} \cdot \frac{\rho a^2}{2\epsilon}$$
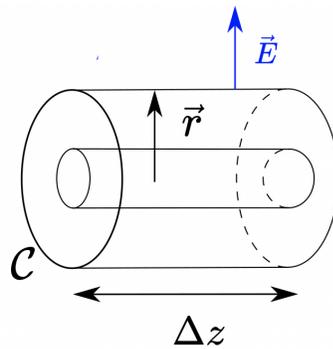
$$\text{Also } V_0 = \int_a^b dr \cdot E = \int_a^b \frac{dr}{r} \cdot \rho \frac{a^2}{2\epsilon} \ln \frac{b}{a} \rightarrow \rho \frac{a^2}{2\epsilon} = \frac{V_0}{\ln \frac{b}{a}}, \text{ so } \vec{E} = \frac{V_0}{\ln \frac{b}{a}} \hat{r}.$$




Magnetic Field:
$$\vec{H} = \frac{I_0}{2\pi r} \cdot \hat{e}_\theta \quad (2)$$

Proof:

$$\vec{\nabla} \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t} \implies \int_C \vec{H} \cdot d\vec{\ell} = \int \vec{J} \cdot d\vec{S} = I_0, \text{ or } 2\pi r \cdot H = I_0 \implies \vec{H} = \frac{I_0}{2\pi r} \cdot \hat{e}_\theta.$$

II. TOWARDS A DISTRIBUTED MODEL OF INDUCTORS, CAPACITANCES, RESISTANCES, CONDUCTANCES

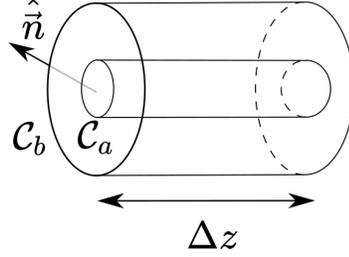Problem: How to connect the electric and magnetic fields to circuit elements.



Answer: Via stored or dissipated energy.

1. Inductance per unit length

$$\text{Magnetic energy} = \frac{\mu}{4} \int ds \cdot (\Delta z) \vec{H}^2 = \frac{(L' \Delta z) I_0^2}{4} \implies L' = \frac{\mu}{I_0^2} \int ds \vec{H}^2$$

$$L' = \frac{\mu}{I_0^2} \int ds H^2 = \frac{\mu}{I_0^2} \cdot I_0^2 \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{1}{(2\pi r)^2} = \frac{\mu}{2\pi} \ln \frac{b}{a}.$$

Therefore,

$$L' = \frac{\mu}{2\pi} \ln \frac{b}{a} \quad (\text{measured in units of H/m}). \quad (3)$$

2. Capacitance per unit length

$$\text{Electrostatic energy} = \frac{\epsilon}{4} \int ds \cdot (\Delta z) \cdot E^2 = \frac{(C' \Delta z) V_0^2}{4} \implies C' = \frac{\epsilon}{V_0^2} \cdot \int ds \cdot E^2$$

$$C' = \frac{\epsilon}{V_0^2} \int ds E^2 = \frac{\epsilon}{V_0^2} \cdot V_0^2 \cdot \frac{1}{\ln^2 \frac{b}{a}} \int_0^{2\pi} d\theta \int_0^b dr \cdot r \cdot \frac{1}{r^2}$$

$$\implies C' = \frac{2\pi\epsilon}{\ln \frac{b}{a}} \quad (\text{measured in units of F/m}). \quad (4)$$

3. Resistance per unit length

$$\text{Power dissipated in the lossy conductors} = \frac{R_s}{2} \int_{C_a+C_b} dl \cdot \Delta z \cdot \vec{J}_s^2 = \frac{R_s}{2} \Delta z \cdot \int_{C_a+C_b} dl \cdot H^2 = \frac{R' \Delta z}{2} I_0^2. \text{ Here } R_s = \text{surface resistance, } \vec{J}_s = \hat{n} \times \vec{H} = \text{surface current, } \hat{n} = \text{vector unit}$$

pointing outwards (normal to the conducting surface), and $R' = \frac{R_s}{I_0^2} \int_{C_a+C_b} d\ell \cdot \vec{H}^2$.

$$R' = \frac{R_s}{I_0^2} \int_{C_a+C_b} d\ell \cdot H^2 = \frac{R_s}{(2\pi)^2} \left[\int_0^{2\pi} d\theta \cdot a \cdot \frac{1}{a^2} + \int_0^{2\pi} d\theta \cdot b \cdot \frac{1}{b^2} \right] = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$$

$$R' = \frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right) \quad (\text{measured in units of } \Omega/\text{m}). \quad (5)$$

4. Conductance (radial) per unit length

$$\epsilon = \epsilon' - i\epsilon'' = \epsilon_0\epsilon_r(1 - i \tan \delta)$$

$$\epsilon' = \epsilon_0\epsilon_r$$

$\epsilon'' = \epsilon \tan \delta \rightarrow$ dissipation in the dielectric between the core metal and the outside shield.

$$\text{Power dissipated} = \frac{\omega\epsilon''}{2} \int ds \cdot \Delta z \cdot E^2 = \frac{G'V_0^2}{2} \rightarrow G'' = \frac{\omega\epsilon''}{V_0^2} \int ds \cdot E^2$$

$$\implies G' = \frac{\omega\epsilon''}{V_0^2} \int ds \cdot E^2 = \frac{\omega\epsilon''}{V_0^2} \cdot \int_0^{2\pi} d\theta \int_a^b dr \cdot r \cdot \frac{V_0^2}{r^2 \ln \frac{b}{a}}$$


$$\implies G' = \frac{2\pi\omega\epsilon''}{\ln \frac{b}{a}} \quad (\text{measured in units of S/m}). \quad (6)$$

– Examples of materials used in coax:

Conductor	Copper Cu	Aluminum Al	Silver Ag	Gold Au
Resistivity ρ [n $\Omega \cdot$ m]	16.9	26.7	16.3	22.0

Dielectric	Dry Air	Polyethylene	PTFE	PVC
ϵ_r	1.0006	2.2	2.1	3.2
$\tan \delta$	low	0.0002	0.0002	0.001
Resistivity ($\Omega \cdot$ m)	high	10^{15}	10^{15}	10^{15}
Breakdown voltage (mV/m)	3	47	59	34

Other transmission lines:

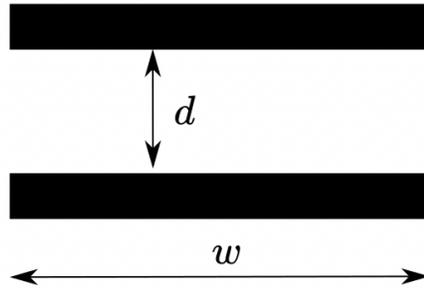


$$L' = \frac{\mu d}{w} \quad (7)$$

$$C' = \frac{\epsilon' w}{d} \quad (8)$$

$$R' = \frac{2R_s}{w} \quad (9)$$
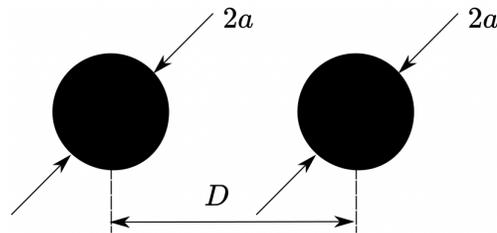
$$G' = \frac{\omega \epsilon'' w}{d} \quad (10)$$



$$L' = \frac{\mu}{\pi} \cosh^{-1} \frac{D}{2a} \quad (11)$$


$$C' = \frac{\pi \epsilon'}{\cosh^{-1} \frac{D}{2a}} \quad (12)$$

$$R' = \frac{R_s}{\pi a} \quad (13)$$

$$G' = \frac{\pi \omega \epsilon''}{\cosh^{-1} \frac{D}{2a}} \quad (14)$$

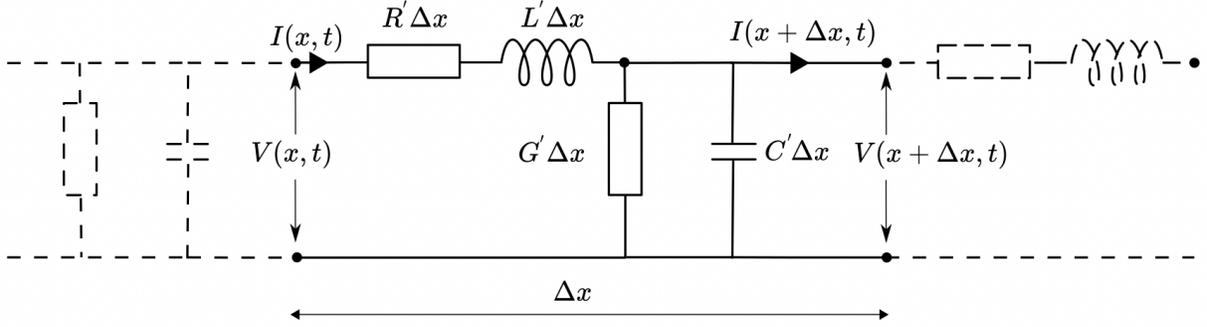III. TRANSMISSION LINES: GENERAL MODELS

- If the length of a circuit is $\gtrsim \lambda$ we have to use either a simulator of Maxwell's equations or a distributed model of lumped elements.
- Transmission lines: Two parallel conductors that guide the electromagnetic field. Examples: two-wire lines, striplines, microstrip lines.



R', L', G', C' = resistance, inductance, conductance, capacitance per unit length.

Kirchoff says:

$$\begin{cases} V(x, t) = I(x, t)R'\Delta x + L'\Delta x \cdot \frac{\partial I(x, t)}{\partial t} + V(x + \Delta x, t) \\ I(x, t) = V(x + \Delta x, t)G'\Delta x + C'\Delta x \frac{\partial V(x + \Delta x, t)}{\partial t} + I(x + \Delta x, t) \end{cases} \quad (15)$$

$$\Delta x \rightarrow 0 \begin{cases} -\frac{\partial V(x, t)}{\partial x} = R'I(x, t) + L'\frac{dI(x, t)}{dt} \\ -\frac{\partial I(x, t)}{\partial x} = G'V(x, t) + C'\frac{\partial V(x, t)}{\partial t} \end{cases} \quad (16)$$

Therefore,

$$\begin{cases} -\frac{\partial^2 V(x, t)}{\partial x^2} = -R'(G'V(x, t) + C'\frac{\partial V(x, t)}{\partial t}) - L'(G'\frac{\partial V(x, t)}{\partial t} + C'\frac{\partial^2 V(x, t)}{\partial t^2}) \\ -\frac{\partial^2 I(x, t)}{\partial x^2} = -G'(R'I(x, t) + L'\frac{\partial I(x, t)}{\partial t}) - C'(R'\frac{\partial I(x, t)}{\partial t} + L'\frac{\partial^2 I(x, t)}{\partial t^2}) \end{cases} \quad (17)$$

or

$$\begin{cases} \frac{\partial^2 V(x, t)}{\partial x^2} = L'C'\frac{\partial^2 V(x, t)}{\partial t^2} + (R'C' + L'G')\frac{\partial V(x, t)}{\partial t} + R'G'V(x, t) \\ \frac{\partial^2 I(x, t)}{\partial x^2} = L'C'\frac{\partial^2 I(x, t)}{\partial t^2} + (R'C' + L'G')\frac{\partial I(x, t)}{\partial t} + R'G'I(x, t) . \end{cases} \quad (18)$$

Harmonic signals:

$$V(x, t) = V(x)e^{i\omega t}, \quad V(x), I(x) = \text{phasors}, \quad I(x, t) = I(x)e^{i\omega t}$$

$$\implies \begin{cases} \frac{d^2 V(x)}{dx^2} - \gamma^2 V(x) = 0, & \text{where } \gamma = \alpha + i\beta = \sqrt{(R' + i\omega L')(G' + i\omega C')} \\ \frac{d^2 I(x)}{dx^2} - \gamma^2 I(x) = 0, & \gamma = \text{propagation constant, } \alpha = \text{attenuation constant, } \beta = \text{phase constant} \end{cases}$$

$$\text{General Solution: } V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x}. \quad (19)$$

From $-\frac{\partial V(x,t)}{\partial x} = RI(x,t) + L\frac{\partial I(x,t)}{\partial t}$, we get $I(x) = -\frac{1}{R+i\omega L} \frac{dV(x)}{dx}$ or $I(x) = \frac{1}{Z_0} V^+ e^{\gamma x} - \frac{1}{Z_0} V^- e^{-\gamma x} = I^+ e^{-\gamma x} + I^- e^{\gamma x}$, where

$$Z_0 = \sqrt{\frac{R' + i\omega L'}{G' + i\omega C'}} = \text{characteristic impedance of the transmission line,}$$

and where $I^\pm = \pm \frac{V^\pm}{Z_0}$.

Lossless transmission case: $R' = G' = 0$

$$\gamma = i\beta = i\omega\sqrt{L'C'}$$

$$Z_0 = \frac{1}{Y_0} = \sqrt{\frac{L'}{C'}} \rightarrow \text{now independent of frequency!}$$

Note: Free-space impedance = 377Ω

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}} = \text{phase velocity.}$$

Exercise: Show that for the loss-less case $R \ll \omega L$, $G \ll \omega C$, we have $\beta \simeq \omega\sqrt{L'C'}$ and $\alpha \simeq \frac{1}{2}\sqrt{L'C'}(\frac{R'}{L'} + \frac{G'}{C'})$.


- Standardized values:

Z_0	Application
50 Ω	Instrumentation, communication
75 Ω	TV, VHF radio
300 Ω	RF
600 Ω	Audio

- Incident and Reflected Waves Along a Loaded Transmission Line

$$V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x}$$
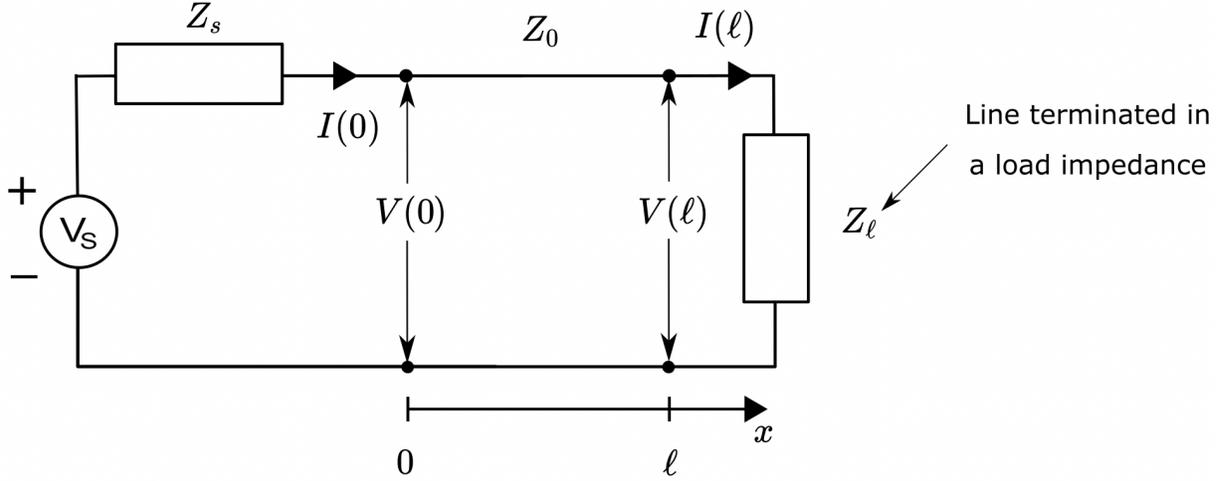
$$I(x) = I^+ e^{-\gamma x} + I^- e^{\gamma x}, \quad I^\pm = \pm \frac{V^\pm}{Z_0}$$



$$\begin{cases} V(0) = V_s - Z_s I(0) \text{ --- Kirchoff's law} \\ V(\ell) = Z_\ell I(\ell) , \end{cases} \quad (20)$$

or

$$\begin{cases} V^+ + V^- = V_s - \frac{Z_s}{Z_0}(V^+ + V^-) \\ V^+ e^{-\gamma \ell} + V^- e^{\gamma \ell} = \frac{Z_\ell}{Z_0}(V^+ e^{-\gamma \ell} - V^- e^{\gamma \ell}) \end{cases} \quad (21)$$

- Define a reflection coefficient of the load at $x = \ell$: $\Gamma_V = \frac{V^- e^{\gamma \ell}}{V^+ e^{-\gamma \ell}}$.

$$\rightarrow 1 + \Gamma_V = \frac{Z_\ell}{Z_0}(1 - \Gamma_V).$$

$$\implies \Gamma_V = \frac{Z_\ell - Z_0}{Z_\ell + Z_0} \quad (22)$$

We can also define a current reflection coefficient at the load

$$\Gamma_I = \frac{I^- e^{\gamma \ell}}{I^+ e^{-\gamma \ell}} = -\Gamma_V \quad (23)$$

- Define the transmission coefficient at the load $x = \ell$: $T_V = \frac{V^+ e^{+\ell} + V^- e^{-\gamma \ell}}{V^+ e^{-\gamma \ell}}$.

$$\therefore T_V = 1 + \Gamma_V , \quad (24)$$

and for the current

$$T_I = \frac{I^+ e^{-\gamma \ell} + I^- e^{\gamma \ell}}{I^+ e^{-\gamma \ell}} = 1 + \Gamma_I . \quad (25)$$

- Average power delivered to the load

$\overline{P}_\ell = \frac{1}{2}\text{Re}[V(\ell)I^*(\ell)]$, where the 1/2 comes from the fact that the field is harmonic.

Now,

$$\begin{cases} 1 - \Gamma_V = \frac{I^- e^{\gamma\ell} + I^+ e^{-\gamma\ell}}{I^+ e^{-\gamma\ell}} = \frac{I(\ell)}{I^+ e^{-\gamma\ell}} \\ 1 + \Gamma_V = \frac{V^+ e^{-\gamma\ell} + V^- e^{-\gamma\ell}}{V^+ e^{-\gamma\ell}} = \frac{V(\ell)}{V^+ e^{-\gamma\ell}} \end{cases} \quad (26)$$


$$\therefore (1 + \Gamma_V^*)(1 + \Gamma_V) = \frac{V(\ell)I^*(\ell)}{I^+ V^+ e^{-\gamma\ell} (e^{-\gamma\ell})^*}, \text{ but } I^+ = \frac{V^+}{Z_0}$$

$V(\ell)I^*(\ell) = \frac{1}{Z_0} |V^+ e^{-\gamma\ell}|^2 \cdot (1 - \Gamma_V^*)(1 + \Gamma_V) \equiv 1 - \Gamma_V^* + \Gamma_V - |\Gamma_V|^2$, where $\Gamma_V^* + \Gamma_V = \text{Imaginary!}$.

$$\overline{P}_\ell = \frac{1}{2Z_0} \cdot |V^+ e^{-\gamma\ell}|^2 (1 - |\Gamma_V|^2). \quad (27)$$

- VSWR (Voltage standing-wave ratio)
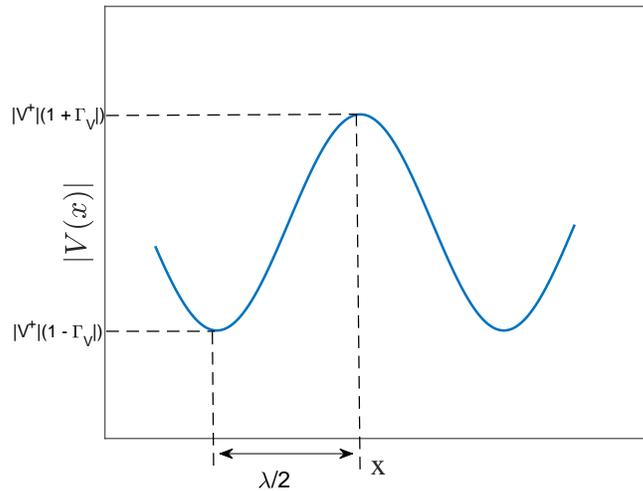
$$V(x) = V^+ e^{-\gamma x} + V^- e^{\gamma x} = V^+ e^{-\gamma x} [1 + \Gamma_V e^{-2\gamma(\ell-x)}] \quad (\text{Remember that } \Gamma_V \equiv \frac{V^- e^{\gamma\ell}}{V^+ e^{-\gamma\ell}}.)$$



Let's consider a lossless line $\alpha = 0$, $\gamma = i\beta = \frac{2\pi i}{\lambda}$

$|V(x)| = |V^+| \cdot |1 + \Gamma_V e^{-2i\beta(\ell-x)}|$ — oscillates, min. and max. separated by $\frac{\pi}{\beta} = \frac{\lambda}{2}$.

$VSWR = \frac{1+|\Gamma_V|}{1-|\Gamma_V|}$ = ratio between the max. line voltage and min. line voltage.

- Impedance along the line

$$Z(x) = \frac{V(x)}{I(x)} = Z_0 \frac{V^+ e^{-\gamma x} + V^- e^{\gamma x}}{V^+ e^{-\gamma x} - V^- e^{\gamma x}} = \frac{1 + \Gamma_V e^{-2\gamma(\ell-x)}}{1 - \Gamma_V e^{-2\gamma(\ell-x)}}.$$


Take $x = 0 \rightarrow$ we get $Z(0) \equiv Z_{in} =$ input impedance of the line, i.e., the impedance seen when looking toward the load.

$$Z_{in} = Z_0 \cdot \frac{Z_\ell + Z_0 \tanh \gamma \ell}{Z_0 + Z_\ell \tanh \gamma \ell} \quad (28)$$

Note that this can be verified immediately by recalling that $\Gamma_V = \frac{Z_\ell - Z_0}{Z_\ell + Z_0}$, and that in general, $Z_{in} \neq Z_0$, so the termination matters! Also, Z_{in} is frequency-dependent.

IV. EXAMPLES OF LOADS (TERMINATIONS)

1. Matched Load

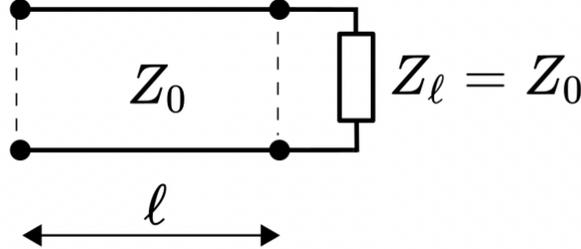


$$Z_\ell = Z_0 \implies \Gamma_V \equiv \frac{Z_\ell - Z_0}{Z_\ell + Z_0} = 0 \quad \text{No reflection!}$$

$\text{VSWR} = 1$, $Z_{in} = Z_0$, $P_\ell = \frac{1}{2Z_0} |V^+|^2 e^{-2\alpha \ell}$ — power delivered is maximum.
This is only obtained if $\alpha \neq 0$.


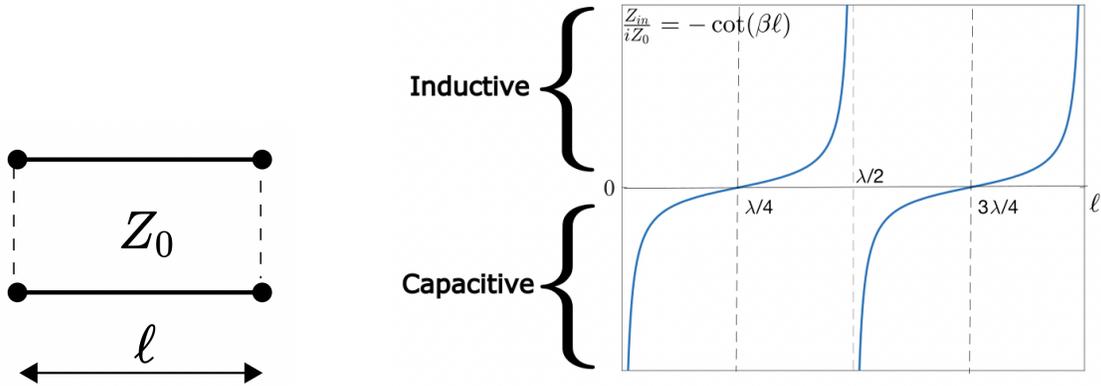
2. Open-Circuit $Z_\ell = \infty \implies \Gamma_V = \frac{Z_\ell - Z_0}{Z_\ell + Z_0} = 1$

$\text{VSWR} = \infty$, $Z_{in} = Z_0 \coth \gamma \ell$, $P_\ell = 0$ — Compare this with the DC-case where all the input power is delivered!

For $\alpha = 0$ (lossless), $Z_{in} = -iZ_0 \cot \frac{2\pi \ell}{\lambda}$ if $\ell = \frac{\lambda}{4}$, $Z_{in} = 0$, so the open line will look as a shortcut!



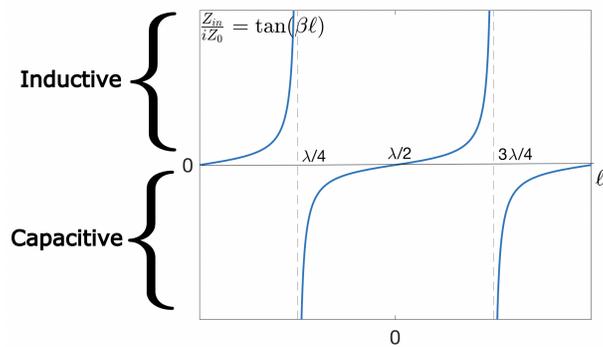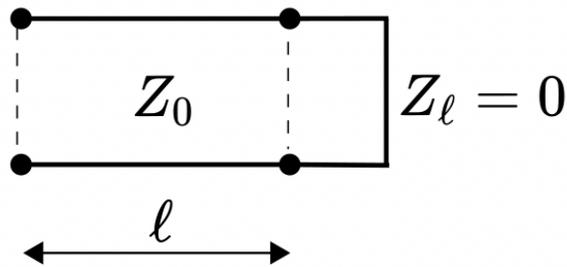3. Short-circuit $Z_\ell = 0 \implies \Gamma_V = \frac{Z_\ell - Z_0}{Z_\ell + Z_0} = -1$,




$$\text{VSWR} = \infty, \quad Z_{in} = Z_0 \tanh \gamma \ell, \quad P_\ell = 0.$$

For $\alpha = 0$ (lossless), $\beta = \frac{2\pi}{\lambda}$ quad $Z_{in} = iZ_0 \tan \frac{2\pi\ell}{\lambda}$ — If $\ell = \frac{\lambda}{4}$, $Z_{in} = \infty$, so the shorted line looks like an infinite impedance to a source! (even if the resistance of the wire is zero!)

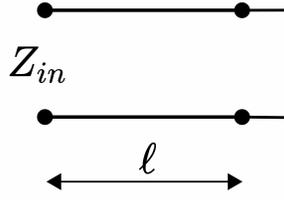V. RESONATORS FROM TRANSMISSION LINES

- It is possible to make resonators from transmission lines, 3D cavities, etc.
- The most usual case is the short-circuited transmission-line resonator.

$$Z_\ell = 0, \quad Z_{in} = Z_0 \tanh(\alpha\ell - i\beta\ell) = Z_0 \frac{\tanh \alpha\ell + i \tan \beta\ell}{1 + i \tan \beta\ell \tanh \alpha\ell}.$$



If losses are not too large, $\alpha\ell \ll 1$, we have $\tanh \alpha\ell \approx \alpha\ell$, so

$$Z_{in} = Z_0 \frac{\alpha\ell + i \tan \beta\ell}{1 + i\alpha\ell \tan \beta\ell}. \quad (29)$$

Now, recall that $\beta = \omega/v_p = \omega\sqrt{L'C'}$, $v_p = 1/\sqrt{L'C'}$, $Z_0 = \sqrt{L'/C'}$, $\alpha = \frac{R'}{2}\sqrt{C'/L'}$.

We will consider $\beta_0\ell = \pi$, or $\ell = \lambda_0/2$ as the resonance condition, leading to a resonance frequency ω_0 .


$$\frac{\omega_0}{v_p}\ell = \omega_0\sqrt{L'C'}\ell = \pi, \text{ so } \omega = \frac{\pi}{\ell\sqrt{L'C'}}.$$

We can expand this around this point: $\tan \beta\ell \simeq \tan(\pi + \pi\frac{\omega-\omega_0}{\omega_0}) = \tan \pi\frac{\omega-\omega_0}{\omega_0} \simeq \pi\frac{\omega-\omega_0}{\omega_0}$, if $|\omega - \omega_0| \ll \omega_0$.

$$\begin{aligned} \text{So, } Z_{in} &= Z_0 \frac{\alpha\ell + i\pi\frac{\omega-\omega_0}{\omega_0}}{1 + \alpha\ell\pi\frac{\omega-\omega_0}{\omega_0}} \simeq Z_0(\alpha\ell + i\pi\frac{\omega-\omega_0}{\omega_0}) \\ &= \sqrt{L'/C'}(\frac{\ell}{2}R'\sqrt{C'/L'} + i\ell\sqrt{L'C'}(\omega - \omega_0)) = \frac{1}{2}R'\ell + iL'\ell(\omega - \omega_0). \end{aligned}$$

- Suppose now that we look back at the series RLC circuit
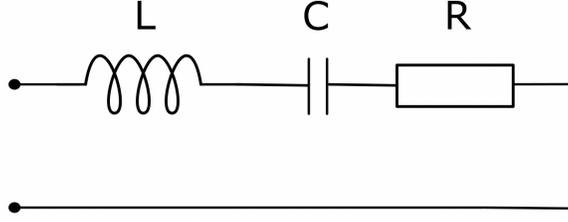
$$Z = R + i\frac{L}{\omega}(\omega^2 - \omega_0^2) \simeq R + 2iL(\omega - \omega_0) \text{ near resonance, } \omega \simeq \omega_0.$$



Therefore, we can identify $R = \frac{1}{2}R'\ell$ and $L = \frac{1}{2}L'\ell$.

$$\text{Quality Factor } Q = \frac{\omega_0 L}{R} = \frac{\omega_0 L'}{R'} = \frac{\beta_0}{2\alpha}. \quad (30)$$

- Interesting question to think about: Why do we get the factor 1/2 in the RLC equivalent above?
- Answer: Because the current in the short-circuited line is half a sinusoid, therefore we obtain only half of the total resistance and inductance of the full length ℓ .

To see this explicitly, let us write the solution

$$\begin{cases} V(x) \simeq V^+ e^{-i\beta x} + V^- e^{i\beta x} \text{ — here we neglect } \alpha. \\ I(x) \simeq -\frac{\beta}{\omega L} (-V^+ e^{-i\beta x} + V^- e^{i\beta x}) \end{cases} \quad (31)$$

Since $I(0) = 0 \implies V^+ \equiv V^-$ at this point (also you can see that $\Gamma_V \equiv \frac{V^-}{V^+} e^{2i\beta_0 \ell} = -1$ and $\beta_0 \ell = \pi$).

So

$$\begin{cases} V(x) = 2V^+ \cos \beta_0 x \\ I(x) = -\frac{2i\beta}{\omega L} V^+ \sin \beta_0 x = I^+ \sin \beta_0 x. \end{cases} \quad (32)$$

Therefore the magnetic-field energy:

$$\overline{W}_{L'} = \int_0^{\lambda_0/2} dx \cdot \frac{1}{4} L' |I(x)|^2 = \frac{1}{4} |I^+|^2 L' \int_0^{\lambda_0/2} \sin^2 \beta_0 x dx = \frac{\lambda_0}{16} \cdot |I^+|^2 L'. \quad (33)$$

At resonance: $\overline{W_{C'}} = \overline{W_{L'}}$, so

$$\overline{W} = \overline{W_{C'}} + \overline{W_{L'}} = \frac{\lambda_0}{8} L' |I^+|^2. \quad (34)$$

$$\overline{P} = \frac{1}{2} \int_0^{\lambda_0} dx \cdot R' |I(x)|^2 = \frac{R'}{2} |I^+|^2 \int_0^{\lambda_0} \sin^2 \beta_0 x dx,$$

so

$$\overline{P} = \frac{\lambda_0}{8} R' |I^+|^2. \quad (35)$$

Therefore,

$$Q = \frac{\omega_0 \overline{W}}{\overline{P}} = \frac{\omega L'}{R'}, \quad (36)$$

or: $Q = \frac{\pi}{\ell R'} \sqrt{\frac{L'}{C'}} = \frac{\pi Z_0}{\ell R'} = \frac{\pi}{2\ell\alpha}$, where we used $\alpha \simeq \frac{R}{2Z_0}$, $\omega_0 = \frac{\pi}{\ell \sqrt{L' C'}}$.

References

- David M. Pozar — Microwave Engineering.
- R.E. Collin — Foundations for Microwave Engineering.