



Aalto University
School of Electrical
Engineering

Lecture 6: DC-DC Conversion

ELEC-E8405 Electric Drives (5 ECTS)

Marko Hinkkanen

Autumn 2022

Learning Outcomes

After this lecture and exercises you will be able to:

- ▶ Explain basic operating principles of switched DC-DC conversion
- ▶ Draw the equivalent circuit of a 4-quadrant DC-DC converter
- ▶ Implement a simple pulse-width modulator in the Simulink software

Outline

Introduction


Buck Converter

4-Quadrant DC-DC Converter

Unipolar Pulse-Width Modulation



Synchronous Sampling

Symbol Used for the DC Motor


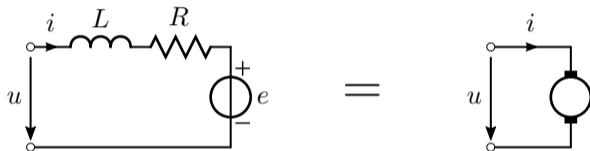


Introduction

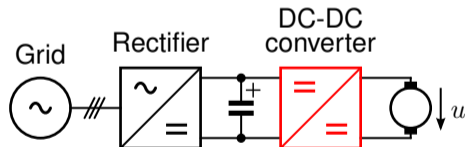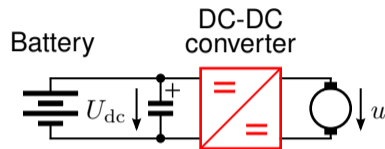- ▶ DC source voltage U_{dc} is typically a battery or a diode bridge
- ▶ Voltage u has to be adjusted in order to be able to control the speed and torque
- ▶ Topologies and control of DC-DC converters are very similar to those of three-phase inverters





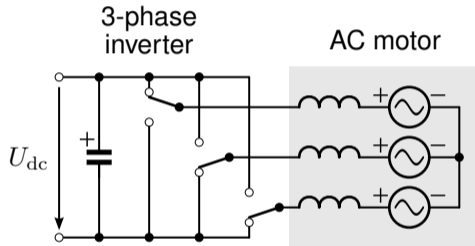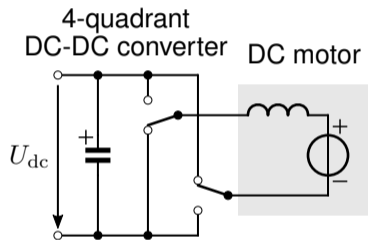DC-DC Converters Are Similar to 3-Phase Inverters



Why Not Linear Voltage Regulation?

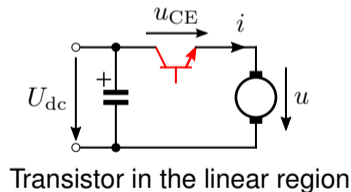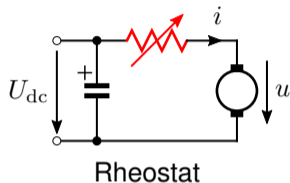- ▶ In principle, u could be adjusted using a rheostat or a transistor in the linear region
- ▶ What would be the efficiency if $U_{dc} = 100\text{ V}$ and $u = 50\text{ V}$? What would be the losses in the transistor if $i = 10\text{ A}$?
- ▶ Why **linear voltage regulation does not work** in practice (except in very low-power drives)?



Outline

Introduction

Buck Converter


4-Quadrant DC-DC Converter

Unipolar Pulse-Width Modulation

Synchronous Sampling

Switched-Mode DC-DC Conversion

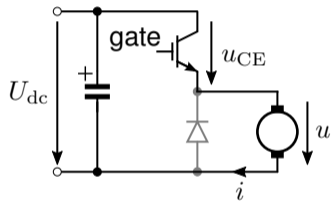- ▶ To avoid high losses, the transistor is **switched periodically on and off**
- ▶ Typical power semiconductors: IGBT, MOSFET, thyristor, GTO
- ▶ We will assume ideal switches
- ▶ Typical switching frequencies $f_{sw} = 1 \dots 50 \text{ kHz}$
- ▶ Figure shows a buck converter (step-down converter)





Buck Converter




- ▶ Low power loss $u_{CE}i_C$ in the transistor


On-state: $u_{CE} \approx 0$

Off-state: $i_C = 0$

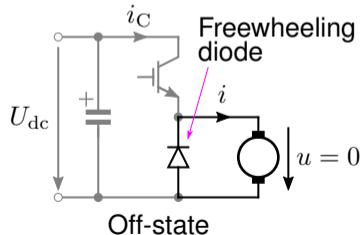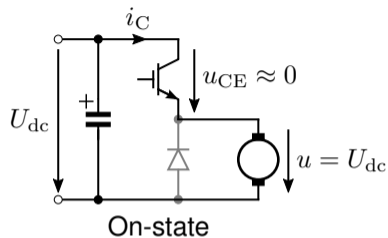- ▶ Motor is an inductive load
 - ▶ Current i must flow even when the transistor is switched off
 - ▶ Freewheeling diode is needed
- ▶ Next we will consider short time periods
 - ▶ $e = \text{constant}$ and $R = 0$ can be assumed



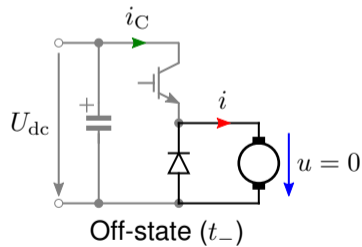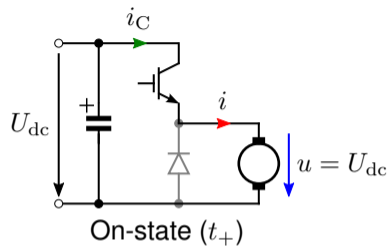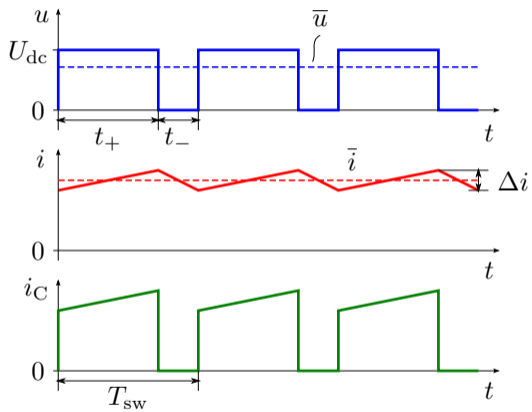

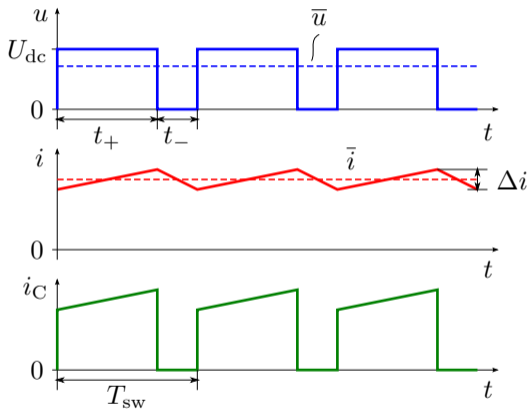

► **Duty cycle**

$$d = \frac{t_+}{T_{sw}} \quad 0 \leq d \leq 1$$

- t_+ is the on-time
- T_{sw} is the switching period
- **Average** of the voltage u **over** the period T_{sw}

$$\begin{aligned} \bar{u} &= \frac{1}{T_{sw}} \int_0^{T_{sw}} u \, dt \\ &= dU_{dc} \end{aligned}$$

Current Ripple

- ▶ Voltage equation


$$L \frac{di}{dt} = u - e$$

- ▶ On-state: $u = U_{dc}$

$$\begin{aligned} \Delta i &= \frac{1}{L} \int_0^{t_+} (U_{dc} - e) dt \\ &= \frac{(U_{dc} - e)t_+}{L} \end{aligned}$$

- ▶ Off-state: $u = 0$
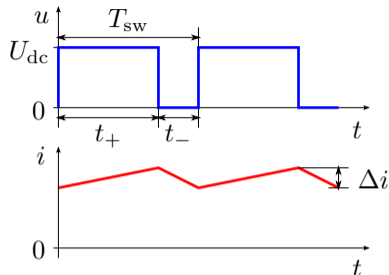
$$-\Delta i = \frac{1}{L} \int_0^{t_-} (-e) dt = -\frac{et_-}{L}$$



- ▶ Duty ratio in steady state

$$d = \frac{t_+}{T_{sw}} = \frac{\bar{u}}{U_{dc}} \quad (\bar{u} = \bar{e} \text{ if } R = 0)$$

- ▶ Current ripple in steady state

$$\Delta i = \frac{d(1-d)U_{dc}}{f_{sw}L}$$

Maximum Current Ripple

- ▶ Maximum ripple with $d = 1/2$ (at about half base speed)

$$\Delta i_{\max} = \frac{U_{\text{dc}}}{4f_{\text{sw}}L}$$

- ▶ Example parameter values for a 1-kW DC motor

$$L = 50 \text{ mH} \quad U_{\text{dc}} = 100 \text{ V} \quad f_{\text{sw}} = 5 \text{ kHz} \quad \Rightarrow \quad \Delta i_{\max} = 0.1 \text{ A}$$

- ▶ If the rated current is 10 A, the current ripple is only 1% (5 kHz is not a high switching frequency at 1-kW power level)
- ▶ Current ripple Δi and torque ripple $\Delta \tau_{\text{M}} = k_{\text{f}} \Delta i$ are typically insignificant

Outline

Introduction

Buck Converter


4-Quadrant DC-DC Converter

Unipolar Pulse-Width Modulation

Synchronous Sampling

Four Quadrants

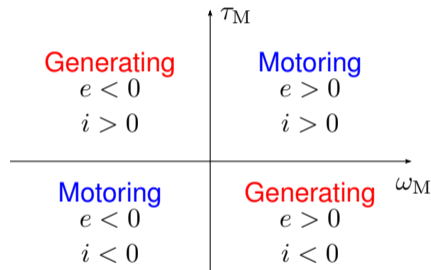- ▶ Back-emf $e = k_f \omega_M$
- ▶ Torque $\tau_M = k_f i$
- ▶ Mechanical power $p_M = \omega_M \tau_M = ei$
- ▶ Converter should allow both its output voltage $u \approx e$ and current i to reverse in 4-quadrant operation




4-Quadrant DC-DC-Converter

S₁ and S₄ switched ON: $u = U_{dc}$

S₂ and S₃ switched ON: $u = -U_{dc}$


S₁ and S₃ switched ON: $u = 0$

S₂ and S₄ switched ON: $u = 0$

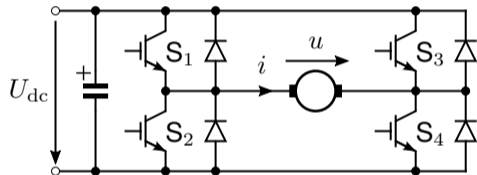


Operation Modes

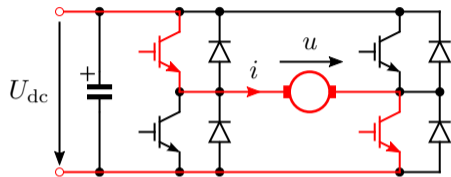
Only Nonzero Voltage Switching States Are Shown




$$u = U_{dc}, \quad i > 0$$

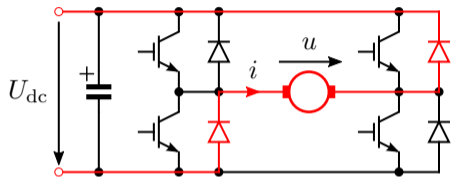

$$u = -U_{dc}, \quad i > 0$$

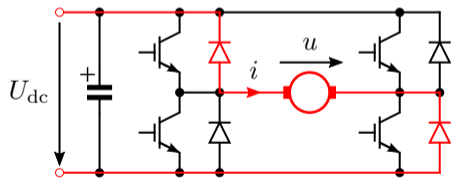

$$u = U_{dc}, \quad i < 0$$


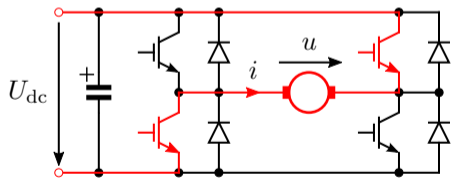


$$u = -U_{dc}, \quad i < 0$$

Notation of Potentials and Voltages

- ▶ Legs can be modelled as bi-positional switches
- ▶ Negative DC-bus potential **N**
- ▶ u_{AN} is the voltage between potentials **A** and **N**
- ▶ u_{BN} is the voltage between potentials **B** and **N**
- ▶ Converter output voltage

$$u = u_{AN} - u_{BN}$$

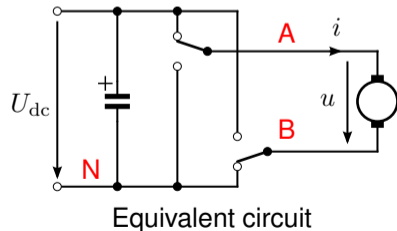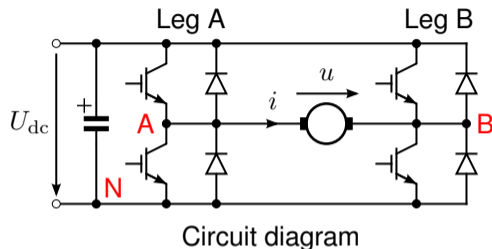

Switching States of the Bi-Positional Switches

- ▶ Switching state q
 - ▶ $q = 0$ if the switch is connected to **N**
 - ▶ $q = 1$ if the switch is connected to **P**


- ▶ Pole voltages

$$u_{AN} = q_A U_{dc} \quad u_{BN} = q_B U_{dc}$$

- ▶ Converter output voltage

$$u = (q_A - q_B) U_{dc}$$

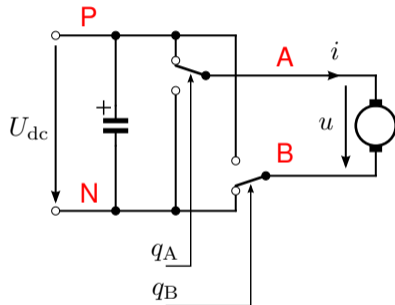- ▶ Figure: $q_A = 1$ and $q_B = 0$, giving $u = U_{dc}$




Switching-Cycle Averaged Quantities

- ▶ Average pole voltage over T_{sw}

$$\bar{u}_{AN} = \frac{1}{T_{sw}} \int_0^{T_{sw}} u_{AN} dt = d_A U_{dc}$$

- ▶ Average voltage \bar{u}_{BN} is obtained similarly
- ▶ Average output voltage

$$\bar{u} = (d_A - d_B) U_{dc}$$

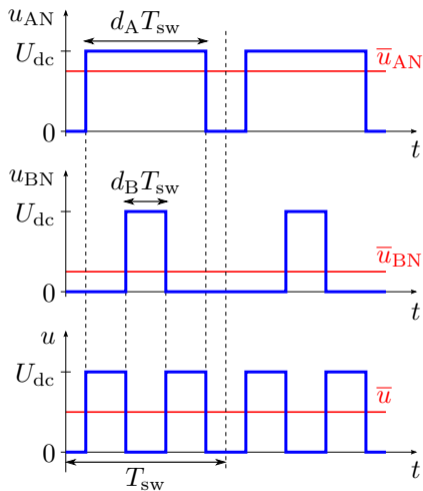

Outline

Introduction

Buck Converter


4-Quadrant DC-DC Converter

Unipolar Pulse-Width Modulation

Synchronous Sampling

Pulse-Width Modulation

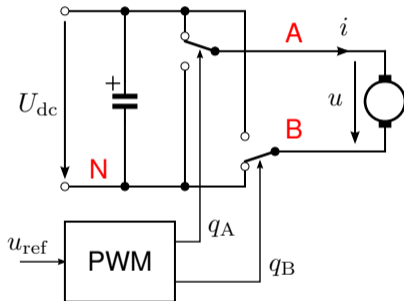- ▶ PWM generates the control signals q_A and q_B for the power switches
- ▶ Goal: switching-cycle averaged voltage \bar{u} equals the reference voltage u_{ref}
- ▶ Various PWM methods exist: they all give $\bar{u} = u_{\text{ref}}$ but produce different pulse patterns
- ▶ **Unipolar PWM** will be considered in the following




Duty Cycles

- Conditions $\bar{u} = u_{\text{ref}}$ and $d_A + d_B = 1$ lead to the duty cycles

$$d_A = \frac{1}{2} \left(1 + \frac{u_{\text{ref}}}{U_{\text{dc}}} \right)$$


$$d_B = \frac{1}{2} \left(1 - \frac{u_{\text{ref}}}{U_{\text{dc}}} \right)$$

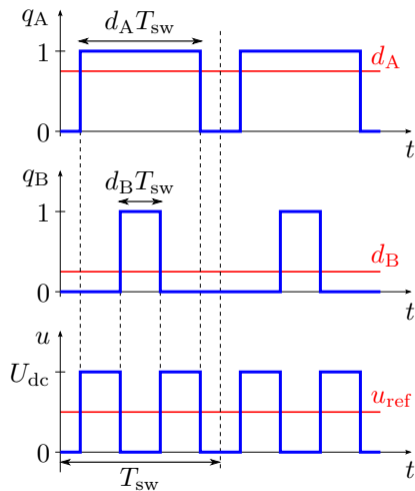- Example in the figure: $u_{\text{ref}} = 0.5U_{\text{dc}}$
- What are the duty cycles d_A and d_B ?
- How to generate the control signals q_A and q_B ?




Carrier Comparison

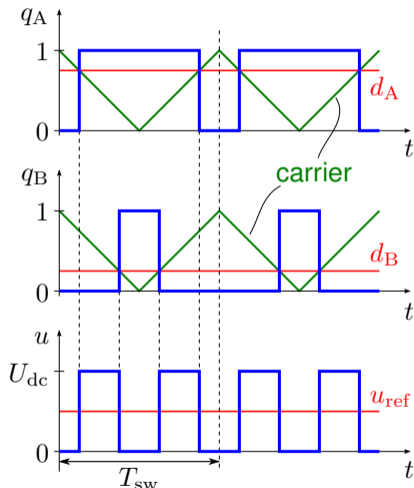- ▶ Carrier comparison is often used for generating the control signals
 - ▶ Triangular carrier with the period T_{sw}
 - ▶ Magnitude varies between 0 and 1
- ▶ If d is higher than the carrier, then $q = 1$ (otherwise $q = 0$)
- ▶ Same carrier for both d_A and d_B
- ▶ Next slide: step change in the voltage reference ($-0.5U_{dc} \rightarrow 0.75U_{dc}$)




There are various ways to scale the carrier waveform and the reference quantities. Using the carrier varying between 0 and 1 together with the duty cycle references is convenient in digital implementation.

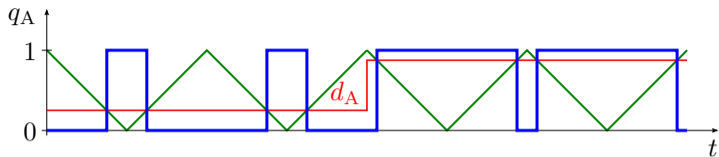
$$d_A = \frac{1}{2} \left(1 + \frac{u_{\text{ref}}}{U_{\text{dc}}} \right)$$


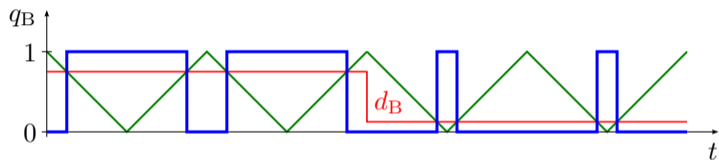
$$d_B = \frac{1}{2} \left(1 - \frac{u_{\text{ref}}}{U_{\text{dc}}} \right)$$



$$\bar{u} = (d_A - d_B)U_{\text{dc}}$$

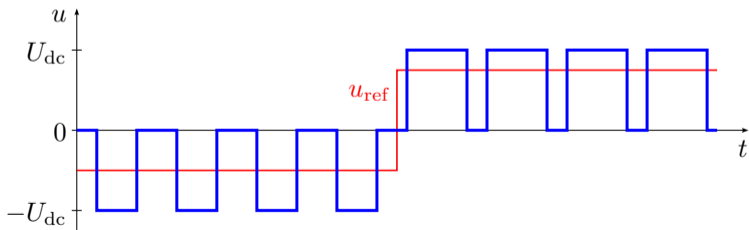

Outline

Introduction

Buck Converter


4-Quadrant DC-DC Converter

Unipolar Pulse-Width Modulation

Synchronous Sampling

Digital Controller

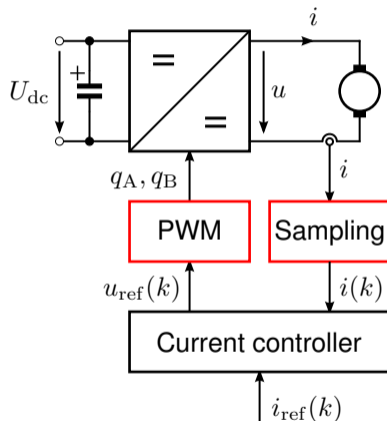- ▶ Current is measured for the feedback of the current controller
- ▶ Digital controllers are used nowadays
- ▶ Sampling of the current is typically synchronized with the PWM
- ▶ Synchronised sampling effectively removes the current ripple from the samples




Synchronous Sampling

- ▶ Voltage reference u_{ref} can be updated in the beginning and in the middle of the carrier (marked with the circles)
- ▶ Current samples (circles) can be taken at these same time instants
- ▶ Next slide: Current response is governed by

$$L \frac{di}{dt} = u - e$$

where $R = 0$ is assumed

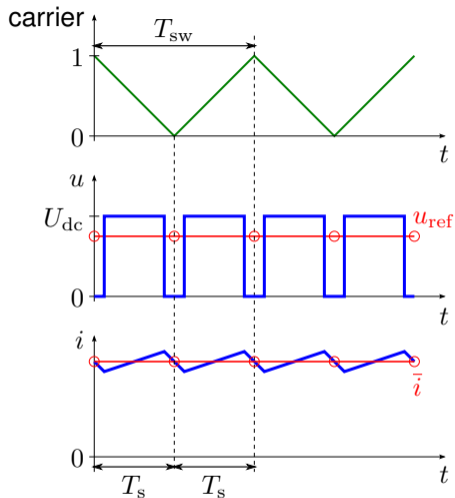

Different variants of sampling synchronized with the PWM exist, while only one is presented here. Furthermore, it can be noticed that actually four current samples per carrier period could be taken without the current ripple in the case of the unipolar PWM.

