

**EX 1 wye and delta connections**

The phase voltage of a wye connected 3-phases source is  $\bar{V}_{an} = 230\angle -40^\circ$ . The source is feeding a delta connected 3-phases load, the impedance of which is  $\bar{Z} = 10\angle -30^\circ$ .

- a. Draw the circuit sketch of this situation
- b. calculate the line-to-line voltages of the source ( $\bar{V}_{ab}, \bar{V}_{bc}, \bar{V}_{ca}$ ) and the phase currents of the load ( $\bar{I}_{ab}, \bar{I}_{bc}, \bar{I}_{ca}$ )

**EX 2 impedances**

The phase voltage of a wye connected 3-phases source is  $\bar{V}_{an} = 230\angle 0^\circ$ . The source is feeding a delta connected 3-phases load, the impedance of which is unknown. The measurement of the c-phase current gives  $\bar{I}_c = 10\angle 75^\circ$ . Calculate the load impedance, i.e., the impedance of one branch of the delta connected load.