

EX 1: Buck-Converter

The dc input voltage of a buck (step-down) converter is 24 V and the desired dc output voltage is 16.8 V. Assume the converter lossless and omit the ripple in the output voltage (i.e., large filter capacitance)

- a) Draw the circuit diagram of the converter
- b) Draw the waveforms of the inductor voltage, the inductor current, and the input current below each other
- c) Calculate the IGBT duty ratio, the average input current, the average output current, and the peak-to-peak ripple in the inductor current. The inductance is 0.1 mH, the output power is 28 W, and the switching frequency is 200 kHz.

EX 2: Boost-Converter

The supply voltage of a step-up converter is 25 V and the output voltage is 40 V. The switching frequency is 1 kHz and the load resistance 100 Ω . Calculate

- a) The peak-to-peak change in the inductor current when $L = 30$ mH
- b) The average of the load current
- c) The power of the load

EX 3 & 4 DC-AC-Converter

A three-phase dc/ac converter is used to supply a star-connected load, where each phase has a 10 Ω resistance. The dc-voltage is 540 V and the inverter works under full control producing the maximum output voltage. This means that each phase is connected half of the time to the positive dc-bus and half of the time to the negative bus. There is 120 degrees phase shift between the phases

- a) Draw the status of the switches in the converter and under these the waveforms of the line currents and phase voltages
- b) Draw the waveform of the line-to-line voltage
- c) The value of the current taken from the dc-bus
- d) The rms value of the phase current
- e) The rms values of the phase and line-to-line voltages