

EX 1 Equivalent circuit

We consider a 14 kV, 10 MVA, 50 Hz, 2 poles, star-connected generator. The generator is running at its rated condition (rated current and complex power) at a lagging power factor of 0.85.

- a) calculate the real (active) and imaginary (reactive) power of the generator (P and Q)
- b) Calculate the rated current of the generator and write it as a phasor (complex number)
- c) The equivalent circuit of the synchronous generator with a typical phasor diagram is shown in the figure below. $X_s = 20\Omega$ per phase and the resistance can be neglected. Use the equivalent circuit and calculate the excitation voltage E_f (complex number).
- d) Under a request from the grid operator, to increase the reactive power, the excitation voltage is increased by 10%, while the active power is kept at its previous value. Calculate the new value of the load angle
- e) calculate the new value of the current (amplitude and phase)
- f) calculate the new value of the reactive power
- g) Is this an operation point of the generator in which it can run continuously? why?

Below is a figure for the reactive power control of the synchronous machine and some equations that might help to solve the exercise


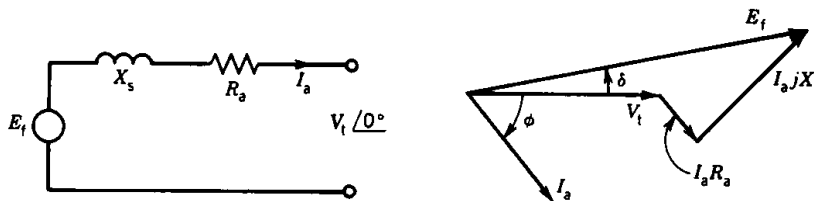


Figure: equivalent circuit of a synchronous generator and a typical phasor diagram.

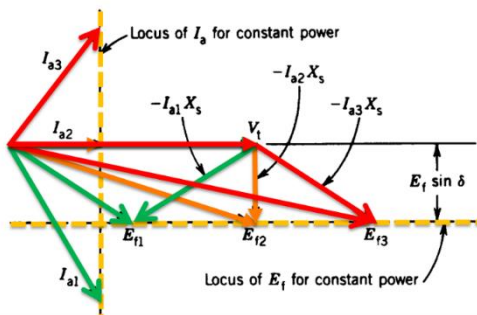

$$P = 3V_t I_a \cos \phi$$

$$P = 3 \frac{V_t E_f}{X_s} \sin \delta$$

