

Homework 2 - **Lecture 2** (3-phases system)

A 3-phases source is feeding two parallel connected 3-phase loads. Both loads are wye-connected. The current of the first load is 20 A and its power factor is 0,9 leading (capacitive). The current of the second load is 30 A and its power factor is 0,8 lagging (inductive).

- a. Draw the sketch of the 3-phases circuit and its corresponding single-phase equivalent circuit
- b. Calculate the line current of the source.
- c. Calculate the power factor of the whole load (it is not the average of the two
 $0,5 \cdot (0,8 + 0,9) = 0,85!$)