

Homework 6 – Converters:

A buck–boost converter with an input voltage of 40 V is used to regulate the load voltage from 10 to 80 V. The on-time of the transistor is always fixed at 0.1 ms and the switching frequency is adjusted to regulate the load voltage. Compute the range of the switching frequency.