

Homework 11 – Transformers:

Draw the equivalent circuit of a transformer and explain the function of its different components.
Use the primary side as a reference.