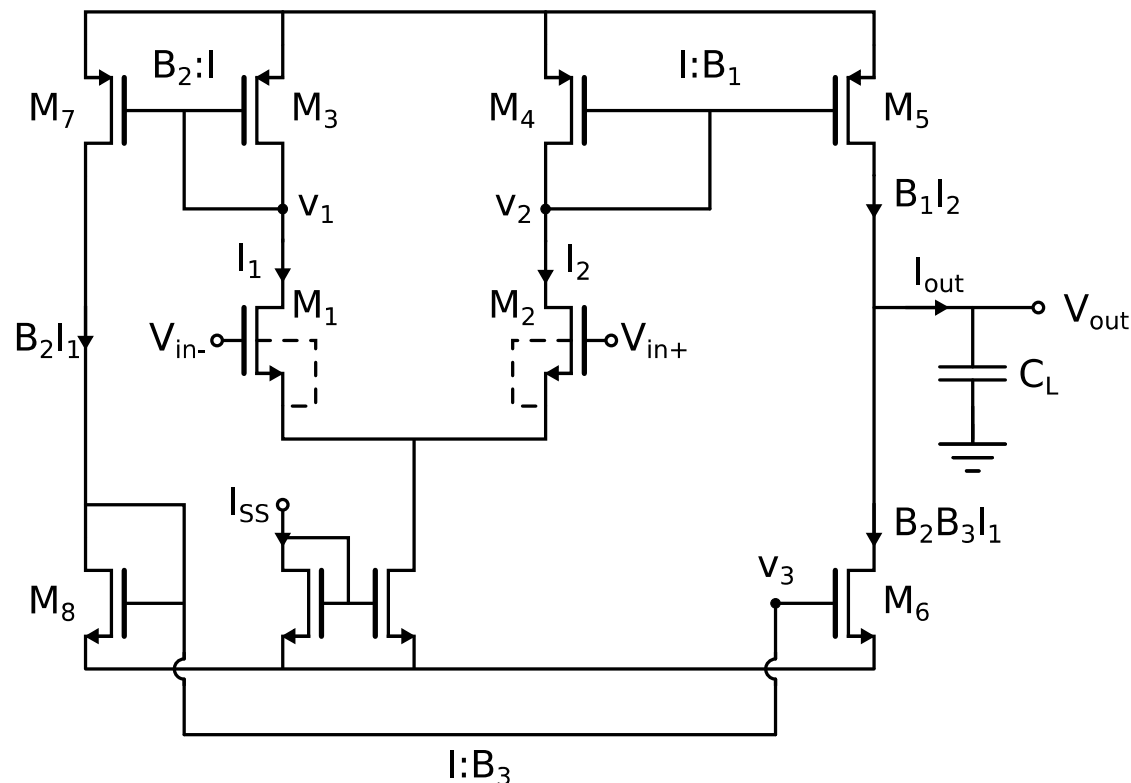


ELEC-E3510 Basics of IC Design

Lecture 5: OTA Amplifiers

OTA – Operational Transconductance Amplifier



Symmetrical input stage:

$$M1 \equiv M2 \quad \text{and} \quad M3 \equiv M4$$

Current mirrors:

$$M4 \& M5 \Rightarrow I_5 = \frac{(W/L)_5}{(W/L)_4} \cdot I_4 = \frac{g_{m5}}{g_{m4}} \cdot I_4 = B_1 \cdot I_4$$

$$M3 \& M7 \Rightarrow I_7 = \frac{(W/L)_7}{(W/L)_3} \cdot I_3 = \frac{g_{m7}}{g_{m3}} \cdot I_3 = B_2 \cdot I_3$$

$$M8 \& M6 \Rightarrow I_6 = \frac{(W/L)_6}{(W/L)_8} \cdot I_8 = \frac{g_{m6}}{g_{m8}} \cdot I_8 = B_3 \cdot I_8$$


Required:

$$B_1 = B_2 \cdot B_3$$

if $M5 \equiv M7$ and $M8 \equiv M6$

$$\Rightarrow B_2 \equiv B_1 \quad \text{and} \quad B_3 = 1$$

OTA transconductance and gain

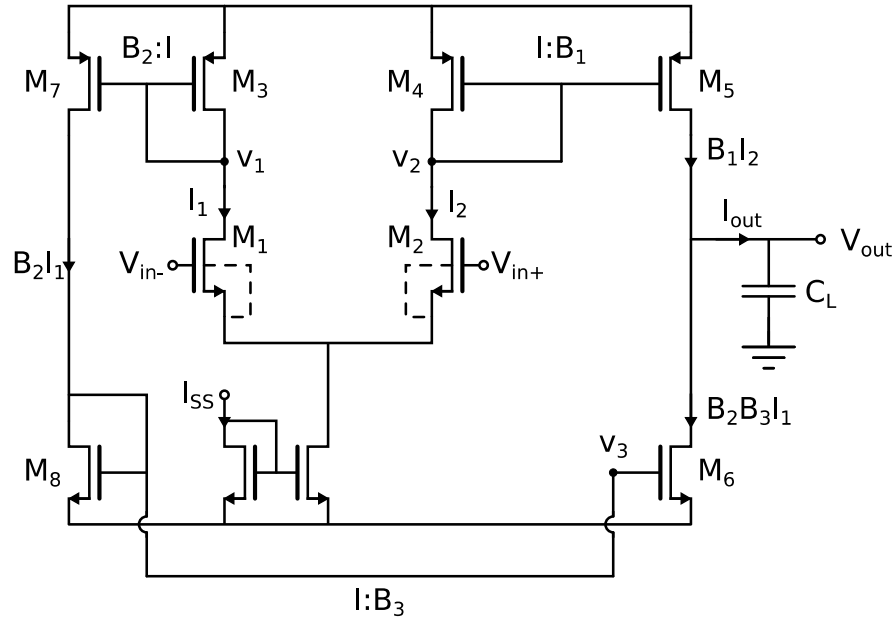

OTA transforms the input voltage difference to the output current:

$$I_1 - I_2 = g_{m1} \cdot \Delta V_{in}$$

$$I_5 = B_1 \cdot I_2$$

$$I_7 = B_2 \cdot I_3 = B_2 \cdot I_1$$

$$I_6 = B_3 \cdot I_8 = B_3 \cdot I_7 = B_2 \cdot B_3 \cdot I_1$$

$$I_{OUT} = I_5 - I_6 = B_1 \cdot I_2 - \underbrace{B_2 \cdot B_3 \cdot I_1}_{B_1} = B_1 \cdot (I_2 - I_1)$$

$$= -B_1 \cdot g_{m1} \cdot \Delta V_{in}$$

Transconductance of OTA:

$$\Rightarrow g_m = B_1 g_{m1}$$

Voltage gain is obtained by feeding the output current into output load resistor.

$$\begin{aligned} V_{OUT} &= I_{OUT} \cdot R_{OUT} \\ &= B_1 g_{m1} \cdot R_{OUT} \cdot \Delta V_{in} \end{aligned}$$


$$A = \frac{V_{OUT}}{\Delta V_{in}} = B_1 g_{m1} \cdot R_{OUT}$$

Without external load resistor:

$$R_{OUT} = \frac{1}{g_{DS5} + g_{DS6}}$$

$$\Rightarrow A = \frac{B_1 g_{m1}}{g_{DS5} + g_{DS6}}$$

Small-signal analysis


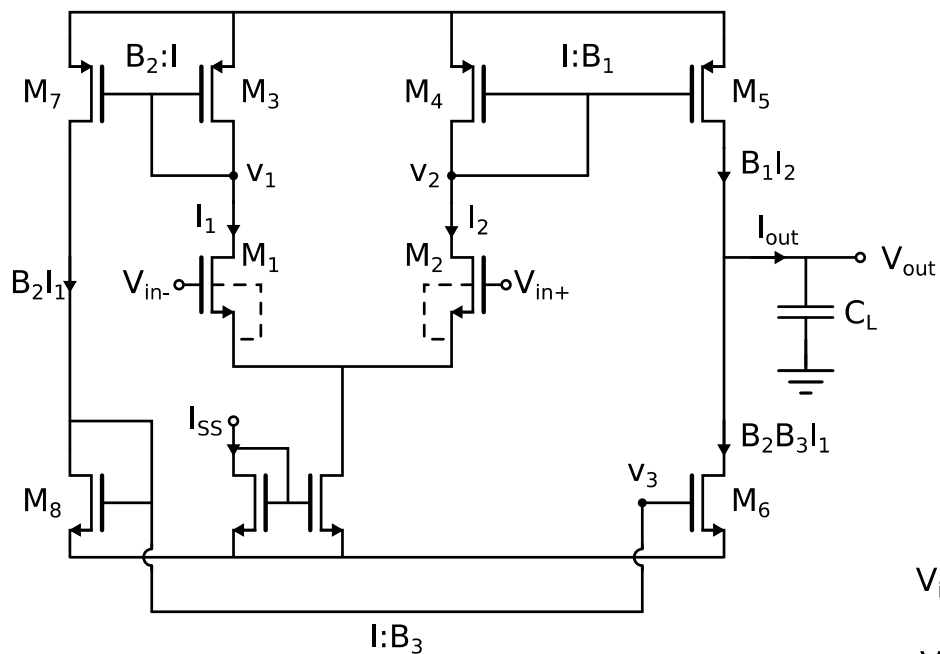


Exclude Miller effect due to a small overlap capacitor

$$V_{in}^+ = \frac{1}{2} \Delta V_{in}$$

$$V_{in}^- = -\frac{1}{2} \Delta V_{in}$$

$$C_L' = C_L + C_{DB5} + C_{DB6}$$

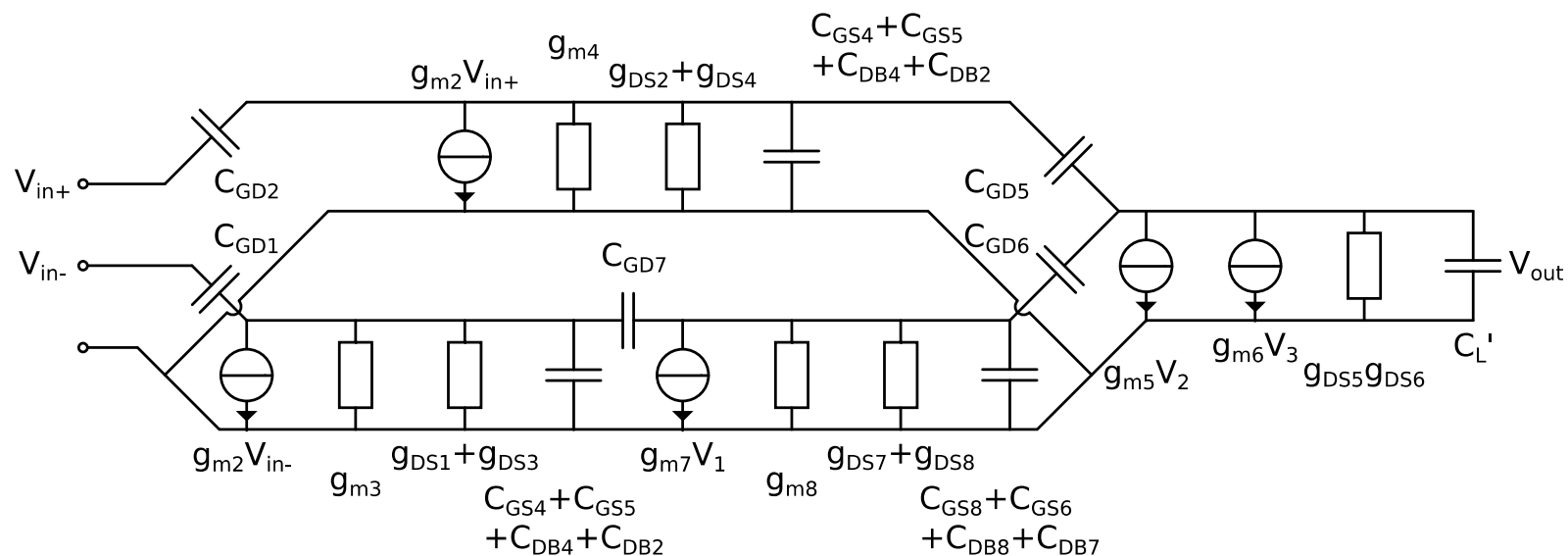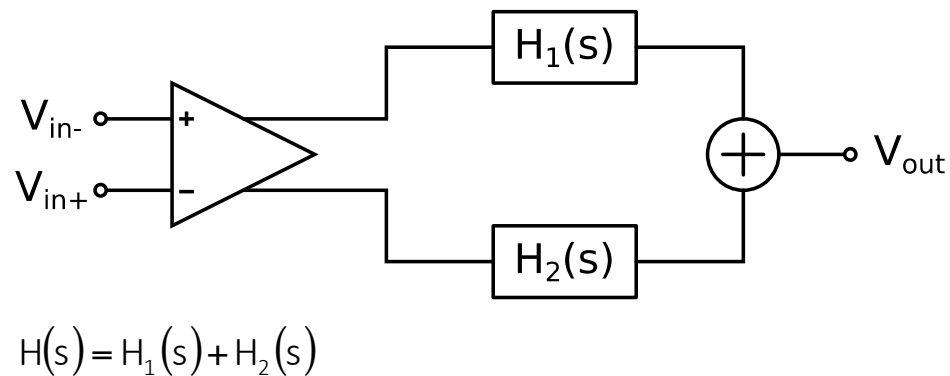

Transferfunction of the two signal branches:

$$H_1(s) = \frac{\frac{1}{2} \frac{g_{m2}}{g_{m4}} \cdot \frac{g_{m5}}{g_{DS5} + g_{DS6}}}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_L}\right)} = \frac{\frac{1}{2} \frac{B_1 g_{m2}}{g_{DS5} + g_{DS6}}}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_L}\right)}$$

$$H_2(s) = \frac{\frac{1}{2} \frac{g_{m1}}{g_{m3}} \cdot \frac{g_{m7}}{g_{m8}} \cdot \frac{g_{m6}}{g_{DS5} + g_{DS6}}}{\left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) \left(1 + \frac{s}{p_L}\right)} = \frac{\frac{1}{2} \frac{B_2 \cdot B_3 \cdot g_{m1}}{g_{DS5} + g_{DS6}}}{\left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) \left(1 + \frac{s}{p_L}\right)}$$

Poles:

$$p_2 = \frac{g_{m3} + g_{DS1} + g_{DS3}}{C_{GS3} + C_{GS7} + C_{DB1} + C_{DB3}} \approx \frac{g_{m3}}{C_{p2}}$$

$$p_1 = \frac{g_{m4} + g_{DS2} + g_{DS4}}{C_{GS4} + C_{GS5} + C_{DB2} + C_{DB4}} \approx \frac{g_{m4}}{C_{p1}}$$

$$p_3 = \frac{g_{m8} + g_{DS7} + g_{DS8}}{C_{GS8} + C_{GS6} + C_{DB7} + C_{DB8}} \approx \frac{g_{m8}}{C_{p3}}$$

$$p_L = \frac{g_{DS5} + g_{DS6}}{C_L'}$$

$$g_{DS5} + g_{DS6} \ll g_{mi}$$

$$p_L \ll p_1, p_2, p_3$$

Symmetrical design:

$$\text{ass. } M_1 = M_2, M_3 = M_4, (M_7 = M_5)(M_8 = M_6)$$

$$\Rightarrow g_{m3} = g_{m4}, C_{p2} = C_{p1}$$


$$\Rightarrow p_1 = p_2$$

$$B_2 = B_1 : B_3 = 1$$

$$\Rightarrow p_1 = p_2$$

Transferfunction of OTA:

Combine the two signal paths

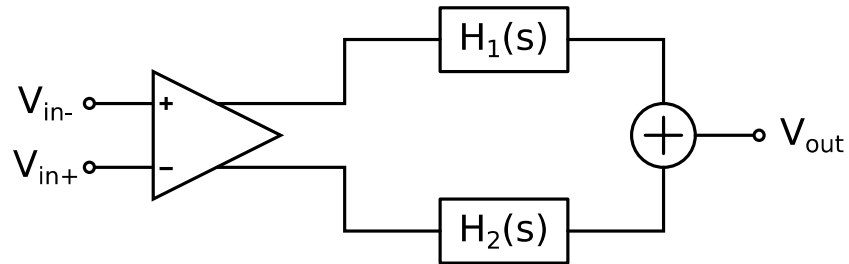

$$H(s) = H_1(s) + H_2(s)$$

$$= \frac{\frac{1}{2} \frac{g_{m1}}{g_{DS5} + g_{DS6}} \left(B_1 \left(1 + \frac{s}{p_3} \right) + B_2 B_3 \right)}{\left(1 + \frac{s}{p_1} \right) \left(1 + \frac{s}{p_3} \right) \left(1 + \frac{s}{p_L} \right)}$$

$$= \frac{\frac{B_1 g_{m1}}{g_{DS5} + g_{DS6}} \left(1 + \frac{s}{2p_3} \right)}{\left(1 + \frac{s}{p_1} \right) \left(1 + \frac{s}{p_3} \right) \left(1 + \frac{s}{p_L} \right)}$$

$$A_0 = \frac{g_{m1} \cdot g_{m5}}{g_{DS5} + g_{DS6}}$$

$$A_0 = \frac{B_1 g_{m1}}{g_{DS5} + g_{DS6}} \quad (100 \dots 5000)$$

Compensation of OTA amplifier:

assume $g_{DS1i} \ll g_{mi}$


$$\Rightarrow p_L = \frac{g_{DS5} + g_{DS6}}{C_L} \ll \frac{g_{mi}}{C_{pi}} = p_i \quad i = 1, 3$$

Output node is
a high impedance node!


→ Compensation is
performed by increasing C_L

$$\text{assume } A(s) \approx \frac{A_0}{\left(1 + \frac{s}{p_L} \right)}$$
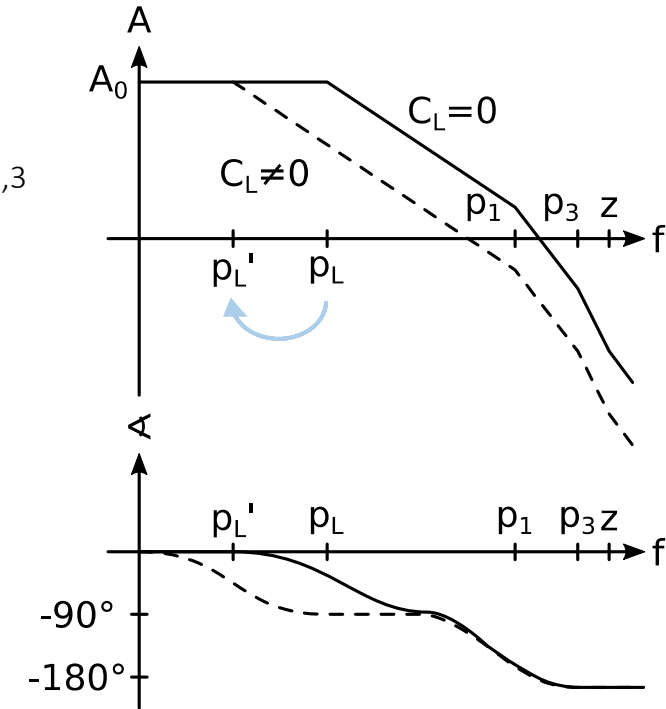
$$\Rightarrow \text{GBW} = A_0 \cdot p_L = \frac{B_1 g_{m1}}{g_{DS5} + g_{DS6}} \cdot \frac{g_{DS5} + g_{DS6}}{C_L} = \frac{B_1 g_{m1}}{C_L} = \frac{g_m}{C_L}$$



Cascode OTA

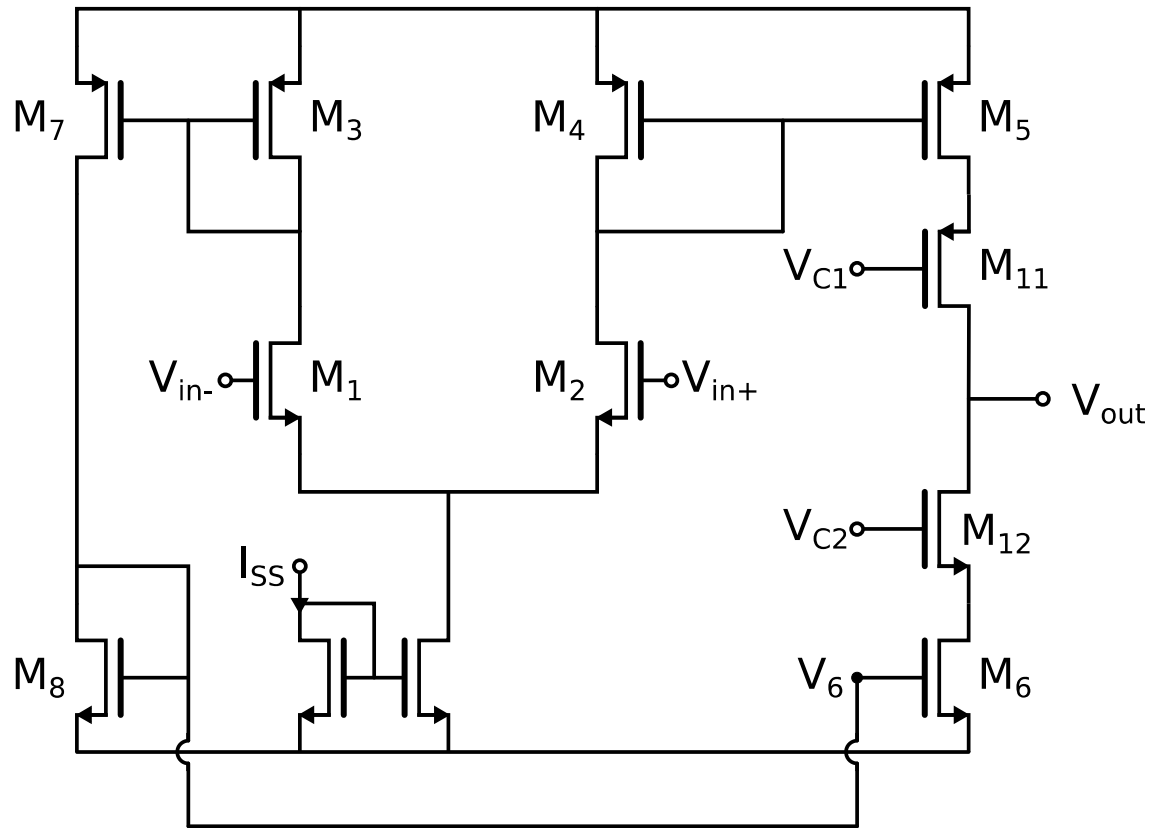

OTA gain is

$$A = \frac{B_1 g_{m1}}{g_L} = \frac{B_1 g_{m1}}{g_{DS5} + g_{DS6}} = B_1 g_{m1} (R_{DS5} || R_{DS6})$$

Larger output resistance gives higher voltage gain


⇒ use cascode transistors to increase the output impedance.

Replace M_5 and M_6 with cascode current sources.


Cascode transistors increase the output impedance by the internal gain of the cascode transistor.

$$r_o = \frac{1}{\frac{g_{DS5} g_{DS11}}{g_{m11}} + \frac{g_{DS6} g_{DS12}}{g_{m12}}}$$

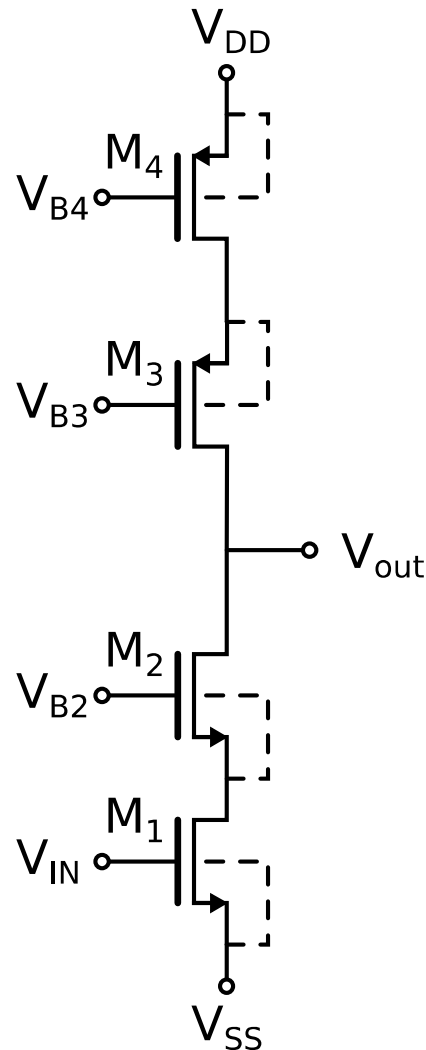Let's calculate the gain of a cascode amplifier. The input voltage is connected to the gate of transistor M_1 and the other transistors are biased with voltages V_{B2} , V_{B3} and V_{B4} . The difference to a simple current source loaded inverter is the addition of the cascode transistors M_2 and M_3 .



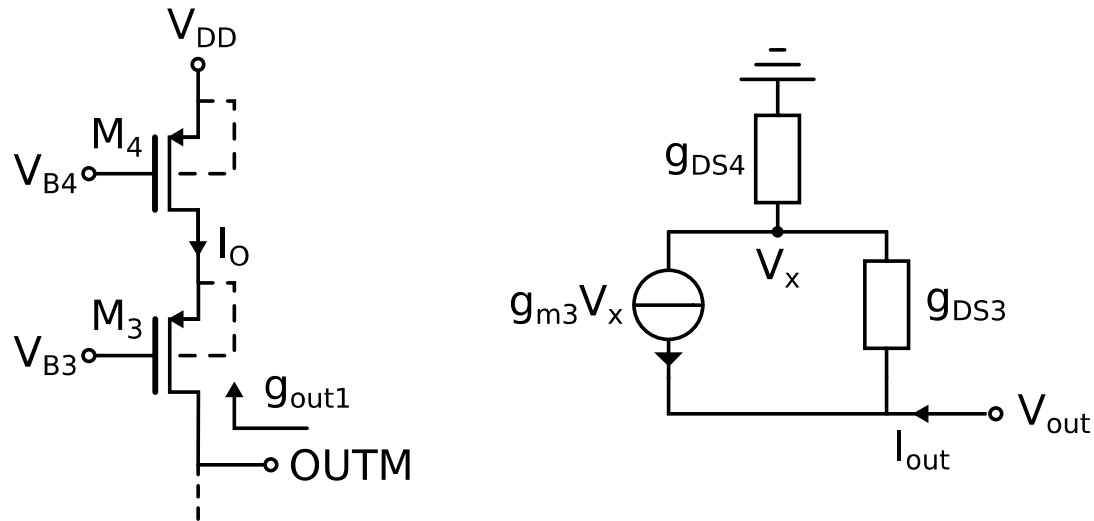Let's start the analysis with the cascode current source of M_3 and M_4 and calculate its small signal output conductance.




Writing the node equations we get

$$\begin{aligned}(g_{DS3} + g_{DS4})v_x - g_{DS3}v_{out} &= -g_{m3}v_x \\ g_{DS3}v_{out} - g_{DS3}v_x &= g_{m3}v_x + i_{out}\end{aligned}$$

The resulting small signal output conductance is

$$g_{out1} = \frac{i_{out}}{v_{out}} = \frac{g_{DS3}g_{DS4}}{g_{DS3} + g_{DS4} + g_{m3}} \approx \frac{g_{DS3}}{g_{m3}} g_{DS4}$$

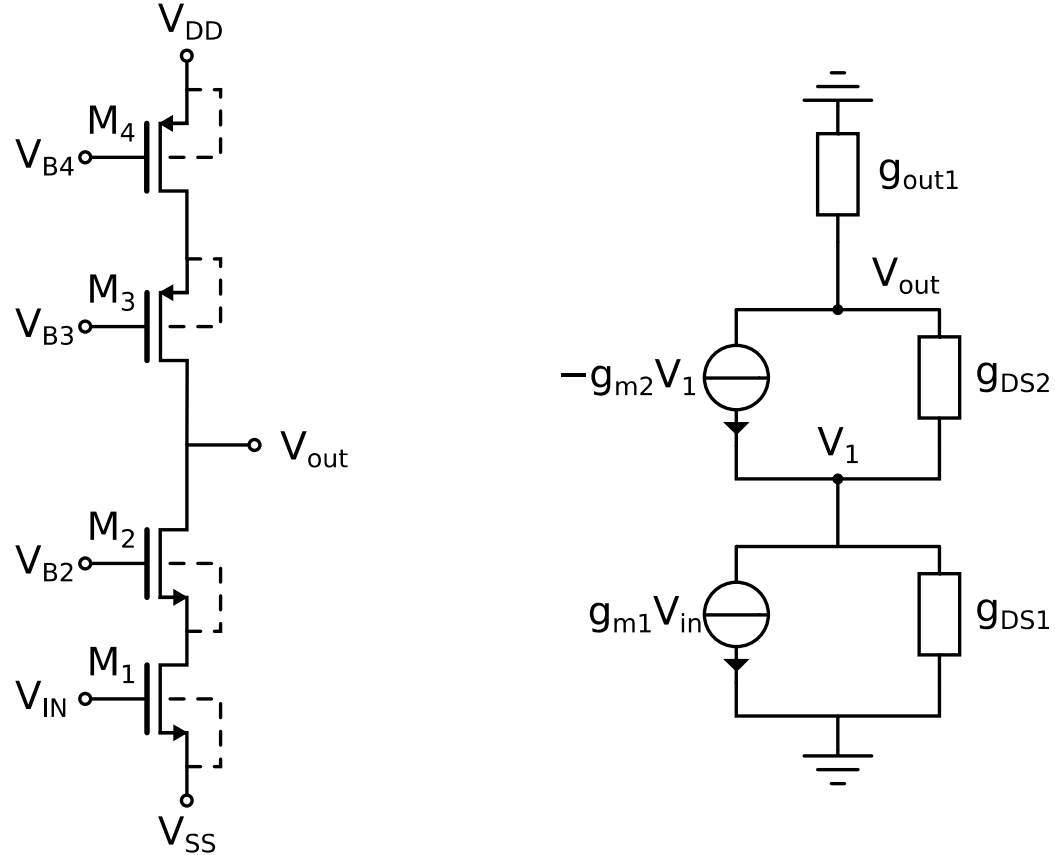Now we can solve the rest of the small signal circuit and the resulting gain.



The node equations are

$$(g_{DS1} + g_{DS2})v_1 - g_{DS2}v_{out} = -g_{m1}v_{in} - g_{m2}v_1$$

$$(g_{out1} + g_{DS2})v_{out} - g_{DS2}v_1 = g_{m2}v_1$$

With some arranging we get

$$(g_{m2} + g_{DS1} + g_{DS2})v_1 - g_{DS2}v_{out} = -g_{m1}v_{in}$$
$$v_1 = \frac{g_{out1} + g_{DS2}}{g_{m2} + g_{DS2}}v_{out}$$

Inserting the value of v_1 to the first equation we get

$$(g_{m2} + g_{DS1} + g_{DS2})\frac{g_{out1} + g_{DS2}}{g_{m2} + g_{DS2}}v_{out} - g_{DS2}v_{out} = -g_{m1}v_{in}$$
$$\frac{(g_{m2} + g_{DS1} + g_{DS2})g_{out1} + g_{DS1}g_{DS2}}{g_{m2} + g_{DS2}}v_{out} = -g_{m1}v_{in}$$

The transfer function after simplification ($g_m \gg g_{DS}$) is

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1}}{\frac{g_{DS2}}{g_{m2}}g_{DS1} + g_{out1}} = \frac{g_{m1}}{\frac{g_{DS2}}{g_{m2}}g_{DS1} + \frac{g_{DS3}}{g_{m3}}g_{DS4}}$$

The output conductance of the whole amplifier is very small due to the g_{DS}/g_m terms.

Cascode OTA

The gain of cascode OTA becomes:

$$A_0 = g_m \cdot R_L = \frac{g_m R_p R_N}{R_p + R_N} = \frac{B_1 g_{m1}}{\frac{g_{DS5} g_{DS11}}{g_{m11}} + \frac{g_{DS6} g_{DS12}}{g_{m12}}}$$

There is also a pole associated with a cascode transistor.
Assuming $M_{11} = M_{12}$ (i.e. matched)

$$p_4 = \frac{g_{m11}}{C_{GS11}} \cong \frac{g_{m12}}{C_{GS12}} = p_5$$

However, as $p_4 = p_5 \Rightarrow$ there is also a zero

$$z = \frac{1}{2}(p_4 + p_5)$$


Which compensates one of the poles!

The dominant pole of the cascode OTA is


$$p_L = \frac{g_L}{C_L} = \frac{1}{R_L C_L} = \frac{\frac{g_{DS5} g_{DS11}}{g_{m11}} + \frac{g_{DS6} g_{DS12}}{g_{m12}}}{C_L}$$

$$A(s) \cong \frac{A_0}{1 + \frac{s}{p_L}}$$

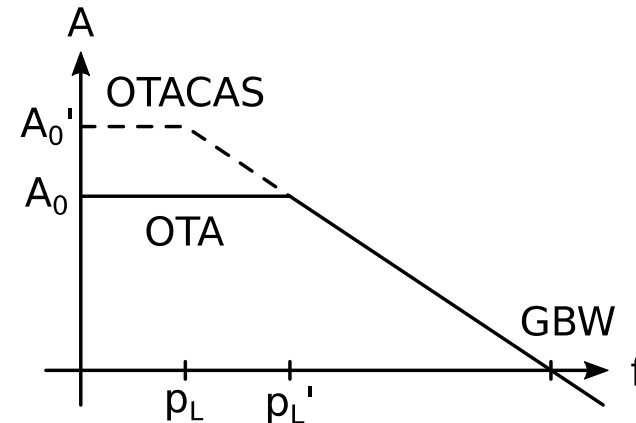
$$GBW = A_0 \cdot p_L = \frac{B_1 g_{m1}}{C_L}$$




Output signal swing of cascode OTA

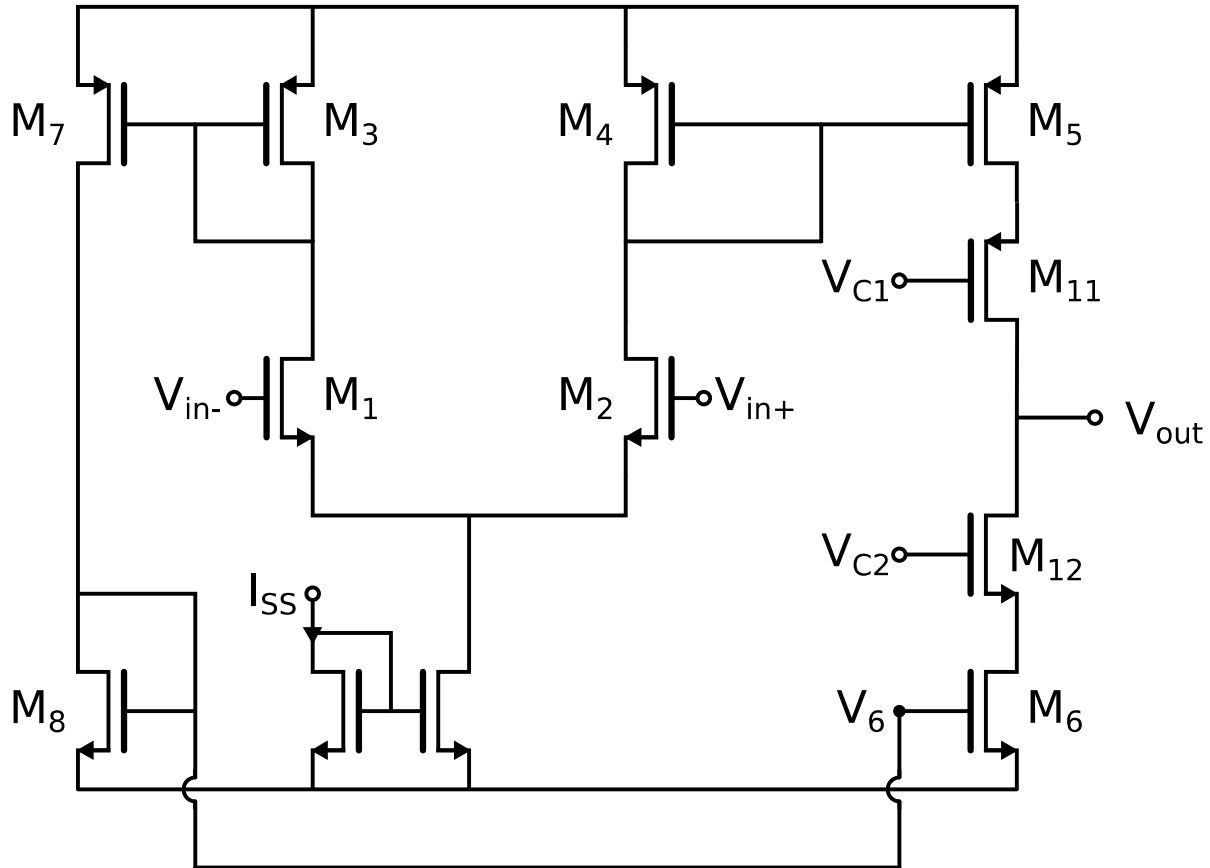


Cascode OTA has limited signal swing

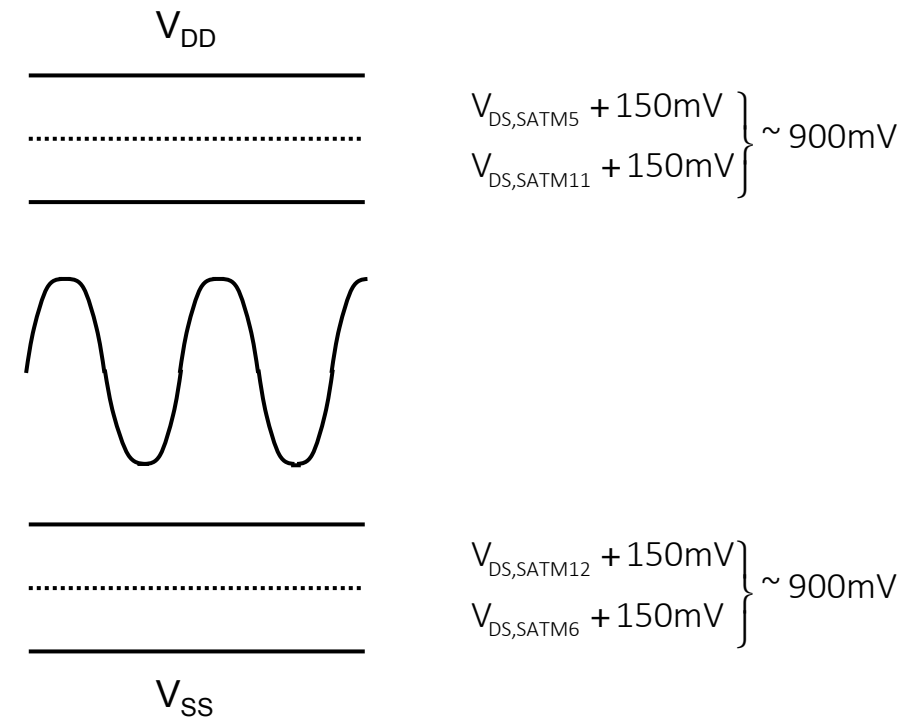

Cascode biasing

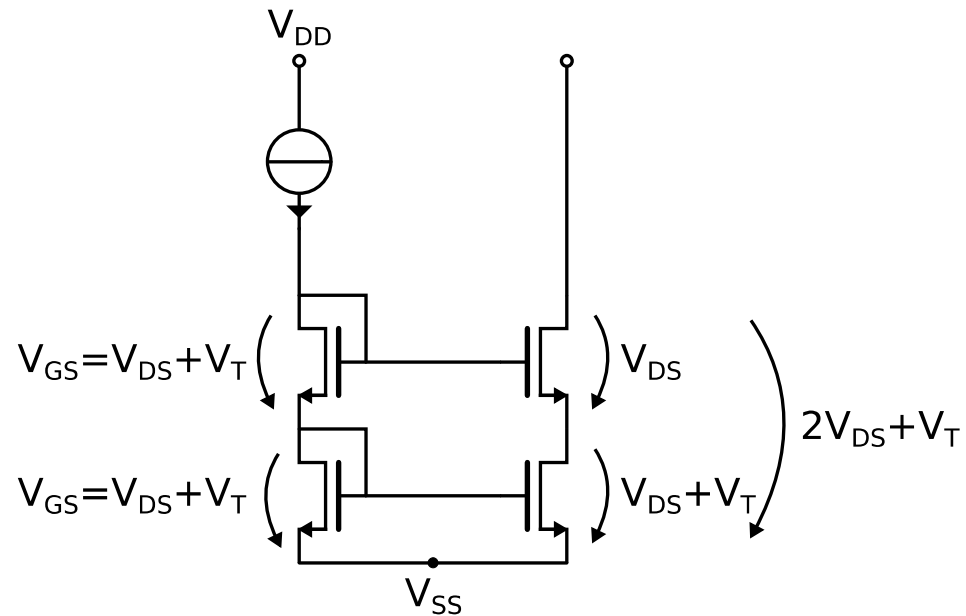

Biasing for maximum output swing

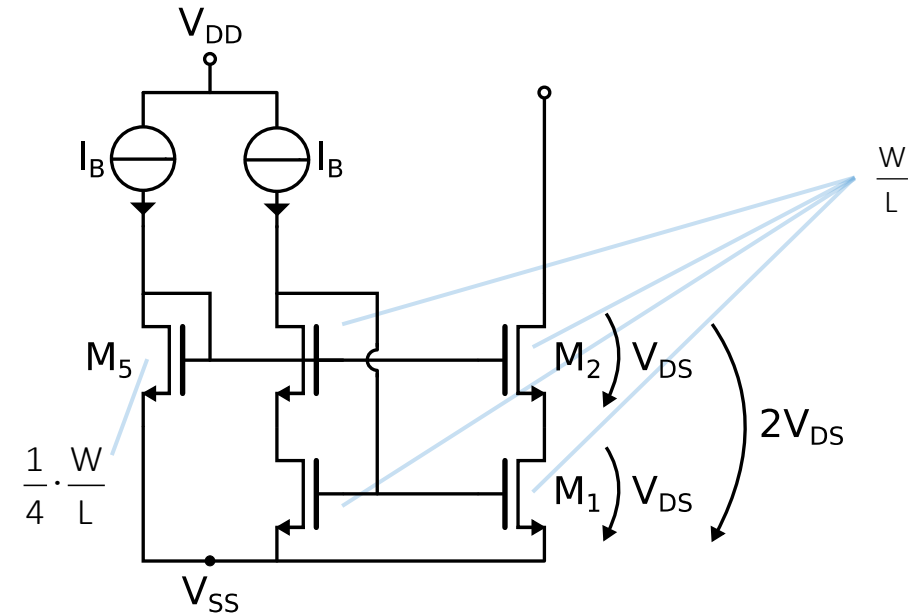

$$\left(\frac{W}{L}\right)_5 = \frac{1}{4} \left(\frac{W}{L}\right)_{1,2}$$

$$\Rightarrow V_{DS5,SAT} = 2V_{DS1,SAT}$$


$$\Rightarrow V_{GS5} = V_{TN} + V_{DS5,SAT} = V_{TN} + 2V_{DS1,SAT}$$

$$H(s) = \frac{A_0 \left(1 + \frac{s}{z}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) \left(1 + \frac{s}{p_L}\right)}$$

	OTA CAS	2 Stage (Miller comp.)
A_0	$\frac{B_1 g_{m1}}{\frac{g_{DS5} g_{DS11}}{g_{m11}} + \frac{g_{DS6} g_{DS12}}{g_{m12}}}$	$\frac{g_{m1} (g_{m8} + g_{m9})}{(g_{DS2} + g_{DS4})(g_{DS8} + g_{DS9})}$
p_1	$\frac{g_{m3}}{2C_{GS} + 2C_{DB}}$	$\frac{g_{m3}}{2C_{GS} + 2C_{DB}}$
p_2	$\frac{g_{m2}}{2C_{GS} + 2C_{DB}}$	$\frac{(g_{DS2} + g_{DS4})(g_{DS8} + g_{DS9})}{(g_{m8} + g_{m9})C_C} = \frac{g_{m1}}{A_0 C_C}$
p_3	$\frac{g_{m11}}{C_{GS11}}$	$\frac{1}{R_z C_C}$

	OTA CAS	2 Stage (Miller comp.)
p_L	$\frac{\frac{g_{DS5}g_{DS11}}{g_{m11}} + \frac{g_{DS6}g_{DS12}}{g_{m12}}}{C_L}$	$\frac{(g_{m8} + g_{m9})C_C}{C_A C_L + (C_A + C_L)C_C} \approx \frac{g_{m8} + g_{m9}}{C_L}$
z	$\frac{1}{2p_3}$	
GBW	$\frac{B_1 g_{m1}}{C_L}$	$\frac{g_{m1}}{C_C}$
SR	$\frac{B_1 I_{SS}}{C_L}$	$\frac{I_{SS}}{C_C}$

Folded – cascode OTA

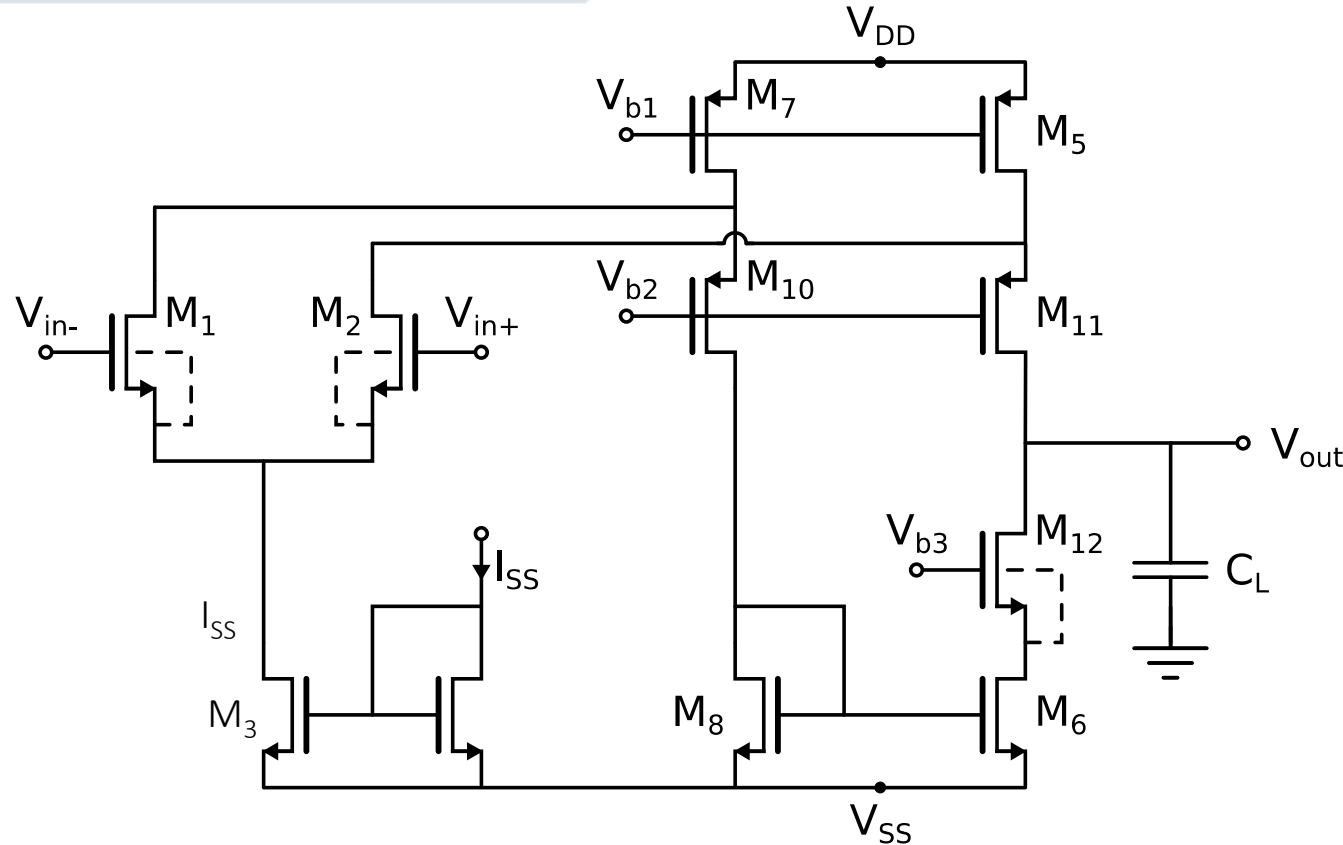

Input voltage divides the input stage biasing current I_{SS} between M_1 and M_2 , on the other hand I_{M1} and I_{M2} defines how much biasing current of M_7 and M_5 goes to output stage through M_{10} and M_{11}


$$I_{OUT} = I_{M1} - I_{M2}$$

Typical biasing $I_{M3} = I_{M7} = I_{M5} = I_{SS}$
and $I_{M1} = I_{M2} = I_{M10} = I_{M11} = I_{M8} = I_{M6} = I_{SS}/2$

- Eliminates the diode connected load transistors of the input stage
 $\Rightarrow$ one pole less
 $\Rightarrow$ broader bandwidth possible
- No current mirror
 $\Rightarrow$ no current gain
 $\Rightarrow g_m = g_{m1}$
- Larger parasitic capacitance at the source of M_{10} and M_{11}
 $\Rightarrow$ cascode pole at lower frequencies

Folded – cascode OTA transferfunction

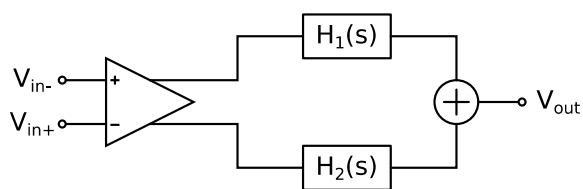
Folded-cascode OTA
transferfunction analysis:



$$H_1(s) = \frac{V_{OUT}}{V_{in}/2} = \frac{A_0}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_L}\right)}$$

$$H_2(s) = \frac{V_{OUT}}{V_{in}/2} = \frac{A_0}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)\left(1 + \frac{s}{p_3}\right)\left(1 + \frac{s}{p_L}\right)}$$
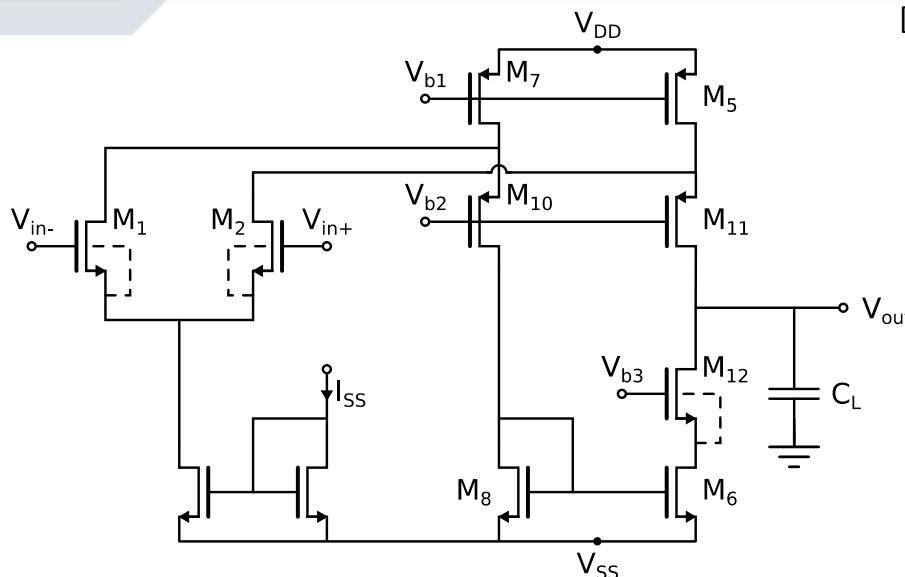
$$H(s) = H_1(s) + H_2(s) = \frac{V_{OUT}}{V_{in}} = \frac{A_0 \left(1 + \frac{s}{z_2}\right)\left(1 + \frac{s}{z_3}\right)}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)\left(1 + \frac{s}{p_3}\right)\left(1 + \frac{s}{p_L}\right)}$$



DC-gain: $A_0 = \frac{g_{m1}}{\frac{g_{DS6}g_{DS12}}{g_{m12}} + \frac{(g_{DS2} + g_{DS5})g_{DS11}}{g_{m11}}}$

Load pole: p_L is the dominant pole

$$p_L = \frac{g_L}{C_L} = -\frac{g_{m12}}{C_L} \frac{g_{m11}}{g_{m11}}$$

Cascode-transistor $M_{11}(=M_{10})$ pole:

$$p_1 = \frac{-g_{m11}}{C_{GS11} + C_{DB2} + C_{DB5} + C_{DB11}}$$

Pole-zero pair of current mirror M_8 and M_6 :

$$p_2 = \frac{-g_{m8}}{C_{GS8} + C_{GS6} + C_{DB8} + C_{DB10}} \quad z_2 \approx p_2$$


Pole-zero pair due to cascode device M_{12} :

$$p_3 = \frac{-g_{m12}}{C_{DB6} + C_{SB12} + C_{GS12}} \quad z_3 \approx p_3$$

p_L is dominant pole $p_L \ll p_i \Rightarrow A(s) \approx \frac{A_0}{1 + \frac{s}{p_L}}$

GBW is given by: $GBW = p_L \cdot A_0 = \frac{g_{m1}}{C_L}$

Modified folded – cascode OTA

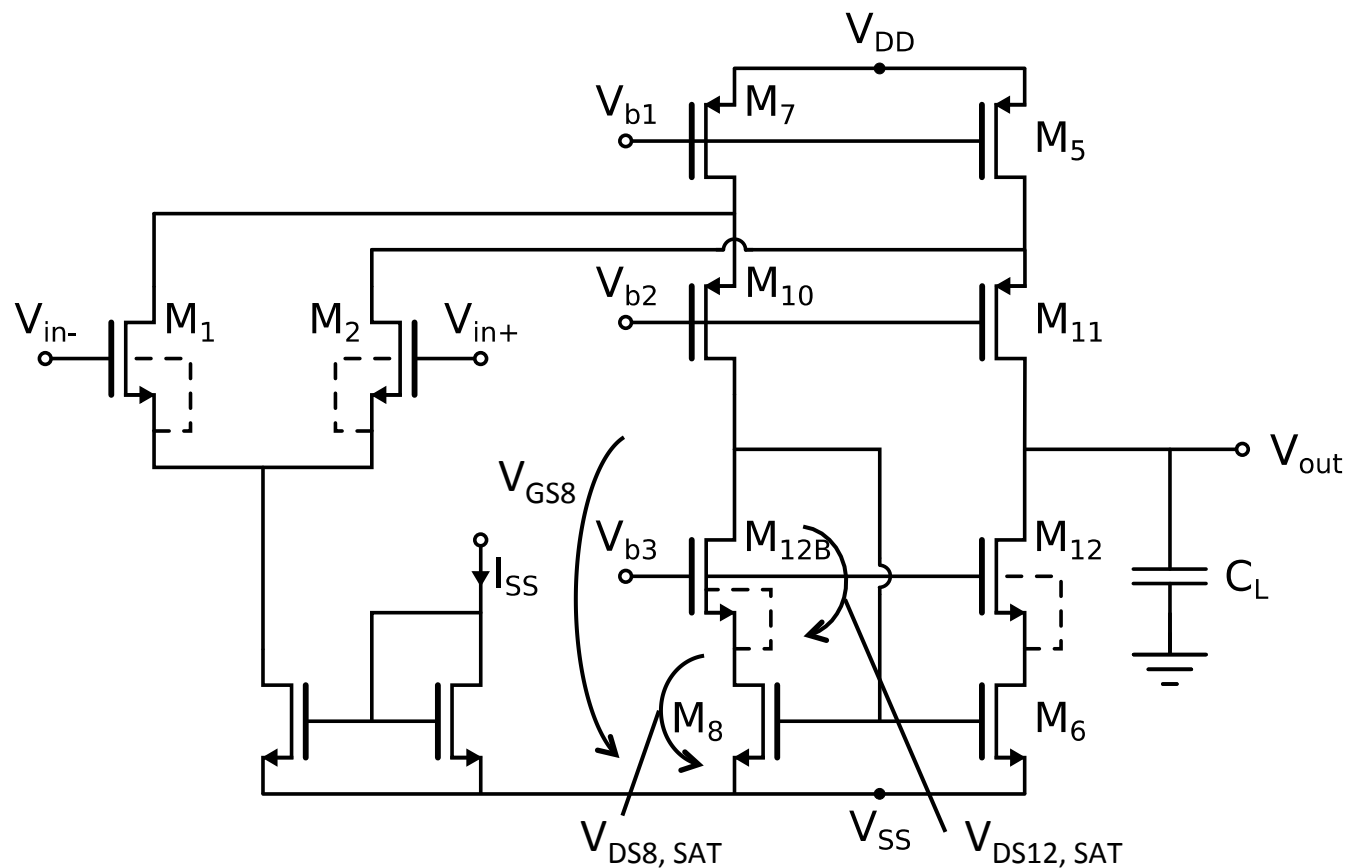


Ideally ZERO offset:

Cascode transistor M_{12B} added so that:

- $V_{DS8} \equiv V_{DS6}$
 $\Rightarrow I_{D,M8} \equiv I_{D,M6}$
- Channel length modulation eliminated
 $\Rightarrow$ systematic offset eliminated
 $\Rightarrow$ also PSRR improved
- DC operating point harder to design to keep M_8 in saturation
 $V_{GS8} > V_{DS12,SAT} + V_{DS8,SAT}$
 $V_{GS8} = V_{DS8,SAT} + V_{T8}$
 $V_{DS12,SAT} < V_{T8}$

Tripple – cascode FOTA

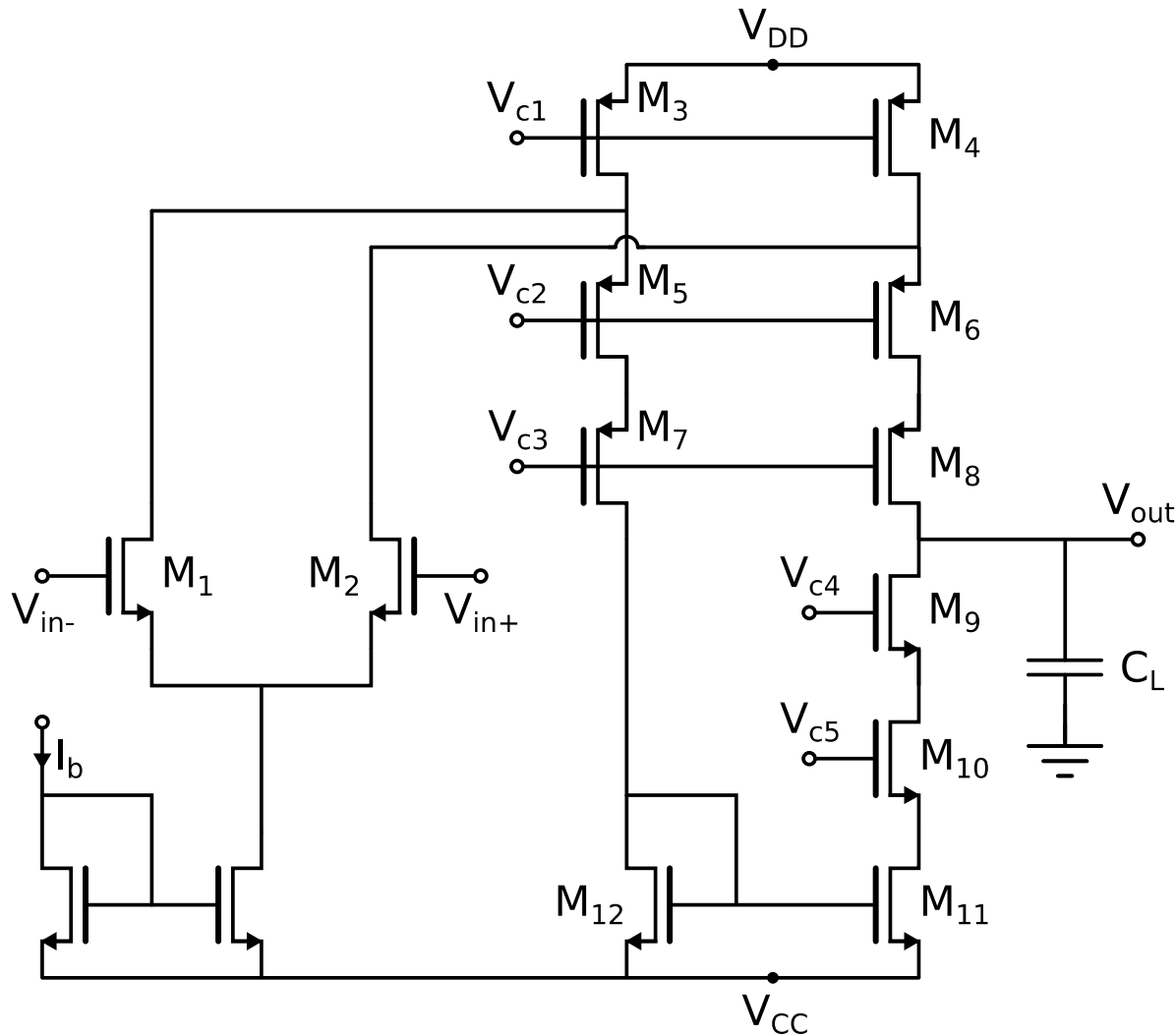


Second cascode transistor added to increase the output impedance and DC-gain:

$$A = \frac{g_{m1}}{\frac{(g_{d4} + g_{d2})g_{d6} \cdot g_{d8}}{g_{m6} \cdot g_{m8}} + \frac{g_{d11} \cdot g_{d10} \cdot g_{d9}}{g_{m10} \cdot g_{m9}}} \approx 10^6 = 120\text{dB}$$

- Reduced output swing due to three devices in series (all need to be in saturation for high gain)

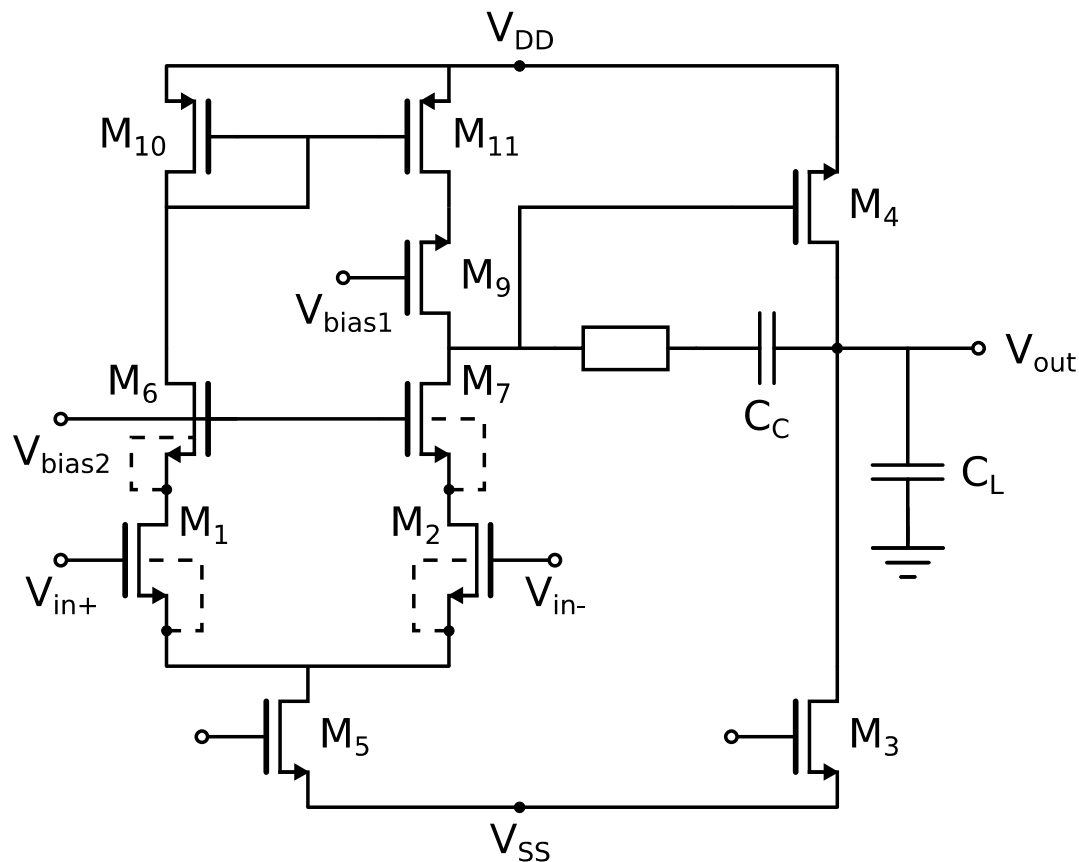Miller compensated amplifier with cascode input stage




Cascode-transistors added to input gain stage to increase the output impedance and gain by gain of cascode transistor.


Cascode transistors do not limit linear signal range because only 10-20 mV signal swing needed at the output of the input stage.

Gain increased by 30-50 dB and can be as high as 120...130 dB.
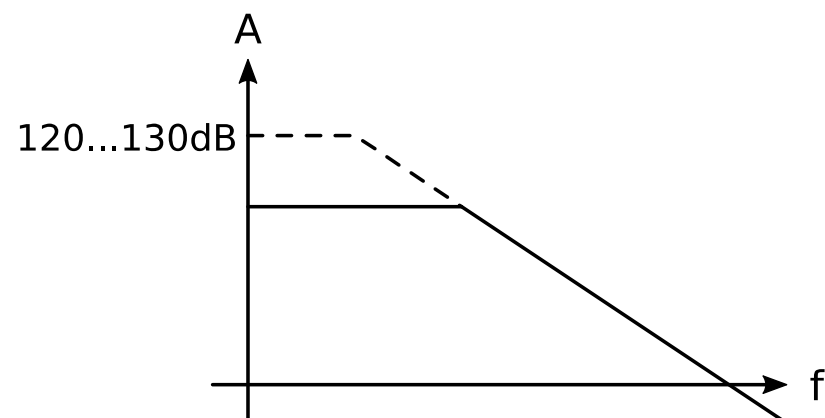
$$A_0 = \frac{g_{m1}g_{m4}}{(g_{DS3} + g_{DS4}) \left(\frac{g_{DS11} \cdot g_{DS9}}{g_{m9}} + \frac{g_{DS2} \cdot g_{DS7}}{g_{m7}} \right)}$$



Regulated cascode OTA

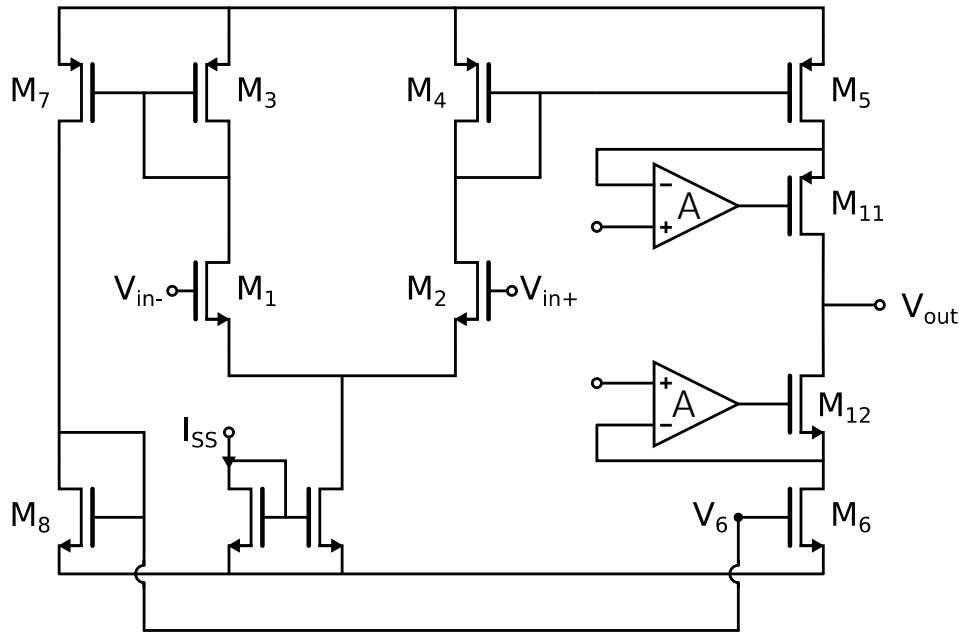


- Regulated cascode transistors increases the output impedance

$$r_{OUT} = \frac{1}{\frac{g_{DS5}g_{DS11}}{Ag_{m11}} + \frac{g_{DS6}g_{DS12}}{Ag_{m12}}}$$


- Output impedance and gain are increased with the gain of A
- Settling is affected by regulation amplifiers, may cause ringing
- The gain of regulated cascode OTA:

$$A = Bg_{m1}V_{OUT}$$
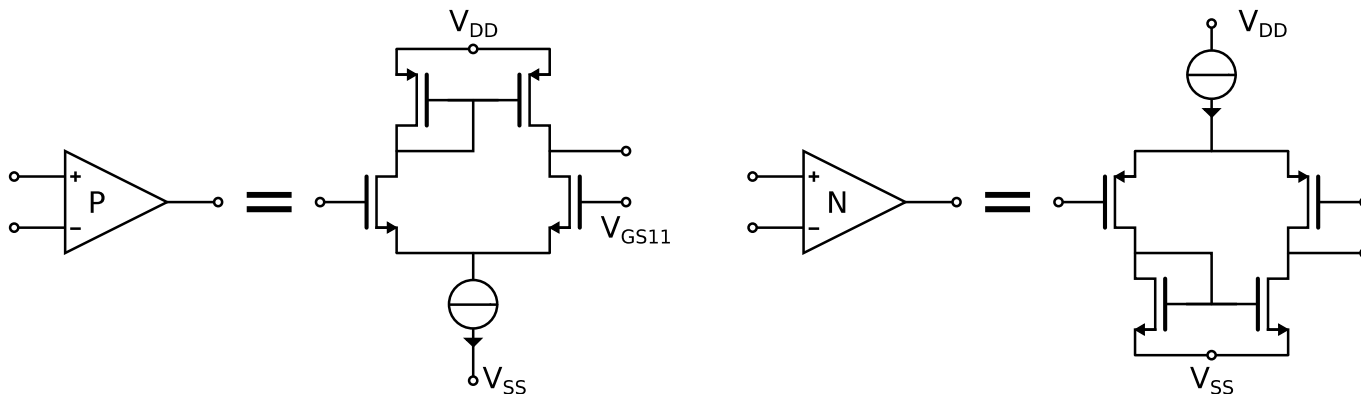
$$= \frac{ABg_{m1}}{\frac{g_{DS5}g_{DS11}}{g_{m1}} + \frac{g_{DS6}g_{DS12}}{g_{m12}}}$$



Fully differential OTA

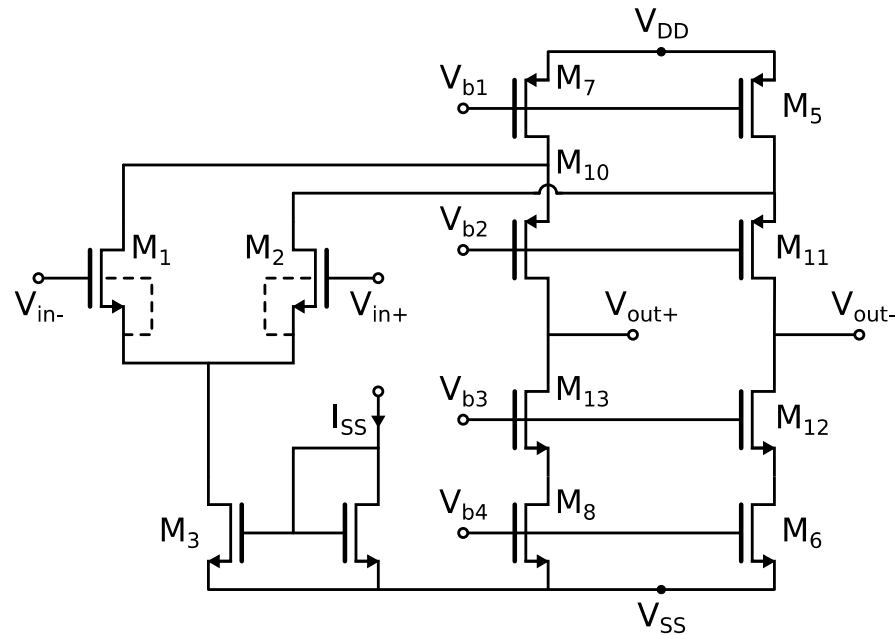

- No diode connection of M_8
 $\Rightarrow$ one zero-pole pair less
 $\Rightarrow$ faster settling
- Fully symmetrical
 $\Rightarrow$ very good PSRR

Disturbances from power lines rejected.

Ideally a 2-pole transfer-function:

$$H(S) = \frac{A_0}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right)}$$

$$A_0 = \frac{g_{m1}}{\frac{g_{DS6}g_{DS12}}{g_{m12}} + \frac{(g_{DS2} + g_{DS5}) g_{DS11}}{g_{m11}}}$$

$$p_1 = -\frac{\frac{g_{DS6}g_{DS12}}{g_{m12}} + \frac{(g_{DS2} + g_{DS5}) g_{DS11}}{g_{m11}}}{C_L}$$

$$p_2 = \frac{-g_{m11}}{C_{GS11} + C_{DB2} + C_{DB5} + C_{DB11}}$$

$p_1 \ll p_2$ p_2 is a dominant pole

$$GBW = p_1 \cdot A_0 = \frac{g_{m1}}{C_L}$$

Needs a common-mode feedback to stabilize output DC-level (output can fluctuate freely).

