

ELEC-E3510 Basics of IC Design

Lecture 6: Noise and PSRR


MOS transistor noise model

- Resistivity of conductive channel causes thermal noise

$$\frac{\partial I_{\text{DN}}^2}{\partial f} = \frac{8}{3} kT g_m$$

- Charge traps in oxide-silicon surface are slow
→ 1/f-noise, i.e. flicker noise



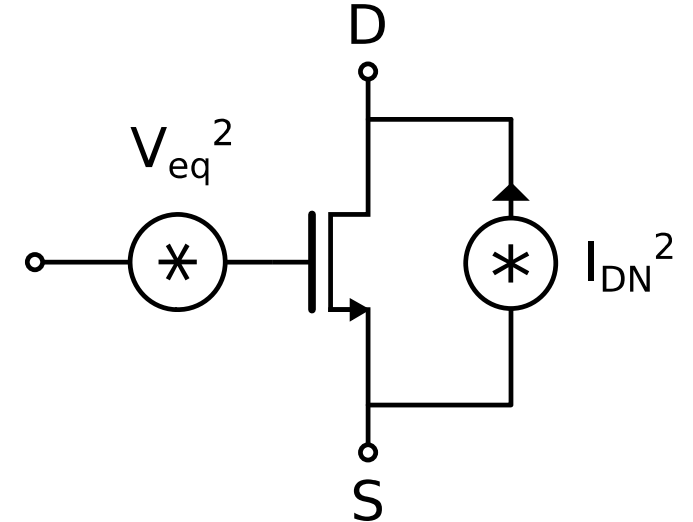
$$\frac{\partial V_{\text{GN}}^2}{\partial f} = \frac{B}{fW \cdot L}$$





Inverter noise analysis

$$A(s) = \frac{-g_{m1}}{(sC_{GS1}R_S + 1)(sC_L + g_{DS1} + g_{DS2})}$$

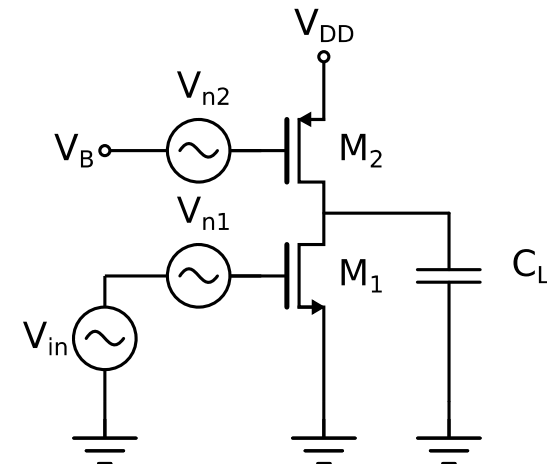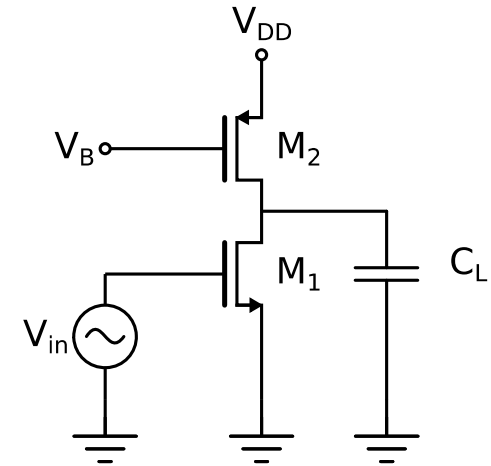
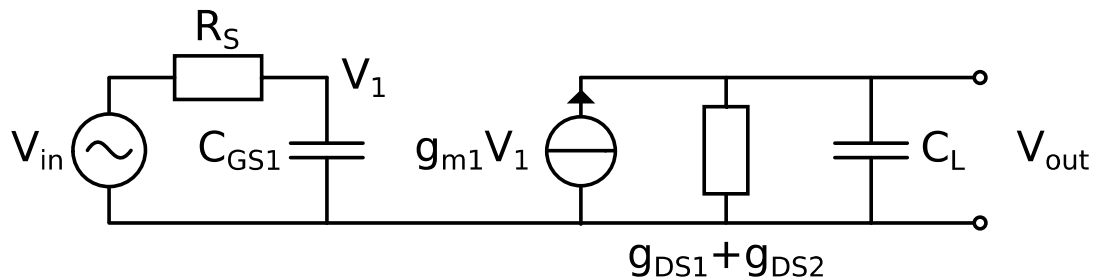
- Contribution of each noise source to the output noise is analysed separately by calculating the corresponding noise transfer functions
- Total output noise is calculated by summing quadratically the noise coming from each noise source



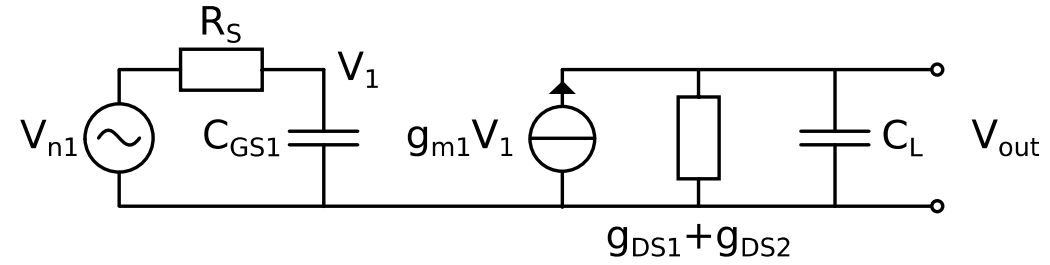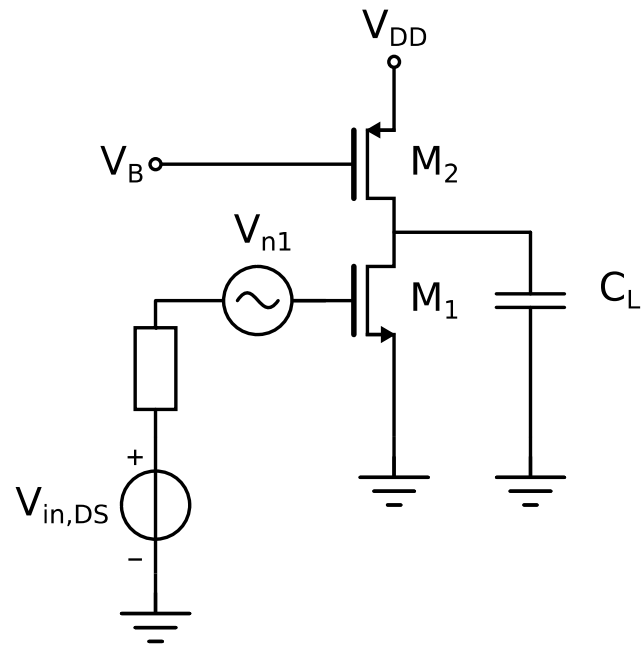

$$A_{n1} = \frac{v_{on1}}{v_{n1}} = \frac{-g_{m1}}{(sC_{GS1}R_S + 1)(sC_L + g_{DS1} + g_{DS2})}$$

$$v_{on1}^2 = |A_{n1}|^2 \cdot v_{n1}^2$$

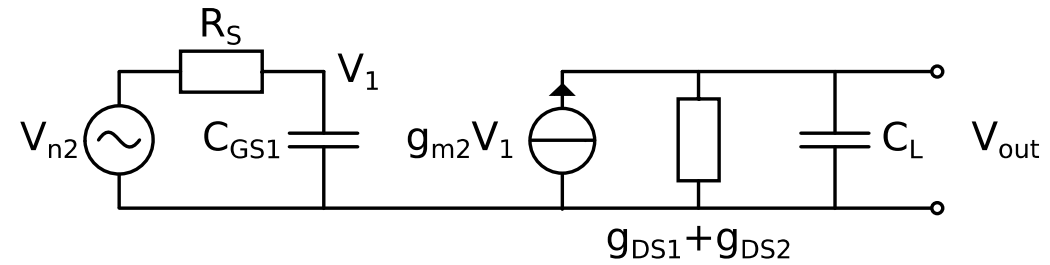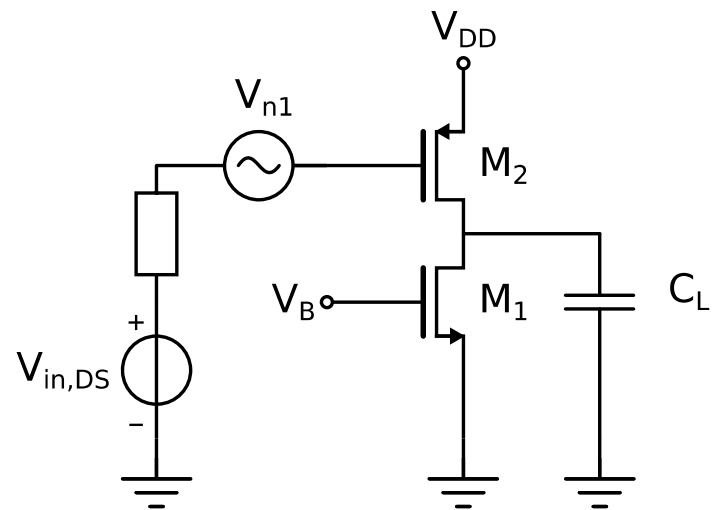

$$A_{n1} = \frac{v_{on2}}{v_{n2}} = \frac{-g_{m2}}{(sC_{GS2}R_S + 1)(sC_L + g_{DS1} + g_{DS2})}$$

$$v_{on2}^2 = |A_{n2}|^2 \cdot v_{n2}^2$$

Output noise voltage:

$$v_{on}^2 = v_{on1}^2 + v_{on2}^2 = |A_{n1}|^2 v_{n1}^2 + |A_{n2}|^2 v_{n2}^2$$

Equivalent input noise voltage:

$$v_{on}^2 = |A|^2 \cdot v_{in,ek}^2$$

$$\Rightarrow v_{in,ek}^2 = \frac{v_{on}^2}{|A|^2} = \frac{|A_{n1}|^2}{|A|^2} v_{n1}^2 + \frac{|A_{n2}|^2}{|A|^2} v_{n2}^2$$

Assume $\frac{g_{DS1} + g_{DS2}}{C_L} \ll \frac{1}{R_S C_{GS1}}$ or $\frac{1}{R_B C_{GS2}}$ (single pole approximation)

$$A_{n1} \approx \frac{-g_{m1}}{(sC_L + g_{DS1} + g_{DS2})}$$



$$A_{n2} \approx \frac{-g_{m2}}{(sC_L + g_{DS1} + g_{DS2})}$$

$$A \approx \frac{-g_{m1}}{(sC_L + g_{DS1} + g_{DS2})}$$



$$\Rightarrow v_{in,ek}^2 = v_{n1}^2 + \left(\frac{g_{m2}}{g_{m1}} \right)^2 v_{n2}^2$$

Note: This is also valid for diode load!



Push-pull inverter

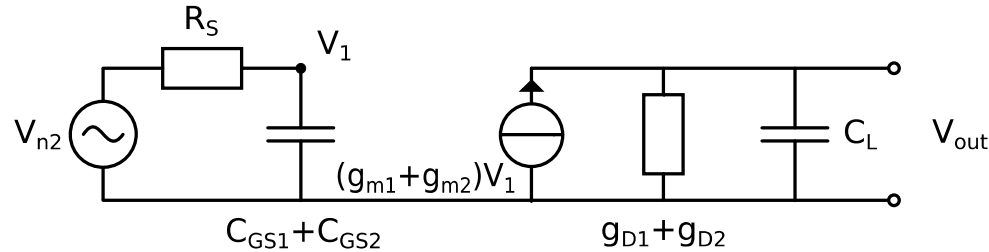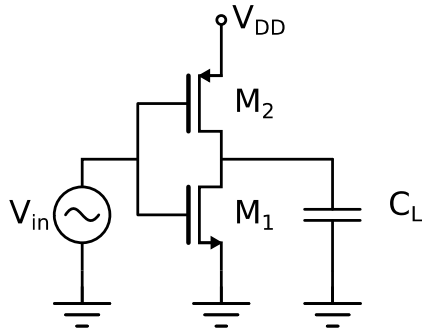
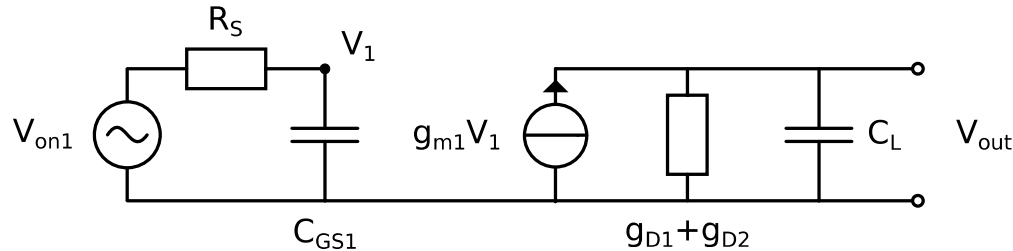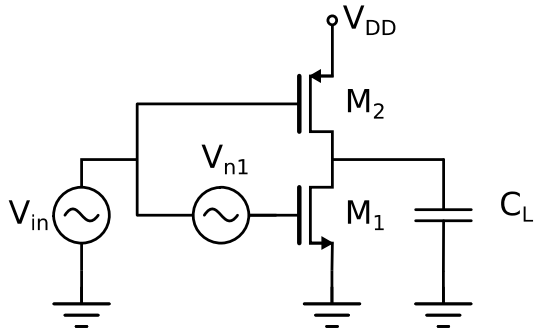
$$A(s) = \frac{-(g_{m1} + g_{m2})}{(s(C_{GS1} + C_{GS2})R_S + 1)(sC_L + g_{D1} + g_{D2})}$$


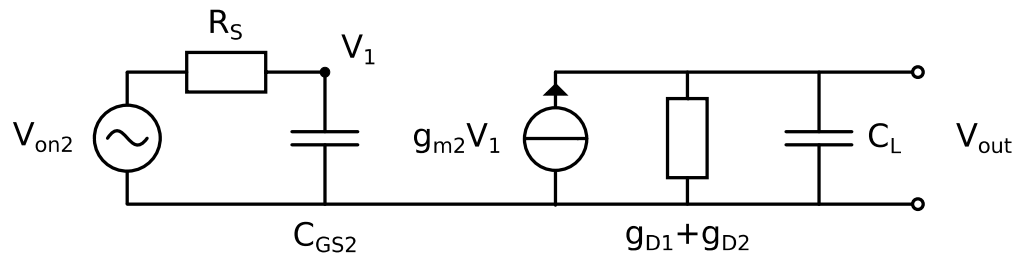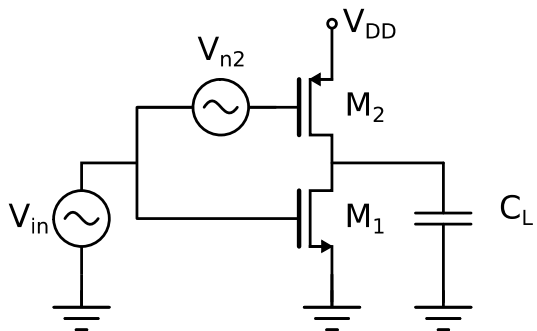
$$A(s) = \frac{-g_{m1}}{(sC_{GS1}R_S + 1)(sC_L + g_{D1} + g_{D2})}$$



$$A(s) = \frac{-g_{m2}}{(sC_{GS2}R_S + 1)(sC_L + g_{D1} + g_{D2})}$$

Output noise voltage:

$$v_{on}^2 = v_{on1}^2 + v_{on2}^2 = |A_{n1}|^2 v_{n1}^2 + |A_{n2}|^2 v_{n2}^2$$

Equivalent input noise voltage:

$$v_{on}^2 = |A|^2 \cdot v_{in,ek}^2$$

$$\Rightarrow v_{in,ek}^2 = \frac{v_{on}^2}{|A|^2} = \frac{|A_{n1}|^2}{|A|^2} v_{n1}^2 + \frac{|A_{n2}|^2}{|A|^2} v_{n2}^2$$

Assume single pole approximation

$$\frac{g_{DS1} + g_{DS2}}{C_L} \ll \frac{1}{R_S C_{GS1}}$$

$$A(s) = - \frac{g_{m1} + g_{m2}}{sC_L + g_{D1} + g_{D2}}$$

$$A_{n1} = - \frac{g_{m1}}{sC_L + g_{D1} + g_{D2}}$$

$$A_{n2} = - \frac{g_{m2}}{sC_L + g_{D1} + g_{D2}}$$

Equivalent input noise voltage:

$$v_{in,ek}^2 = \frac{g_{m1}^2 v_{n1}^2 + g_{m2}^2 v_{n2}^2}{(g_{m1} + g_{m2})^2}$$

Assume:

$$g_{m1} = g_{m2} = g_m$$

$$v_{n1}^2 = v_{n2}^2$$

$$v_{in,ek}^2 = \frac{2|g_m|^2 v_n^2}{(2g_m)^2} = \frac{1}{2} v_n^2$$

Noise of differential input stage

Assume single pole approximation with the dominant pole

$$p_1 = \frac{g_{DS2} + g_{DS4}}{C_L}$$

and the transfer function of


$$A(s) = \frac{V_1}{V_{in}} = -\frac{g_{m1}}{sC_L + g_{DS2} + g_{DS4}}$$

Noise transfer functions from sources V_{n1} and V_{n2}

$$A_{n1} = -A_{n2} = -\frac{g_{m1}}{sC_L + g_{DS2} + g_{DS4}}$$

and from sources V_{n3} and V_{n4}
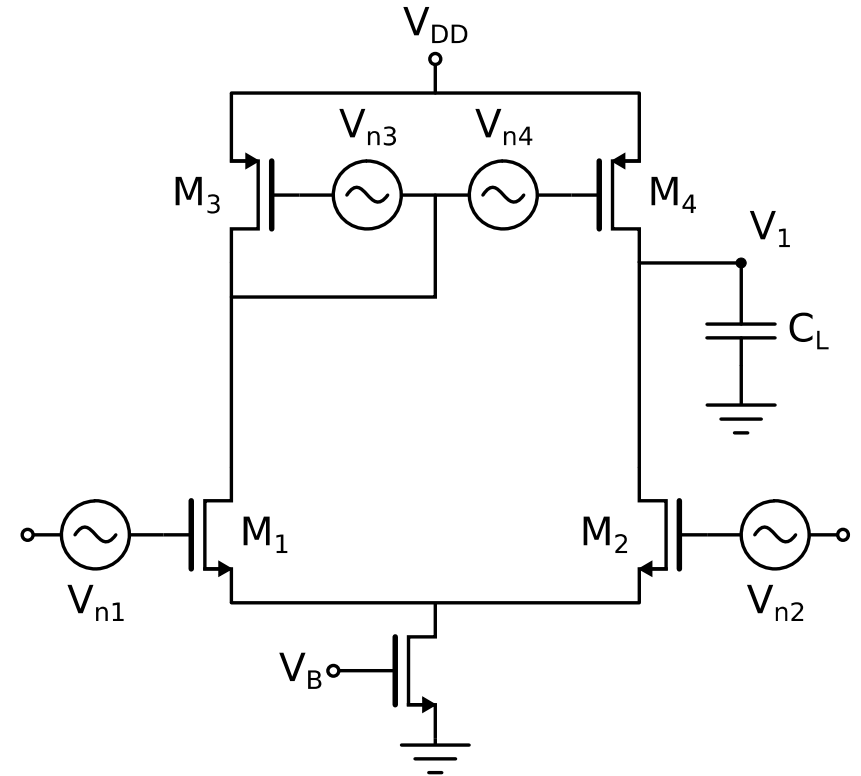
$$A_{n3} = -A_{n4} = -\frac{g_{m3}}{sC_L + g_{DS2} + g_{DS4}}$$



Total output noise is

$$V_{on}^2 = |A_{n1}|^2 (V_{n1}^2 + V_{n2}^2) + |A_{n3}|^2 (V_{n3}^2 + V_{n4}^2)$$


Equivalent noise source at the input is

$$V_{in,ek}^2 = \frac{|V_{on}|^2}{|A|^2} = \frac{|A_{n1}|^2}{|A|^2} (V_{n1}^2 + V_{n2}^2) + \frac{|A_{n3}|^2}{|A|^2} (V_{n3}^2 + V_{n4}^2)$$


Insert the noise and signal transfer functions

$$V_{in,ek}^2 = V_{n1}^2 + V_{n2}^2 + \left(\frac{g_{m3}}{g_{m1}} \right)^2 (V_{n3}^2 + V_{n4}^2)$$

Noise of two stage operational amplifier

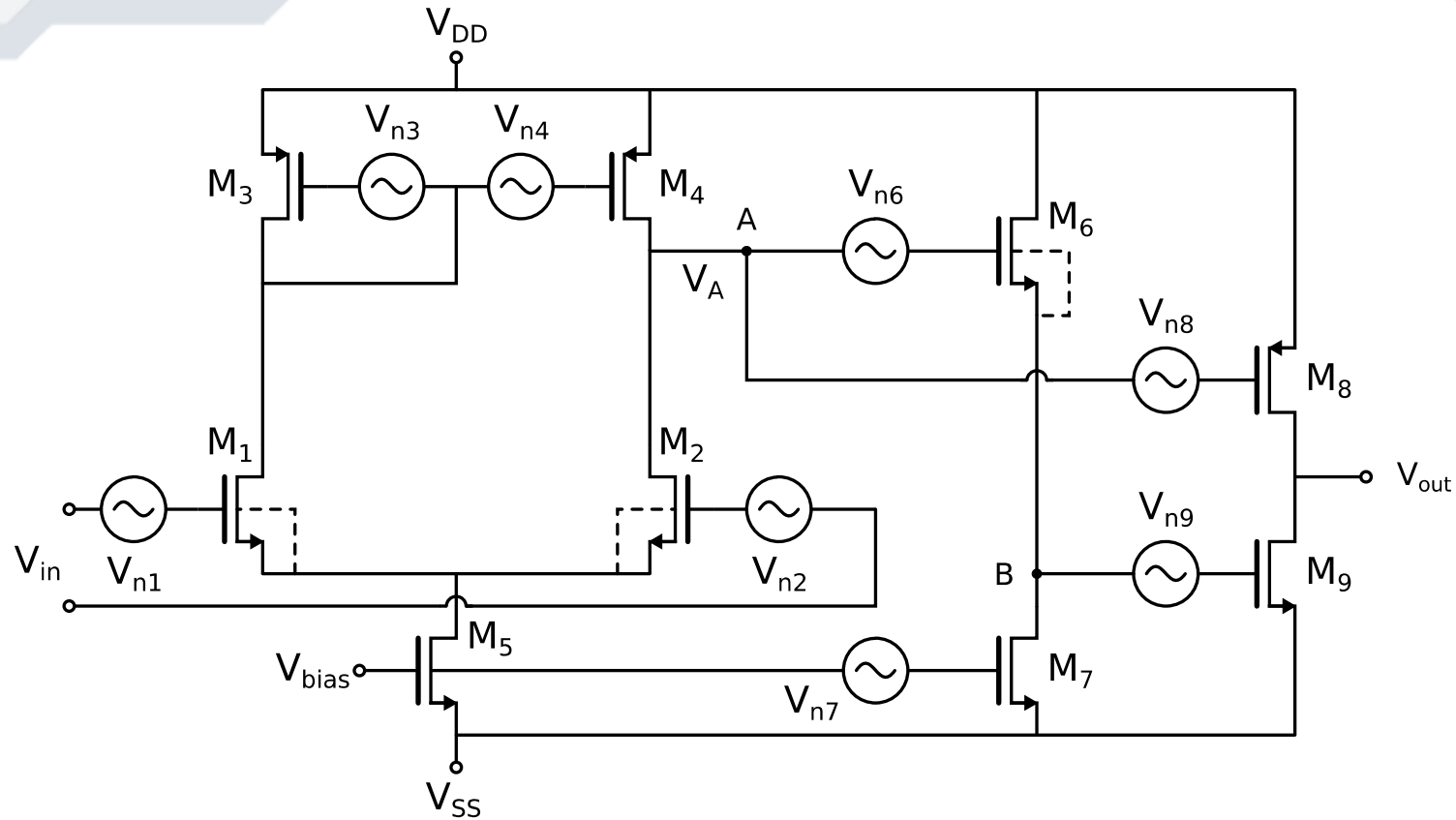

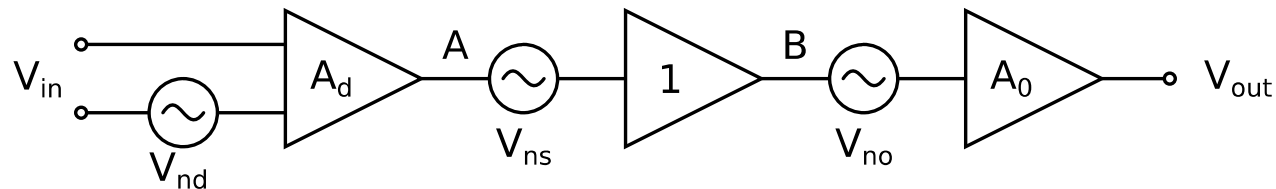Noise reduced to the inputs of different stages



Output noise of the amplifier (assume for source follower $A = 1$):

$$v_{on}^2 = |A_d A_0|^2 v_{nd}^2 + |A_0|^2 (v_{no}^2 + v_{ns}^2)$$

Equivalent input noise source:

$$\begin{aligned} v_{in,ek}^2 &= \frac{v_{on}^2}{|A_d A_0|^2} = v_{nd}^2 + \frac{|A_0|^2}{|A_d A_0|^2} (v_{no}^2 + v_{ns}^2) \\ &= v_{nd}^2 + \frac{1}{|A_d|^2} (v_{no}^2 + v_{ns}^2) \approx v_{nd}^2 (\approx v_{n1}^2 + v_{n2}^2) \end{aligned}$$

Noise of input stage:

$$v_{nd}^2 = v_{n1}^2 + v_{n2}^2 + \left(\frac{g_{m3}}{g_{m1}} \right)^2 (v_{n3}^2 + v_{n4}^2)$$

Noise of source follower:

$$v_{ns}^2 = v_{n6}^2 + \left(\frac{g_{m7}}{g_{m6}} \right)^2 v_{n7}^2$$

Noise of output stage:

$$v_{no}^2 = \frac{g_{m8}^2 v_{n8}^2 + g_{m9}^2 v_{n9}^2}{(g_{m8} + g_{m9})^2}$$

Noise analysis of OTA

Amplification in the input stage

$$A_1 = \frac{g_{m1}}{g_{m3}}$$


A_1 is small $\rightarrow$ noise of output stage also has to be taken into account!

Equivalent input noise source:

$$\begin{aligned} v_{in,eq}^2 &= v_{n1}^2 + v_{n2}^2 + \left(\frac{g_{m3}}{g_{m1}}\right)^2 (v_{n3}^2 + v_{n4}^2) + \left(\frac{g_{m5}}{g_{m1}}\right)^2 (v_{n5}^2 + v_{n6}^2) + \left(\frac{g_{m7}}{g_{m1}}\right)^2 (v_{n7}^2 + v_{n8}^2) \\ &= v_{n1}^2 + v_{n2}^2 + \left(\frac{g_{m3}}{g_{m1}}\right)^2 (v_{n3}^2 + v_{n4}^2) + B^{-2} \left(\frac{g_{m3}}{g_{m1}}\right)^2 (v_{n5}^2 + v_{n6}^2 + v_{n7}^2 + v_{n8}^2) \end{aligned}$$

$$\text{Assume } \begin{cases} B_1 = B_2 = B \\ B_3 = 1 \end{cases}$$

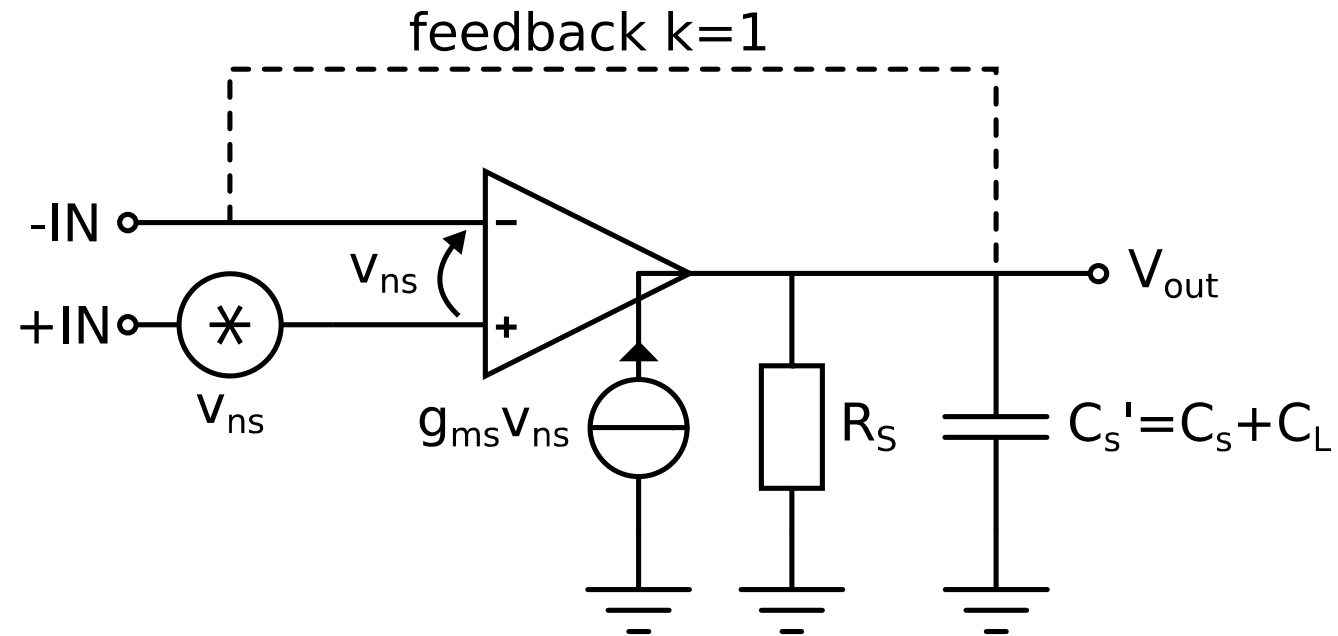Noise bandwidth of single stage amplifiers




Assume $A(s)$ is the amplification of amplifier and k is the feedback factor

$$\begin{aligned} A(s)v_{ns} - kA(s) \cdot V_{out} &= V_{out} \\ \Rightarrow V_{out} + kA(s) \cdot V_{out} &= A(s)v_{ns} \\ \Rightarrow \frac{V_{out}}{v_{ns}} &= \frac{A(s)}{1 + kA(s)} \end{aligned}$$

Assume single stage approximation
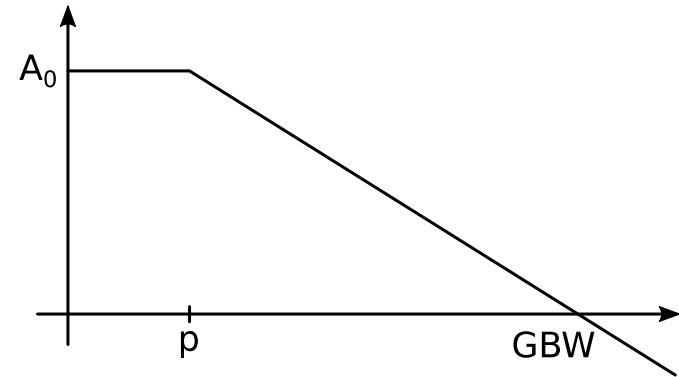
$$A(s) = \frac{g_{ms}R_s}{1 + sR_sC_s} \quad ; A_0 = g_{ms}R_s, p = R_sC_s, GBW = \frac{g_{ms}}{C_s}$$




and assume $k = 1$

$$\begin{aligned} \Rightarrow \frac{V_{out}}{v_{ns}} &= \frac{g_{ms}R_s}{1 + g_{ms}R_s + sR_sC_s} \quad ; A_0 = g_{ms}R_s \gg 1 \\ &\approx \frac{g_{ms}R_s}{g_{ms}R_s + sR_sC_s} = \frac{1}{1 + s\frac{C_s}{g_{ms}}} = \frac{1}{1 + \frac{s}{GBW}} \end{aligned}$$

$$\frac{V_{out}}{v_{ns}} = \frac{1}{1 + \frac{s}{GBW}}$$

Noise bandwidth in 2-stage amplifiers

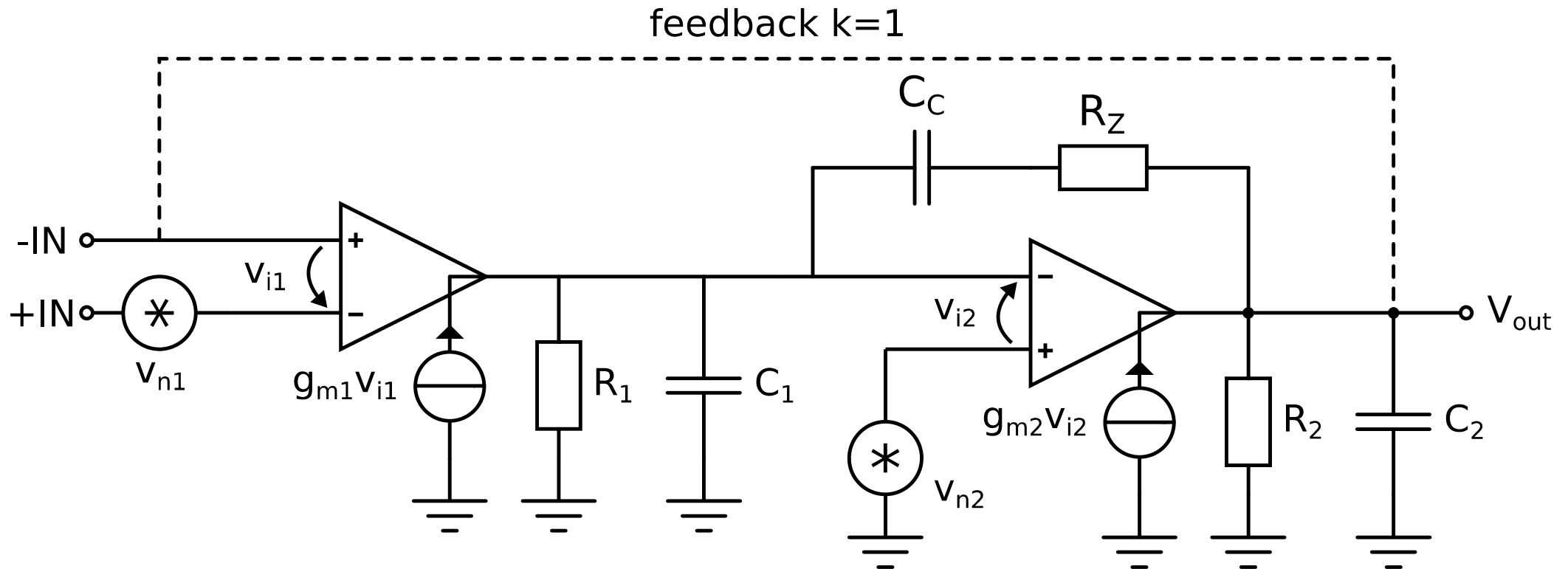

Open loop amplification:

$$A(s) = \frac{A_0 \left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right)}$$

For feedback amplifier

A) Noise of input stage

$$\begin{aligned} \frac{V_{on1}}{V_{n1}} &= \frac{A(s)}{1 + k(A(s))} \\ &= \frac{A_0 \left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) + A_0 \left(1 - \frac{s}{z}\right)} \\ &\approx \frac{\left(1 - sC_c \left(\frac{1}{g_{m2}} - R_z\right)\right)}{\underbrace{\left(1 - \frac{sC_c}{g_{m1}}\right)}_{1 - \frac{s}{GBW}} \underbrace{\left(1 - \frac{sC_L}{g_{m2}}\right)}_{\frac{p_2}{p_2}} \underbrace{\left(1 - sC_1 R_z\right)}_{\frac{p_3}{p_3}}} \\ &\approx \frac{\left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{GBW}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right)} \quad ; p_3 = -z \end{aligned}$$

B) Noise of output stage

$$\begin{aligned} \frac{V_{on2}}{V_{n2}} &= \frac{A_2(s)}{1 + k(A(s))} \quad ; A_2(s) = \frac{A_2 \left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right)} \\ &= \frac{A_2 \left(1 + \frac{s}{p_1}\right) \left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) + A_0 \left(1 - \frac{s}{z}\right)} \\ &\text{assume } p_3 = z \\ &\Rightarrow \frac{V_{on2}}{V_{n2}} = \frac{A_2 \left(1 + \frac{s}{p_1}\right) \left(1 - \frac{s}{z}\right)}{\left(1 + \frac{s}{p_1 A_0}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) A_0} \\ &= \frac{\left(1 + \frac{s}{p_1}\right)}{\left(1 - \frac{s}{GBW}\right) \left(1 + \frac{s}{p_2}\right) A_1} = \frac{\left(1 - s \frac{A_1}{GBW}\right)}{\left(1 - \frac{s}{GBW}\right) \left(1 - \frac{s}{p_2}\right) A_1} \\ &= \frac{(1 + sC_1 R_1)}{\left(1 - \frac{s}{GBW}\right) \left(1 - \frac{sC_L}{g_{m2}}\right) A_1} \end{aligned}$$

Denominator:

$$\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) \left(1 + \frac{s}{p_3}\right) + A_0 \left(1 - \frac{s}{z}\right)$$

Assume $-z = p_3$



$$\left[\left(1 + \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) + A_0 \right] \left[\left(1 + \frac{s}{p_3}\right) \right]$$
$$\left[A_0 + 1 + s \left(\frac{1}{p_1} + \frac{1}{p_2} \right) + \frac{s^2}{p_1 p_2} \right] \left[1 + \frac{s}{p_3} \right]$$

Assume $A_0 \gg 1$, $p_1 \ll p_2$


$$A_0 \left[1 + s \frac{1}{p_1 A_0} + \frac{s^2}{A_0 p_1 p_2} \right] \left[1 + \frac{s}{p_3} \right]$$

Assume $GBW = A_1 p_1 \ll p_2$
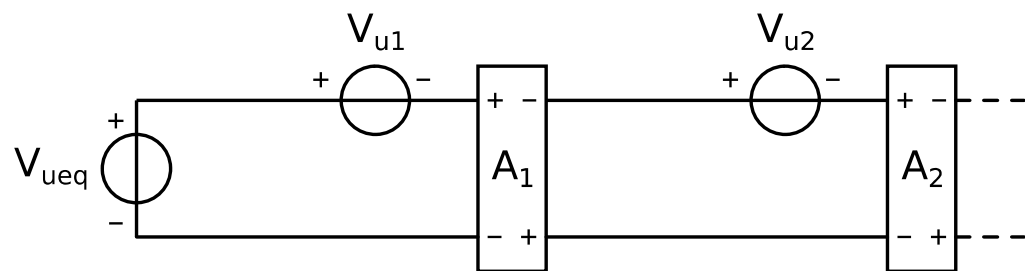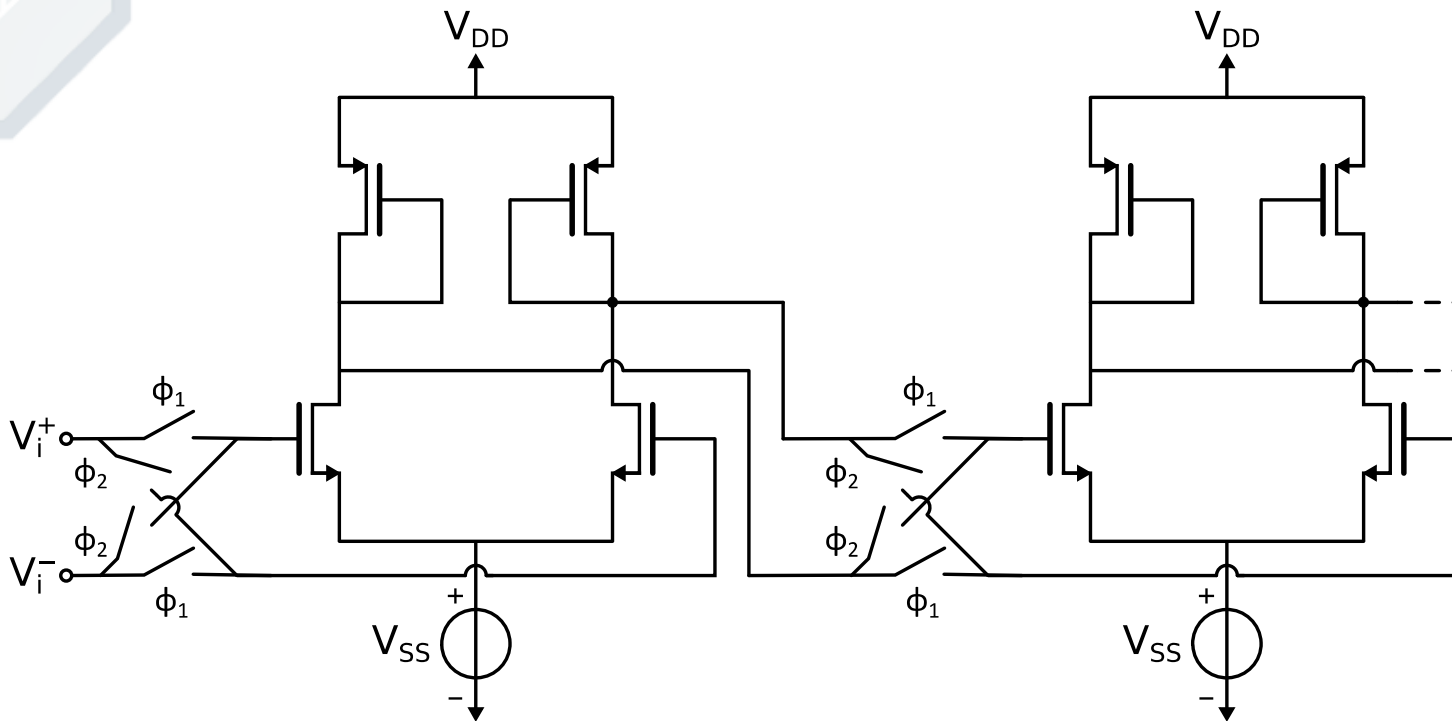
$$A_0 \left[1 + s \frac{1}{p_1 A_0} \right] \left[1 + \frac{s}{p_2} \right] \left[1 + \frac{s}{p_3} \right]$$



$$V_{ueq} = V_{u1} + V_{u2}/A_1$$

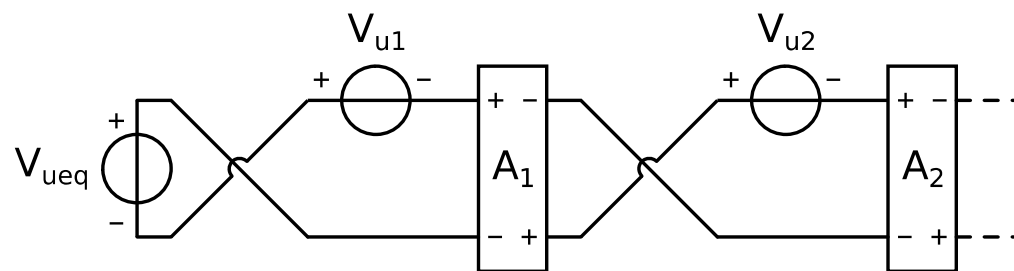

$$V_{ueq} = V_{u1} + V_{u2}/A_1$$

$$V_{ueq}(\text{Average}) = V_{u2}/A_1$$

PSRR – Power Supply Rejection Ratio

Definition:


$$\text{PSRR} = 20 \log \left| \frac{A_V}{A_{V_{DD}}} \right|$$

$$\text{PSRR} = 20 \log \left| \frac{A_V}{A_{V_{SS}}} \right|$$


$$A_V = \frac{V_{\text{out}}}{V_{\text{in}}}$$

$$A_{V_{DD}} = \frac{V_{\text{out}}}{V_{DD}}$$
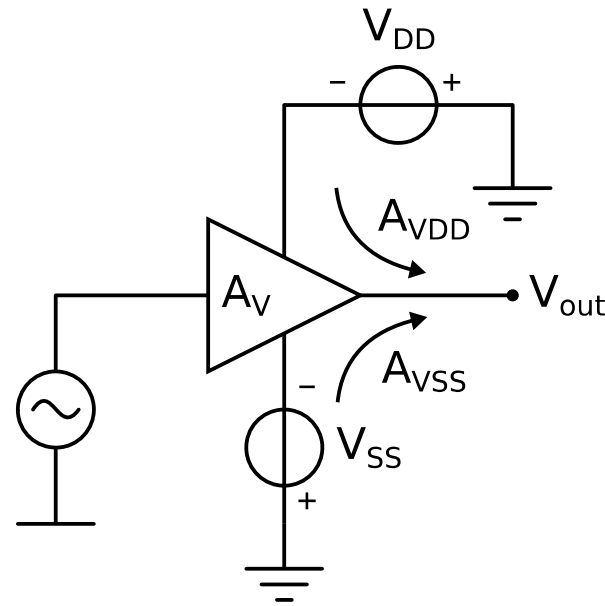
$$A_{V_{SS}} = \frac{V_{\text{out}}}{V_{SS}}$$




Feedback amplifier

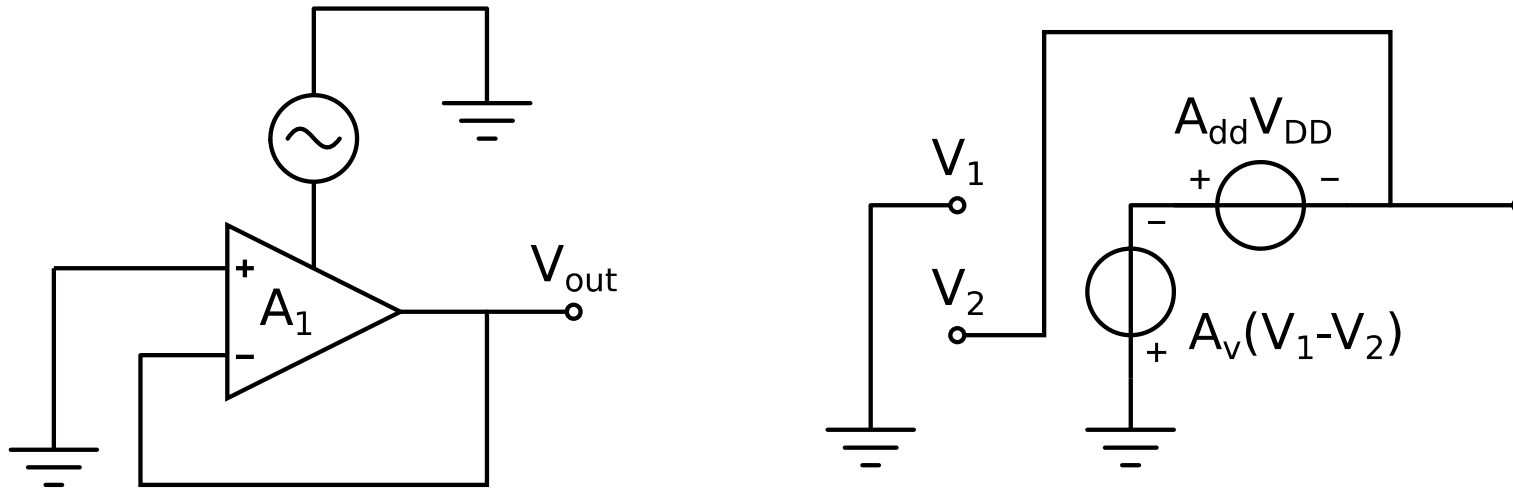



$$V_{out} = \frac{A_{dd}}{1 + A_v} V_{dd} \approx \frac{A_{dd}}{A_v} V_{dd} = \frac{1}{PSRR} V_{dd}$$

Definition: $PSRR \approx \frac{A_v}{A_{vdd}} \Rightarrow PSRR = \frac{V_{dd}}{V_{out}}$

PSRR of V_{DD} in 2-stage amplifier

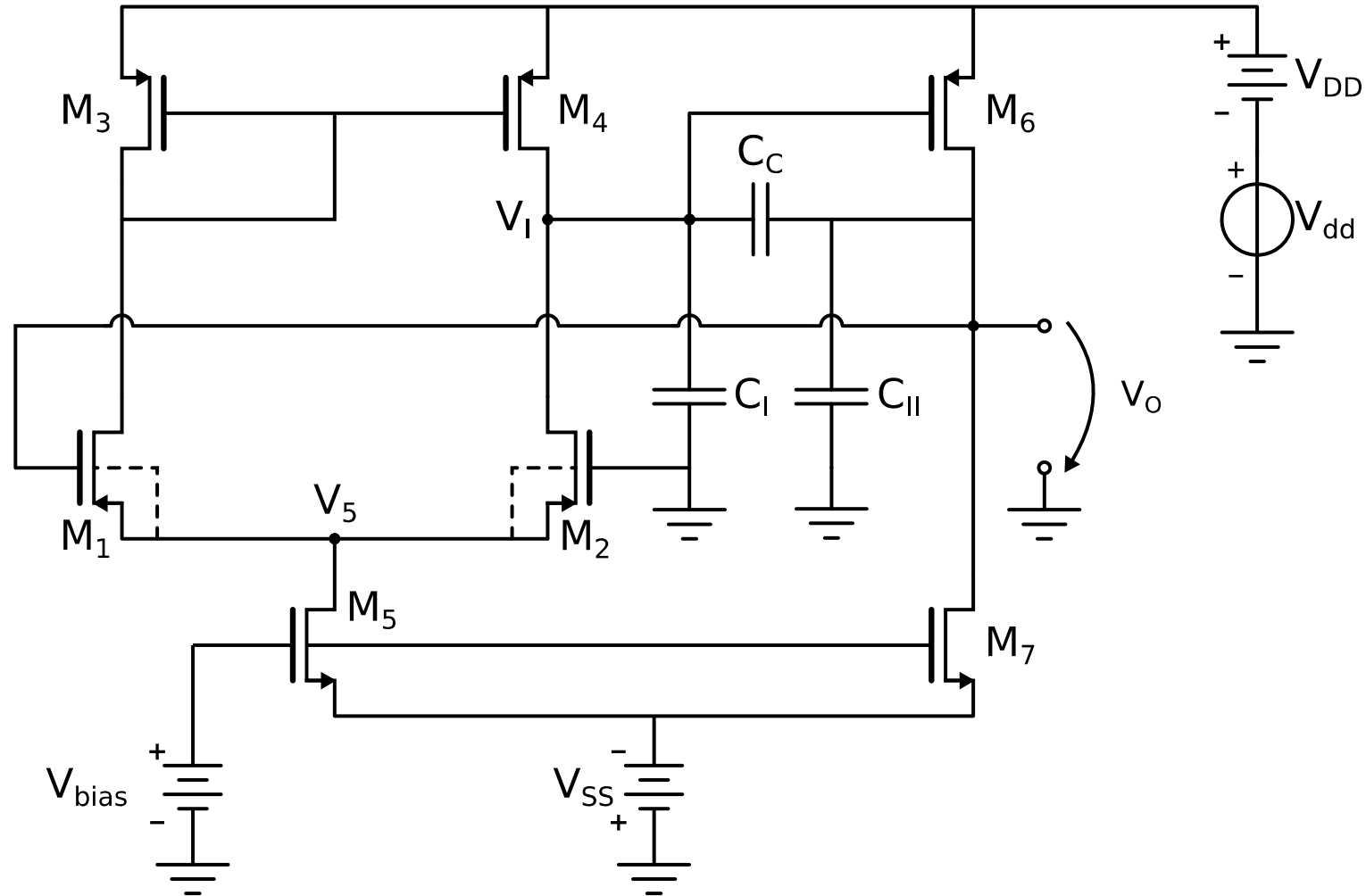

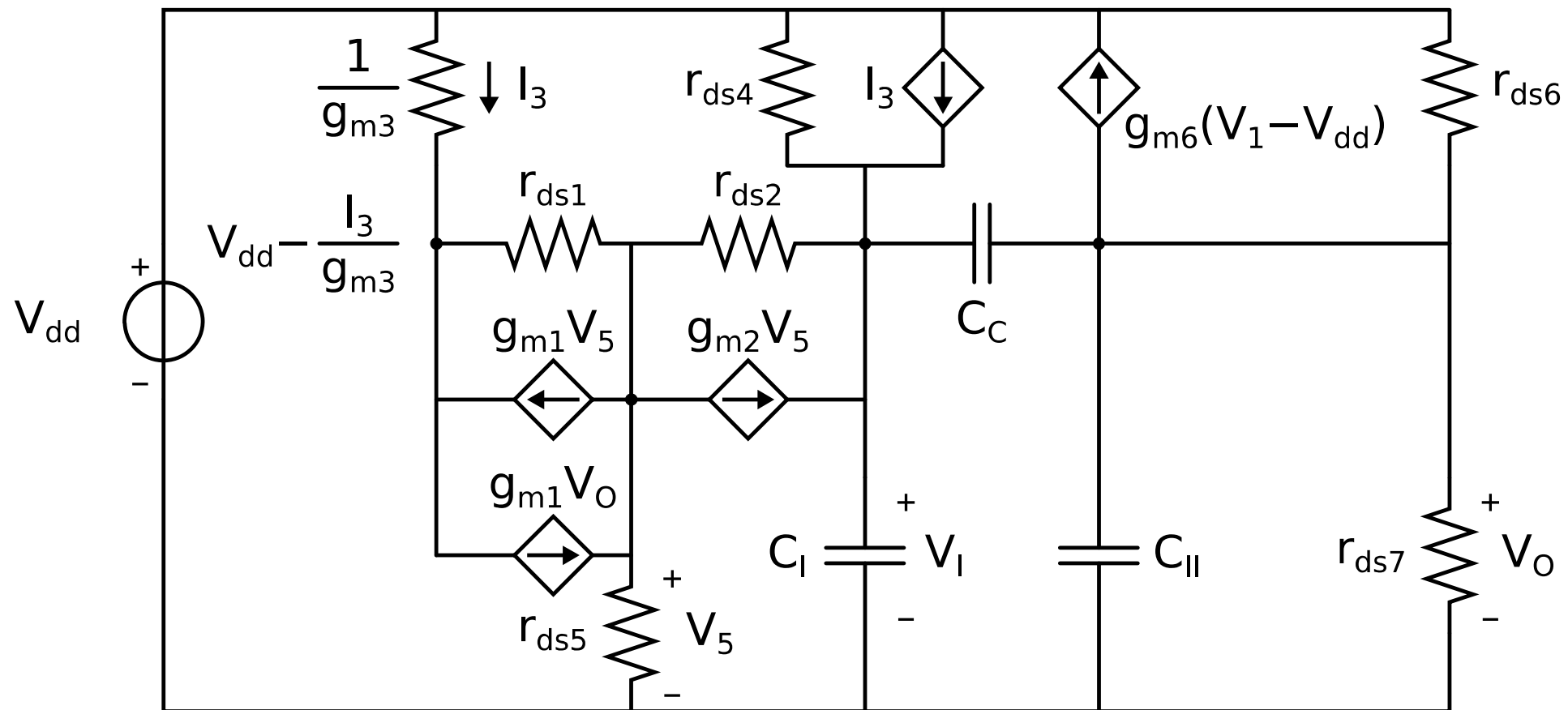

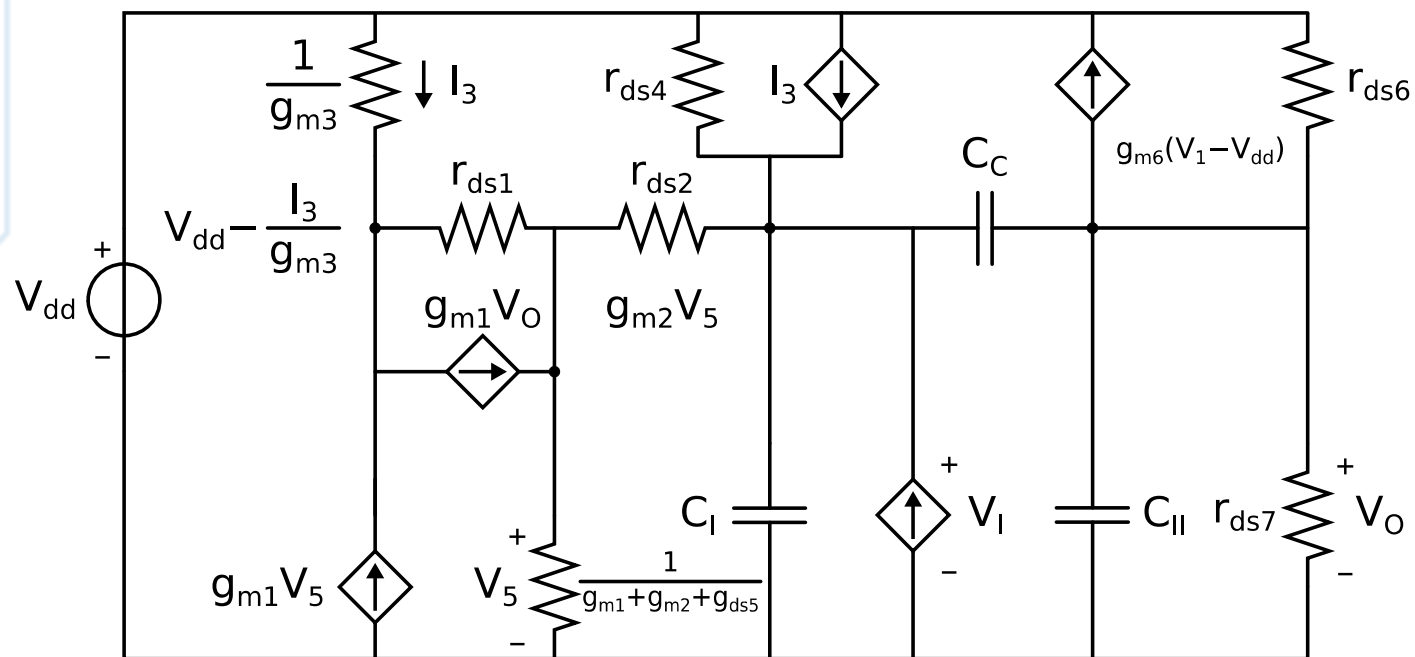



$$I_3 = g_{m1} V_O + g_{ds1} \left(V_{DD} - \frac{I_3}{g_{m3}} \right)$$

$$\approx g_{m1} V_O + g_{ds1} V_{dd}$$

$$I_3 + \frac{g_{DS1}}{g_{m3}} \cdot I_3 = \left(1 + \frac{g_{DS1}}{g_{m3}} \right) I_3 \approx I_3$$

$$g_{DS1} \ll g_{m3}$$

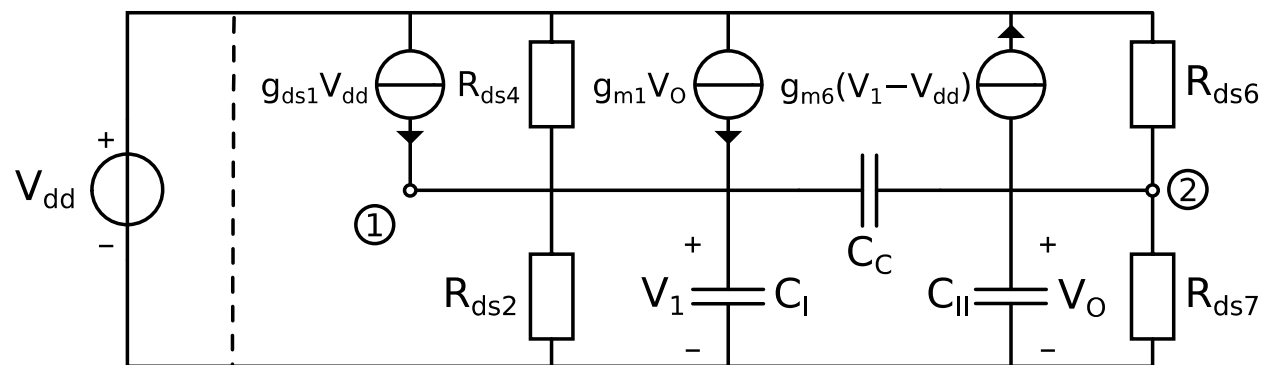

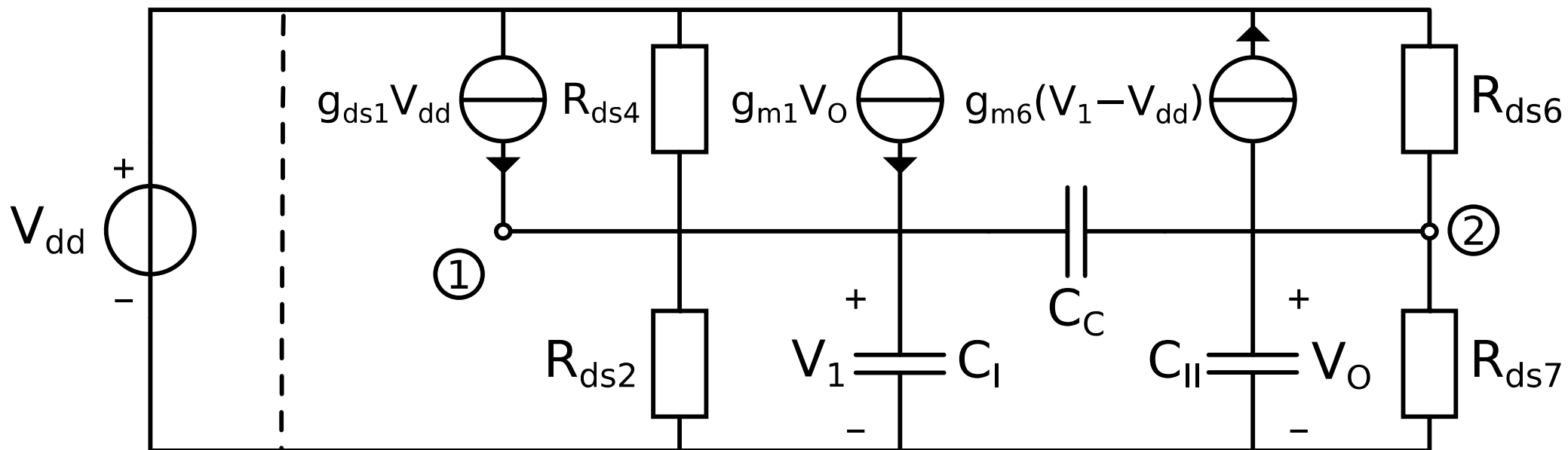

Current equations for nodes 1 and 2


$$(1) (g_{DS1} + g_{DS4})V_{DD} = (g_{DS2} + g_{DS4} + sC_c + sC_l)V_1 - (g_{m6} + sC_c)V_O$$

$$(2) (g_{m6} + g_{DS6})V_{DD} = (g_{m6} - sC_c)V_1 + (g_{DS6} + g_{DS7} + sC_c + sC_l)V_O$$



$$\Rightarrow \frac{V_{DD}}{V_O} = \frac{s^2(C_c C_l + C_l C_c + C_c C_c) + s[(g_{DS2} + g_{DS4})(C_c + C_l) + (g_{DS6} + g_{DS7})(C_c + C_l) + C_c(g_{m6} - g_{m1})] + (g_{DS2} + g_{DS4})(g_{DS6} + g_{DS7}) + g_{m1}g_{m6}}{s[C_c(g_{m6} + g_{DS2} + g_{DS4} + g_{DS6}) + C_l(g_{m6} + g_{DS6})] + (g_{DS2} + g_{DS4})g_{DS6}}$$

Let us solve the zeros by using the dominant pole method:

$$PSRR = \frac{V_{DD}}{V_O} \approx \frac{g_{m1}g_{m6}}{\underbrace{(g_{DS2} + g_{DS4})g_{DS6}}_{\approx 2A_0}} \left[\frac{\left(\frac{sC_c}{g_{m1}} + 1 \right) \left(\frac{s(C_c C_l + C_l C_c + C_c C_c)}{g_{m6}C_c} + 1 \right)}{\frac{sg_{m6}C_c}{(g_{DS2} + g_{DS4})g_{DS6}} + 1} \right] \approx 2A_{V_O} \left[\frac{\left(\frac{s}{GBW} + 1 \right) \left(\frac{s}{p_2} + 1 \right)}{\underbrace{\frac{2sA_0}{GBW} + 1}_{p_1}} \right]$$

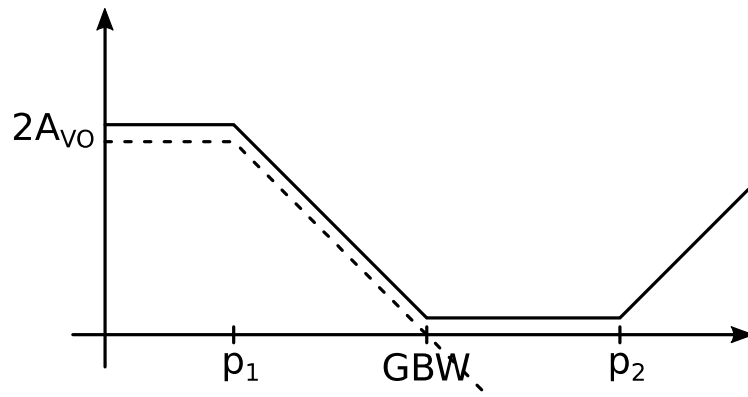

PSRR of V_{SS} in 2-stage amplifier

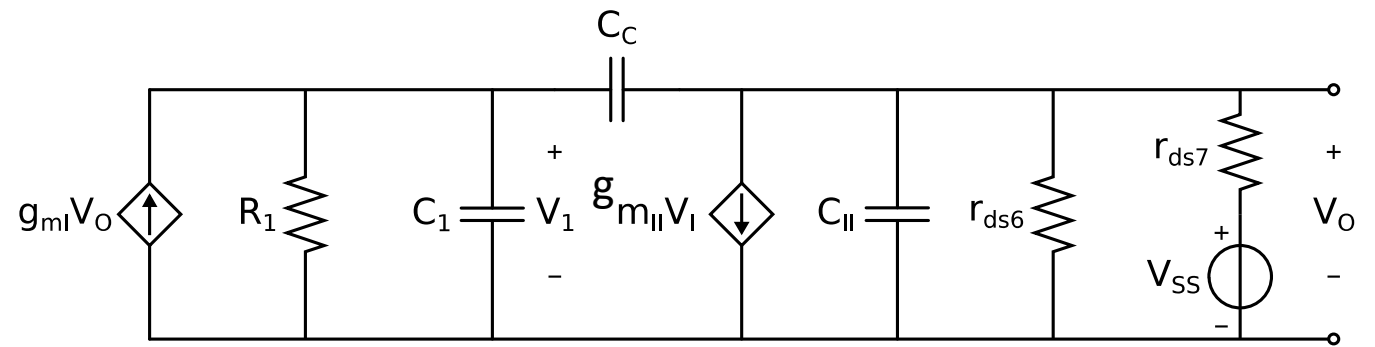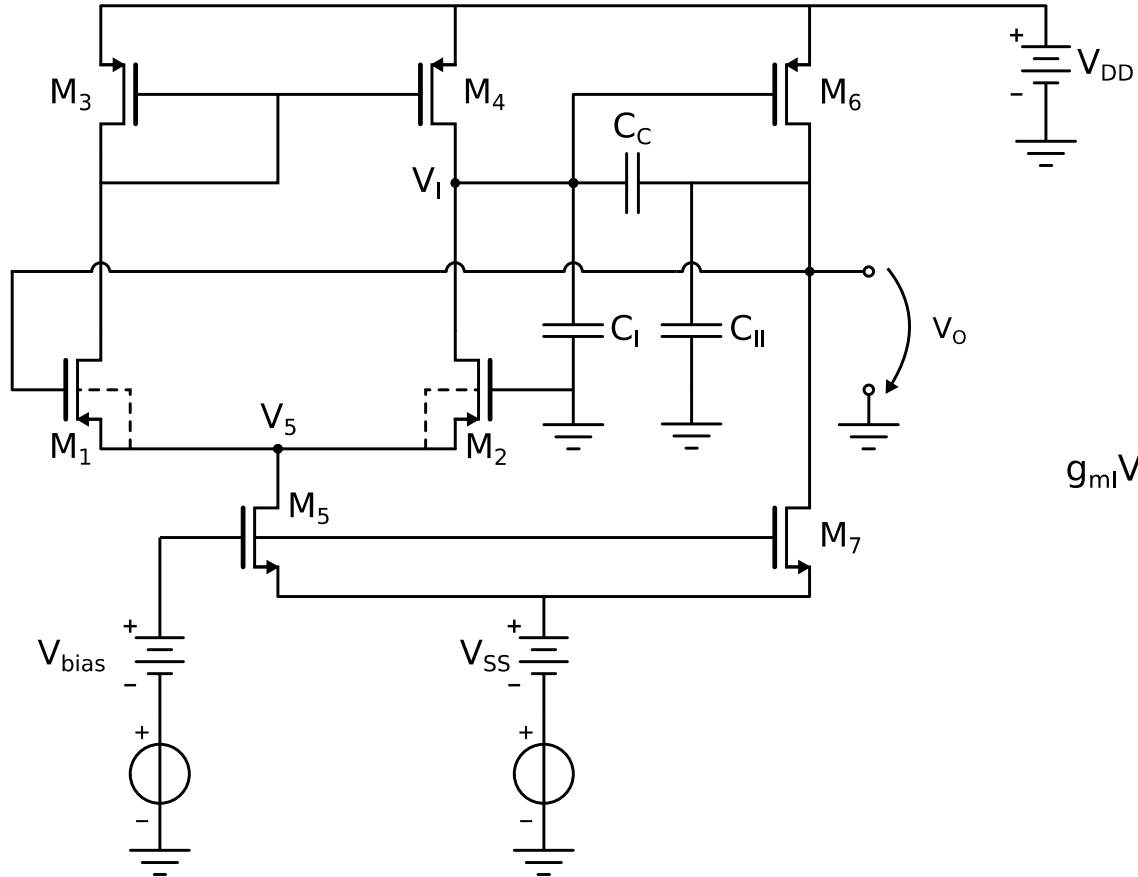

$$\frac{1}{g_{DS2} + g_{DS4}} = R_1$$

$$g_{mII} = g_{m6}$$

Current equations for nodes 1 and 2


$$1 \quad (g_{DS2} + g_{DS4} + sC_c + sC_l)V_1 - (g_{m1} + sC_c)V_O = 0$$

$$2 \quad (g_{m6} - sC_c)V_1 + (g_{DS6} + g_{DS7} + sC_c + sC_L)V_O = g_{DS7}V_{SS}$$


$$\Rightarrow \frac{V_{SS}}{V_O} = \frac{s^2(C_c C_l + C_l C_L + C_L C_c) + s[(g_{DS2} + g_{DS4})(C_c + C_L) + (g_{DS6} + g_{DS7})(C_c + C_l) + C_c(g_{m6} - g_{m1})] + (g_{DS2} + g_{DS4})(g_{DS6} + g_{DS7}) + g_{m1}g_{m6}}{s[(C_c + C_l) + (g_{DS2} + g_{DS4})]g_{DS7}}$$

Let us solve the zeroes by using the dominant pole method:
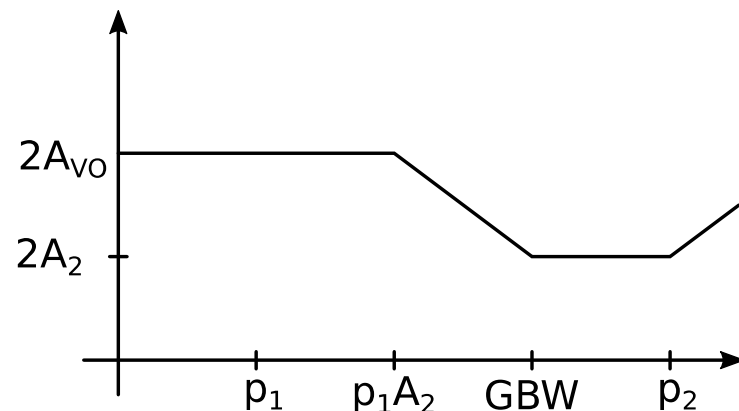
$$PSRR = \frac{V_{SS}}{V_O} \approx \frac{g_{m1}g_{m6}}{(g_{DS2} + g_{DS4})g_{DS7}} \left[\frac{\left(\frac{sC_c}{g_{m1}} + 1 \right) \left(\frac{s(C_c C_l + C_l C_L + C_L C_c)}{g_{m6}C_c} \right)}{\frac{s(C_c + C_l)}{g_{DS2} + g_{DS4}} + 1} \right] \approx 2A_{V_O} \left[\frac{\left(\frac{s}{GBW} + 1 \right) \left(\frac{s}{p_2} + 1 \right)}{\frac{s}{\left(\frac{GBW}{A_1} \right)} + 1} \right]$$



Note: $\frac{GBW}{A_1} = A_2 \cdot p_1$

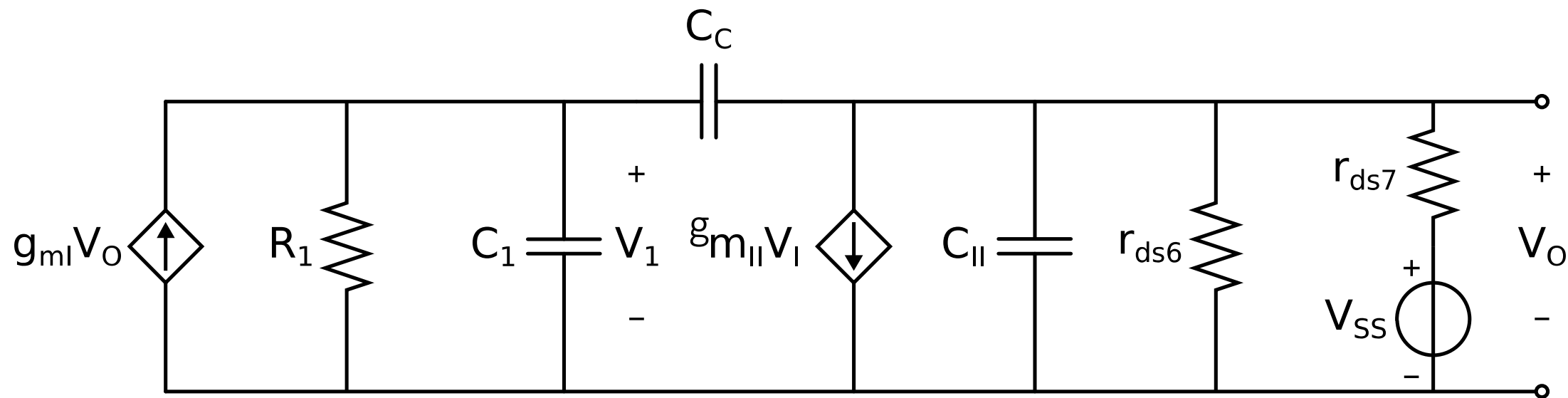

$$\frac{1}{g_{DS2} + g_{DS4}} = R_1$$

$$g_{mII} = g_{m6}$$