


Problem 1: Transfer functions of a DC motor

The block diagram of a DC motor is shown in the figure.

(a) Derive the transfer functions


$$G_{\omega u}(s) = \frac{\omega_M(s)}{u_a(s)} \quad \text{and} \quad G_{\omega T}(s) = \frac{\omega_M(s)}{T_L(s)}$$

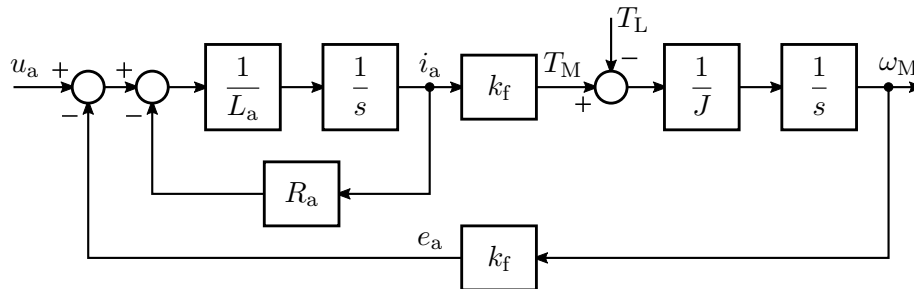(b) Replace the electric dynamics of the machine with the DC gain and formulate the transfer functions $G_{\omega u}(s)$ and $G_{\omega T}(s)$.



Solution

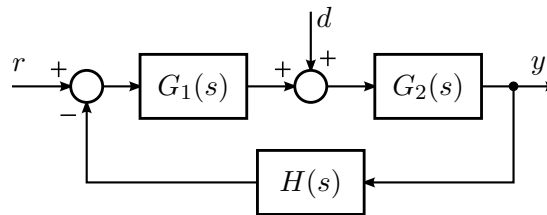(a) Consider a closed-loop system shown in the figure.




The following equations hold for the closed-loop transfer functions:

$$\frac{y(s)}{r(s)} = \frac{G_1(s)G_2(s)}{1 + G_1(s)G_2(s)H(s)} \tag{1}$$

$$\frac{y(s)}{d(s)} = \frac{G_2(s)}{1 + G_1(s)G_2(s)H(s)} \tag{2}$$

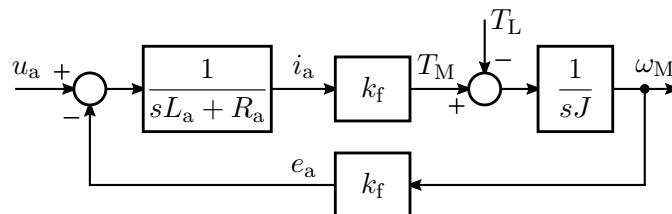It is relatively easy to derive these equations if one has forgotten them. Using (1), the block diagram given in the problem is first transformed to the following form:



Using (1), we can write the transfer function from the voltage to the speed as

$$G_{\omega u}(s) = \frac{\omega_M(s)}{u_a(s)} = \frac{\frac{1}{sL_a + R_a} k_f \frac{1}{sJ}}{1 + \frac{1}{sL_a + R_a} k_f \frac{1}{sJ} k_f} = \frac{\frac{k_f}{JL_a}}{s^2 + s \frac{R_a}{L_a} + \frac{k_f^2}{JL_a}}$$


Using (2), the transfer function from the load torque to the speed becomes

$$G_{\omega T}(s) = \frac{\omega_M(s)}{T_L(s)} = -\frac{\frac{1}{sJ}}{1 + \frac{1}{sL_a + R_a} k_f \frac{1}{sJ} k_f} = -\frac{\frac{1}{J} \left(s + \frac{R_a}{L_a} \right)}{s^2 + s \frac{R_a}{L_a} + \frac{k_f^2}{JL_a}}$$

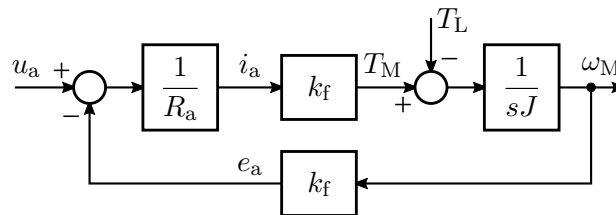(b) The electric dynamics of the machine

$$Y_a(s) = \frac{1}{sL_a + R_a}$$

is replaced with the DC gain by substituting $s = 0$. The corresponding block is shown in the following figure:



The transfer functions can be derived from this block diagram in a fashion similar to Part (a) of the problem. The same result is obtained by multiplying the numerator and denominator of the derived transfer functions by L_a and then substituting $L_a = 0$:

$$G_{\omega u}(s) = \frac{\omega_M(s)}{u_a(s)} = \frac{\frac{k_f}{JR_a}}{s + \frac{k_f^2}{JR_a}}$$

$$G_{\omega T}(s) = \frac{\omega_M(s)}{T_L(s)} = -\frac{1/J}{s + \frac{k_f^2}{JR_a}}$$


The time constant of the first-order system is

$$\tau = \frac{JR_a}{k_f^2}$$

which depends strongly on the flux factor k_f of the motor (and increases when the flux factor is decreased).

Problem 2: Current ripple

The parameters of a DC motor are: $R_a = 1 \Omega$, $L_a = 10 \text{ mH}$, and $k_f = 4 \text{ Vs}$. The average steady-state current taken by the motor is $I_a = 100 \text{ A}$ and the rotor speed is 560 r/min . The motor is supplied from a four-quadrant DC-DC converter, where the unipolar PWM is applied. The DC-bus voltage is $U_{dc} = 450 \text{ V}$ and the switching (carrier) frequency is $f_{sw} = 4 \text{ kHz}$. Calculate the peak-to-peak current ripple.

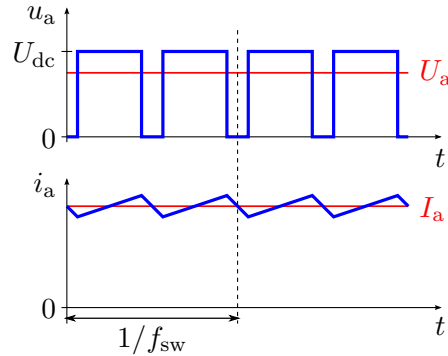**Solution**

The electrical dynamics of the DC motor are governed by

$$L_a \frac{di_a(t)}{dt} = u_a(t) - R_a i_a(t) - e_a(t) \quad (3)$$

The rotor angular speed is

$$\omega_M = 2\pi \cdot \frac{560 \text{ r/min}}{60 \text{ s/min}} = 58.6 \text{ rad/s}$$

and the back-emf is $E_a = k_f \omega_M = 4 \text{ Vs} \cdot 58.6 \text{ rad/s} = 234.6 \text{ V}$. Based on (3), the average armature voltage is

$$U_a = R_a I_a + E_a = 1 \Omega \cdot 100 \text{ A} + 234.6 \text{ V} = 334.6 \text{ V}$$

in steady state.


The figure below illustrates the waveforms of the armature voltage u_a and the armature current i_a . The average voltage during the switching period T_{sw} is

$$\bar{u}_a = \frac{1}{T_{sw}} \int_0^{T_{sw}} u_a(t) dt = \frac{2\Delta t}{T_{sw}} U_{dc} \quad (4)$$

where Δt is the duration of the positive voltage pulse (see the figure). The duration is

$$\Delta t = \frac{U_a}{U_{dc}} \frac{T_{sw}}{2} = \frac{U_a}{U_{dc}} \frac{1}{2f_{sw}}$$

since $U_a = \bar{u}_a$ in steady state.

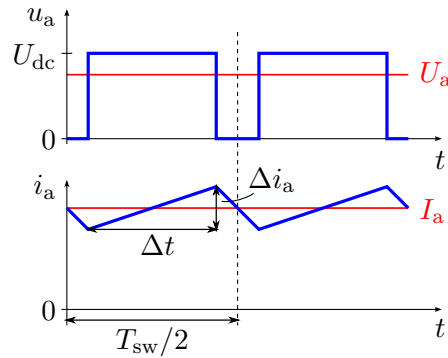

In the time scale of switching periods, the dynamics in (3) can be approximated as

$$L_a \frac{di_a(t)}{dt} = u_a(t) - R_a I_a - E_a = u_a(t) - U_a \quad (5)$$

The change Δi_a in the current during the positive voltage pulse $u_a(t) = U_{dc}$ is

$$\begin{aligned} \Delta i_a &= \frac{U_{dc} - U_a}{L_a} \Delta t \\ &= \frac{U_{dc} - U_a}{L_a} \frac{U_a}{U_{dc}} \frac{1}{2f_{sw}} \\ &= \frac{450 \text{ V} - 334.6 \text{ V}}{10 \text{ mH}} \cdot \frac{334.6 \text{ V}}{450 \text{ V}} \frac{1}{2 \cdot 4 \text{ kHz}} = 1.1 \text{ A} \end{aligned}$$

This peak-to-peak current ripple is roughly 1% of the average current.

Remark 1: Naturally, the same result would be obtained, if the zero-voltage condition $u_a(t) = 0$ were used:

$$\Delta i_a = \frac{U_a}{L_a} \left(\frac{T_{sw}}{2} - \Delta t \right)$$

Remark 2: The switching period is $T_{sw} = 1/f_{sw} = 1/(4 \text{ kHz}) = 250 \mu\text{s}$ and the electrical time constant of the armature winding is $\tau_a = L_a/R_a = 10 \text{ ms}$. Since τ_a is much longer (40 times) than T_{sw} , the approximation (5) holds well.