

ELEC-E8412 Power Electronics

HW#2_ Solutions

Problem 1:

For a half-wave rectifier with resistive load with $v_{in}=100\sin(400t)$ V and $R=10\ \Omega$ determine

- (a) the average load current,
- (b) the rms load current,
- (c) the apparent power supplied by the source, and
- (d) the power factor of the rectifier.

Solution:

Part (a)

The voltage across the resistor in a half-wave rectified sine wave with peak value $V_m = 100$ V.

The average voltage in a half-wave rectifier is V_m/π , and average current is:

$$\langle i \rangle = \frac{V_m}{\pi R} = \frac{100}{\pi * 10} = 3.18\text{ A}$$

Part (b) the rms load current

$$I_{rms} = \frac{V_m}{2R} = \frac{100}{2 * 10} = 5\text{ A}$$

Part (c) the apparent power supplied by the source

$$\text{Apparent power} = V_{in,rms} * I_{in,rms} = \frac{100}{\sqrt{2}} * 5 = 353.553\text{ VA}$$

Part (d) power factor

$$Pf = \frac{R * I_{rms}^2}{V_{in-rms} * I_{in-rms}} = \frac{10 * 5^2}{\frac{100}{\sqrt{2}} * 5} = 0.707$$

Problem 2:

A half-wave rectifier has a source of 120 V rms at 60 Hz and an R-L load with $R=10\ \Omega$ and $L=10\ \text{mH}$. Determine

- (a) an expression for the load current,
- (b) the average current,
- (c) the power absorbed by the resistor, and
- (d) the power factor.

Hint: $\beta=3.5\ \text{Rad}$.

Solution:

Part (a)

For a half-wave rectifier with R-L load:

$$i(t) = \frac{V_m}{\sqrt{R^2 + (L\omega)^2}} \sin(\omega t - \theta) + A e^{-t/L/R}$$

$$\text{Where, } \theta = \tan^{-1}\left(\frac{L\omega}{R}\right) \text{ and } A = \frac{V_m \sin \theta}{\sqrt{R^2 + (L\omega)^2}}$$

For the given problem:

$$Z = \sqrt{R^2 + (L\omega)^2} = \sqrt{(10)^2 + (0.01 * 377)^2} = 10.687$$

$$\theta = \tan^{-1}\left(\frac{L\omega}{R}\right) = \tan^{-1}\left(\frac{3.77}{10}\right) = \tan^{-1}(0.377) = 0.36\ \text{rad} = 20.64^\circ$$

$$i(\omega t) = \frac{120\sqrt{2}}{10.687} \sin(\omega t - 0.36) + \frac{120\sqrt{2} * \sin(0.36)}{10.687} e^{-\omega t/0.377}$$

$\beta = 3.5\ \text{rad}$ is given by the problem, so

$$i(\omega t) = 15.88 \sin(\omega t - 0.36) + 5.59 e^{-\omega t/0.377} \quad \text{for } 0 \leq \omega t \leq 3.5$$

$$i(\omega t) = 0 \quad \text{for } 3.5 \leq \omega t \leq 2\pi$$

Part (b)

$$\langle i(\omega t) \rangle = \frac{1}{2\pi} \int_0^{3.5} [15.88 \sin(\omega t - 0.36) + 5.59e^{-\omega t/0.377}] d(\omega t) = 5.23 \text{ A}$$

Part (c) the power absorbed by the resistor is $P = R * I_{rms}^2$

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{3.5} [15.88 \sin(\omega t - 0.36) + 5.59e^{-\omega t/0.377}]^2 d(\omega t)} = 8.037 \text{ A}$$

$$P = R * I_{rms}^2 = 10 * (8.037)^2 = 645.93 \text{ W}$$

Part (d)

$$Pf = \frac{P}{V_{in-rms} * I_{in-rms}} = \frac{645.93}{120 * 8.037} = 0.67$$

Problem 3:

A half-wave rectifier has a 120 V rms, 60 Hz ac source. The load is 500 Ω . Determine the value of the filter capacitor to keep the peak-to-peak ripple across the load to less than 2 V. Determine the average and peak values of the diode current.

Solution:

$$\Delta V_0 \approx \frac{V_m}{fRC} \quad C > \frac{120\sqrt{2}}{60 * 500 * 2} = 2828 \mu\text{F}$$

$$\Delta V_0 = V_m(1 - \sin\alpha)$$

$$\alpha = \sin^{-1}\left(1 - \frac{\Delta V_0}{V_m}\right) = \sin^{-1}\left(1 - \frac{2}{120\sqrt{2}}\right) = 1.417 \text{ rad} = 81.2^\circ$$

$$i_{d-peak} = V_m \left(\omega C \cos\alpha + \frac{\sin\alpha}{R} \right) = 120\sqrt{2} \left(2828 * 10^{-6} * 2\pi * 60 * \cos(81.2^\circ) + \frac{\sin(81.2^\circ)}{500} \right)$$

$$i_{d-peak} = 28.03 \text{ A}$$

$$\langle i_d \rangle = \frac{\langle V_o \rangle}{R}$$

$$\langle V_o \rangle \approx V_{o,peak} - \frac{\Delta V_o}{2} = V_m - \frac{V_m}{2fRC} \approx V_m$$

$$\langle i_d \rangle = \frac{V_m}{R} = \frac{120\sqrt{2}}{500} = 0.339 \text{ A}$$

Problem 4:

A controlled half-wave rectifier has an ac source of 240 V rms at 60 Hz. The load is a 30- Ω resistor.

- Determine the delay angle such that the average load current is 3.0 A.
- Determine the power absorbed by the load.
- Determine the power factor.

Solution:

Part (a):

$$\langle i \rangle = \frac{V_m}{2\pi R} (1 + \cos\alpha) = \frac{240\sqrt{2}}{2\pi * 30} (1 + \cos\alpha) = 3 \text{ A}$$

$$\rightarrow \alpha = \cos^{-1} \left(\frac{6\pi R}{V_m} - 1 \right) = 48.235^\circ = 0.843 \text{ rad}$$

Part (b):

$$P = \frac{V_{rms}^2}{R} = \frac{V_m^2}{4R} \left(\frac{1}{2} - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi} \right) = 854$$

Part (c):

$$pf = \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}} = \sqrt{\frac{1}{2} - \frac{0.843}{2\pi} + \frac{\sin(2 * 0.843)}{4\pi}} = 0.67$$