

**Problem1:**

A single-phase full-wave rectifier has a resistive load of  $10 \Omega$  and an ac source of  $150 \sin(2\pi 60t)$ .

Determine

- (a) the average, peak, and rms currents in the load and in each diode.
- (b) the peak reverse voltage across each of the diodes

**Solution:**

**Part (a)**

The average current in the load and in each diode:

$$\langle i_o \rangle = \frac{\langle V_o \rangle}{R} = \frac{2V_m}{\pi R} = \frac{2 * 150}{\pi * 10} = 9.55 \text{ A}$$

$$\langle i_D \rangle = \frac{\langle i_o \rangle}{2} = 4.775 \text{ A}$$

The peak current of load and each diode:

$$\langle i_{o,m} \rangle = \langle i_{D,m} \rangle = \frac{V_m}{R} = \frac{150}{10} = 15 \text{ A}$$

The rms current of load and each diode:

$$I_{o,rms} = \frac{V_{o,rms}}{R} = \frac{\left(\frac{150}{\sqrt{2}}\right)}{10} = 10.608 \text{ A}$$

$$I_{D,rms} = \frac{I_{o,rms}}{\sqrt{2}} = 7.5 \text{ A}$$

**Part (b)**

The maximum voltage across a reverse-biased diode is the peak value of the source voltage

$$V_m = 150 \text{ V}$$

### Problem2:

The full-wave rectifier has a 130-V rms 60 Hz source,  $R=150\ \Omega$  and  $C=300\ \mu F$ . Determine

- (a) the peak-to-peak voltage variation of the output
- (b) the filter capacitance required to limit the peak-to-peak output voltage ripple to 3 volt.

### Solution:

#### Part (a)

$$\theta = \pi - \tan^{-1}(RC\omega) = \pi - \tan^{-1}(150 * 300 * 10^{-6} * 377) = 1.6297\ rad$$

$$\sin\alpha - \sin\theta \cdot e^{-(\pi+\alpha-\theta)/\omega RC} = 0$$

$$\alpha = 59.23^\circ = 1.0337\ rad$$

$$\Delta V_0 = V_m(1 - \sin\alpha) = 130\sqrt{2}(1 - 0.8592) = 25.882\ V$$

#### Part (b)

$$\Delta V_0 \approx \frac{V_m}{2fRC} \rightarrow C \approx \frac{V_m}{2fR \cdot \Delta V_0} = \frac{130\sqrt{2}}{2(60)(150)(3)} = 3404\ \mu F$$

### Problem3:

A boost converter has an input of 5 V and an output of 25 W at 15 V. The switching frequency is 100 kHz. Determine

- (a) the duty ratio,
- (b) the minimum inductor value which allows the converter to work in continuous conduction mode (CCM)
- (c) the average and the peak value of inductor current
- (d) the average and peak value of diode current

Assume ideal components

**Hint: Continuous conduction mode means the inductor current is positive through the whole period.**

**Solution:**

$$P_{out} = 25 = \frac{V_o^2}{R} = \frac{(15)^2}{R} \rightarrow R = 9\Omega$$

**Part (a):**

$$\frac{V_o}{V_{in}} = \frac{15}{5} = \frac{1}{1-D} \rightarrow D = 0.666$$

**Part (b):**

Working in continuous conduction mode means the inductor current is positive through the whole period, so, to calculate the minimum value for inductor, we should consider  $I_{min} = 0$  :

$$I_{min} = \frac{V_{in}}{(1-D)^2 R} - \frac{V_{in} \cdot D}{2L_{min} f} = 0 \rightarrow L_{min} = \frac{D \cdot (1-D)^2 \cdot R}{2f} = 3.34 \mu\text{H}$$

**Part (c):**

$$\langle i_L \rangle = \frac{V_{in}}{(1-D)^2 R} = \frac{5}{(1-0.666)^2 * 9} = 4.98 \text{ A}$$

$$I_{max} = \frac{V_{in}}{(1-D)^2 R} + \frac{V_{in}}{2L} DT = 9.96 \text{ A}$$


**Part (d):**

$$I_{D-max} = I_{max} = 9.96 \text{ A}$$

$$\langle i_D \rangle = \langle i_L \rangle * (1-D) = 4.98 * (1-0.666) = 1.663 \text{ A}$$

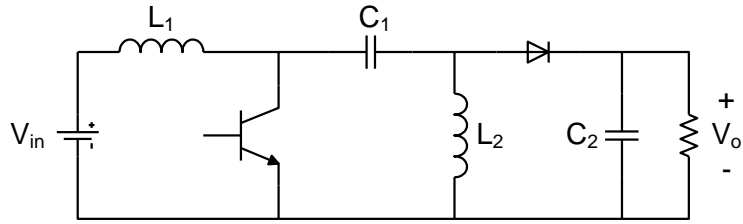
**Problem4:**

For the dc-dc converter (operating in CCM) depicted in the figure below, make all the required assumptions and find the input-output voltage ratio ( $V_o/V_{in}=?$ ).



**Solution:**

Mode 1: S:on ,  $0 < t < DT$

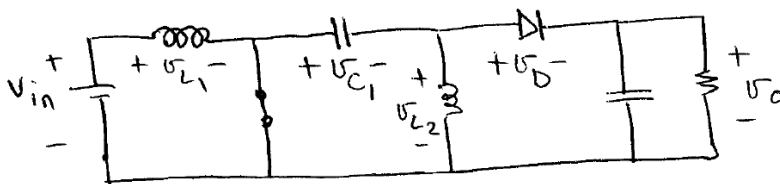


$$V_D = -V_{c1} - V_o \quad \text{if } V_{c1} > 0 \text{ \& } V_o > 0$$

Diode is off

$$V_{L1} = V_{in} \quad , \quad V_{L2} = -V_{c1}$$

Mode 2: S:off ,  $DT < t < T$

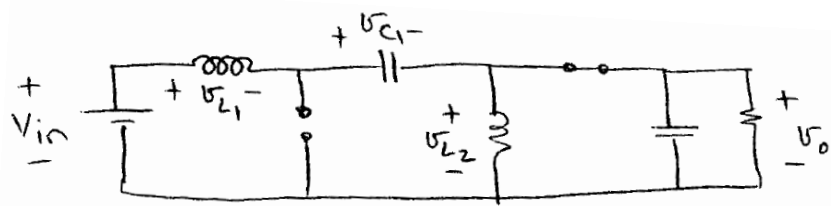$L_1$  and  $L_2$  force diode to conduct



$$V_{L1} = V_{in} - V_o - V_{c1} \quad , \quad V_{L2} = V_o$$

Steady state:  $\langle V_{L1} \rangle = \langle V_{L2} \rangle = 0$

$$\langle V_{L1} \rangle = 0 \quad \rightarrow \quad DV_{in} + (1 - D)(V_{in} - V_o - V_{c1}) = 0$$

$$\langle V_{L2} \rangle = 0 \quad \rightarrow \quad D(-V_{c1}) + (1 - D)(V_o) = 0 \quad \rightarrow \quad V_{c1} = \frac{1 - D}{D} V_o$$

$$\frac{V_o}{V_{in}} = \frac{D}{1-D}$$

$V_{c1} > 0$  &  $V_o > 0 \rightarrow$  "Diode is off" was a correct assumption