

ELEC-E8412 Power Electronics

/ Exercise # 3 _ Solutions

22.10.2020

Problem 1:

A half-wave rectifier with a 1-k Ω load has a parallel capacitor. The source is 120 V rms, 60 Hz. Determine the peak-to-peak ripple of the output voltage when the capacitor is

- 4000 μF and
- 20 μF .

Solution:

Part (a):

the approximation $\Delta V_0 \approx \frac{V_m}{fRC}$ is valid when $\omega RC \gg 1$

$$C=4000 \mu\text{F} \quad \omega RC = 377 * 1000 * 4 * 10^{-3} = 1508 \gg 1$$

$$\Delta V_0 \approx \frac{V_m}{fRC} = \frac{120\sqrt{2}}{60 * 1000 * 4 * 10^{-3}} = 0.707 \text{ V}$$

Part (b):

$$C=20 \mu\text{F} \quad \omega RC = 377 * 1000 * 20 * 10^{-6} = 7.54 > 1 \text{ (approximation is not valid here)}$$

$$\theta = \pi - \tan^{-1}(RC\omega) = \pi - \tan^{-1}(7.54) = 1.7027 \text{ rad}$$

$$\sin\alpha - \sin\theta \cdot e^{-(2\pi+\alpha-\theta)/\omega RC} = 0$$

$$\alpha = 30.2^\circ = 0.5275 \text{ rad}$$

$$\Delta V_0 = V_m(1 - \sin\alpha) = 120\sqrt{2}(1 - 0.5034) = 83.26 \text{ V (correct answer)}$$

$$\Delta V_0 \approx \frac{V_m}{fRC} = \frac{120\sqrt{2}}{60 * 1000 * 20 * 10^{-6}} = 141.42 \text{ V}$$

Matlab code for calculating α (you do not need it in your exam, because α will be given to you in your exam)

```
>> syms a
>> sola=solve(sin(a)-0.991*exp(-(2*pi+a-1.7027)/7.54)==0,a)
```

sola =

0.52746105862587760015291337830798

Problem 2:

A half-wave rectifier with a capacitor filter has $V_m=200$ V, $R=10$ k Ω , $C=1000$ μ F, and $\omega=377$.

- Determine the peak-to-peak ripple voltage using the exact equations.
- Determine the ripple (using the approximate formula).

Solution:

Part (a):

$$\theta = \pi - \tan^{-1}(RC\omega) = \pi - \tan^{-1}(10000 * 1000 * 10^{-6} * 377) = 1.5711rad$$

$$\sin\alpha - \sin\theta \cdot e^{-(2\pi+\alpha-\theta)/\omega RC} = 0$$

$$\alpha = 86.7^\circ = 1.513rad$$

$$\Delta V_0 = V_m(1 - \sin\alpha) = 200(1 - \sin\alpha) = 200(1 - 0.9983) = 0.34 V$$

Part (b):

$$\Delta V_0 \approx \frac{V_m}{fRC} = \frac{200}{60 * 10000 * 1000 * 10^{-6}} = 0.333 V$$

Problem 3:

For the controlled half-wave rectifier with resistive load, the source is 120 V rms at 60 Hz. The resistance is 100 Ω , and the delay angle α is 45° .

- Determine the average voltage across the resistor.

- b) Determine the power absorbed by the resistor.
- c) Determine the power factor as seen by the source.

Solution:

Part (a): Average voltage across the resistor

$$V_o = \frac{V_m}{2\pi} (1 + \cos\alpha) = \frac{120\sqrt{2}}{2\pi} (1 + \cos 45) = 46.11 \text{ V}$$

Part (b): the power absorbed by the resistor

$$P = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} = \frac{120\sqrt{2}}{2} \sqrt{1 - \frac{0.785}{\pi} + \frac{\sin 2\alpha}{2\pi}} = \frac{120\sqrt{2}}{2} * 0.953 = 80.91 \text{ V}$$

$$\alpha = 45^\circ = \frac{\pi}{4} \text{ rad} = 0.785 \text{ rad}$$

$$P = \frac{V_{rms}^2}{R} = \frac{(80.91)^2}{100} = 65.46 \text{ W}$$

Part (c): Power factor

$$pf = \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}} = 0.67$$

Problem 4:

A half-wave rectifier has a 120 V rms, 60 Hz ac source. The load is 750 Ω .

- a) Determine the value of a filter capacitor to keep the peak-to-peak ripple across the load to less than 2 V.
- b) Determine the average and peak values of diode current.

Solution:

Part (a): the value of C

$$\Delta V_0 \approx \frac{V_m}{fRC} \quad C > \frac{120\sqrt{2}}{60 * 750 * 2} = 1885 \mu F$$

Part (b): average and peak values of diode current

$$\Delta V_0 = V_m(1 - \sin\alpha)$$

$$\alpha = \sin^{-1}\left(1 - \frac{\Delta V_0}{V_m}\right) = \sin^{-1}\left(1 - \frac{2}{120\sqrt{2}}\right) = 1.417 \text{ rad} = 81.20^\circ$$

$$i_{d-peak} = V_m \left(\omega C \cos\alpha + \frac{\sin\alpha}{R} \right) = 120\sqrt{2} \left(1885 * 10^{-6} * 2\pi * 60 * \cos(81.2^\circ) + \frac{\sin(81.2^\circ)}{750} \right)$$

$$i_{d-peak} = 18.7 \text{ A}$$

$$\langle i_d \rangle = \frac{\langle V_o \rangle}{R}$$

$$\langle V_o \rangle \approx V_{o,peak} - \frac{\Delta V_0}{2} = V_m - \frac{V_m}{2fRC} \approx V_m$$

$$\langle i_d \rangle = \frac{V_m}{R} = \frac{120\sqrt{2}}{750} = 0.2262 \text{ A}$$