

## ELEC-E8412 Power Electronics

/ Exercise # 4\_ Solutions

5.11.2020

### Problem 1:

A single-phase full-wave rectifier has a resistive load of  $12 \Omega$  and an ac source of 120-V rms and 60 Hz. Determine

- the average, peak, and rms currents in the load and in each diode.
- Determine the peak reverse voltage across each of the diodes

### Solution:


$$V_{rms} = 120 V, V_m = 120\sqrt{2} = 169.7 V$$

### Part (a)

The average current in the load and in each diode:

$$\langle i_o \rangle = \frac{\langle V_o \rangle}{R} = \frac{2V_m}{\pi R} = \frac{2 * 120\sqrt{2}}{\pi * 12} = 9 A$$
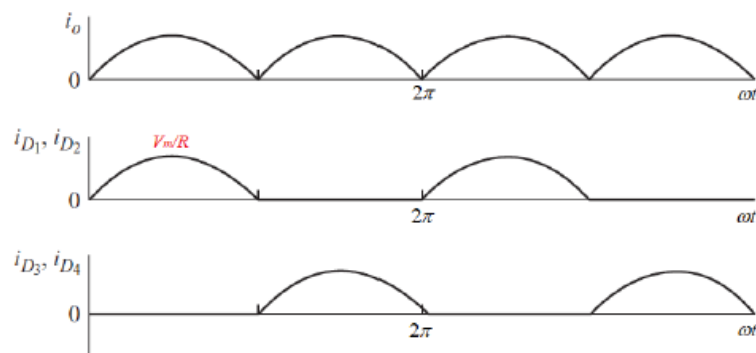
$$\langle i_D \rangle = \frac{\langle i_o \rangle}{2} = 4.5 A$$



The peak current of load and each diode:

$$\langle i_{o,m} \rangle = \langle i_{D,m} \rangle = \frac{V_m}{R} = \frac{169.7}{12} = 14.14 A$$

The rms current of load and each diode:

$$I_{o,rms} = \frac{V_{o,rms}}{R} = \frac{120}{12} = 10 \text{ A}$$

$$I_{D,rms} = \frac{I_{o,rms}}{\sqrt{2}} = 7.07 \text{ A}$$


$$I_{o,rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \frac{V_m^2}{R^2} (\sin wt)^2 d(wt)} = \frac{V_m}{\sqrt{2}R}$$

$$I_{D,rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} \frac{V_m^2}{R^2} (\sin wt)^2 d(wt)} = \frac{V_m}{2R}$$

### Part (b)

The maximum voltage across a reverse-biased diode is the peak value of the source voltage

$$V_m = 120\sqrt{2} = 169.7 \text{ V}$$

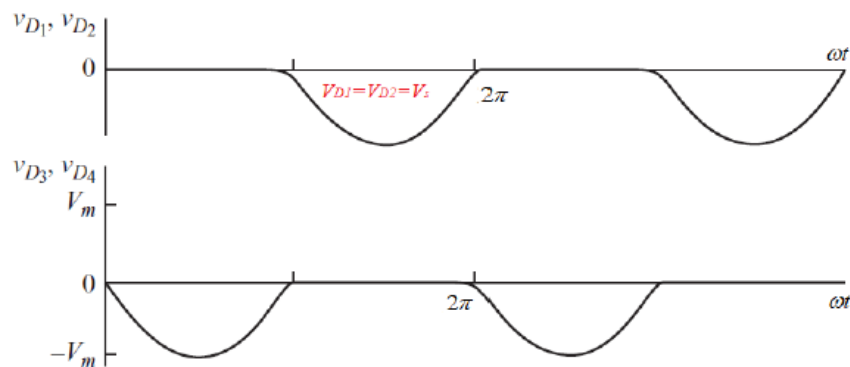

### Problem 2:

A single-phase full-wave rectifier with an ac source of  $200 \sin(377t)$  V has a resistive load of  $20 \Omega$ .

Determine

- the average current in the load and in each diode,
- the peak reverse voltage across each of the diodes,
- the power factor

### Solution:

### Part (a)

$$\langle i_o \rangle = \frac{\langle V_o \rangle}{R} = \frac{2V_m}{\pi R} = \frac{2 * 200}{\pi * 20} = 6.366 \text{ A}$$

$$\langle i_D \rangle = \frac{\langle i_o \rangle}{2} = 3.183 \text{ A}$$

### Part (b)

peak reverse voltage across each of the diodes  $= V_m = 200 \text{ V}$

### Part (c)

$$PF = \frac{\text{average output power}}{\text{apparent input power}} = \frac{R * I_{o,rms}^2}{V_{in,rms} * I_{in,rms}} = \frac{20 * \left(\frac{200}{20 * \sqrt{2}}\right)^2}{\frac{200}{\sqrt{2}} * \frac{200}{20 * \sqrt{2}}} = 1$$

$$I_{o,rms} = \frac{V_{o,rms}}{R} = \frac{V_m}{\sqrt{2}R} = I_{in,rms}$$

### Problem 3:

The controlled single-phase bridge rectifier has an  $18 \Omega$  resistive load and has a 120-V rms, 60-Hz ac source. The delay angle is  $45^\circ$ . Determine

- the average load current,
- the rms load current,
- the rms source current,
- the power factor.

### Solution:

$$V_{rms} = 120 \text{ V}, V_m = 120\sqrt{2} = 169.7 \text{ V}$$

### Part (a)

$$\langle i_o \rangle = \frac{\langle V_o \rangle}{R} = \frac{V_m(1 + \cos\alpha)}{\pi R} = \frac{120\sqrt{2}(1 + 0.707)}{\pi * 18} = 5.12 \text{ A}$$

**Part (b)**

$$I_{rms} = \frac{V_m}{R} \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}} = \frac{169.7}{18} \sqrt{\frac{1}{2} - \frac{0.785}{2\pi} + \frac{1}{4\pi}} = 6.35 \text{ A}$$

$$\alpha = 45^\circ = 0.785 \text{ rad}$$

**Part (c)**

The rms current in the source is the same as the rms current in the load. So,

$$I_{in,rms} = I_{o,rms} = 6.35 \text{ A}$$

**Part (d)**

$$pf = \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}} = \sqrt{1 - \frac{0.785}{\pi} + \frac{1}{2\pi}} = 0.953$$

$$pf = \frac{R * I_{o,rms}^2}{V_{in,rms} * I_{in,rms}} = \frac{18 * (6.35)^2}{120 * 6.35} = 0.953$$

**Problem 4:**

The full-wave rectifier has a 120-V rms 60 Hz source,  $R=200 \Omega$  and  $C=200 \mu F$ . Determine

- the peak-to-peak voltage variation of the output
- the filter capacitance required to limit the peak-to-peak output voltage ripple to 1 percent of the dc output.

**Solution:**

$$V_{rms} = 120 \text{ V}, V_m = 120\sqrt{2} = 169.7$$

**Part (a)**

$$\theta = \pi - \tan^{-1}(RC\omega) = \pi - \tan^{-1}(200 * 200 * 10^{-6} * 377) = 1.637 \text{ rad}$$

$$\sin\alpha - \sin\theta \cdot e^{-(\pi+\alpha-\theta)/\omega RC} = 0$$

$$\alpha = 57.7^\circ = 1.007 \text{ rad}$$

$$\Delta V_0 = V_m(1 - \sin\alpha) = 169.7(1 - 0.8452) = 26.27 \text{ V}$$

### Part (b)

$$\Delta V_0 \approx \frac{V_m}{2fRC} \rightarrow \frac{\Delta V_0}{V_m} \approx \frac{1}{2fRC} \approx 0.01 \rightarrow C \approx \frac{1}{2fR\left(\frac{\Delta V_0}{V_m}\right)} = \frac{1}{2(60)(200)(0.01)} = 4166 \mu F$$

### Problem 5:

The full-wave rectifier has a 60-Hz ac source with maximum voltage of 100 V. It is to supply a load that requires a dc voltage of 100 V and will draw 0.4 A. Determine the filter capacitance required to limit the peak-to-peak output voltage ripple to 1 percent of the dc output.

### Solution:

$$V_m = 100, \quad \text{output dc voltage} = 100 \text{ V}$$

$$R = \frac{100}{0.4} = 250 \Omega$$

$$\Delta V_0 \approx \frac{V_m}{2fRC} \rightarrow \frac{\Delta V_0}{V_m} \approx \frac{1}{2fRC} \approx 0.01 \rightarrow C \approx \frac{1}{2fR\left(\frac{\Delta V_0}{V_m}\right)} = \frac{1}{2(60)(250)(0.01)} = 3333 \mu F$$