

**Problem 1:**

A buck converter has an input of 6 V and an output of 1.5 V. The load resistor is 3 Ω, the switching frequency is 400 kHz, L = 5 μH, and C = 10 μF. Determine

- the duty ratio
- the average and peak inductor currents
- the average source current,
- the peak and average diode current.

**Solution:****Part (a):**

$$D = \frac{V_o}{V_{in}} = \frac{1.5}{6} = 0.25$$

**Part (b):**

$$\langle i_L \rangle = \frac{I_{max} + I_{min}}{2} = \frac{V_o}{R} = \frac{1.5}{3} = 0.5 \text{ A}$$

$$I_{max} = V_o \left( \frac{1}{R} + \frac{1-D}{2Lf} \right) = 1.5 \left( \frac{1}{3} + \frac{1-0.25}{2 * 5 * 10^{-6} * 4 * 10^5} \right) = 0.78 \text{ A}$$

**Part (c):**

$$\langle i_{in} \rangle = ?$$

$$V_{in} \cdot \langle i_{in} \rangle = \frac{V_o^2}{R} = \frac{(D * V_{in})^2}{R} \quad \rightarrow \quad \langle i_{in} \rangle = \frac{D^2 V_{in}}{R} = \frac{(0.25)^2 * 6}{3} = 0.125 \text{ A}$$

**Part (d):**

Fig 5-5 b

$$I_{D\_max} = I_{max} = 0.78 \text{ A}$$

$$\langle i_D \rangle = \langle i_L \rangle * (1 - D) = \frac{V_o}{R} * (1 - D) = \frac{1.5}{3} * (1 - 0.25) = 0.375 \text{ A}$$

### Problem 2:

A buck converter has an input of 50 V and an output of 25 V. The switching frequency is 100 kHz, and the output power to a load resistor is 125 W. Determine

- (a) the duty ratio
- (b) the value of inductance to limit the peak inductor current to 6.25 A.
- (c) the minimum inductor current

### Solution:

$$R = \frac{V_o^2}{P_{out}} = \frac{(25)^2}{125} = 5 \Omega$$

### Part (a):

$$D = \frac{V_o}{V_{in}} = \frac{25}{50} = 0.5$$

### Part (b):

$$I_{max} = V_o \left( \frac{1}{R} + \frac{1-D}{2Lf} \right) = 25 \left( \frac{1}{5} + \frac{1-0.5}{2 * L * 10^5} \right)$$

$$I_{max} = 6.25 A \quad \rightarrow \quad L = 50 \mu H$$

### Part (c):

$$I_{min} = V_o \left( \frac{1}{R} - \frac{1-D}{2Lf} \right) = 25 \left( \frac{1}{5} - \frac{1-0.5}{2 * 50 * 10^{-6} * 10^5} \right) = 3.75 A$$

### Problem 3:

A boost converter has the following parameters:

$$V_{in} = 5 V, V_{out} = 20 V, \text{ and } P_{out} = 40 W$$

The minimum value of the inductor current must be at least 80% of the average inductor current. The switching frequency is 85 kHz. Determine the duty ratio and the minimum inductor value.

**Solution:**

$$I_{min} > 0.8 \langle i_L \rangle \rightarrow \langle i_L \rangle - \frac{\Delta i_L}{2} > 0.8 \langle i_L \rangle \rightarrow 0.2 \langle i_L \rangle > \frac{\Delta i_L}{2}$$

$$0.2 \frac{V_{in}}{(1-D)^2 R} > \frac{V_{in} D T}{2L}$$

$$L > \frac{D(1-D)^2 R}{0.4f}$$

D=? R=?

$$\frac{V_o}{V_{in}} = \frac{20}{5} = \frac{1}{1-D} \rightarrow D = 0.75$$

$$P_{out} = 40 = \frac{V_o^2}{R} = \frac{(20)^2}{R} \rightarrow R = 10\Omega$$

$$L > 13.79 \mu\text{H}$$

**Problem 4:**

A boost converter has parameter  $V_s = 20 \text{ V}$ ,  $D = 0.6$ ,  $R = 12.5 \Omega$ ,  $L = 10 \mu\text{H}$ ,  $C = 40 \mu\text{F}$ , and the switching frequency is 200 kHz. Determine

- (a) the output voltage
- (b) the average, maximum, and minimum inductor currents.
- (c) the average current in the diode

Assume ideal components.

**Solution:**

**Part (a):**

$$V_o = V_{in} * \frac{1}{1-D} = 20 * \frac{1}{1-0.6} = 50 \text{ V}$$

**Part (b):**

$$\langle i_L \rangle = \frac{I_{max} + I_{min}}{2} = \frac{V_{in}}{(1-D)^2 R} = \frac{20}{(1-0.6)^2 * 12.5} = 10 \text{ A}$$

$$I_{max} = \frac{V_{in}}{(1-D)^2 R} + \frac{V_{in}}{2L} DT = \frac{20}{(1-0.6)^2 * 12.5} + \frac{20 * 0.6}{2 * 10 * 10^{-6} * 2 * 10^5} = 13 A$$

$$I_{min} = \frac{V_{in}}{(1-D)^2 R} - \frac{V_{in}}{2L} DT = \frac{20}{(1-0.6)^2 * 12.5} - \frac{20 * 0.6}{2 * 10 * 10^{-6} * 2 * 10^5} = 7 A$$

**Part (c):**

$$\langle i_D \rangle = \langle i_L \rangle * (1 - D) = 10 * (1 - 0.6) = 4 A \quad \text{or} \quad \langle i_D \rangle = \frac{V_o}{R} = \frac{50}{12.5} = 4 A$$

**Problem 5:**

A buck-boost converter has the following parameters:

$V_{in} = 24 V$ ,  $D = 0.65$ ,  $R = 7.5 \Omega$ ,  $L = 50 \mu H$ ,  $C = 200 \mu F$ , and switching frequency = 100 KHz. Determine

- (a) the output voltage,
- (b) the average, maximum, and minimum inductor currents.

**Solution:**

**Part (a):**

$$\frac{V_o}{V_{in}} = \frac{D}{1-D}, D = 0.65, V_{in} = 24 V \quad \rightarrow \quad V_o = 44.571 V$$

**Part (b):**

$$\langle i_L \rangle = \frac{V_{in} D}{(1-D)^2 R} = \frac{24 * 0.65}{(1-0.65)^2 * 7.5} = 16.98 A$$

$$\Delta i_L = \frac{V_{in} DT}{L} = \frac{24 * 0.65}{50 * 10^{-6} * 10^5} = 3.12 A$$

$$I_{max} = \langle i_L \rangle + \frac{\Delta i_L}{2} = 16.98 + \frac{3.12}{2} = 18.54 A$$

$$I_{min} = \langle i_L \rangle - \frac{\Delta i_L}{2} = 16.98 - \frac{3.12}{2} = 15.42 A$$

### Problem 6:

A buck-boost converter has parameters  $V_s=12\text{ V}$ ,  $D=0.6$ ,  $R=10\ \Omega$ ,  $L=10\ \mu\text{H}$ ,  $C=20\ \mu\text{F}$ , and a switching frequency of  $200\text{ kHz}$ . Determine

- (a) the output voltage
- (b) the average, maximum, and minimum inductor currents, and
- (c) the average value of input current.

### Solution:

#### Part (a):

$$V_o = V_{in} * \frac{D}{1-D} = 12 * \frac{0.6}{1-0.6} = 18\text{ V}$$

#### Part (b):

$$\langle i_L \rangle = \frac{V_{in}D}{(1-D)^2R} = \frac{12 * 0.6}{(1-0.6)^2 * 10} = 4.5\text{ A}$$

$$\Delta i_L = \frac{V_{in}DT}{L} = \frac{12 * 0.6}{10 * 10^{-6} * 2 * 10^5} = 3.6\text{ A}$$

$$I_{max} = \langle i_L \rangle + \frac{\Delta i_L}{2} = 4.5 + \frac{3.6}{2} = 6.3\text{ A}$$

$$I_{min} = \langle i_L \rangle - \frac{\Delta i_L}{2} = 4.5 - \frac{3.6}{2} = 2.7\text{ A}$$

#### Part (c):

$$\langle i_{in} \rangle = ?$$

$$V_{in} \cdot \langle i_{in} \rangle = \frac{V_o^2}{R} = \frac{(D * V_{in})^2}{(1-D)^2R} \rightarrow \langle i_{in} \rangle = \frac{D^2 * V_{in}}{(1-D)^2R} = \frac{(0.6)^2 * 12}{(1-0.6)^2 * 10} = 2.7\text{ A}$$