

**Problem 1:**

A square-wave inverter has a dc source of 125 V, an output frequency of 50 Hz, and an RL series load with  $R=12\ \Omega$  and  $L=35\ \text{mH}$ . Determine

- a) an expression for load current,
- b) rms load current, and
- c) average source current.

**Problem 2:**

A square-wave inverter has a dc input of 150 V and supplies a series  $RL$  load with  $R=20\ \Omega$  and  $L=40\ \text{mH}$ . The output frequency is 60 Hz.

- a) Determine an expression for steady state load current.
- b) Sketch the load current and indicate the time intervals when each switch component (Q1, D1; . . . Q4, D4) is conducting.
- c) Determine the peak current in each switch component.
- d) What is the maximum voltage across each switch?

Assume ideal components.

**Problem 3:**

A square-wave inverter has  $V_{dc}=125\ \text{V}$ , an output frequency of 60 Hz, and a resistive load of  $12.5\ \Omega$ . Sketch the currents in the load, each switch, and the source, and determine the average and rms values of each.