

Problem 1:

A square-wave inverter has a dc source of 125 V, an output frequency of 50 Hz, and an RL series load with $R=12\ \Omega$ and $L=35\ \text{mH}$. Determine

- an expression for load current,
- rms load current, and
- average source current.

Solution:

$$T = \frac{1}{f} = \frac{1}{50} = 0.02\ \text{s}$$

$$\tau = \frac{L}{R} = \frac{0.035}{12} = 0.00292$$

$$\frac{T}{2\tau} = \frac{0.02}{2 * 0.00292} = 3.425$$

Part (a)

$$I_{max} = -I_{min} = \frac{V_{in}}{R} \left(\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right) = \frac{125}{12} \left(\frac{1 - e^{-3.425}}{1 + e^{-3.425}} \right) = 9.76\ \text{A}$$

$$\begin{aligned} i_o(t) &= \frac{V_{in}}{R} + \left(I_{min} - \frac{V_{in}}{R} \right) e^{-t/\tau} = \frac{125}{12} + \left(-9.76 - \frac{125}{12} \right) e^{-t/0.00292} \\ &= 10.417 - 20.177e^{-t/0.00292} \quad 0 \leq t \leq \frac{1}{100} \end{aligned}$$

$$i_o(t) = \frac{-V_{in}}{R} + \left(I_{max} + \frac{V_{in}}{R} \right) e^{-(t-T/2)/\tau} = \frac{-125}{12} + \left(9.76 + \frac{125}{12} \right) e^{-(t-0.01)/0.00292}$$

$$= -10.417 + 20.177 e^{-(t-0.01)/0.00292} \quad \frac{1}{100} \leq t \leq \frac{1}{50}$$

Part (b)

$$I_{rms} = \sqrt{\frac{2}{T} \int_0^{T/2} \left(\frac{V_{in}}{R} + \left(I_{min} - \frac{V_{in}}{R} \right) e^{-t/\tau} \right)^2 dt} = \sqrt{100 \int_0^{0.01} (10.417 - 20.177 e^{-t/0.00292})^2 dt}$$

$$= 7.0143 \text{ A}$$

Part (c)

$$I_{in} = \frac{p_{in}}{V_{in}}$$

$$p_{in} = p_{out} = R I_{rms}^2 = 12 * (7.0143)^2 = 590.4 \text{ W}$$

$$I_{in} = \frac{p_{in}}{V_{in}} = \frac{590.4}{125} = 4.72 \text{ A}$$

Problem 2:

A square-wave inverter has a dc input of 150 V and supplies a series RL load with $R=20\Omega$ and $L=40 \text{ mH}$. The output frequency is 60 Hz.

- Determine an expression for steady state load current.
- Sketch the load current and indicate the time intervals when each switch component (Q1, D1; . . . Q4, D4) is conducting.
- Determine the peak current in each switch component.
- What is the maximum voltage across each switch?

Assume ideal components.

Solution:

$$T = \frac{1}{f} = \frac{1}{60} = 0.0167 \text{ s}$$

$$\tau = \frac{L}{R} = \frac{0.040}{20} = 0.002$$

$$\frac{T}{2\tau} = \frac{0.0167}{2 * 0.002} = 4.175$$

Part (a):

$$I_{max} = -I_{min} = \frac{V_{in}}{R} \left(\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right) = \frac{150}{20} \left(\frac{1 - e^{-4.175}}{1 + e^{-4.175}} \right) = 7.27 \text{ A}$$


$$i_o(t) = \frac{V_{in}}{R} + \left(I_{min} - \frac{V_{in}}{R} \right) e^{-t/\tau} = 7.5 + (-7.27 - 7.5) e^{-t/0.002}$$

$$= 7.5 - 14.77 e^{-t/0.002} \quad 0 \leq t \leq \frac{1}{120}$$

$$i_o(t) = \frac{-V_{in}}{R} + \left(I_{max} + \frac{V_{in}}{R} \right) e^{-(t-\frac{T}{2})/\tau} = -7.5 + (7.27 + 7.5) e^{-(t-0.0084)/0.002}$$

$$= -7.5 + 14.77 e^{-(t-0.0084)/0.002} \quad \frac{1}{120} \leq t \leq \frac{1}{60}$$

Part (b):

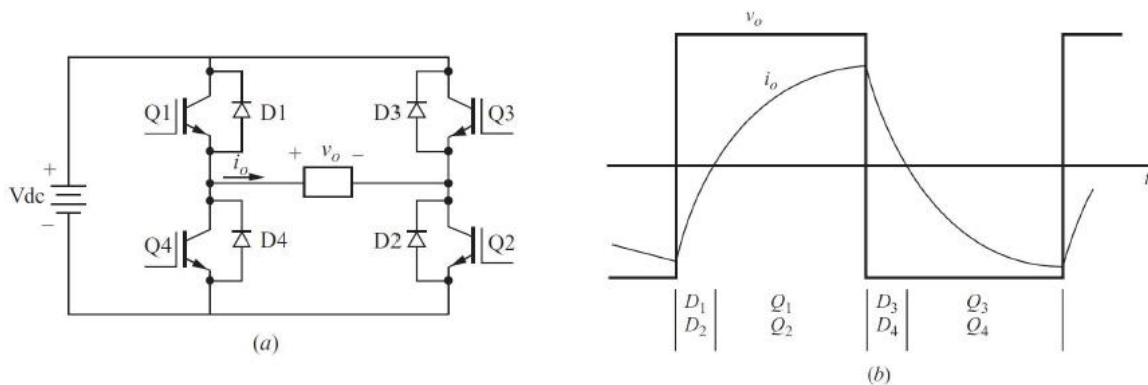

Part (c): the peak current in each switch component is equal to the peak output current,

$$I_{max} = \frac{V_{in}}{R} \left(\frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} \right) = \frac{150}{20} \left(\frac{1 - e^{-4.175}}{1 + e^{-4.175}} \right) = 7.27 \text{ A}$$


Part (d):

The maximum voltage across each switch is $V_{in} = 150 \text{ V}$

Problem 3:

A square-wave inverter has $V_{dc}=125 \text{ V}$, an output frequency of 60 Hz , and a resistive load of 12.5Ω . Sketch the currents in the load, each switch, and the source, and determine the average and rms values of each.

Solution:

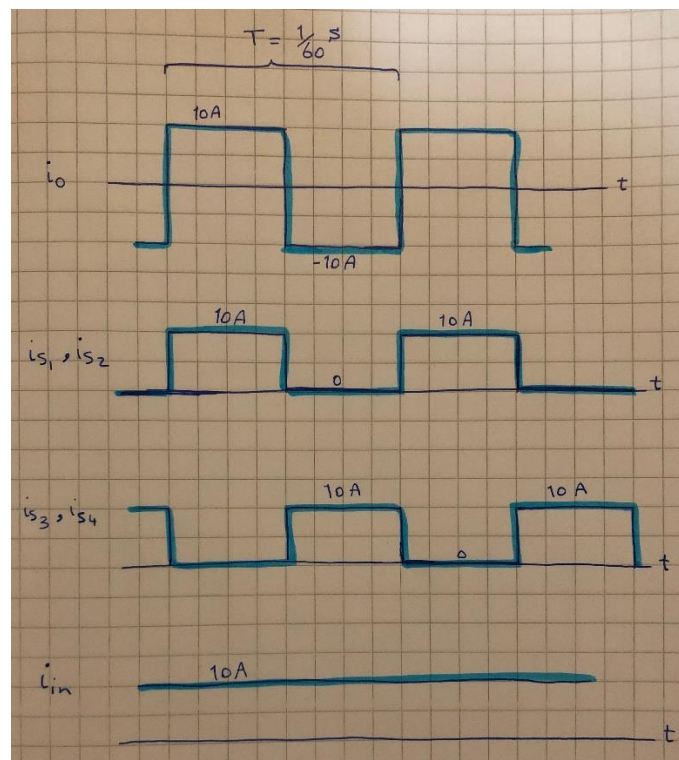

$$\langle i_o \rangle = 0$$

$$\langle i_{s1} \rangle = \langle i_{s2} \rangle = \langle i_{s3} \rangle = \langle i_{s4} \rangle = 5 \text{ A}$$

$$\langle i_{in} \rangle = 10 \text{ A}$$

$$I_{o,rms} = 10 \text{ A}$$

$$I_{s,rms} = \sqrt{50} = 7.07 \text{ A}$$

$$I_{in,rms} = 10 \text{ A}$$