



**Aalto-yliopisto**  
Teknillinen korkeakoulu


# EXERCISE 3

**ELEC-E8409 HIGH VOLTAGE  
ENGINEERING**

arslan.bashir@aalto.fi  
Tuas 3532
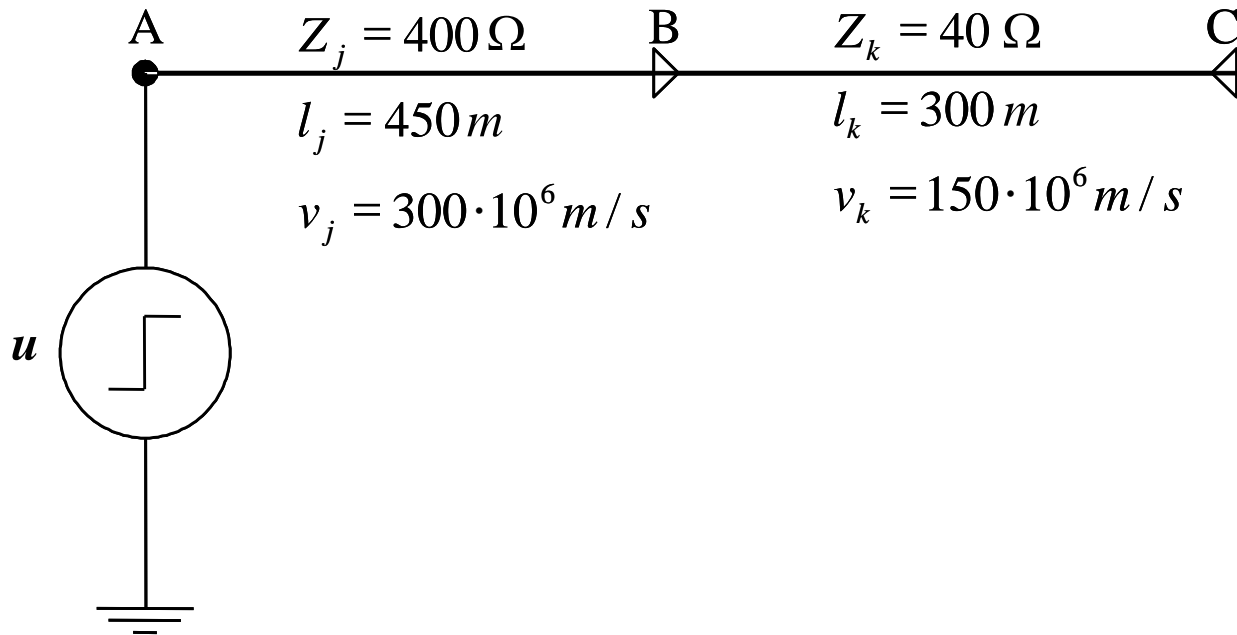
# Question 1

- A step wave of amplitude  $u$  is applied to the open line illustrated in the figure. Study voltage as a function of time at points A, B and C.




**Transmission coefficient:**

$$\tau = \frac{2Z_2}{Z_1 + Z_2} \quad (\tau = \rho + 1)$$

**Reflection coefficient:**

$$\rho = \frac{Z_2 - Z_1}{Z_1 + Z_2}$$

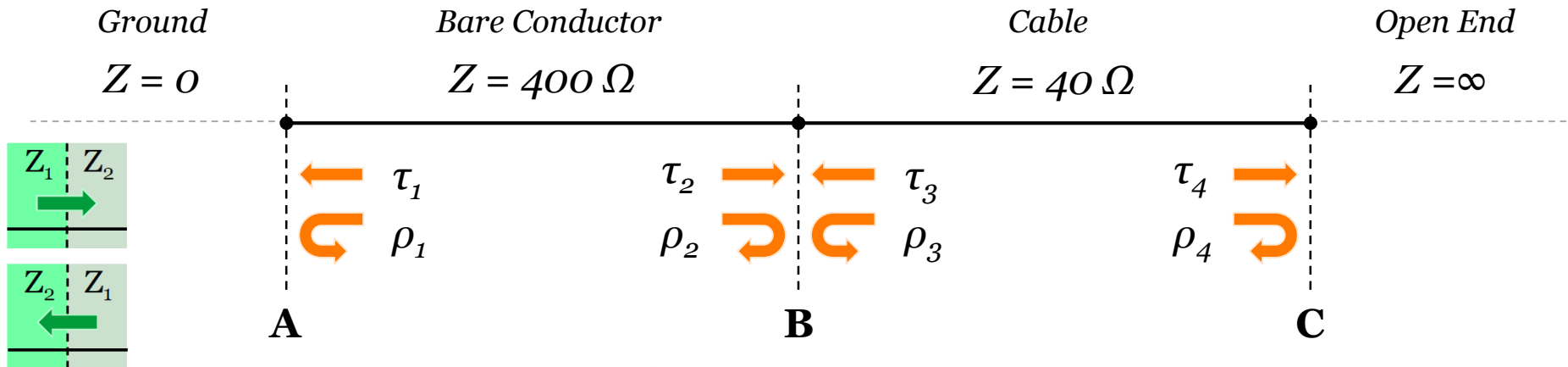

**$(\tau_1, \rho_1): Z_1 = 400 \Omega, Z_2 = 0$**

$$\tau_1 = \frac{2Z_2}{Z_1 + Z_2} = \frac{2(0)}{400 + 0} = 0$$

$$\rho_1 = \frac{Z_2 - Z_1}{Z_1 + Z_2} = \frac{0 - 400}{400 + 0} = -1$$

**$(\tau_2, \rho_2): Z_1 = 400 \Omega, Z_2 = 40 \Omega$**

$$\tau_2 = \frac{2Z_2}{Z_1 + Z_2} = \frac{2(40)}{400 + 40} = \frac{80}{440} = 0.18$$

$$\rho_2 = \frac{Z_2 - Z_1}{Z_1 + Z_2} = \frac{40 - 400}{400 + 40} = \frac{-360}{440} = -0.82$$

**$(\tau_3, \rho_3): Z_1 = 40 \Omega, Z_2 = 400 \Omega$**

$$\tau_3 = \frac{2Z_2}{Z_1 + Z_2} = \frac{2(400)}{40 + 400} = \frac{800}{440} = 1.82$$

$$\rho_3 = \frac{Z_2 - Z_1}{Z_1 + Z_2} = \frac{400 - 40}{40 + 400} = \frac{360}{440} = 0.82$$

**$(\tau_4, \rho_4): Z_1 = 40 \Omega, Z_2 = \infty$**


$$\tau_4 = \frac{2Z_2}{Z_1 + Z_2} = \frac{2(\infty)}{40 + \infty} = \frac{2\infty}{\infty} = 2$$


$$\rho_4 = \frac{Z_2 - Z_1}{Z_1 + Z_2} = \frac{\infty - 40}{40 + \infty} = \frac{\infty}{\infty} = 1$$
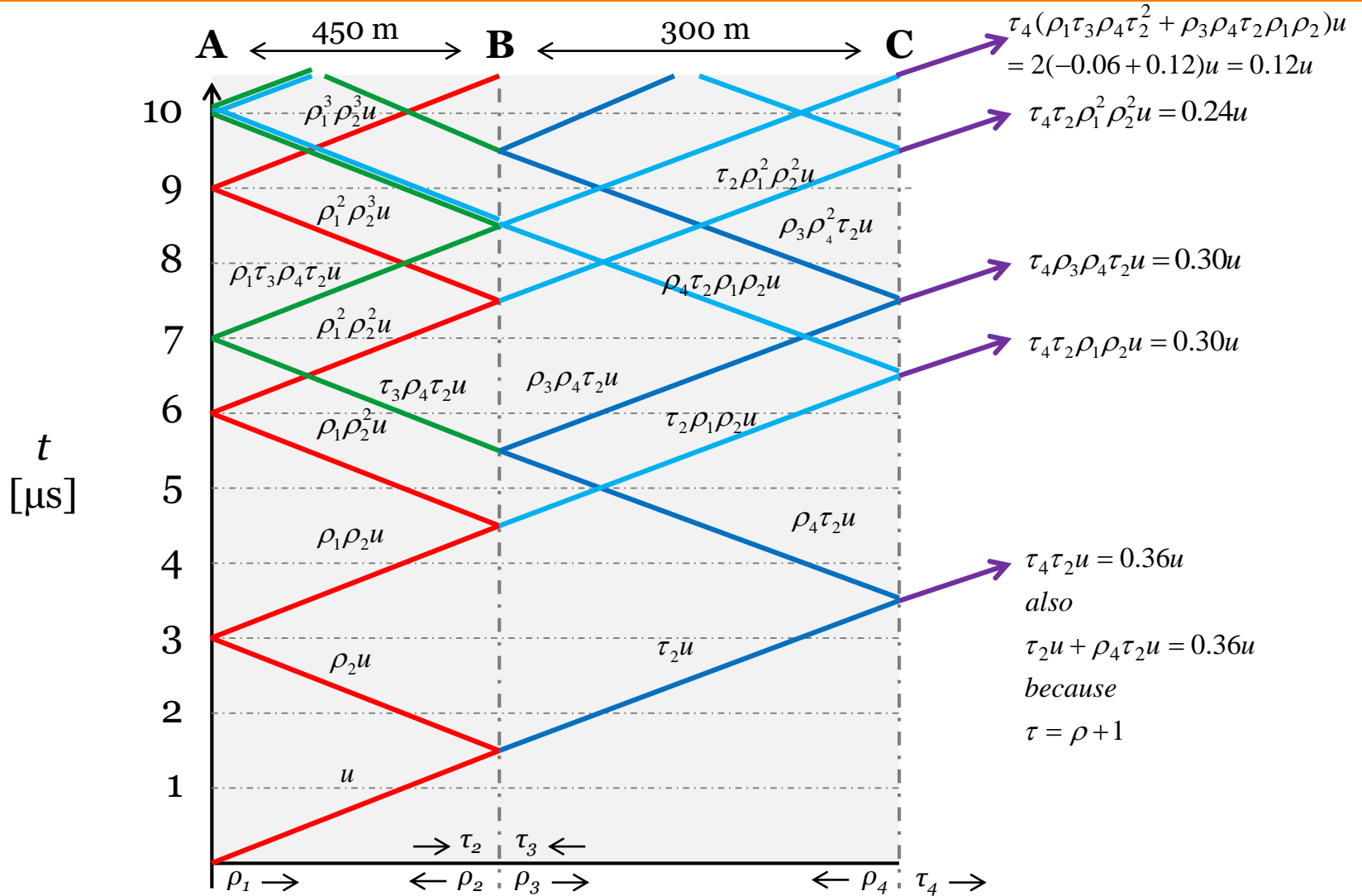
# Propagation of waveform:

$$t_{AB} = \frac{l_j}{v_j} = 1.5 \mu\text{s}$$


$$t_{BC} = \frac{l_k}{v_k} = 2.0 \mu\text{s}$$



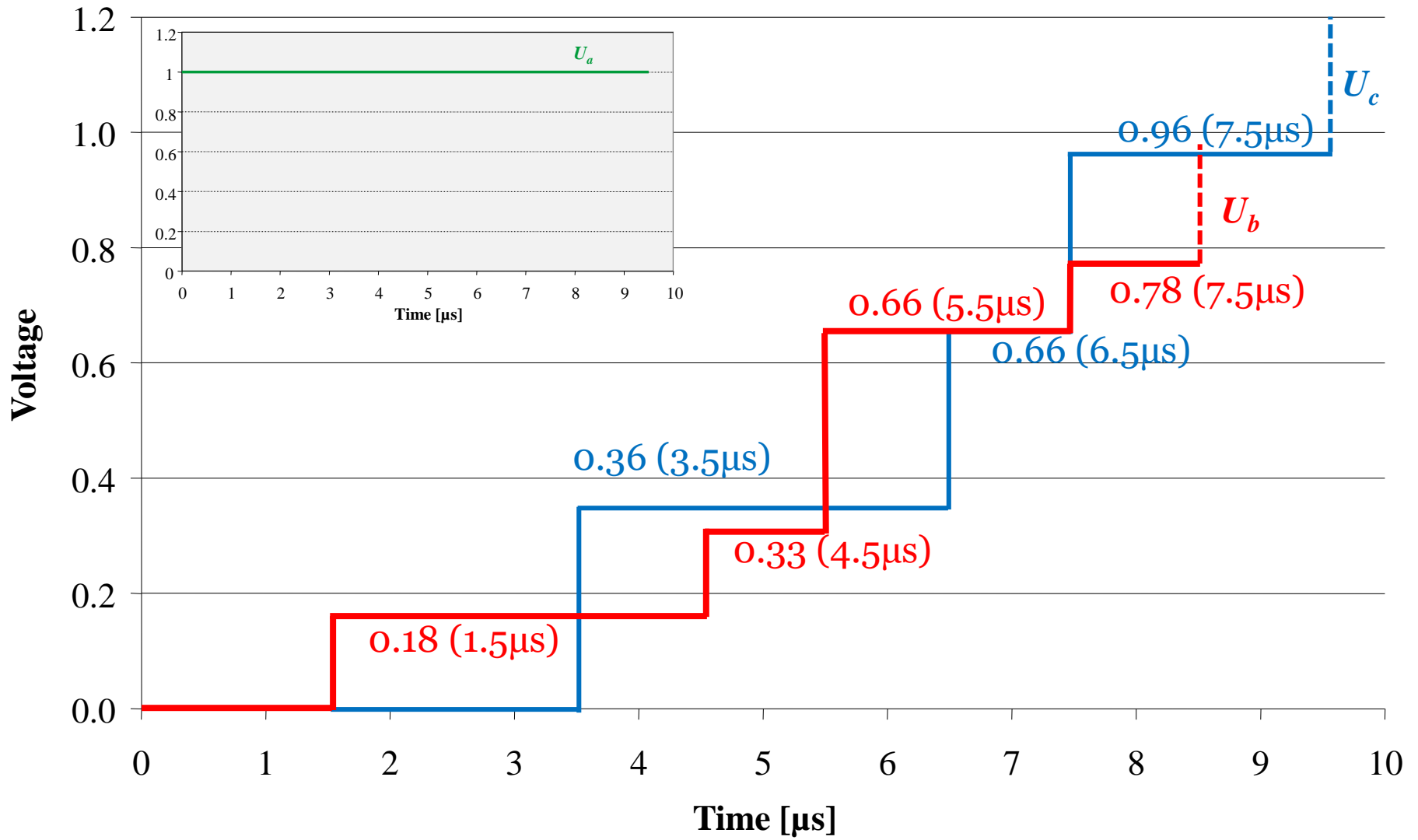
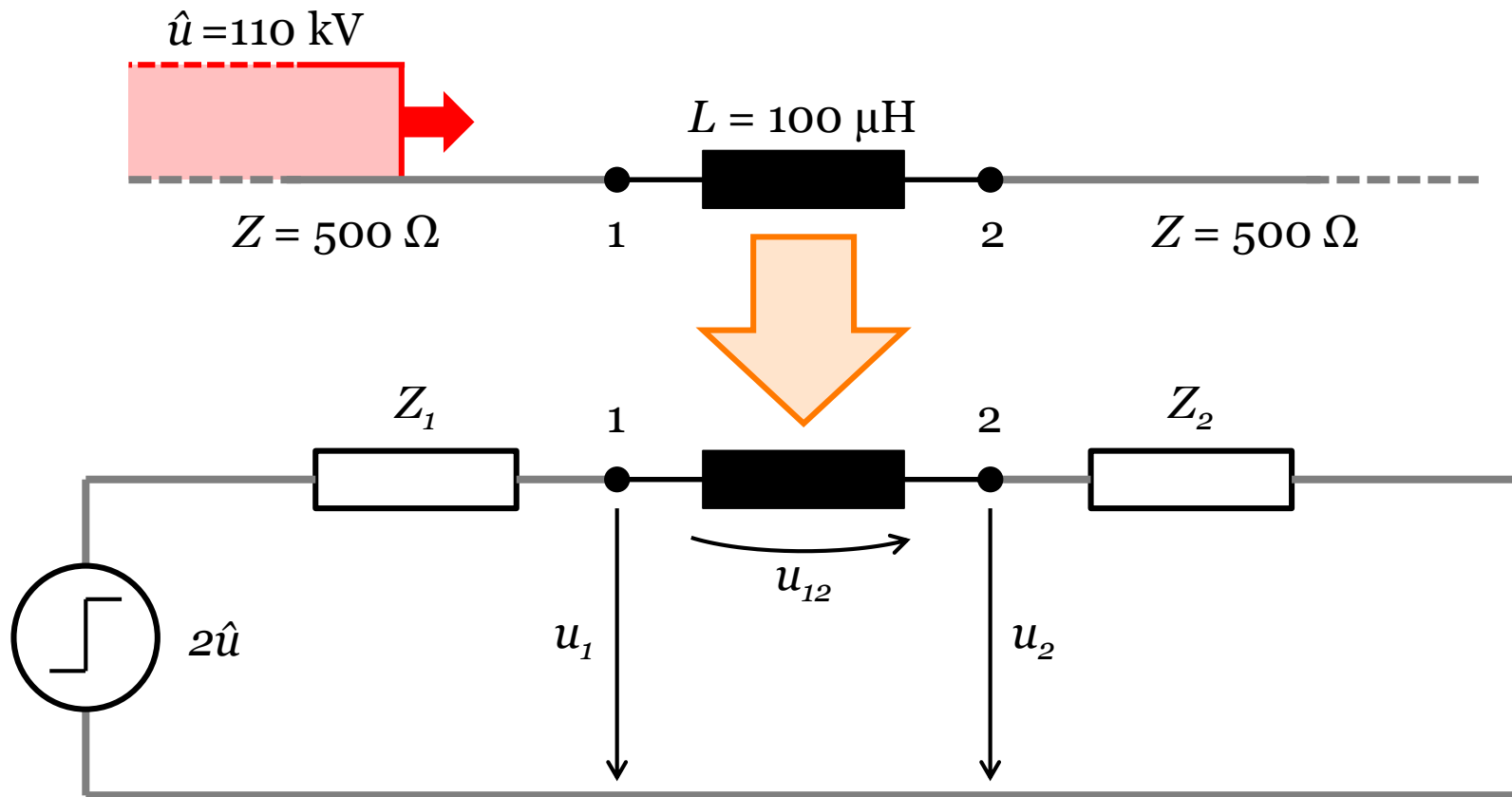
## Question 2

- A current transformer is linked to a 20-kV bare conductor line. The primary coil inductance is  $100 \mu\text{H}$ . Wave impedance of the line is  $500 \Omega$ . A step wave of amplitude 110 kV arrives at the current transformer. Show, using equations and approximate drawings, both of the transformer's 20-kV terminals against ground and also the voltage between the terminals.



Easy  
Solution

Lecture slides:

$$u_1(t) = 2\hat{u} - \frac{Z_1}{Z_1 + Z_2} 2\hat{u}(1 - e^{-t/\tau})$$

$$u_2(t) = \frac{Z_2}{Z_1 + Z_2} 2\hat{u}(1 - e^{-t/\tau})$$

$$u_{12}(t) = 2\hat{u}e^{-t/\tau}$$


$$\tau = \frac{L}{Z_1 + Z_2}$$

$$u_1(t) = 110(1 + e^{-t/0.1\mu\text{s}}) \text{ kV}$$


$$u_2(t) = 110(1 - e^{-t/0.1\mu\text{s}}) \text{ kV}$$

$$u_{12}(t) = 220e^{-t/0.1\mu\text{s}} \text{ kV}$$
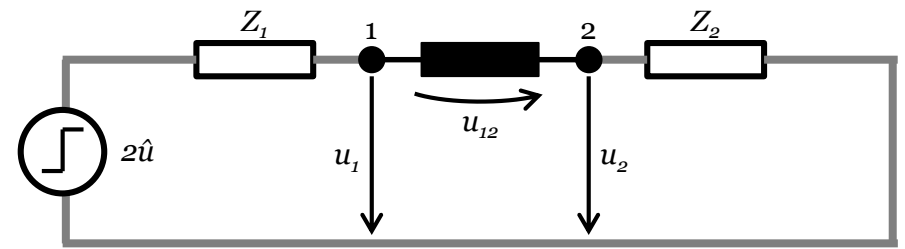
# Derive the equations using Laplace transformation:



$u_1$

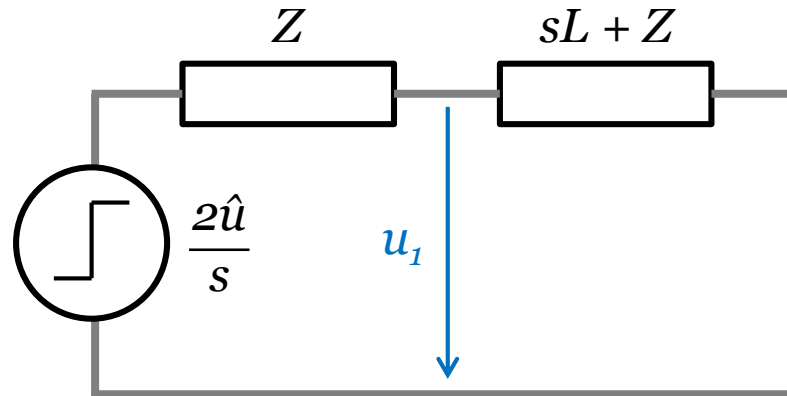

$$u_1 = \frac{sL + Z}{sL + 2Z} \cdot \frac{2\hat{u}}{s}$$

$$u_1 = \left( \frac{sL + 2Z}{sL + 2Z} - \frac{Z}{sL + 2Z} \right) \frac{2\hat{u}}{s} = \left( 1 - \frac{Z}{sL + 2Z} \right) \frac{2\hat{u}}{s} = \frac{2\hat{u}}{s} - \frac{2\hat{u}Z}{sL \left( s + \frac{2Z}{L} \right)}$$

Laplace

$$\frac{1}{s} \Rightarrow u_s(t)$$

Laplace


$$\frac{a}{s(s+a)} \Rightarrow 1 - e^{-at}$$

$$\left[ \tau = \frac{L}{Z_1 + Z_2} = \frac{L}{2Z} \right]$$


$$\rightarrow L^{-1} = 2\hat{u} - \hat{u}(1 - e^{-\frac{2Z}{L}t}) = \hat{u}(2 - 1 + e^{-\frac{2Z}{L}t}) = \hat{u}(1 + e^{-\frac{t}{\tau}}) = 110(1 + e^{-t/0.1\mu s}) \text{ kV}$$


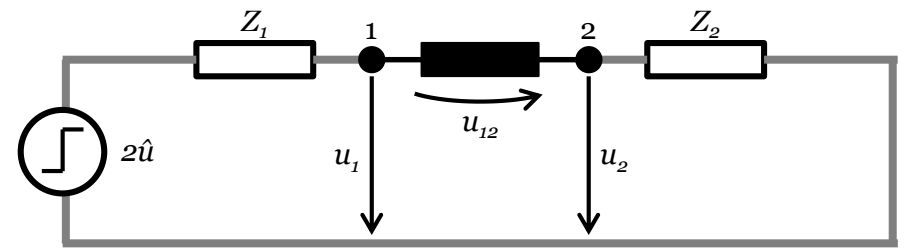
# Derive the equations using Laplace transformation:



$u_2$

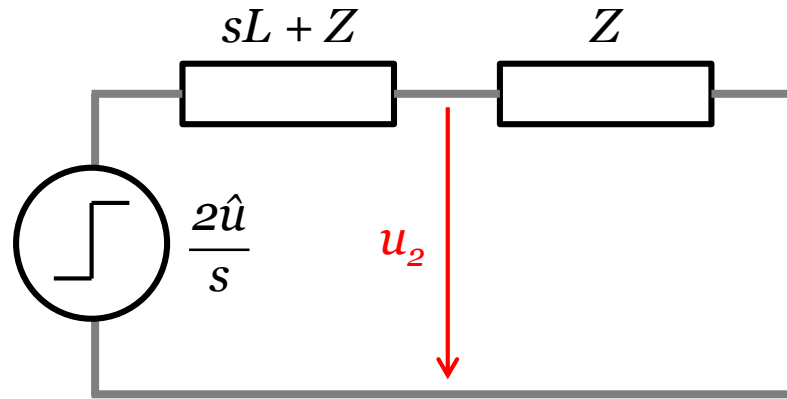


$$u_2 = \frac{Z}{sL + 2Z} \cdot \frac{2\hat{u}}{s}$$

$$u_2 = \frac{2\hat{u}Z}{s(sL + 2Z)} = \frac{2\hat{u}Z}{sL \left( s + \frac{2Z}{L} \right)} = \hat{u} \frac{\frac{2Z}{L}}{s \left( s + \frac{2Z}{L} \right)}$$


Laplace  $\frac{a}{s(s+a)} \Rightarrow 1 - e^{-at}$

→  $L^{-1} = \hat{u}(1 - e^{-\frac{2Z}{L}t}) = \hat{u}(1 - e^{-\frac{t}{\tau}}) = 110(1 - e^{-t/0.1\mu s}) \text{ kV}$
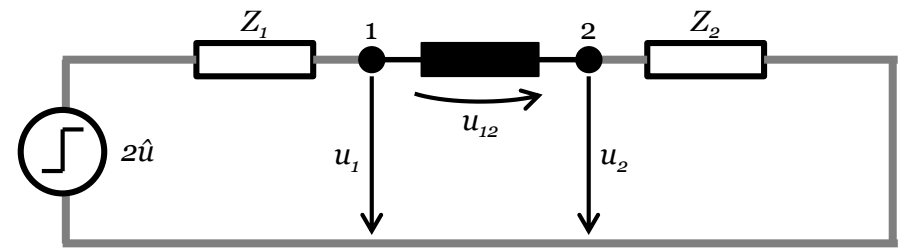
# Derive the equations using Laplace transformation:



$u_{12}$

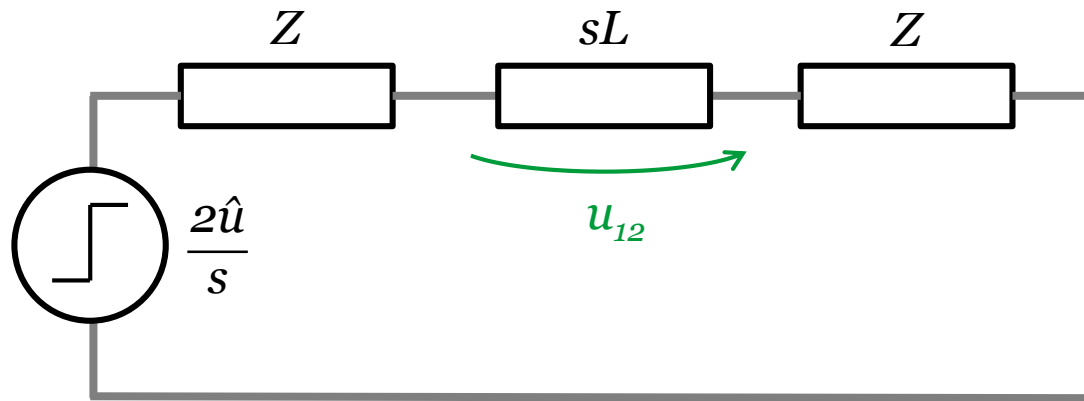


$$u_{12} = \frac{sL}{sL + 2Z} \cdot \frac{2\hat{u}}{s}$$

$$u_{12} = \frac{2\hat{u}L}{sL + 2Z} = \frac{2\hat{u}L}{L\left(s + \frac{2Z}{L}\right)} = 2\hat{u} \frac{1}{s + \frac{2Z}{L}}$$

Laplace


$$\frac{1}{s + a} \Rightarrow e^{-at}$$

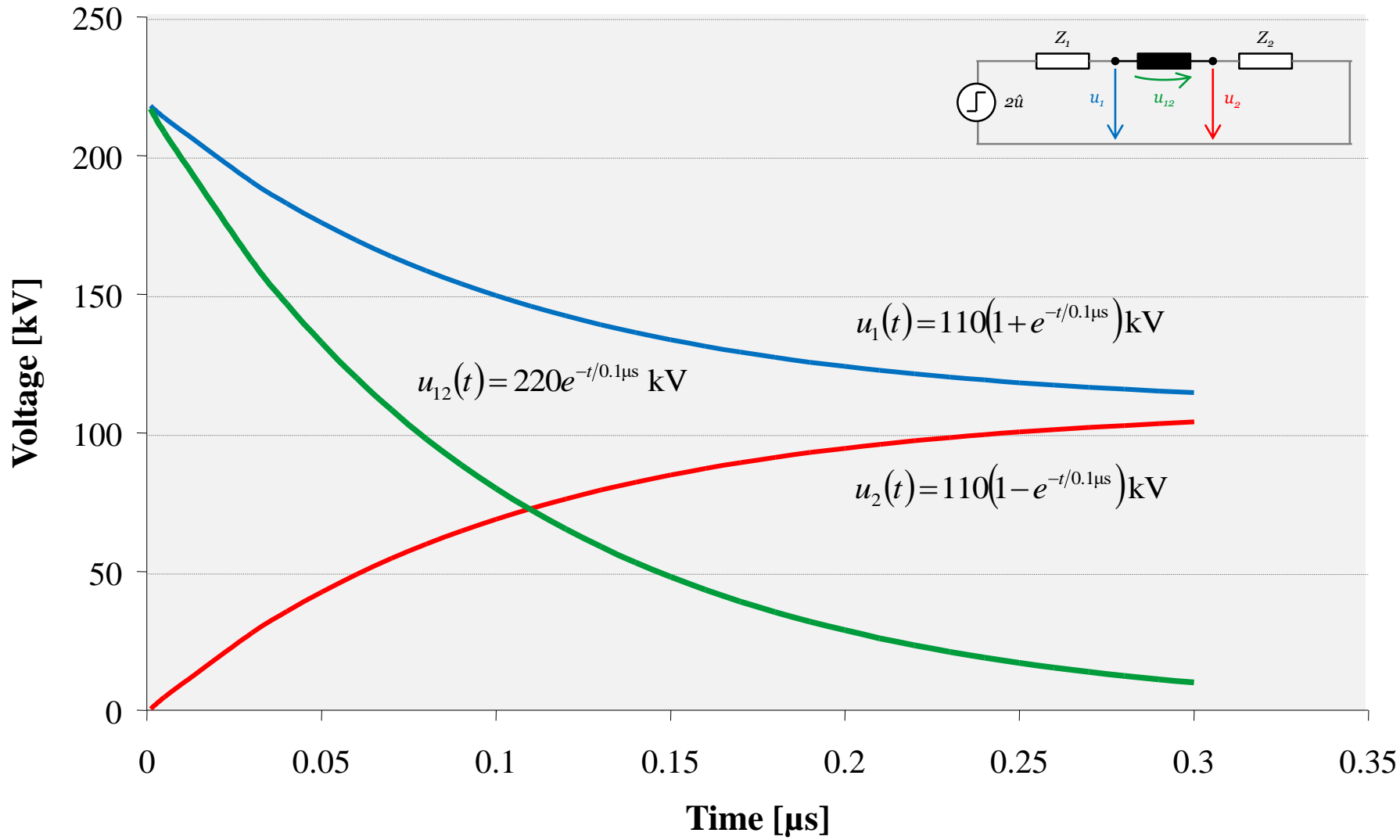
$$\Rightarrow L^{-1} = 2\hat{u} \cdot e^{-\frac{2Z}{L}t} = 2\hat{u}e^{-\frac{t}{\tau}} = 220e^{-t/0.1\mu s} \text{ kV}$$



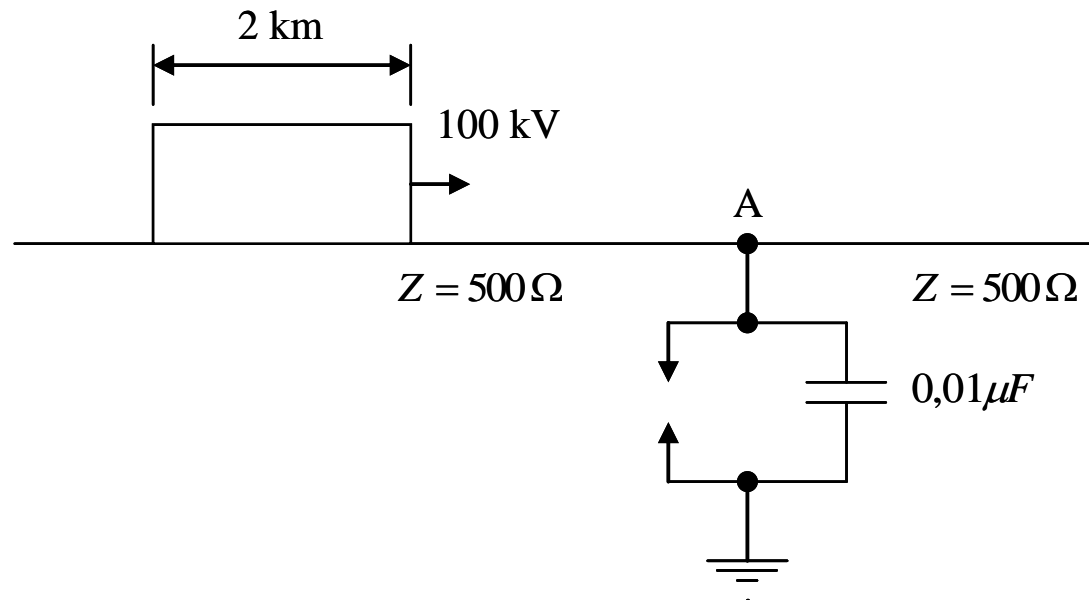
## Question 3

- An overhead line receives a square impulse of amplitude 100 kV and length 2 km at point A. Point A is connected to a spark gap parallel with a  $0.01 \mu\text{F}$  capacitor. The inception voltage of the gap is 50 kV. Draw the reflecting waveform at point A and define the waveform parameters.



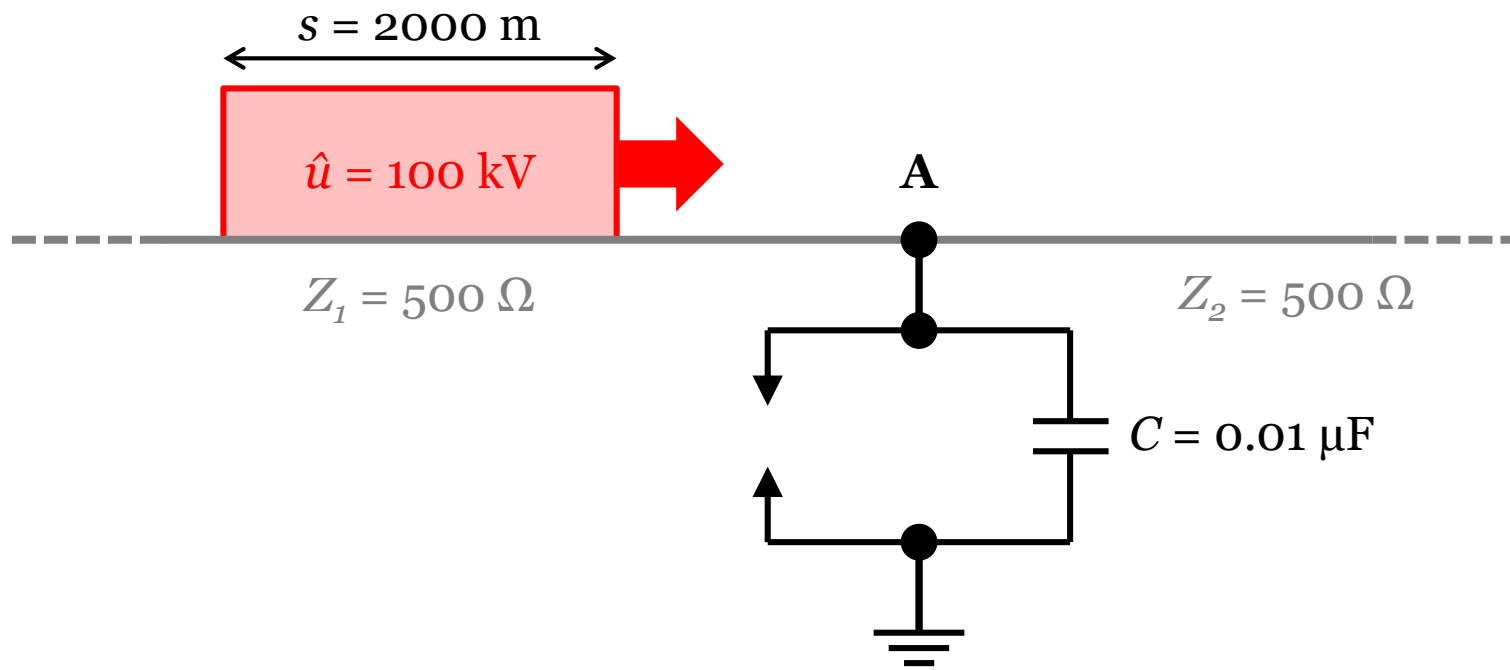

Equivalent  
Circuit

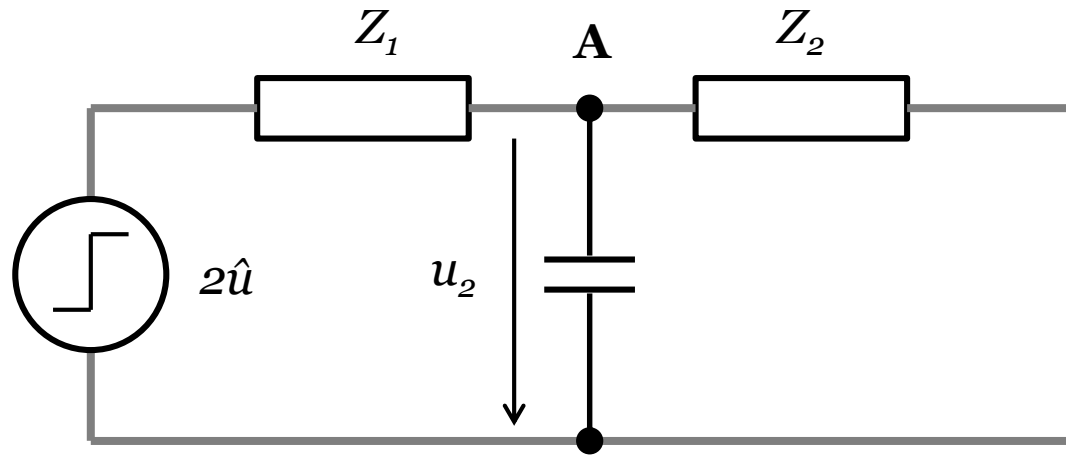

$$u_2 = \frac{Z_2}{Z_1 + Z_2} 2\hat{u} (1 - e^{-t/\tau})$$

$$\tau = \frac{Z_1 Z_2}{Z_1 + Z_2} C$$

$$u_2 = 100(1 - e^{-t/\tau}) \text{ kV}$$

$$u_2 = 100(1 - e^{-t/\tau}) \text{ kV}$$

**Inception voltage of spark gap = 50 kV:**

$$50 = 100(1 - e^{-t/\tau}) \Rightarrow 0.5 = 1 - e^{-t/\tau} \Rightarrow 0.5 = e^{-t/\tau} \Rightarrow \ln 0.5 = -\frac{t}{\tau}$$


$$\tau = \frac{Z_1 Z_2}{Z_1 + Z_2} C$$

**Inception time**  
(moment of ignition)

$$t = -\tau \ln 0.5 = -\frac{500 \cdot 500}{500 + 500} (0.01 \cdot 10^{-6}) \ln 0.5 = 1.73 \mu\text{s}$$

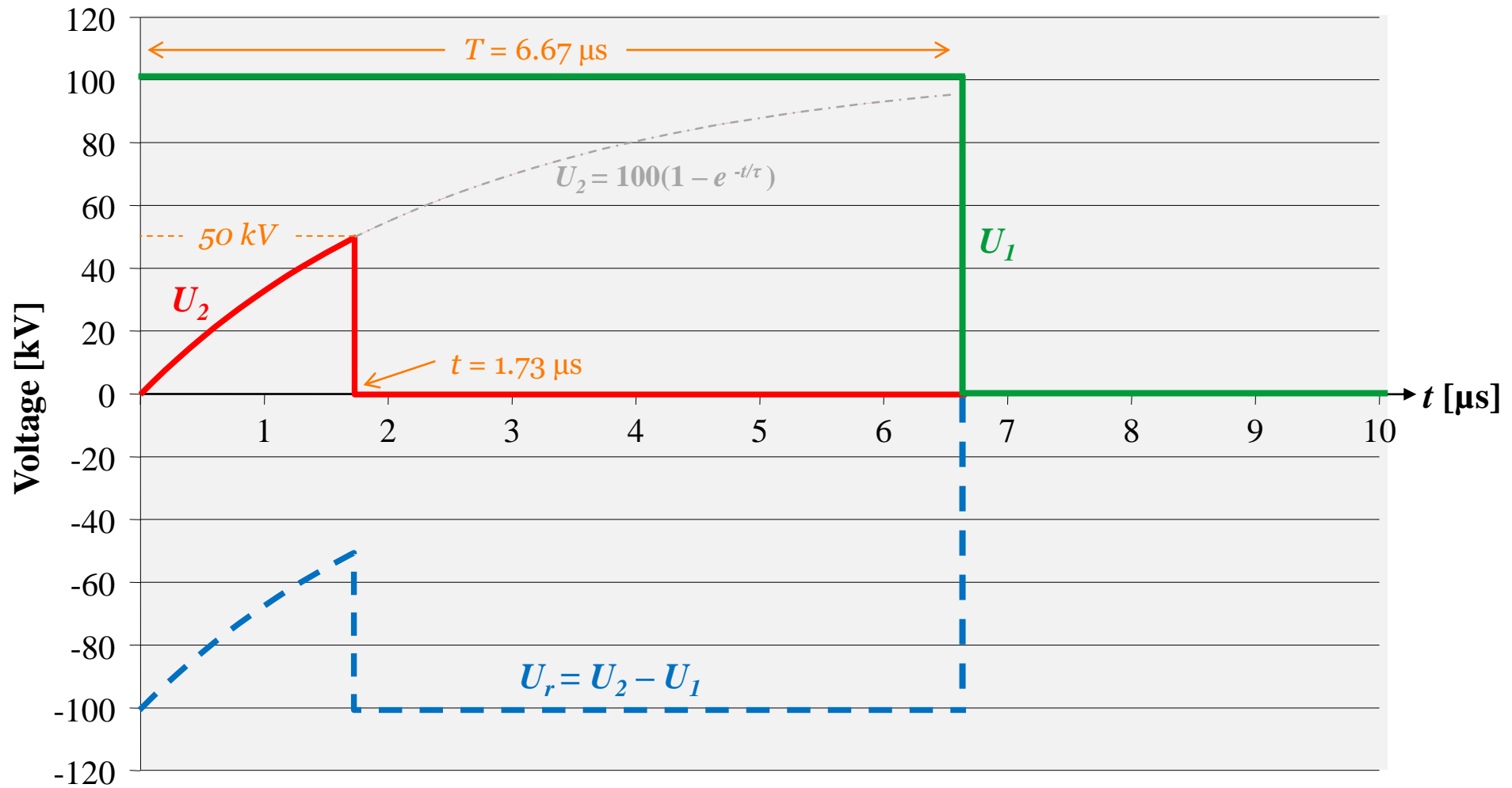**Duration of impulse**




$$T = \frac{s}{v} = 6.67 \mu\text{s} \quad (v = \text{speed of light } c)$$



**Reflected wave:**

$$u_{1r} = u_2 - u_1$$
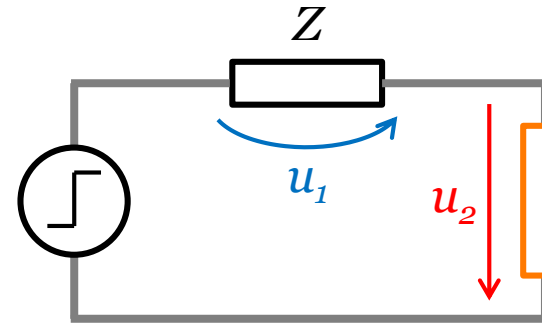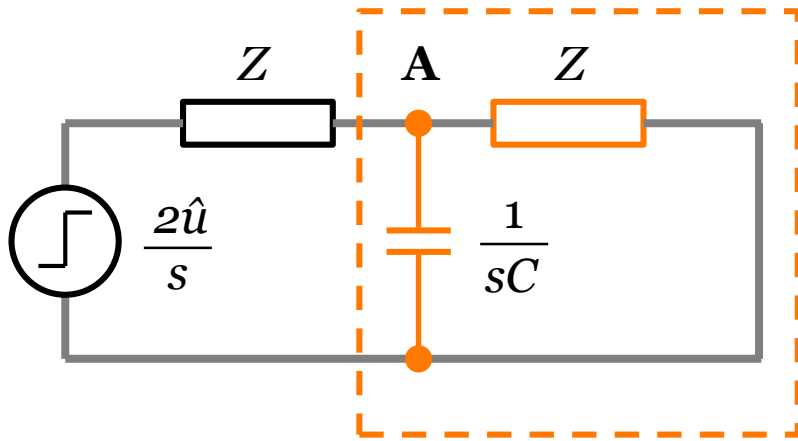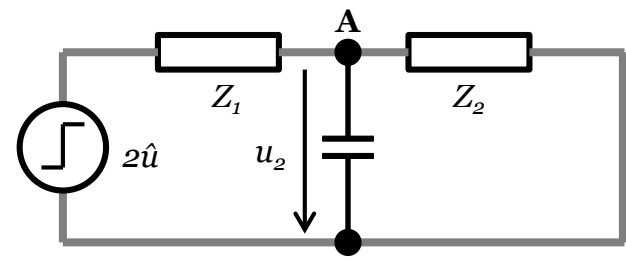
# Derive the equations using Laplace transformation:



$$\frac{Z \cdot \frac{1}{sC}}{Z + \frac{1}{sC}} = \frac{Z}{ZCs + 1}$$

$$u_2 = \frac{\frac{Z}{ZCs + 1}}{Z + \frac{Z}{ZCs + 1}} \cdot \frac{2\hat{u}}{s} = \frac{Z}{Z(ZCs + 1) + Z} \cdot \frac{2\hat{u}}{s} = \frac{1}{(ZCs + 1) + 1} \cdot \frac{2\hat{u}}{s} = \frac{1}{ZCs + 2} \cdot \frac{2\hat{u}}{s} = \frac{2\hat{u}}{s(ZCs + 2)} = \frac{2\hat{u}}{sZC \left( s + \frac{2}{ZC} \right)} = \hat{u} \frac{\frac{2}{ZC}}{s \left( s + \frac{2}{ZC} \right)}$$

$$\Rightarrow L^{-1} \Rightarrow \hat{u} \left( 1 - e^{-\frac{2}{ZC}t} \right) = 100 \left( 1 - e^{-t/\tau} \right) \text{ kV}$$

$$\tau = \frac{ZC}{2}$$

Laplace

$$\frac{a}{s(s+a)} \Rightarrow 1 - e^{-at}$$