
 


Frequency Synthesizers (SX)

 

- System level & concepts
 - SX principles
- Phase-locked loop
 - "theory" / CP-PLL / ADPLL
- Oscillators
 - Ring & LC
 - Frequency dividers
 - Quadrature generation


SX Requirements




- Frequency span --- cover the required bandwidth + margin for PVT
- Channel spacing & settling time
- Phase noise
- IQ-generation --- Amplitude and phase imbalance (IRR)

Impact of Phase Noise

Reciprocal mixing

 

Phase noise impacts IQ-constellation

 

In TX, phase noise causes out-of-band spurious emission.

Phase noise requirement depends on:

- Channel spacing
- Modulation method (eg. compare QAM-16 vs. QAM-256)
- Required sensitivity and selectivity
- Specified environment ("hostile" / "friendly")
- TX: emission mask

Phase Noise Specifications


Phase noise specification for SX given either by

- Noise/Carrier at certain offset, e.g. $N/C @ 1 \text{ MHz} < -120 \text{ dBc/Hz}$
- Integrated N/C profile \rightarrow can be then converted to jitter spec


System	Band [MHz]	Ch. spacing [kHz]	N/C [dBc/Hz] @kHz	norm-N/C* [dBc/Hz]
IS54	824-849	30	-115@60	-132
GSM	880-915	200	-141@3000	-125
DECT	1880-1900	1728	-97@1800	-91
WCDMA	1920-1980	5000	-129@8000	-111
WLAN (b)	2400-2483.5	22000	-103@1000	-105
BlueTooth	2400-2483.5	1000	-109@1000	-111
GPS	1575.42	-	-95@1000	-93
DOCSIS**	47-862	6000	-82@10	-100
DVB-S	10700-12750	fixed LO1	-95@100	-131
* Normalized to 2GHz and 1MHz, $N/C \sim (f_o/f_m)^2$ **data over cable-TV				

IQ Imbalance

Hartley Receiver

 

DCR

 

- LO signals (I) and (Q): equal amplitude (A) and 90-degree phase shift (ϕ)
- ΔA and $\Delta\phi$ results in imperfect image rejection or reduced SNR for DRC
- Every signal path element contribute to IRR, but usually LO imperfections dominate
- Image-Reject Ratio (IRR) is a measure of LO signal imbalance


$$IRR = \frac{1 + 2A_{bal} \cos \Delta\theta + A_{bal}^2}{1 - 2A_{bal} \cos \Delta\theta + A_{bal}^2}$$

- Typically DCRs need **IRR > 30 dB** $\rightarrow A_{bal} < 0.5$ dB and $\Delta\theta < 4^\circ$
- LO chain often includes limiting amplifiers \rightarrow phase error remains a challenge

Frequency Synthesis Methods

- | | |
|-------------------------------|---------|
| 1. Direct analog synthesis | "DAS" |
| 2. Direct digital synthesis | "DDS" |
| 3. Indirect digital synthesis | } "PLL" |
| 4. Indirect analog synthesis | |

Direct Analog Synthesis (DAS)

 

- Filters are filter banks and/or tunable filters
- Amplifiers not drawn
- Chain may include dividers as well

Main problem for RF IC implementation: good filters can not be integrated.


DAS is in use e.g. in measurement instruments – High perf, high price

Direct Analog Synthesis


At RF IC context we may use simplified versions of DAS.

”Manipulate a frequency tone with basic mathematical operators”

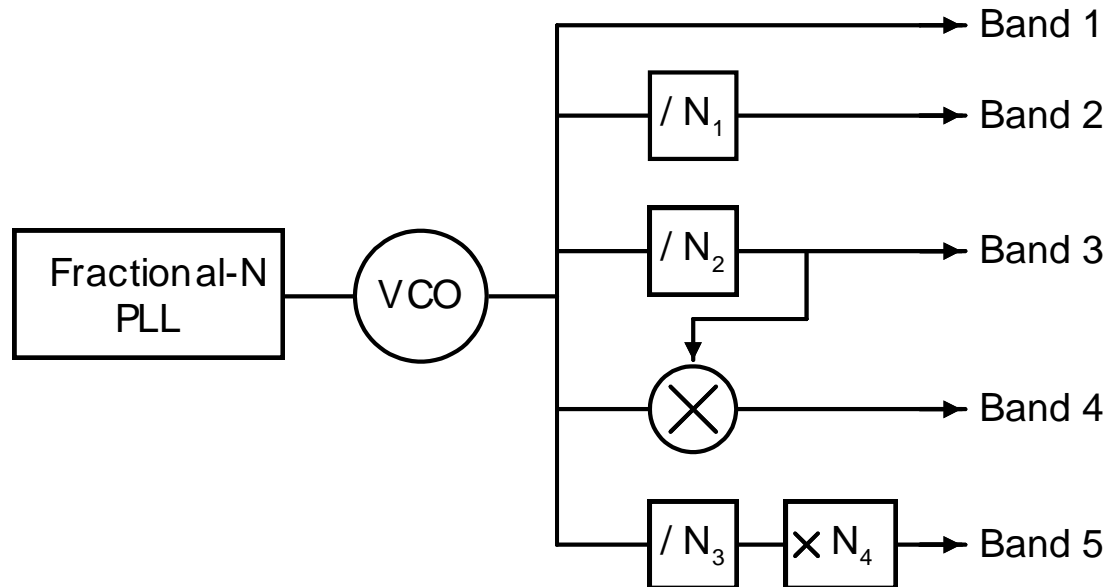- addition → mixer
- subtraction → mixer
- division → frequency divider
- multiplication → frequency doubler / tripler



Direct Digital Synthesis (DDS)

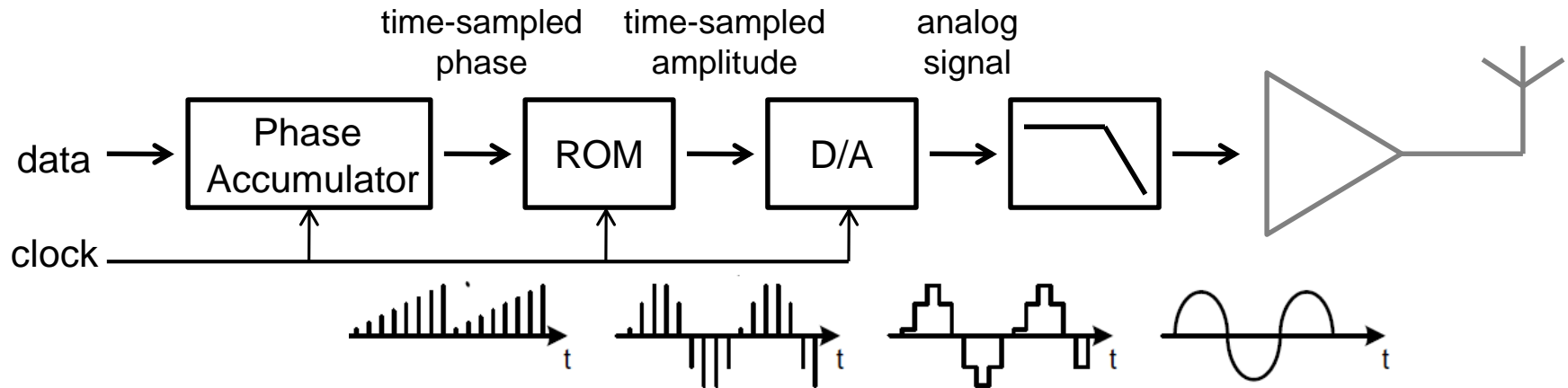

Problems:


needs a high-speed D/A

needs $f_{\text{clock}} > 3 * f_{\text{out}}$

DDS is used in base stations and LF radios (e.g. military)


Enables very complex modulations (military)

 Indirect Frequency Synthesis -- Phase-Locked Loop



Basic idea is to lock the oscillator into the incoming signal using a feedback loop.

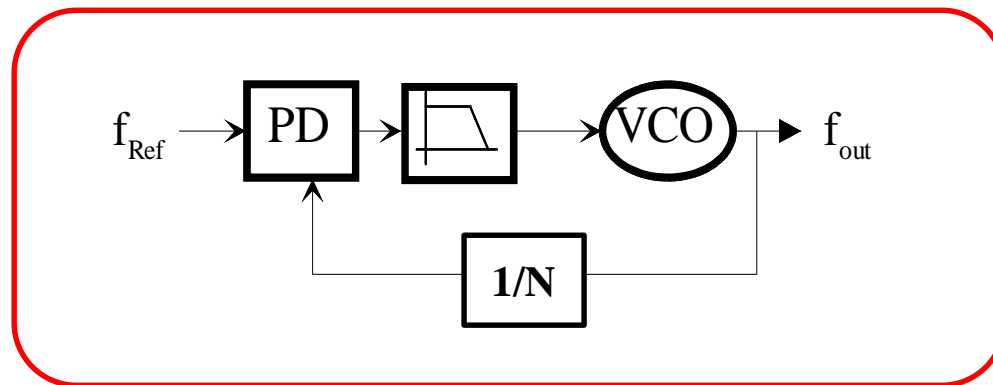
Compare to: feedback amplifier analysis in electronics
 feedback systems in control theory and automation



Some Books on PLL's

- Many basic text books on RF/analog IC electronics include a chapter on PLLs
 - Razavi: RF Microelectronics,
 - Lee: The Design of CMOS RF IC,
 - Grebene: Bipolar and MOS Analog IC Desing, etc.
- U. Rohde: many books on PLL's, not RF IC oriented
- F. Gardner: Phaselock Techniques
- R. Best: Phase-Locked Loops: design, simulation and applications
- J. Crawford: Frequency Synthesizer Design Handbook
- D. Wolaver: Phase-Locked Loop Circuit Design
- C. Vaucher: Architectures for RF Frequency Synthesizers
- D. Banerjee: PLL Performance, Simulation and Design (wireless.national.com)
- ... and many more 😊

Typical Results of Linear Analysis

 

PLL performs a high-pass filtering for the phase-error \rightarrow flat in-band noise

Fractional-N Concept


Integer-N PLL:

- reference frequency = channel spacing
- if N is very large
 - stability requires loop-BW $< f_{\text{ref}}/10 \rightarrow$ loop-BW small
 \rightarrow long settling time & poor phase noise reduction at high offset
 - ref. source & PD noise is multiplied by N
- Recall: GSM1800 ch. spacing=200 kHz, N~10000

Basic integer-N PLL is not good for small channel-spaced systems

\Rightarrow Improvements on PLL architecture (mixers in loop, dual-loop, frac-N PLL)

Dual-modulus divider

 

$$\frac{T_A}{T_A + T_B} \cdot \frac{f_{in}}{N} + \frac{T_B}{T_A + T_B} \cdot \frac{f_{in}}{N+1} = f_{out}$$

$$\frac{f_{out}}{f_{in}} = \frac{1}{N_{eff}} = \frac{1}{\frac{T_A + T_B}{T_A} \cdot N} + \frac{1}{\frac{T_A + T_B}{T_B} \cdot (N+1)}$$

Fractional-N Concept

- With the aid of dual-modulus divider division ratio can be set to $N \dots N+1$
Example: $T_A/(T_A+T_B)=90\%$, $T_B/(T_A+T_B)=10\%$ and $N=100 \Rightarrow N_{\text{eff}} \approx 100.1$

→ Frac-N PLL provides small channel step and still large loop-BW.


- Main problem : "fractional spurs"

→ Can be partly compensated by randomizing the timing
and using $\Sigma\Delta$ noise shaping.

(for details, Razavi presents an easy-to-read presentation in *RF Microelectronics*)

- Frac-N PLL requires more hardware and suffers from high spurious content and increased noise level compared to int-N PLL.
→ use only when integer-N is not feasible.


Charge-Pump PLL

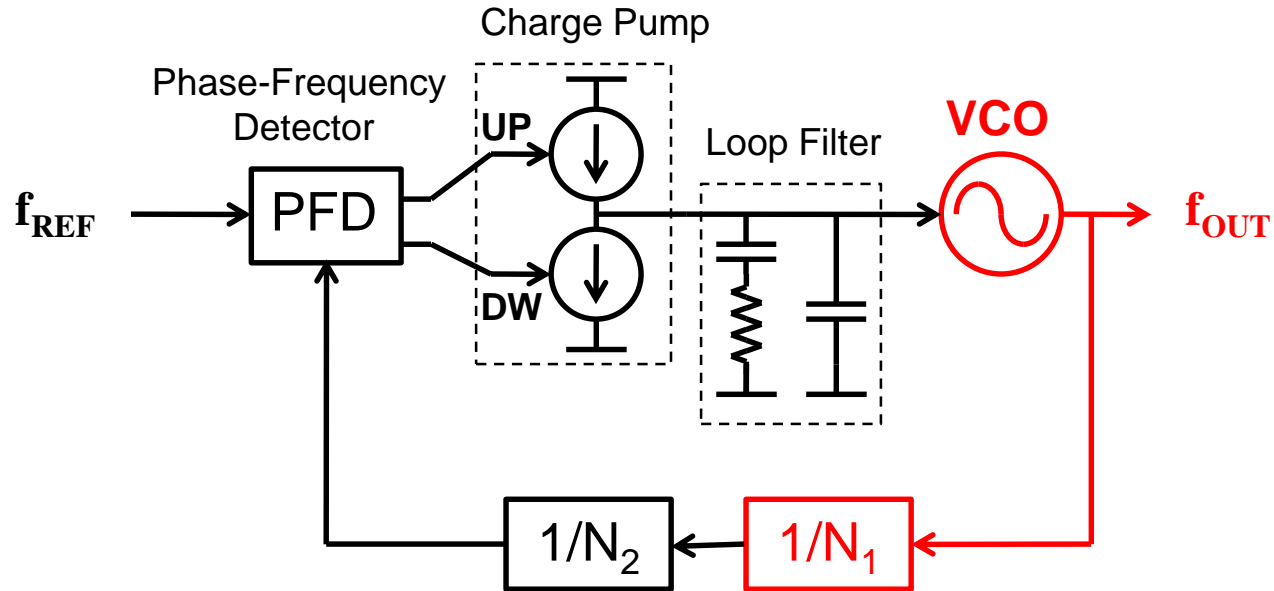

Impact of Technology Evolution

Recall our earlier paradigm changes, e.g.

 
- GaAs MESFET → Si Bipolar → CMOS
- Superheterodyne receiver → DCR
- Monolithic capacitors: vertical field → lateral field
- Gilbert cell mixer → current-mode passive mixer



"In a highly-scaled CMOS technology, time-domain resolution of a digital signal edge transition is superior to voltage resolution of analog signals"

R. Bogdan Staszewski
Manager of
TI's DRP group

All-Digital PLL

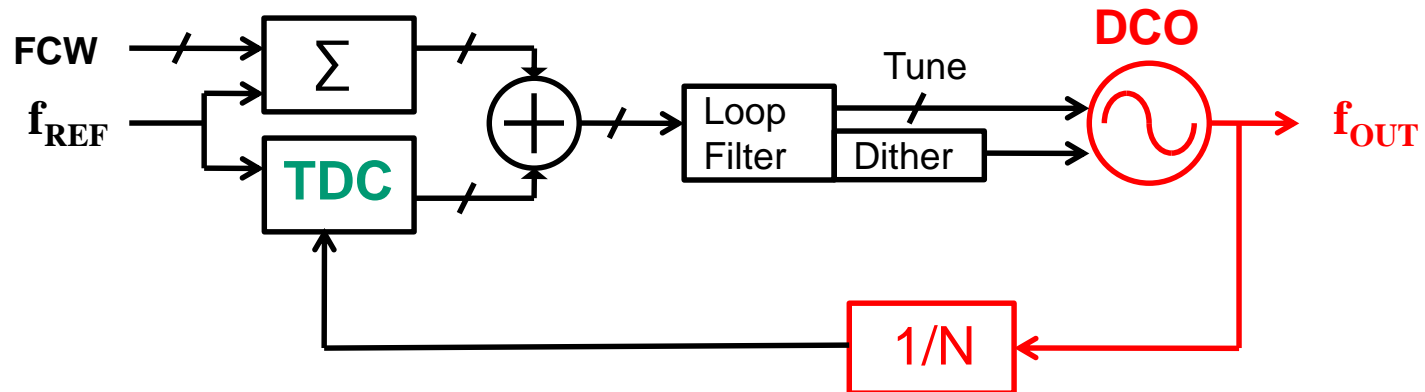

- Frequency control word (FCW) defines the target frequency
- Time-to-Digital converter (TDC) describes the output frequency with a digital word
- Error signal (digital) is filtered in the digital loop filter
- Digital-controlled oscillator (DCO) is tuned accordingly
- Dithering (compare to frac-N principle) is used to achieve fine frequency step
- Prescaler used to lower f_{out} (only if needed!) (65-nm CMOS: TDC $f_{\text{max}} \sim 1.7$ GHz)

Oscillators

Oscillator is an autonomous device which generates a waveform

→ It converts power from DC to "AC"

Variable frequency oscillator converts a control signal into frequency

→ information is converted from one mode to another

- VCO – voltage-controlled oscillator
- ICO – current-controlled oscillator
- DCO – digitally controlled oscillator

Oscillator waveform can be


- Sinusoidal : low level of higher harmonics
- Square : high level of higher harmonics, "clock signal"
- ramp or triangular is used at LF control circuits



Oscillator Classification

oscillation mode

 - Stable (no oscillation)
- Harmonic (sinusoidal)
- Relaxation
- Chaotic



No correlation !!

oscillator structure

- Phase shift (RC)
- G_m -C
- Crystal
- Multivibrator


- Ring
- LC

Oscillator Terms and Figures of Merit

- Tuning Range : ratio of maximum and minimum oscillation frequency
- VCO gain (K_{VCO}) and its deviation (linearity)
- Output power (preferably constant)
- supply voltage / current consumption / power efficiency
- Distortion in "sinusoidal" oscillators
- Temperature stability ($\Delta\text{freq}/\Delta T$)
- Pushing (PSRR) ($\Delta\text{freq}/\Delta\text{supply}$)
- Pulling (load) : Frequency shift caused by load impedance variation
- Pulling (injection) : Frequency shift caused by external disturbance
- Phase Noise / Jitter
- Die Area (IC implementation) / Component count (discrete circuits)


$$FOM \propto \frac{\text{Tuning Range}}{\text{Phase Noise} * \text{Power consumption}}$$

Ring Oscillator

 

$$f_{osc} = \frac{1}{2\tau N}$$
 
$$\tau \propto \frac{C_{load}}{I} \Rightarrow f_{osc} \propto \frac{I}{C_{load} N}$$




Real implementation is differential and simple cross-coupling creates proper fb.

- + can be transistor-only circuit
→ small area
- + Easy to tune, large tuning range

- 💣 power cons. is relative to freq.
(although follows technology-nodes)
- 💣 moderate (poor) phase noise


LC Oscillator

 

$$\omega_{osc} = \sqrt{\frac{1}{LC}}$$
$$G_{loss} - G_{neg} \leq 0$$

Is negative resistor a plausible device at all?

LC Oscillator

 


$$\omega_{osc} = \sqrt{\frac{1}{LC}}$$


$$G_{loss} - G_{neg} \leq 0$$

Is negative resistor a plausible device at all?

Transconductor in unity feedback

 


Gunn diode

 







Negative Conductance : Unity Feedback

(most of modern RFIC VCOs use these)

 


- Cross-coupled pair (CCP) : NMOS / PMOS / CMOS
- Biasing : top / bottom / none
- Advanced techniques like noise filtering
→ Really many different topologies exist


NMOS CCP Biasing

      

CMOS Cross-Coupled Pair

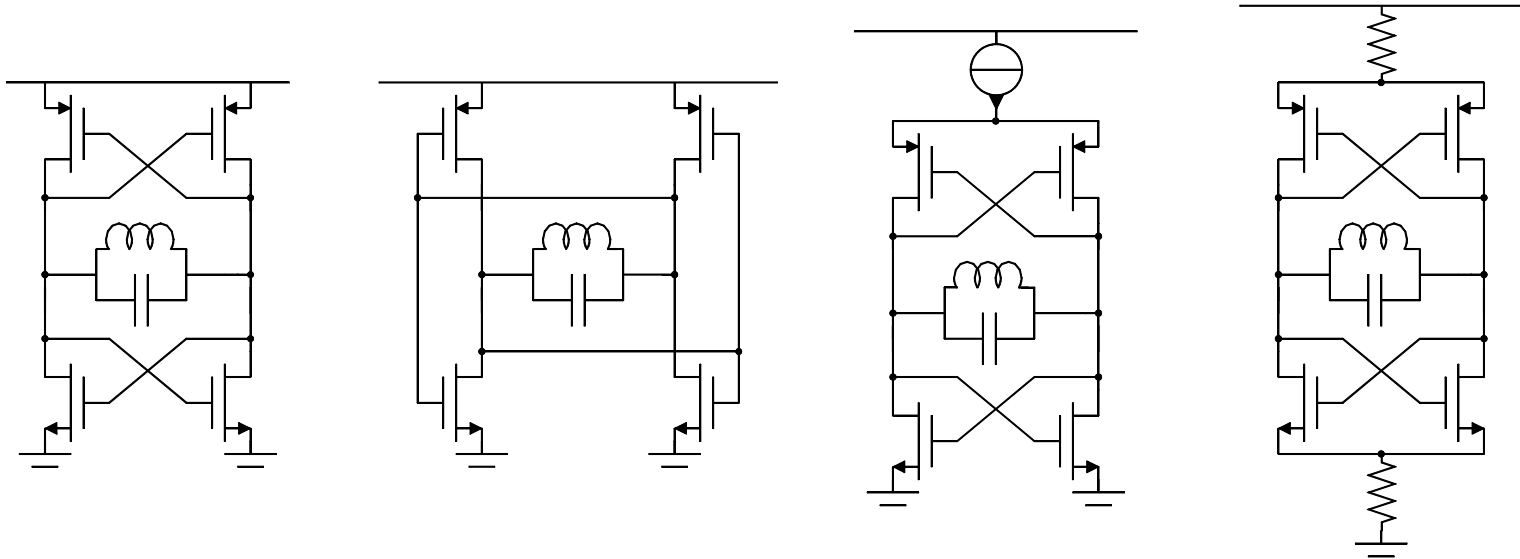

Negative conductance : reactive feedback






 


$nmos = g_m$ and V_{bias} -node is signal ground

$$Z_{in} = -\frac{g_m}{\omega^2 C^2} + \frac{1}{j\omega \frac{C}{2}} + \underbrace{(R_{coil} + j\omega L)}$$


Add a coil \rightarrow oscillator

Some Classical Oscillators

      


Linear Analysis Methods

1) Loop-Gain

 

$$|A(j\omega_{osc})B(j\omega_{osc})| \geq 1$$
$$\angle A(j\omega_{osc})B(j\omega_{osc}) = 180^\circ$$

2) Negative-Resistance

 

$$R = R_G(\omega_0) + R_L(\omega_0) \leq 0$$
$$X = X_G(\omega_0) + X_L(\omega_0) = 0$$

3) Nodal Equation



See details:

L. Larson : RF and microwave circuit
design for wireless communications

$$[Y] \cdot [V] = 0 \Rightarrow |Y| = 0 \Rightarrow \begin{aligned} RE\{|Y|\} &= 0 \\ IM\{|Y|\} &= 0 \end{aligned}$$

in each case you get two equations
one for f_{osc} and second for $-g_m$

Example: Common-Drain Colpitts

  

$$\begin{vmatrix} \frac{1}{j\omega L} + Y_{in} + j\omega C_1 + G_L & -Y_{in} - j\omega C_1 \\ -Y_{in} - j\omega C_1 - g_m & j\omega(C_1 + C_2) + Y_{in} + \frac{1}{R} + Y_o + g_m \end{vmatrix} = 0$$


$$\omega = \sqrt{\frac{1}{L \frac{C_2(C_1 + C_{in})}{C_1 + C_2 + C_{in}}} + \frac{G_L(\frac{1}{R} + g_o + g_m)}{C_2(C_1 + C_{in})}}$$

$$g_m > \frac{C_1 + C_{in}}{C_2} \left(\frac{1}{R} + g_o \right) + G_L \left(2 + \frac{C_1 + C_{in}}{C_2} + \frac{C_2}{C_1 + C_{in}} \right)$$

Oscillator Phase Noise


Intuitive approach : "noise mixing"

 - Oscillator is a nonlinear circuit
- oscillation swing is "internal LO"
- noise (int. & ext.) is mixed into carrier
- fb-loop performs filtering



Intuitive approach II : "Frequency modulation"

 - Oscillator is a VCO & ICO
- noise is modulating the oscillator frequency



Narrowband FM
approximation

$$v_{osc}(t) \approx A \cos \omega_0 t + \frac{A \cdot V_m \cdot K_{VCO}}{2\omega_m} [\cos(\omega_0 + \omega_m)t - \cos(\omega_0 - \omega_m)t]$$

Low phase noise

- Minimize nonlinearity
- Minimize K_{VCO} and other sensitivities

Oscillator Phase Noise

Consider ideal parallel LCR-type oscillator with noiseless G_{neg} .

There are losses in the resonator and corresponding noise source is $\frac{\overline{i_n^2}}{\Delta f} = 4kTG$

Impedance of the LC-tank $Z(\omega_0 + \Delta\omega) \approx -j \frac{\omega_0 L}{2 \frac{\Delta\omega}{\omega_0}}$

Tank quality factor $Q = \frac{1}{\omega_0 LG} \Rightarrow L = \frac{1}{\omega_0 QG}$


We have $|Z(\omega_0 + \Delta\omega)| \approx \frac{\omega_0}{2 \frac{\Delta\omega}{\omega_0} \omega_0 QG} = \frac{1}{2QG} \frac{\omega_0}{\Delta\omega}$

Noise voltage is $\frac{\overline{v_n^2}}{\Delta f} = \frac{\overline{i_n^2}}{\Delta f} \cdot |Z|^2 = 4kTR \left(\frac{1}{2Q} \frac{\omega_0}{\Delta\omega} \right)^2$

This is both amplitude and phase noise. Oscillator performs amplitude clipping \rightarrow no amplitude noise. Thus, divide above by two. Also recall $\overline{v_{sig}^2} = P_{sig} \cdot R$

Noise-to-carrier ratio is $N/C = \frac{2kT}{P_{sig}} \left(\frac{1}{2Q} \frac{\omega_0}{\Delta\omega} \right)^2$ Low phase noise \rightarrow Maximize P_{sig} and Q

Leeson's Phase Noise Model

 

$$\mathcal{L}(\Delta\omega) = 10 \cdot \log \left\{ \frac{2kT \cdot F}{P_{sig}} \left(1 + \left(\frac{1}{2Q} \frac{\omega_0}{\Delta\omega} \right)^2 \right) \cdot \left(1 + \frac{f_c}{\Delta\omega} \right) \right\}$$

Heurestical model (based on experiments)

- f_c is 1/f-noise corner \rightarrow close-in noise
- constant term "1" is included to describe the noise floor
- F is for additional noise due to $-g_m$

- 💣 f_c is not the same as device's 1/f-corner
- 💣 F is difficult to estimate *a priori*
- 💣 Based on linear time-invariant model

Frequency Dividers

From RF designer's point of view there are two types of logic: dynamic & static

Dynamic logic:

- "memory" element needs to be refreshed
- transistors operate as switches
- many logic families
- on/off switching → limited speed
- power consumption is related to speed :

$$P_{DC} = f \cdot V_{dd}^2 \cdot C$$

- speed scales with the technology
- power consumption scales with the technology

Static logic (SCL = source-coupled logic)



- "memory" element has continuous current
- devices have constant bias (no saturation)
- no speed limitation (as with dyn. logic)
- power – frequency dependency weaker
- differential signals (dyn. logic single-ended)
→ Better immunity to noise, glitches etc.

→ There is a frequency limit, set by the limited speed of dynamic logic or increased power consumption, where static logic becomes superior.

With 65-nm CMOS this limit is in range of 2-3 GHz, in 28-nm at 5-7 GHz.

SCL D-flipflop divider

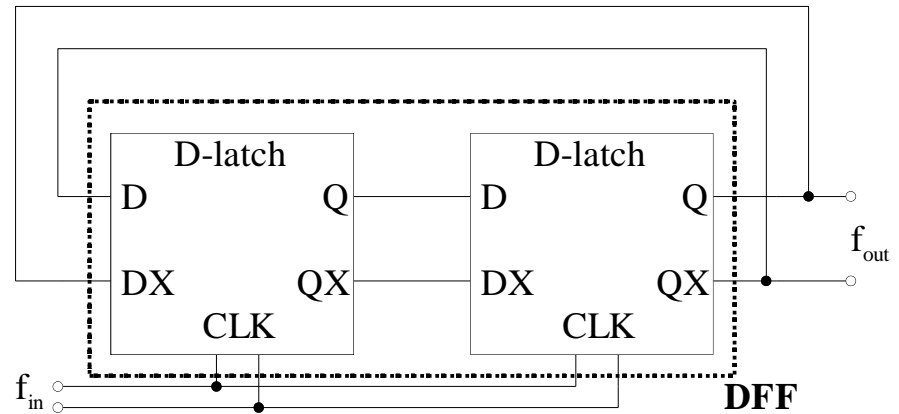 
- D-flipflop in unity feedback is a divide-by-two circuit
- D-flipflop consists of two D-latches



Divider Chains

Asynchronous chain


Divide by 2^N

 

- Power consumption lower after each division
- Higher noise (jitter)

Johnson counter


Divide by $2N$

 


- Each DFF runs at f_{in}
→ higher power cons.
- smaller noise (jitter)

Dual-modulus dividers


Div-2/3

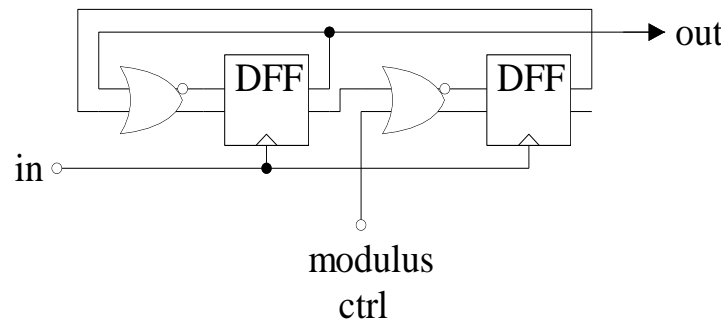

Div-3/4

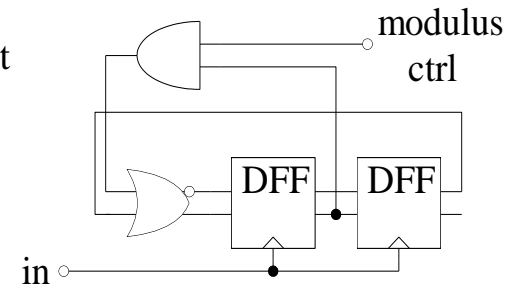

IQ Generation

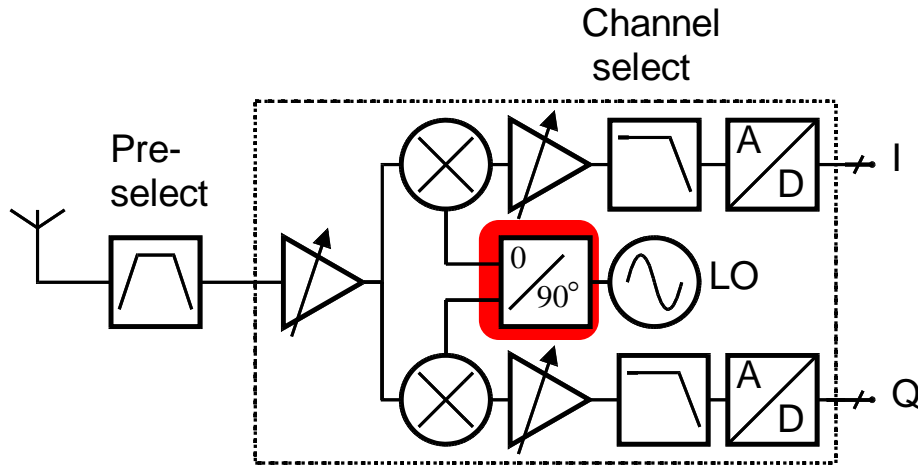


Four LO signals needed:
 $0^\circ / 90^\circ / 180^\circ / 270^\circ$


IQ amplitude and phase
balance (IRR) very important.

1. RC phase shifters \rightarrow polyphase RC filter
2. Divide-by-two circuit
3. Quadrature oscillators

RC Phase Shifters

 

constant IQ phase balance


 


constant IQ amplitude balance


RC-CR network

- Narrow bandwidth
- Sensitive to process spread
- Post-tuning possible
- Clipping amplifier helps


Polyphase RC filter

  




Divide-by-two IQ Generation

 

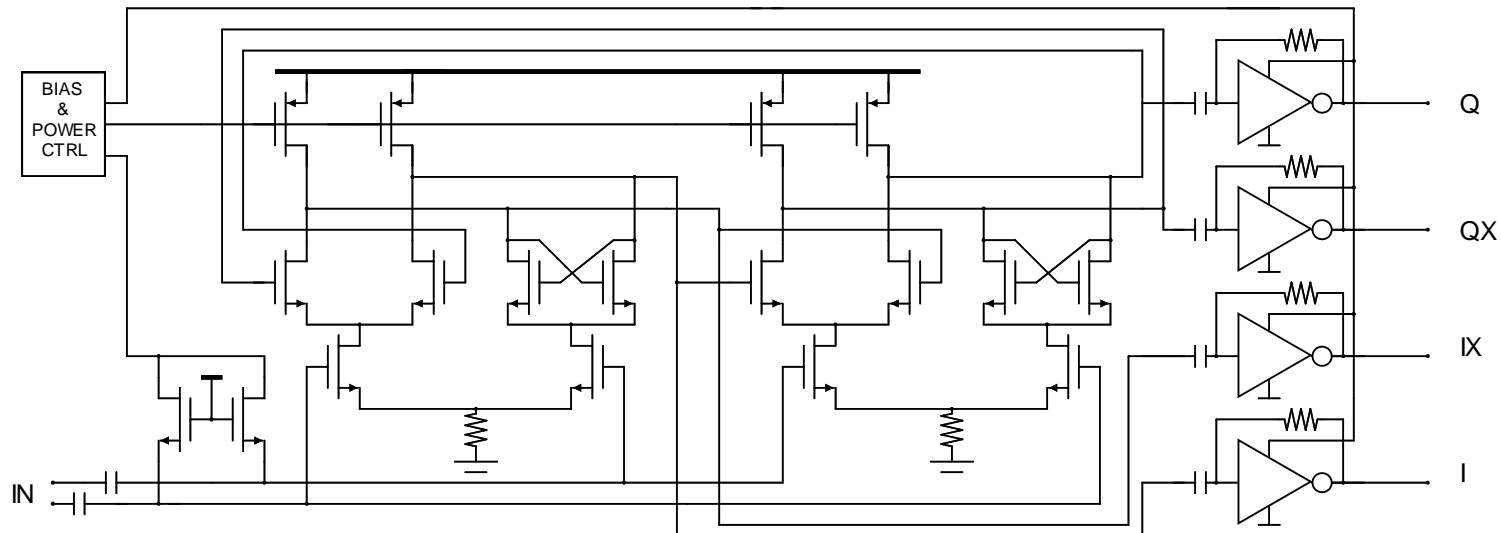- Wide bandwidth
- Compact size, easy to design well
- IRR limited by latch matching
- Requires double-freq signal
- Non-perfect input signal:
 - Amplitude error => phase error
 - Phase error attenuates a bit



Quadrature Oscillators

   

- Quadrature coupling results in increased phase noise
- Large die area

Summary

- SX requirements, impact of phase noise, IQ imbalance (IRR)
- DAS / DDS / PLL
- CP-PLL
- ADPLL
- Oscillators: Ring & LC
 - LC-oscillators: unity feedback / reactive feedback
 - Phase noise
- Frequency Dividers: dynamic "CMOS" / static "SCL"
- IQ signal generation: RC polyphase / Div-2 / quadrature osc.

Self-Learning Assignment 5

Objective is to familiarize yourself with frequency synthesizers.

All-digital phase-locked loops have become the main research and product development trend in the field of RF IC frequency synthesizers.

This topic also serves as an example of "digital RF".

Read a journal paper and find answers to some questions.

You can find the assignment from

MyCourses / Assignments - SLA / Self-learning assignment 5

Return your answer as a pdf-file to Return Box in the same page.

Last Meeting Tuesday 17.5.

Wrap-up & project presentations

PROJECT PRESENTATION

- 1) Create a slide set that represents your circuit and simulation results.
- 2) Return it to MyCourses / Project Work Return Box as a **PDF file**.
- 3) Prepare to present your work. Presentation should last about 10 minutes (= 5...7 slides).
- 4) Participation as audience is a part of the course. Therefore, reserve enough time for the last meeting.