
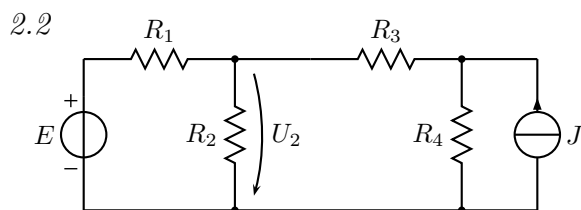
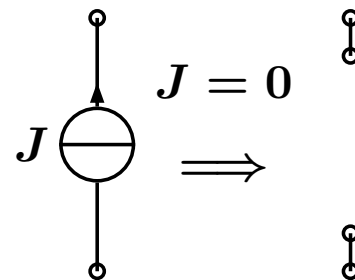


# ELEC-C9610 Basics of Electronics


## Calculation assignment 2. Deadline 14:00, September 28th, 2021

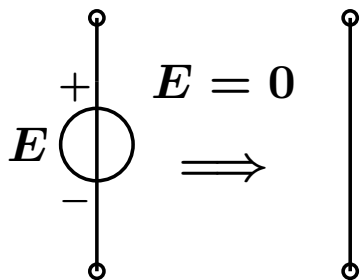- 2.1 When using the superposition method to analyze a circuit, we turn off sources in turn. Turning off a voltage source means to replace it by a short circuit. Turning off a current source is realized by replacing it by an open circuit. Now, explain,
- why turning off a voltage source canNOT be realized by replacing it by an open circuit and
  - why turning off a current source canNOT be realized by replacing it by a short circuit.



$R_1 = 3 \Omega$ ,  $R_2 = 6 \Omega$ ,  $R_3 = 2 \Omega$ ,  $R_4 = 8 \Omega$ ,  $E = 9 \text{ V}$  and  $J = 5 \text{ A}$ .

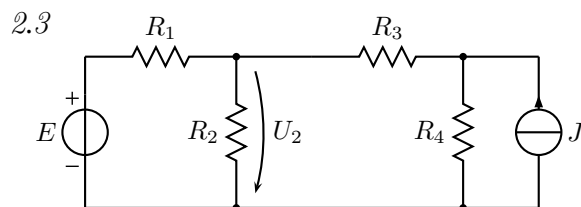- The use of thevenin's method: Find the voltage  $U_2$  over the resistance  $R_2$  by expressing the circuit by voltage sources and resistances (NO use of a current source).
- The use of the norton's method: Find the voltage  $U_2$  over the resistance  $R_2$  by expressing the circuit by current sources and resistances (NO use of a voltage source). Do you get the same voltage value as a)?



$R_1 = 3 \Omega$ ,  $R_2 = 6 \Omega$ ,  $R_3 = 2 \Omega$ ,  $R_4 = 8 \Omega$ ,  $E = 9 \text{ V}$  and  $J = 5 \text{ A}$ .

Find the voltage  $U_2$  over the resistance  $R_2$  using the superposition method. Do you get the same voltage value as exercise 2.2?