
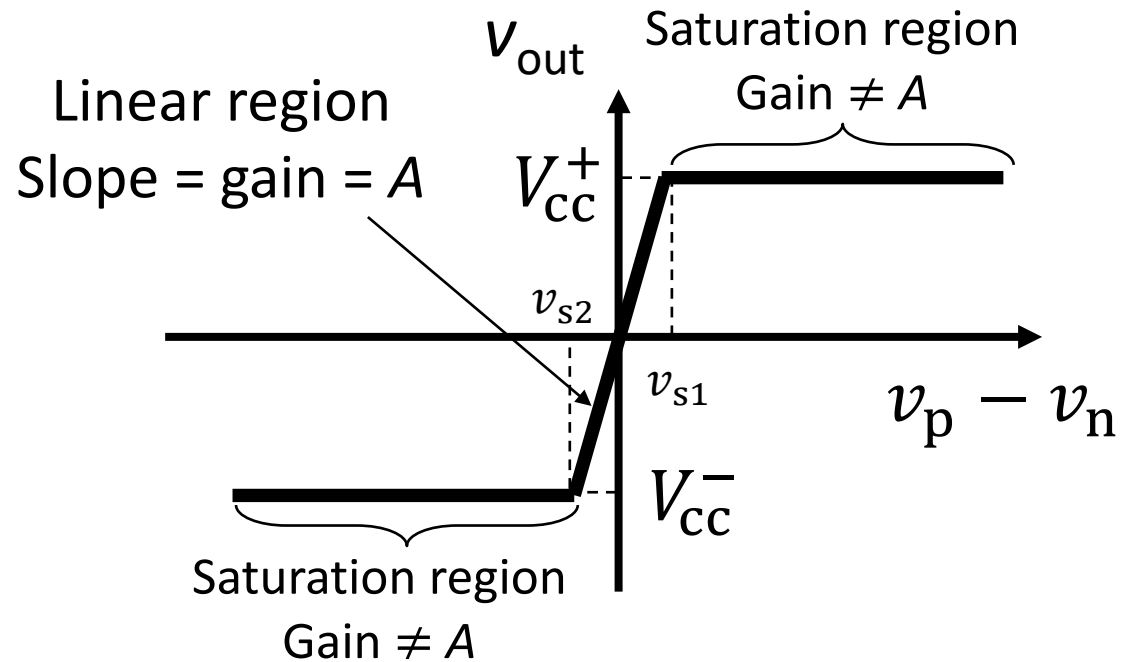


# Gain model of an ideal opamp

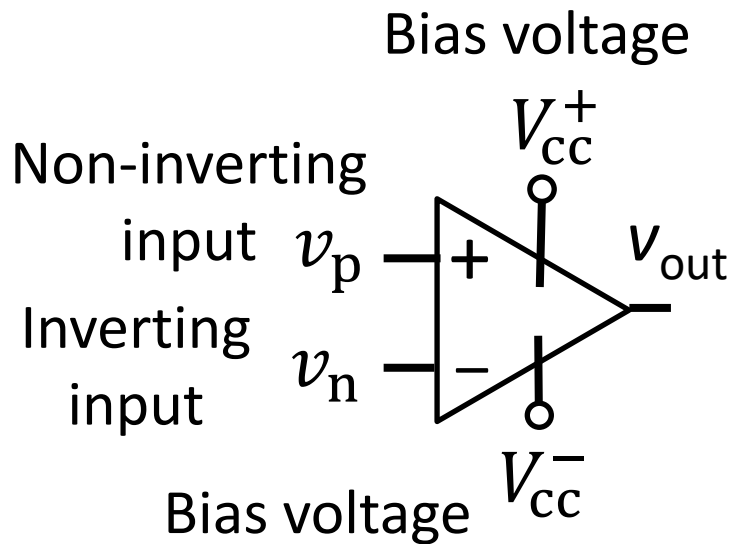


$$v_{out} = \begin{cases} V_{cc}^+, & v_{s1} < (v_p - v_n) \\ (v_p - v_n)A, & v_{s2} < (v_p - v_n) < v_{s1} \\ V_{cc}^-, & (v_p - v_n) < v_{s2} \end{cases}$$

Practically,  
 $|v_{s1}|, |v_{s2}| \sim \text{mV}$ ,  
 while  $V_{cc}^+, V_{cc}^- \sim \text{V}$
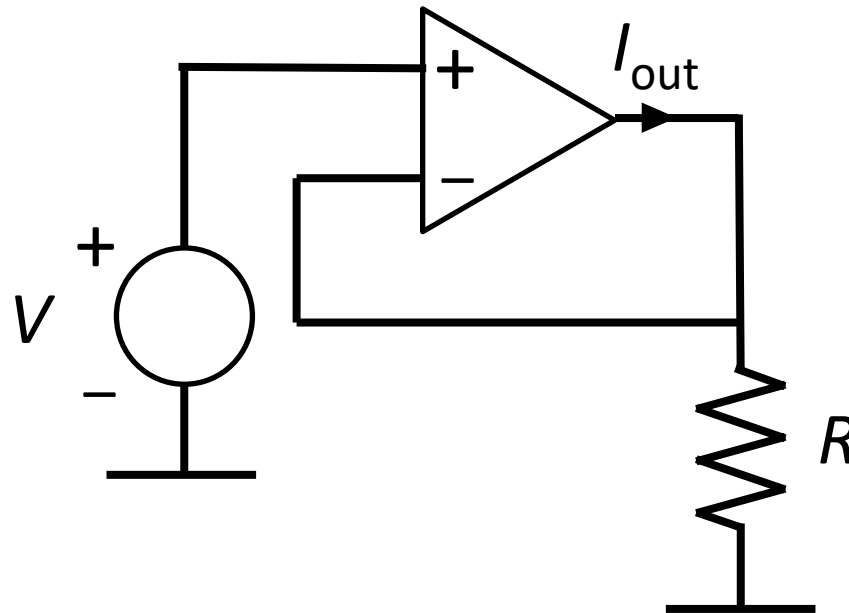
# Quiz 8


- Assume an ideal opamp. Derive the current  $I_{out}$ . [If bias voltage is not mentioned in the circuit, we can think  $V_{cc}^+ = \infty V$  and  $V_{cc}^- = -\infty V$ ]



$$V = 1 V$$
$$R = 1 k\Omega$$

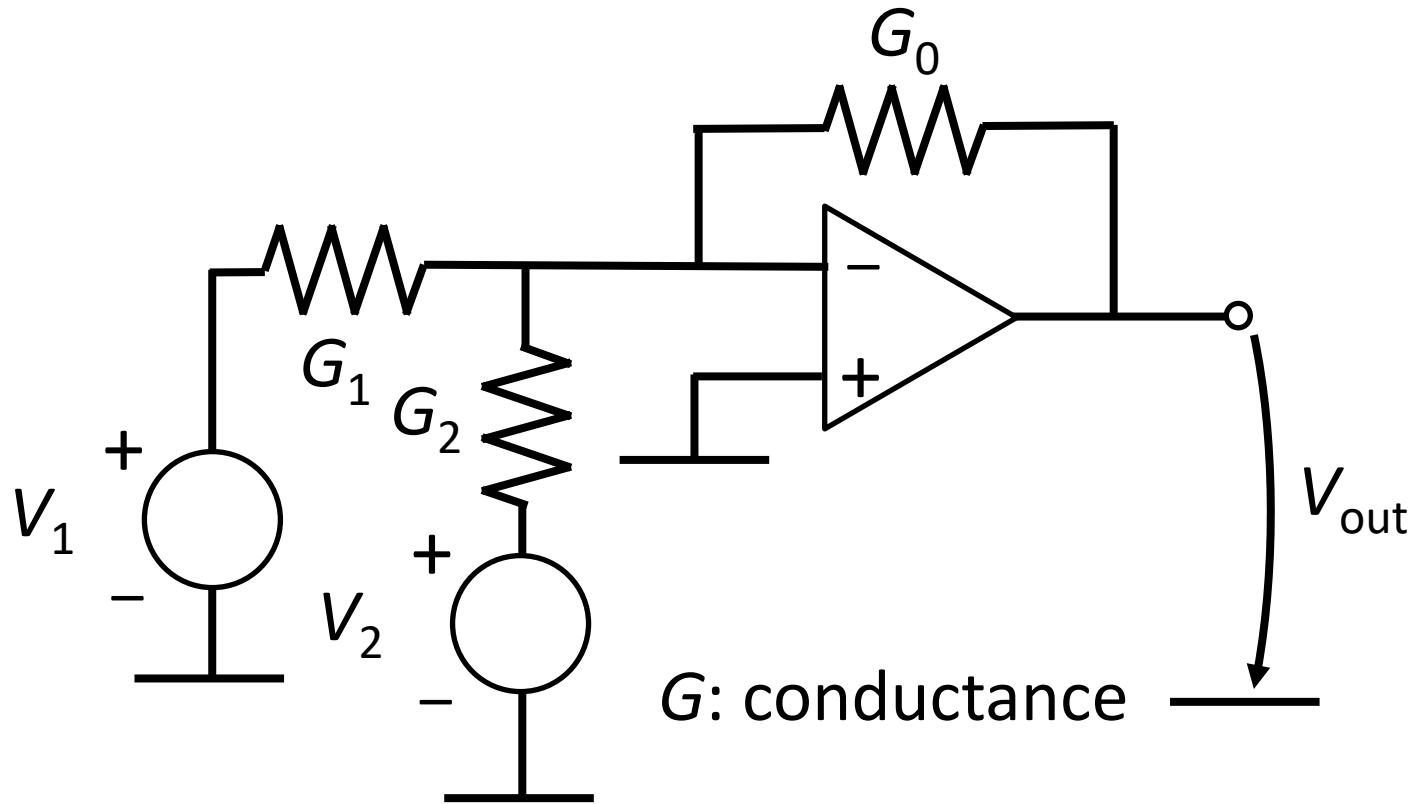
# Quiz 9

- Assume an ideal opamp. Express voltage  $V_{out}$  using  $V_1$  and  $V_2$ . What does this circuit do for  $V_1$  and  $V_2$ ?



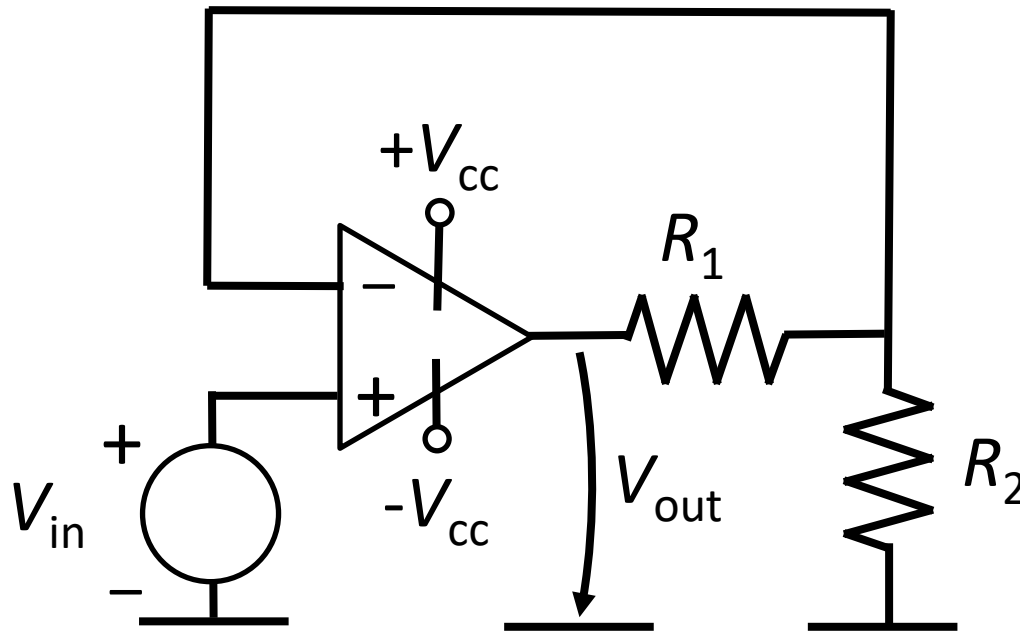
# Quiz 10-1

- Is this a non-inverting or inverting amplifier? Check by expressing  $V_{out}$  using  $V_{in}$ .


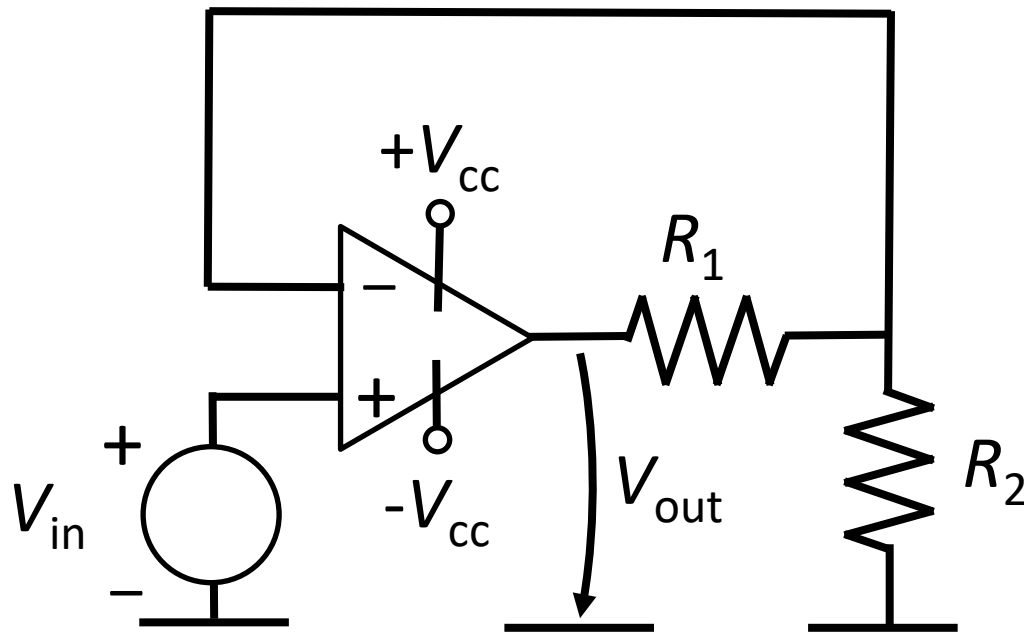
# Quiz 10-2

- Calculate  $V_{out}$ . Is the opamp in linear or saturation mode?



$$V_{in} = 1 \text{ V}$$


$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 1 \text{ k}\Omega$$

$$V_{cc} = 12 \text{ V}$$
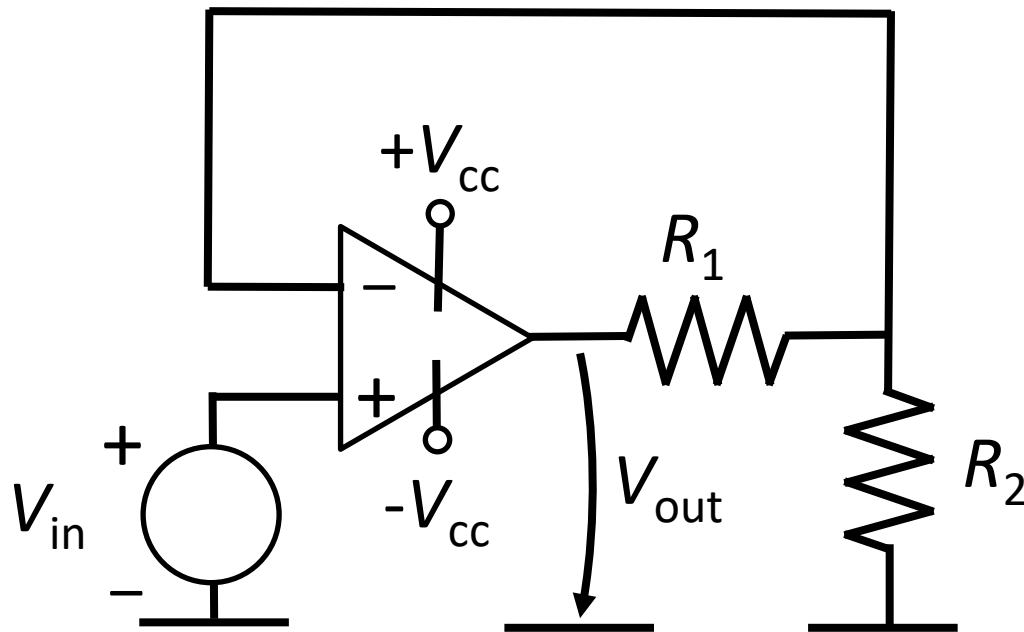
# Quiz 10-3

- Calculate  $V_{out}$ . Is the opamp in linear or saturation mode?



$$V_{in} = -7 \text{ V}$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 1 \text{ k}\Omega$$

$$V_{cc} = 12 \text{ V}$$