

In-class exercise

- Deadline: 18:00 today
- Submission:
<https://mycourses.aalto.fi/course/view.php?id=33521§ion=2>

Derive a matrix equation for node voltages at A and B, i.e., U_A and U_B using the heuristic method.

