



Aalto University  
School of Electrical  
Engineering

# ELEC-C9610 Basics in Electronics

## Lecture 1: Kirchhoff's laws

Anu Lehtovuori and Katsuyuki Haneda




*No electricity without charge.*

- ▶ **Current** is movement of charges. DC current has constant magnitude.
- ▶ A flow of charges means a flow of the energy. When charge flows, it arises **potential** (energy per unit charge).
- ▶ **Voltage** is difference in potential between two points.
- ▶ **Circuit** consists of **branches, where currents travel** and **nodes having potential** between them.

power  $P$  [W], voltage  $U$  [V], current  $I$  [A]

# Passive components


---

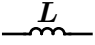graphic symbol	component	property
	resistance	resistance $R$ [ $\Omega$ ]
	condensator	capacitance $C$ [F]
	coil	inductance $L$ [H]



Instead of resistance, we can also use conductance  $G = 1/R$  [S]

# Ohm's law

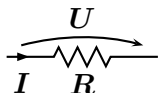

A circuit diagram showing a resistor symbol (a zigzag line) with a current  $I$  flowing through it from left to right, indicated by a horizontal arrow below the resistor. A voltage  $U$  is applied across the resistor, indicated by a curved arrow above it pointing from left to right.

$$U = RI$$

Voltage over the resistor depends linearly on current through the component.

With conductance:

$$I = GU, \quad G = \frac{1}{R}$$



# Open circuit and short circuit

---

Current in capacitance depends on the change of the voltage:

$$i = C \frac{du}{dt}$$

In DC, current is zero and capacitance corresponds to **an open circuit**.

  
 $I = 0$




$R = \infty$

$U = ?$

Voltage over inductance depends on the change of the current:

$$u = L \frac{di}{dt}$$

In DC, voltage is zero and inductance corresponds **a short circuit**.

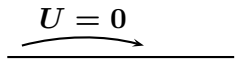  
 $U = 0$


$R = 0$

$I = ?$

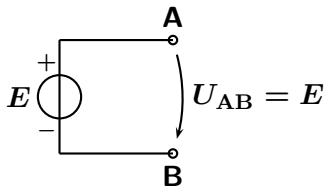
## Ideal sources

---

**Ideal voltage source  $E$**  determines voltage  $U_{AB}$  between nodes (**A** and **B**).



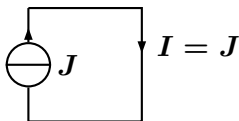**Ideal current source  $J$**  determines current  $I$ . For this reason, current through the current source is always equal the value of the source.



**Power produced in the circuit = power consumed in the circuit**

$$P = UI$$


By substituting Ohm's law, we can write also

$$P = RI^2 = \frac{U^2}{R} = GU^2$$

If power is positive, element consumes power.

# Kirchhoff's current law

---

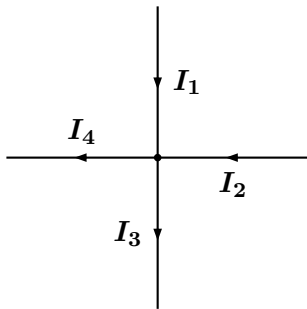


$$I_1 + I_2 = I_3 + I_4$$

The sum of the current coming to the node is same as the sum of the currents going out of the node.



# Kirchhoff's voltage law

---

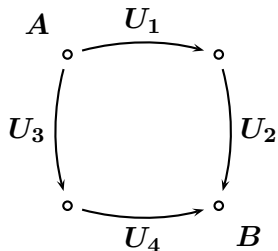

$$U_1 + U_2 = U_3 + U_4$$


Voltage between two points is same via all routes.  
OR Voltage in closed path is zero.

## Important issues

---

Especially, note direction of currents and voltages and signs.

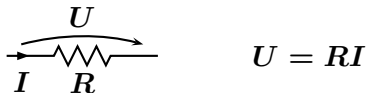**If current and voltage have the same direction  $\implies$  positive sign**




If current and voltage are in opposite direction  $\implies$  negative sign

- ▶ Currents and voltages drawn to the circuit are 'auxiliary variables'. The real currents and voltages in the circuit might be to the opposite direction. - Then you see a negative sign in your answer!
- ▶ Lines can be drawn at several ways, but the circuit doesn't change, if nodes doesn't change.

## Resistors in series


---

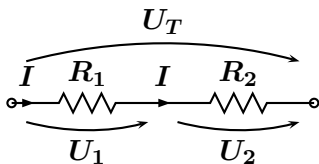

Components are connected one after the other (concatenate) in the same loop. **Same current goes through all components.**

$$R_{\text{tot}} = \sum_{n=1}^N R_n = R_1 + R_2$$

## Resistors in parallel

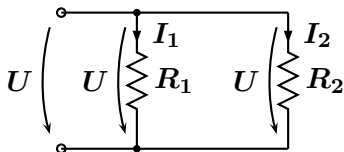

Components are connected parallel between the same nodes. **Same voltage** over all components.



$$G_{\text{tot}} = \sum_{n=1}^N G_n = G_1 + G_2$$
$$\frac{1}{R_{\text{tot}}} = \sum_{n=1}^N \frac{1}{R_n} = \frac{1}{R_1} + \frac{1}{R_2}$$

For two resistors 'product-divided-by-sum-formula':

$$R_{\text{tot}} = \frac{R_1 R_2}{R_1 + R_2}$$

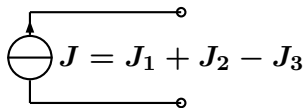
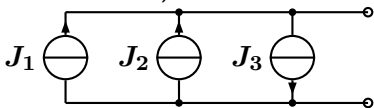
## Sources in series and in parallel

**Current sources in parallel** are added up (taking directions into account)



Component in series with **ideal** current source doesn't affect current!

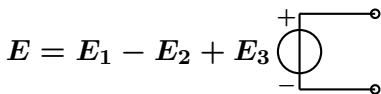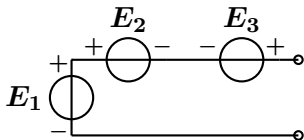**Voltage sources in series** are added up (taking directions into account)



Component in parallel with **ideal** voltage source doesn't affect voltage!