

ELEC-E8413

POWER SYSTEMS

Aalto University

Department of Electrical Engineering

Hannu Jyrki
Jyväskylä

ELEC-E8413 power systems

Lectures

Lecture 1 Network components
Referring, p.u. computation

Lecture 2 p.u. computation
Load flows

Lecture 3 Power stations
Load modeling

Lecture 4 Stability

Lecture 5 Faults

Lecture 6 P and Q control

Lecture 7 Power Quality

Lecture 8 High voltage engineering

Lecture 9 Substation equipment
Transformers

Lecture 10 Lines

Lecture 11 Protection

Lecture 12 Earthing, hazard voltages

Course materials

- **Course books:**
- 7 B. M. Weedy , B. J. Cory , N. Jenkins, J. B. Ekanayake, G. Strbac, "Electric Power Systems" fifth edition, December 26, 2012 , ISBN-10: 047068268X, ISBN-13: 978-0470682685.
- John J. Grainger, William D. Stevenson, Jr., "Power System Analysis, " Singapore, 1994. ISBN-10: 0070612935, ISBN-13: 978-0070612938.
- Harrison, John Anthony, "The essence of electric power systems" Prentice Hall, 1996, ISBN 0133975142, 9780133975147
- Kirtley, James, "Electrical Power Principles: Sources, Conversion, Distribution & Use", Wiley, 2010. ISBN: 9780470686362. (Available at Aalto ebrary)
<http://site.ebrary.com/lib/aalto/docDetail.action?docID=10411610>
- **Books in Finnish: Liisa Haarla & Jarmo Elovaara, Sähköverkot 1&2, Otatieto**
- **Slides and exercise materials available in MyCourses**

Transmission and distribution systems

Power station

- generator (10,5 kV, 20 kV)
- generator transformer (20/400 kV)

Transmission system

- transformers (400/220 kV)
- 400, 220 (ja 110) kV lines
- switching station (220 kV)
- transformer station (400/220 kV)

Subtransmission system


- 110 kV lines
- primary substation (110/20 kV)

Medium voltage distribution

- 20 kV lines

Low voltage distribution

- 0,4 kV lines and customers

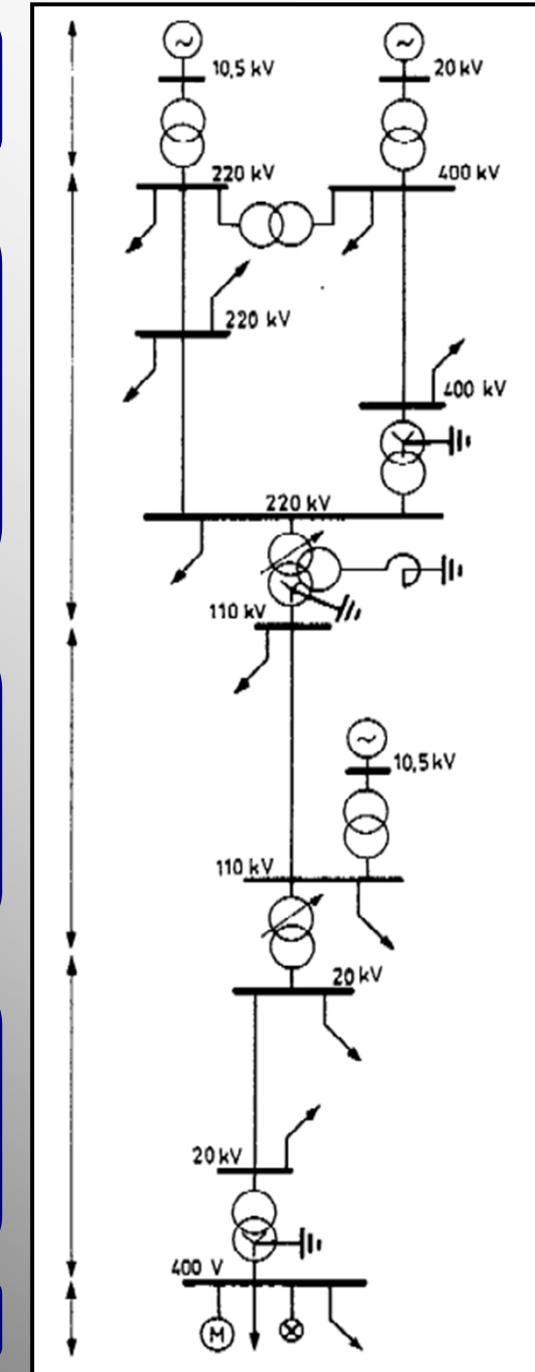


Nordic transmission system

Nordel




Alternating current & phasors

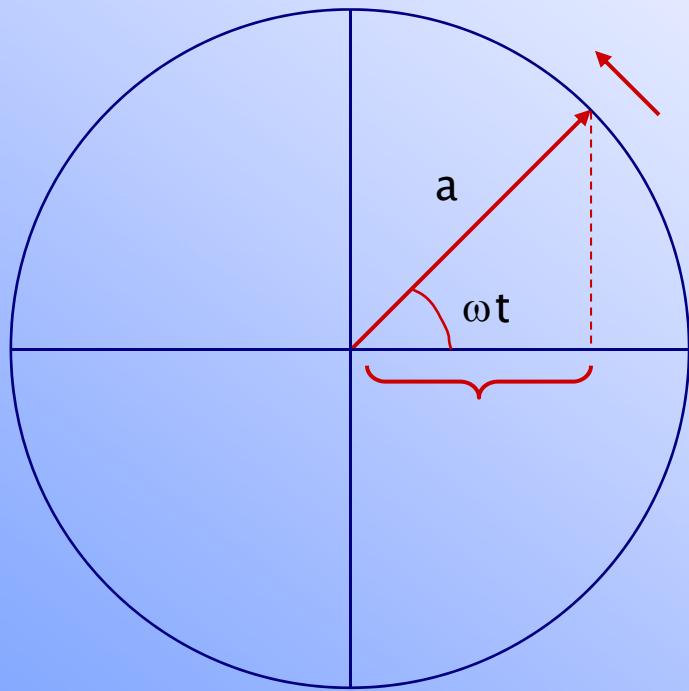


$$u(t) = a \cos \omega t$$

$$\omega = \text{angular freq} = 2\pi f$$
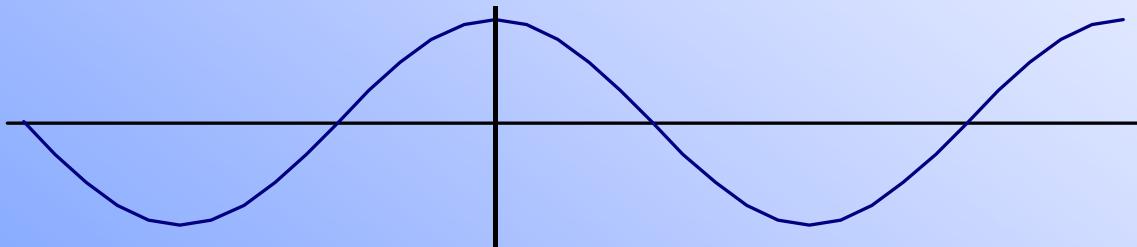
$$\text{Rms value } U = \frac{a}{\sqrt{2}}$$




3-phase system

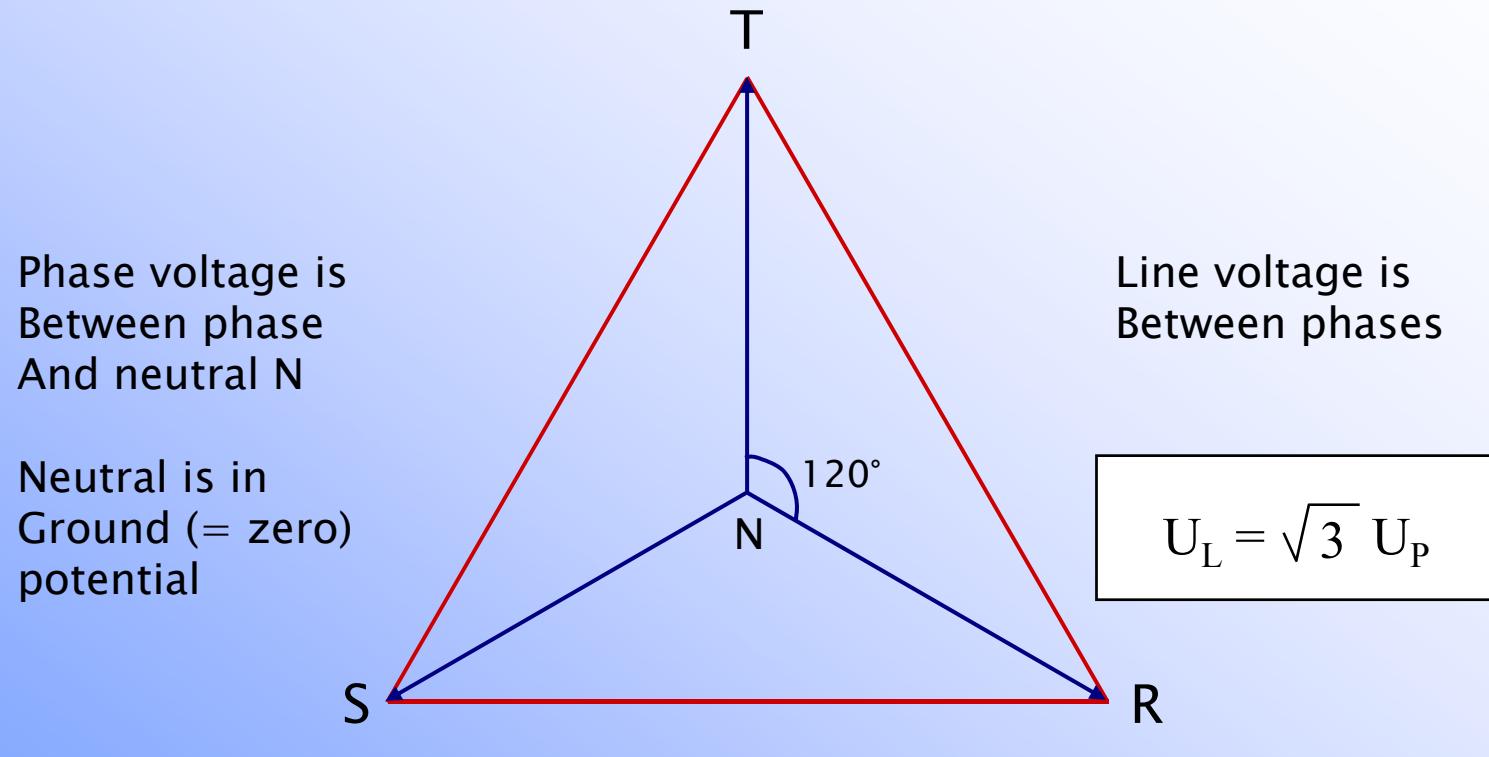

Phase voltage U_P U_R U_S U_T

Line voltage U_L U_{RS} U_{ST} U_{TR}

Single line diagram of a 3-ph system

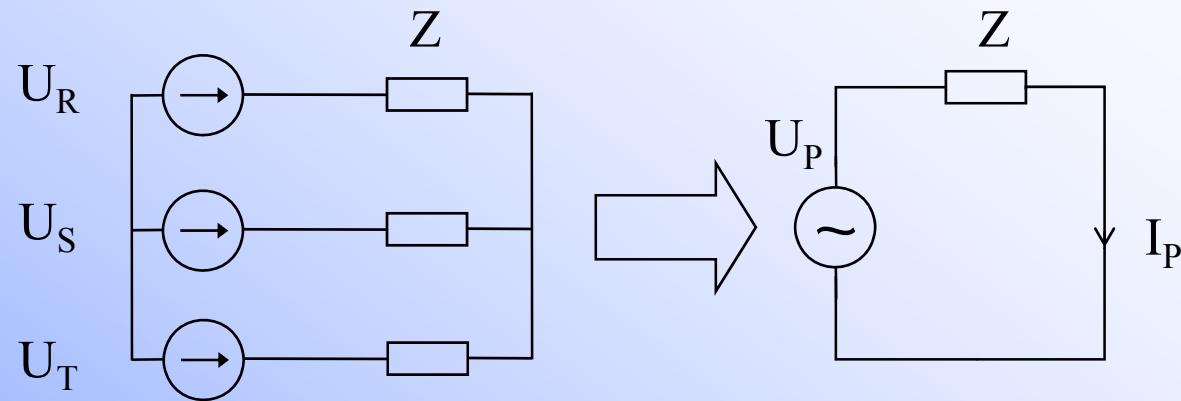


In a three phase system, phase quantities U_p and I_p cancel when summed

Hence the voltages and currents in neutrals behind the load and source are zero

A single line diagram of a three phase system is made by connecting neutrals

Hence only one phase is analysed, and the other two exhibit similar behavior

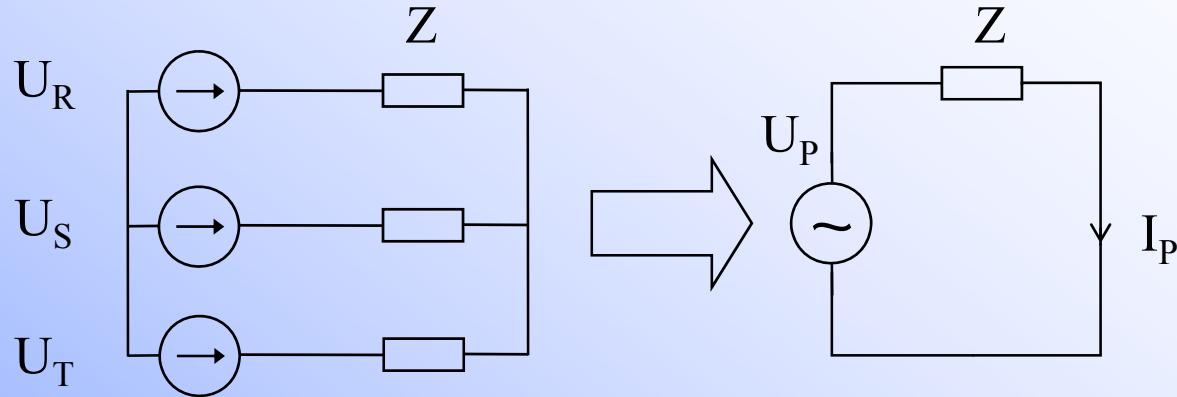Powers & single line diagram of a 3-ph system



$$\text{Power: } S = 3 U_P I_P = \sqrt{3} U_L I_P$$


Impedance Z :

$$Z = \frac{U_P}{I_P} = U_P \cdot \frac{3 U_P}{S}$$


$$= \frac{3 U_P^2}{S} = \frac{U_L^2}{S}$$

Powers in a 3-ph system
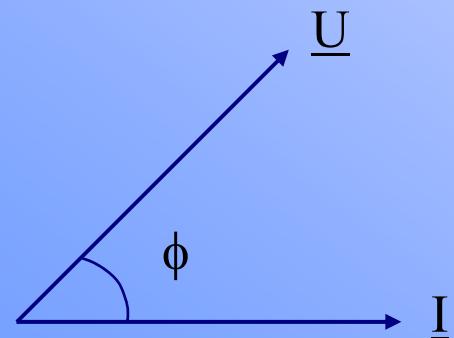
$$\begin{aligned}
 S &= 3 U_p I = \sqrt{3} U_L I \\
 P &= S \cos \phi \\
 Q &= S \sin \phi \\
 S &= \sqrt{P^2 + Q^2} \\
 S &= P + jQ
 \end{aligned}$$



$P/S = \cos\phi$ is power factor

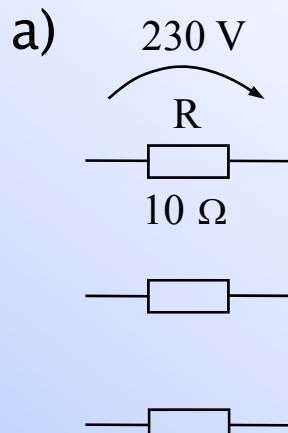


Resistance R

$$U = RI \Rightarrow I = 23 \text{ A}$$


\underline{U} $\phi = 0^\circ$

\underline{I}
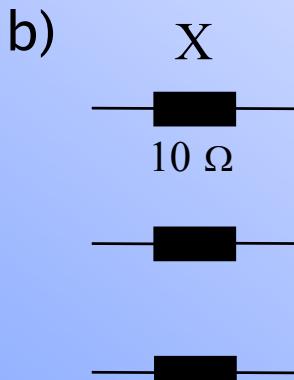
$$\begin{aligned}
 P &= 3U_p I \cos\phi \\
 &= 3 \cdot 230 \cdot \cos 0^\circ \cdot 23 \text{ W} = 15,9 \text{ kW} \\
 Q &= 3U_p I \sin\phi = 0
 \end{aligned}$$




Reactance $X = j\omega L$
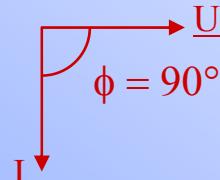
$$I = 23 \text{ A} \quad (\underline{U} = \underline{XI})$$


$$\begin{aligned}
 P &= 3U_p I \cos 90^\circ = 0 \\
 Q &= 3U_p I \sin 90^\circ = 3 * 230 * 23 \text{ var} = 15,9 \text{ kVAr}
 \end{aligned}$$

Powers in a 3-ph system (continued)


c)

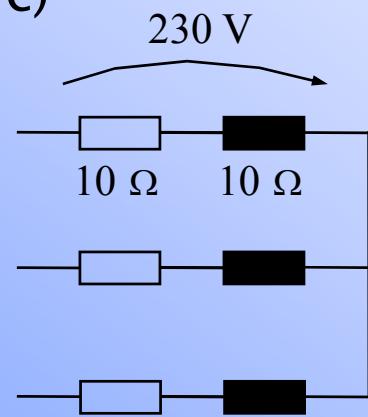

$$\underline{Z} = R + jX = 10 + j10 = 14,1 \angle 45^\circ$$

$$\underline{U} = \underline{ZI} \Rightarrow I = \frac{\underline{U}}{\underline{Z}} = \frac{230 \angle 0^\circ}{14,1 \angle 45^\circ}$$

$$= 16,26 \angle -45^\circ A$$

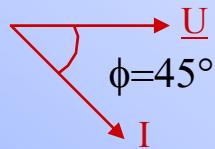

$$P = 3 U_p I \cos \phi = 3 \cdot 230 \cdot 16,26 \cdot \cos 45^\circ = 7,9 \text{ kW}$$

$$Q = 3 U_p I \sin \phi = 3 \cdot 230 \cdot 16,26 \cdot \sin 45^\circ = 7,9 \text{ kVAr}$$

$$S = 3 U_p I = 3 \cdot 230 \cdot 16,26 = 11,2 \text{ kVA}$$

$$S = \sqrt{P^2 + Q^2} = 11,2 \text{ kVA}$$

Another way

$$S = 3 U_p I_p^* = 3 U_p \angle 0^\circ \cdot I_p \angle 45^\circ = 3 U_p I_p \angle 45^\circ$$

$$= 3 \cdot 230 \cdot 16,26 \angle 45^\circ \text{ VA} = 11,2 \angle 45^\circ \text{ kVA}$$

$$= 7,9 + j7,9 \text{ kVA}$$

$$\begin{cases} \underline{U} = U \angle 0^\circ \\ \underline{I} = I \angle -\phi \\ \underline{I}^* = I \angle \phi \end{cases}$$

Computation usually using line voltages


$$\Rightarrow S = 3 U_p I_P^*$$

$$S = \sqrt{3} U_L I_P^*$$


Reactance (ind)




$$\underline{X} = j\omega L$$

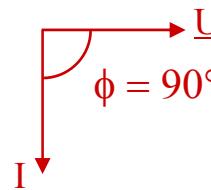

Capacitance

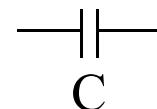
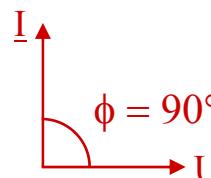
$$\underline{X} = \frac{1}{j\omega C} = -j \frac{1}{\omega C}$$



EXAMPLE: RESISTIVE-INDUCTIVE LOAD

In a 0.4 kV three phase system there is a load, which takes 10 A with power factor $\cos\phi = 0.9$. Calculate real power P, reactive power Q and apparent power S.

$$U_L=400 \text{ V} \Leftrightarrow U_P = \frac{400}{\sqrt{3}} \text{ V} = 230 \text{ V}$$

Power per phase: $P=U_P I_P \cos\phi = 230 * 10 * 0.9 \text{ W} = 2070 \text{ W} = 2.07 \text{ kW}$

Three phase power: $P = 3 U_P I_P \cos\phi = 6.2 \text{ kW}$

Using line voltages

$$P = \sqrt{3} U_L I_P \cos\phi = \sqrt{3} * 400 * 10 * 0.9 \text{ W} = 6.2 \text{ kW}$$

Three phase reactive power: $P = 3 U_P I_P \sin\phi = 3 \text{ kvar}$ ($\phi = 26 \text{ deg}$)

Using line voltages

$$Q = \sqrt{3} U_L I_P \sin\phi = \sqrt{3} * 400 * 10 * 0.44 \text{ var} = 3 \text{ kvar}$$

Example (continued)

In a 0.4 kV three phase system there is a load, which takes 10 A with power factor $\cos\phi = 0.9$. Calculate real power P, reactive power Q and apparent power S.

$$P = \sqrt{3} U_L I_P \cos \phi = \sqrt{3} * 400 * 10 * 0.9 \text{ W} = 6.2 \text{ kW}$$

$$Q = \sqrt{3} U_L I_P \sin \phi = \sqrt{3} * 400 * 10 * 0.44 \text{ var} = 3 \text{ kvar}$$

Apparent power S:

$$S = P + jQ = 6.2 + j3 \text{ kVA}$$

$$S = \sqrt{P^2 + Q^2} = 6.9 \text{ kVA}$$

$$S = \sqrt{3} U_L I_P = \sqrt{3} * 400 * 10 \text{ VA} = 6.9 \text{ kVA}$$


Example (continued)

In a 0.4 kV three phase system there is a load, which takes 10 A with power factor $\cos\phi = 0.9$. Calculate real power P, reactive power Q and apparent power S.

$$P = \sqrt{3} U_L I_P \cos \phi = \sqrt{3} * 400 * 10 * 0.9 \text{ W} = 6.2 \text{ kW}$$

$$Q = \sqrt{3} U_L I_P \sin \phi = \sqrt{3} * 400 * 10 * 0.44 \text{ var} = 3 \text{ kvar}$$

Apparent power S:

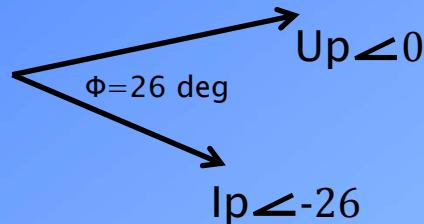



$$S = 3 U_P I_P^* = 3 * 230 < 0^\circ * 10 < 26^\circ \text{ VA} = 6.9 < 26^\circ \text{ kVA}$$

$$S = \sqrt{3} U_L I_P^* = \sqrt{3} * 400 < 0^\circ * 10 < 26^\circ \text{ VA} = 6.9 < 26^\circ \text{ kVA}$$

$$S = 6.9 < 26^\circ \text{ kVA} = 6.9 \cos 26^\circ \text{ kW} + j 6.9 \sin 26^\circ \text{ kvar} = 6.2 \text{ kW} + j 3 \text{ kvar}$$

DELTA AND STAR CONNECTIONS

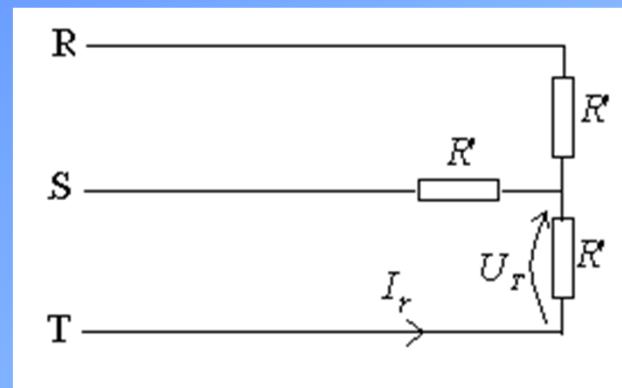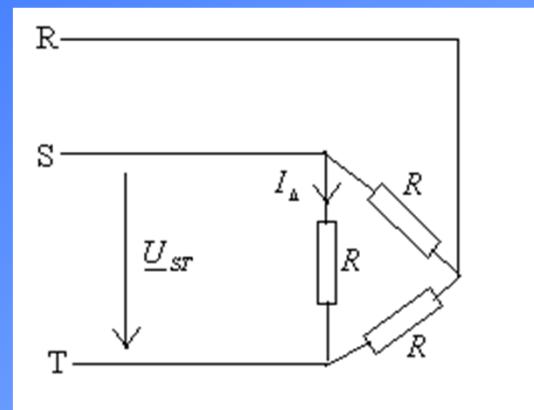In 3-phase system loads and equipment (like generator or transformer windings) can be connected either in delta (between phases) or star (between phase and neutral)



Power in delta and star connection

Let consider a set of three $10\ \Omega$ resistors connected in star or delta in low voltage network.

In star connection, the voltage of resistors is $230\text{ V} \Leftrightarrow I = U/R = 23\text{ A}$


Three phase power $P = 3UI = 3*230*23\text{ W} = 16\text{ kW}$

In delta connection, the voltage of resistors is $400\text{ V} \Leftrightarrow I = U/R = 40\text{ A}$

Three phase power $P = 3UI = 3*400*40\text{ W} = 48\text{ kW}$

In delta-connection both the current and the voltage is $\sqrt{3}$ - fold, and hence the power will be 3-fold compared to star connection.

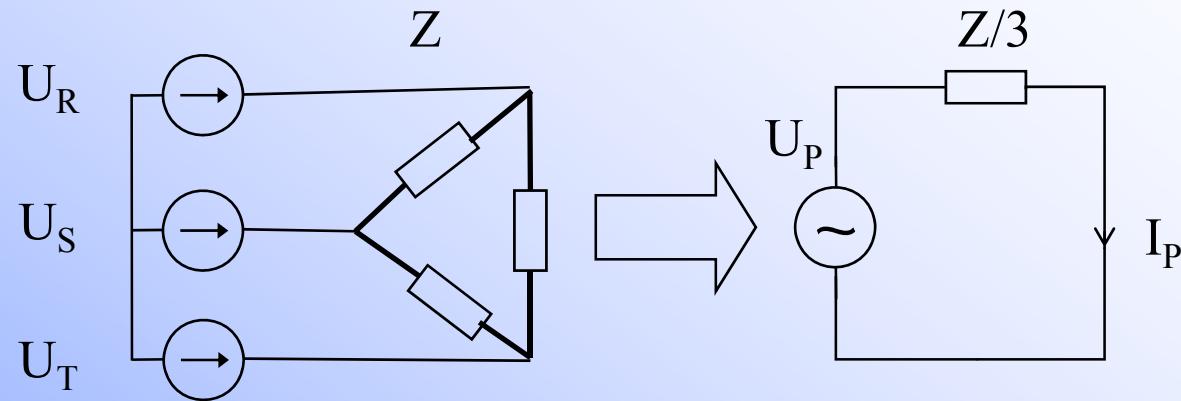Delta–Star transformation in a 3-ph system





In three phase systems, the analytical solutions are made using single line diagrams where impedances are between phase and neutral, i.e. in star

Hence, the delta connection must be transformed to star.

This is done by dividing the impedances by three.

(proof: the powers are the same in both cases)

Lines

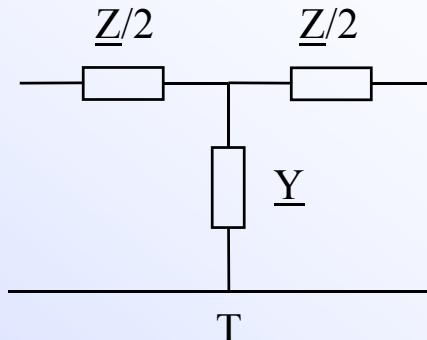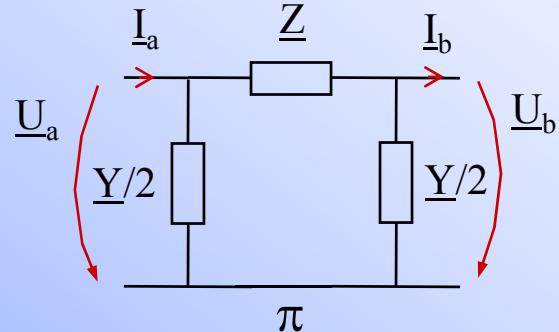

$$\underline{Z} = (r + j\omega l) s$$

$$\underline{Y} = (g + j\omega c) s$$

s = length
 r = resistance / s
 l = inductance / s
 g = conductance / s
 c = capacitance / s


Long lines

$$\begin{bmatrix} \underline{U}_a \\ \underline{I}_a \end{bmatrix} = \begin{bmatrix} \cos \underline{\beta} s & j\underline{Z}_c \sin \underline{\beta} s \\ j\frac{1}{\underline{Z}_c} \sin \underline{\beta} s & \cos \underline{\beta} s \end{bmatrix} \begin{bmatrix} \underline{U}_b \\ \underline{I}_b \end{bmatrix}$$

$$\underline{\beta} = \sqrt{(r + j\omega l) \cdot (g + j\omega c)}$$


$$\underline{Z}_c = \sqrt{(r + j\omega l)/(g + j\omega c)}$$

Generators
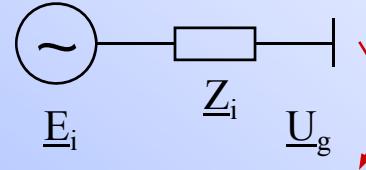
$$\underline{Z}_i = R + jX_d$$

$$X_d = x_d \frac{U_N^2}{S_N}$$
$$x_d > x_d' > x_d''$$



synchronous, transient, subtransient reactance

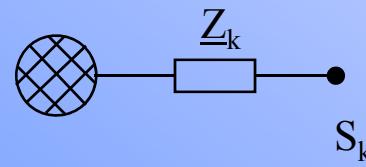Feeding transmission grid



$$S_k = \text{short circuit power MVA}$$

$$\underline{Z}_k \approx jX_k$$
$$X_k = \frac{U^2}{S_k}$$

$$\begin{cases} U_N = \text{rated voltage (kV)} \\ S_N = \text{rated power (MVA)} \\ x_d = \text{p.u. synchronous reactance} \end{cases}$$

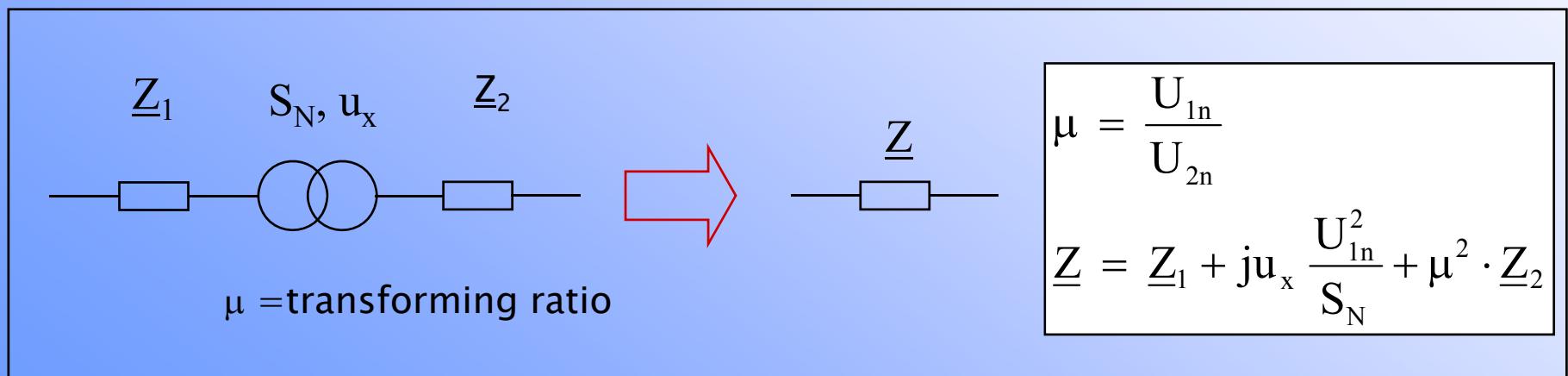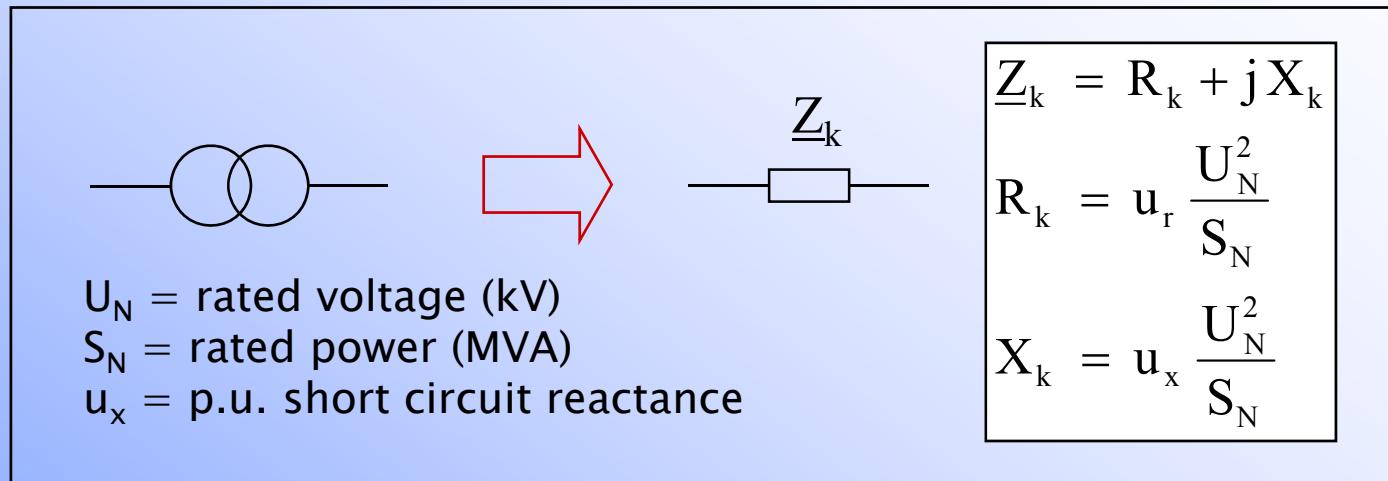Transformer

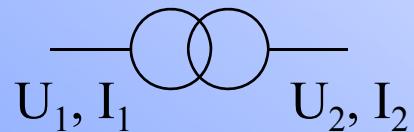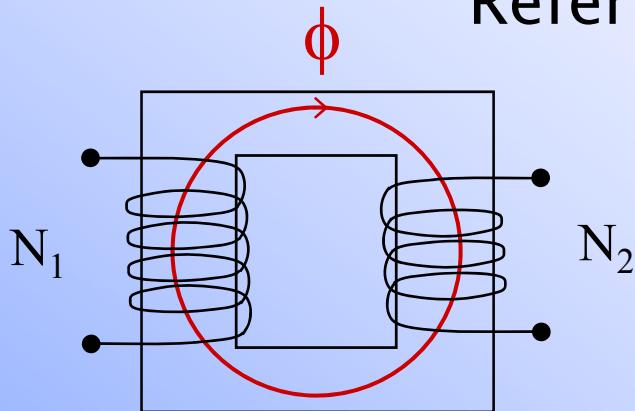

Referring over a transformer



Voltage over a turn
is constant


$$\frac{U_1}{U_2} = \frac{N_1}{N_2}$$

Power is constant

$$S = \sqrt{3} U_2 I_2 = \sqrt{3} U_1 I_1$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{U_2}{U_1} = \frac{N_2}{N_1}$$

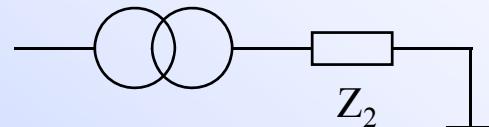Secondary impedance Z_2 referred to primary ?





$$\text{in secondary } Z_2 = \frac{U_2}{I_2}$$

$$\text{in primary } Z'_2 = \frac{U_1}{I_1} = \frac{U_2 \cdot \frac{N_1}{N_2}}{I_2 \cdot \frac{N_2}{N_1}} = \left(\frac{N_1}{N_2} \right)^2 \cdot Z_2$$

$$\text{usually we write } \frac{N_1}{N_2} = \frac{U_{1n}}{U_{2n}}$$

Referring over a transformer

An example

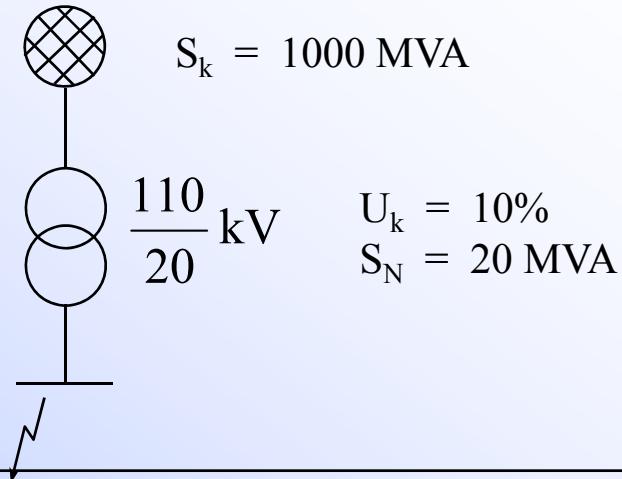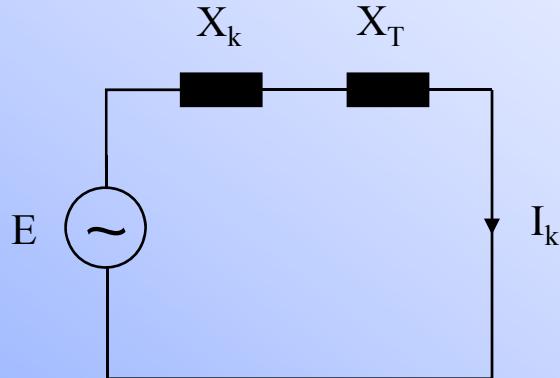

$$X_k = \frac{U_1^2}{S_k} = \frac{110^2}{1000} = 12,1 \Omega \quad (110 \text{ kV})$$

$$X_T = u_k \frac{U_2^2}{S_N} = 0,1 \cdot \frac{20^2}{20} = 2 \Omega \quad (20 \text{ kV})$$

$$20 \text{ kV level} \quad E = \frac{U_2}{\sqrt{3}}$$

$$I_{k_2} = \frac{U_2}{\sqrt{3}(X_k' + X_T)} = \frac{20 \text{ kV}}{\sqrt{3}\left(\left(\frac{20}{110}\right)^2 \cdot 12,1 + 2\right) \Omega} = \underline{\underline{4,81 \text{ kA}}}$$

$$110 \text{ kV level} \quad E = \frac{U_1}{\sqrt{3}}$$

$$I_{k_1} = \frac{U_1}{\sqrt{3}(X_k + X_T')} = \frac{110 \text{ kV}}{\sqrt{3}(12,1 + \left(\frac{110}{20}\right)^2 \cdot 2) \Omega} = \underline{\underline{0,875 \text{ kA}}}$$

check :

$$I_{k_1} = \frac{U_{2n}}{U_{1n}} I_{k_2} = \frac{20}{110} \cdot 4,81 \text{ kA} = 0,875 \text{ kA}$$

Referring and p.u. values

1. Referring over a transformer (from U_1 to U_2)

$$U'_1 = \left(U_{2n} / U_{1n} \right) \cdot U_1$$

$$I'_1 = \left(U_{1n} / U_{2n} \right) \cdot I_1$$

$$Z'_1 = \left(U_{2n} / U_{1n} \right)^2 \cdot Z_1$$

Referring is easy when only two voltage levels

2. In case of several voltage levels p.u. computation

Select for the base values some base power S_b and voltage of one selected voltage level U_b

⇒ Other base voltages by transforming ratios:

$$U_{2b} = \left(U_{2n} / U_{1n} \right) \cdot U_{1b}$$

⇒ Current base value by base power and base voltage:

$$I_b = S_b / \sqrt{3} U_b$$

⇒ Impedance base value by base power and base voltage:

$$Z_b = U_b^2 / S_b$$

3-ph power as a p.u. value using the equation $s = ui^*$
Other computation as with single line diagram

Calculations using p.u. values

The actual $U(\text{kV})$, $I(\text{A})$, $Z(\Omega)$, $S(\text{MVA})$, $P(\text{MW})$, $Q(\text{Mvar})$ values are first scaled by corresponding base values of the voltage level in question

$$u = U/U_b \quad i = I / I_b \quad z = Z/Z_b \quad s = S / S_b$$

As the result we have per unit (p.u.) values. Now all the different voltage Levels have been transformed to the same general domain and no any Referring over transformers is needed any more.

The calculations are done with single line diagram. For 3ph powers $\underline{s} = \underline{ui}^*$

Once the calculations are done, we have the results in the form of Dimensionless p.u. values.

Finally the results are transformed back to actual physical values by Multiplying the p.u. values by the base values of the concerned voltage level.

$$U = uU_b \quad I = iI_b \quad Z = zZ_b \quad S = sS_b$$