



Aalto-yliopisto
Teknillinen korkeakoulu

Exercise Session 2

Power systems

Question 1


- A 220-kV overhead line has the following properties:
 - $s=200$ km
 - $r=0.07 \Omega/\text{km}$
 - $x=0.32 \Omega/\text{km}$
 - $b=3.6 \mu\text{S}/\text{km}$

Define the parameters for medium-length line with the

- a) Π -model
- b) T-model

and calculate the open circuit voltage at the end of the line if the voltage at the beginning is 220 kV.

Question 2

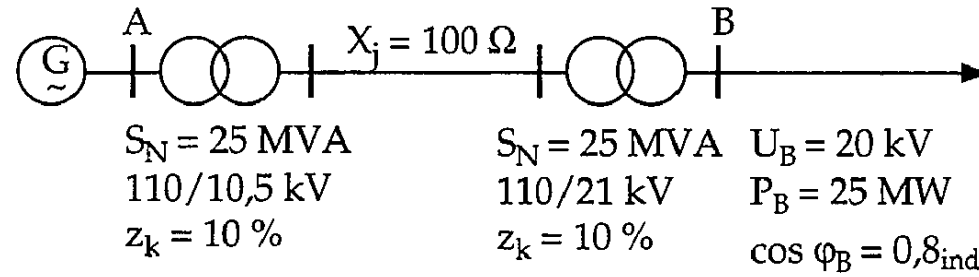

- Calculate per-unit values for all the parameters in the picture above. Use base values: $S_b = 50 \text{ MVA}$ and $U_b = 110 \text{ kV}$

Question 3

- Based on the results obtained from Question 2, calculate the voltage in busbar A (per-unit value and in volts).

Question 4

A 50-Hz, 50-MVA transformer with a 132-kV primary and a 33-kV secondary has a reactance of 0.1pu per phase. What is the reactance in ohms per phase:

- (a) referred to the primary;
- (b) referred to the secondary.