



Aalto-yliopisto
Teknillinen korkeakoulu


Exercise Session 1

Power systems


Question 1

Show that the ratio of phase-to-phase-voltage and phase-to-earth-voltage is $\sqrt{3}$

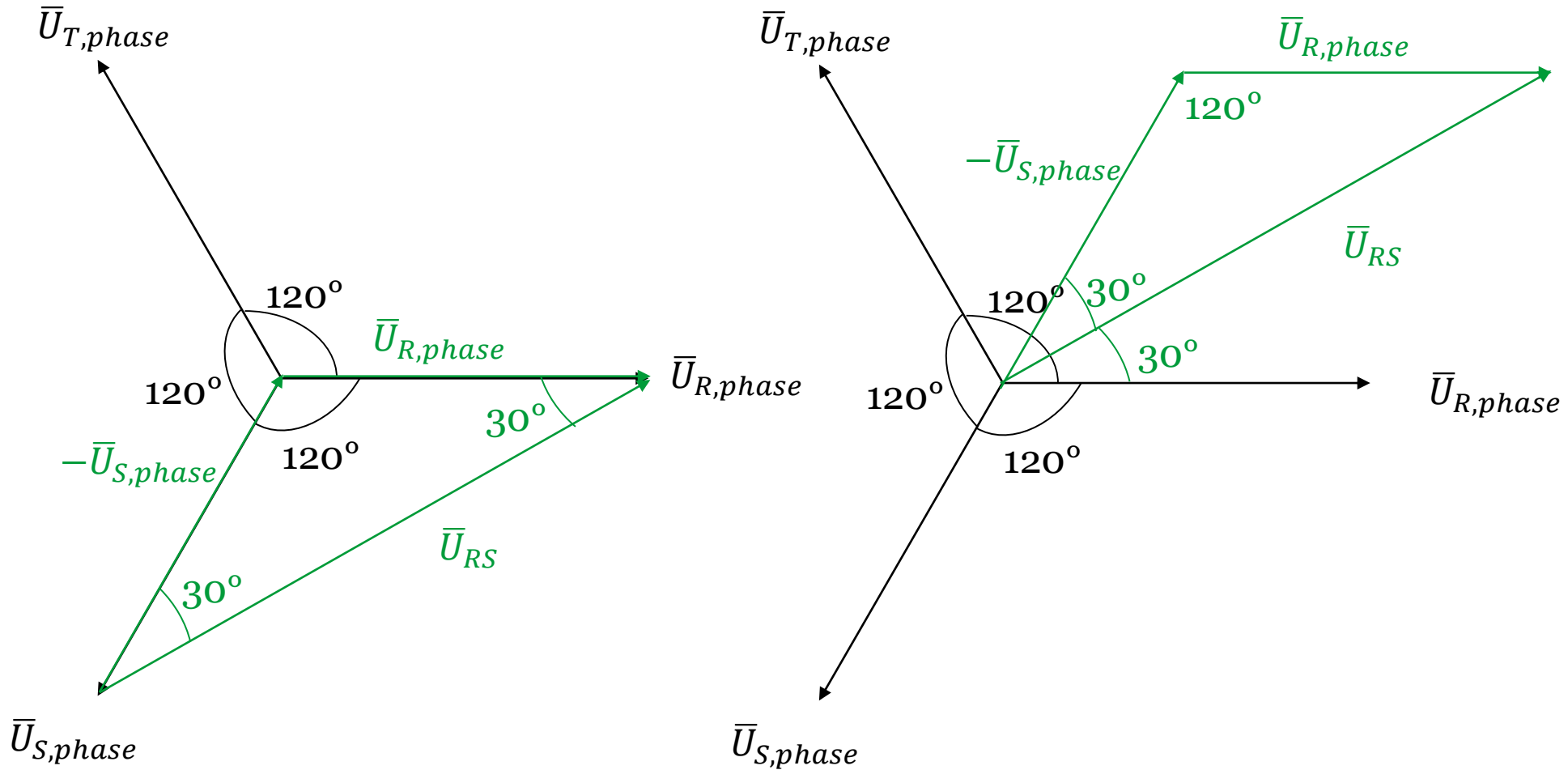Question 1 Show that the ratio of phase-to-phase-voltage and phase-to-earth-voltage is $\sqrt{3}$



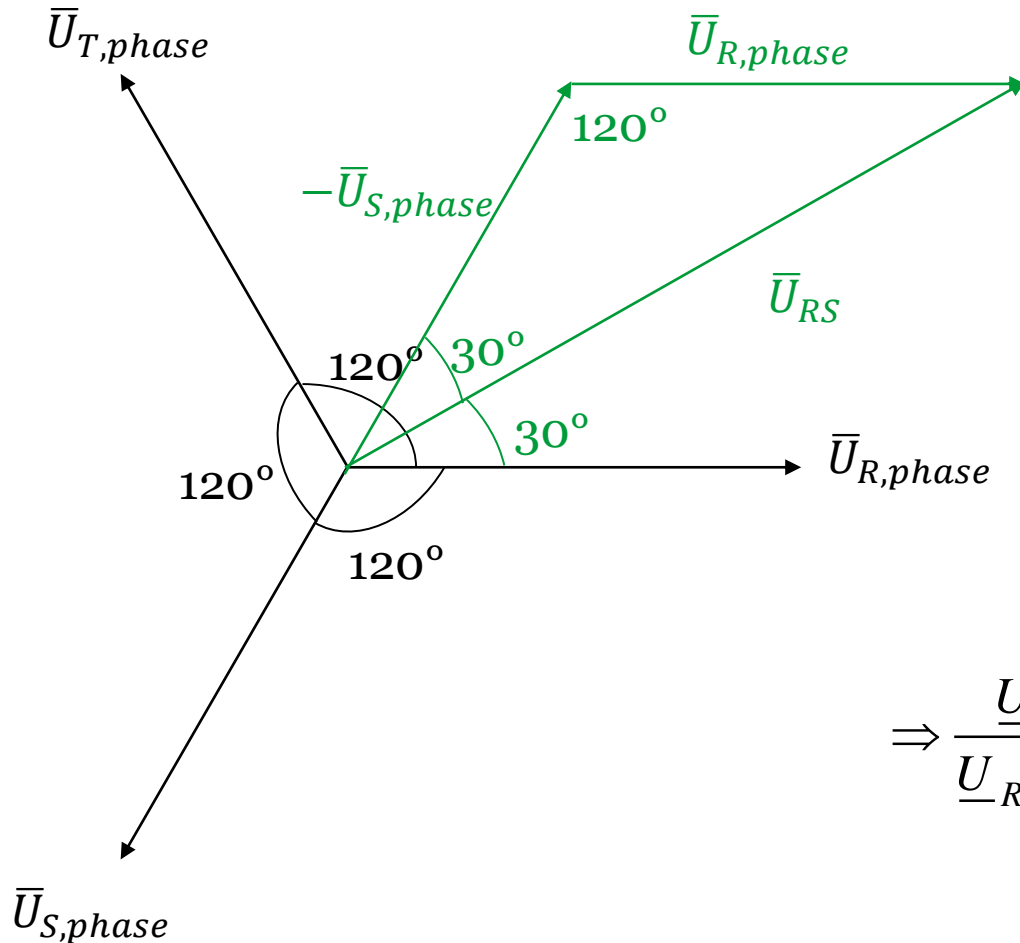Question 1 Show that the ratio of phase-to-phase-voltage and phase-to-earth-voltage is $\sqrt{3}$



$$\underline{U}_{RS,phase} = \underline{U}_{R,phase} - \underline{U}_{S,phase}$$

by Sine Rule:

$$\frac{\underline{U}_{RS,phase}}{\sin 120^\circ} = \frac{\underline{U}_{R,phase}}{\sin 30^\circ}$$



$$\Rightarrow \frac{\underline{U}_{RS}}{\underline{U}_{R,phase}} = \frac{\sin 120^\circ}{\sin 30^\circ}$$

$$\Rightarrow \frac{\underline{U}}{\underline{U}_{phase}} = \frac{\frac{\sqrt{3}}{2}}{\frac{1}{2}} = \underline{\underline{\sqrt{3}}}$$

Question 2

Derive the equation for delta-star transformation.

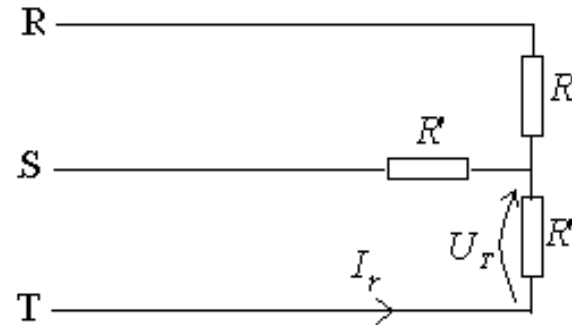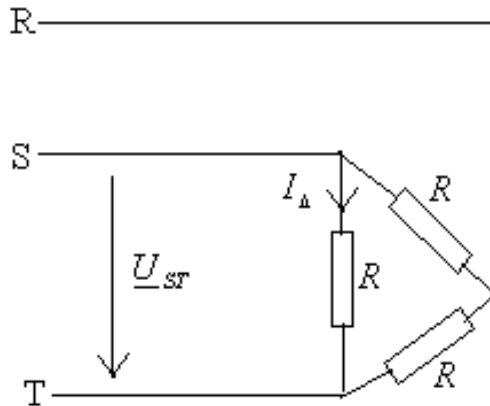Question 2 Derive the equation for delta-star transformation



The power lost to resistance must remain unchanged

$$P_{\Delta} = 3UI_{\Delta} = 3U \frac{U}{R} = 3 \frac{U^2}{R} \quad P_{\gamma} = 3U_{phase}I_{\gamma} = 3U_{phase} \frac{U_{phase}}{R'} = 3 \frac{U_{phase}^2}{R'}$$

$$P_{\Delta} = P_{\gamma} \Leftrightarrow 3 \frac{U^2}{R} = 3 \frac{U_{phase}^2}{R'} \Leftrightarrow \frac{U^2}{R} = \left(\frac{U}{\sqrt{3}} \right)^2 \frac{1}{R'}$$

$$\Leftrightarrow R' = \frac{R}{3}$$

Question 3

A delta-connected three-phase load of $(80+j60) \Omega$ per phase is connected to a 440-V three-phase supply. Calculate:

- a) the current in the load component
- b) the current in the phase of power line
- c) the total real power consumed (active power).

Question 3

a) Current in the load component

In delta connected load, the voltage across the load component is line voltage, i.e. phase-to-phase voltage:


$$\underline{Z}_{\Delta} = 80 + j60 = 100 \angle 36,87^{\circ}$$

$$U = 440V$$

And the current


flowing through the load is

$$\bar{I}_{\text{load}} = \bar{I}_{\Delta} = \frac{\bar{U}}{\underline{Z}_{\Delta}} = \frac{440 \angle 0^{\circ} V}{100 \angle 36.87^{\circ} \Omega} = 4.4 \angle -36.87^{\circ} A$$

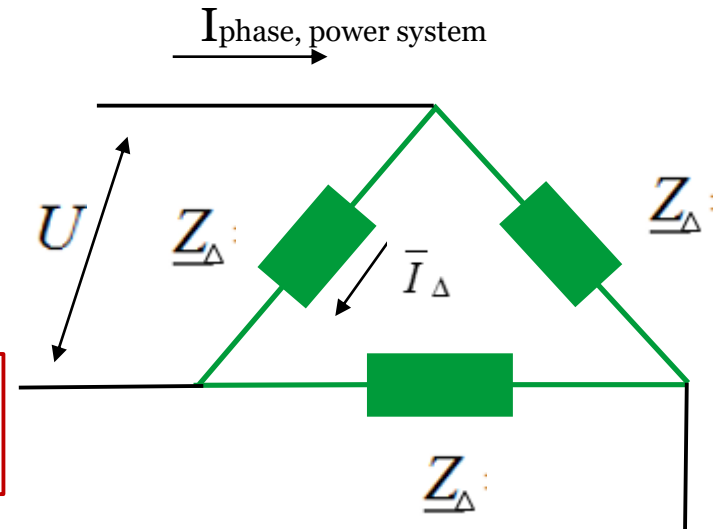

Question 3

b) Current

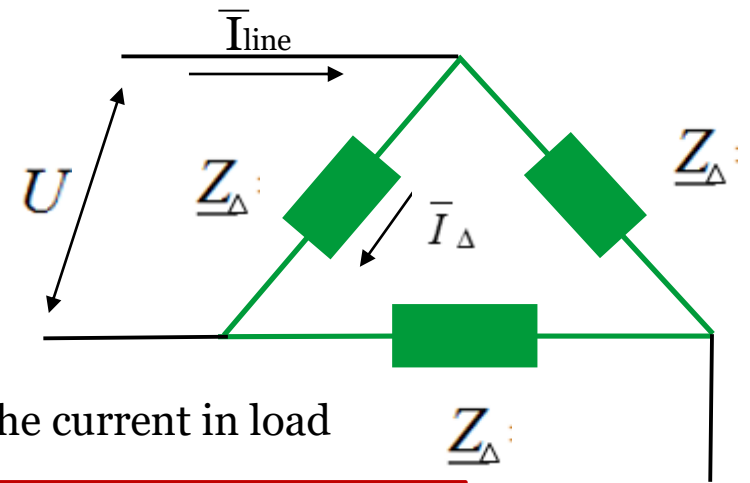


For Δ -connected load, current in power line is $\sqrt{3}$ times the current in load

$$\bar{I}_{\text{power line}} = \sqrt{3} * \bar{I}_{\Delta} = \sqrt{3} * 4.4 \angle -36.87^{\circ} \text{ A} = 7.62 \angle -36.87^{\circ} \text{ A}$$

Option 2) Solution using delta-star-transformation

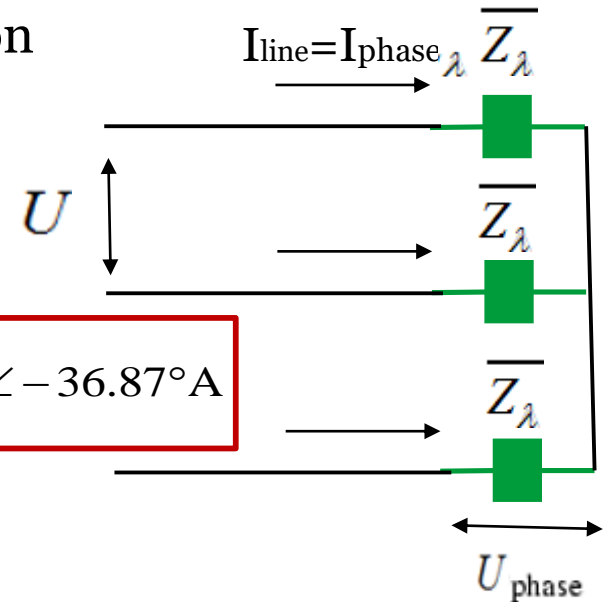
$$\bar{Z}_{\lambda} = \frac{\bar{Z}_{\Delta}}{3} = \left(\frac{80}{3} + j \frac{60}{3} \right) \Omega = 33.33 \angle 36.87^{\circ} \Omega$$



$$\bar{I}_{\text{power line}} = \frac{U_{\text{phase}}}{\bar{Z}_{\lambda}} = \frac{U_{\text{line}}}{\sqrt{3} * \bar{Z}_{\lambda}} = \frac{440 \text{ V}}{\sqrt{3} * 33.33 \angle 36.87^{\circ} \Omega} = 7.62 \angle -36.87^{\circ} \text{ A}$$


Question 3

c) Active power

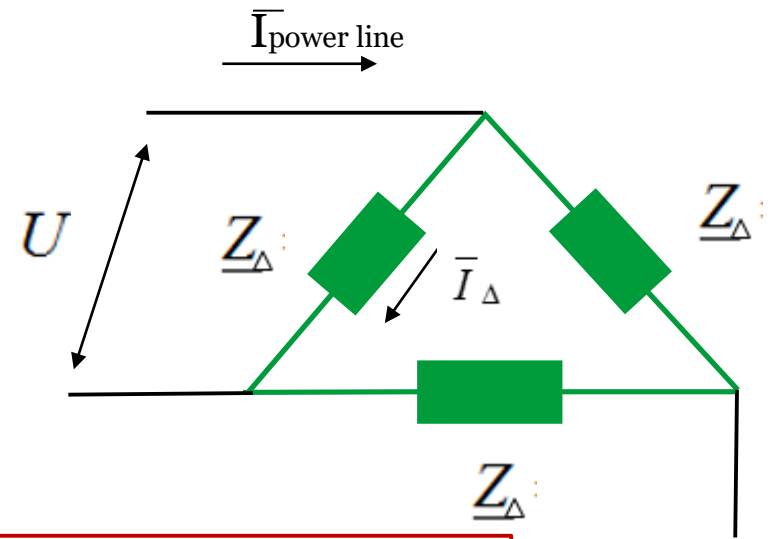

$$P_{\Delta} = 3 * U_{ph-ph} * I_{\Delta} \cos \varphi = 3 * 440V * 4.4 * \cos(36.87^{\circ}) = 4646W = 4.6kW$$
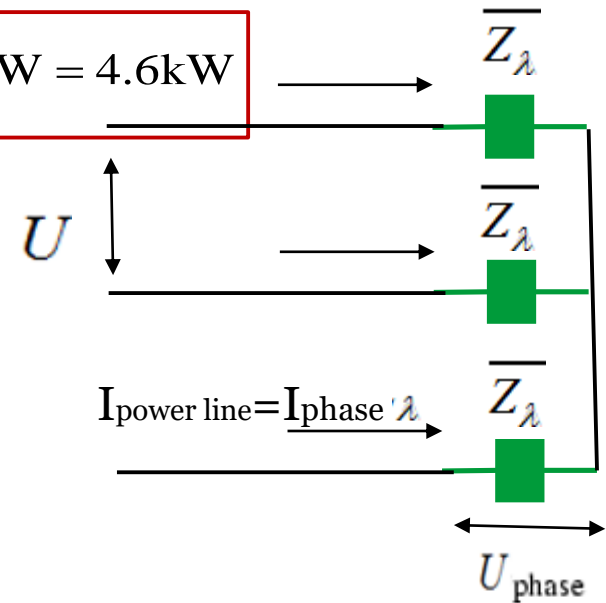
$$P_{\lambda} = 3 * U_{phase} I_{power\ line} \cos \varphi = 3 * \frac{440V}{\sqrt{3}} * 7.62 \cos(36.87^{\circ}) = 4645W = 4.6kW$$



Triple check...

$$\begin{cases} S_{\lambda} = 3U_{phase} \cdot I_{line}^* = 3 \cdot \frac{440V}{\sqrt{3}} \cdot 7,62 / -36,87^{\circ} = 5807,2 / 36,87^{\circ} \\ S_{\Delta} = 3U I_{\Delta} = 3 \cdot 440V \cdot 4,4 / -36,87^{\circ} = 5807,2 / 36,87^{\circ} \end{cases}$$

$$= 4646 + j3484 = P + jQ \rightarrow P = 4.6kW$$

Question 4

A star-connected load consisting of a resistor of 80Ω and inductor of 0.191 H in each phase is connected to a 415-V , three-phase, 50-Hz supply. Calculate:

- (a) the phase current I ;
- (b) the real power P consumed by the load; and
- (c) the reactive power Q consumed by the load.
- (d) From P and Q calculate the load phase angle ϕ , and show that:

$$P = \sqrt{3}VI \cos \phi$$

$$Q = \sqrt{3}VI \sin \phi$$

Question 4

a) **Inductor:**
 $X_L = 2\pi fL = 2 \times \pi \times 50 \times 0.191 \Omega = 60 \Omega$

$$U_{Ph} = \frac{415V}{\sqrt{3}} = 240V$$

Lagging current (inductive load)

$$\Rightarrow \underline{I} = \frac{240}{(80 + j60)} A = \underline{\underline{2.4 \angle -37^\circ A}}$$

b) $\bar{S} = \sqrt{3} \bar{V} \bar{I}^* = \sqrt{3} \times 415 \times \frac{240}{(80 - j60)} = (1380 + j1035) \text{ VA}$
 $= 1725 \angle 37^\circ \text{ VA}$

$$\Rightarrow \underline{\underline{P = 1380W}}$$

c) $\Rightarrow \underline{\underline{Q = 1035 \text{ var}}}$


d) $P = \sqrt{3} \times U \times I \times \cos \varphi$ $Q = \sqrt{3} \times U \times I \times \sin \varphi$
 $\Rightarrow \tan \varphi = \frac{Q}{P}$

$$\Rightarrow \varphi = \arctan\left(\frac{Q}{P}\right) = \arctan(0.75)$$

$$\approx \underline{\underline{37^\circ}}$$

$$\Rightarrow P = \sqrt{3} \times UI \times \cos \varphi \approx 1380W$$
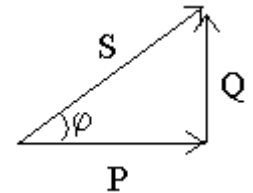
$$Q = \sqrt{3} \times UI \times \sin \varphi \approx 1035 \text{ var}$$



Use of reactance (ind)

Generation

Consumption

“Generation” of reactance (cap)

