



Aalto-yliopisto
Teknillinen korkeakoulu

Exercise Session 2

Power systems

Question 1

- A 220-kV overhead line has the following properties:
 - $s=200$ km
 - $r=0.07 \Omega/\text{km}$
 - $x=0.32 \Omega/\text{km}$
 - $b=3.6 \mu\text{S}/\text{km}$

Define the parameters for medium-length line

- a) Π -model
- b) T-model

and calculate the open circuit voltage at the end of the line if the voltage at the beginning is 220 kV.


Question 1

- A 220-kV overhead line has the following properties:
 - $s=200$ km
 - $r=0.07 \Omega/\text{km}$
 - $x=0.32 \Omega/\text{km}$
 - $b=3.6 \mu\text{S}/\text{km}$

$$\begin{array}{l} \underline{Z} = (r + j\omega l) s \\ \underline{Y} = (g + j\omega c) s \end{array} \left\{ \begin{array}{l} s = \text{length} \\ r = \text{resistance} / s \\ l = \text{inductance} / s \\ g = \text{conductance} / s \\ c = \text{capacitance} / s \end{array} \right.$$

Define the parameters for a medium-length line with the


- Π -model
- T-model

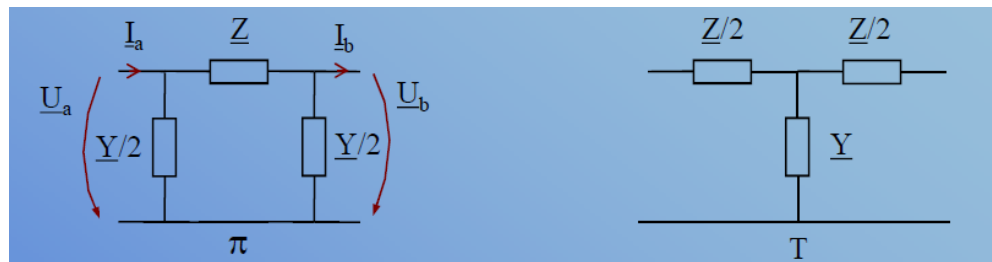

and calculate the open circuit voltage at the end of the line if the voltage at the beginning is 220 kV.

Question 1

a) Π -model

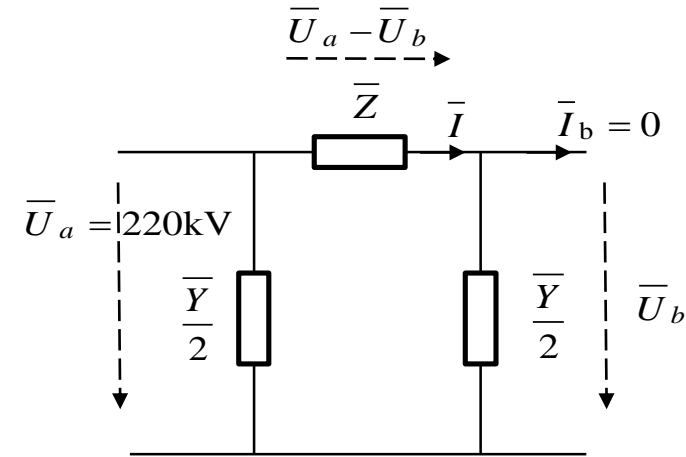

$$\bar{Z} = (r + j\omega l)s = (r + jx)s = \left(0.07 \frac{\Omega}{\text{km}} + j0.32 \frac{\Omega}{\text{km}}\right)200\text{km} = 65.51 \angle 77.66^\circ \Omega$$

$$\frac{\bar{Y}}{2} = \frac{(g + j\omega c)s}{2} = \frac{(g + jb)s}{2} = \frac{\left(0 \frac{\mu\text{S}}{\text{km}} + j3.6 \frac{\mu\text{S}}{\text{km}}\right)200\text{km}}{2} = 360 \angle 90^\circ \mu\text{S}$$

$$\bar{U}_b = \bar{I} \frac{2}{\bar{Y}} = \frac{\bar{U}_a - \bar{U}_b}{\bar{Z}} \frac{2}{\bar{Y}}$$


$$\Leftrightarrow \bar{U}_b \bar{Z} \bar{Y} = 2\bar{U}_a - 2\bar{U}_b$$

$$\Leftrightarrow \bar{U}_b (\bar{Z} \bar{Y} + 2) = 2\bar{U}_a$$

$$\bar{U}_b = \frac{2\bar{U}_a}{(\bar{Z} \bar{Y} + 2)} = \frac{2 \times 220\text{kV}}{(65.51 \angle 77.66^\circ \Omega \times 2 \times 360 \angle 90^\circ \mu\text{S} + 2)} = 225 \angle -0.3^\circ \text{kV}$$

Question 1

b) T-model

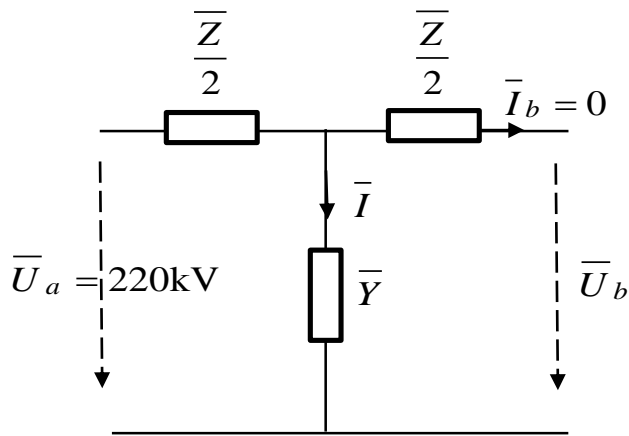


$$\frac{\bar{Z}}{2} = \frac{65.51 \angle 77.66^\circ \Omega}{2} = 32.76 \angle 77.66^\circ \Omega$$

$$\bar{Y} = 2 \times \frac{\bar{Y}}{2} = 2 \times 360 \angle 90^\circ \mu\text{S} = 720 \angle 90^\circ \mu\text{S}$$

$$\begin{aligned} \bar{U}_b &= \bar{I} \frac{1}{\bar{Y}} = \frac{\bar{U}_a}{\frac{\bar{Z}}{2} + \frac{1}{\bar{Y}}} = \frac{2\bar{U}_a}{\bar{Z}\bar{Y} + 2} \\ &= \frac{2 \times 220 \text{ kV}}{(65.51 \angle 77.66^\circ \Omega \times 720 \angle 90^\circ \mu\text{S} + 2)} = 225 \angle -0.3^\circ \text{ kV} \end{aligned}$$


Both models give the same result!

Question 2

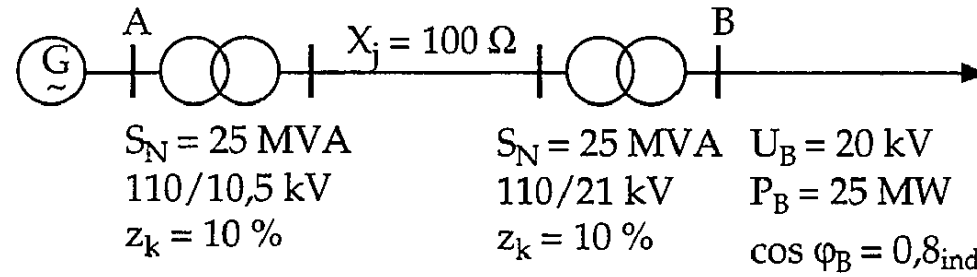

- Calculate per-unit values for all the parameters in the picture above. Use base values: $S_b = 50 \text{ MVA}$ and $U_b = 110 \text{ kV}$

Question 2

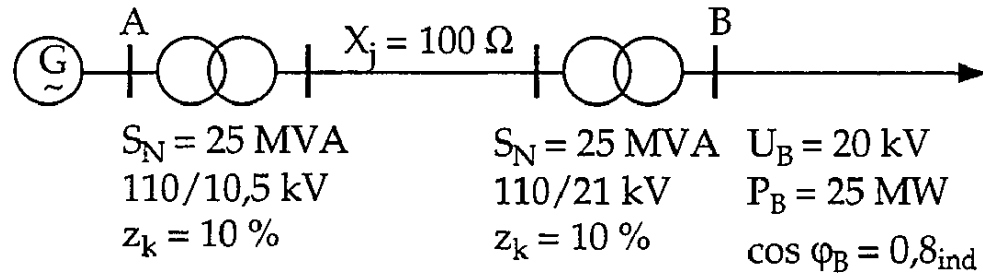

- Calculate per-unit values for all the parameters in the picture above. Use base values: $S_b = 50 \text{ MVA}$ and $U_b = 110 \text{ kV}$

$$x = \frac{X}{\frac{U_b^2}{S_b}} = \frac{Z_k \frac{U_n^2}{S_n}}{\frac{U_b^2}{S_b}}$$

⇒ Other base voltages by transforming ratios:

$$U_{2b} = (U_{2n}/U_{1n}) \cdot U_{1b}$$


⇒ Current base value by base power and base voltage:

$$I_b = S_b / \sqrt{3} U_b$$

⇒ Impedance base value by base power and base voltage:

$$Z_b = U_b^2 / S_b$$

Question 2

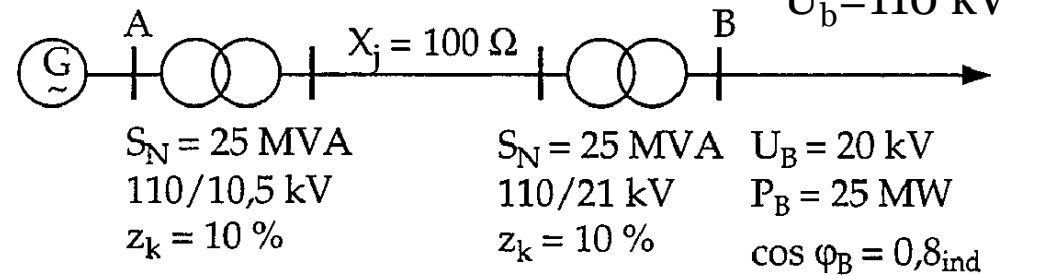

$$x_{T1} = \frac{Z_k \frac{U_N^2}{S_N}}{\frac{U_b^2}{S_b}} = \frac{0.10 \cdot \frac{(110 \text{ kV})^2}{25 \text{ MVA}}}{\frac{(110 \text{ kV})^2}{50 \text{ MVA}}} = \underline{\underline{0.200}}$$

$$x_j = \frac{X_j}{\frac{U_b^2}{S_b}} = \frac{100 \Omega}{\frac{(110 \text{ kV})^2}{50 \text{ MVA}}} = \underline{\underline{0.413}}$$

$$x_{T2} = \frac{Z_k \frac{U_N^2}{S_N}}{\frac{U_b^2}{S_b}} = 0.10 \cdot \frac{\frac{(110 \text{ kV})^2}{25 \text{ MVA}}}{\frac{(110 \text{ kV})^2}{50 \text{ MVA}}} = \underline{\underline{0.200}}$$

$$u_B = \frac{20 \text{ kV}}{\left[U_b \cdot \frac{U_{N2}}{U_{N1}} \right]} = \frac{20 \text{ kV}}{\left[110 \text{ kV} \cdot \frac{21 \text{ kV}}{110 \text{ kV}} \right]} = \underline{\underline{0.952}}$$


$$p_B = \frac{P_B}{S_b} = \frac{25 \text{ MW}}{50 \text{ MVA}} = \underline{\underline{0.500}}$$

Question 3

- Based on the results obtained from Question 2, calculate the voltage in busbar A (per-unit value and in volts).

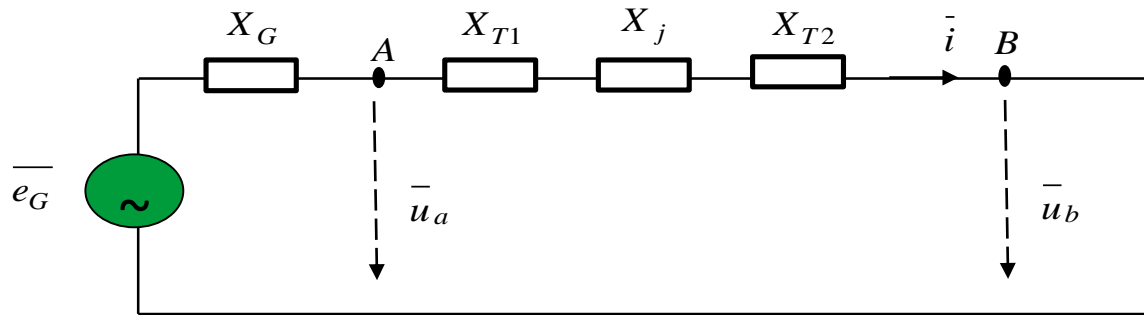Question 3

- Based on the results obtained from Question 2, calculate the voltage in busbar A (per-unit value and in volts).



$$x_{T2} = \underline{\underline{0.200}}$$

$$x_{T1} = \underline{\underline{0.200}}$$


$$u_B = \underline{\underline{0.952}}$$

$$x_j = \underline{\underline{0.413}}$$

$$p_B = \underline{\underline{0.500}}$$

$$\cos \varphi_B = 0.8_{\text{ind}}$$

Question 3

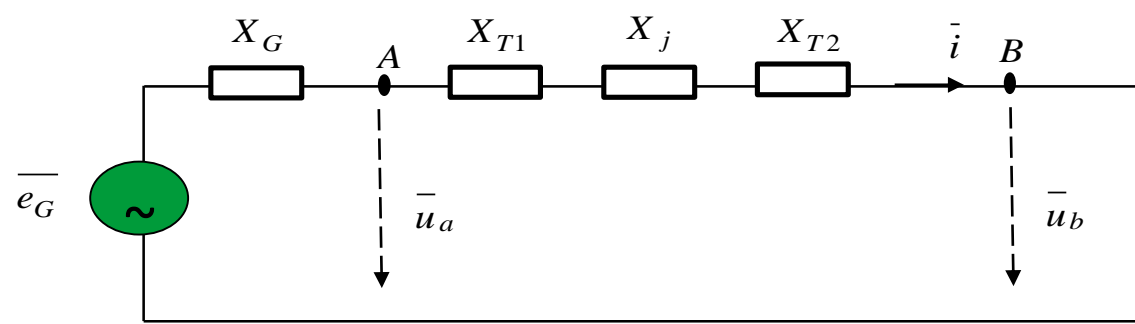

$$\underline{s}_B = \underline{u}_B \underline{i}^*$$

$$\cos \varphi_B = 0.8_{\text{ind}}$$

$$\underline{i} = \frac{\underline{s}_B^*}{\underline{u}_B^*} = \left(\frac{P_B}{\cos \varphi} \angle -\varphi \right) \cdot \frac{1}{u_B} = \left(\frac{0.500}{0.8} \angle -\arccos 0.8 \right) \cdot \frac{1}{0.952} \approx 0.656 / \underline{\underline{-36.9^\circ}}$$

$$\underline{u}_A = \underline{u}_B + j(x_{T1} + x_j + x_{T2}) \cdot \underline{i}$$

$$\underline{\underline{\underline{u}_A}} = 0.952 / \underline{0^\circ} + j(0.200 + 0.413 + 0.200) \cdot 0.656 / \underline{-36.9^\circ} \approx \underline{\underline{\underline{1.34 / 18.5^\circ}}}$$

$$\underline{U}_A = \underline{u}_A \cdot U_b \left(\frac{U_{N2}}{U_{N1}} \right) = 1.34 / \underline{18.5^\circ} \cdot 110 \text{ kV} \cdot \left(\frac{10.5 \text{ kV}}{110 \text{ kV}} \right) \approx \underline{\underline{\underline{14.1 \text{ kV} / 18.5^\circ}}}$$

Original base value was in 110-kV level (the line)
 The "new" base value in 10.5-kV level (at point A).
 Note the reference over the transformer!

Question 4

A 50-Hz, 50-MVA transformer with a 132-kV primary and a 33-kV secondary has a reactance of 0.1pu per phase. What is the reactance in ohms per phase:

- (a) referred to the primary;
- (b) referred to the secondary.

Question 4

A 50-Hz, 50-MVA transformer with a 132-kV primary and a 33-kV secondary has a reactance of 0.1pu per phase. What is the reactance in ohms per phase:

- (a) referred to the primary;
- (b) referred to the secondary.

⇒ Other base voltages by transforming ratios:

$$U_{2b} = (U_{2n}/U_{1n}) \cdot U_{1b}$$

⇒ Current base value by base power and base voltage:

$$I_b = S_b / \sqrt{3} U_b$$

⇒ Impedance base value by base power and base voltage:

$$Z_b = U_b^2 / S_b$$

Question 4

a) referred to the primary

Primary :

$$Z_B = \frac{U_B^2}{S_B} = \frac{(132 \times 10^3)^2}{50 \times 10^6} \Omega = 348.5 \Omega = X_B$$

$$X = x \times X_B = 0.1 \times 348.5 \Omega = \underline{\underline{34.85 \Omega}}$$

b) referred to the secondary

Secondary :

$$Z_B = \frac{(33 \times 10^3)^2}{50 \times 10^6} \Omega = 21.78 \Omega = X_B$$

$$X = x \times X_B = 0.1 \times 21.78 \Omega = \underline{\underline{2.178 \Omega}}$$