



Aalto-yliopisto
Teknillinen korkeakoulu

Exercise 7


Power systems

Question 1

In the middle of the line there is a zero resistance three-phase short circuit.
What is the voltage at the fault location prior to the fault? Calculate


- a) sub-transient
- b) transient
- c) steady state

short-circuit current.


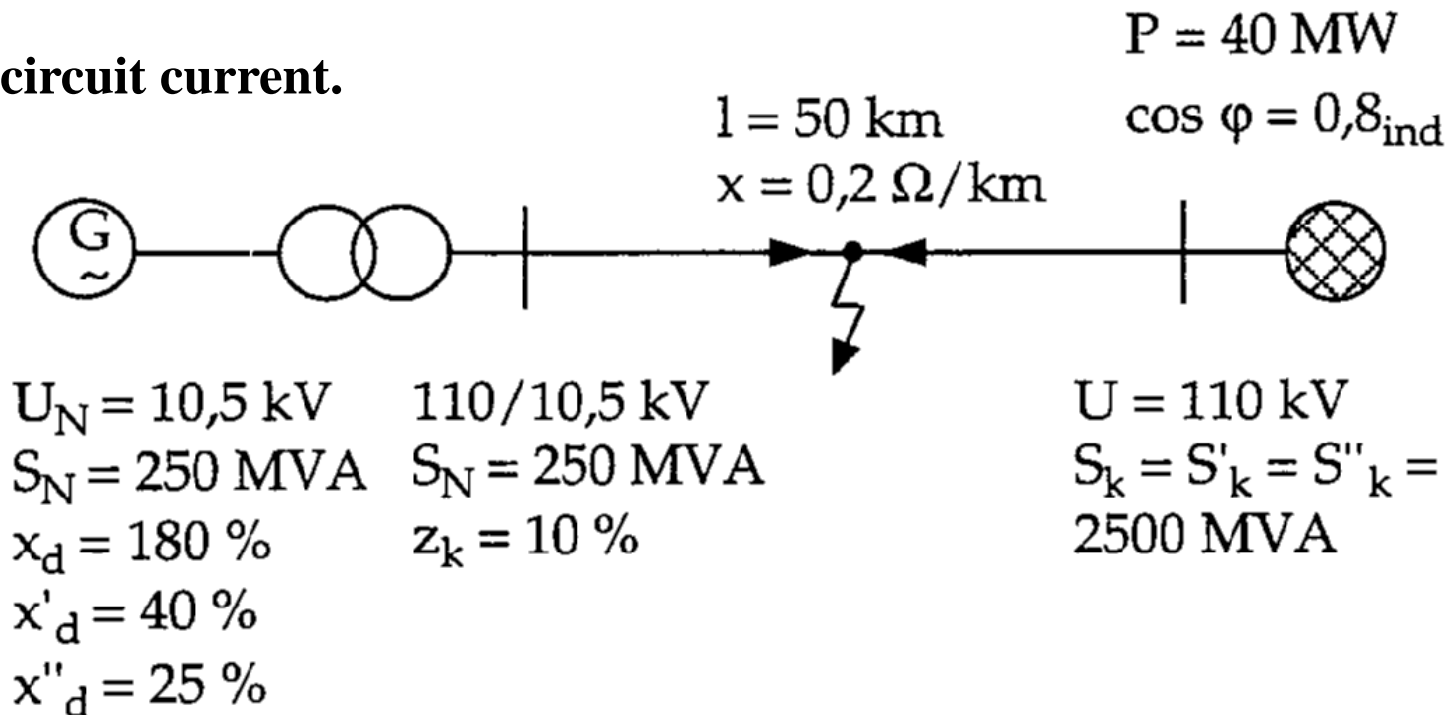


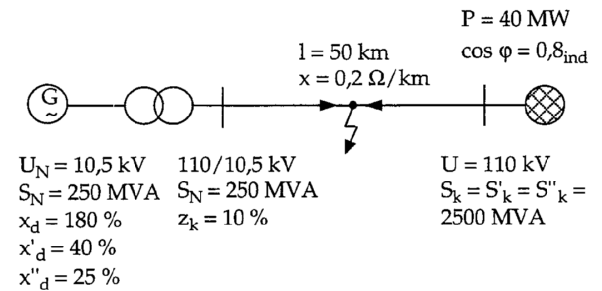Question 1

What is the voltage at the fault location prior to the fault?



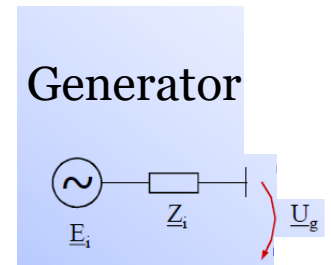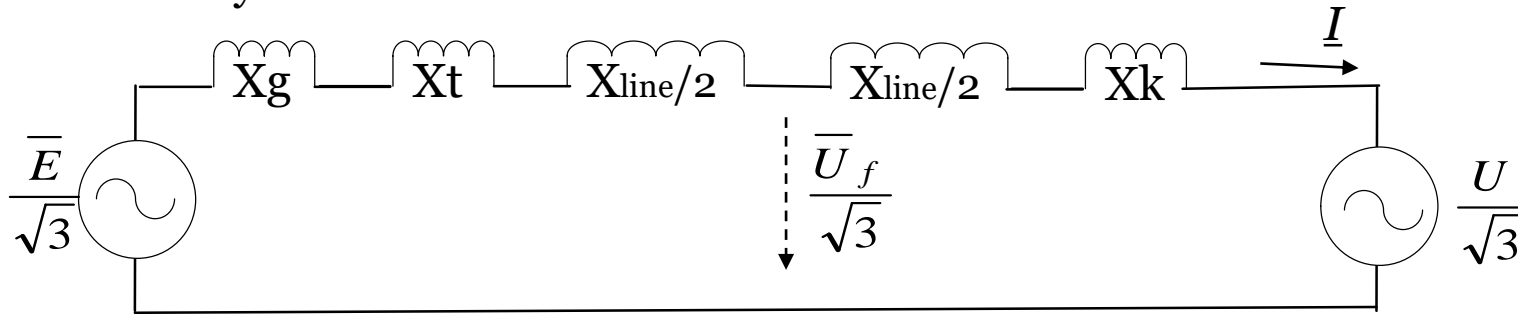Let's calculate the voltage U_f with the help of given information: P , U , power factor and steady-state reactances:



First, calculate the current flowing through each component:



$$\underline{S} = 3 \cdot U_{ph} \cdot \underline{I}^* = 3 \cdot \frac{U}{\sqrt{3}} \cdot \underline{I}^* = \sqrt{3} \sqrt{3} \cdot \frac{U}{\sqrt{3}} \cdot I = \sqrt{3} U \cdot \underline{I}^*$$

$$\underline{S} = \frac{P}{\cos \varphi} \underbrace{\angle \arccos(0.8)}_{\text{positive(ind.)}}$$

$$\Rightarrow \underline{I} = \left(\frac{1}{\sqrt{3} U} \frac{P}{\cos \varphi} \angle 36.9^\circ \right)^* = \frac{1}{\sqrt{3} \cdot 110 \text{ kV}} \frac{40 \text{ MW}}{0.8} \angle -36.9^\circ = 262.4 \text{ A} \angle -36.9^\circ$$

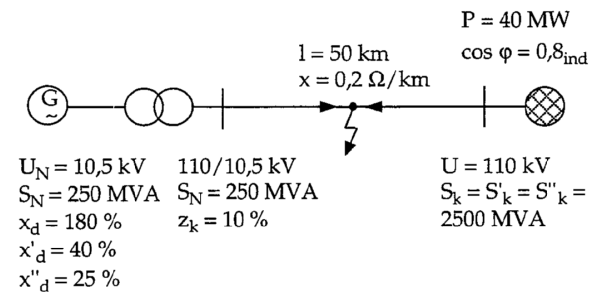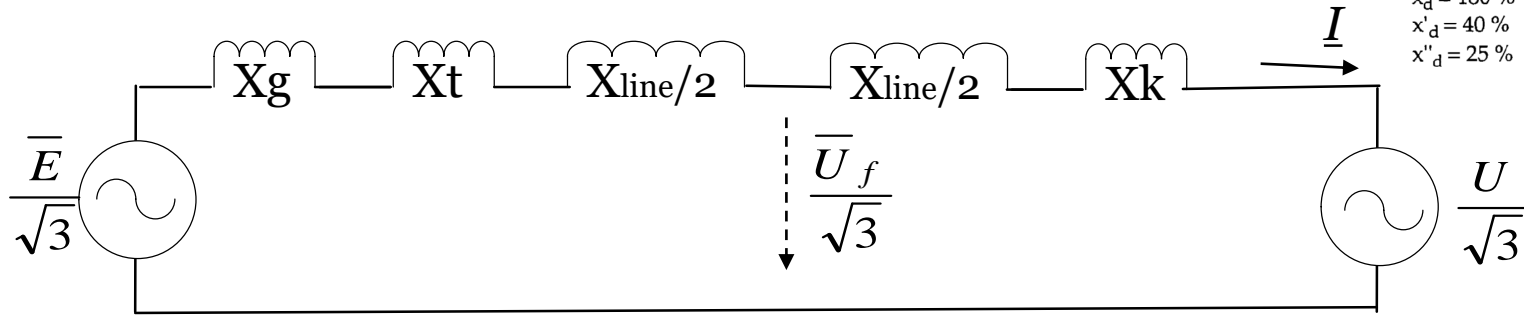Question 1

What is the voltage at the fault location prior to the fault?



Next, the reactance values as seen from the line (110-kV level):

$$X_g = x_d \cdot \frac{U_N^2}{S_N} \cdot \left(\frac{U_{N1}}{U_{N2}} \right)^2 = 1.80 \cdot \frac{(10.5 \text{ kV})^2}{250 \text{ MVA}} \cdot \left(\frac{110}{10.5} \right)^2 = 87.12 \Omega$$


$$X_t = z_k \cdot \frac{U_N^2}{S_N} = 0.10 \cdot \frac{(110 \text{ kV})^2}{250 \text{ MVA}} = 4.84 \Omega$$

$$\frac{X_{line}}{2} = x \cdot \frac{l}{2} = 0.2 \frac{\Omega}{\text{km}} \cdot 25 \text{ km} = 5 \Omega$$

$$X_k = X'_k = X''_k = \frac{U^2}{S_k} = \frac{(110 \text{ kV})^2}{2500 \text{ MVA}} = 4.84 \Omega \quad \text{since } S_k = S'_k = S''_k$$

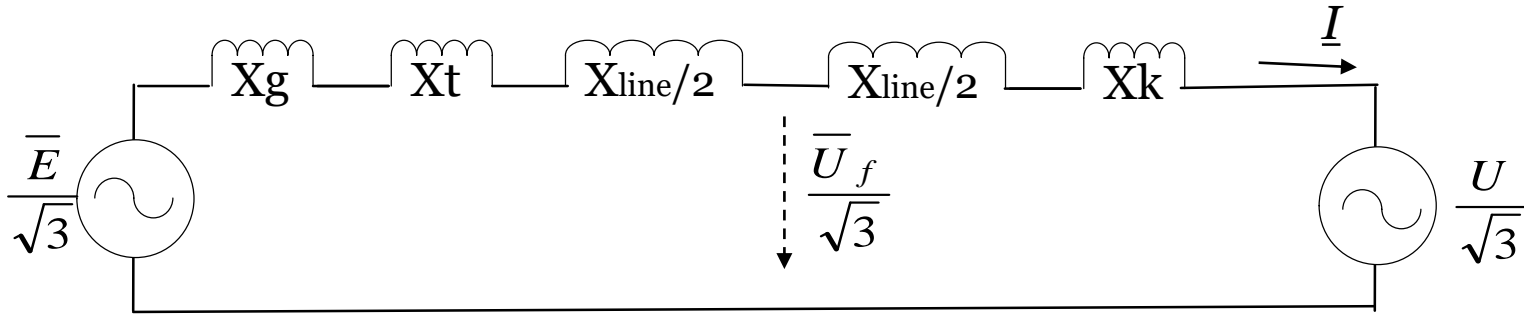Question 1

What is the voltage at the fault location prior to the fault?



The fault voltage is the grid voltage plus voltage over X_k and half of the line ($X_{line}/2$)

$$\frac{\underline{U}_f}{\sqrt{3}} = \frac{U}{\sqrt{3}} + j \left(X_k + \frac{X_{line}}{2} \right) \cdot \underline{I}$$


$$\underline{U}_f = U + j\sqrt{3} \cdot \left(X_k + \frac{X_{line}}{2} \right) \cdot \underline{I} = 110 \text{ kV} + j\sqrt{3} \cdot (4.84 + 5) \Omega \cdot 262.4 \text{ A} \angle -36.9^\circ$$

$$\approx 112.74 \text{ kV} \angle 1.82^\circ$$

$$\underline{U}_f = \underline{\underline{112.74 \text{ kV}}}$$

Question 1

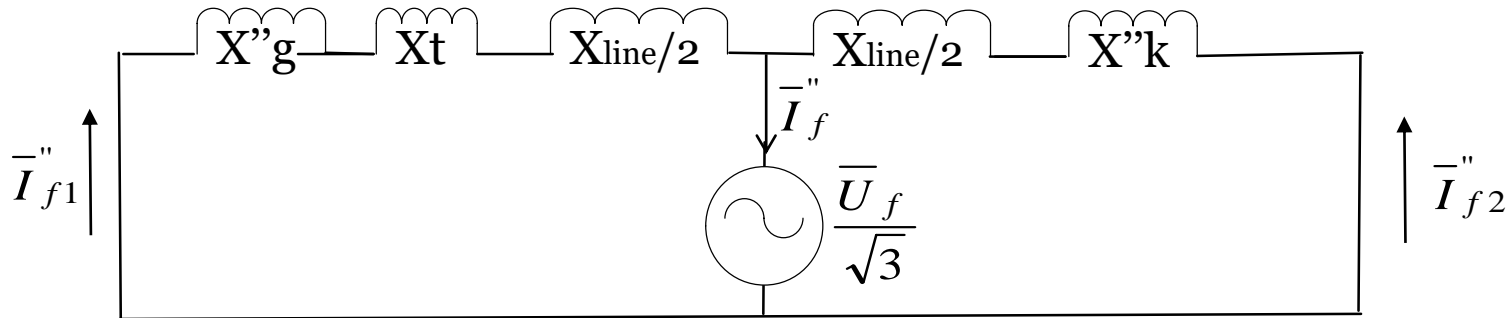a) Calculate sub-transient currents (from the grid and from the generator)



The subtransient reactances are:


$$X_g'' = \frac{x_d''}{x_d} \cdot X_g = \frac{0.25}{1.80} \cdot 87.12 \, \Omega = 12.10 \, \Omega \quad X_k'' = 4.84 \, \Omega$$

$$\underline{I}_{f1}'' = \frac{\frac{U_f}{\sqrt{3}}}{j \left(X_g'' + X_t + \frac{X_{line}}{2} \right)} = \frac{\frac{112.74 \text{ kV}}{\sqrt{3}} \angle 1.82^\circ}{j(12.10 + 4.84 + 5) \, \Omega} \approx 2.97 \text{ kA} \angle -88.2^\circ \quad I_{f1}'' = \underline{\underline{2.97 \text{ kA}}}$$

$$\underline{\underline{I}}_{f2}'' = \frac{\frac{U_f}{\sqrt{3}}}{j \left(\frac{X_{line}}{2} + X_k'' \right)} = \frac{\frac{112.74 \text{ kV}}{\sqrt{3}} \angle 1.82^\circ}{j(5 + 4.84) \, \Omega} \approx 6.61 \text{ kA} \angle -88.2^\circ \quad I_{f2}'' = \underline{\underline{6.61 \text{ kA}}}$$

Question 1

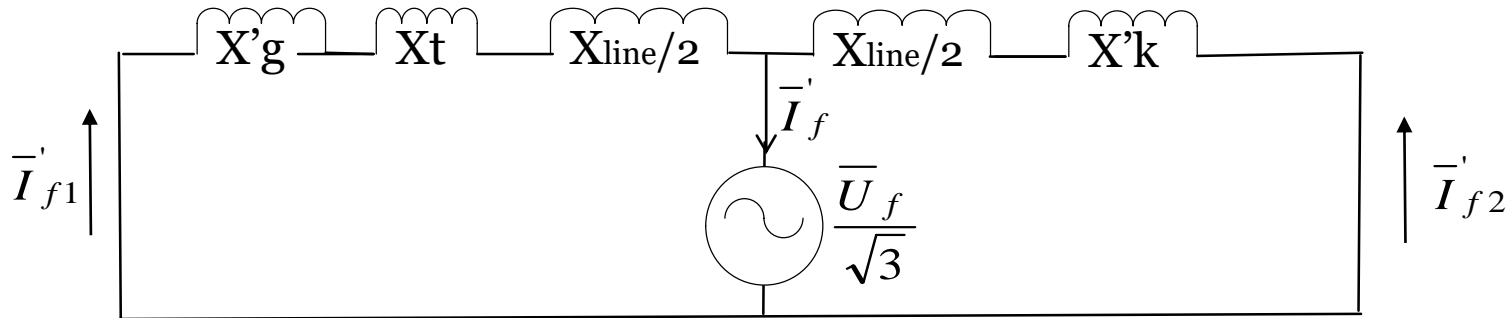b) Calculate transient currents (from the grid and from the generator)



The transient reactances are:


$$X'_g = \frac{x'_d}{x_d} \cdot X_g = \frac{0.4}{1.80} \cdot 87.12 \, \Omega = 19.36 \, \Omega \quad X'_k = 4.84 \, \Omega$$

$$\underline{I}'_{f1} = \frac{\frac{U_f}{\sqrt{3}}}{j \left(X'_g + X_t + \frac{X_{line}}{2} \right)} = \frac{\frac{112.74 \text{ kV}}{\sqrt{3}} / 1.82^\circ}{j(19.36 + 4.84 + 5) \, \Omega} \approx \underline{\underline{2.23 \text{ kA} / -88.2^\circ}} \quad I_{f1} = \underline{\underline{2.23 \text{ kA}}}$$

$$\underline{I}'_{f2} = \frac{\frac{U_f}{\sqrt{3}}}{j \left(\frac{X_{line}}{2} + X'_k \right)} = \underline{I}''_{f2} \approx \underline{\underline{6.61 \text{ kA} / -88.2^\circ}} \quad I_{f2} = \underline{\underline{6.61 \text{ kA}}} \quad X'_k = X''_k$$

Question 1

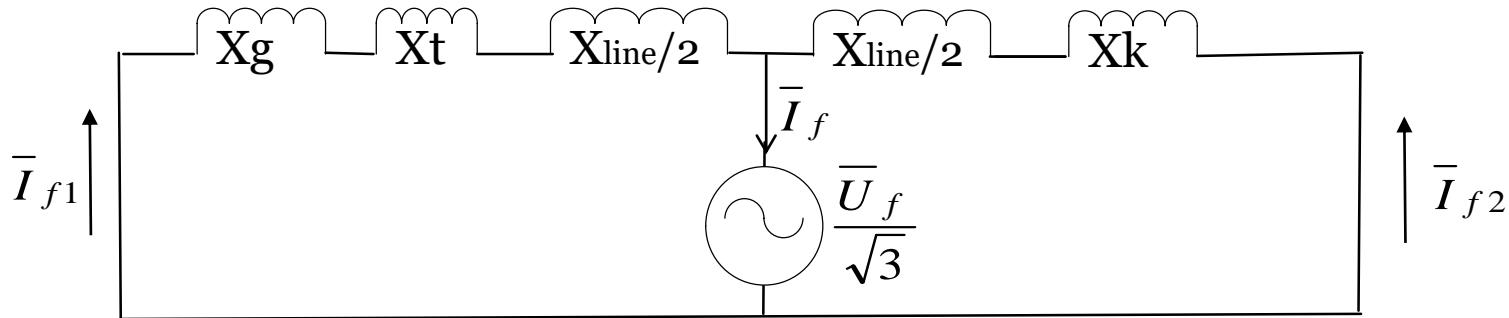c) Calculate steady-state currents (from the grid and from the generator)




$$\underline{I}_{f1} = \frac{\frac{\underline{U}_f}{\sqrt{3}}}{j\left(X_g + X_t + \frac{X_{line}}{2}\right)} = \frac{\frac{112.74 \text{ kV}}{\sqrt{3}} / 1.82^\circ}{j(87.12 + 4.84 + 5) \Omega} \approx 0.67 \text{ kA} / -88.2^\circ \quad \underline{I}_{f1} = \underline{\underline{0.67 \text{ kA}}}$$

$$\underline{I}_{f2} = \frac{\frac{\underline{U}_f}{\sqrt{3}}}{j\left(\frac{X_{line}}{2} + X_k\right)} = \underline{I}_{f2}'' \approx 6.61 \text{ kA} / -88.2^\circ \quad \underline{\underline{I}_{f2} = 6.61 \text{ kA}}$$

$$X_k = X_k''$$

Question 2

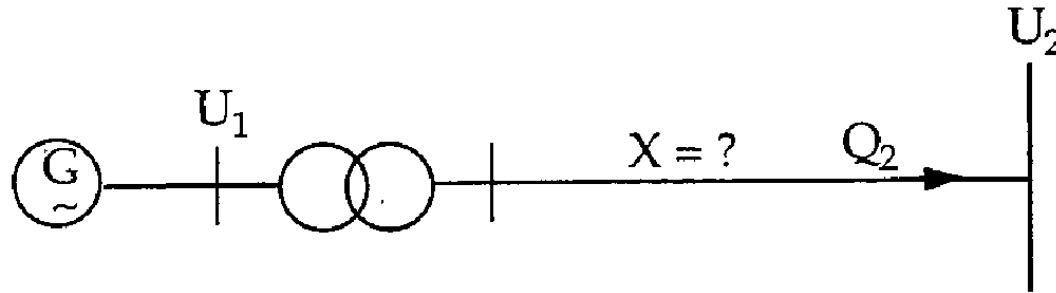


Generator	Transformer
$P_N = 880 \text{ MW}$	$S_N = 1000 \text{ MVA}$
$S_N = 980 \text{ MVA}$	410/20 kV
$U_N = 20 \text{ kV}$	$z_k = 0,15$

Starting from the power-angle equations, **define the maximum line reactance X** so that the power plant can feed its full active power P_N without exceeding the maximum apparent power S_N . Voltage of the transmission network is constant $U_2 = 410 \text{ kV}$ and it doesn't consume any reactive power, that is $Q_2 = 0$.

Question 2


Define maximum line reactance

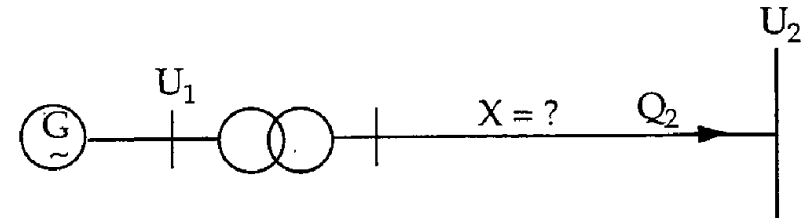

Generator
 $P_N = 880 \text{ MW}$
 $S_N = 980 \text{ MVA}$
 $U_N = 20 \text{ kV}$

Transformer
 $S_N = 1000 \text{ MVA}$
 $410/20 \text{ kV}$
 $z_k = 0,15$

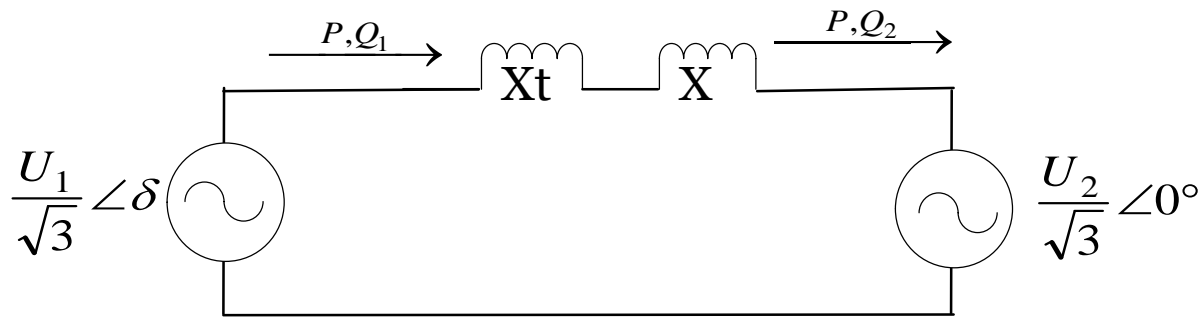$U_2 = 410 \text{ kV}$
 $Q_2 = 0 \text{ var}$





Resistances are neglected: $\Rightarrow P_1 = P_2 = P = P_N$

$$X_t = z_k \cdot \frac{U_N^2}{S_N} = 0.15 \cdot \frac{(410 \text{ kV})^2}{1000 \text{ MVA}} \approx 25.2 \Omega$$

Question 2

Define maximum line reactance

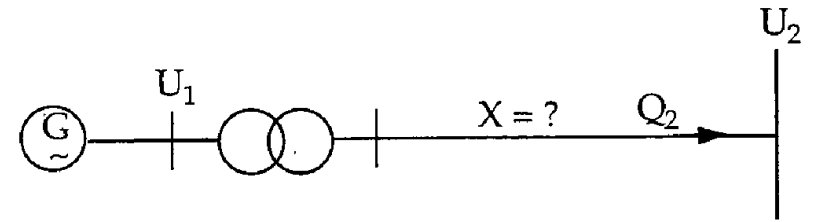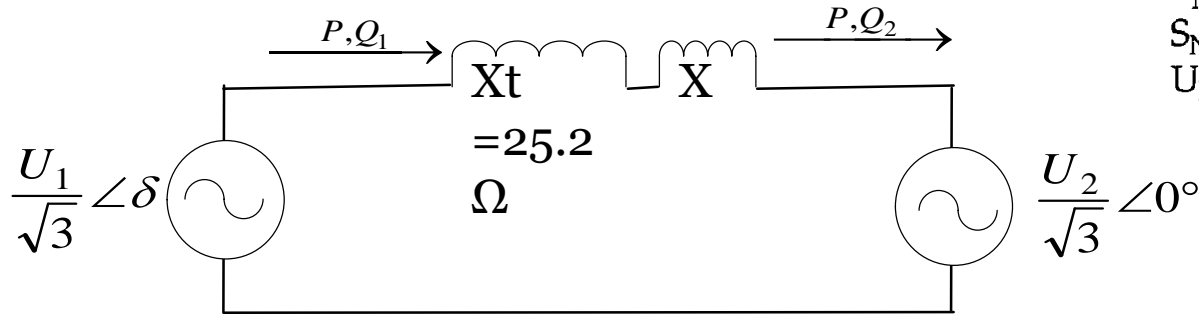

Generator	Transformer
$P_N = 880 \text{ MW}$	$S_N = 1000 \text{ MVA}$
$S_N = 980 \text{ MVA}$	$410/20 \text{ kV}$
$U_N = 20 \text{ kV}$	$z_k = 0,15$

$U_2 = 410 \text{ kV}$
 $Q_2 = 0 \text{ var}$

$$S_1 = \sqrt{P^2 + Q_1^2} = S_N$$

$$\begin{cases} P = \frac{U_1 U_2}{X_t + X} \sin \delta = P_N \\ Q_1 = \frac{U_1^2 - U_1 U_2 \cos \delta}{X_t + X} = \sqrt{S_N^2 - P_N^2} \\ Q_2 = \frac{U_1 U_2 \cos \delta - U_2^2}{X_t + X} = 0 \Leftrightarrow U_1 \cos \delta = U_2 \end{cases}$$



$$\begin{cases} \sin \delta = \frac{P_N (X_t + X)}{U_1 U_2} \\ \frac{U_1^2 - U_2^2}{X_t + X} = \sqrt{S_N^2 - P_N^2} \\ \cos \delta = \frac{U_2}{U_1} \end{cases}$$

Question 2

Define maximum line reactance

$$\begin{cases} \sin \delta = \frac{P_N (X_t + X)}{U_1 U_2} \\ \frac{U_1^2 - U_2^2}{X_t + X} = \sqrt{S_N^2 - P_N^2} \\ \cos \delta = \frac{U_2}{U_1} \end{cases}$$

$$\sin^2 \delta + \cos^2 \delta = 1$$

$$\Leftrightarrow \frac{P_N^2 \cdot (X_t + X)^2}{U_1^2 U_2^2} + \frac{U_2^2}{U_1^2} = 1 \quad | \cdot U_1^2$$


$$\Leftrightarrow U_1^2 = \frac{P_N^2 \cdot (X_t + X)^2}{U_2^2} + U_2^2$$

$$\frac{U_1^2 - U_2^2}{X_t + X} = \frac{\left(\frac{P_N^2 \cdot (X_t + X)^2}{U_2^2} + U_2^2 \right) - U_2^2}{X_t + X} = \frac{P_N^2 \cdot (X_t + X)}{U_2^2} = \sqrt{S_N^2 - P_N^2}$$

$$\Leftrightarrow X = \frac{U_2^2}{P_N^2} \cdot \sqrt{S_N^2 - P_N^2} - X_t = \frac{(410 \text{ kV})^2}{(880 \text{ MW})^2} \cdot \sqrt{(980 \text{ MVA})^2 - (880 \text{ MW})^2} - 25.2 \Omega$$

Maximum reactance: $X \approx 68.4 \Omega$

Question 3

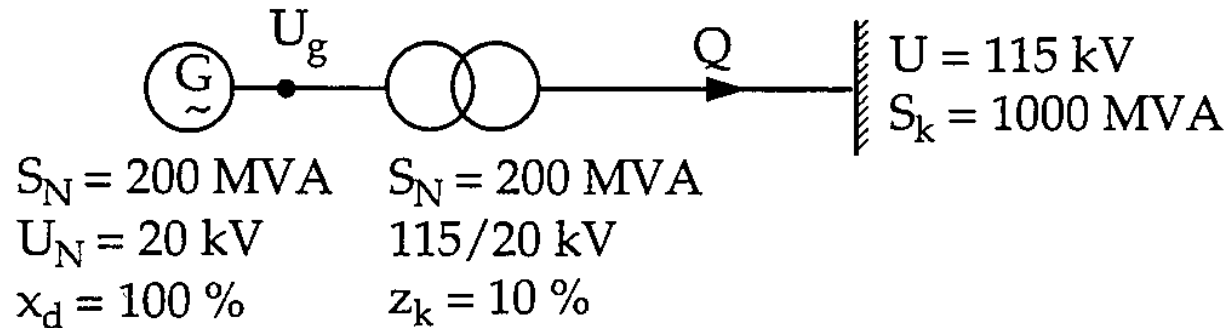


A synchronous generator is synchronized through a transformer to a bus. At the bus, the short circuit power is 1000 MVA and the voltage is 115 kV. After synchronizing, the generator's power is increased to 100 MW without changing the excitation. **Calculate the generator's terminal voltage U_g and reactive power Q .**

When synchronizing, the voltages of the generator are first tuned to same frequency, amplitude and phase order as in power system. Then connecting switch is then closed. At this moment the generator internal emf, terminal voltage and system bus V are same.

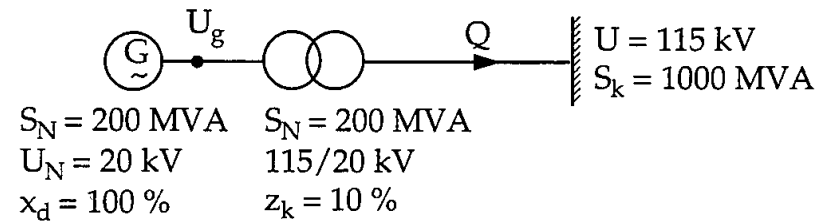Question 3


generator's terminal voltage U_g and reactive power Q .



Selecting base values: $S_b = 200 \text{ MVA}$, $U_b = 115 \text{ kV}$


We get:

$$\left\{ \begin{array}{l} p = \frac{P}{S_b} = \frac{100}{200} = 0.5 \\ x_g = 1.00 \\ x_t = 0.10 \\ x_{grid} = \frac{X_{grid}}{Z_b} = \frac{\left(\frac{U^2}{S_k}\right)}{\left(\frac{U_b^2}{S_b}\right)} = \frac{\left(\frac{115^2 \cdot 10^6}{1000 \cdot 10^6}\right)}{\left(\frac{115^2 \cdot 10^6}{200 \cdot 10^6}\right)} = 0.20 \end{array} \right.$$

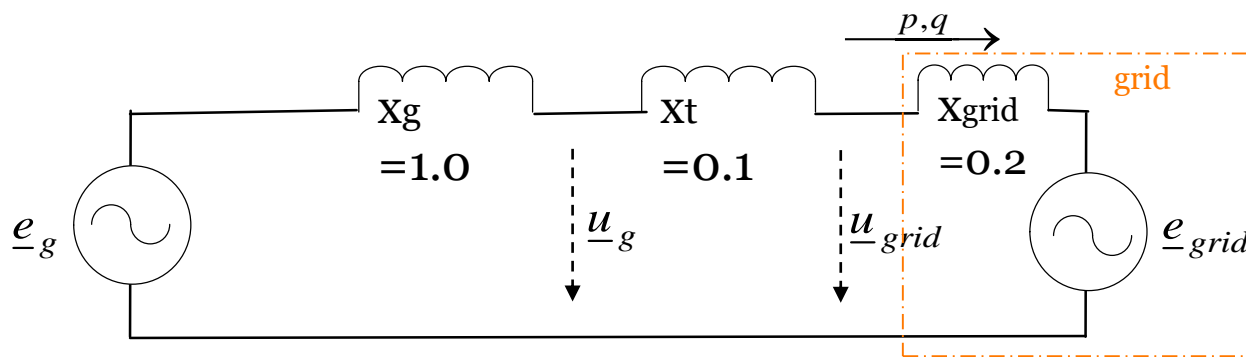

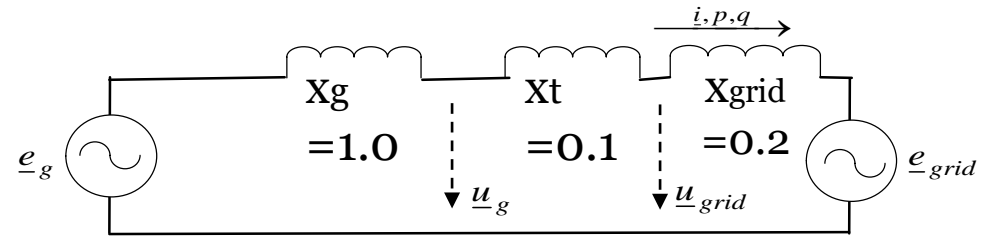Question 3

generator's terminal voltage U_g and reactive power Q .



When connecting to the grid: $e_g = u_g = u_{grid} = e_{grid} = 1$

If magnetizing is not changed after the synchronization, the generator emf stays the same:

$$e_g = 1$$


$$p = \frac{e_g \cdot e_{grid}}{x_g + x_t + x_{grid}} \cdot \sin \delta$$

$$0.5 = \frac{1 \cdot 1}{1.00 + 0.10 + 0.20} \cdot \sin \delta \Rightarrow \sin \delta = 0.5 \cdot 1.30$$

$$\Rightarrow \delta = 40.54^\circ$$

Current leading load voltage \rightarrow capacitive load

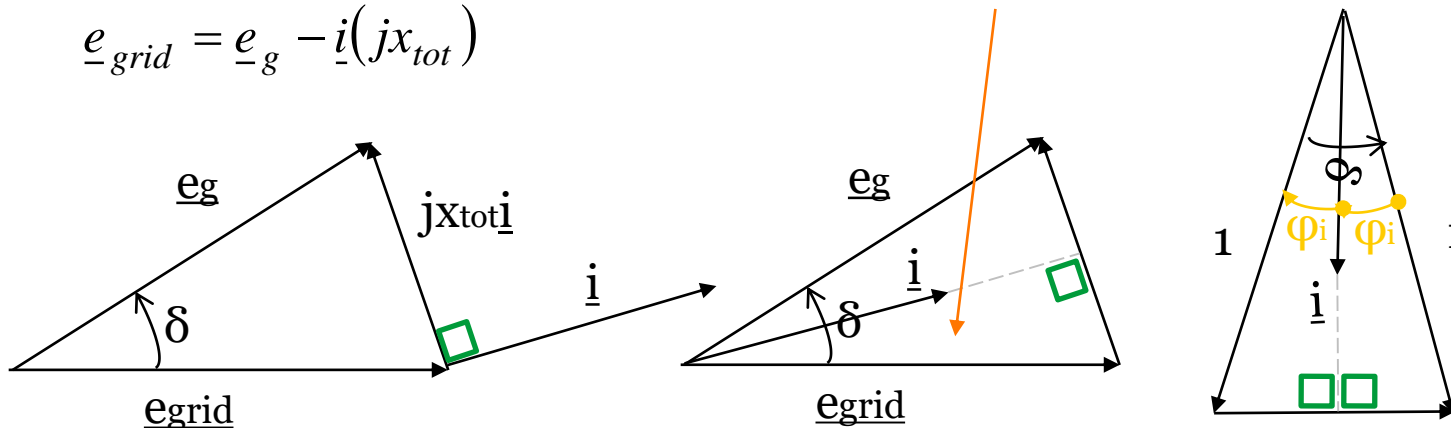
$$e_{grid} = e_g - \underline{i}(jx_{tot})$$



$$\begin{aligned} \varphi_i &= \frac{\delta}{2} \\ &= \frac{40.54^\circ}{2} = 20.27^\circ \\ \cos \varphi_i &= 0.938_{cap} \end{aligned}$$

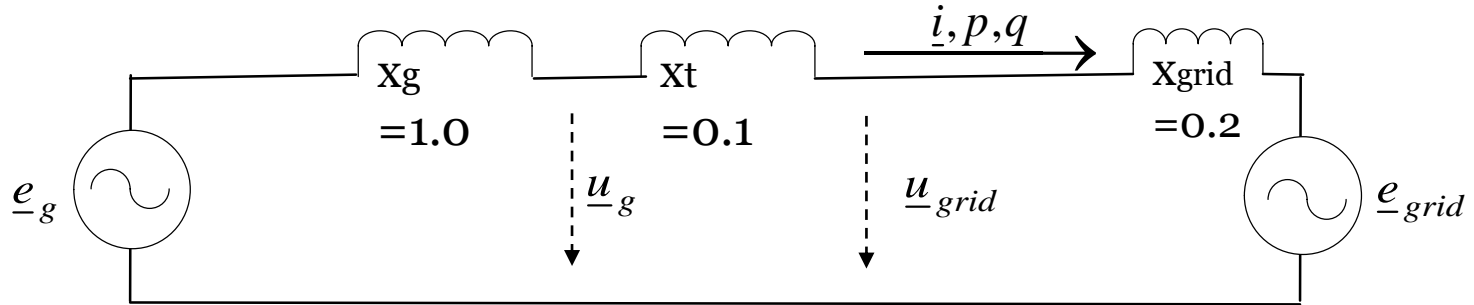Question 3

generator's terminal voltage U_g and reactive power Q .




$$\underline{e}_{grid} = e_{grid} / 0^\circ = 1 / 0^\circ$$

$$\underline{s} = \underline{u} \underline{i}^* = \frac{p}{\cos \varphi_i} \angle \underbrace{-\varphi_i}_{\text{neg. (cap.)}}$$

$$\underline{i} = \left(\frac{p}{e_{grid} \cos \varphi_i} \angle -\varphi_i \right)^* = \frac{0.5}{1 \cdot \cos 20.27^\circ} \angle 20.27^\circ = 0.533 \angle 20.27^\circ \text{ pu}$$

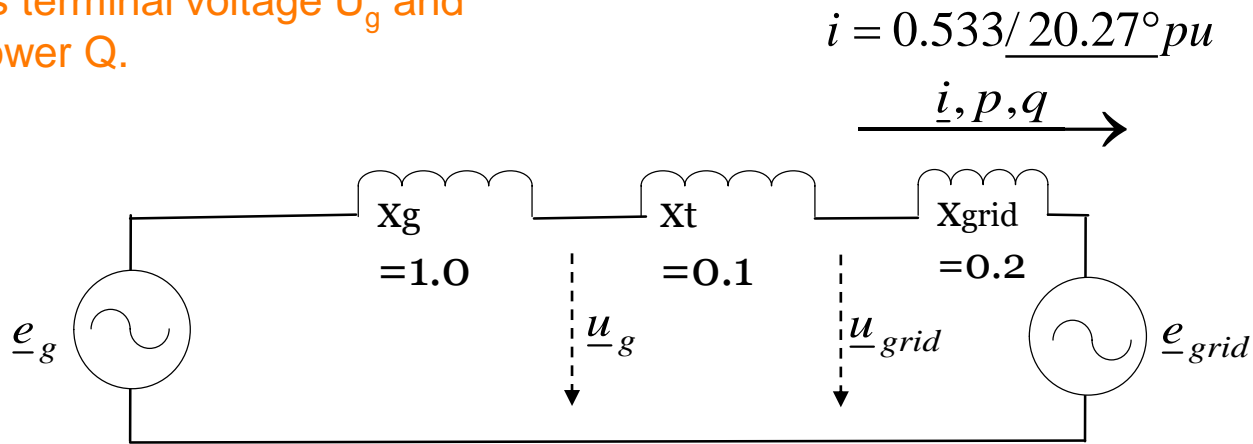Question 3

generator's terminal voltage U_g and reactive power Q .




Generator terminal voltage is:

$$\begin{aligned} \underline{u}_g &= \underline{e}_{grid} + j(x_t + x_{grid}) \cdot \underline{i} \\ &= 1 / 0^\circ + (0.10 + 0.20) / 90^\circ \cdot 0.533 / 20.27^\circ \\ &= 0.956 / 9.02^\circ pu \end{aligned}$$


20 - kV level: $U_b = 115 \frac{20}{115} = 20 \text{ kV}$

$$\underline{U}_g = u_g \cdot U_b = 0.956 \cdot 20 \text{ kV} = \underline{\underline{19.1 \text{ kV}}}$$

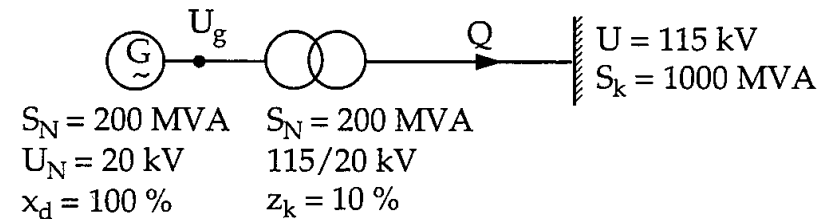

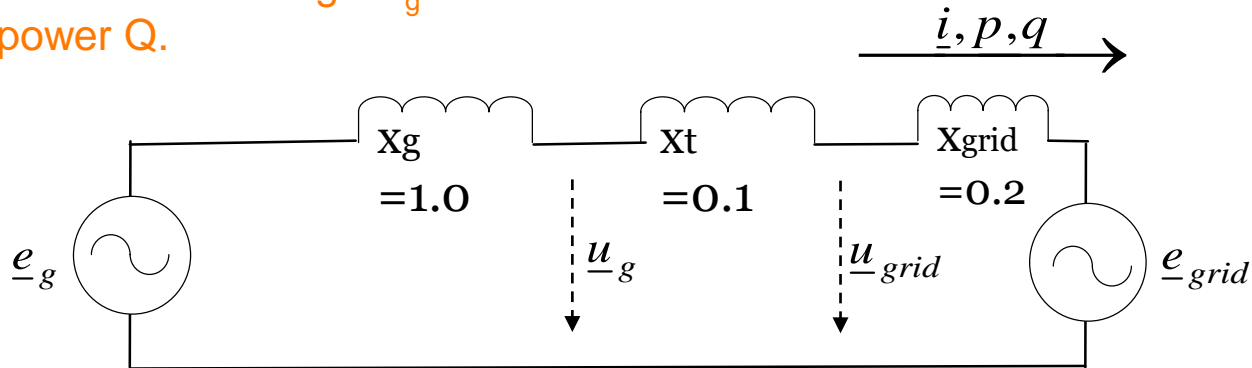Question 3

generator's terminal voltage U_g and reactive power Q .



Voltage at the station is:

$$\begin{aligned} \underline{u}_{grid} &= \underline{e}_{grid} + jx_{grid} \cdot \underline{i} \\ &= 1 \angle 0^\circ + 0.20 \angle 90^\circ \cdot 0.533 \angle 20.27^\circ \\ &= 0.968 \angle 5.93^\circ pu \end{aligned}$$

Reactive power flowing to the grid:

$$\begin{aligned} q &= u_{grid} \cdot i \cdot \sin \left(\underbrace{\varphi_{u_{grid}} - \varphi_i}_{\varphi} \right) \\ &= 0.968 \cdot 0.533 \cdot \sin(5.93^\circ - 20.27^\circ) \\ &= -0.128 pu \end{aligned}$$

The phasor diagram shows a horizontal reference axis. A green vector labeled \underline{i} is at an angle φ_i above the axis. Another green vector labeled \underline{U}_{grid} is at a larger angle $\varphi_{u_{grid}}$ above the axis. The angle between them is φ . A purple vector labeled $\varphi_{u_{grid}}$ and a blue vector labeled φ_i are also shown.


$$\underline{\underline{Q}} = q \cdot S_b = -0.128 \cdot 200 = \underline{\underline{-25.6 \text{ Mvar}}}$$

Question 4

$$S_N = 400 \text{ MVA}$$

$$U_N = 20 \text{ kV}$$

$$x_d = 200 \%$$

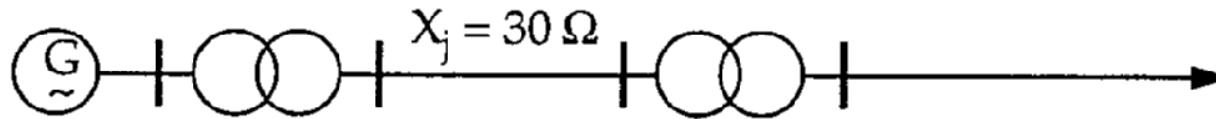

$$S_N = 420 \text{ MVA}$$
$$415/20 \text{ kV}$$
$$z_k = 15 \%$$

$$S_N = 400 \text{ MVA}$$
$$410/120 \text{ kV}$$
$$z_k = 12 \%$$



$$U = 115 \text{ kV}$$
$$P = 300 \text{ MW}$$
$$\cos \varphi = 0,95_{\text{ind}}$$

For the transmission system shown in the picture, calculate **generator's load current and terminal voltage**

- by reducing the network to generator's voltage level
- by using per-unit values

Question 4

a) at generator voltage level

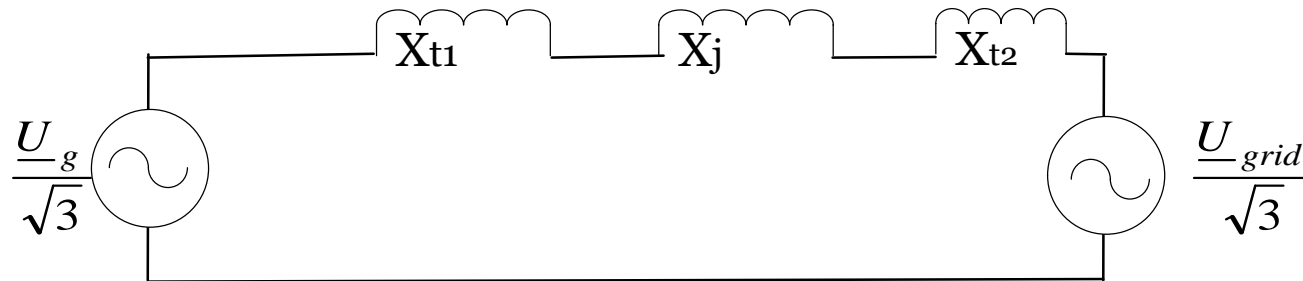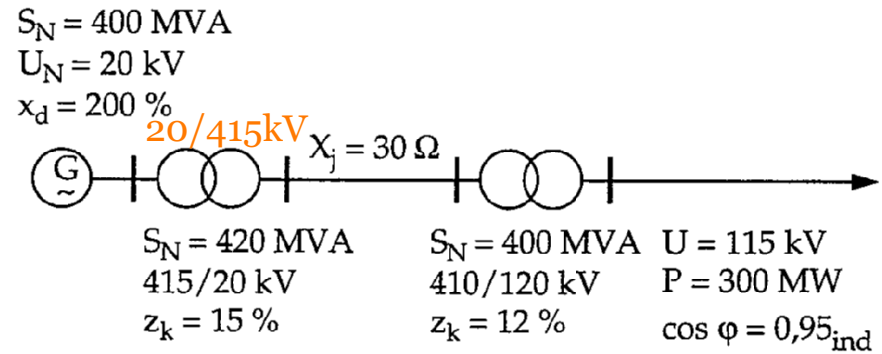

System reactances seen from the generator:

Transformer 1: $X_{t1} = z_k \frac{U_N^2}{S_N} = 0.15 \cdot \frac{20^2 \cdot 10^6}{420 \cdot 10^6} \Omega = 0.143 \Omega$

Line: $X_j = 30 \cdot \left(\frac{20}{415}\right)^2 \Omega = 0.070 \Omega$


Transformer 2: $X_{t2} = 0.12 \cdot \frac{410^2 \cdot 10^6}{400 \cdot 10^6} \cdot \left(\frac{20}{415}\right)^2 \Omega = 0.117 \Omega$

in secondary $Z_2 = \frac{U_2}{I_2}$


in primary $Z_2' = \frac{U_1}{I_1} = \frac{U_2 \cdot \frac{N_1}{N_2}}{I_2 \cdot \frac{N_2}{N_1}} = \left(\frac{N_1}{N_2}\right)^2 \cdot Z_2$

Question 4

a) current and voltage at generator

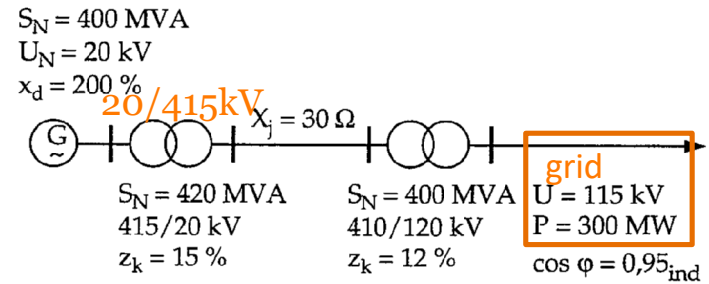

$U_n = 20 \text{ kV}$

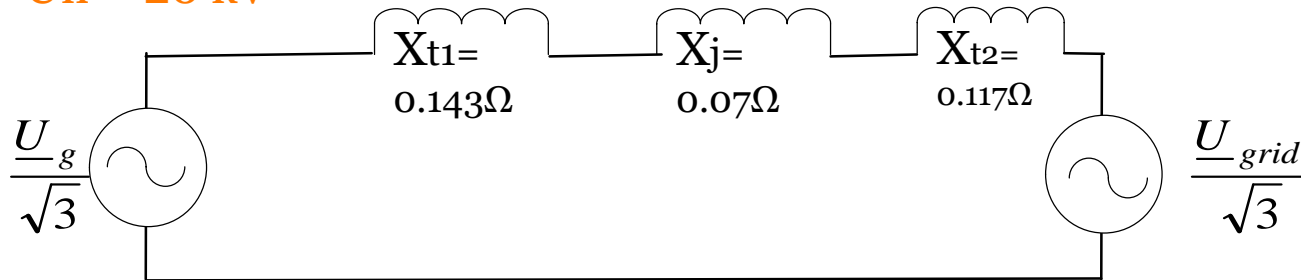

Let's choose: $\underline{U}_{grid} = U_{grid} \angle 0^\circ$ Jump over transf.2 and tranfs.1

Current at Generator: $\underline{I} = \frac{P_{grid}}{\sqrt{3} \cdot U_{grid} \cdot \cos \varphi} \angle -\arccos 0.95 \cdot \frac{120}{410} \cdot \frac{415}{20}$ Current at grid: $\left(\underline{S} = 3 \cdot \frac{U}{\sqrt{3}} \underline{I}^* = \frac{P}{\cos \varphi} \right)$


$$= \frac{300 \cdot 10^6}{\sqrt{3} \cdot 115 \cdot 10^3 \cdot 0.95} \cdot \frac{120}{410} \cdot \frac{415}{20} \angle -\arccos 0.95 \text{ A} \quad \left(\underline{I} = \frac{\underline{S}^*}{\sqrt{3} \underline{U}^*} \right)$$

$$= 9628 \angle -18.19^\circ \text{ A} \approx 9.6 \angle -18.2^\circ \text{ kA}$$

Question 4

a) current and voltage at generator


$$U_n = 20 \text{ kV}$$

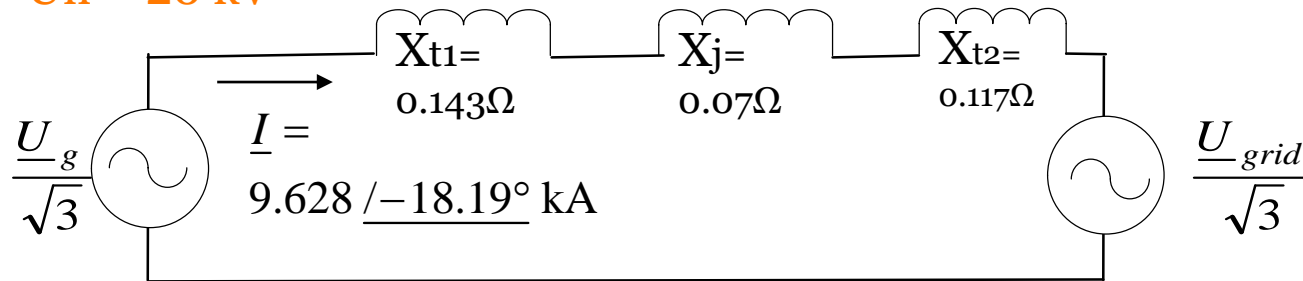

$$S_N = 400 \text{ MVA}$$

$$U_N = 20 \text{ kV}$$

$$x_d = 200 \%$$

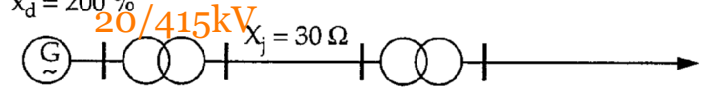

$$S_N = 420 \text{ MVA}$$

$$415/20 \text{ kV}$$

$$z_k = 15 \%$$

$$S_N = 400 \text{ MVA}$$

$$410/120 \text{ kV}$$

$$z_k = 12 \%$$

$$U = 115 \text{ kV}$$

$$P = 300 \text{ MW}$$

$$\cos \varphi = 0,95_{\text{ind}}$$

Grid voltage seen from the generator: $U_{grid} = 115 \cdot \frac{410}{120} \cdot \frac{20}{415} \text{ kV} = 18.936 \text{ kV}$

Generator terminal voltage:


$$\frac{U_g}{\sqrt{3}} = \frac{U_{grid}}{\sqrt{3}} + \underline{I} \cdot j(X_{t1} + X_j + X_{t2})$$

$$\begin{aligned} \underline{U}_g &= 18.936 / \underline{0}^\circ \text{ kV} + \sqrt{3} \cdot 9.628 / \underline{-18.19}^\circ \cdot (0.143 + 0.070 + 0.117) / \underline{90}^\circ \text{ kV} \\ &= (20.655 + j5.228) \text{ kV} = 21.306 / \underline{14.20}^\circ \text{ kV} \end{aligned}$$

$$\approx \underline{\underline{21.3 / 14.2^\circ \text{ kV}}}$$

Question 4

b) per unit approach

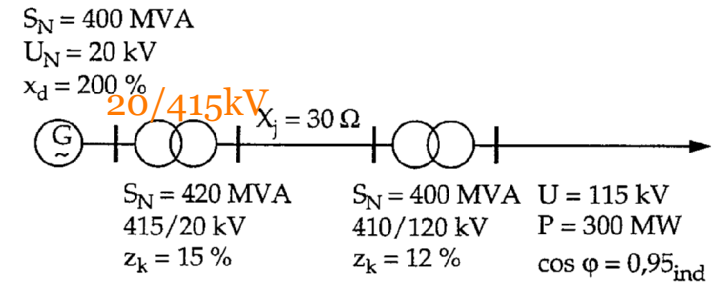

Let's choose base power: $S_b = 400 \text{ MVA}$



and base voltage level at line between the transformers: $U_b = 400 \text{ kV}$

The transformer ratios determine the other base voltages.


- 20-kV level: $U_b = 400 \text{ kV} \cdot \frac{20}{415} = 19.277 \text{ kV}$
- 110-kV level: $U_b = 400 \text{ kV} \cdot \frac{120}{410} = 117.073 \text{ kV}$

Question 4

b) per unit approach

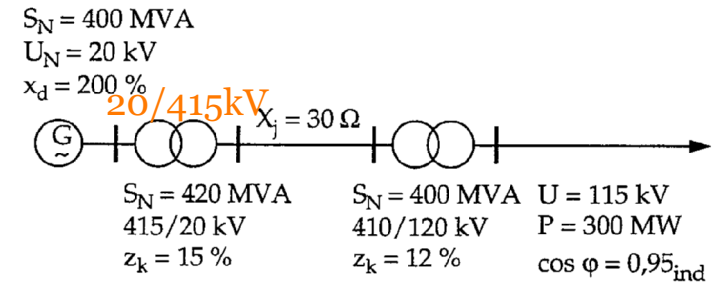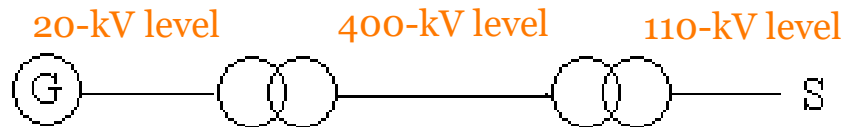

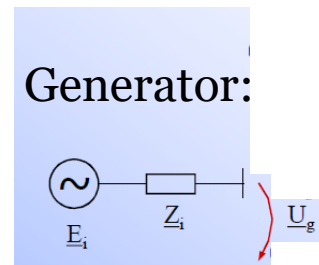20-kV level: has only generator X_d . Not needed because we are calculating generator terminal voltage which already includes voltage drop caused by X_d .



$$S_b = 400 \text{ MVA}, \quad U_b = 400 \cdot \frac{20}{415} = 19.277 \text{ kV}$$

400-kV level: $S_b = 400 \text{ MVA}, \quad U_b = 400 \text{ kV} \Rightarrow Z_b = \frac{400^2}{400} = 400 \Omega$


$$x_{t1} = \frac{z_{k1} \cdot \frac{U_N^2}{S_N}}{Z_b} = \frac{0.15 \cdot \frac{415^2}{420}}{400} = 0.154 \text{ pu}$$

$$x_j = \frac{X_j}{Z_b} = \frac{30}{400} = 0.075 \text{ pu}$$

$$x_{t2} = \frac{z_{k2} \cdot \frac{U_N^2}{S_N}}{Z_b} = \frac{0.12 \cdot \frac{410^2}{400}}{400} = 0.126 \text{ pu}$$

Question 4

b) per unit approach

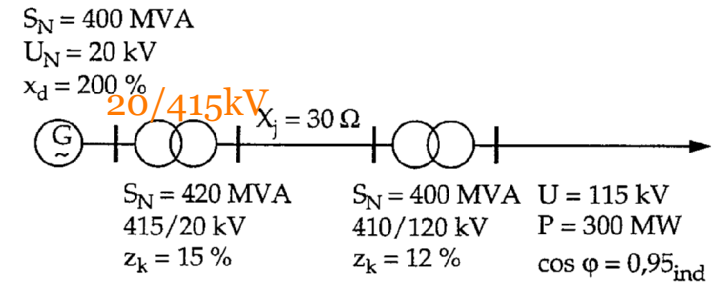

110-kV level: $S_b = 400 \text{ MVA}$, $U_b = 400 \frac{120}{410} = 117.073 \text{ kV}$ $\left(Z_b = \frac{117.073^2}{400} = 34.265 \Omega \right)$

$$P_{grid} = \frac{P_{grid}}{S_b} = \frac{300}{400} = 0.75$$

$$u_{grid} = \frac{U_{grid}}{U_b} = \frac{115}{117.073} = 0.982 \quad ; \text{choose } \underline{u}_{grid} = u_{grid} / 0^\circ$$



$$\underline{i} = \frac{P_{grid}}{u_{grid} \cdot \cos \varphi} / -\arccos 0.95 = \frac{0.75}{0.982 \cdot 0.95} / -\arccos 0.95 = 0.804 / -18.19^\circ$$

$$\underline{I} = \underline{i} \cdot \underline{I}_b = \underline{i} \cdot \frac{S_b}{\sqrt{3} U_b} = 0.804 / -18.19^\circ \cdot \frac{400 \cdot 10^6}{\sqrt{3} \cdot 19.277 \cdot 10^3} \text{ A} \approx 9.6 \angle -18.2^\circ$$

$$I = \underline{9.6 \text{ kA}}$$

Question 4

b) per unit approach

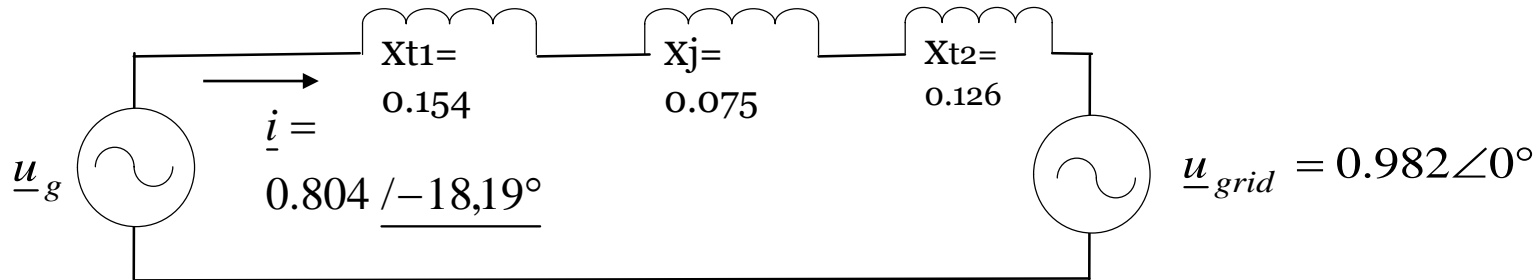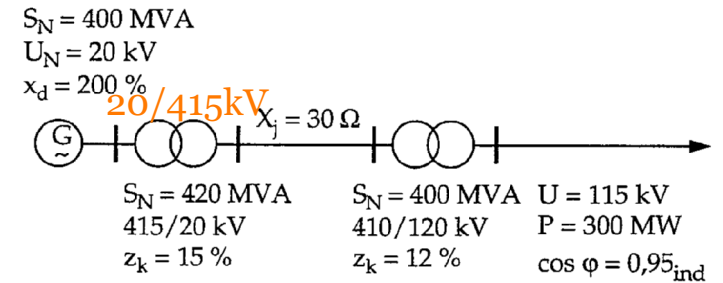

$$\underline{u}_g = \underline{u}_{grid} + \underline{i} \cdot j(x_{t1} + x_j + x_{t2})$$

$$= 0.982 \angle 0^\circ + 0.804 \angle -18,19^\circ \cdot j(0.154 + 0.075 + 0.126)$$

$$= 1.105 \angle 14,21^\circ$$

$$\underline{U}_g = \underline{u}_g \cdot U_{b20kV} = 1.105 \angle 14,21^\circ \cdot 19.277 \text{ kV} \approx 21.3 \angle 14,2^\circ \text{ kV}$$

$$U_g \approx 21.3 \text{ kV}$$