

## DC MACHINES

1. A dc machine (6 kW, 120 V, 1200 rpm) has the following magnetization characteristics at 1200 rpm.

$I_f$ [A]	0.0	0.1	0.2	0.3	0.4	0.5	0.6	0.8	1.0	1.2
$E_a$ [V]	5	20	40	60	79	93	102	114	120	125

The machine parameters are  $R_a=0.2 \Omega$ ,  $R_{fw}=100 \Omega$ . The machine is driven at 800 rpm and is separately excited. The field current is adjusted at  $I_f=0.8$  A. A load resistance  $R_L=2\Omega$  is connected to the armature terminals. Neglect armature reaction fields.

- a) Determine the quantity  $K_a\Phi$  for the machine.
  - b) Determine  $E_a$  and  $I_a$ .
  - c) Determine the torque  $T$  and load power  $P_L$ .
2. The dc machine in the previous problem has a field control resistance whose value can be changed from 0 to 150  $\Omega$ . The machine is driven at 1200 rpm. The machine is separately excited and the field winding is supplied from a 120 V supply.
- a) Determine the maximum and minimum values of the no-load terminal voltage.
  - b) The field control resistance ( $R_{fc}$ ) is adjusted to provide a no-load terminal voltage of 120V. Determine the value of  $R_{fc}$ . Determine the terminal voltage at full load for no armature reaction an also if  $I_{f(AR)}=0.1$  A.
3. The dc machine in the first problem is separately excited. The machine is driven at 1200 rpm and operates as a generator. The rotational loss 400 W at 1200 rpm and the rotational loss is proportional to speed.
- a) For field current of 1.0A, with the generator delivering rated current, determine the terminal voltage, the output power and the efficiency.
  - b) Repeat part a) if the generator is driven at 1500 rpm.

## DC MACHINES (2)

4. A dc shunt generator (20kW, 200V, 1800rpm) has  $R_a=0.1\Omega$ ,  $R_{fw}=150\ \Omega$ . Assume that  $E_a=U_t$  at no load. The machine is self-excited. Data for the magnetization curve at 1800 rpm are:

$I_f$ [A]	0.0	0.125	0.25	0.5	0.625	0.75	0.875	1.0	1.25	1.5
$E_a$ [V]	5	33.5	67	134	160	175	190	200	214	223

- a) At full-load condition,  $U_t=U_t$  (rated),  $I_a=I_a$  (rated),  $I_f=1.25$  A. Determine the value of the field control resistance ( $R_{fc}$ ).
  - b) Determine the electromagnetic power and torque developed at full-load condition.
  - c) Determine the armature reaction effect in equivalent field amperes ( $I_{f(AR)}$ ) at full load.
  - d) Determine the maximum value of the armature current assuming that  $I_{f(AR)}$  is proportional to  $I_a$ .
5. A dc shunt motor is connected to a 230V supply and delivers power to a load drawing an armature current of 200A and running at a speed of 1200rpm. The armature resistance is  $R_a=0.2\Omega$ .
- a) Determine the value of the generated voltage at this load condition.
  - b) Determine the value of the load torque. The rotational losses are 500W.
  - c) Determine the efficiency of the motor if the field circuit resistance is 115 $\Omega$ .
6. A dc shunt machine (10kW, 250 V, 1200 rpm) has  $R_a=0.25\Omega$ . The machine is connected to a 250V dc supply, draws rated armature current and rotates at 1200rpm.
- a) Determine the generated voltage, the electromagnetic power developed and the torque developed.
  - b) The mechanical load on the motor shaft is thrown off and the motor draws 4A armature current. Determine the rotational loss and the speed assuming no armature reaction.