

Previous Topics

Basic Amplifiers

- Biasing schemes



Low-Noise Amplifiers

- Concepts
- Resistively terminated
- Parallel feed-back
- Common gate
- Inductively degenerated
- Wide bandwidth - - low noise ?? → Noise cancelling

Power Amplifiers

- Concepts
- Current mode: A, B, C
- Switch mode: D, E, F

Mixers

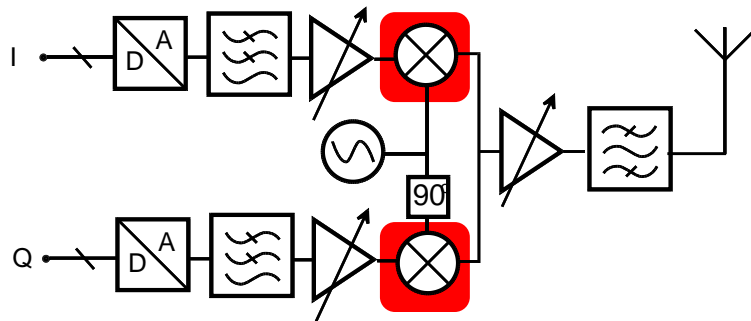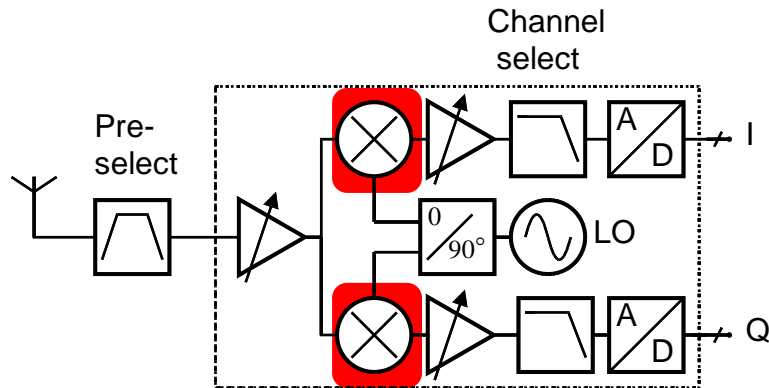

Focus on specific RF IC mixers

- Down-conversion (RX)
- Up-conversion (TX)


TX and RX mixers are quite similar
→ RX only for simplicity

- Active mixers (Gilbert cell)
- Passive mixers
- Advanced cases / examples

Exercises & Homework

- Self-access learning material
- CAD-exercise
- Homeworks

Ideal Multiplier / Mixer

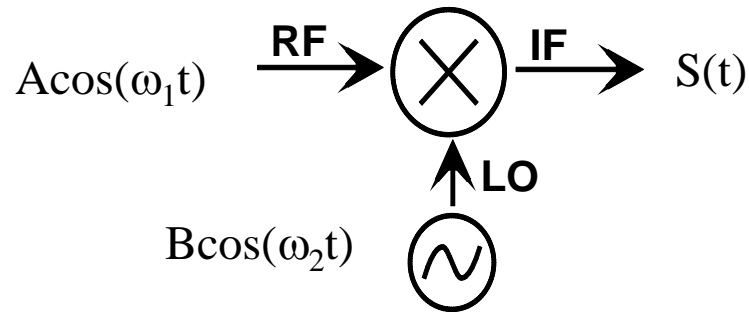


$$S(t) = A \cos(\omega_1 t) B \cos(\omega_2 t) = \frac{AB}{2} (\cos(\omega_1 - \omega_2)t + \cos(\omega_1 + \omega_2)t)$$

up-conversion

down-conversion

Ideal Multiplier / Mixer

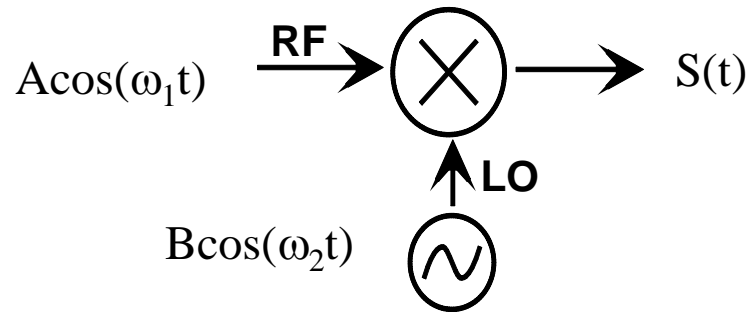


$$S(t) = A \cos(\omega_1 t) B \cos(\omega_2 t) = \frac{AB}{2} (\cos(\omega_1 - \omega_2)t + \cos(\omega_1 + \omega_2)t)$$

up-conversion

down-conversion

”mixing” = multiplication in time-domain = frequency shift in frequency domain

Any nonlinear element can act as a mixer

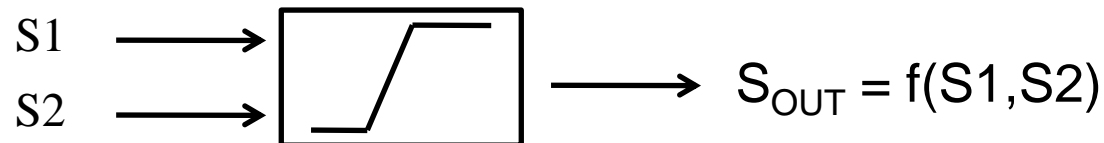

Reminder: IIP3 Analysis

- Nonlinear circuit with 2nd and 3rd order nonlinearity


$$y(t) = \alpha_1 x(t) + \alpha_2 x^2(t) + \alpha_3 x^3(t)$$

- Inputs: $A_1 \cos(\omega_1 t) + A_2 \cos(\omega_2 t) \rightarrow$ Output


$$\begin{aligned} v_{out}(t) = & \frac{1}{2} \alpha_2 (A_1^2 + A_2^2) + \left(\alpha_1 A_1 + \alpha_3 \frac{3A_1^3 + 6A_1 A_2^2}{4} \right) \cos(\omega_1 t) + \left(\alpha_1 A_2 + \alpha_3 \frac{3A_2^3 + 6A_1^2 A_2}{4} \right) \cos(\omega_2 t) \\ & + \frac{1}{2} \alpha_2 A_1^2 \cos(2\omega_1 t) + \frac{1}{2} \alpha_2 A_2^2 \cos(2\omega_2 t) + \frac{1}{4} \alpha_3 A_1^3 \cos(3\omega_1 t) + \frac{1}{4} \alpha_3 A_2^3 \cos(3\omega_2 t) \\ & + \alpha_2 A_1 A_2 [\cos(\omega_1 t - \omega_2 t) + \cos(\omega_1 t + \omega_2 t)] + \frac{3}{4} \alpha_3 A_1^2 A_2 \cos(2\omega_1 t + \omega_2 t) + \frac{3}{4} \alpha_3 A_1 A_2^2 \cos(\omega_1 t + 2\omega_2 t) \\ & + \frac{3}{4} \alpha_3 A_1^2 A_2 \cos(2\omega_1 t - \omega_2 t) + \frac{3}{4} \alpha_3 A_1 A_2^2 \cos(2\omega_2 t - \omega_1 t) \end{aligned}$$

Concepts

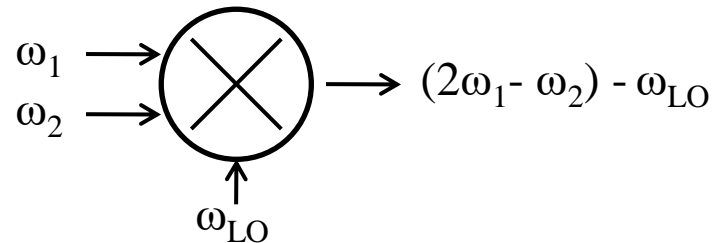- Conversion gain = V_{IF} / V_{RF}
- Noise Figure
 - Single-sideband (SSB)
 - Double-sideband (DSB)
- Linearity
 - IIP2
 - IIP3; in-band / out-of-band
- Compression point (ICP)
- Port-to-port isolation




Mixer Noise Figure; SSB

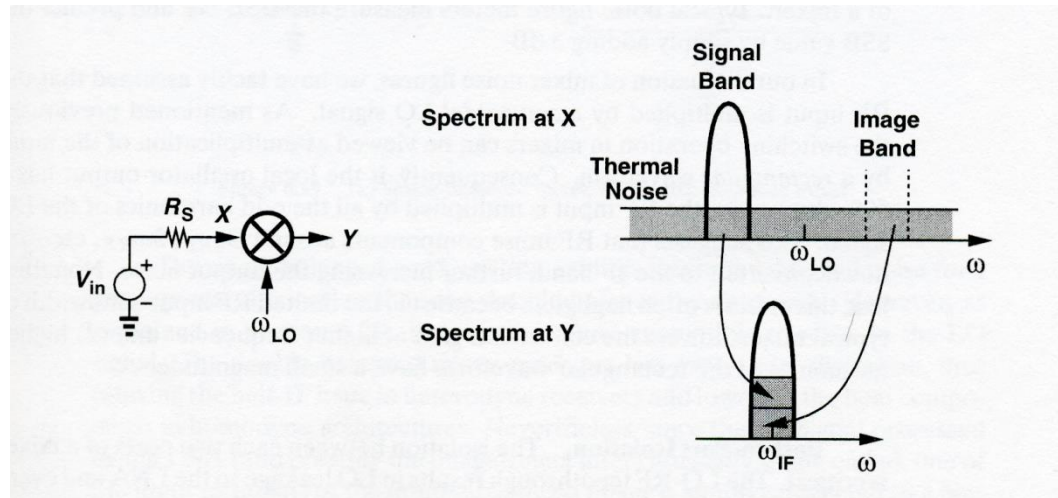

- In single-sideband mixer ($f_{RF} \neq f_{LO}$)
 - Noise is on both sidebands
 - Signal is on ONE sideband
- The NF of "noiseless SSB mixer" is 3 dB
- Heterodyne receivers: image filter before mixer

Mixer Noise Figure; DSB

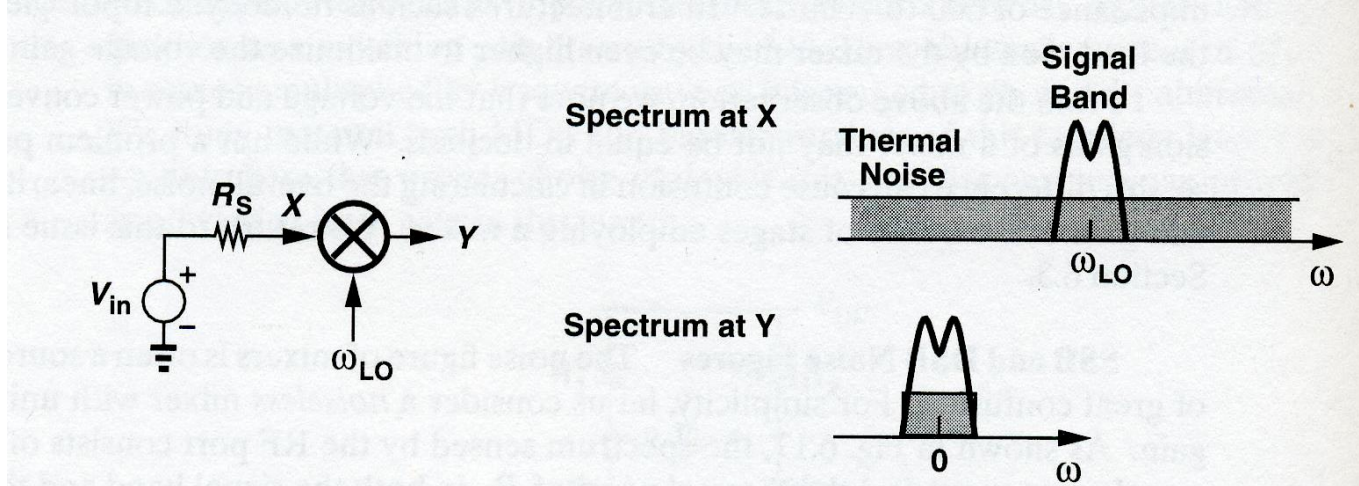

- In double-sideband mixer
 - Noise is on both sidebands
 - Signal is on both sideband
- The NF of "noiseless DSB mixer" is 0 dB
- Valid parameter for **direct-conversion receivers**

Simple Mixer Example: MOSFET Drain Current

MOSFET drain current with two input signals:

$$I_{DS} = \frac{K'_n W}{2L} (V_{GS0} - V_T + v_{RF} + v_{LO})^2$$
$$= \frac{K'_n W}{2L} \left[(V_{GS0} - V_T)^2 - 2(V_{GS0} - V_T)(v_{RF} + v_{LO}) + v_{RF}^2 + v_{LO}^2 + 2v_{RF}v_{LO} \right]$$


Simple Mixer Example: MOSFET Drain Current

MOSFET drain current with two input signals:



$$I_{DS} = \frac{K'_n W}{2L} (V_{GS0} - V_T + v_{RF} + v_{LO})^2$$
$$= \frac{K'_n W}{2L} \left[(V_{GS0} - V_T)^2 - 2(V_{GS0} - V_T)(v_{RF} + v_{LO}) + v_{RF}^2 + v_{LO}^2 + 2v_{RF}v_{LO} \right]$$

The output includes


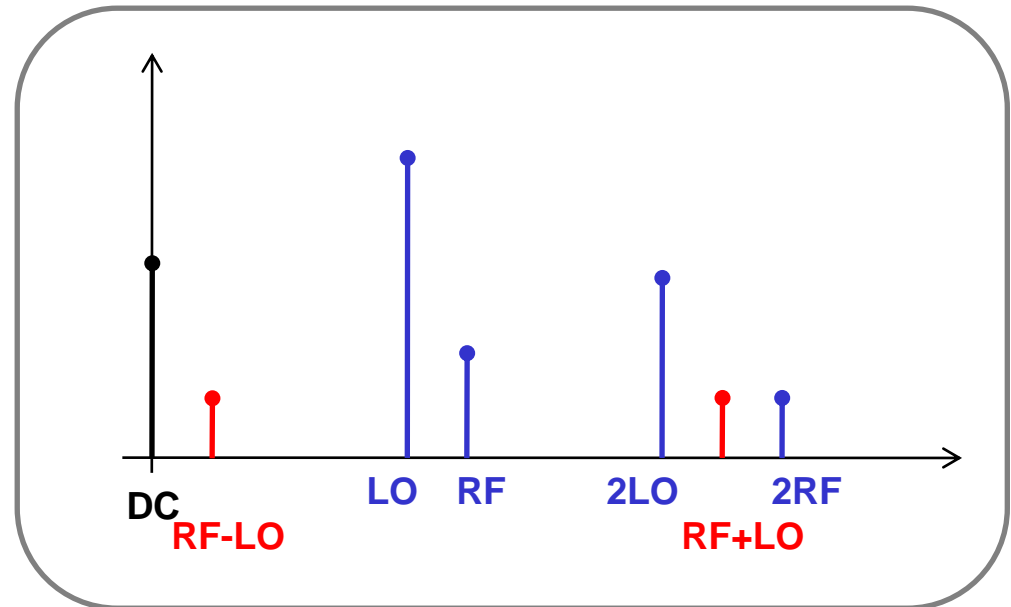
- DC component
- Feedthrough components
- Distortion components
- Mixing product components



Example: MOSFET Drain Current

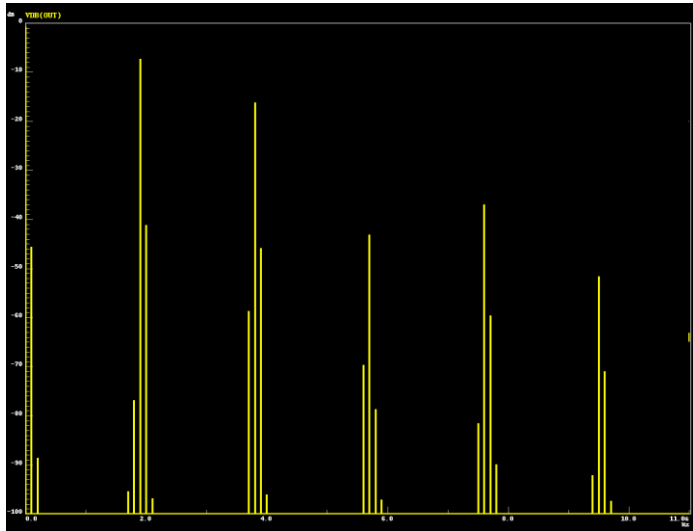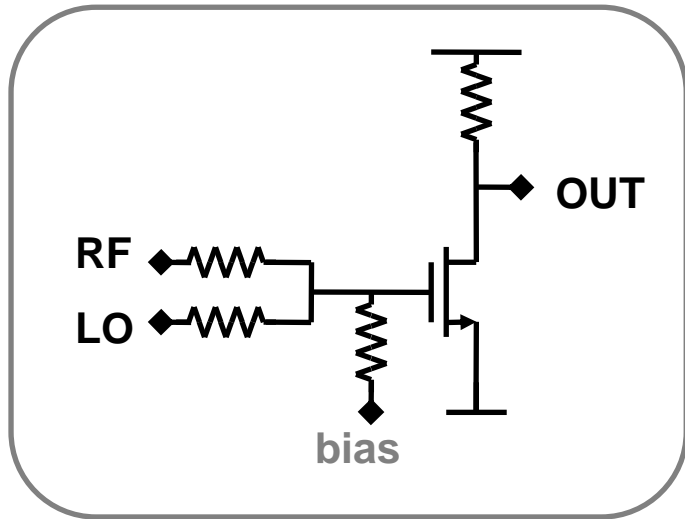



Example: MOSFET Drain Current

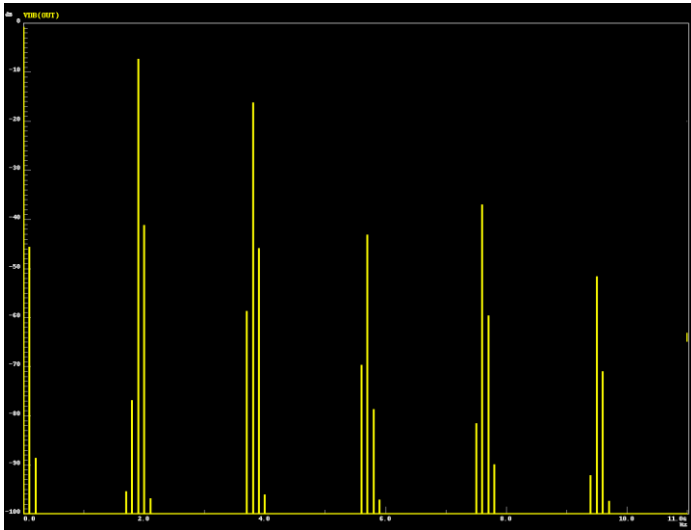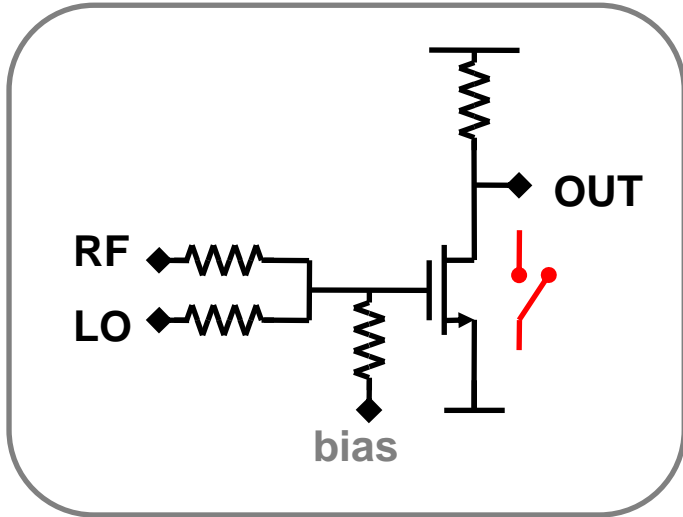



Three "modes"

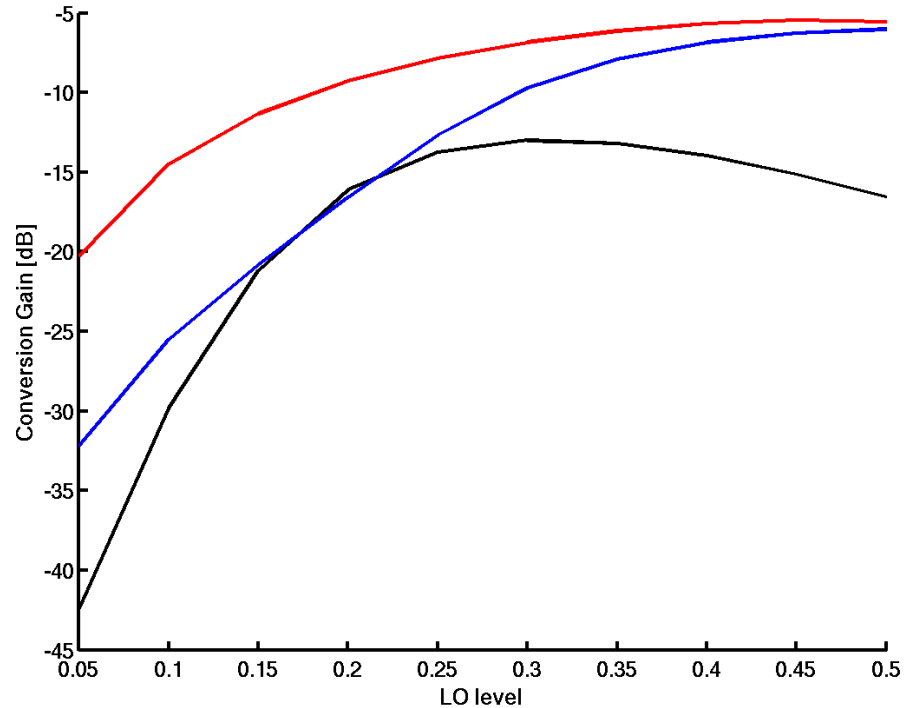- Good amplifier, bias=0.6V
- **Switch, "class-C", bias=0.4V**
- **Resistive mixer, bias=0.8V**




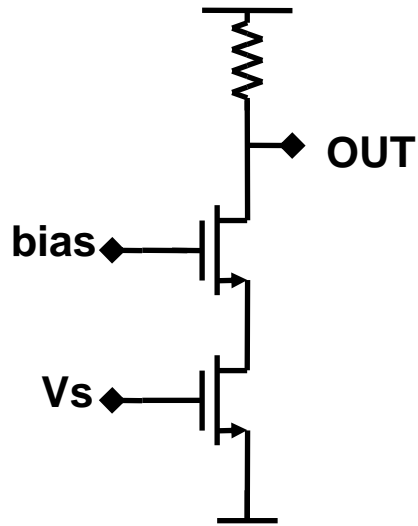



Cascode Amplifier → Mixer

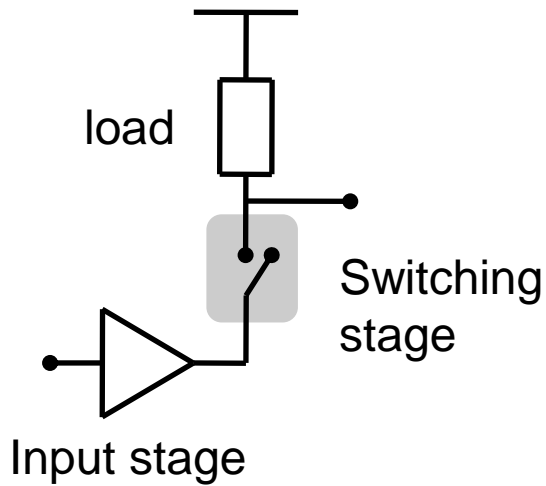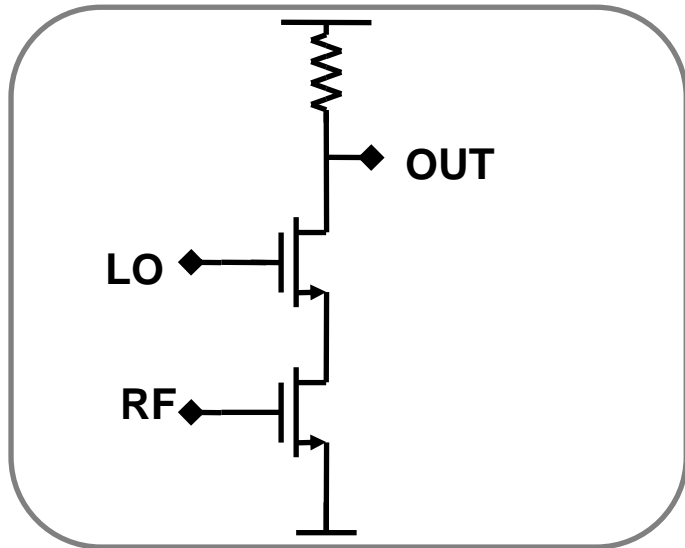


Cascode Amplifier → Mixer

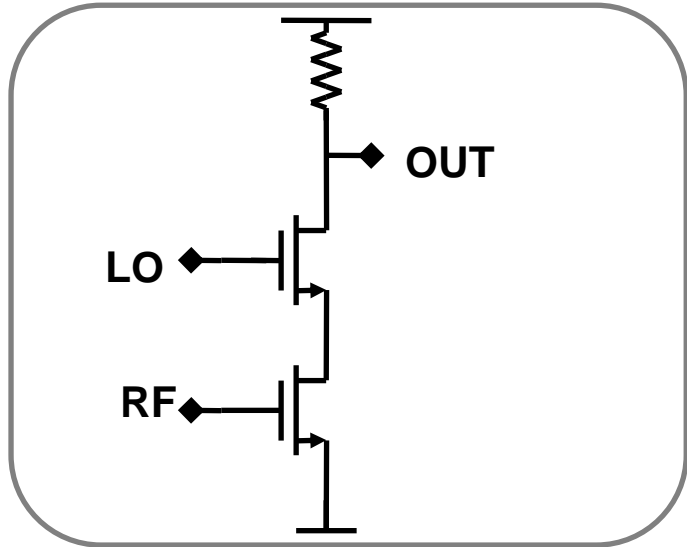

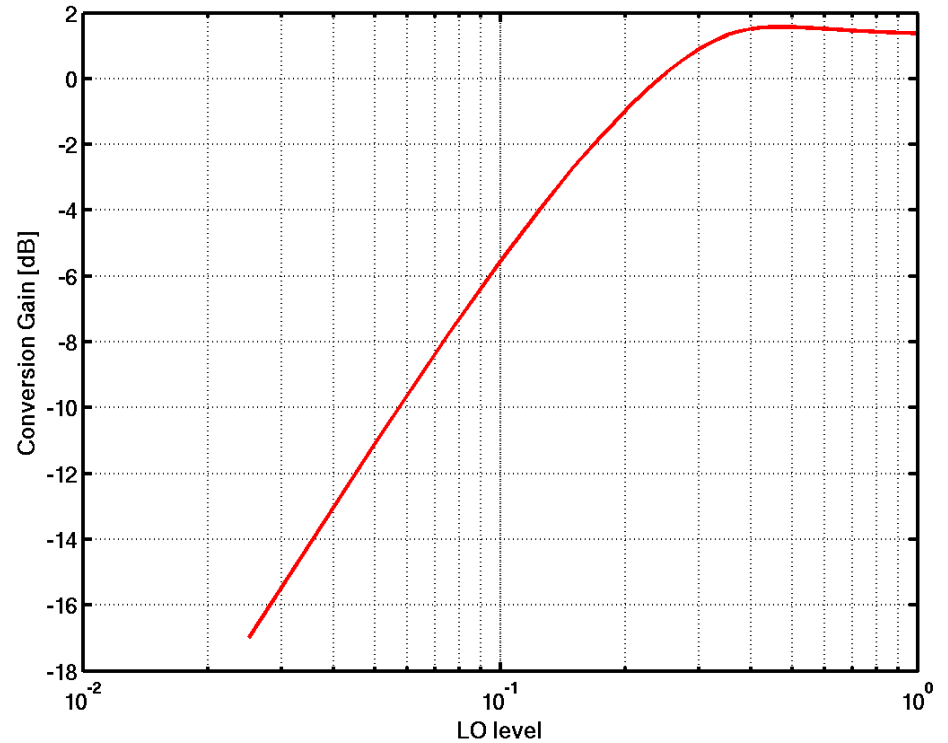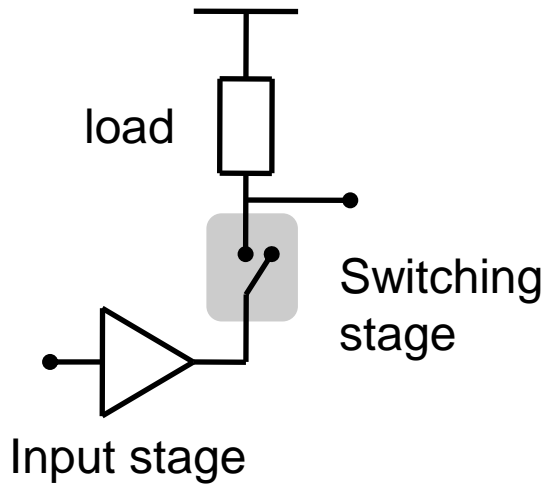- Active mixer = conversion gain > 0
- Poor port-to-port isolation
→ *What to do ?*




Single-Balanced Mixer

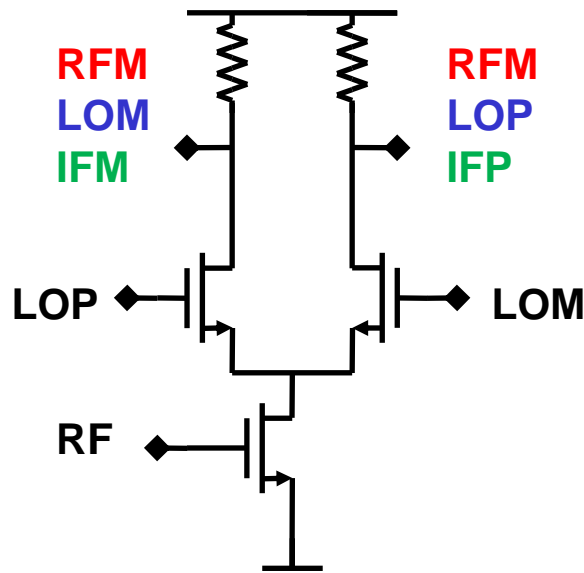

- Differential LO signal → differential output w/o RF
- Rest of performance essentially same as previously
- Differential LO cancels out RF; how to cancel LO leakage ?


Double-Balanced Mixer (derivation)

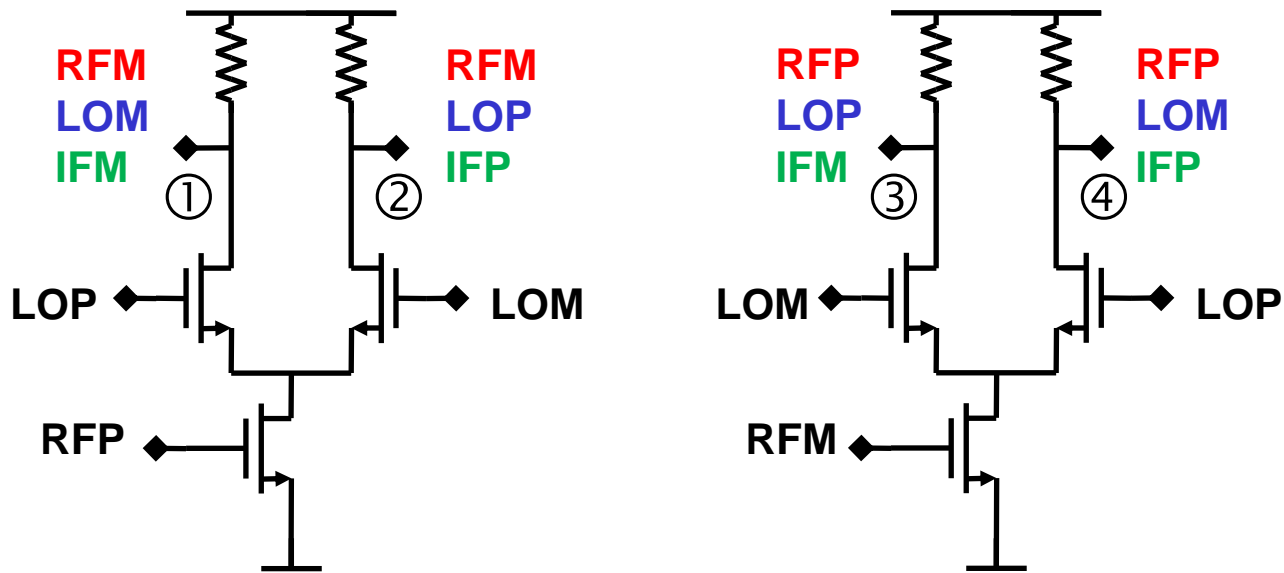

- Differential LO signal → differential output w/o RF
- Differential RF signal → differential output w/o LO

How to combine ① ② ③ ④ ?


Double-Balanced Mixer (derivation)

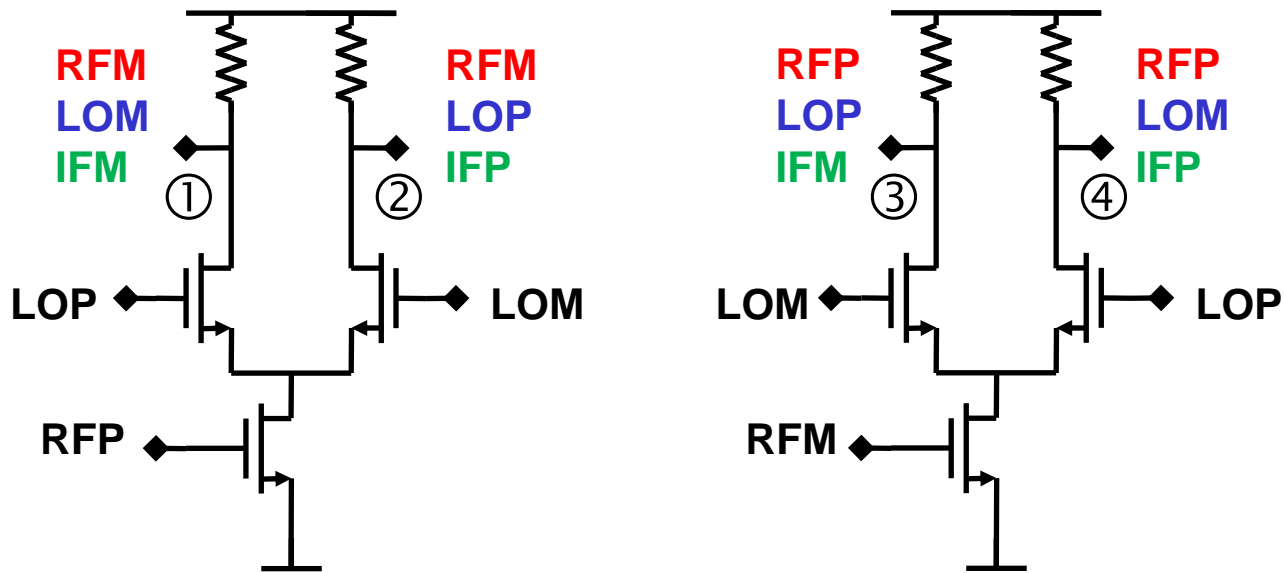

- Differential LO signal \rightarrow differential output w/o RF
- Differential RF signal \rightarrow differential output w/o LO


How to combine ① ② ③ ④ ? \rightarrow $(\text{①} + \text{③}) - (\text{②} + \text{④})$

Double-balanced Mixer (derivation 2)

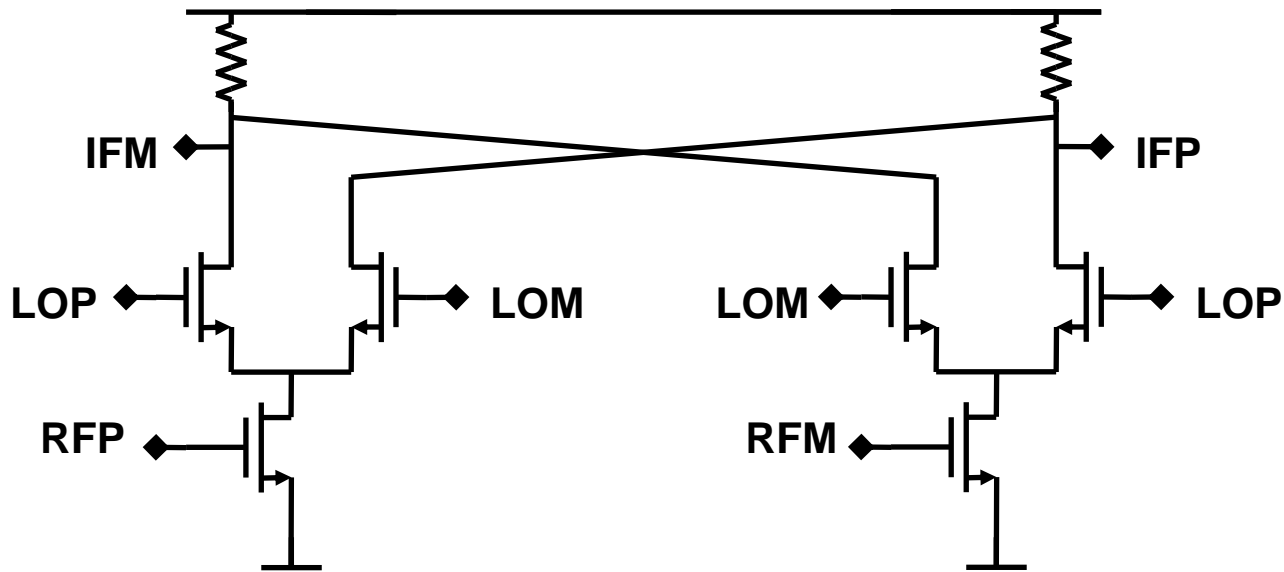


- Independent RF transistors have poor matching
→ Differential pair helps

Gilbert Cell Mixer

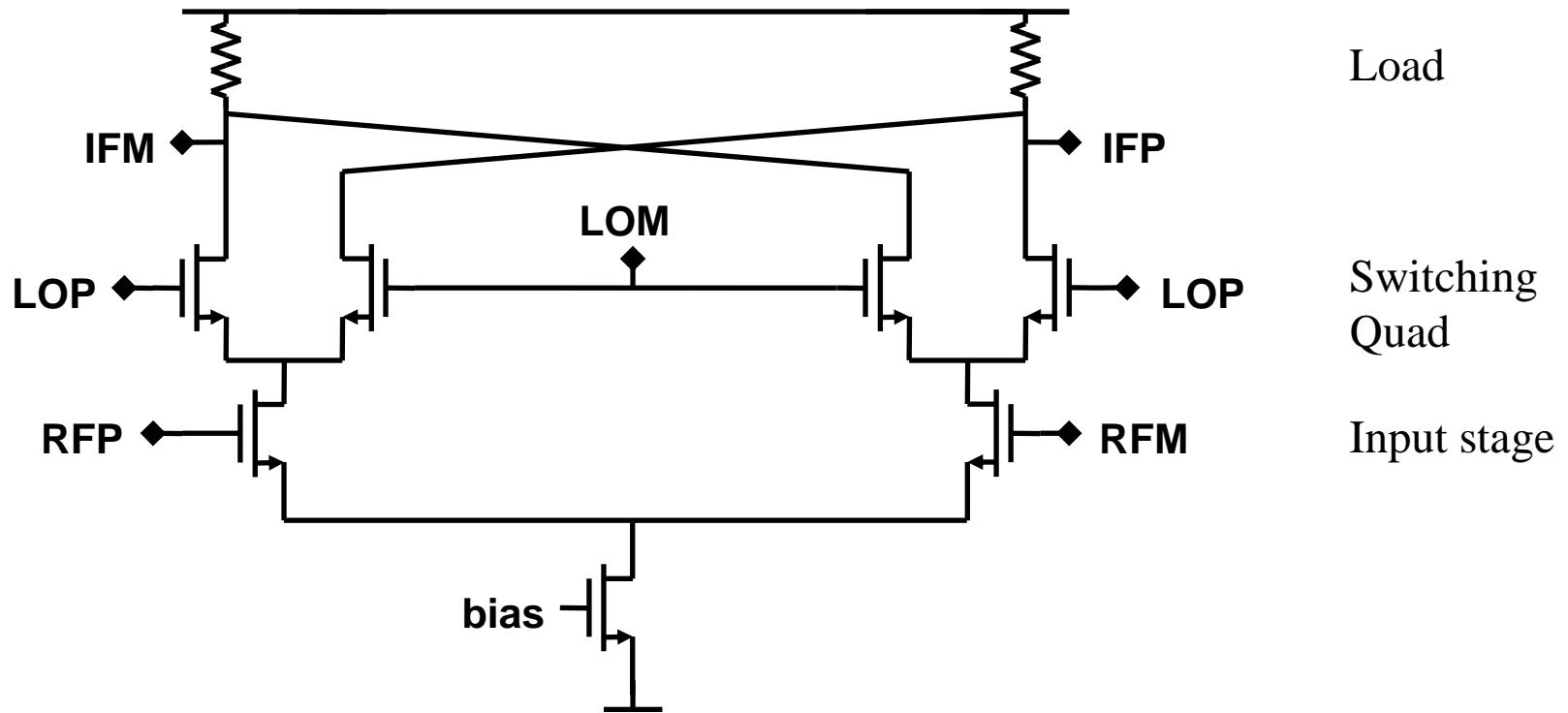

Gilbert cell mixer was the work horse of RF IC transceivers. It dominated until some problems appeared ...

Gilbert Cell Mixer

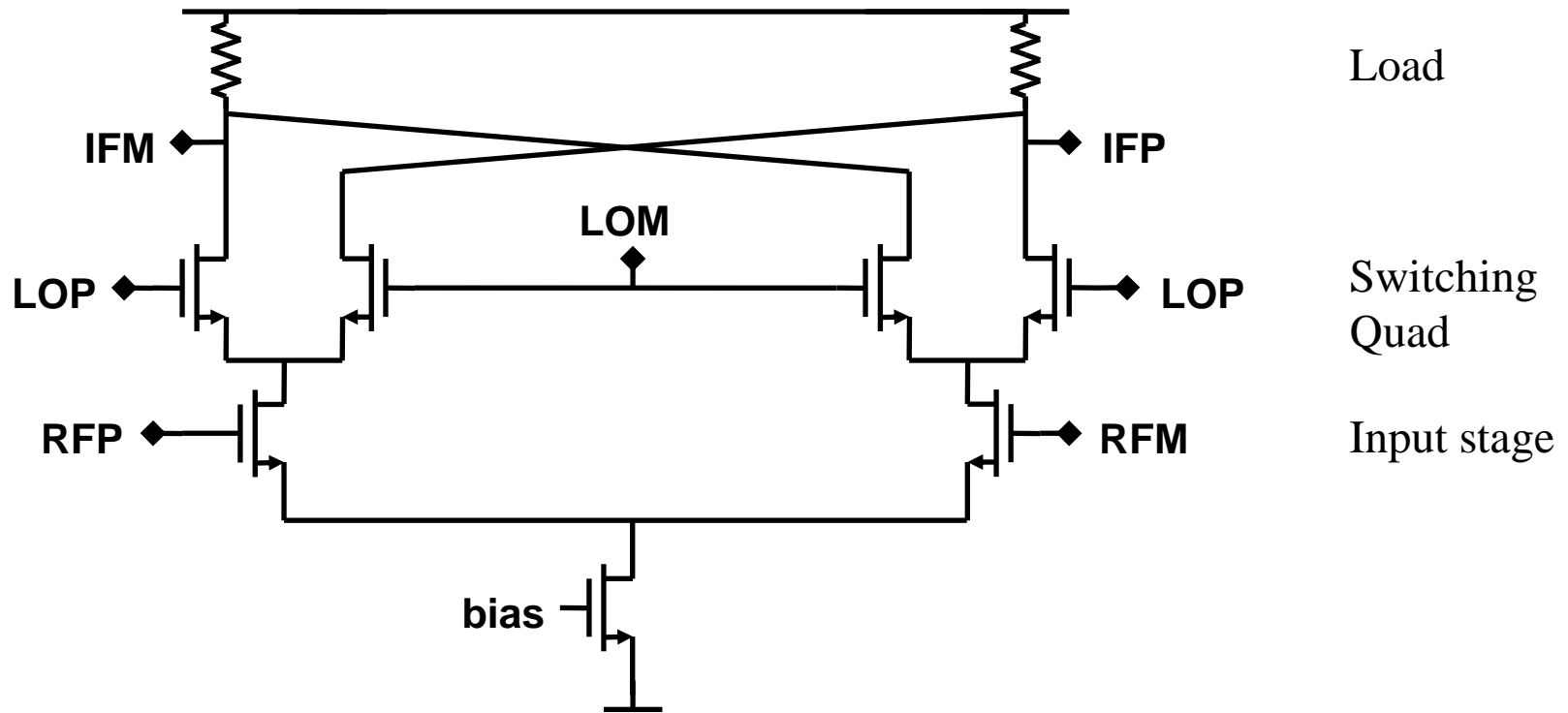


Gilbert cell mixer was the work horse of RF IC transceivers. It dominated until some problems appeared ...



This circuit needs a high supply voltage.

Low-voltage versions have poor characteristics.

Gilbert Mixer, Examples

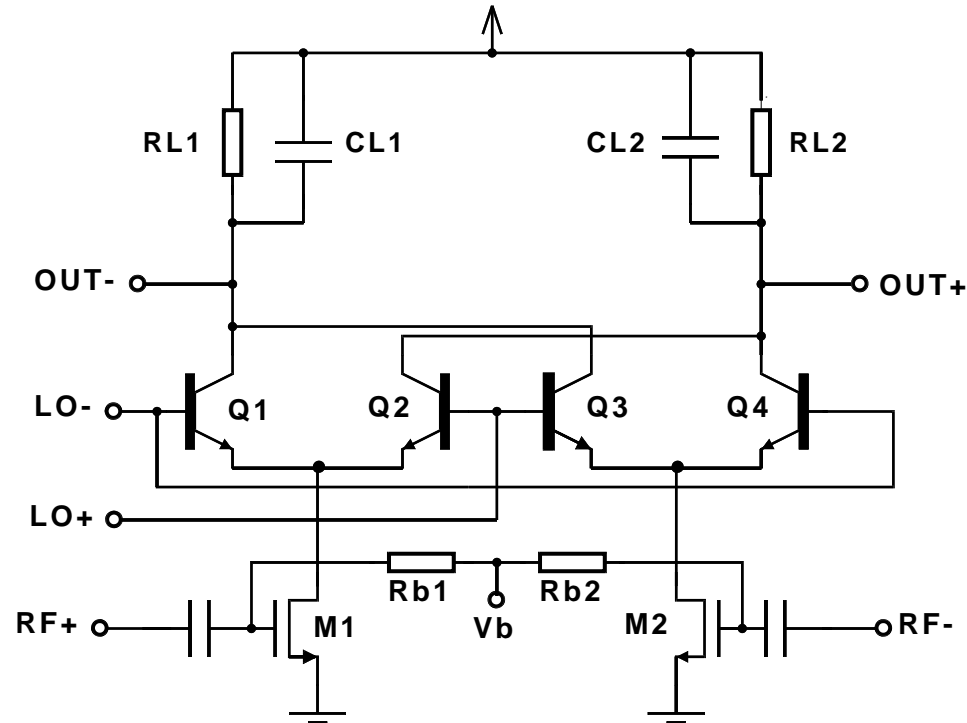


Gilbert Mixer, Examples

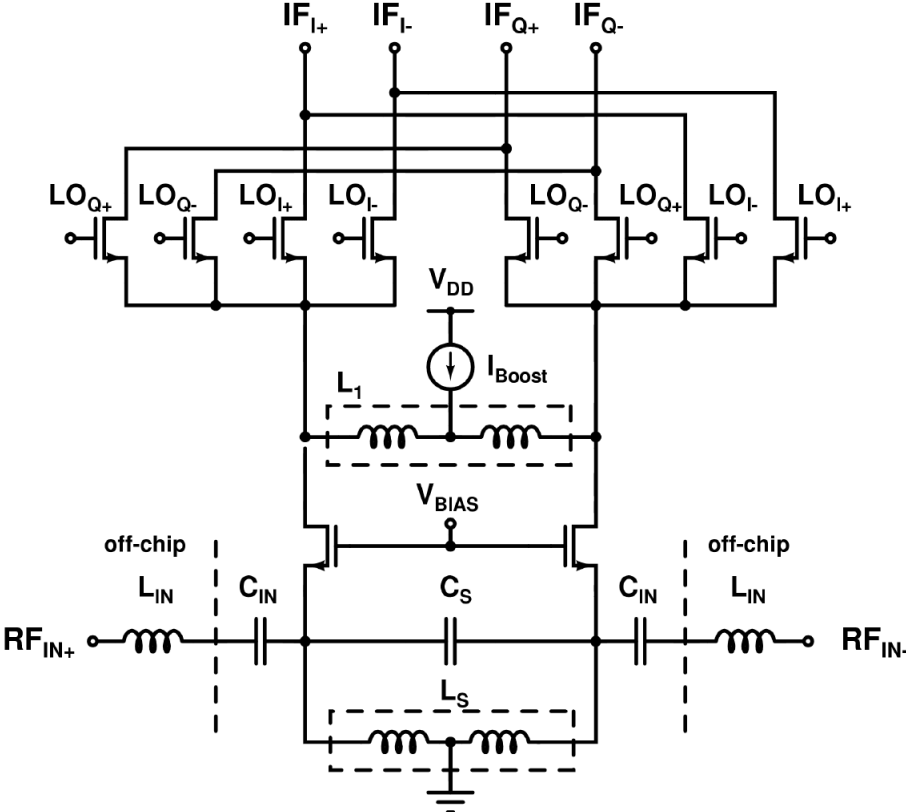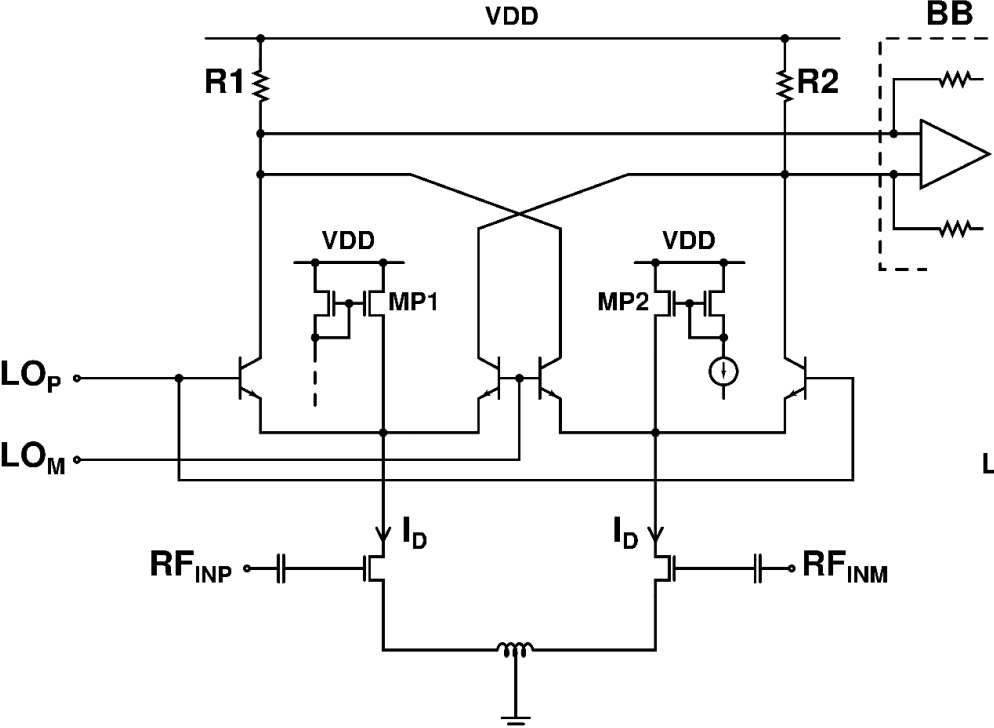


Passive Mixers

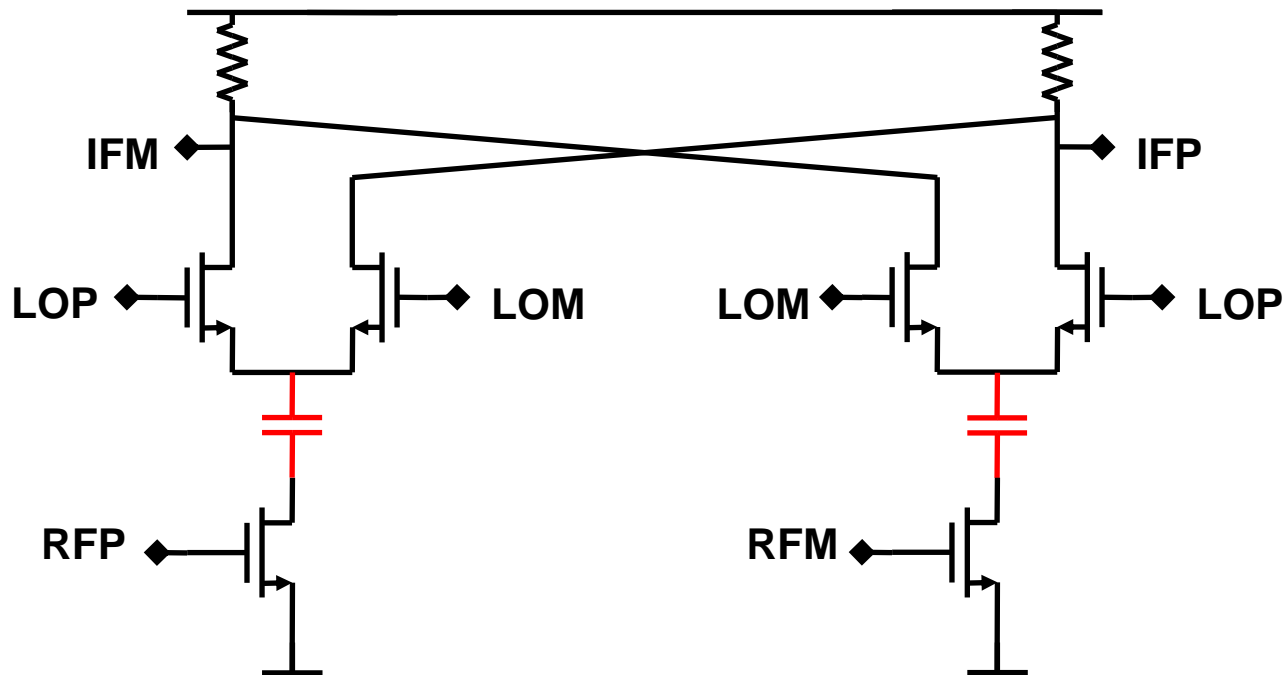WHY ? Demand for **low supply voltage** and high linearity
→ Gilbert cell and its variants do not work well




If we ignore DC bias matters, would this work ?

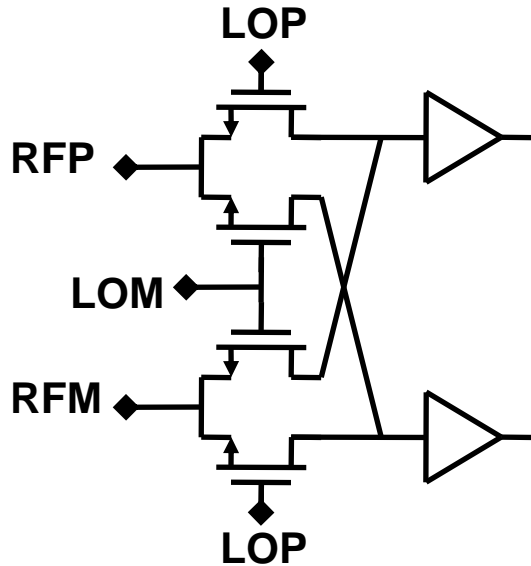Voltage-Mode / Current-Mode Passive Mixer




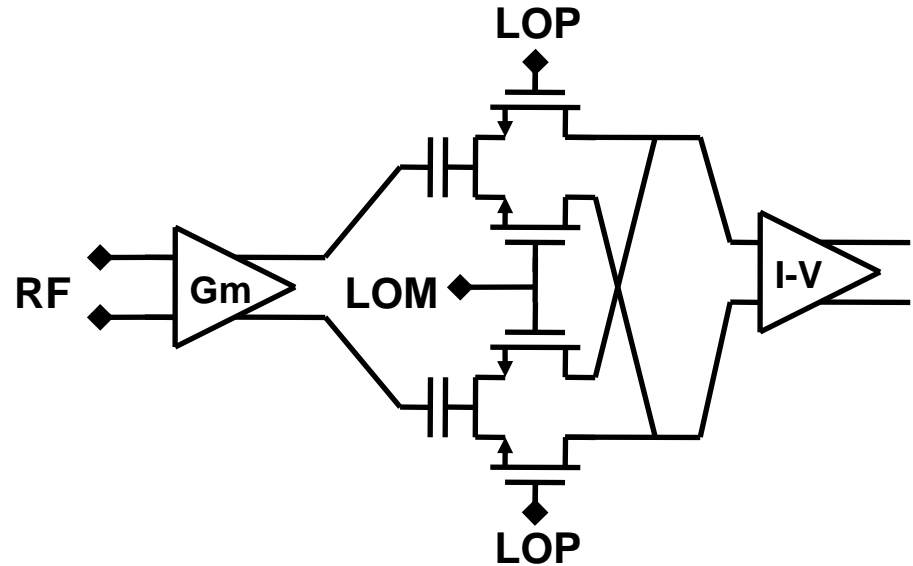
- Input $V_{in} \rightarrow$ output V_{out}
- $R_{DS(ON)} \ll Z_{in}$
 \rightarrow high imp output buffer



- Input $I_{in} \rightarrow$ output I_{out}
- Requires I-V converter (TIA)
 \rightarrow low imp output buffer

Identification of voltage or current-mode mixer may be difficult and even unnecessary; Main feature is that **no DC current flows** in the mixing FETs

Active / Passive Mixer

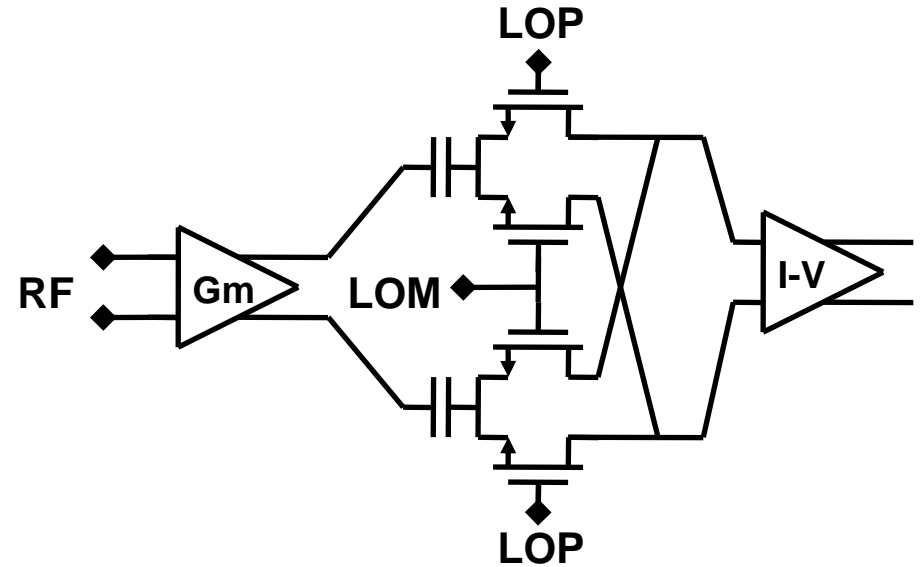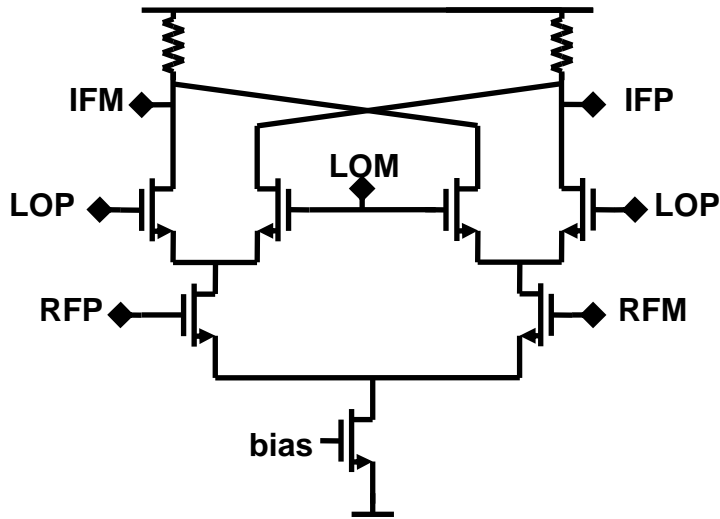


Passive mixer is just a "folded" version of active mixer


- In an active mixer DC current flows through the switching quad
→ CG FETs provide gain but also contribute to noise

Principles


”current re-use”

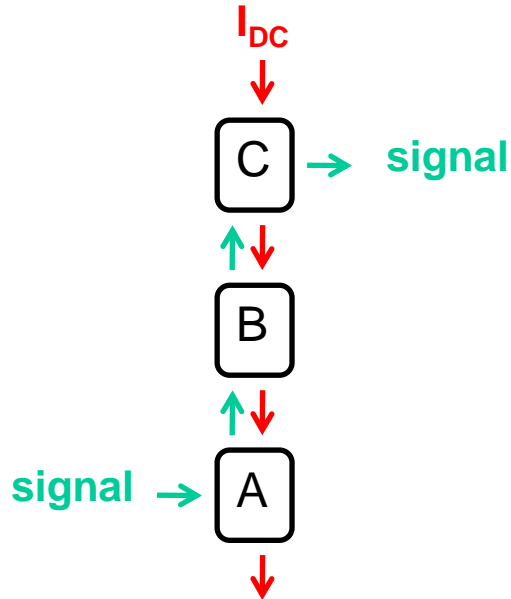


”low voltage”

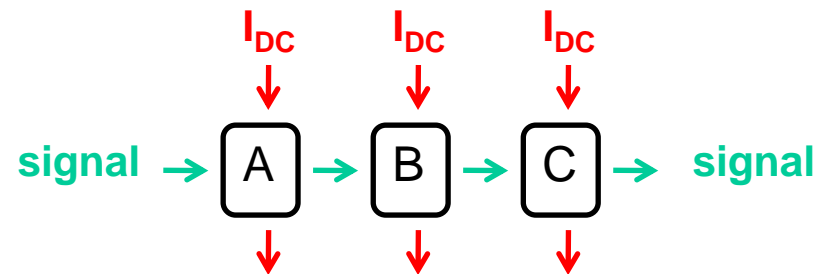

Passive Mixer, Use Case 1

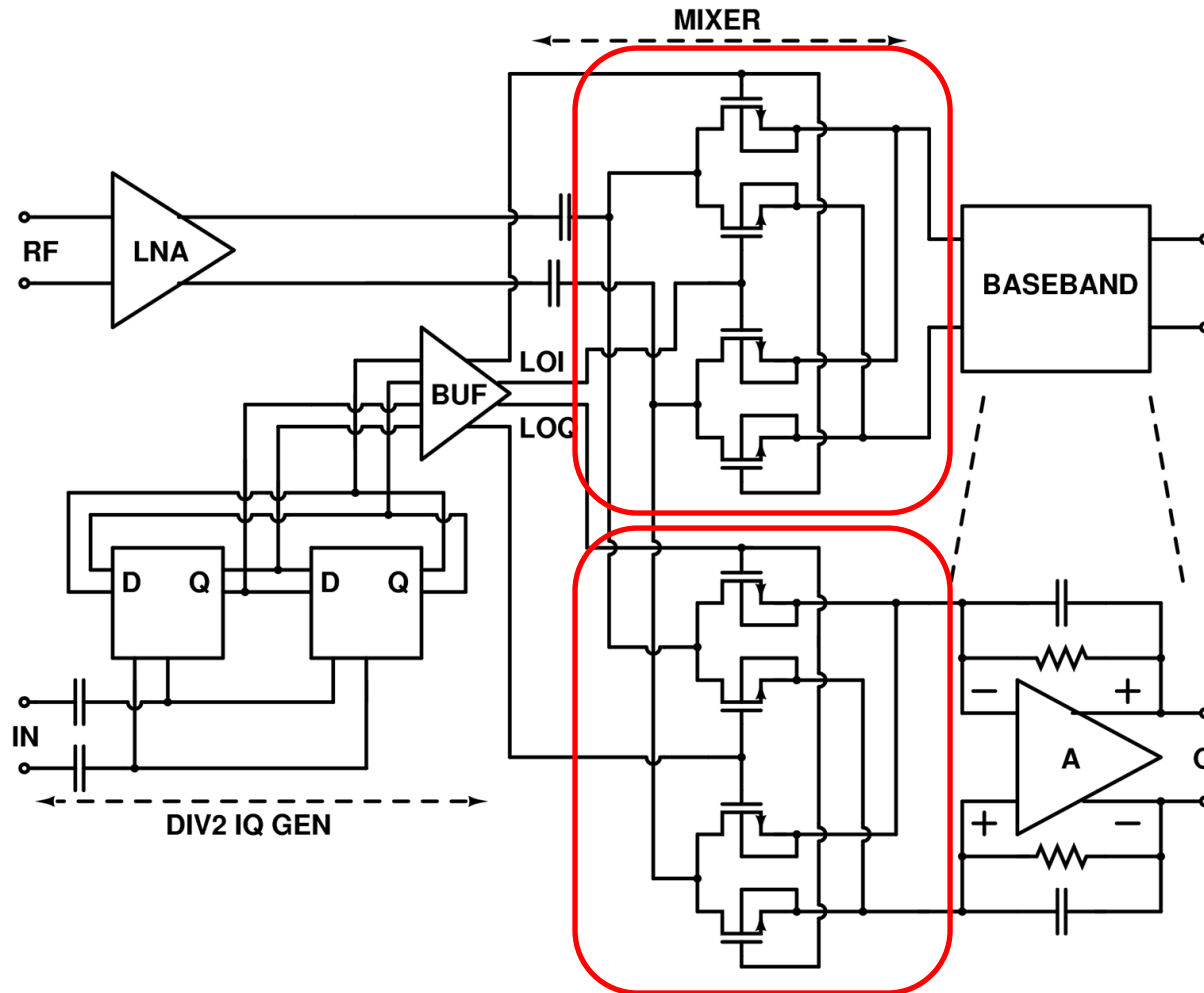


Passive Mixer, Use Case 2

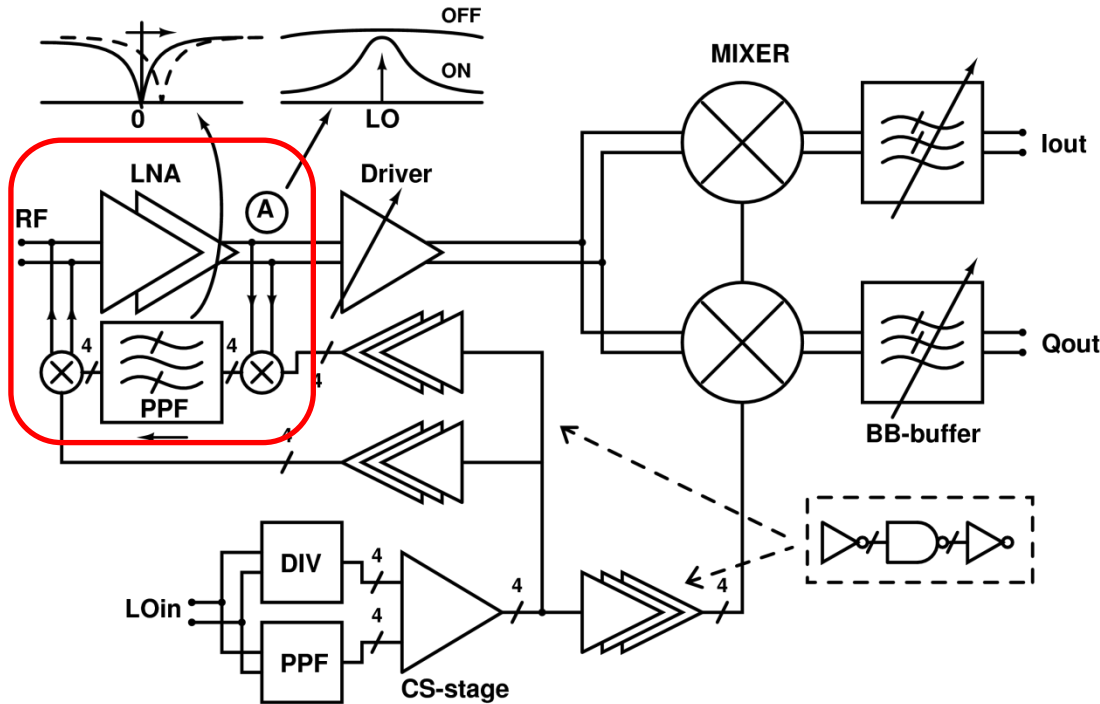


	TIF OFF/ON	TIF OFF/ON	TIF OFF/ON
LO Freq (GHz)	2.4	4.0	5.3
Gain (dB)	42/40	43/41	42/40
IIP3 (dBm)	-11/-5	-13/-5	-11/-7
Blocker ICP (dBm)	-20/-15	-23/-16	-23/-18
NF (dB)	4.3/5.8	3.2/5.7	3.9/5.9
S11 < -10dB (GHz)	2.5-5.5		
LO leak (dBm)	-85/-63	-56/-54	-58/-56
Idc (mA)	45/53	44/56	46/58
Gain Adjustment (dB)	15		
BB bandwidth (MHz)	5-50		
Active area (mm ²)	0.25		
Technology	1.2V 65nm CMOS		



Passive Mixer, Use Case 2

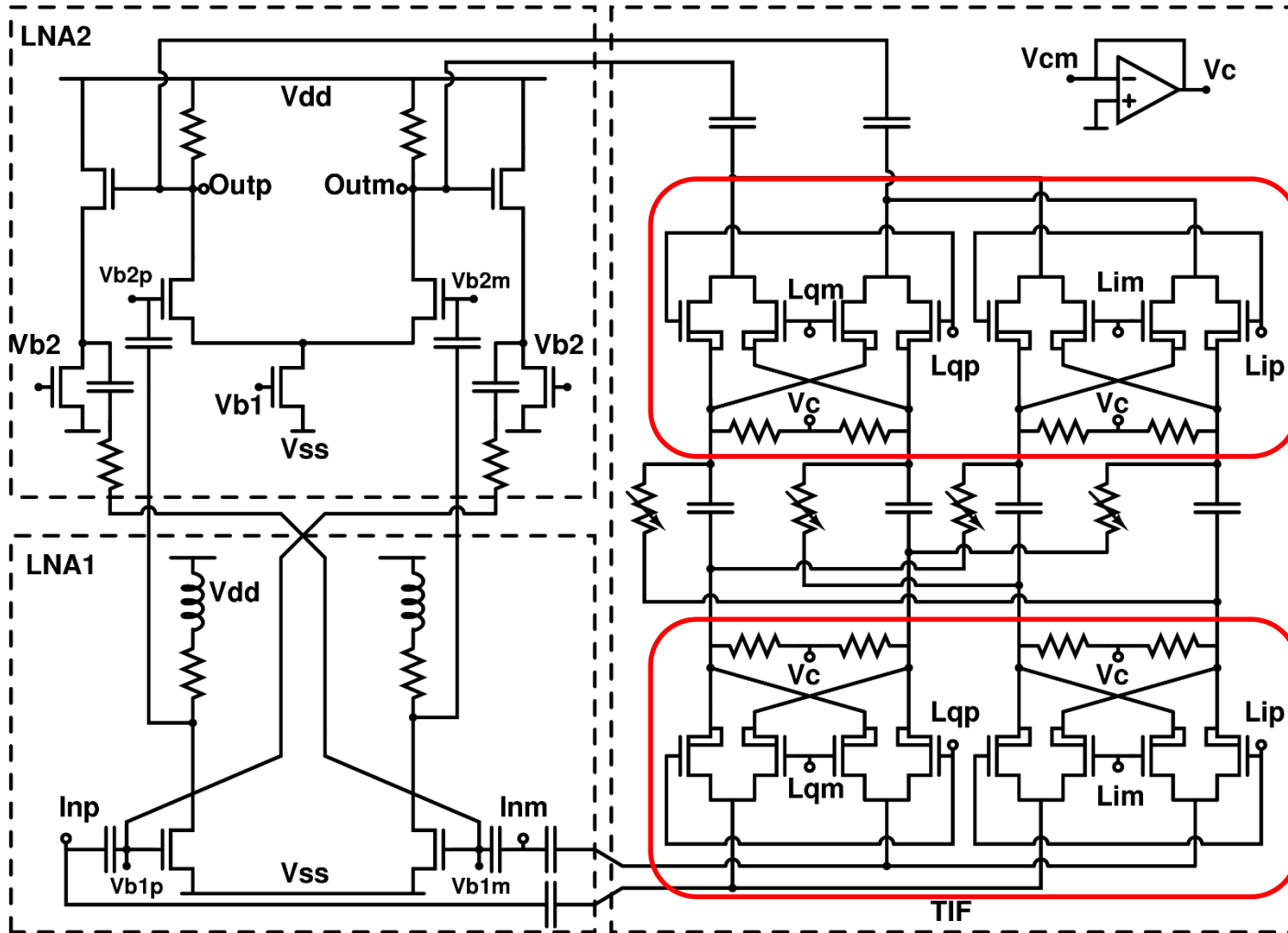

Passive Mixer, Case 3

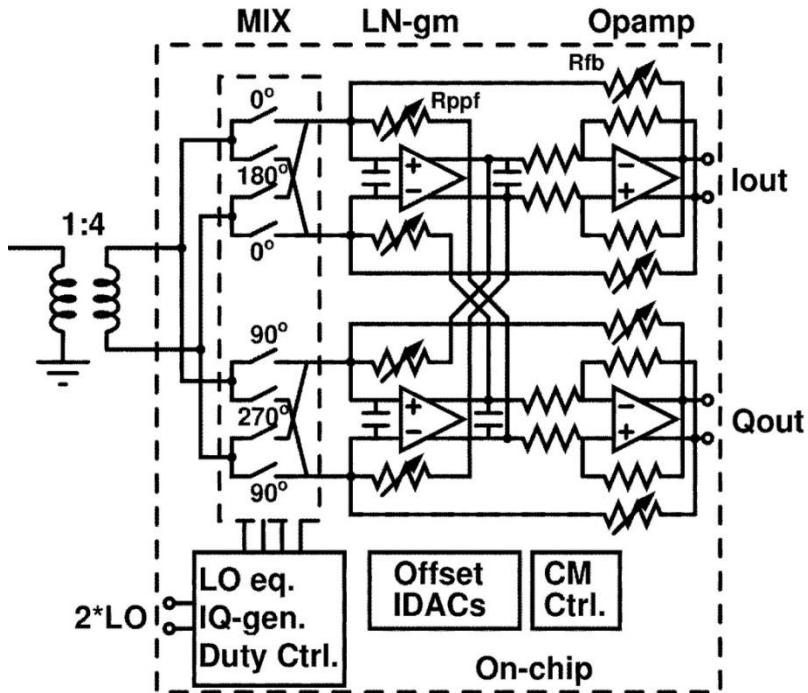

Measured results

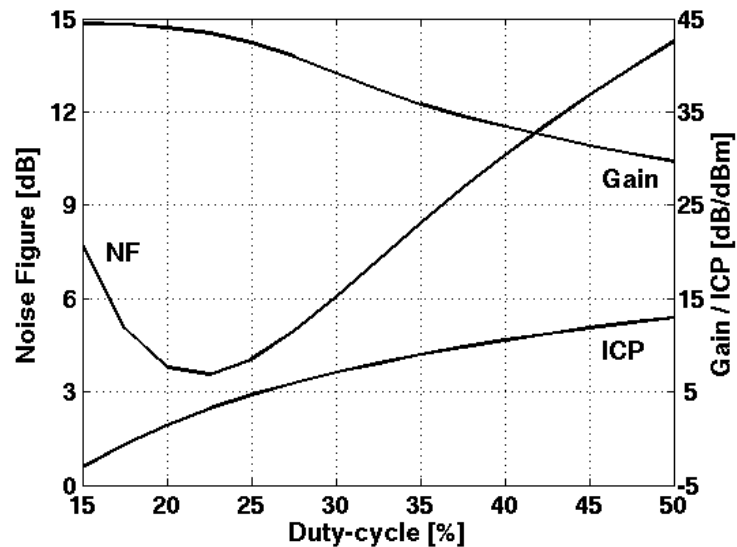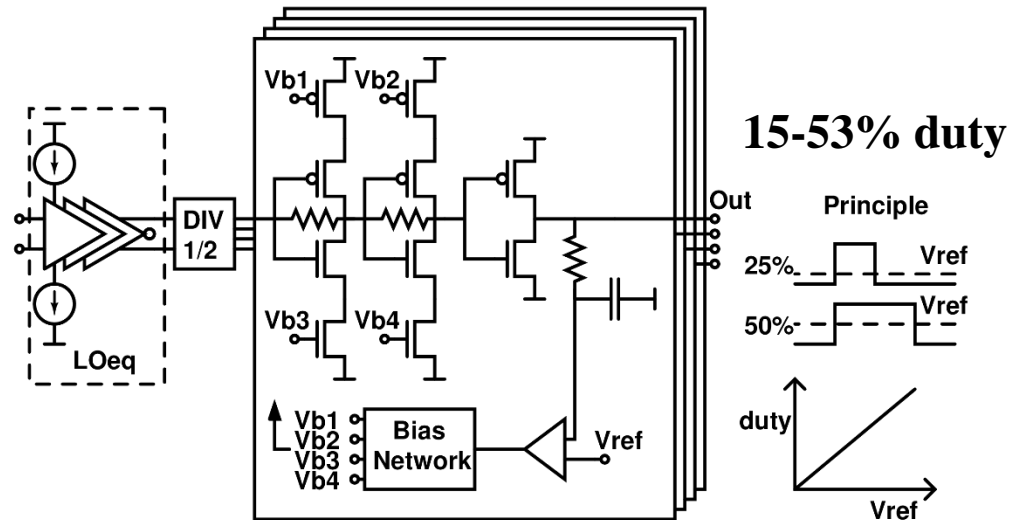

Self-Learning Assignment 4

Objective is to familiarize yourself with passive mixers.

Read three journal papers and write a reference essay.

You can find the assignment from

MyCourses / Assignments - SLA / Self-learning assignment 4

Return your answer as a pdf-file to Return Box in the same page

Next Meeting Tuesday 9.5.

Synthesizers

Topics will be

- concepts related to LO / CLK generation
- Synthesis methods
- Oscillators
- Frequency dividers
- IQ generation